



- [1] Draw the normalized resonance curves for the current in a series resonance circuit having a quality factor $Q_s = 20$ in the narrow band near resonance (for $\delta = +1\%$, $+2\%$,, $+5\%$). Plot the phase angle of the current in the same band and show the effect of increasing Q_s .
- [2] In a series resonance circuit $L = 65 \text{ mH}$, $C = 1.56 \text{ nF}$ and $R = 5.1 \Omega$, calculate the resonance frequency, the quality factor of the circuit, the bandwidth and the impedance of the circuit at frequencies 1% and 10% above resonance.
- [3] For the circuit shown in Fig. 1, calculate the frequency at which series resonance occurs (the input impedance is real). At what value of the conductance G will it be impossible to obtain resonance?
- [4] A generator is connected to a series oscillating circuit has a frequency of 250 KHz. The oscillating circuit has a constant $L = 600 \mu\text{H}$, $R = 30 \Omega$ and a variable capacitor C . For which value of the capacitor C will the circuit be at resonance? and for which value of frequency will the current flowing through the circuit decrease to one fourth of its value at resonance.
- [5] The cutoff frequencies of a series resonance circuit are 5600 and 6000 Hz :
- Calculate the B.W. of the circuit and Q_s .
 - If the resistance of the circuit is 2Ω , calculate X_L , X_C , L and C at resonance.
- [6] A series resonance circuit has a resonance frequency of 10 KHz. The resistance of the circuit is 5Ω and X_C at resonance is 200Ω , find :
- The Bandwidth and the cutoff frequencies.
 - Q_s of the circuit.
 - The voltage across the coil and the capacitor at resonance and at a frequency 10% below resonance if the input voltage is $30 \angle 0^\circ$.
 - The power dissipated in the circuit at resonance and at a frequency 4% above resonance.
- [7] Design a series resonance circuit with an input voltage $5 \angle 0^\circ \text{ V}$ to have the following specifications :
- A peak current of 500 mA.
 - A Bandwidth of 120 Hz.
 - A resonance frequency of 8400 Hz.

Handwritten notes on the right side of the page:

- 15x
- X_C X_L
- (w) قوس
- 11

Calculate the circuit elements and the cutoff frequencies .

18] A series resonance circuit of L, C and R is required to be at resonance at a frequency of 1 MHz . Its Bandwidth is 5 KHz and its input impedance at resonance is 50Ω . Calculate L, C and R .

19] Make the necessary derivations to sketch the magnitude of the current I shown in Fig.2 in amperes against frequency in Hertz showing its value at the resonance frequency F_s and the cutoff frequencies F_1 and F_2 , hence , prove that : $F_s = \sqrt{F_1 F_2}$.

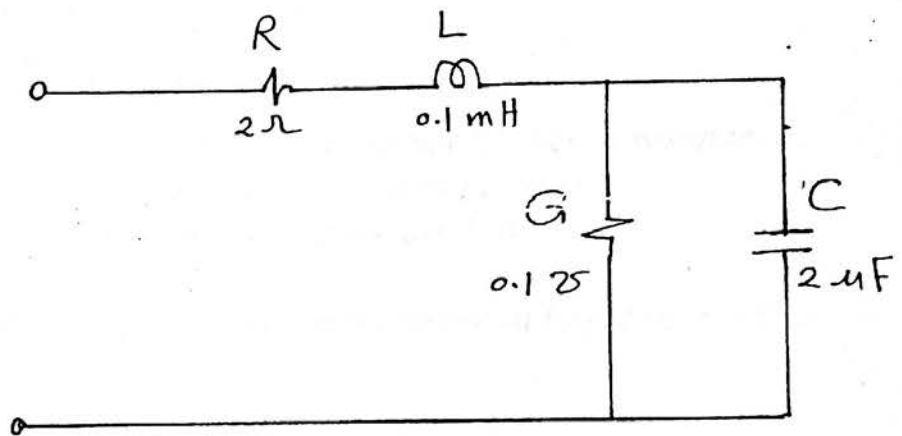


Fig.1

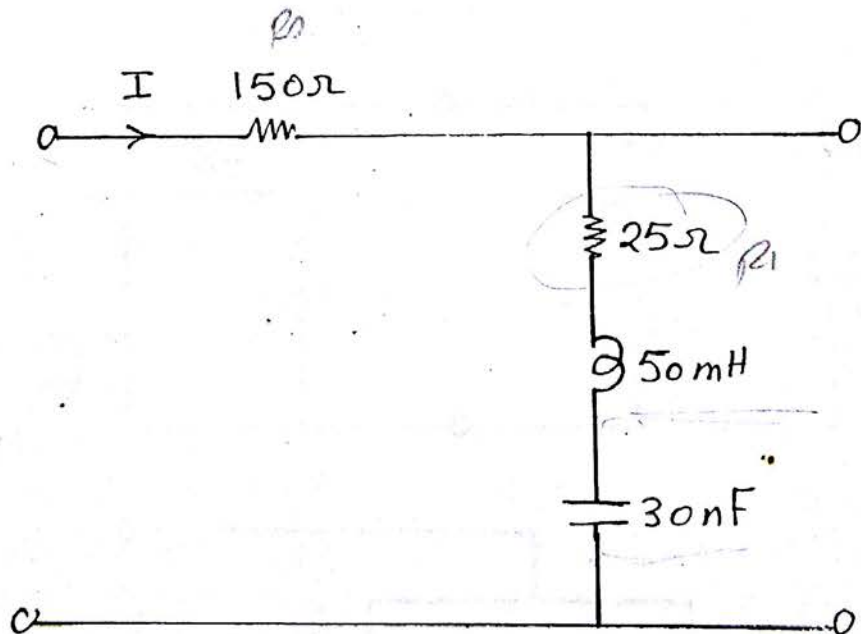


Fig.2

Sheet 2

* Series Resonance *

II


$$\delta = 0.01 \rightarrow 0.05 \leq 0.05$$

$$\therefore R = 2\delta$$

$Q = 20 \rightarrow$ high quality


$\therefore \omega_s$ at the middle of cut off frequencies

$$\left| \frac{I}{I_s} \right| = \frac{1}{\sqrt{1 + 4Q^2\delta^2}}$$

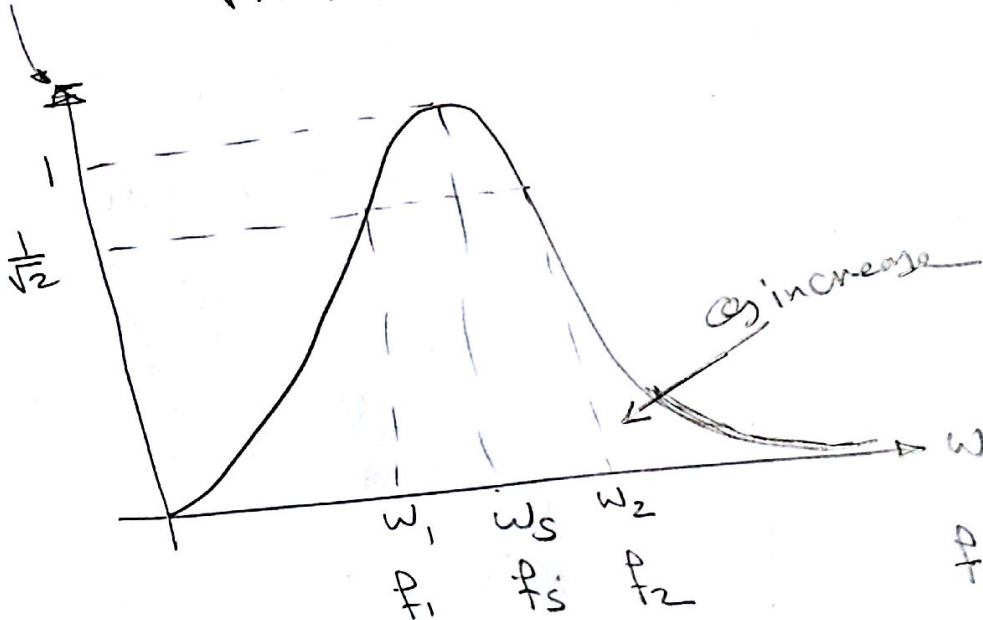

when Q increases, $\left| \frac{I}{I_s} \right| \uparrow$ (decreases)

So the curve compresses.

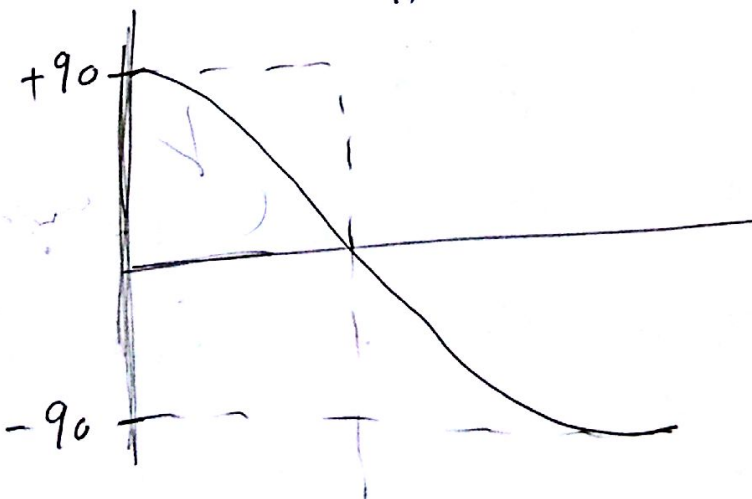

$$\phi = -\tan^{-1} \frac{2Q\delta}{1}$$

$$f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{65 \times 10^{-3} \times 1.56 \times 10^{-9}}} = 15.8 \times 10^3 \text{ Hz} \approx 15.8 \text{ kHz}$$

$$Q_s = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{5.1} \times \sqrt{\frac{65 \times 10^{-3}}{1.56 \times 10^{-9}}} = 1265.68 > 10$$

$$BW = \frac{f_s}{Q_s} \approx 12.4834 \text{ Hz}$$

1% above resonance

$$\delta = 0.01 < 0.05$$

∴ we are near resonance

$$Z_T = R(1 + j2\delta Q_s)$$

$$Z_T = 5.1(1 + j25.3136) = 5.1 + j129.039 \Omega$$

10% above resonance


$$\delta = 0.1$$

$$\alpha = \frac{\delta(\delta+2)}{\delta+1} = 0.1909$$

$$Z_T = R(1 + j\alpha Q_s)$$

$$Z_T = 5.1 + j1232.25 \Omega$$

3

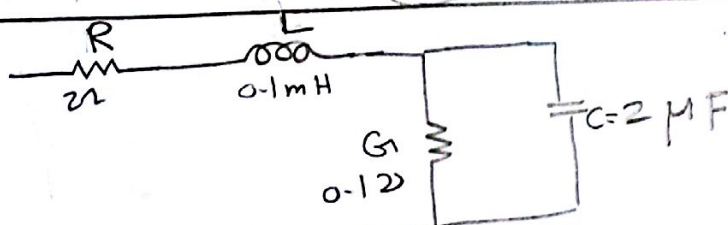

$$Z_{in} = R + j\omega L + \frac{\frac{1}{G} \times \frac{1}{j\omega C}}{\frac{1}{G} + \frac{1}{j\omega C}}$$

$$Z_{in} = R + j\omega L + \frac{1}{j\omega C + G}$$

$$Z_{in} = R + j\omega L + \frac{G - j\omega C}{G^2 + \omega^2 C^2}$$

$$Z_{in} = R + \frac{G}{G^2 + \omega^2 C^2} + j\left(\omega L - \frac{\omega C}{G^2 + \omega^2 C^2}\right)$$

At Resonance, Z_{in} is a real

$$\therefore \text{Im}(Z) = 0 \Rightarrow \therefore L = \frac{C}{\omega_s^2 C^2 + G^2}$$

$$\therefore G^2 + \omega_s^2 C^2 = \frac{C}{L}$$

$$\omega_s^2 C^2 = \frac{C}{L} - G^2$$

$$\omega_s^2 = \frac{1}{CL} - \frac{G^2}{C^2}$$

$$\omega_s = \sqrt{\frac{1}{LC} - \frac{G^2}{C^2}}$$

$$\therefore \omega_s = \sqrt{\frac{1}{0.1 \times 10^{-3} \times 2 \times 10^{-6}} - \frac{(0.1)^2}{(2 \times 10^{-6})^2}}$$

$$\therefore \omega_s = 5 \times 10^4 \text{ rad/s}$$

$$f_s = \frac{\omega_s}{2\pi} = \underline{7957.747 \text{ Hz}}$$

It's possible to obtain Resonance if ω_s exists.

So

$$\frac{G^2}{C^2} < \frac{1}{LC}$$

$$\frac{G^2}{C} < \frac{1}{L} \Rightarrow G^2 < \frac{C}{L} \Rightarrow G < \sqrt{\frac{C}{L}}$$

So if $G \geq \sqrt{\frac{C}{L}}$ it's impossible to obtain Resonance

$$G \geq \frac{\sqrt{2}}{10} \quad , \quad \boxed{G \geq 0.14142} \Rightarrow$$

4

$$f_s = 250 \text{ kHz} = \frac{1}{2\pi\sqrt{LC}}$$

$$\therefore \sqrt{LC} = 6.36619 \times 10^{-7}$$

$$LC = 4.052847 \times 10^{-13}$$

$$C = \frac{4.052847 \times 10^{-13}}{600 \times 10^{-6}} = 6.754 \times 10^{-10} \text{ F} = 0.6754 \text{ nF}$$

$$\omega_0 = \frac{1}{R} \sqrt{\frac{L}{C}} = 31.4159 > 10$$

$$\left| \frac{I}{I_s} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2}}$$

$$\frac{\frac{1}{4} I_s}{I_s} = \frac{1}{\sqrt{1 + \omega^2 R^2}} \Rightarrow \frac{1}{16} = \frac{1}{1 + \omega^2 R^2}$$

$$\therefore \frac{1}{16} = \frac{1}{1 + \omega^2 R^2}$$

$$\therefore \omega^2 R^2 = 15$$

$$R^2 = \pm \frac{\sqrt{15}}{\omega}$$

$$f/f_s = \frac{f_s}{f} = \pm \frac{\sqrt{15}}{10\pi}$$

$$f^2 - f_s^2 = \pm \frac{\sqrt{15}}{10\pi} f f_s$$

$$f^2 \mp \frac{\sqrt{15}}{10\pi} f f_s - f_s^2 = 0$$

$$f^2 \pm 30820.2222 f - 6.25 \times 10^6 = 0$$

$f_1 = 265.884 \text{ kHz}$	$f = -235.064 \text{ kHz}$	$f_2 = 235.064 \text{ kHz}$	$f = -265.84$
	موجب		موجب

5

$$f_1 = 5600 \text{ Hz}$$

$$f_2 = 6000 \text{ Hz}$$

$$BW = f_2 - f_1 = 400 \text{ Hz}$$

$$= \frac{P}{S} \rightarrow \sqrt{f_1 f_2} = 5795.5 \text{ Hz}$$

$$\therefore W_s = \frac{36420.8}{\dots}$$

$$Q_s = \frac{5795.5}{400} = 14.49 = \frac{X_L}{R}$$

$$14.49 = \frac{W_s L}{R}$$

$$28.96 = 36420.8 L$$

$$L = 7.9569 \times 10^{-4} = 795.699 \mu\text{H}$$

$$X_L = W_s L = 28.96 = X_C$$

$$Q_s = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$(28.96)^2 = \frac{7.9569 \times 10^{-4}}{C}$$

$$C = 9.48739 \times 10^{-7} \text{ F}$$

$$\approx \boxed{948.739} \text{ nF}$$

$$\textcircled{\text{or}} \quad X_C = \frac{1}{W_s C}$$

$$C = \frac{1}{X_C W_s}$$

$$C = \frac{1}{28.96 \times 36420.8}$$

$$\approx \boxed{948.095} \text{ nF}$$

5 $f_s = 10 \text{ kHz} = 10^4 \text{ Hz}$

$R = 5 \Omega$

$X_C = X_L = 200 \Omega$

$L = 3.183 \text{ mH}$

$C = 79.57 \text{ nF}$

$$BW = \frac{P}{Q_s} = \frac{P}{\frac{X_L}{R}} = \frac{10^4}{\frac{200}{5}} = 250 \text{ Hz}$$

$Q_s = 40 > 10 \Rightarrow \text{high quality}$

$f_1 = f_s - \frac{BW}{2} = 10^4 - 125 = 9875 \text{ Hz}$

$f_2 = f_s + \frac{BW}{2} = 10^4 + 125 = 10125 \text{ Hz}$

$I_s = \frac{V}{R} = \frac{30}{5} = 6 \angle 0^\circ \text{ A}$

$V_L = I_s \times jX_L = 1200 \angle 90^\circ \text{ V}$

$V_C = 1200 \angle -90^\circ \text{ V}$

@ 10% below Res. : $s = -0.1$
 $\omega = \frac{-10}{90} \approx -0.21 = \frac{\omega}{\omega_s} - \frac{\omega_s}{\omega}$
 $\omega = 56548.66776 \text{ rad/sec}$
 $X_L = 180 \Omega$
 $Z_T = R(1 + j\omega L) = 5 - j \frac{380}{9}$
 $I = \frac{E}{Z_T} = 0.7056 \angle 83.246^\circ$
 $V_L = I \times jX_L = 127 \angle 173.246^\circ \text{ Volts}$

$P_{\text{at resonance}} = |I_s|^2 R = 36 \times 5 = 180 \text{ Watt}$

$X_C = 222.222 \Omega$
 $V_C = I \times (jX_C)$
 $V_C = 156.8 \angle -6.75^\circ \text{ Volts}$

\Rightarrow at 4% above resonance

$s = 0.04 \angle 0.05$

$\therefore R = 2s$

$Z_T = R(1 + 2j\delta\omega_s)$

$= 5(1 + 2j \times 0.04 \times 40) = 5 + j16 \Omega$

$I = \frac{V}{Z_T} = \frac{30}{5 + j16} = 1.789649959 \angle -72.64597^\circ \text{ A}$

$P_{\text{at resonance}}^{4\% \text{ above}} = |I|^2 R = 16.014 \text{ watt}$

$\frac{10}{200} \frac{9}{180}$
 $\frac{10}{200} \frac{1}{200}$