



[1] A parallel resonance circuit consists of 1 mH inductance having  $Q = 30$  (at resonance) in parallel with a condenser of 1000 pF. Calculate the resonance frequency and plot the magnitude and phase of the normalized impedance of the circuit near resonance ( $\delta = \pm 1\%, \pm 2\%, \dots, \pm 5\%$ ).

For the resonance circuit shown in Fig. 1, find:

- The value of  $X_C$  at resonance.
- The total impedance at resonance.
- The currents  $I_L$  and  $I_C$  at resonance and at a frequency 8% below resonance.
- If the resonance frequency is 20 KHz, find the value of  $L$  and  $C$ .
- The quality factor of the circuit  $Q_P$  and the bandwidth  $B.W$ .

[3] If it is required that the impedance  $Z_T$  of the circuit shown in Fig. 2 be a resistor of 50 K $\Omega$  at resonance:

- Find the value of  $X_L$  and  $X_C$ .
- Calculate the resonance frequency if  $L = 16$  mH.
- Find the value of  $C$  in  $\mu F$ .

Fig.1


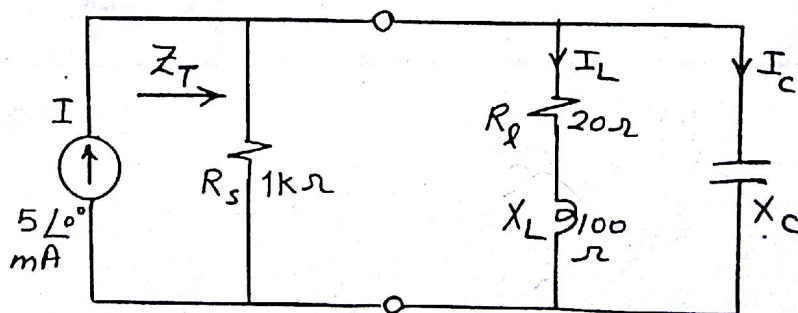


Fig.2

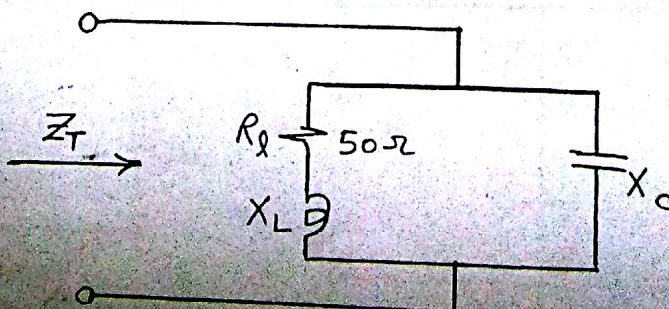


4] For the circuit shown in Fig. 3, find  $f_p$  and the voltage  $V_C$  at resonance and calculate the power absorbed from the source at resonance and the Bandwidth.

5] For the circuit shown in Fig. 4, the following specifications are given :  
 $f_p = 100 \text{ KHz}$ ,  $B.W. = 2500 \text{ Hz}$ ,  $L = 2 \text{ mH}$ ,  $Q = 80$ . Find  $R_L$ ,  $R_S$  and  $C$ .

6] For the circuit shown in Fig. 5, find :

- The value of  $X_L$  at resonance.
- $Q$  of the coil at resonance.
- The resonance frequency if the B.W. is  $1000 \text{ Hz}$ .
- The maximum value of the voltage  $V_C$ .
- Sketch the curve of  $V_C$  versus frequency indicating the amplitudes at resonance and the cutoff frequencies.

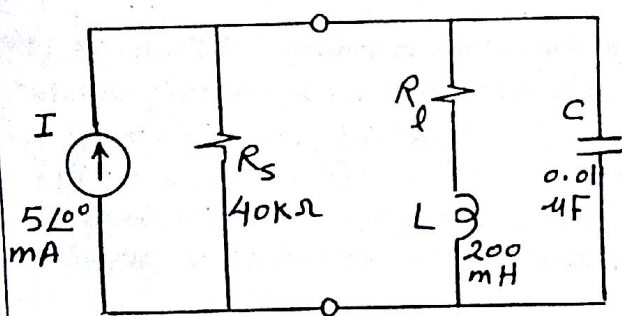7] For the circuit shown in Fig. 6, find the resonance frequency (for which  $Z_{in}$  is real).  
 What are the conditions on  $r_1$  and  $r_2$  to produce resonance?



$Q = 20$

Fig.3

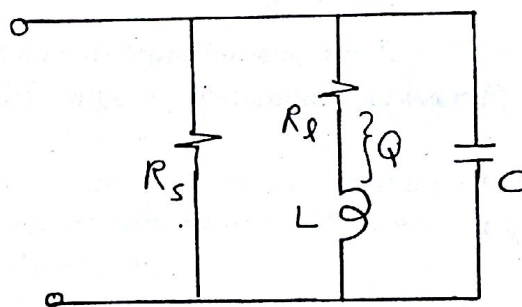


Fig.4

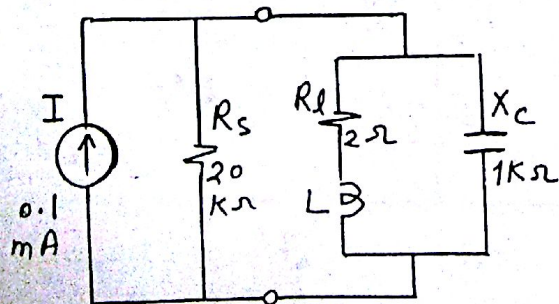


Fig.5

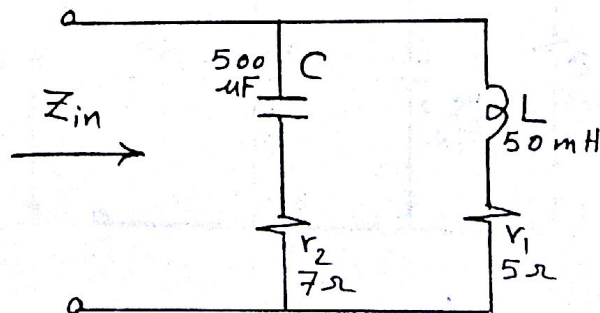


Fig.6

8] A parallel resonance circuit has  $L = 159 \mu\text{H}$  and  $Q = 50$  at resonance, and  $C = 636 \text{ pF}$ . Draw its all parallel circuit. If the circuit is operated from a current source having a resistance of  $10 \text{ K}\Omega$ , calculate the quality factor of the circuit  $Q_p$ .

9] a) Design the circuit elements of a parallel resonance circuit such that the input impedance to the circuit has a maximum value of  $20 \text{ K}\Omega$ , its resonance frequency is  $100 \text{ K rad./sec.}$  and the quality factor of the coil at resonance is  $20$ .

b) If a current source of  $10 \text{ mA}$  and internal resistance  $20 \text{ K}\Omega$  is applied to the parallel resonance circuit designed in a), make the necessary derivations to sketch the magnitude of the voltage across the circuit in volts against frequency in  $\text{Hz}$  indicating the amplitudes at resonance and the cutoff frequencies.

c) Calculate the average power delivered to the circuit at a frequency  $10\%$  below resonance.

10] For the parallel resonance circuit shown in Fig. 7, calculate:

a) The current in the capacitor  $C$  at a frequency  $20 \text{ KHz}$ .


b) The range of frequencies for which  $|V_p| \leq 0.75 V_{p \text{ maximum}}$ .

c) The additional parallel resistance required to change the Bandwidth of the output voltage signal to  $6 \text{ KHz}$ .

11] The parallel resonance circuit shown in Fig. 8 has an input impedance  $Z_{in}$ :

a) Make the necessary derivations to calculate the range of frequencies between  $F_a$  and  $F_b$  for which  $|Z_{in}| \geq 1.5 \text{ K}\Omega$ .

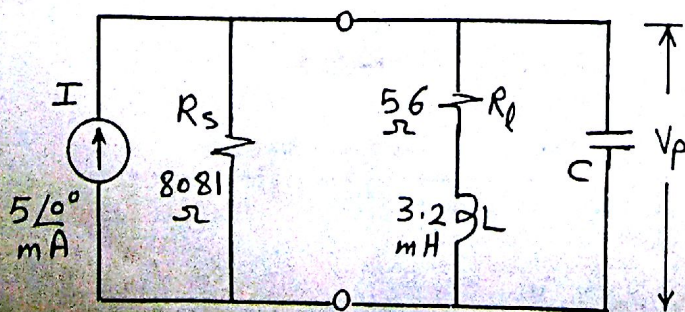b) If the circuit is fed from a current source of  $10 \text{ mA}$  and an internal resistance  $10 \text{ K}\Omega$ , calculate the circulating currents in the coil and the condenser at the upper cutoff frequency of the output voltage signal across the circuit.



$$F_p = 2.2 \text{ KHz}$$

Fig. 7


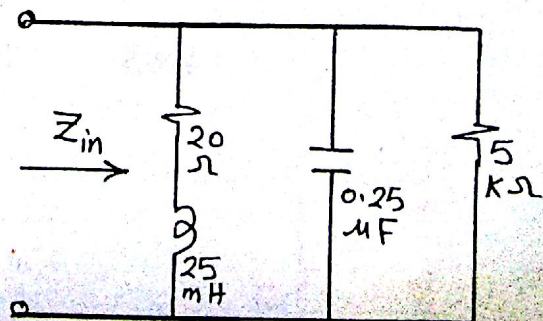


Fig. 8

3

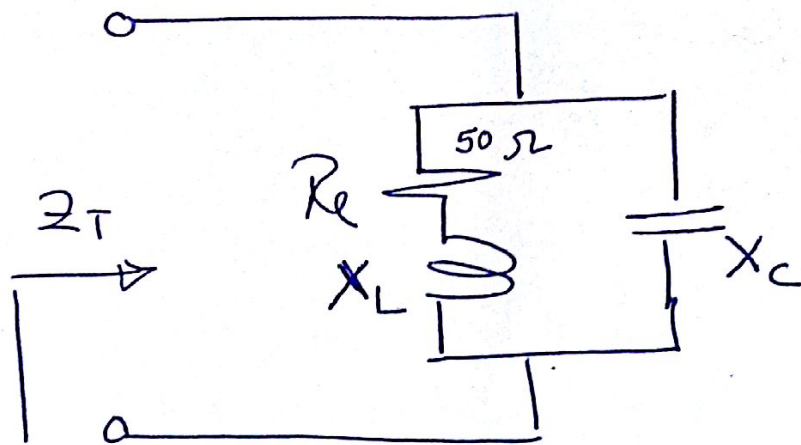

Required  $Z_T$  to be resistor  $\rightarrow \infty$  At Resonance

a)  $\therefore Z_T = R_{tot} = R_p = \frac{R_e^2 + X_L^2}{R_e} \rightarrow \boxed{X_L = 1580.348 \Omega}$

$\downarrow$   $50 \text{ k}\Omega$        $50 \Omega$   $\leftarrow R_e$


$\phi \quad X_C = X_{Lp} = \frac{R_e^2 + X_L^2}{X_L} = 1581.93 \Omega$

or  $Q_{coil} = X_L / R_e = 31.6710 \rightarrow X_C = X_{Lp} \approx X_L = 1580.348 \Omega$

b)  $X_L = \omega_p L \Rightarrow \omega_p = \frac{X_L}{L} = \frac{1580.348}{16 \times 10^{-3}} \approx 98771.75 \text{ r/s}$

c)  $\omega_p = \frac{1}{\sqrt{LC}} \rightarrow C = 6.4 \text{ nF}$

Due to high quality coil

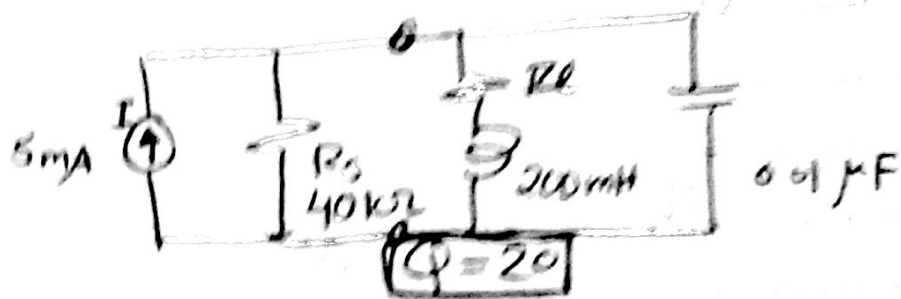

Required:  $f_p$ ,  $V_c / |Q_{res.}|$ ,  $P_{source @ res.}$ ,  $BW$

Soln.

Remember, if  $Q$  is given without any subscript, it is  $Q_{coil}$  @ Resonance.

$$Q = 20 > 10$$

$$f_p = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{200 \times 10^{-3} \times 0.01 \times 10^{-6}}} \approx 3.558 \text{ kHz}$$

$$\begin{aligned} V_c = V_{pres.} &= I Z_{Tp} \\ &= I (R_s // R_p) \\ &= I \left( R_s // \frac{R_e^2 + X_L^2}{R_e} \right) \end{aligned}$$

$$Q = \frac{X_L}{R_e}$$

$$R_e = \frac{X_L}{Q}$$

$$= \frac{2\pi f_p L}{Q}$$

$$\approx 223.6 \Omega$$

$$= (5 \text{ mA})(40 \text{ k}\Omega // 89.6691 \Omega)$$

$$\approx \underline{\underline{138.3 \text{ V}}}$$

$$P_{source} = P_{dir} = \frac{V_{pres.}^2}{R_{tot}} = \frac{(138.3)^2}{27660.9 \Omega} \approx 0.691 \text{ Watts}$$

$$\approx P_{source} = |I| |V_p| \cos \theta = 5 \text{ mA} \times 138.3 \text{ V} \times (\cos 0) = 0.691 \text{ Watts}$$


$$B_w = \frac{W_p}{q_p} \approx \frac{1}{cR}$$

$$= \frac{1}{0.01 \times 10^{-6} \times 27.66 \times 10^3}$$

$$\approx 3615.32 \text{ r/s}$$

$$\approx 575.39 \text{ Hz}$$

5)

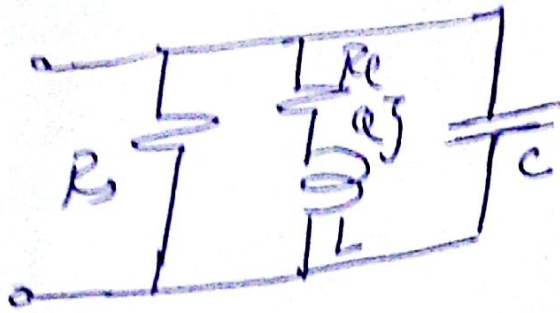

$f_p = 100 \text{ kHz}$   
 $B_w = 2500 \text{ Hz}$

$L = 2 \text{ mH}$

$Q = 80$

Required  $R_e, R_o$  and  $C$

$\rightarrow Q = 80 > 10 \rightarrow Q_p \approx Q$

$Q_p = f_p / B_w = 10^5 / 2500 = 40 > 10$

$= R / X_L = \frac{R}{\omega_p L}$

$\therefore R = \omega_p L Q_p = 2\pi \times 10^5 \times 2 \times 10^{-3} \times 40 \approx 50.265 \text{ k}\Omega$

also,  $Q = \frac{\omega_p L}{R_e} = 80$

$R_e = \frac{\omega_p L}{Q} = \frac{2\pi \times 10^5 \times 2 \times 10^{-3}}{80} \approx 15.7 \Omega$

$R = R_p \parallel R_o$

$50.265 \text{ k}\Omega$

$100.48 \text{ k}\Omega$

Get  $R_o = 100.58 \text{ k}\Omega$

$R_p = \frac{X_L^2 + R_e^2}{R_e}$   
 $\approx Q^2 R_e$   
 $\approx 100.48 \text{ k}\Omega$


Also,  $Q_p = R / X_c = \omega_p C R = 40$

$\rightarrow$  Get  $C = 1.2665 \text{ nF}$

$\uparrow 2\pi \times 10^5$   
 $\downarrow 50.265 \text{ k}\Omega$

$\odot f_p = \frac{1}{2\pi \sqrt{LC}}$

7

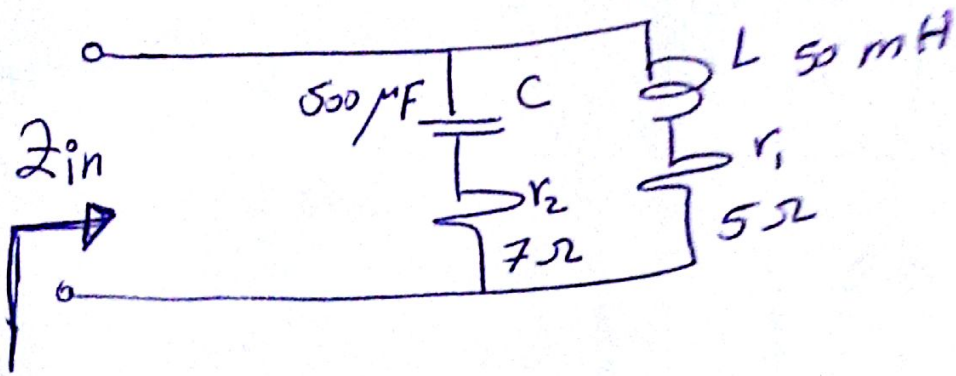

$$\begin{aligned}
 Y_{in} &= \frac{1}{j\omega L + r_1} + \frac{1}{\frac{1}{j\omega C} + r_2} \\
 &= \frac{1}{r_1 + j\omega L} + \frac{j\omega C}{1 + j\omega C r_2} \\
 &= \frac{r_1 - j\omega L}{r_1^2 + \omega^2 L^2} + \frac{j\omega C (1 - j r_2 \omega C)}{1 + \omega^2 C^2 r_2^2}
 \end{aligned}$$

@ Resonance  $\text{Im}(Y_{in}) = 0$

$$\therefore \frac{-\omega_p L}{r_1^2 + \omega_p^2 L^2} + \frac{\omega_p C}{1 + \omega_p^2 C^2 r_2^2} = 0$$

$$r_1^2 C + \omega_p^2 L^2 C = L + \omega_p^2 C^2 r_2^2 L$$

$$\omega_p^2 (L C (L - r_2^2 C)) = L - r_1^2 C$$

$$\omega_p = \sqrt{\frac{L - r_1^2 C}{L C (L - r_2^2 C)}}$$

for  $\omega_p$  to be  $> 0$

Denominator & Numerator must be +ve together  
or -ve together.

the

$$L - r_1^2 C > 0$$

$$\frac{L}{C} > r_1^2$$

$$r_1 < \sqrt{\frac{L}{C}}$$

and

$$L - r_2^2 C > 0$$

$$r_2 < \sqrt{\frac{L}{C}}$$

$$r_1 \& r_2 < \sqrt{\frac{L}{C}}$$

$$r_1 \& r_2 < 10 \Omega$$

the

$$L - r_1^2 C < 0$$

$$r_1 > \sqrt{\frac{L}{C}}$$

$$L - r_2^2 C < 0$$

$$r_2 > \sqrt{\frac{L}{C}}$$

$$r_1 \& r_2 > \sqrt{\frac{L}{C}}$$

$$r_1 \& r_2 > 10 \Omega$$


For the given values,

$$\omega_p = \sqrt{\frac{50 \times 10^{-3} - (25)(500 \times 10^{-6})}{50 \times 10^{-3} \times 500 \times 10^{-6} (50 \times 10^{-3} - (49)(500 \times 10^{-6}) )}}$$

$$= 242.535 \text{ rad/sec}$$

Good Luck

10

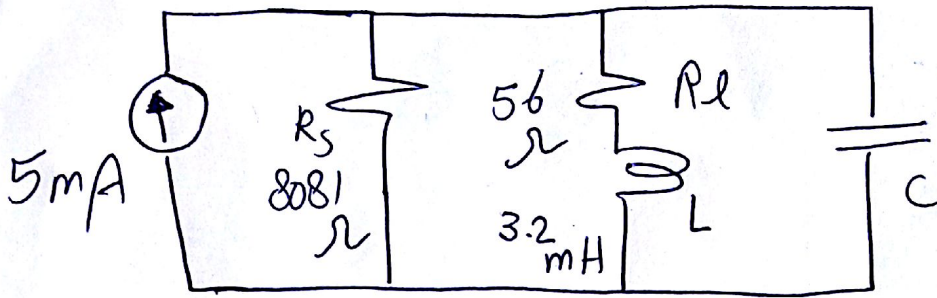

$$F_p = 22 \text{ kHz}$$

a) to get  $I_c \rightarrow I_c = \frac{V_p}{-jX_c} \rightarrow$  We need to get  $V_p$  &  $X_c$   
 @  $f = 20 \text{ kHz}$

$V_p = \frac{V_{pres}}{1 + j\omega R_p}$   $\rightarrow$  we need to get  $V_{pres}$ ,  $\phi_p$  &  $R$

$$\omega = \frac{f}{f_p} - \frac{f_p}{f} = \frac{20}{22} - \frac{22}{20} = \frac{-21}{110}$$

$$R_p = \frac{X_L^2 + R_e^2}{X_L} = 3549.94 \Omega$$

$$\omega_p = \frac{R_{tot}}{X_{LP}} = \frac{(8081 // 3549.94)}{449.426} \approx 5.487$$

$$X_L = \omega p L = 2\pi \times 22000 \times 3.2 \times 10^{-3}$$

$$\approx 442.336 \Omega$$

$$\phi = \frac{\omega p L}{R_e} = 7.89 < 10$$

$$X_{LP} = X_c \Big|_{res} = \frac{R_e^2 + X_L^2}{X_L} = 449.426 \Omega$$

Then,  $V_{pres} = I Z_{T_p} = I R_{tot} = 5 \times 10^{-3} \times 2466.4 \approx 12.332 \text{ volts}$

Then,  $V_p = \frac{V_{pres}}{1 + j\omega R_p} = \frac{12.332}{1 - j \frac{21}{110} (5.487)} \approx 8.5153 / 46.329^\circ \text{ volts}$

-1-

$$\begin{aligned} \phi I_c &= \frac{V_p}{-jX_c} \\ & \quad \omega = 20 \text{ kHz} \\ &= \frac{8.5153 \angle 46.329^\circ}{-j * 494.36} \\ &\approx 17.22 \angle 136.3^\circ \text{ mA} \end{aligned}$$

$$\begin{aligned} \text{let } X_c|_{\omega=20 \text{ kHz}} &= X_c' \\ X_c' &= \frac{1}{\omega' C} \\ &= \frac{V_p}{\omega' (V_p C)} X_c|_{\omega=20} \\ &= \frac{2\pi * 22 * 494.4}{2\pi * 20} \\ &= 494.36 \Omega \end{aligned}$$

② You can get C  
 $X_c|_{\text{res}} = \frac{1}{\omega_p C}$

$$\begin{aligned} C &= 16.09 \text{ nF} \\ \phi X_c' &= \frac{1}{\omega' C} \\ & \quad \omega = 20000 \\ &= 494.36 \Omega \end{aligned}$$

b)  $|V_p| \leq 0.75 V_{P_{\text{maximum}}}$ . Required range of frequencies?!

$$\Rightarrow V_{P_{\text{maximum}}} = V_{P_{\text{resonance}}}$$

$$\Rightarrow \frac{|V_p|}{V_{P_{\text{res}}}} \leq 0.75$$

$$\frac{1}{\sqrt{1 + Q_p^2 \Omega^2}} \leq 0.75$$

$$1 + \omega_p^2 \Omega^2 \geq \frac{16}{9}$$

$$\Omega^2 \geq \frac{\frac{16}{9} - 1}{\omega_p^2} = \frac{7/9}{\omega_p^2}$$

$$\Omega^2 \geq 0.025833$$

$$\Omega \geq \pm 0.1606991807$$


$$f/f_p - f_p/f \geq \pm 0.1606$$

$$f^2 \mp f(3535.38) - 484 \times 10^6 \geq 0$$

$$\hookrightarrow f^2 \mp f(3535.38) - 484 \times 10^6 = 0$$

$$\hookrightarrow \text{solve } f_1 = 20.3 \text{ kHz}$$

$$f_2 = 23.83 \text{ kHz}$$

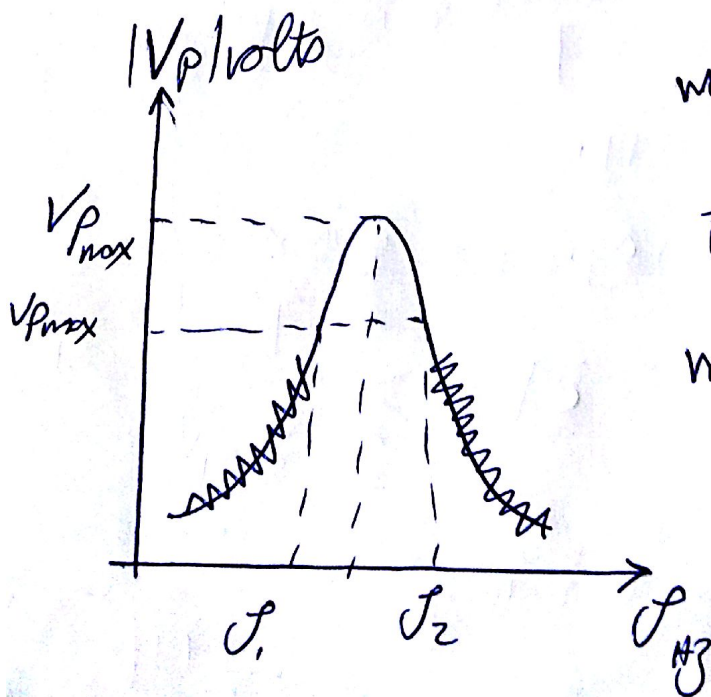

we need the range at which

$$\frac{V_p}{V_{p_{max}}} \leq (3/4)$$

which is the range below  $f_1$

and above  $f_2$

$$\text{Range: } f < 20.3 \text{ kHz}$$

$$\text{and } f > 23.83 \text{ kHz}$$


© Required BW = 6 KHz = 6000 Hz

$$BW = \frac{f_p}{Q_p}$$

$$6000 = \frac{22000}{Q_p}$$

$$Q_p = \frac{22}{6}$$

$$Q_p = \frac{R_{tot}}{X_L}$$

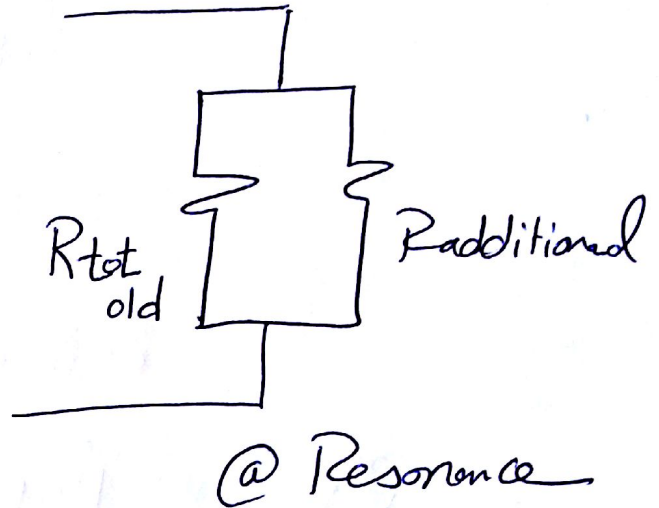

$$\frac{22}{6} = \frac{R_{tot} \parallel R_{add.}}{X_L}$$

$$X_L \rightarrow 449.426 \Omega$$

$$R_{tot} \parallel R_{add.} = 1647.89 \Omega$$

$$\frac{1}{R_{tot}} + \frac{1}{R_{add.}} = \frac{1}{1647.89}$$

$$R_{tot} \rightarrow 2466.4 \Omega$$

$$R_{add.} = 41965 \text{ k}\Omega$$

① a) Design Parallel Resonance circuit such that

1]  $Z_T |_{\max} = 20 \text{ k}\Omega$

2]  $\omega_p = 100 \text{ krad/s}$

3]  $Q = 20 > 10 \rightarrow X_p \approx X_L \text{ " } L_p \approx L \text{ "}$

$\Rightarrow Z_T |_{\max} = Z_{T_p} = R_{\text{tot}} = R_p \approx Q^2 R_e$

$R_e = \frac{20000}{(20)^2} = \underline{\underline{50 \Omega}}$

$Q = \frac{X_L}{R_e} \rightarrow X_L \approx Q R_e = (50)(20) = \underline{\underline{1000 \Omega}}$   
 $= X_C$



$\omega_p L = 1000 \rightarrow L = 10 \text{ mH}$


$\frac{1}{\omega_p C} = 1000 \rightarrow C = 10 \text{ nF}$

②  $I_s = 10 \text{ mA}, R_s = 20 \text{ k}\Omega$

{ make Derivations } to get  $\left( V_p = \frac{V_{p_{\text{res}}}}{1 + jQ_p} \right)$   
 as in lecture

$V_{p_{\text{res}}} = V_{p_{\text{max}}} = I_s Z_{T_p} = 10 \text{ mA} \times (20 \text{ k}\Omega // 20 \text{ k}\Omega) = 100 \text{ V}$

$V_p |_{j=0} = I R' = I (R_s // R_e) \approx 0.5 \text{ V}$   
 $\downarrow$   
 $R_p = R_e$

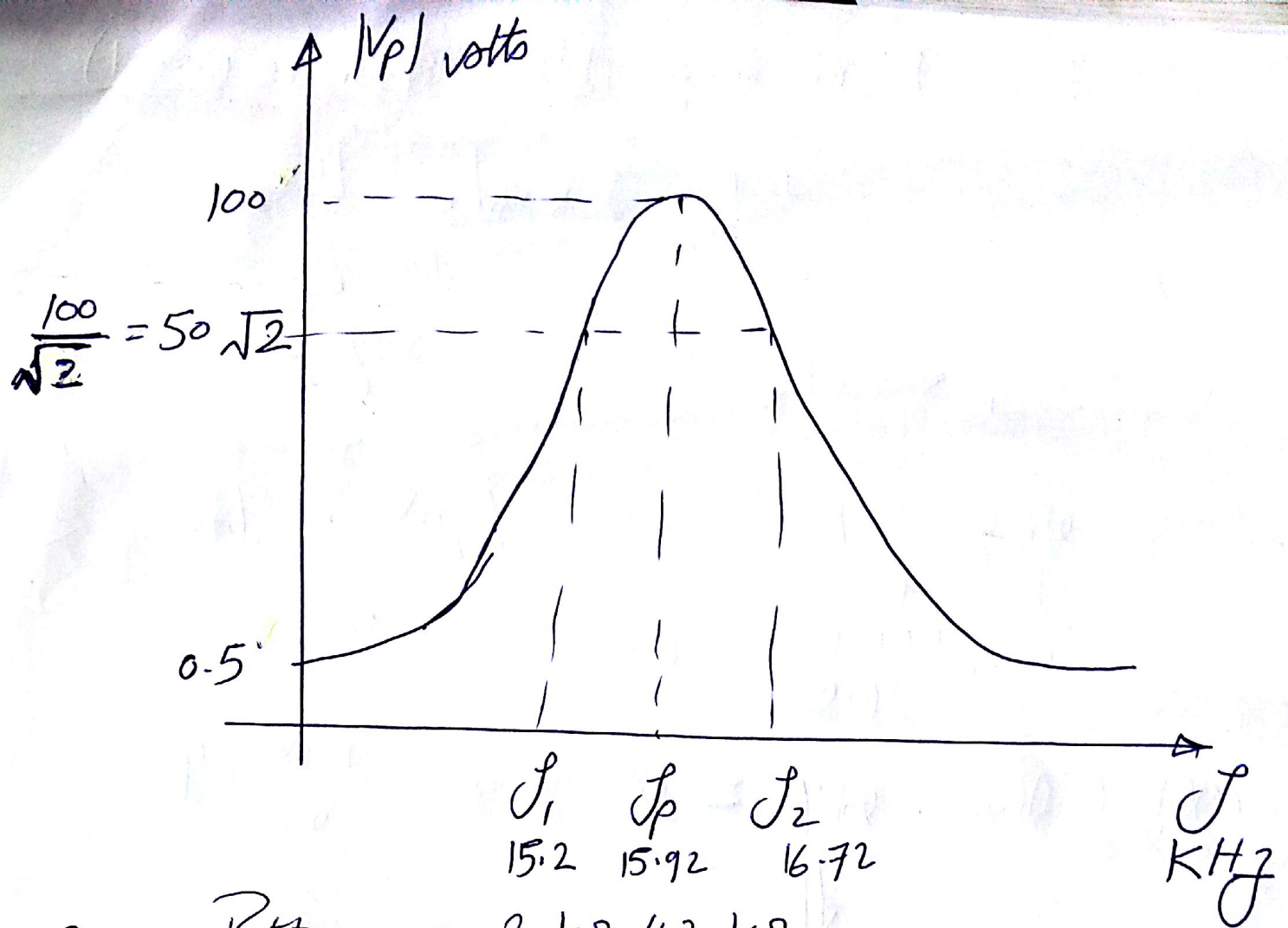

$$C_p = \frac{R_{tot}}{X_{Lp} \approx X_L} = \frac{20 \text{ k}\Omega // 20 \text{ k}\Omega}{1000} = 10$$

$$BW = \frac{f_p}{C_p} = \frac{(100 \times 10^3) / 2\pi}{10} = 1591.55 \text{ Hz}$$

$$f_{1,2} = f_p \pm \frac{BW}{2} = 15.2 \text{ KHz}, 16.72 \text{ KHz}$$

$$\Delta f_p = \frac{\omega_p}{2\pi} = 15.92 \text{ KHz}$$

©

$$P_{\text{delivered}} = \frac{|V_p|^2}{R_{\text{tot.}}}$$

$$V_p /_{10\% \text{ below } V_{\text{res.}}} = \frac{V_p /_{\text{res.}}}{1 + j\omega p \Omega}$$

$$= \frac{I R_{\text{tot.}}}{1 + j\omega p \Omega}$$

$$= 42.8 \angle 64.65^\circ \text{ V}$$

$$\Omega = 0.9 - \frac{1}{0.9} = -0.21$$

$$P_p = 10$$


$$P_{\text{tot}} = \frac{42.8^2}{(20k\Omega // 20\Omega)} = \boxed{0.18326 \text{ Watts}}$$

But,  $P_{\text{delivered to the ckt.}} = P_{R_p} = \frac{|V_p|^2}{R_p}$

$$= \frac{42.8^2}{20k\Omega} = 0.091592 \text{ W}$$

$$= \underline{\underline{91.592 \text{ mW}}}$$

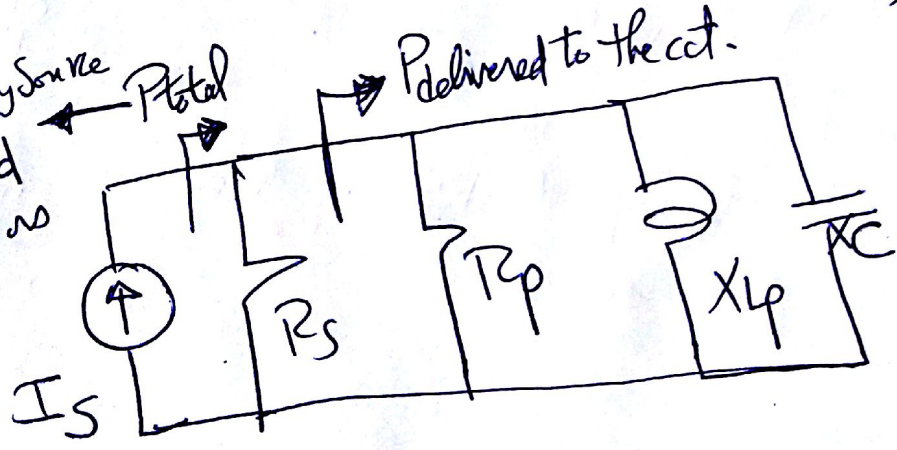$V_p \cos \theta$   
 $P_{\text{supplied by source}} = P_{\text{dissipated by resistors}}$




(11)

(a)

$$Z_{in} = \frac{Z_{TP}}{1 + j\omega R}$$

$$|Z_{in}| = \frac{|Z_{TP}|}{\sqrt{1 + \omega^2 R^2}} \rightarrow R_{tot}$$

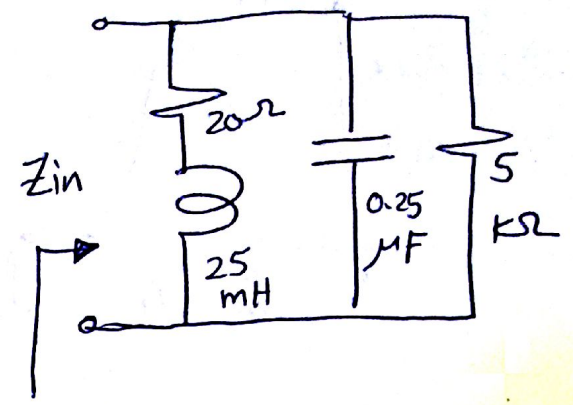

$$\omega_p = \frac{1}{\sqrt{LC}} \sqrt{1 - R_e^2 \frac{C}{L}} = 12623.787 \text{ rad/s}$$

$$Q = \frac{X_L}{R_e} = \frac{\omega_p L}{R_e} = 15.78 > 10$$

$$R_p \approx Q^2 R_e = 4980.168 \Omega$$

$$\phi R_{tot} = R_p \parallel R_L = (4980.168 \parallel 5000) \approx 2495 \Omega$$

$$\therefore \sqrt{1 + \omega_p^2 R^2} = \frac{R_{tot}}{|Z_{in}|} = \frac{2495}{1500}$$

$$\sqrt{1 + \omega_p^2 R^2} = 1.66$$

$$\omega_p^2 R^2 = 1.7556$$

$$\begin{aligned} \omega_p &= \omega_p C R \\ &= 12623.787 \times \\ &\quad 0.25 \times 10^{-6} \times \\ &\quad 2495 \\ &\approx 7.87 \end{aligned}$$

You may proceed as problem (10)

put  $\omega_p = 7.87$

$$\omega = \omega_p - \omega_p / Q$$

solve to get  $\omega_1$  &  $\omega_2$ .


$$\omega = \pm \left( 1.3249 \frac{1}{\omega_p} \pm \frac{1}{\omega_p} \right)$$

$$\therefore \omega_{1,2} = \omega_p \left( \sqrt{1 + \frac{1}{4Q^2}} \mp \frac{1}{2Q} \right)$$

2009.1 Hz

$$\frac{\omega_p}{1.3249} = 5.94$$
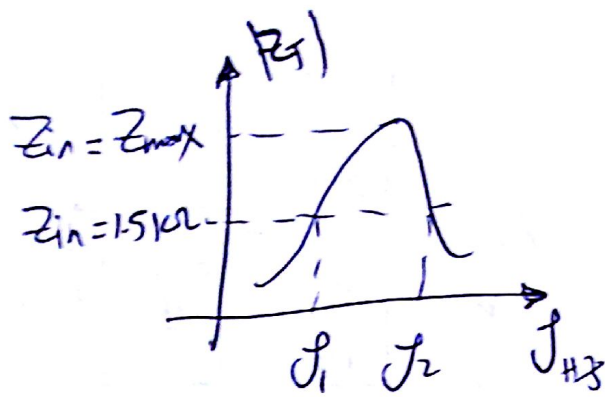
$$\text{Get } \omega_1 = 1847 \text{ Hz}, \omega_2 = 2185.3 \text{ Hz}$$



we need the range @ which  $Z_{in} > 1.5 k\Omega$ , that is the range between  $f_1$  &  $f_2$

$$|Z_{in}| > 1.5 k\Omega \text{ if } 1845 \leq f \leq 2185 \text{ Hz}$$

b)  $I_S = 10 \text{ mA}$ ,  $R_S = 10 k\Omega$

$$R_{tot} = R_S \parallel R_p \parallel R_L = 2495 \parallel 10000 \approx 1996.8 \Omega$$

$$f_{z \text{ upper cut } \omega} = \omega \left( \sqrt{1 + \frac{1}{4Q^2}} + \frac{1}{2Q} \right) = 2140.77 \text{ Hz}$$

$$\Omega = \omega / \omega_0 - \omega_0 / \omega = 0.127$$

$$V_p = \frac{V_{pres}}{1 + j\omega p \Omega} = \frac{I R_{tot}}{1 + j\omega p \Omega} = 14.12 \angle -45^\circ \text{ V}$$

$$I_L = \frac{V_p}{R_e + jX_{L2}} = \frac{14.12 \angle -45^\circ}{20 + j336.271} \approx 0.04196 \angle -131.596^\circ \text{ A}$$

$$I_C = \frac{V_p}{-jX_{C2}} = \frac{14.12 \angle -45^\circ}{-j297.486} \approx 0.0474 \angle 45^\circ \text{ A}$$