



- [1] For the circuit shown in Fig.1 , find the value of the current $i(t)$ after 0.4m sec. and 1.0m sec. respectively.
- [2] For the two circuits shown in Fig.2a,b , derive an expression for the current through the resistance and the voltage across it as a function of time .
- [3] Derive the expression of the output voltage of the network shown in Fig.3 , $v(t)$. What would be its value at $t = 0$ and as t tends to ∞ .
- [4] For the network shown in Fig.4 , find $v_o(t)$ for $t > 0$ using loop analysis . Verify your answer using the superposition theorem .
- [5] Find $v_o(t)$, $t > 0$, for the network shown in Fig.5 using node analysis .
- [6] Derive an expression for the current $i_o(t)$, $t > 0$, in the network shown in Fig.6 . What would be the value of this current as t tends to ∞ .
- [7] In the network shown in Fig.7 , use Thevenin's Theorem to derive an expression for $v_o(t)$, $t > 0$.
- [8] In the circuit shown in Fig.8 find the branch currents $i_1(t)$, $i_2(t)$, $i_3(t)$, $t > 0$. Apply the initial and final value theorems to the S-domain expressions .
- [9] Using the Laplace Transform Technique , find an expression for the current $i(t)$ shown in Fig.9 , $t > 0$, hence calculate its initial and final values .
- [10] For the circuit shown in Fig.10 , calculate the branch currents which will result when the switch is closed at $t=0$.
- [11] When the switch in the circuit shown in Fig.11 is closed , the condenser was charged such that $v_c(0) = 20 V$ and the current in the coil was $i_L(0) = 2 A$. Derive expressions for the instantaneous currents $i_1(t)$, $i_2(t)$ and $i_3(t)$ for $t > 0$.
- [12] In the circuit shown in Fig.12 , the capacitor is initially charged such that $v_c(0)=50V$. Calculate $v_c(t)$, $t > 0$. Using current sources only , derive an expression for the Capacitor current in the time domain $i_c(t)$, $t > 1$ msec. Calculate also $i_c(\infty)$ and verify your result using the final value theorem .

[13] The circuit shown in Fig. 13 is fed from a source $v(t)$ given by :

$$v(t) = 100 e^{-100t} \text{ V}$$

Calculate $i(t)$, $t > 0$.

[14] For the circuit shown in Fig. 14, calculate the potentials at nodes 1, 2 $v_1(t)$ and $v_2(t)$. Using the initial and final value theorems, calculate $v_1(0)$, $v_2(0)$, $v_1(\infty)$ and $v_2(\infty)$.

[15] Using the Laplace Transform, find $v_o(t)$ for $t > 0$, in the circuit shown in Fig. 15. Assume that the circuit has reached steady state before switching the source off.

[16] For the circuit shown in Fig. 16, find $i(t)$ for $t > 0$.

[17] Find the Z-Parameters of the two-port network shown in Fig. 17a. If the same network is used in Fig. 17b, calculate $i_2(t)$ for $t > 0$.

[18] Find $v_o(t)$ for $t > 0$ in the circuit shown in Fig. 18.

[19] Derive the expression of the output voltage $v_o(t)$ for the circuit shown in Fig. 19a if the input is $v(t)$ shown in :

i) Fig. 19b.

ii) Fig. 19c.

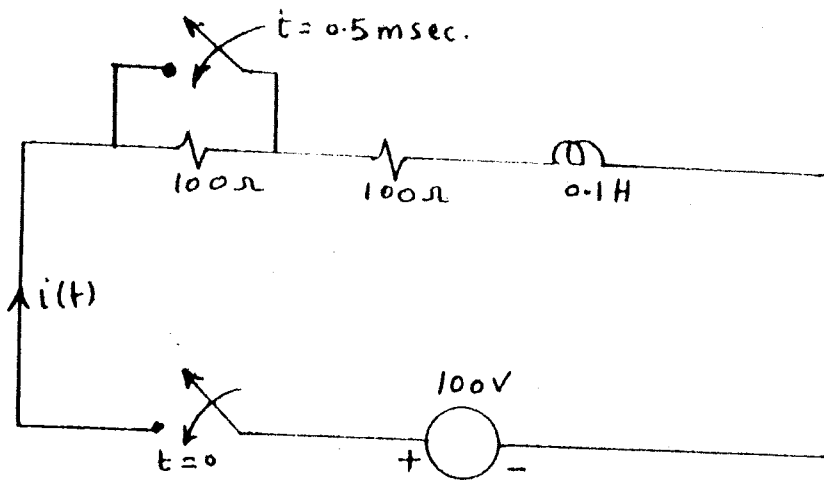


Fig. 1

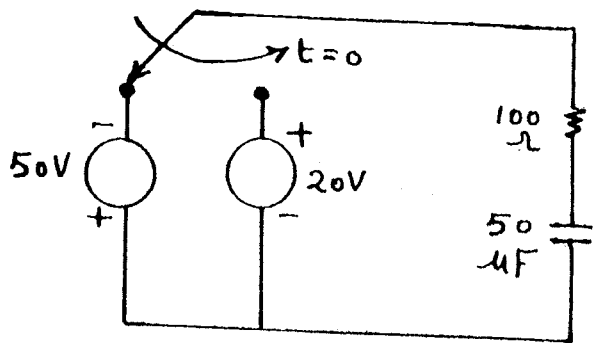


Fig. 2a

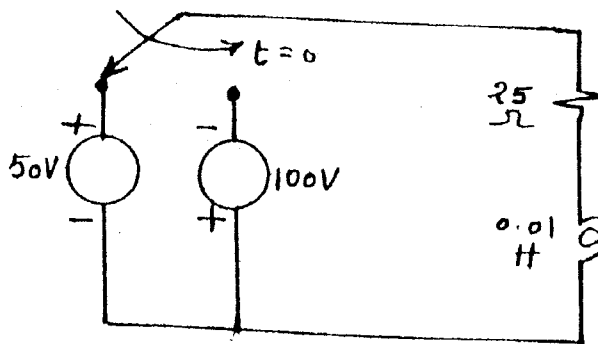


Fig. 2b

Fig. 3

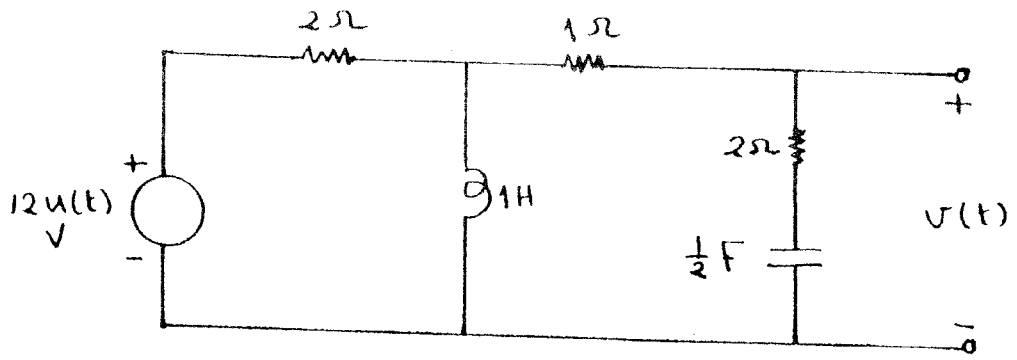


Fig. 4

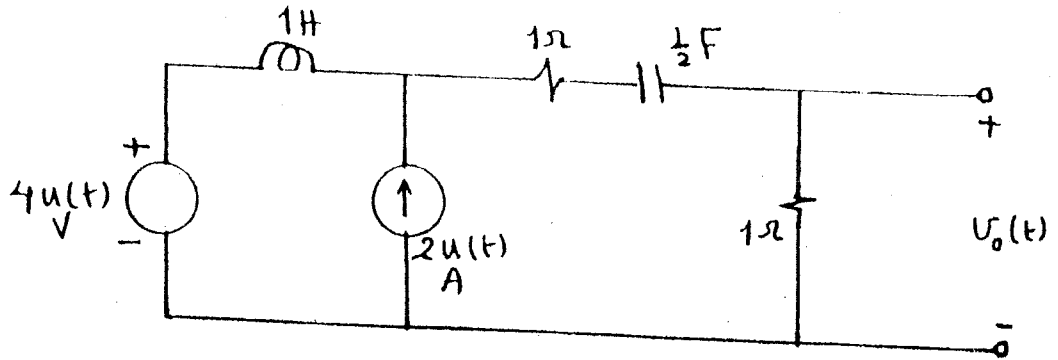


Fig. 5


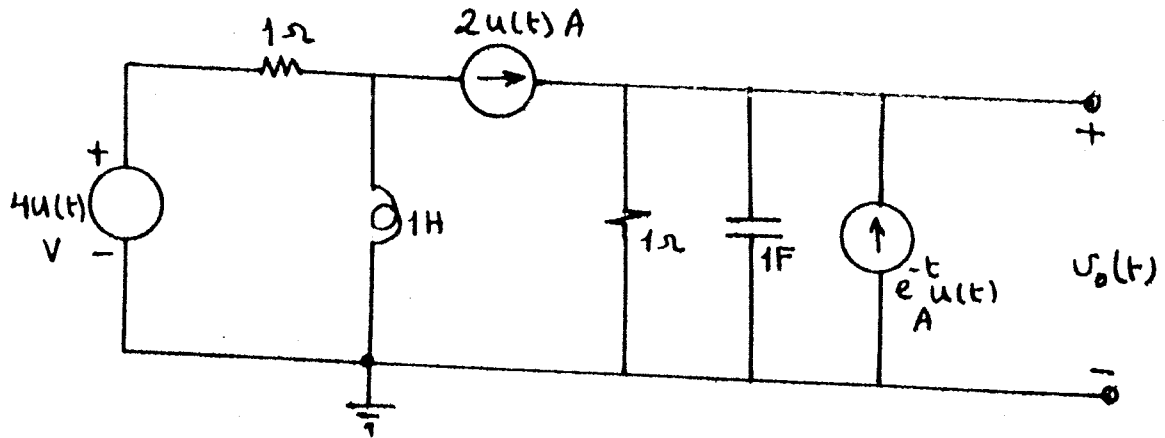


Fig. 6

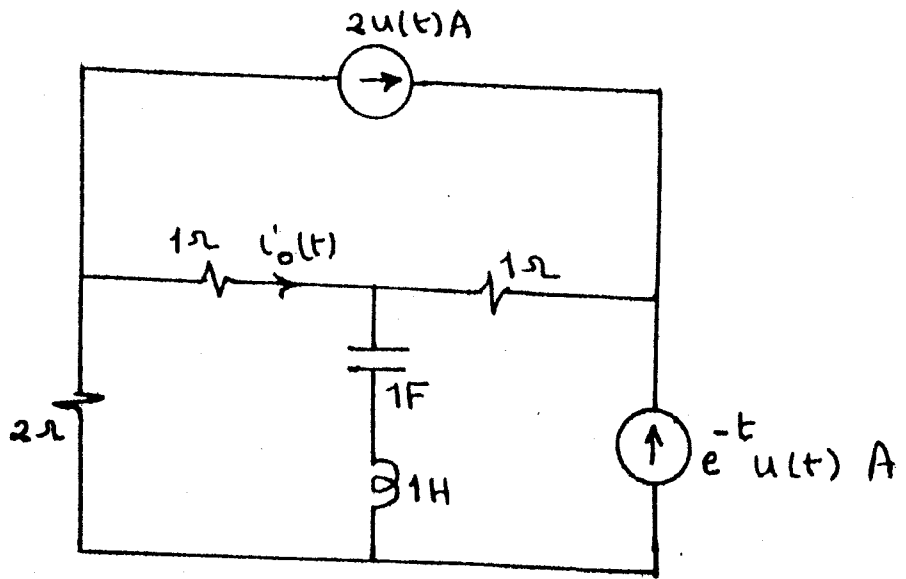

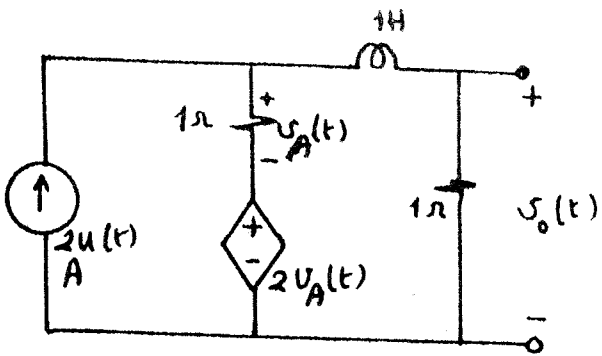


Fig. 7

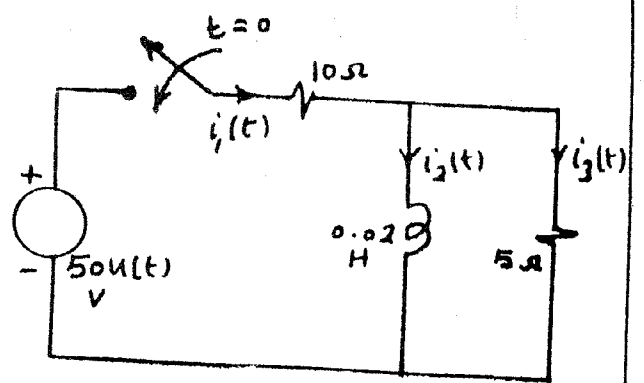


Fig. 8

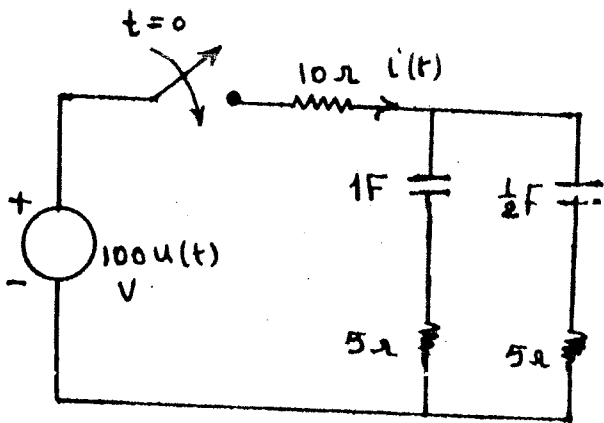


Fig. 9

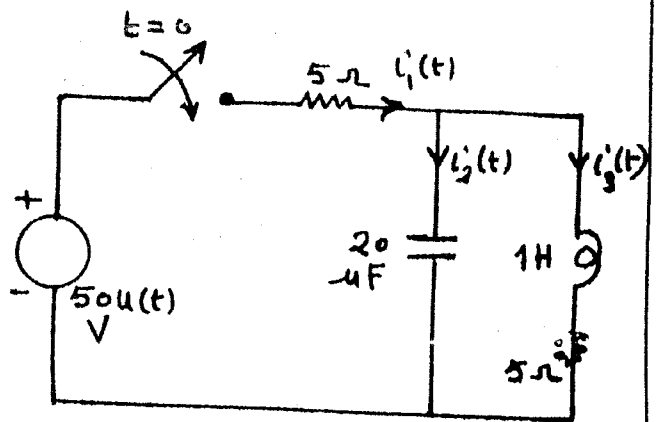


Fig. 10

Fig. 11

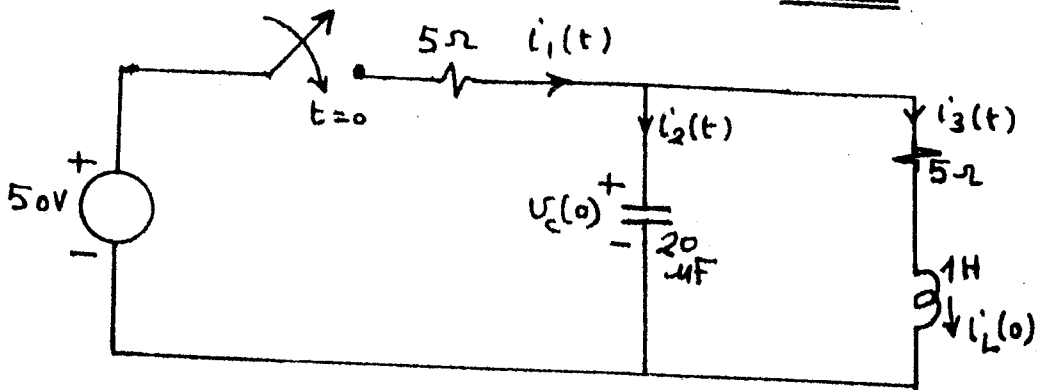


Fig. 12

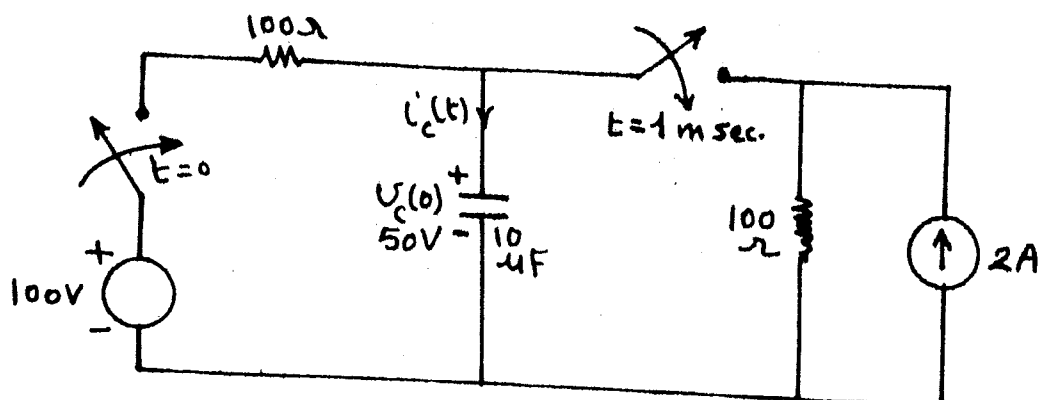


Fig. 13

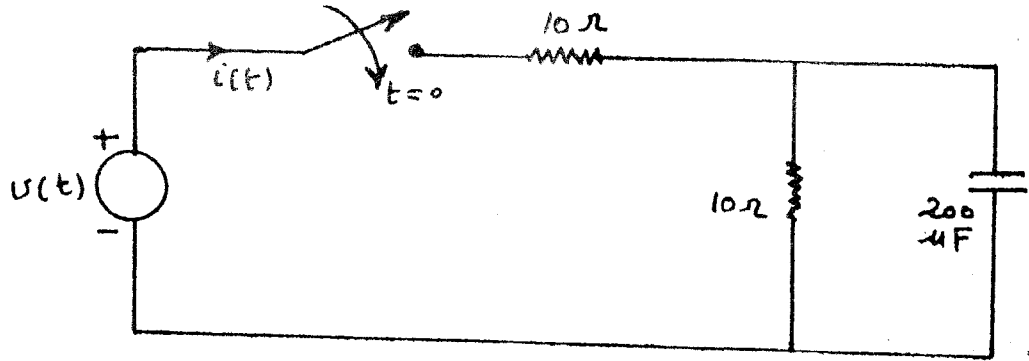


Fig. 14

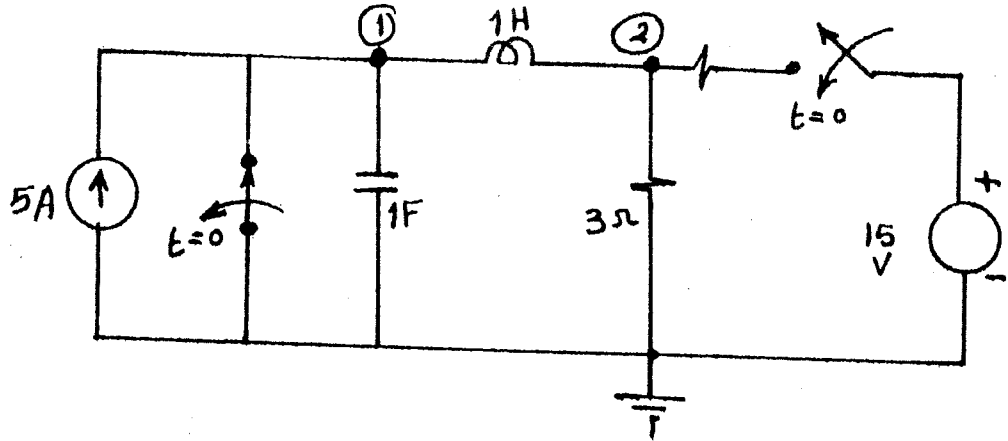


Fig. 15


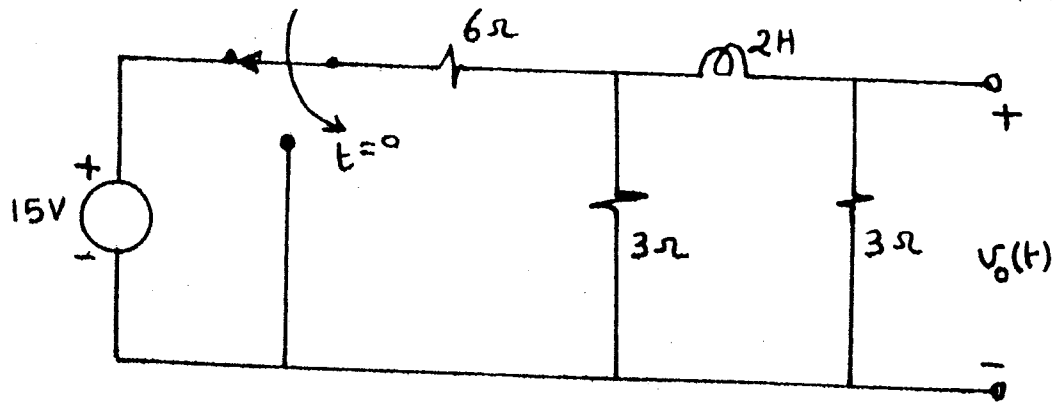


Fig. 16

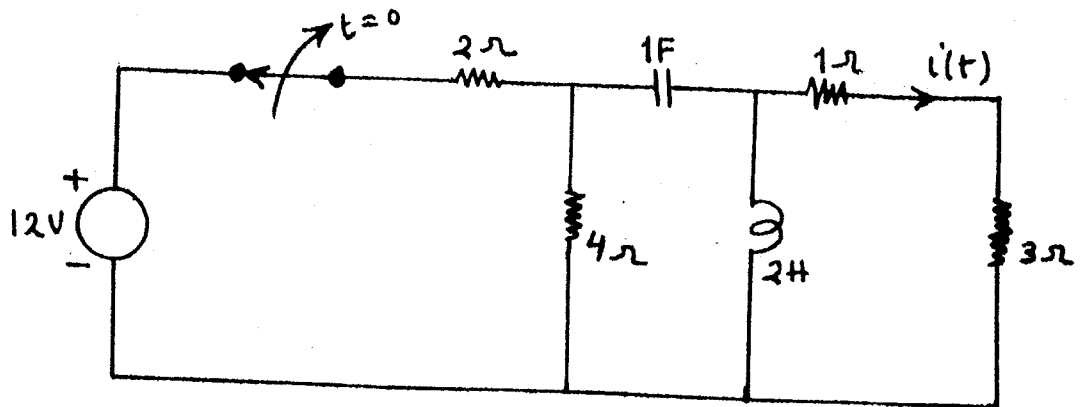

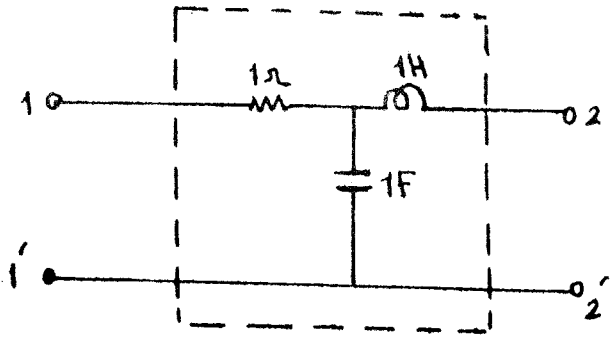


Fig. 17a

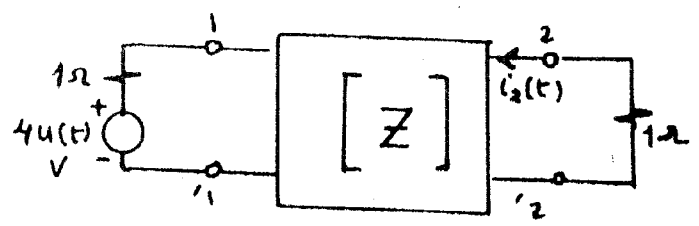


Fig. 17b

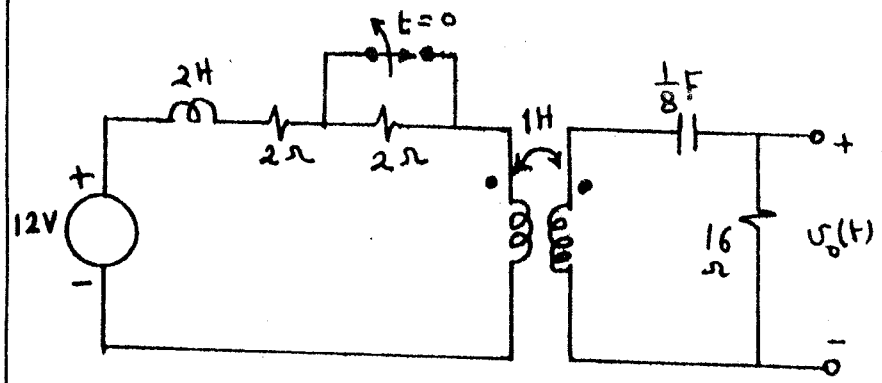


Fig. 18

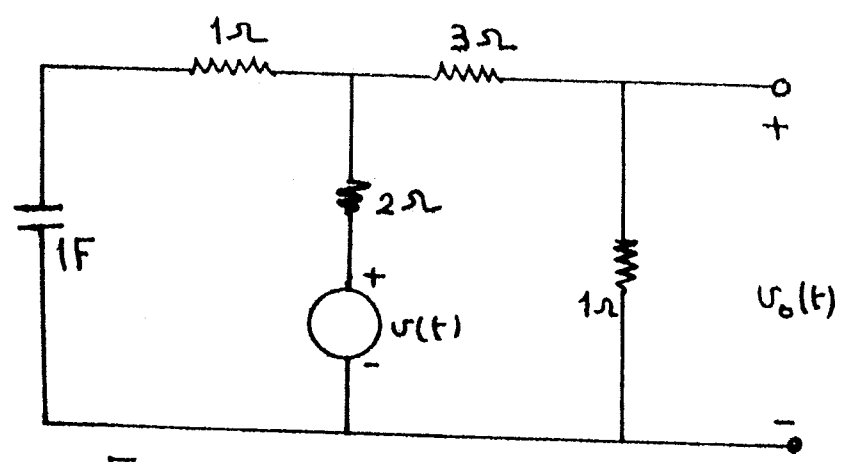


Fig. 19a

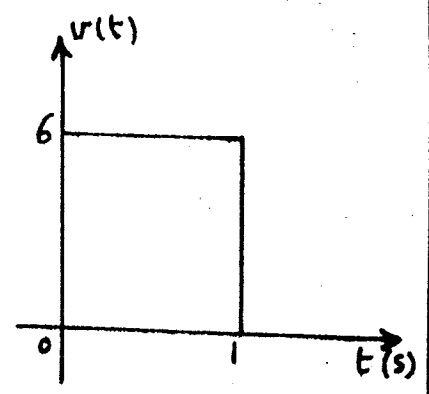


Fig. 19b

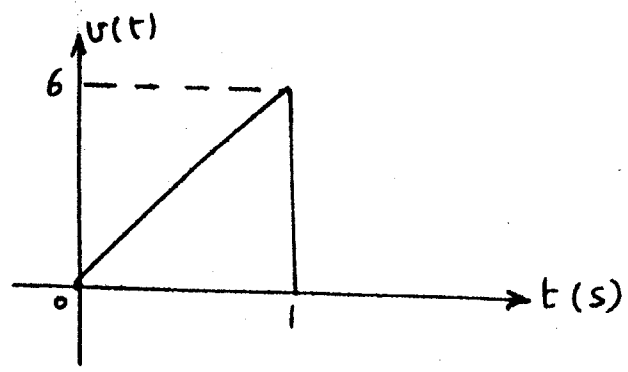


Fig. 19c



Question[1]: Answer of Question 2

For the two circuits shown in Figs.a,b, derive an expression for the current through the resistance and the voltage across it as a function of time.

Insert your results in Table 1.

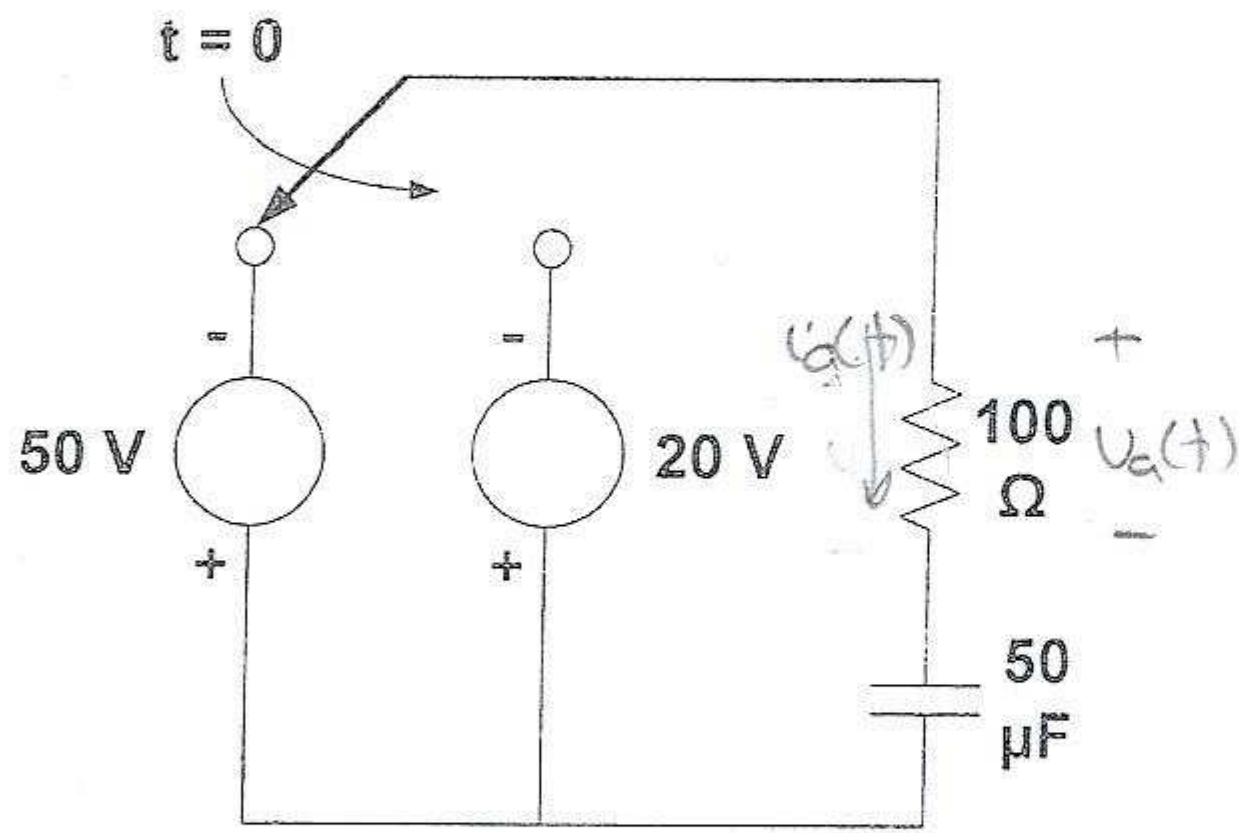


Fig.a


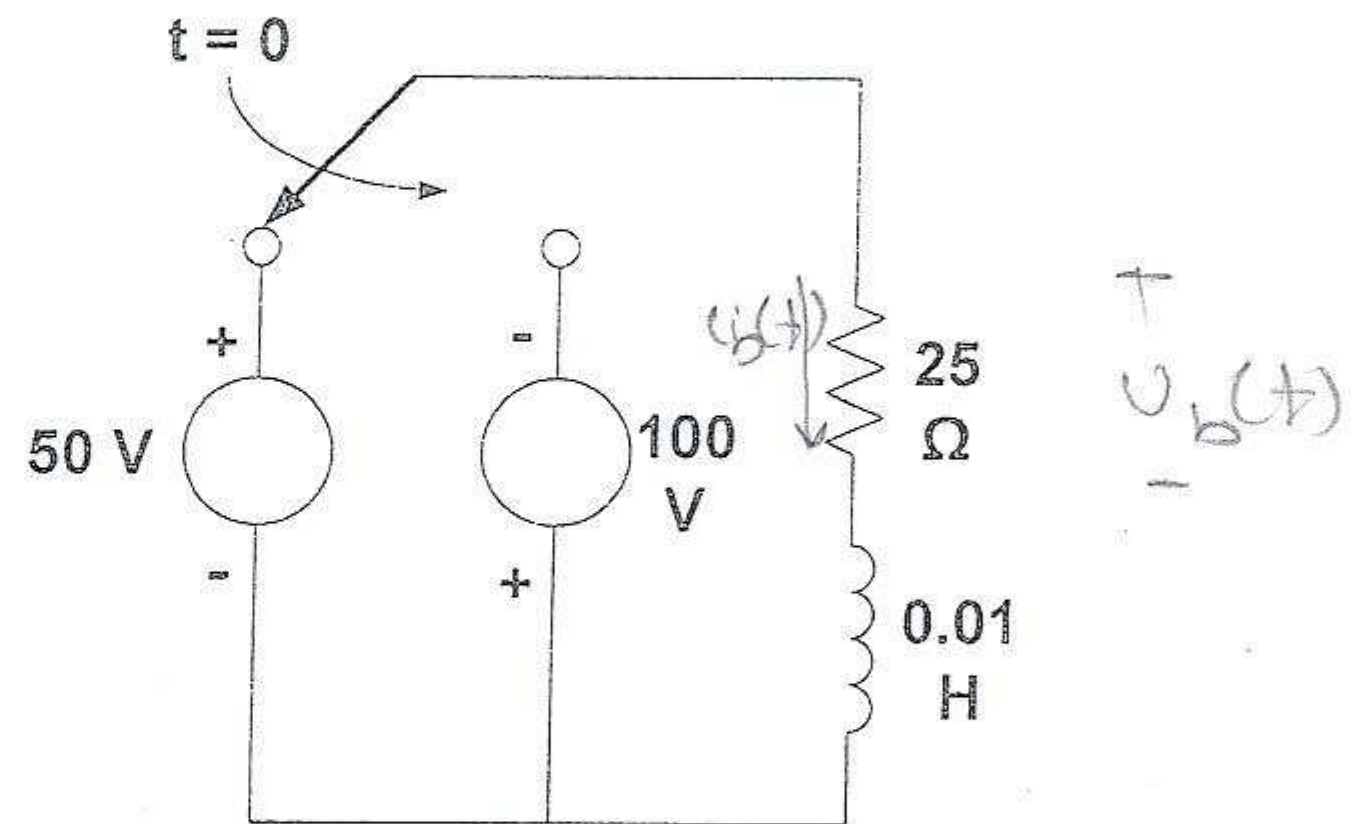


Fig.b

For Fig. a

→ Initial Condition


$$U_c(0) = 50V$$

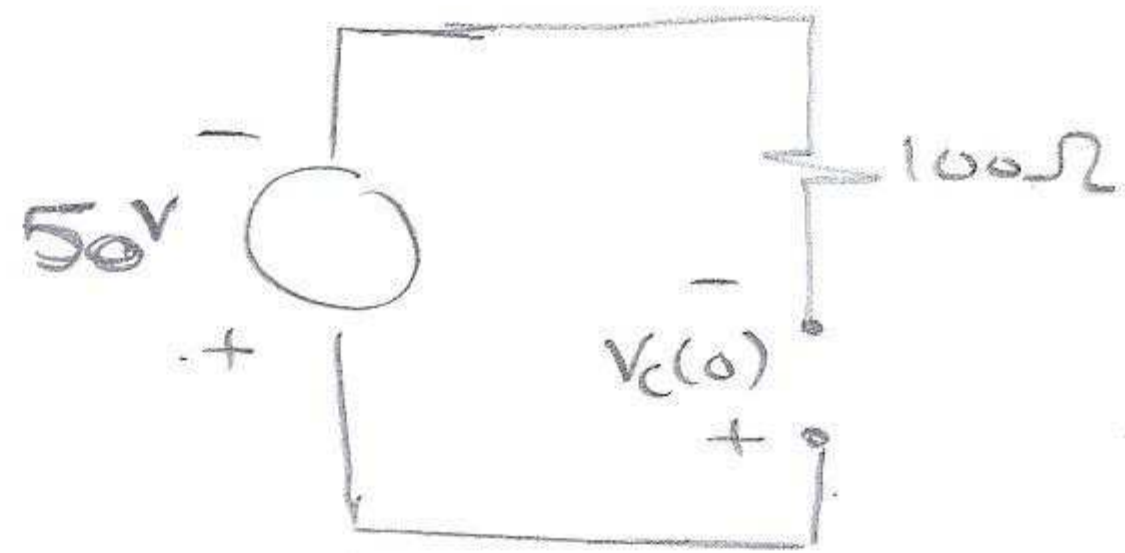

$$I_a(s) = \frac{\frac{50}{s} - \frac{20}{s}}{100 + \frac{1}{sC}}$$

$$= \frac{30}{100s + \frac{1}{C}}$$

$$= \frac{0.3}{s + 200}$$

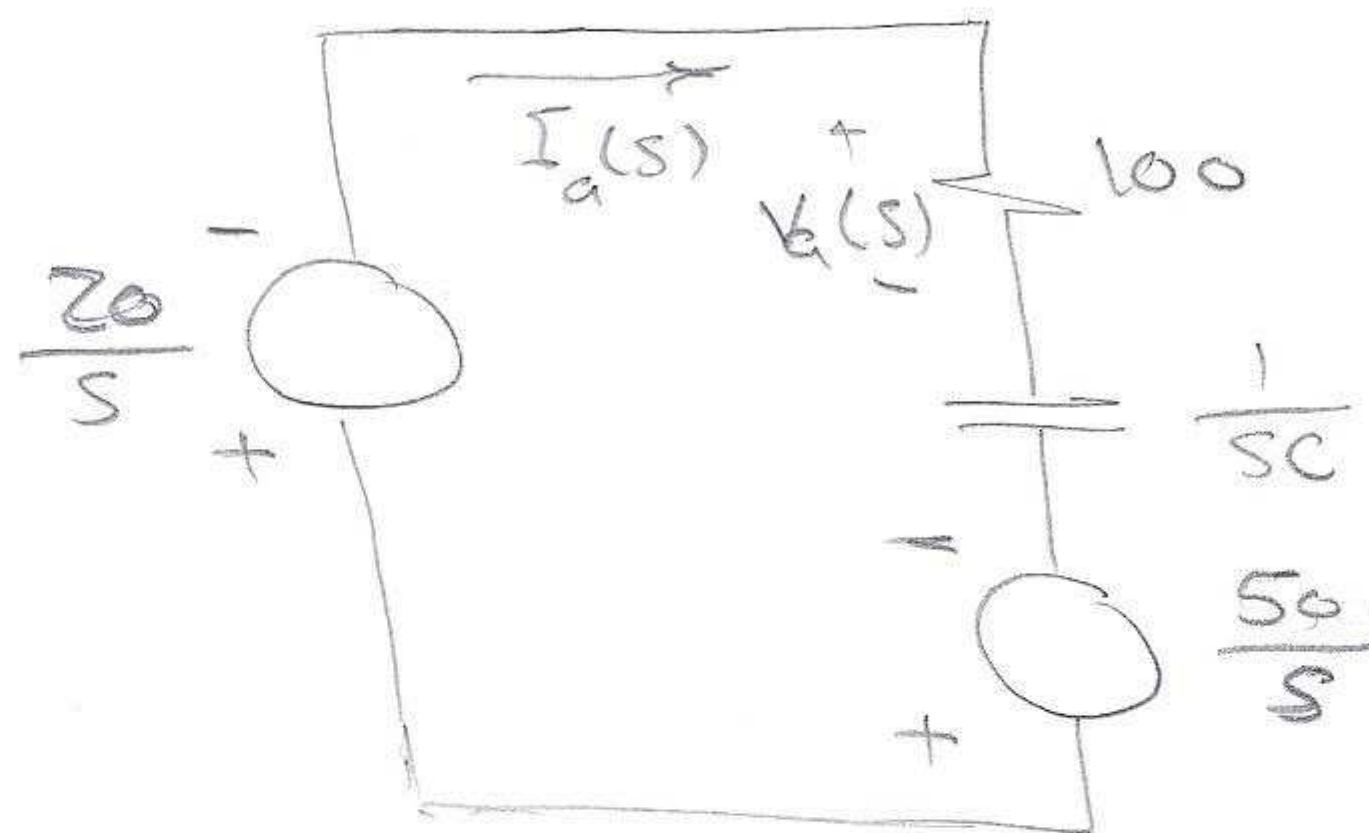


$$\therefore i_a(t) = 0.3 e^{-200t} \text{ Amp}$$

$$U_a(t) = 30 e^{-200t} \text{ Volts}$$



For Fig. b


$$i_L(0) = \frac{50}{25} = 2A$$

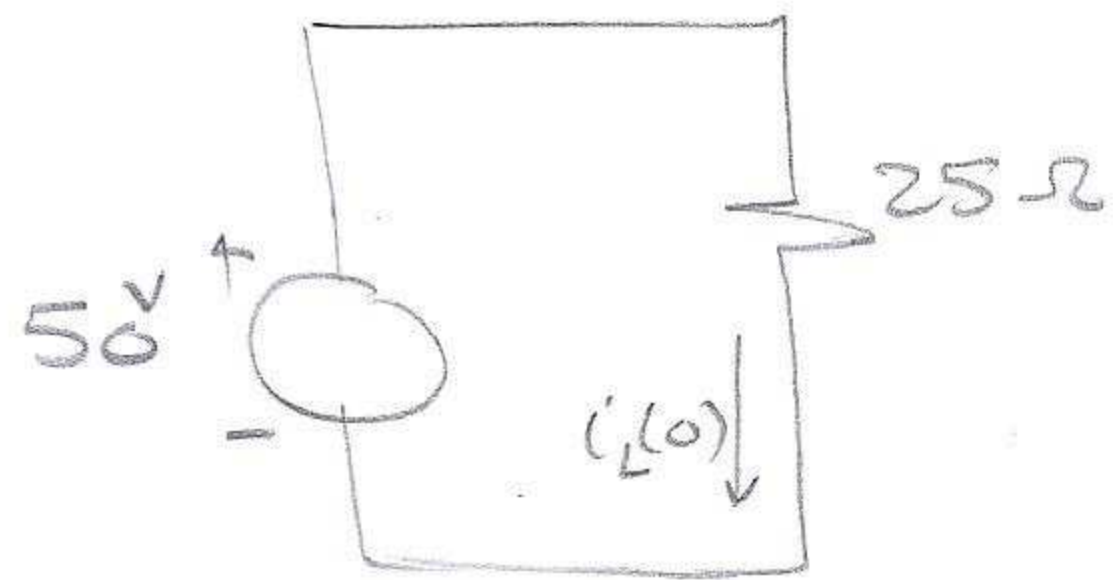

$$I_b(s) = \frac{0.02 - \frac{100}{s}}{0.01s + 25}$$

$$= \frac{25 - 10^4}{s(s + 2500)}$$

$$= \frac{-4}{s} + \frac{6}{s + 2500}$$

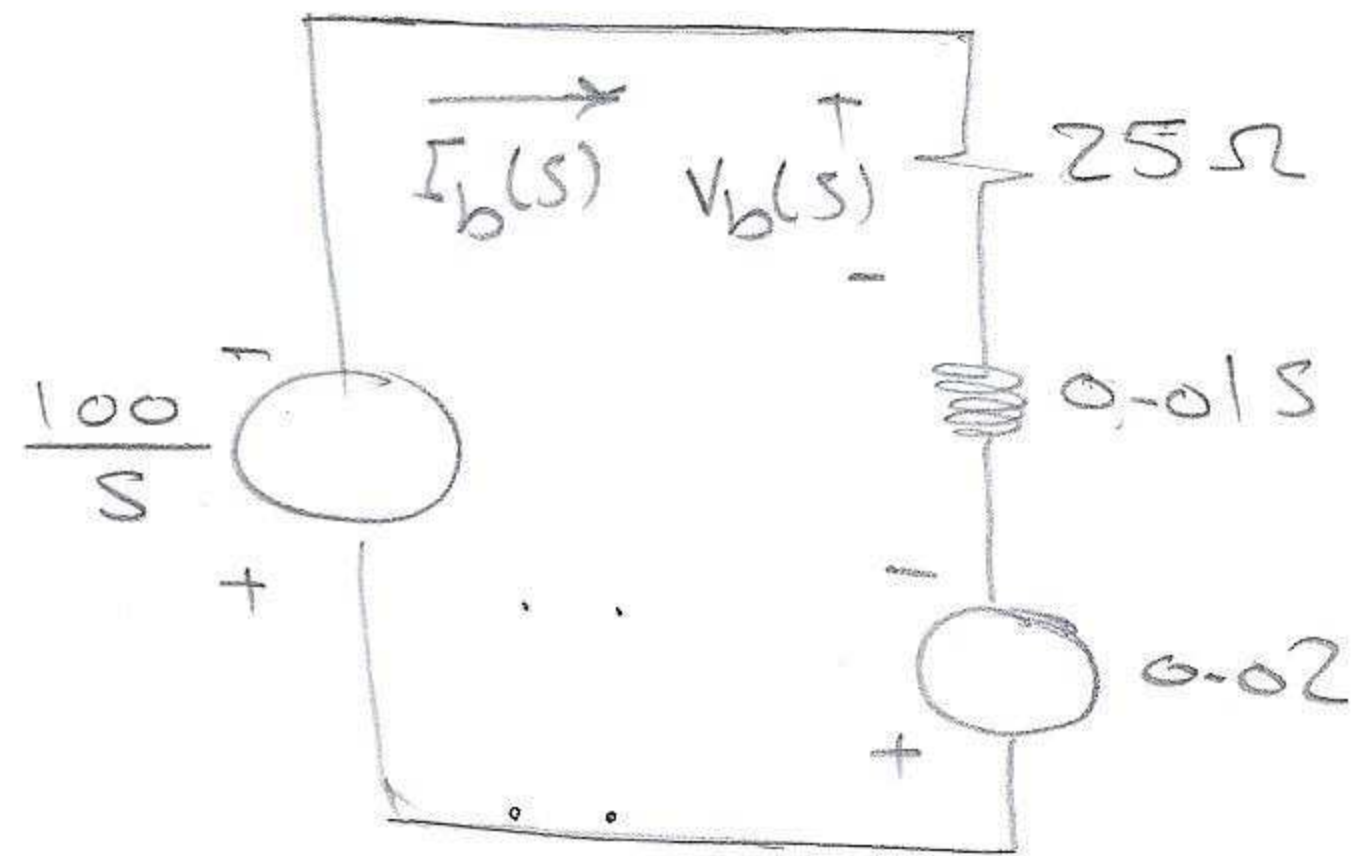

$$\therefore i_b(t) = -4 + 6e^{-2500t} \quad \text{Amp}$$

$$V_b(t) = -100 + 150e^{-2500t} \quad \text{Volts}$$





$i_a(t)$	$0.3 e^{-200t}$ Amp
$v_a(t)$	$30 e^{-200t}$ Volts
$i_b(t)$	$-4 + 6 e^{-2500t}$ Amp
$v_b(t)$	$-100 + 150 e^{-2500t}$ Volts.


Table 1



Question[2]: Answer of Question 1

For the circuit shown in figure, find the value of the current $i(t)$ at 0.4 m.sec. and 1.0 m.sec. respectively.

Insert your results in Table 2.

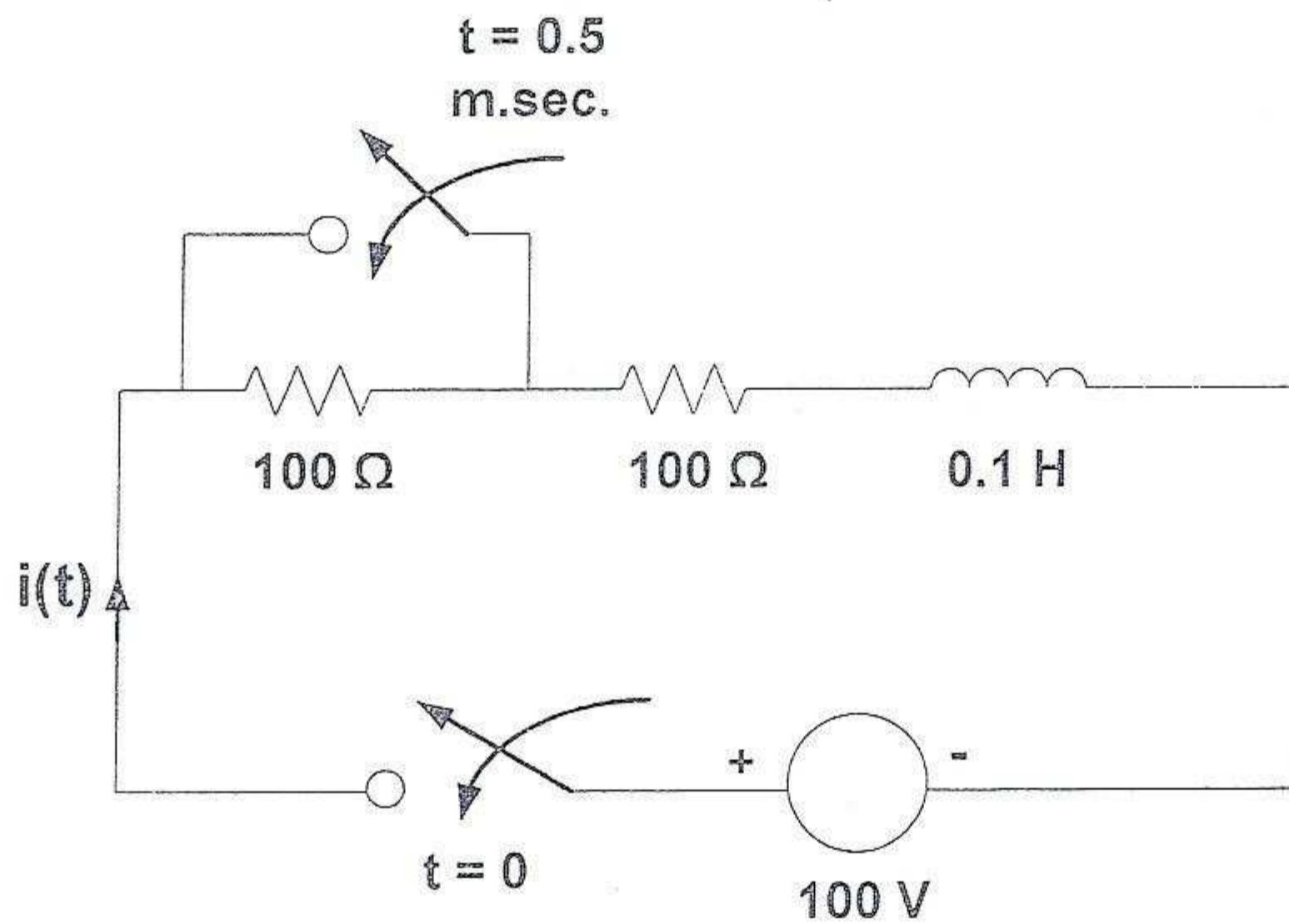

* at $0 < t < 0.5 \text{ msec}$

→ no-initial conditions


$$I(s) = \frac{\frac{100}{s}}{0.1s + 200}$$

$$= \frac{1000}{s(s + 2000)}$$

$$= \frac{1/2}{s} - \frac{1/2}{s + 2000}$$

$$\therefore i(t) = \frac{1}{2} (1 - e^{-2000t}) \{ u(t) - u(t - 0.5 \text{ msec}) \}. \text{ Amp.}$$
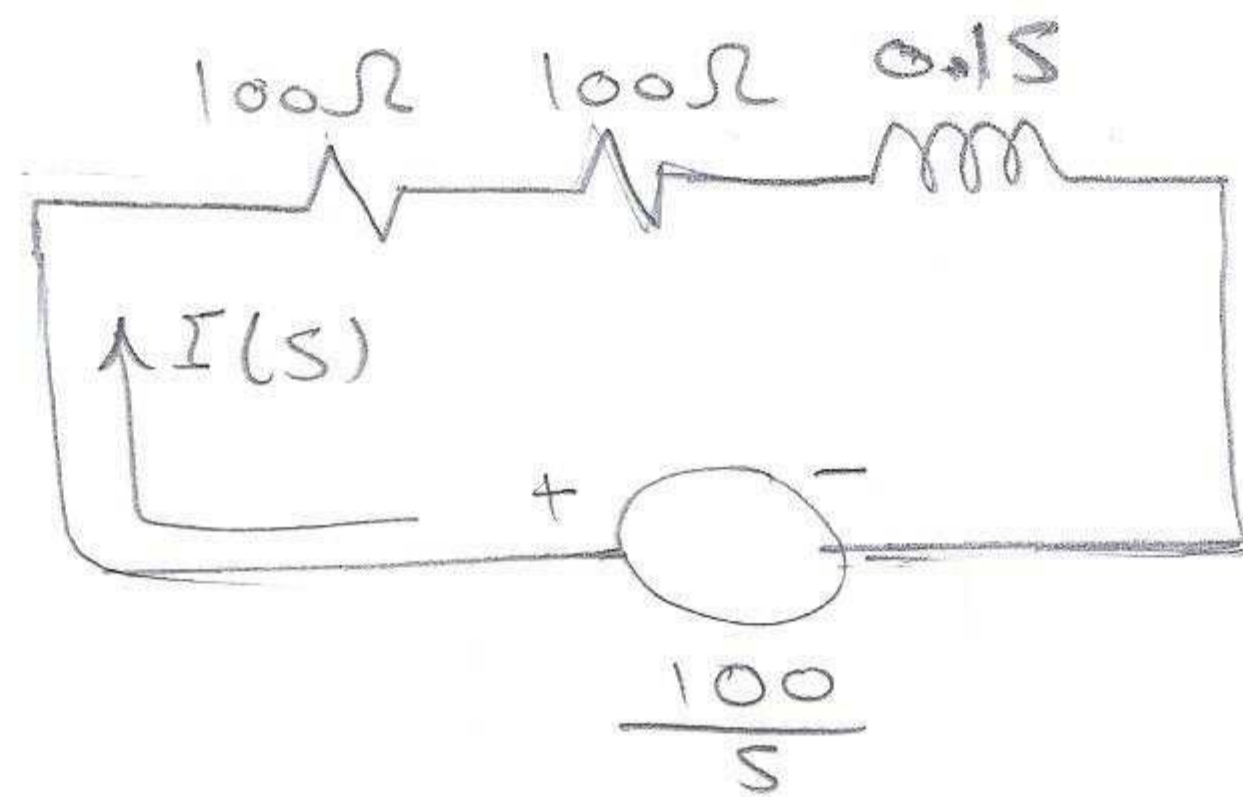
$$i_L(0.5 \text{ msec}) = 0.316 \text{ Amp.}$$





$$I(s) = \frac{\frac{100}{s} + 0.0316}{0.1s + 100}$$

$$= \frac{0.316s + 1000}{s(s + 1000)}$$

$$= \frac{1}{s} - \frac{0.684}{s + 1000}$$

$$\therefore i(t) = (1 - 0.684 e^{-1000t}) u(t)$$


$$\therefore i(t - 0.5 \text{ msec}) = (1 - 0.684 e^{-1000(t - 0.5 \text{ msec})}) u(t - 0.5 \text{ msec}) \text{ A}$$

$$i(0.4 \text{ msec}) = \frac{1}{2} (1 - e^{-2000 \times 0.4 \times 10^{-3}})$$

$$\boxed{i(0.4 \text{ msec}) = 0.275 \text{ Amp}}$$

$$i(1 \text{ msec}) = 1 - 0.684 e^{-1000 \times 0.5 \times 10^{-3}}$$
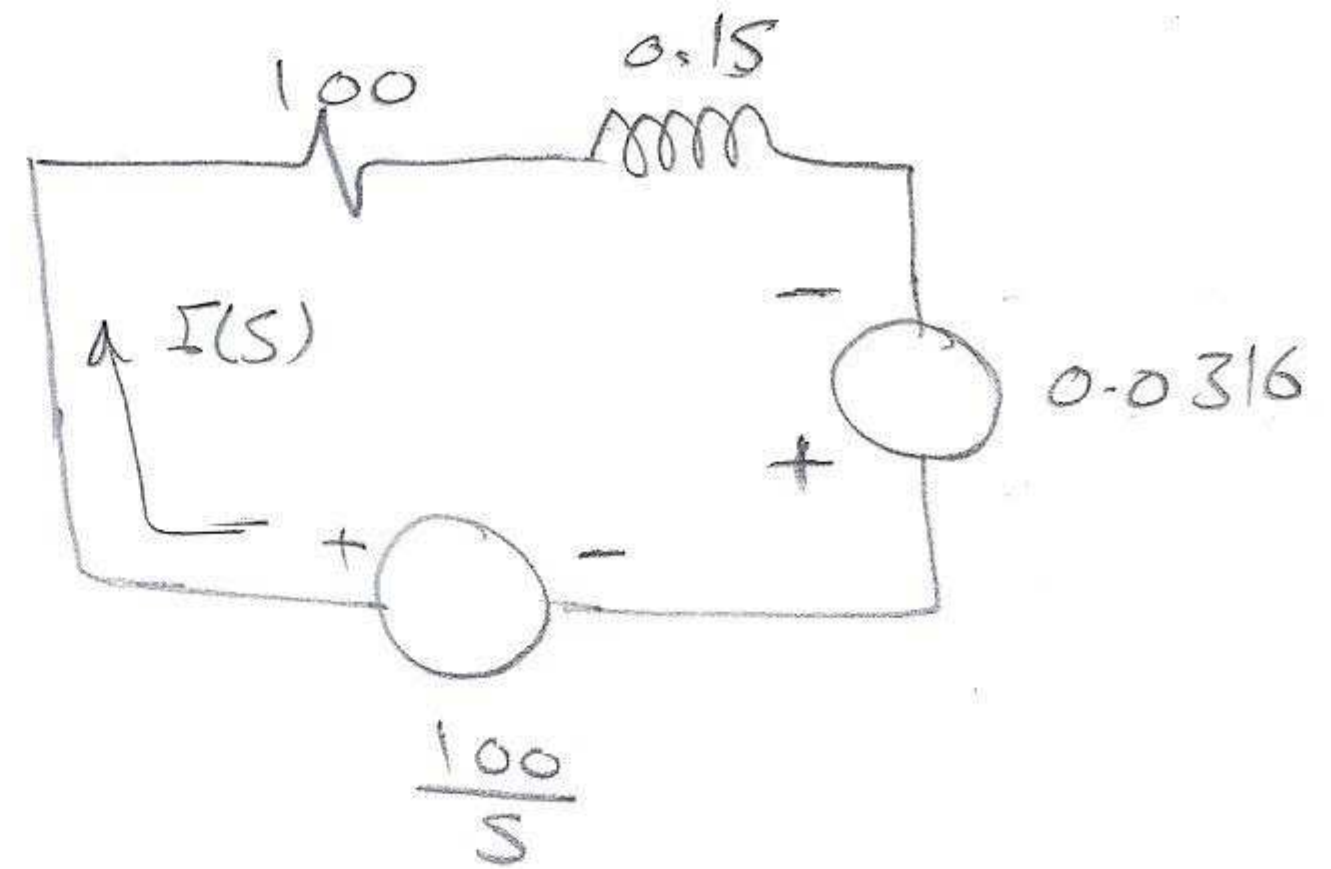
$$\boxed{\therefore i(1 \text{ msec}) = 0.585 \text{ A}}$$





$i(t)$ (at 0.4 msec.)	0.275 Amp
$i(t)$ (at 1.0 msec.)	0.585 Amp.


Table 2



Question[3]: Answer of Question 4

For the network shown in figure, find $v_o(t)$ for $t > 0$ using loop analysis. Verify your answer using the superposition theorem.


Insert your result in Table 3.

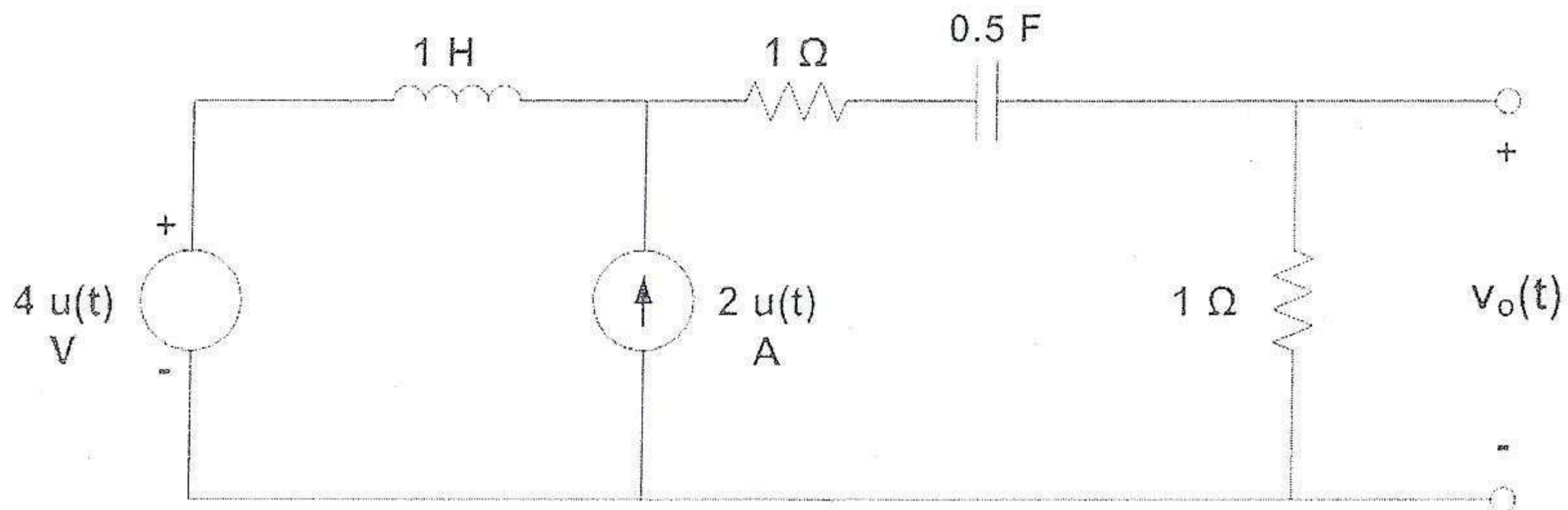

⇒ No - initial conditions

* using loop Analysis :-
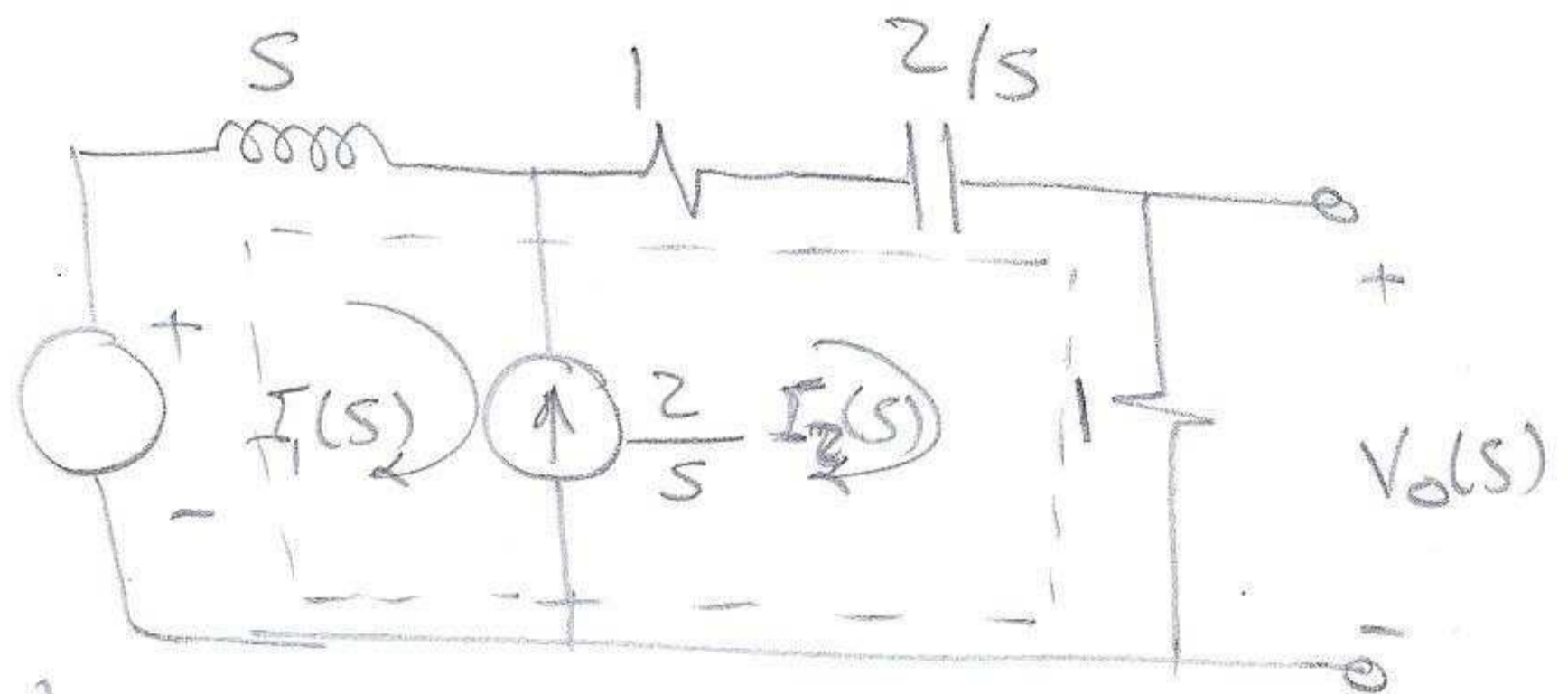
$$I_2(s) - I_1(s) = \frac{2}{s} \quad \text{--- (1)} \quad \frac{4}{s}$$



$$\frac{4}{s} = sI_1(s) + \left(2 + \frac{2}{s}\right) I_2(s)$$

$$\therefore \begin{bmatrix} -1 & 1 \\ s & 2 + \frac{2}{s} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} \frac{2}{s} \\ \frac{4}{s} \end{bmatrix}$$

$$\Delta = -2 - \frac{2}{s} - s = \frac{-(s^2 + 2s + 2)}{s}$$




$$\Delta_2 = \begin{vmatrix} -1 & \frac{2}{s} \\ s & \frac{4}{s} \end{vmatrix} = \frac{-4}{s} - 2 = \frac{-(2s+4)}{s}$$

$$I_2(s) = \frac{\Delta_2}{\Delta} = \frac{-(2s+4)}{s} * \frac{-s}{s^2+2s+2} = \frac{2s+4}{s^2+2s+2}$$

$$V_o(s) = 1 * I_2(s) \quad \therefore V_o(s) = \frac{2s+4}{s^2+2s+2} \quad \leftarrow \textcircled{1}$$

⇒ using super position

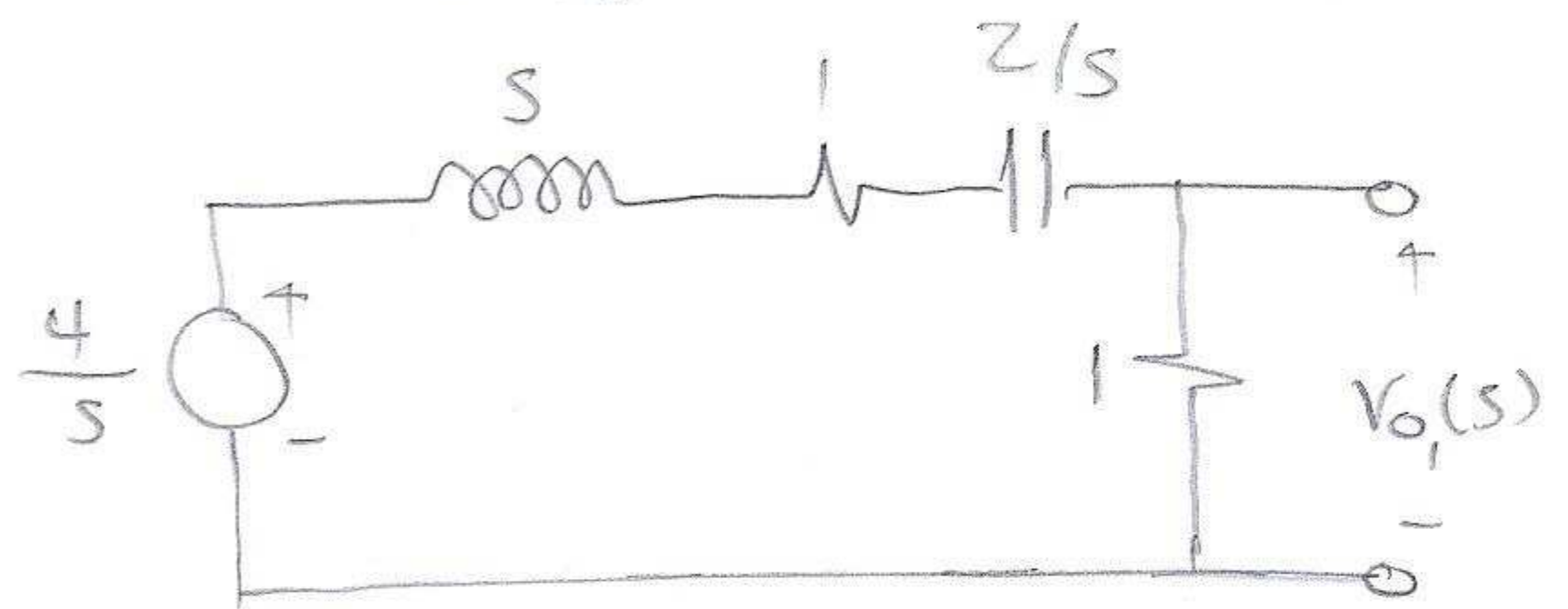
① due to $(\frac{4}{s} \text{ V})$ Source



$$V_{o_1}(s) = \frac{4}{s} * \frac{1}{2+s+\frac{2}{s}}$$

$$\therefore V_{o_1}(s) = \frac{4}{s^2+2s+2}$$

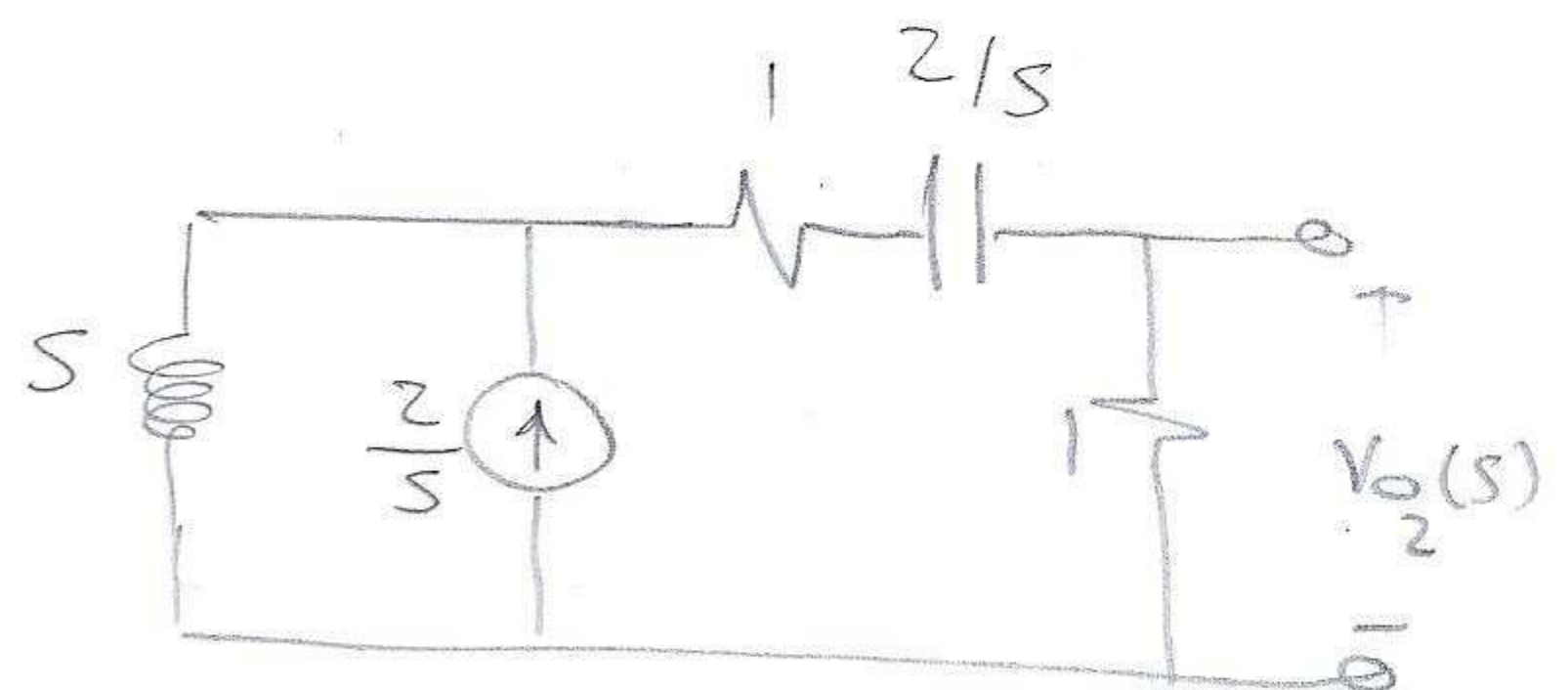② due to $(\frac{2}{s} \text{ A})$ Source



$$V_{o_2}(s) = 1 * \frac{2}{s} * \frac{s}{2+s+\frac{2}{s}} = \frac{2s}{s^2+2s+2}$$

$$V_o(s) = V_{o_1}(s) + V_{o_2}(s) \quad \therefore V_o(s) = \frac{2s+4}{s^2+2s+2} \quad \leftarrow \textcircled{2}$$



From ①, ② $V_o(s) \Big|_{\text{Loop Analysis}} = V_o(s) \Big|_{\text{Superposition}} = \frac{2s+4}{s^2+2s+2}$

$$V_o(s) = \frac{2s+4}{(s+1-j)(s+1+j)}$$

Poles at $s = -1 \pm j$

$$= \frac{k}{s+1-j} + \frac{k^*}{s+1+j}$$

$$k = \sqrt{2} \angle -45^\circ$$

$$\therefore v_o(t) = \left(2\sqrt{2} e^{-t} \cos(t - 45^\circ) \right) u(t) \text{ volts}$$


$v_o(t)$	$\left(2\sqrt{2} e^{-t} \cos(t - 45^\circ) \right) u(t)$
----------	---

Table 3




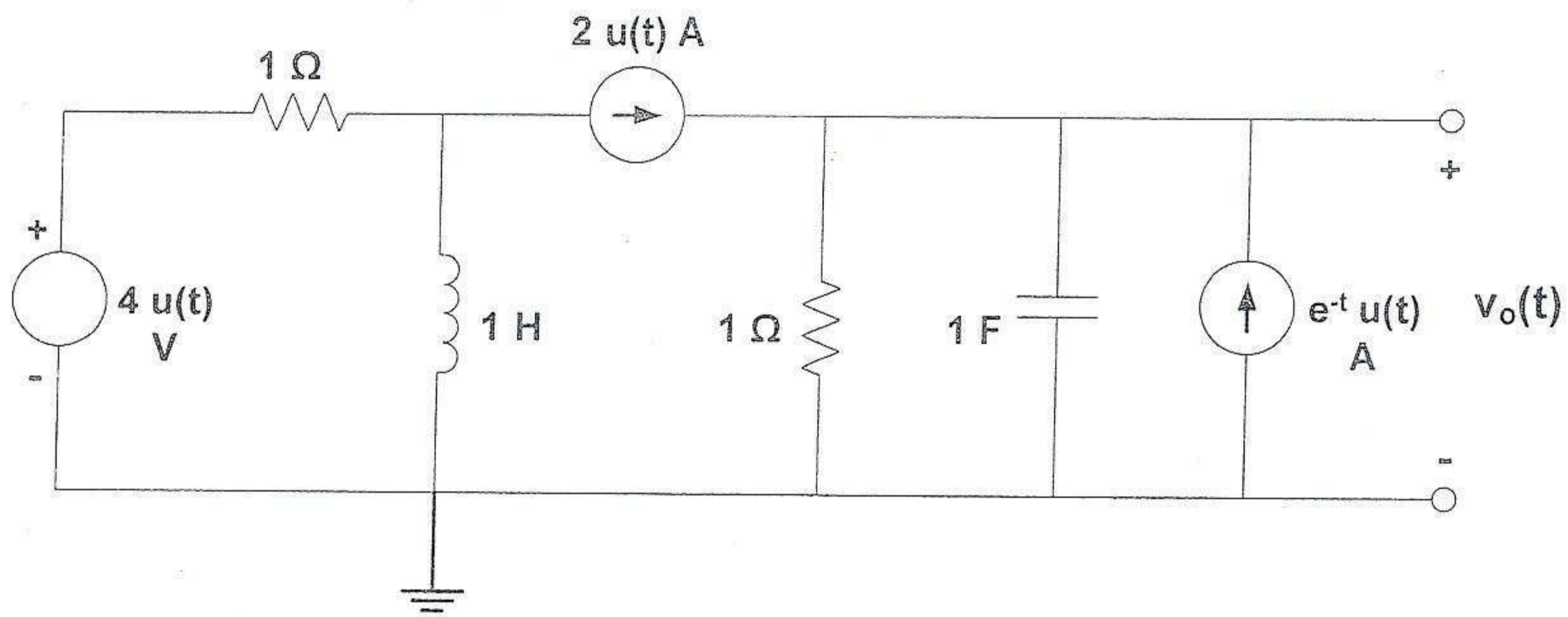Question[4]: Answer of Question 5

Find $v_o(t)$, $t > 0$, for the network shown in figure using node analysis.
Insert your result in Table 4.



\Rightarrow no-initial conditions

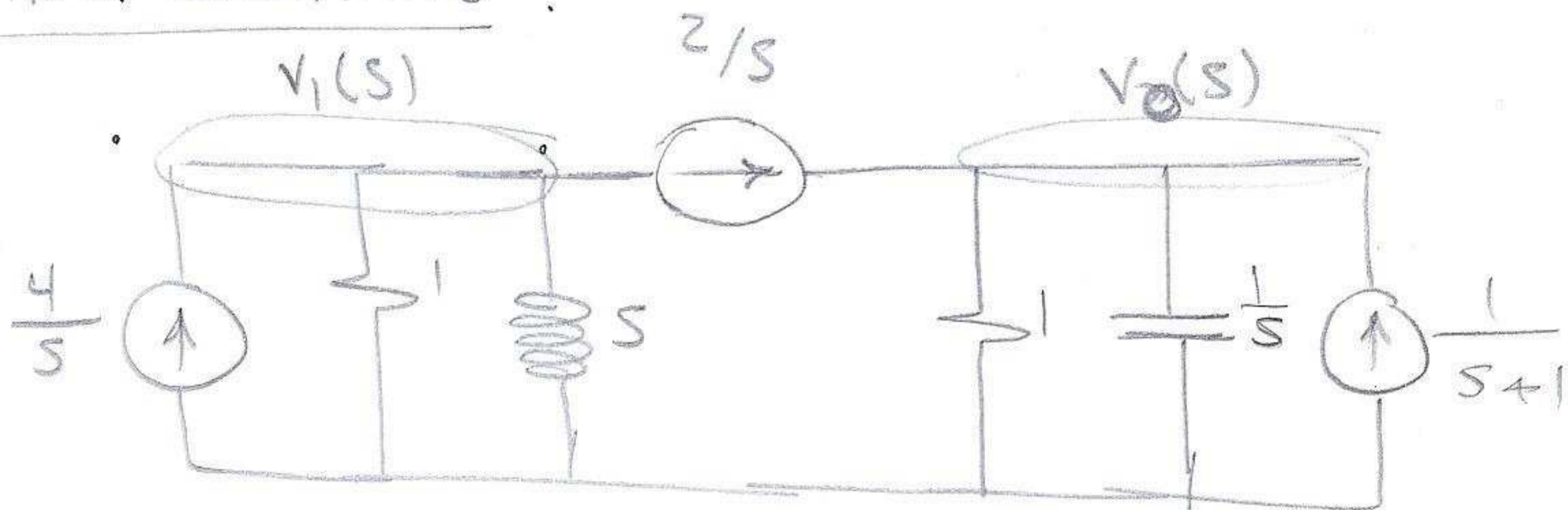

$$\begin{bmatrix} 1 + \frac{1}{s} & 0 \\ 0 & 1 + s \end{bmatrix} \begin{bmatrix} v_1(s) \\ v_o(s) \end{bmatrix} = \begin{bmatrix} \frac{4}{s} - \frac{2}{s} \\ \frac{2}{s} + \frac{1}{s+1} \end{bmatrix}$$

$$\therefore \begin{bmatrix} \frac{s+1}{s} & 0 \\ 0 & s+1 \end{bmatrix} \begin{bmatrix} v_1(s) \\ v_o(s) \end{bmatrix} = \begin{bmatrix} \frac{2}{s} \\ \frac{3s+2}{s(s+1)} \end{bmatrix}$$



$$\Delta = \frac{(s+1)}{s} * (s+1) - 0 = \frac{(s+1)^2}{s}$$

$$\Delta_2 = \begin{vmatrix} \frac{s+1}{s} & \frac{2}{s} \\ 0 & \frac{3s+2}{s(s+1)} \end{vmatrix} = \frac{3s+2}{s^2}$$

$$V_0(s) = \frac{\Delta_2}{\Delta} = \frac{3s+2}{s^2} * \frac{s}{(s+1)^2} = \frac{3s+2}{s(s+1)^2}$$

$$= \frac{k_0}{s} + \frac{k_1}{s+1} + \frac{k_2}{(s+1)^2}$$

$$3s+2 = k_0(s+1)^2 + k_1 s(s+1) + k_2 s$$

$$k_0 = 2$$

$$k_2 = 1$$

$$k_1 + k_0 = 0 \quad \therefore k_1 = -2$$

$$\therefore V_0(s) = \frac{2}{s} - \frac{2}{s+1} + \frac{1}{(s+1)^2}$$

$$\boxed{\therefore V_0(t) = (2 - 2e^{-t} + te^{-t})u(t)}$$





$v_o(t)$	$(z - ze^{-t} + te^{-t})u(t)$
----------	-------------------------------

Table 5




Question[5]:

Answer of Question 6

Derive an expression for the current $i_o(t)$, $t > 0$, in the network shown in figure. What would be the steady state value of this current?

Insert your results in Table 5.

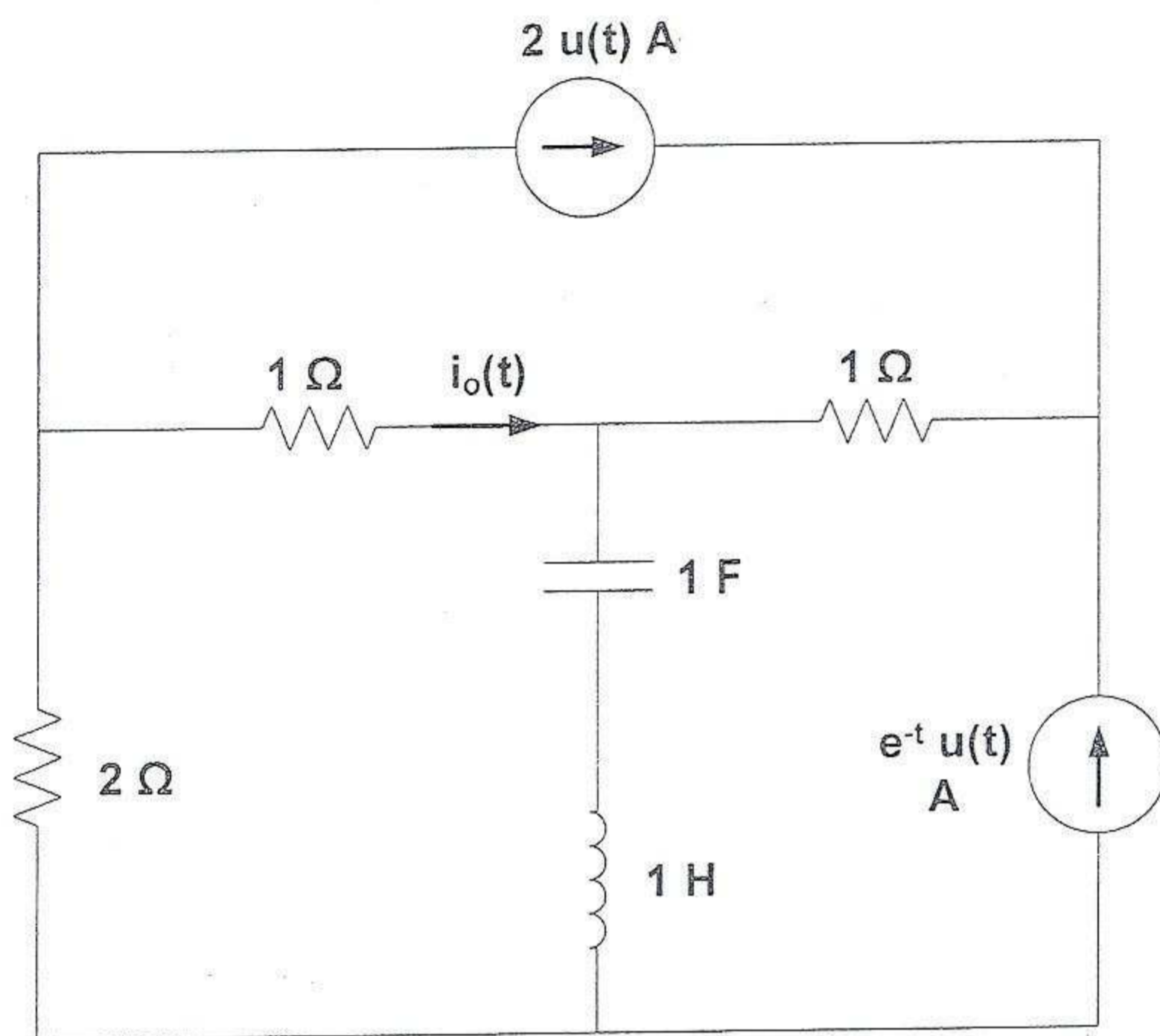


⇒ no-initial conditions

$$I_1 = \frac{2}{s}$$

$$I_2 = \frac{-1}{s+1}$$
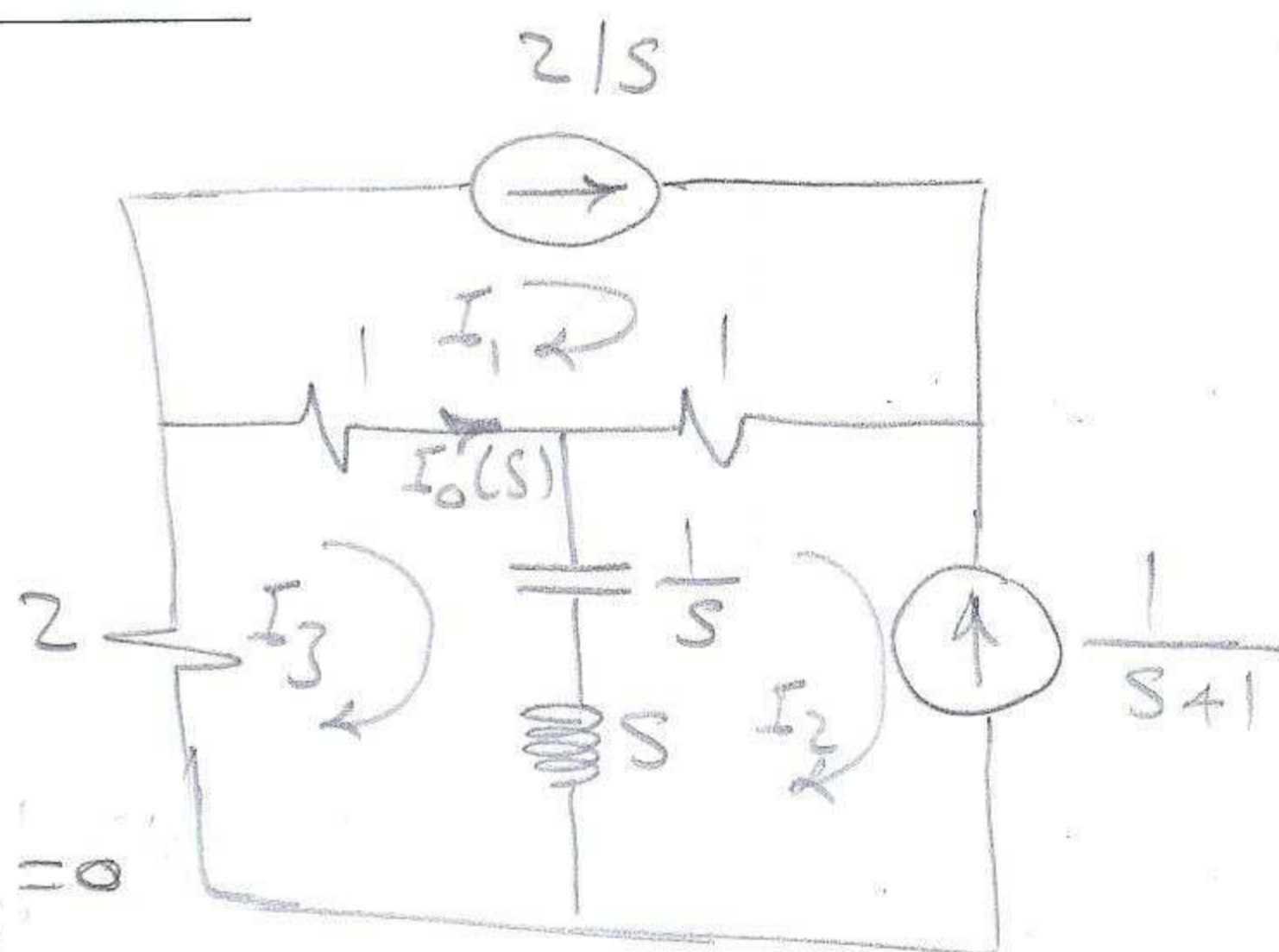
$$-I_1 - (s + \frac{1}{s})I_2 + (3 + s + \frac{1}{s})I_3 = 0$$



$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ -1 & \frac{-(s^2+1)}{s} & \frac{s^2+3s+1}{s} & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} \frac{2}{s} \\ \frac{-1}{s+1} \\ 0 \end{bmatrix}$$



$$\Delta = \frac{s^2 + 3s + 1}{s}$$

$$\Delta_1 = \begin{vmatrix} \frac{2}{s} & 0 & 0 \\ -1 & 1 & 0 \\ s+1 & \frac{-(s^2+1)}{s} & \frac{s^2+3s+1}{s} \end{vmatrix} = \frac{2}{s} * \frac{s^2+3s+1}{s}$$

$$\Delta_3 = \begin{vmatrix} 1 & 0 & \frac{2}{s} \\ 0 & 1 & \frac{-1}{s+1} \\ -1 & \frac{-(s^2+1)}{s} & 0 \end{vmatrix} = \frac{-(s^2+1)}{s(s+1)} + \frac{2}{s}$$
$$= \frac{-s^2 - 1 + 2s + 2}{s(s+1)}$$

$$\Delta_3 = \frac{-s^2 + 2s + 1}{s(s+1)}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{2}{s}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{-s^2 + 2s + 1}{s(s+1)} * \frac{s}{(s^2 + 3s + 1)}$$

$$\therefore I_3 = \frac{-s^2 + 2s + 1}{(s+1)(s^2 + 3s + 1)}$$

$$I_0 = I_3 - I_1 = \frac{-s^2 + 2s + 1}{(s+1)(s^2 + 3s + 1)} - \frac{2}{s}$$



$$\therefore I_o(s) = \frac{-s^2 + 2s + 1}{(s+1)(s+0.382)(s+2.618)} - \frac{2}{s}$$

$$= \frac{2}{s+1} + \frac{0.065}{s+0.382} - \frac{3.065}{s+2.618} - \frac{2}{s}$$

$$\therefore i_o(t) = (2e^{-t} + 0.065e^{-0.382t} - 3.065e^{-2.618t} - 2)u(t)$$

$$i_o(\infty) = -2 \text{ Amp}$$



$v_o(t)$ for $t > 0$	$(2e^{-t} + 0.065e^{-0.382t} - 3.065e^{-2.618t} - 2)u(t)$
v_o (Steady State)	-2 Amp.


Table 5



Question[6]: Answer of Question 7

In the network shown in figure, use Thevenin's Theorem to derive an expression for $v_o(t)$, $t > 0$.

Insert your result in Table 6.

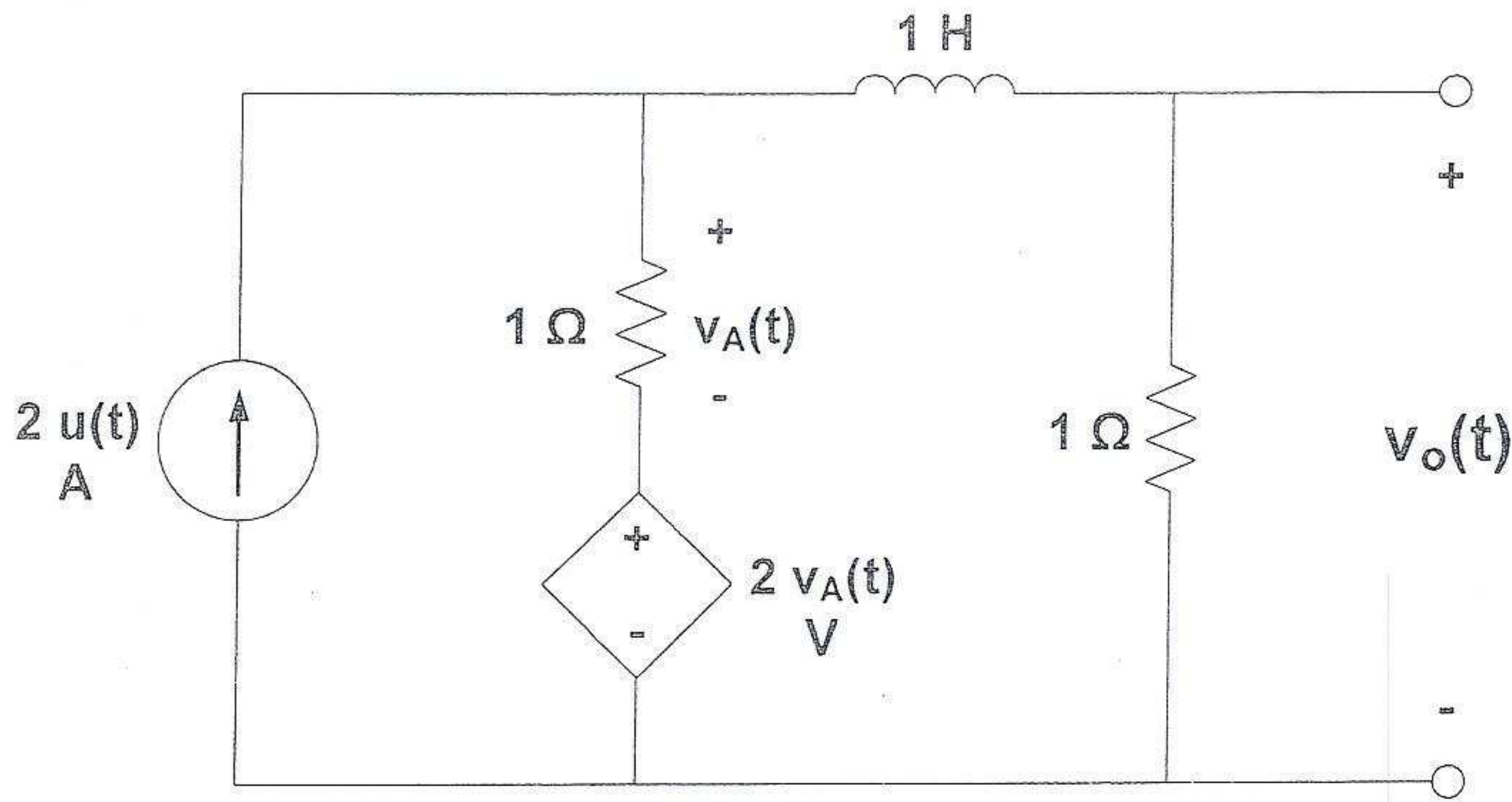


⇒ no - initial conditions

$$V_{th} = v_A + 2v_A$$

$$= 3v_A$$

$$v_A = \frac{2}{s} \times 1 = \frac{2}{s}$$

$$\therefore V_{th} = \frac{6}{s}$$

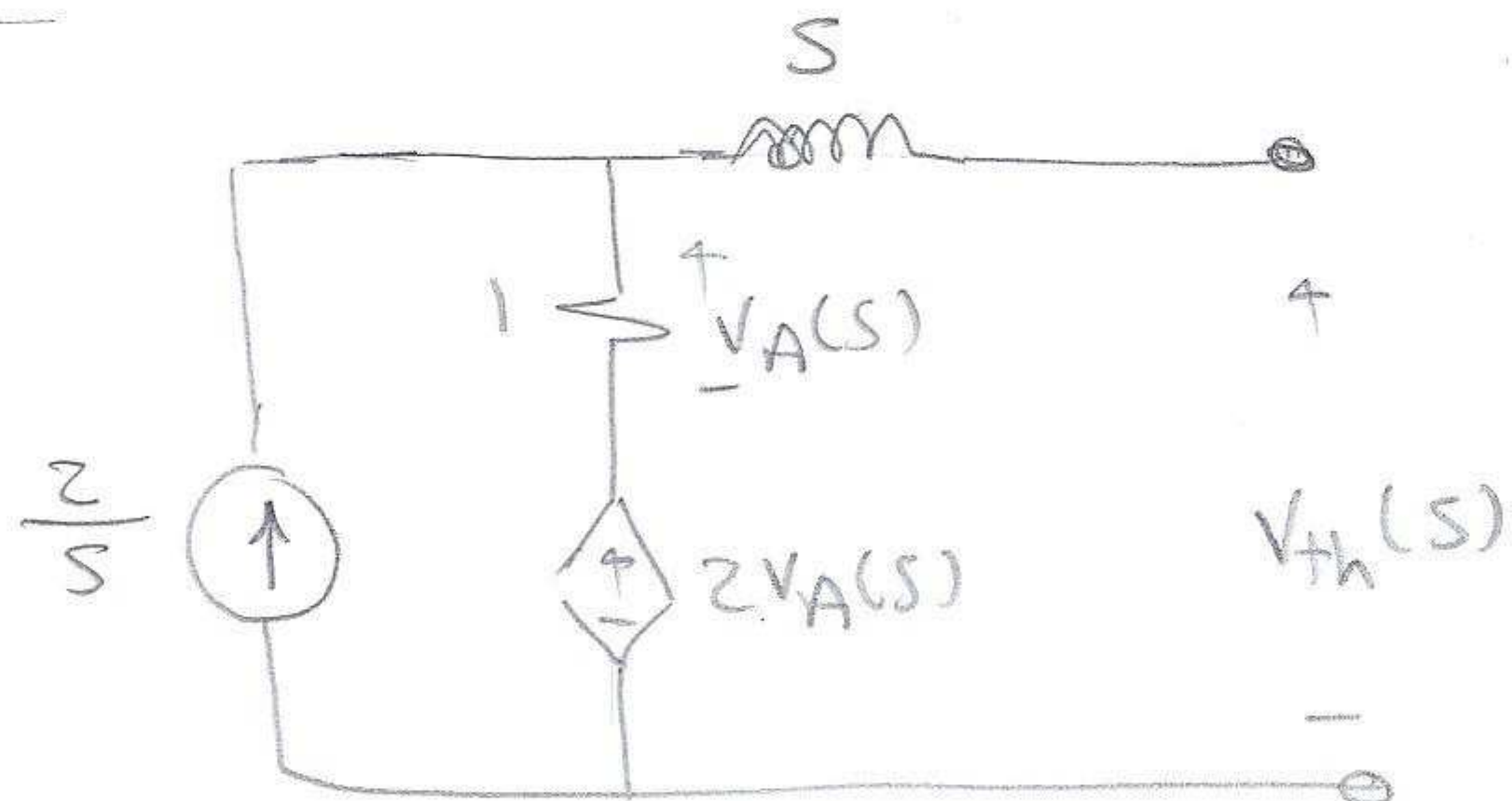



KCL at ①

$$\frac{2}{s} = \frac{V_A}{1} + I_N$$



$$\therefore I_N + V_A = \frac{2}{s}$$

$$I_N = \frac{V_A + 2V_A}{s} = \frac{3V_A}{s} \quad \therefore V_A = \frac{s}{3} I_N$$

$$\therefore I_N + \frac{s}{3} I_N = \frac{2}{s} \quad \Rightarrow I_N \left(\frac{s+3}{3} \right) = \frac{2}{s}$$

$$\therefore I_N = \frac{6}{s(s+3)}$$

$$Z_{th} = \frac{V_{th}}{I_N} = s+3$$

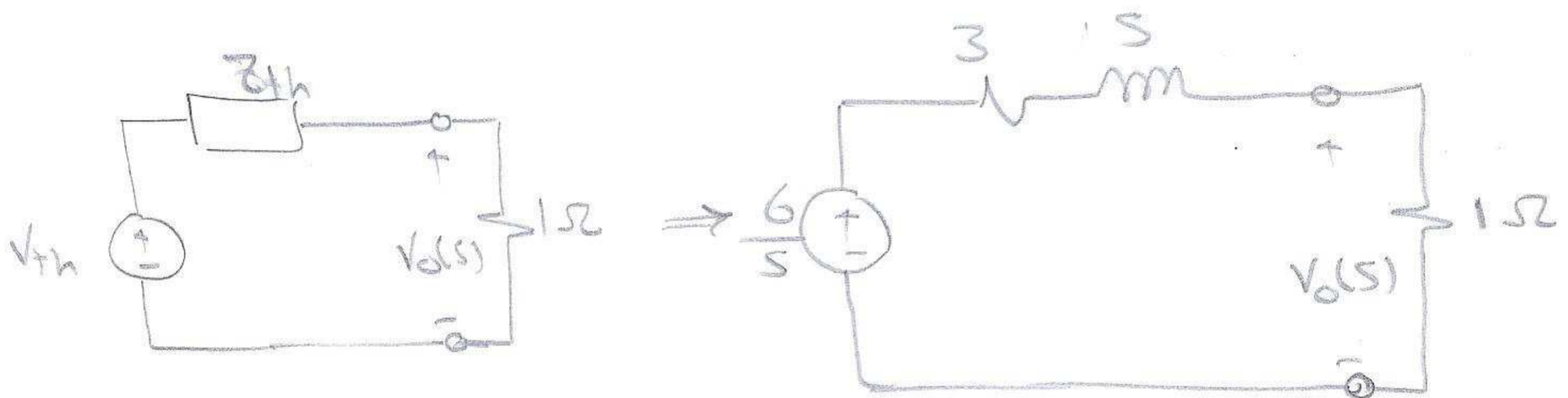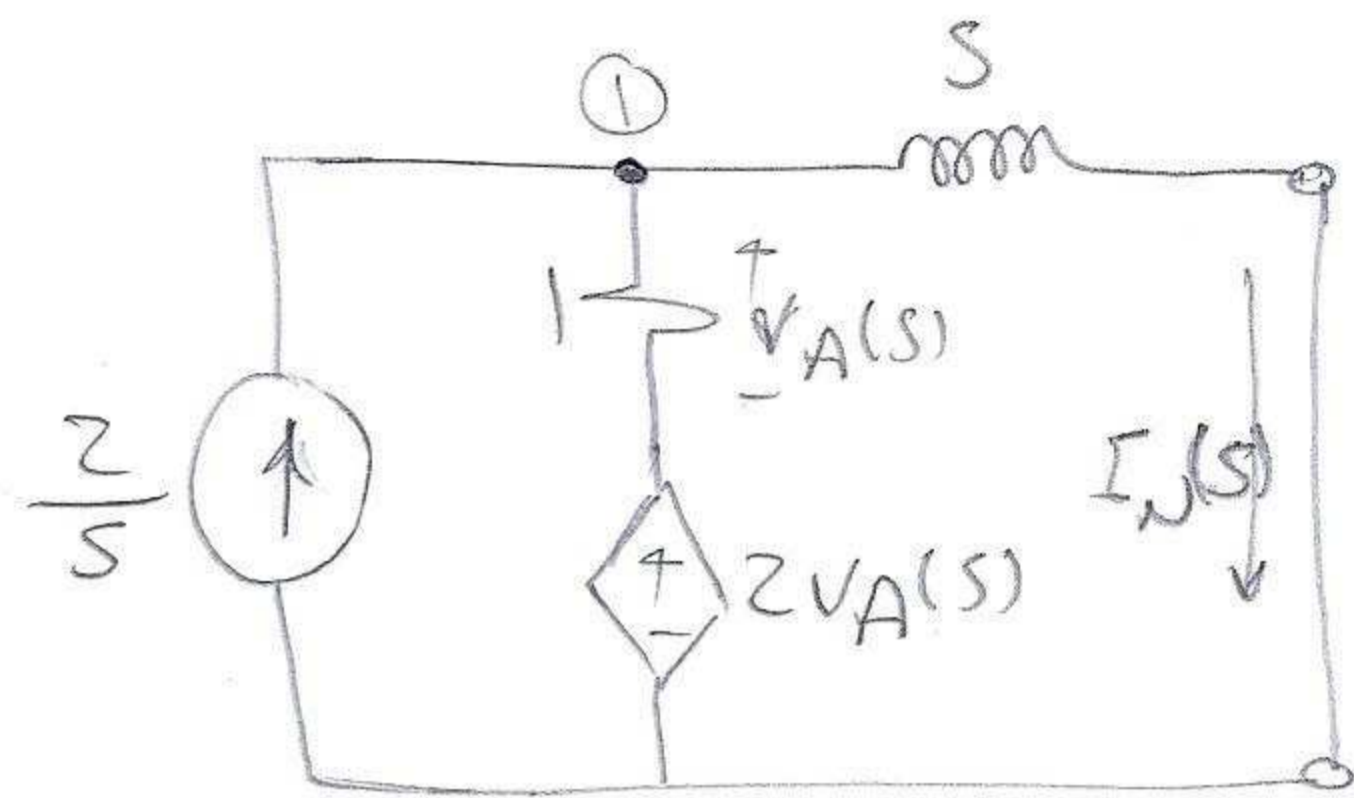

$$V_o(s) = \frac{6}{s} \times \frac{1}{s+4} = \frac{6}{s(s+4)}$$

$$= \frac{1.5}{s} - \frac{1.5}{s+4}$$

$$\therefore v_o(t) = 1.5 (1 - e^{-4t}) u(t) \text{ volts}$$





$v_o(t)$	$1.5(1 - e^{-4t})u(t)$ volt
----------	-----------------------------


Table 6




Question[7]: **Answer of Question 9**

Using the Laplace Transform Technique, derive an expression for the current $i(t), t > 0$, shown in figure, hence, calculate its initial and steady state values. Verify your results using the Initial and Final Value Theorems.

Insert your results in Table 7.

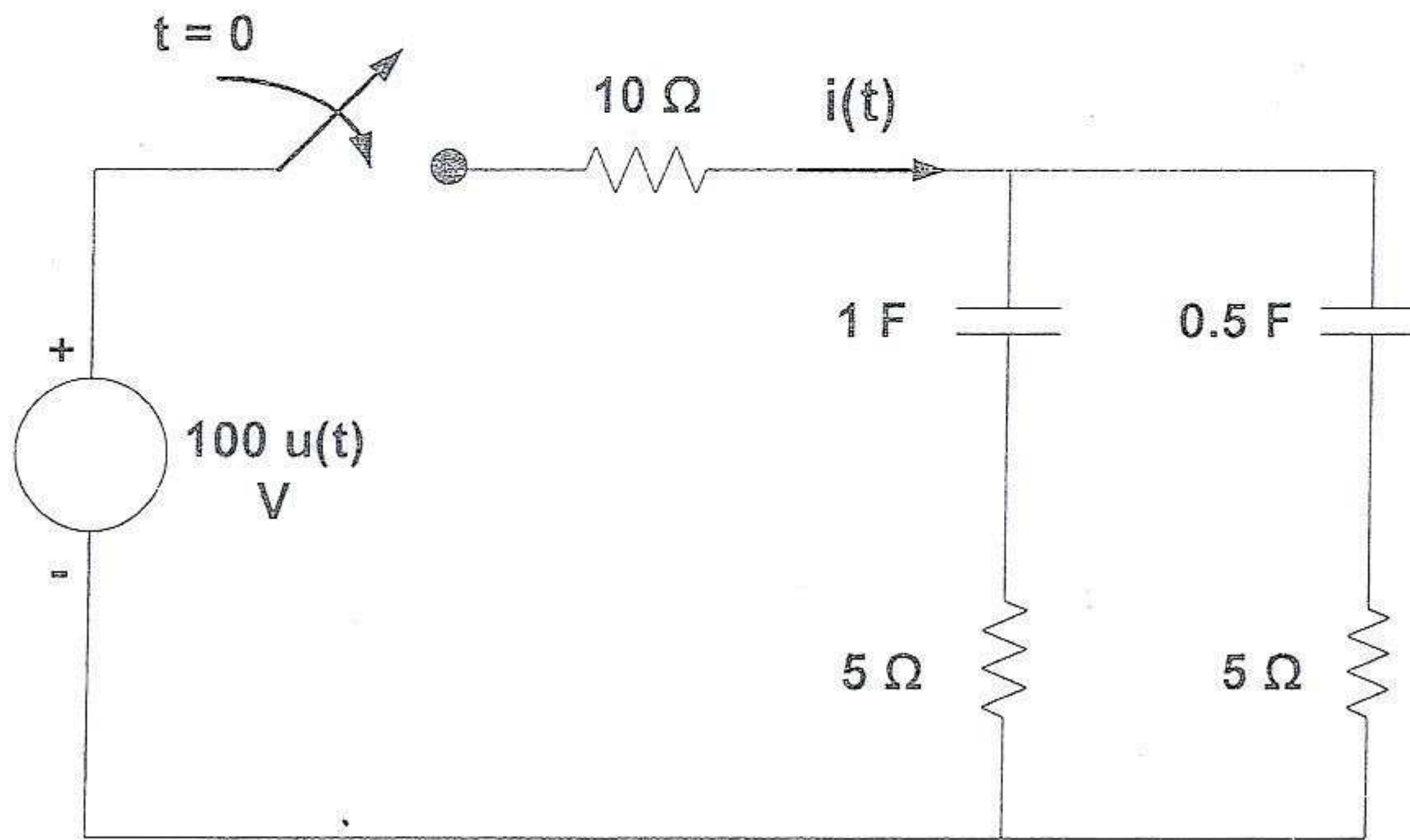

⇒ no - initial conditions

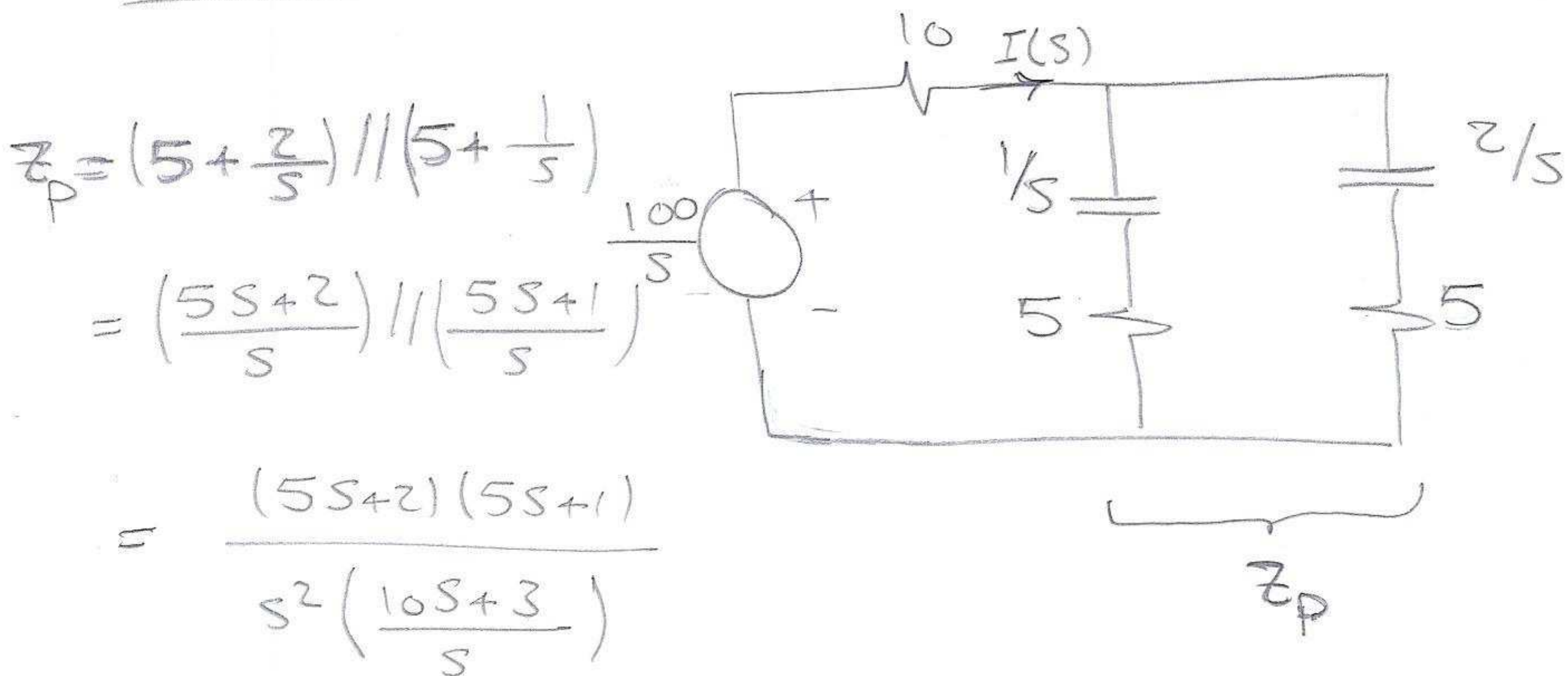

$$Z_p = (5 + \frac{2}{s}) \parallel (5 + \frac{1}{s})$$

$$= (\frac{5s+2}{s}) \parallel (\frac{5s+1}{s})$$

$$= \frac{(5s+2)(5s+1)}{s^2 (\frac{10s+3}{s})}$$

$$Z_p = \frac{(5s+2)(5s+1)}{s(10s+3)}$$



$$Z = 10 + Z_p$$

$$I(s) = \frac{\frac{100}{s}}{10 + Z_p} = \frac{\frac{100}{s}}{10 + \frac{(5s+2)(5s+1)}{s(10s+3)}}$$

$$\therefore I(s) = \frac{100(10s+3)}{10s(10s+3) + (5s+2)(5s+1)}$$

$$= \frac{100(10s+3)}{125s^2 + 45s + 2} = \frac{0.8(10s+3)}{s^2 + 0.36s + 0.016}$$

$$= \frac{0.8(10s+3)}{(s+0.052)(s+0.308)} = \frac{7.75}{s+0.052} + \frac{0.25}{s+0.308}$$

$$\therefore i(t) = (7.75 e^{-0.052t} + 0.25 e^{-0.308t}) u(t)$$

$$i(0) = 8 \text{ Amp}$$

$$i(\infty) = 0$$

$$i(0) = \lim_{s \rightarrow \infty} \frac{0.8(10s^2 + 3s)}{s^2 + 0.36s + 0.016} = 8 \text{ Amp}$$

$$i(\infty) = \lim_{s \rightarrow 0} \frac{0.8(10s^2 + 3s)}{s^2 + 0.36s + 0.016} = 0$$





$i(t)$	$(7.75 e^{-0.052t} + 0.25 e^{-0.308t})u(t)$
<i>Initial Value</i>	8 Amp
<i>Final Value</i>	0



Table 7



Question[8]: **Answer of Question 10**

When the switch in the circuit shown in figure is closed, the condenser was charged such that $v_c(0)=20$ volts and the current in the coil was $i_L(0)=2A$. Derive expressions for the instantaneous currents $i_1(t)$, $i_2(t)$ and $i_3(t)$ for $t > 0$.

Insert your results in Table 8.

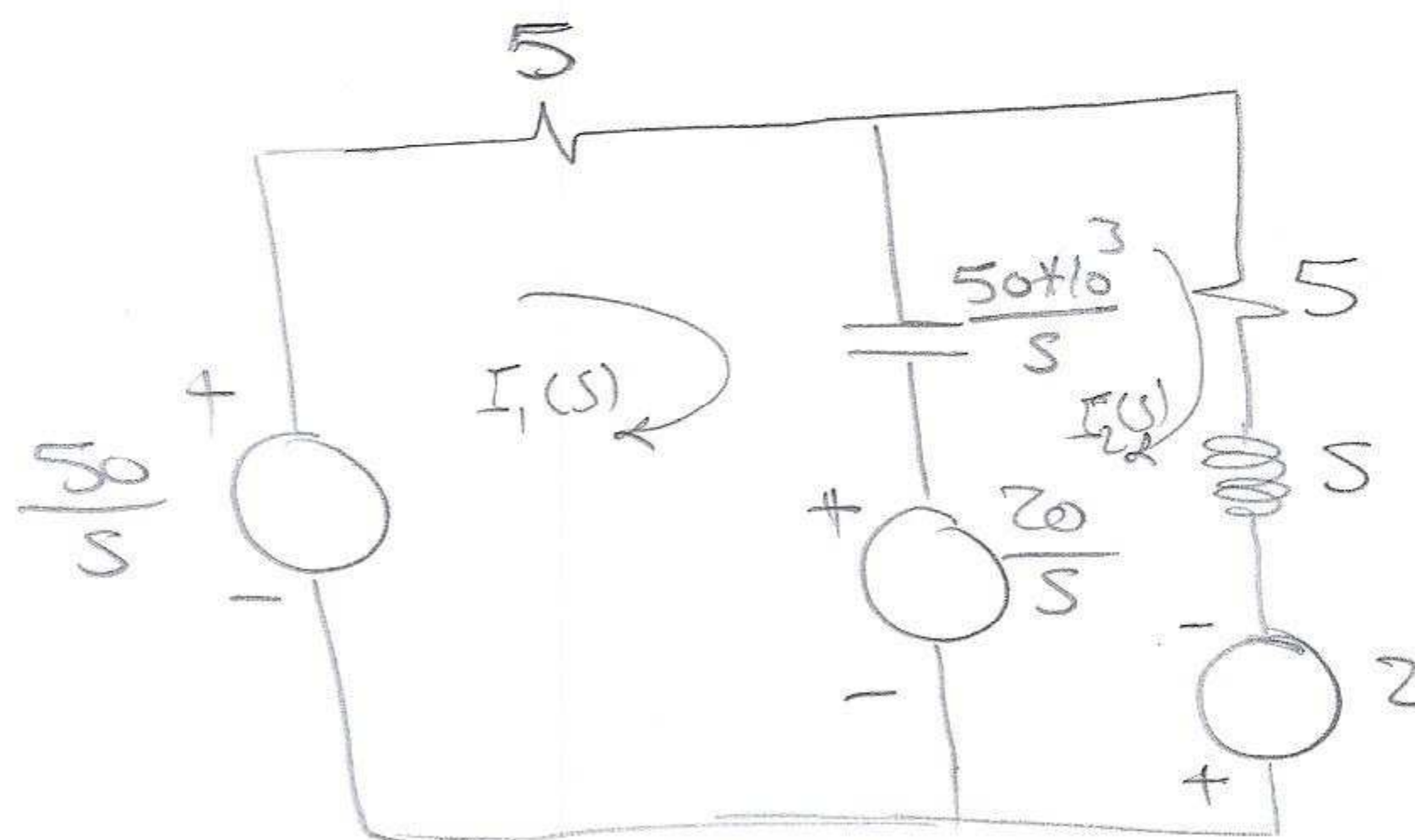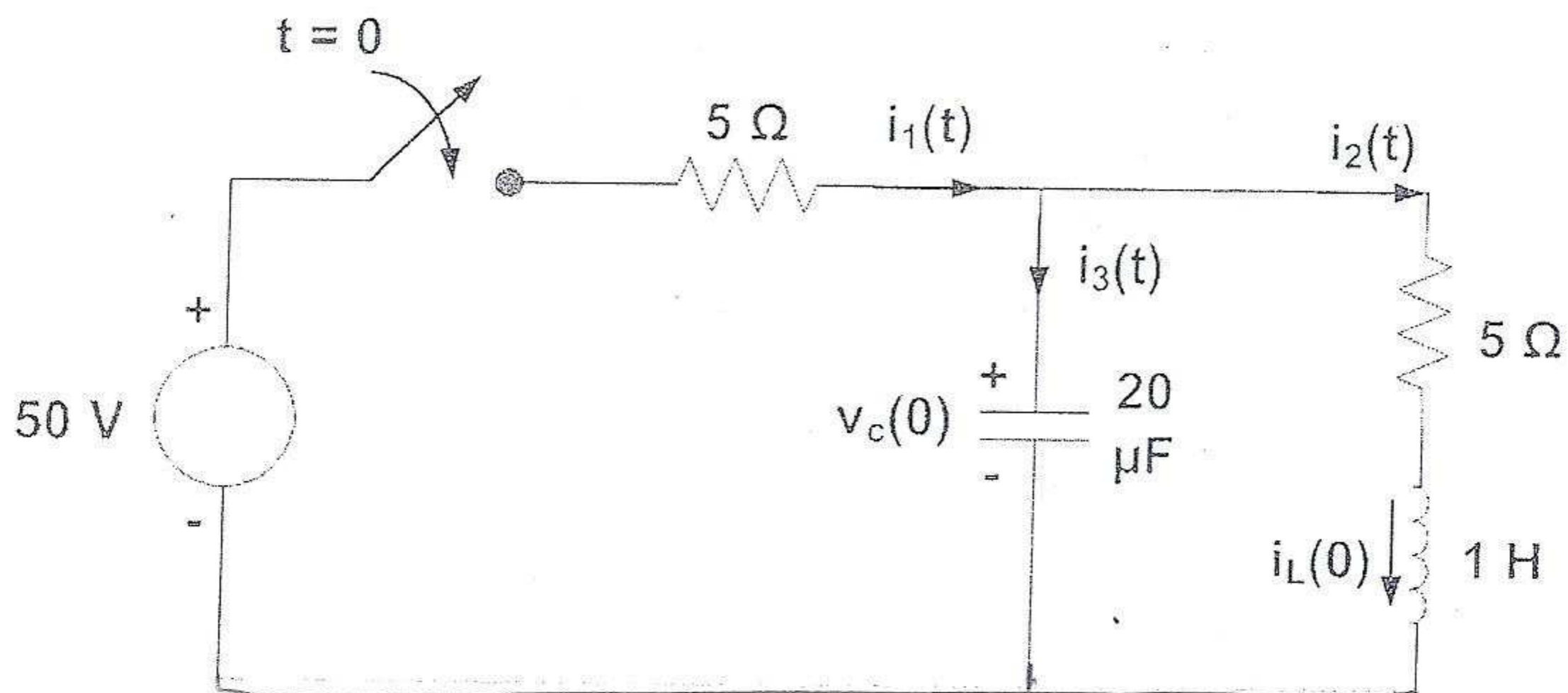

$$\begin{bmatrix} 5 + \frac{5 \times 10^4}{s} & -\frac{5 \times 10^4}{s} \\ -\frac{5 \times 10^4}{s} & 5 + \frac{5 \times 10^4}{s} + s \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} \frac{30}{s} \\ \frac{2(s+10)}{s} \end{bmatrix}$$



$$\Delta = \left(5 + \frac{5 \times 10^4}{s}\right)^2 + 5s + 5 \times 10^4 - \left(\frac{5 \times 10^4}{s}\right)^2$$

$$= 25 + \frac{5 \times 10^5}{s} + 5s + 5 \times 10^4$$

$$= \frac{5(s^2 + 10005s + 10^5)}{s}$$

$$\Delta_1 = \begin{vmatrix} \frac{30}{s} & -\frac{5 \times 10^4}{s} \\ \frac{2(s+10)}{s} & 5 + s + \frac{5 \times 10^4}{s} \end{vmatrix}$$

$$= \frac{150}{s} + 30 + \frac{15 \times 10^5}{s^2} + \frac{10^5(s+10)}{s^2}$$

$$= \frac{5(6s^2 + 20030s + 5 \times 10^5)}{s^2}$$

$$\Delta_2 = \begin{vmatrix} 5 + \frac{5 \times 10^4}{s} & \frac{30}{s} \\ -\frac{5 \times 10^4}{s} & \frac{2(s+10)}{s} \end{vmatrix} = \frac{10(s+10)}{s} + \frac{10^5(s+10)}{s^2} + \frac{15 \times 10^5}{s^2}$$

$$= \frac{10s^2 + 100s + 10^5s + 25 \times 10^5}{s^2}$$

$$= \frac{5(2s^2 + 20020 + 5 \times 10^5)}{s^2}$$



$$\begin{aligned} I_1(s) &= \frac{\Delta_1}{\Delta} = \frac{6s^2 + 20030s + 5 \times 10^5}{s(s^2 + 10025s + 10^5)} \\ &= \frac{6s^2 + 20030s + 5 \times 10^5}{s(s^2 + 10005s + 10^5)} = \frac{6s^2 + 20030s + 5 \times 10^5}{s(s+10)(s+9995)} \\ &= \frac{5}{s} - \frac{3}{s+10} + \frac{4}{s+9995} \end{aligned}$$

$$\therefore i_1(t) = \left(5 - 3e^{-10t} + 4e^{-9995t} \right) u(t)$$

$$\begin{aligned} I_2(s) &= \frac{\Delta_2}{\Delta} = \frac{2s^2 + 20020s + 5 \times 10^5}{s(s+10)(s+9995)} \\ &= \frac{5}{s} - \frac{3}{(s+10)} + \frac{2 \times 10^{-3}}{(s+9995)} \end{aligned}$$

$$\therefore i_2(t) = \left(5 - 3e^{-10t} + 2 \times 10^{-3} e^{-9995t} \right) u(t)$$

$$I_3(s) = I_1(s) - I_2(s) = \frac{3.998}{s+9995}$$

$$\therefore i_3(t) = \left(3.998 e^{-9995t} \right) u(t)$$





$i_1(t)$	$(5 - 3e^{-10t} + 4e^{-9995t})u(t)$
$i_2(t)$	$(5 - 3e^{-10t} + 2 \times 10^{-3} e^{-9995t})u(t)$
$i_3(t)$	$(3.998 e^{-9995t})u(t)$


Table 8



Question[9]: Answer of Question 12

In the circuit shown in figure, the capacitor is initially charged such that $v_c(0) = 50$ volts. Calculate $v_c(t)$, $t > 0$. Derive an expression for the capacitor current in the time domain $i_c(t)$, $t > 1$ m.sec. and calculate its steady state value $i_c(\infty)$. Verify your result using the final value theorem.


Insert your results in Table 9.

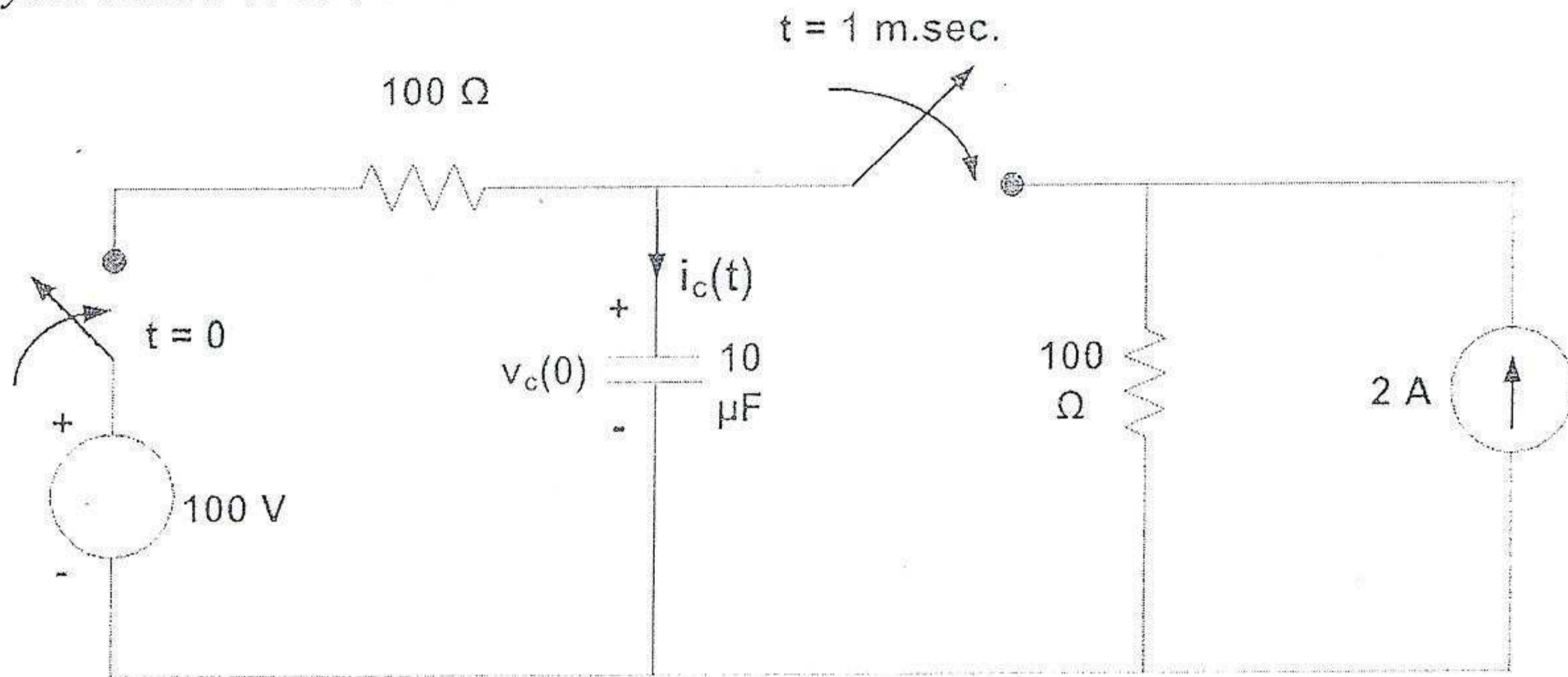

* at $0 < t < 1$ msec

$$I(s) = \frac{\frac{100}{s} - \frac{50}{s}}{100 + \frac{10^5}{s}}$$
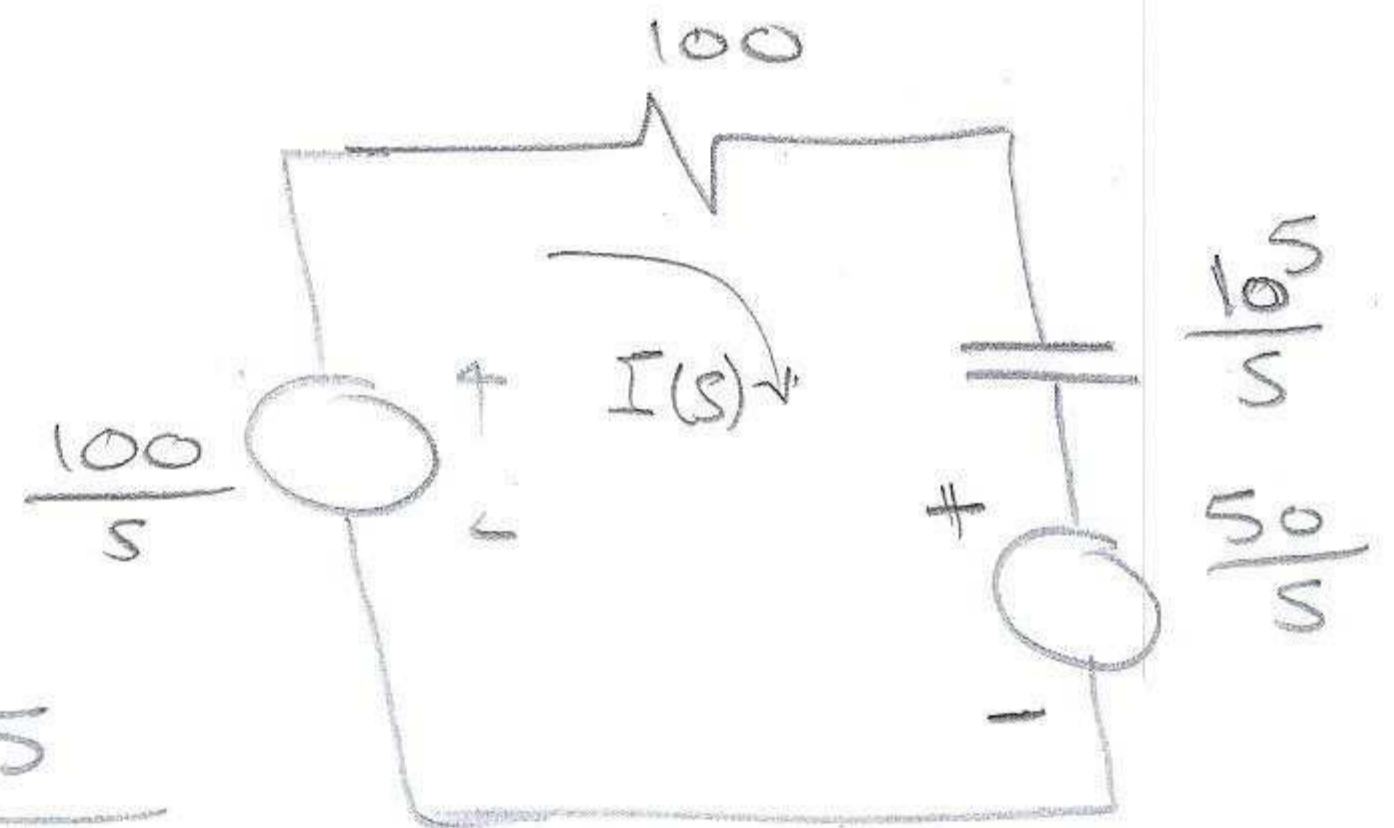
$$= \frac{50}{100s + 10^5} = \frac{0.5}{s + 1000}$$



$$\therefore I_c(s) = \frac{0.5}{s + 1000}$$



$$\therefore i_c(t) = 0.5 e^{-1000t} \{ u(t) - u(t - 1 \text{ msec}) \}$$



$$\begin{aligned}
 V_C(s) &= \frac{10^5}{s} * I_C(s) + \frac{50}{s} \\
 &= \frac{5 * 10^4}{s(s+1000)} + \frac{50}{s} \\
 &= \frac{100}{s} - \frac{50}{s+1000}
 \end{aligned}$$

$$\therefore V_C(t) = 50(2 - e^{-1000t}) \{ u(t) - u(t-1\text{msec}) \}$$
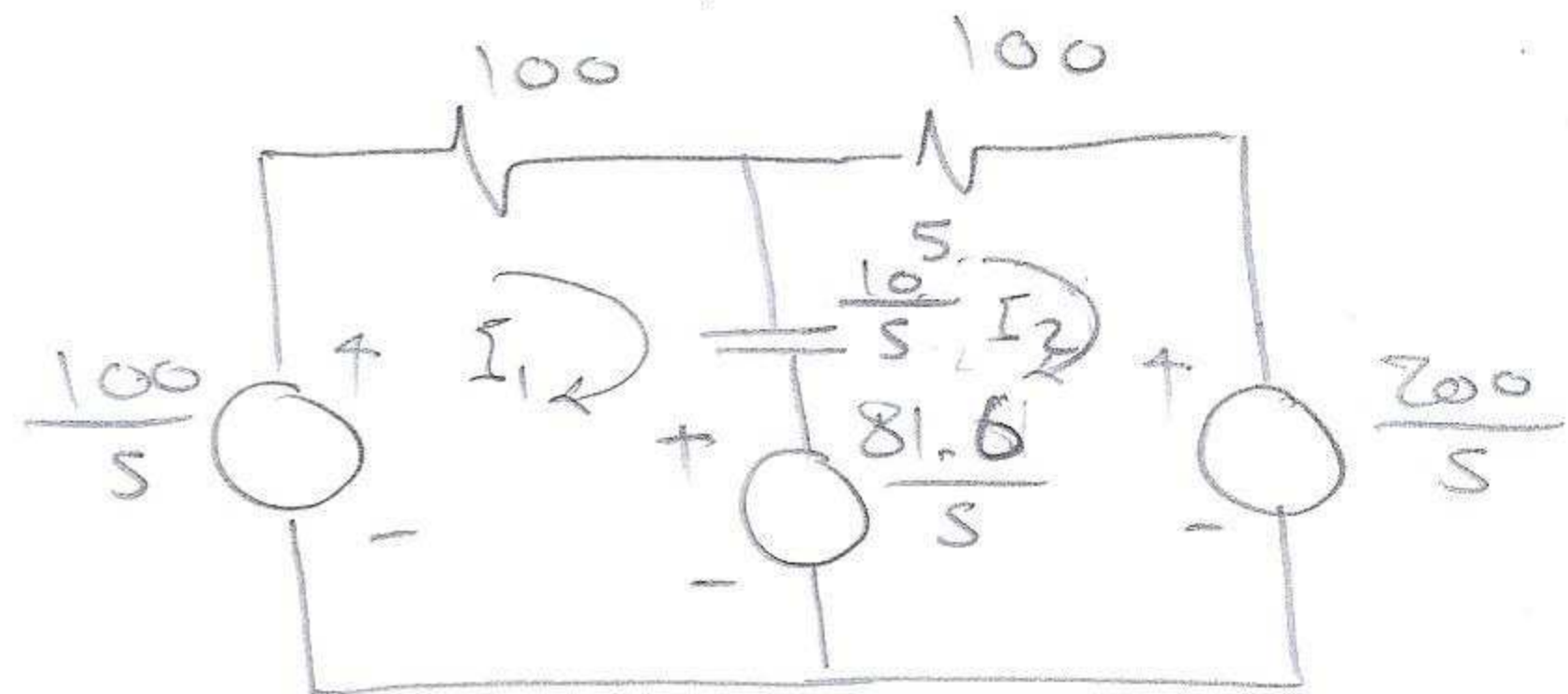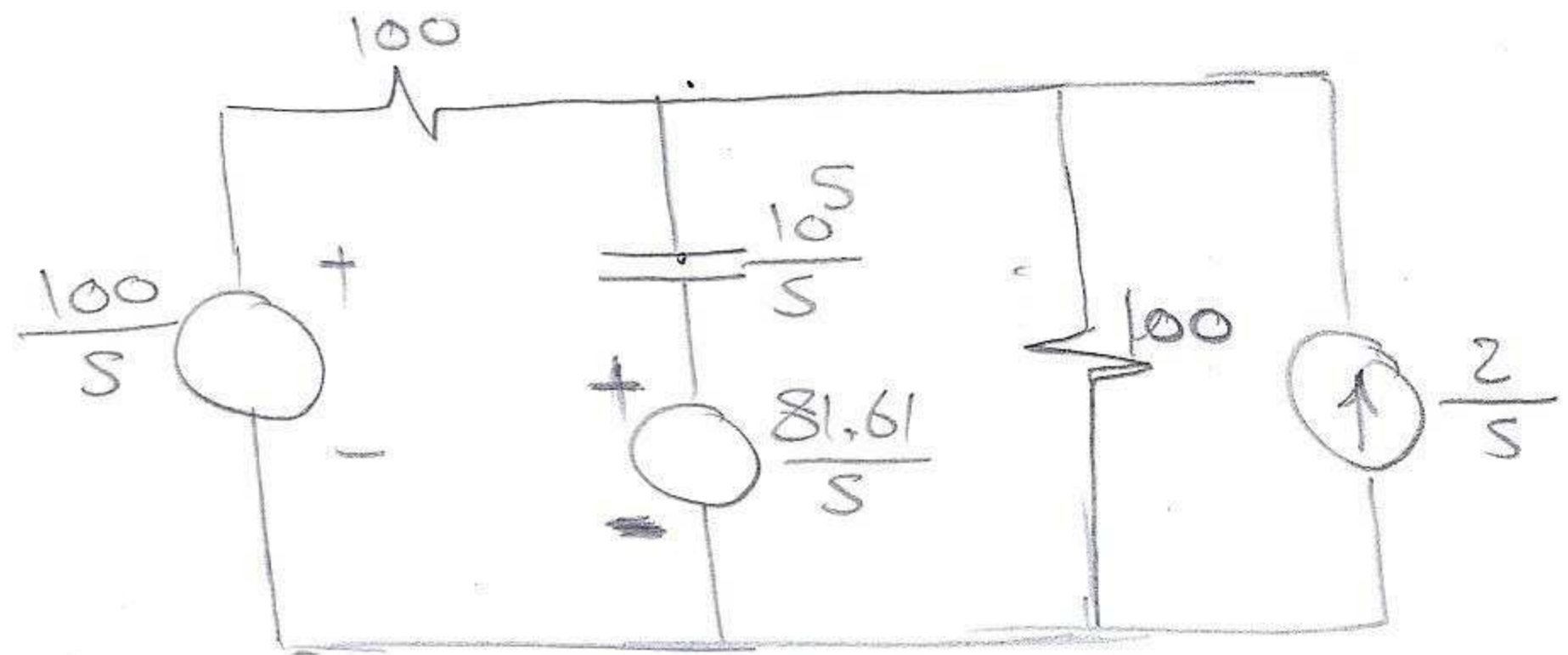
$$V_C(1\text{msec}) = 50(2 - e^{-1}) = 81.6 \text{ volts.}$$



$$\begin{bmatrix} 100 + \frac{10^5}{s} & -\frac{10^5}{s} \\ -\frac{10^5}{s} & 100 + \frac{10^5}{s} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{18.4}{s} \\ -\frac{118.4}{s} \end{bmatrix}$$



$$\Delta = \left(100 + \frac{10^5}{s}\right)^2 - \left(\frac{10^5}{s}\right)^2 = 10^4 + \frac{2 \times 10^7}{s} = \frac{10^4 (s + 2000)}{s}$$

$$\Delta_1 = \begin{vmatrix} \frac{18.4}{s} & -\frac{10^5}{s} \\ -\frac{118.4}{s} & 100 + \frac{10^5}{s} \end{vmatrix} = \frac{1840}{s} + \frac{18.4 \times 10^5}{s^2} - \frac{118.4 \times 10^5}{s^2}$$

$$= \frac{1840s - 100 \times 10^5}{s^2}$$

$$\Delta_2 = \begin{vmatrix} 100 + \frac{10^5}{s} & \frac{18.4}{s} \\ -\frac{10^5}{s} & -\frac{118.4}{s} \end{vmatrix} = -\frac{11840}{s} - \frac{118.4 \times 10^5}{s^2} + \frac{18.4 \times 10^5}{s^2}$$

$$= \frac{-11840s - 100 \times 10^5}{s^2}$$

$$I_1(s) = \frac{\Delta_1}{\Delta} = \frac{1840s - 100 \times 10^5}{s^2} \times \frac{s}{10^4 (s + 2000)}$$

$$= \frac{0.184s - 1000}{s(s + 2000)} = \frac{-1/2}{s} + \frac{0.684}{s + 2000}$$

$$I_2(s) = \frac{\Delta_2}{\Delta} = \frac{-11840s - 100 \times 10^5}{s^2} \times \frac{s}{10^4 (s + 2000)}$$

$$= \frac{-1.184s - 1000}{s(s + 2000)} = \frac{-1/2}{s} - \frac{0.684}{s + 2000}$$

$$I_c(s) = I_1(s) - I_2(s) = \frac{1.368}{s + 2000}$$

$$\therefore i_c(t) = (1.368 e^{-2000t}) u(t)$$



$$i_c(t-1\text{msec}) = (1.368 e^{-2000(t-1\text{msec})}) u(t-1\text{msec})$$

$$V_c(s) = \frac{1.368 \times 10^5}{s(s+2000)} + \frac{81.61}{s}$$

$$= \frac{150}{s} - \frac{68.4}{s+2000}$$

$$\therefore V_c(t) = (150 - 68.4 e^{-2000t}) u(t)$$

$$V_c(t-1\text{msec}) = (150 - 68.4 e^{-2000(t-1\text{msec})}) u(t-1\text{msec})$$

$$i_c(\infty) = 0$$

$$i_c(\infty) = \lim_{s \rightarrow 0} \frac{1.368s}{s+2000} = 0$$

$v_c(t), t > 0$	$50(2 - e^{-1000t}) \{u(t) - u(t-1\text{msec})\} + (150 - 68.4 e^{-2000(t-1\text{msec})}) u(t-1\text{msec})$
$i_c(t), t > 1\text{msec.}$	$(1.368 e^{-2000(t-1\text{msec})}) u(t-1\text{msec})$
$i_c(\infty)$	0

Table 9




Question [10]: **Answer of Question 13**

The circuit shown in figure is fed from a source $v(t)$ given by :


$$v(t) = 100 e^{-100t} \text{ Volts}$$

Calculate $i(t)$, $t > 0$.


Insert your result in Table 10.

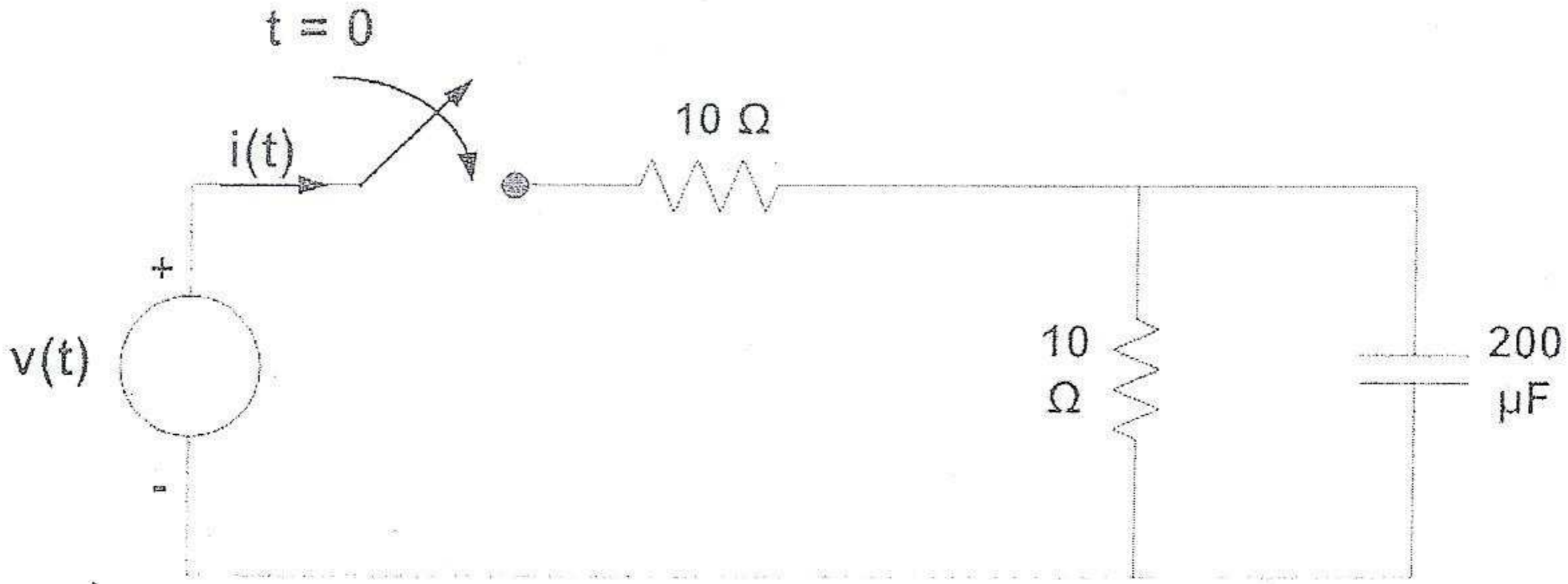

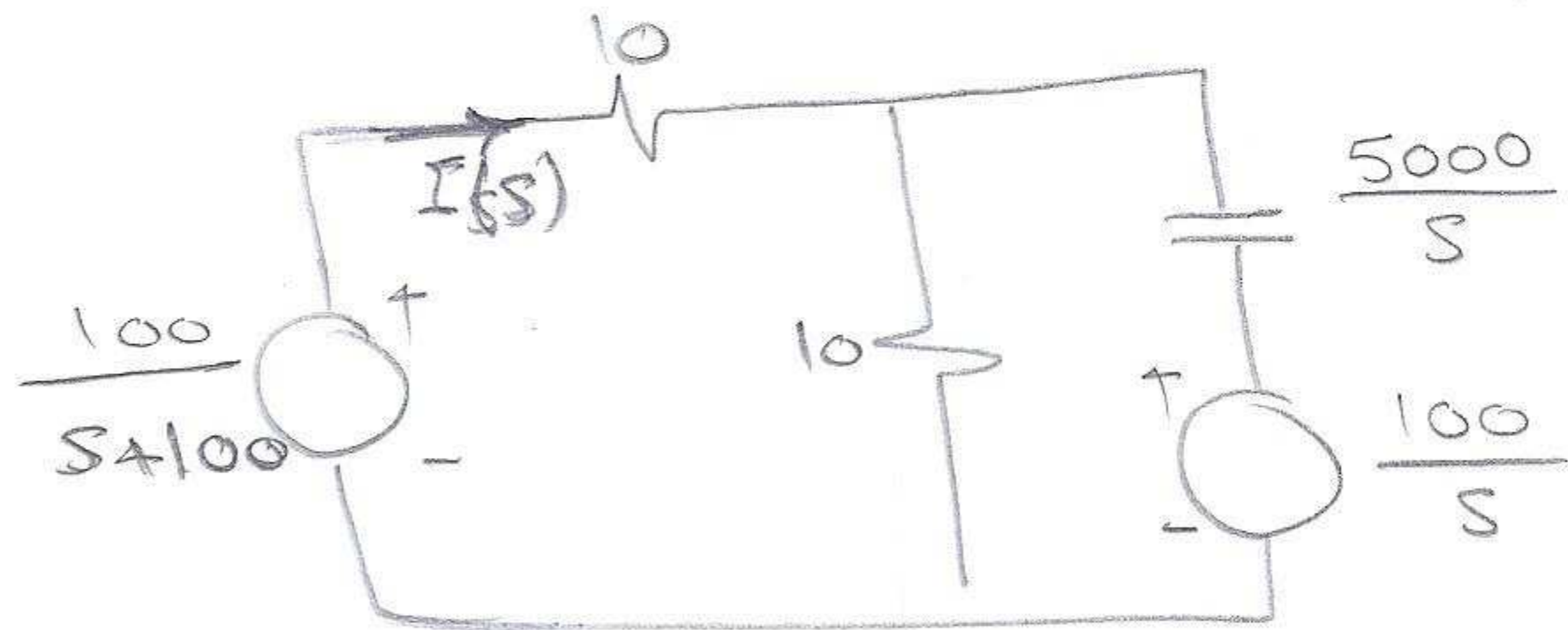\Rightarrow at $t=0$ $v(t) = 100 e^0 = 100 \text{ Volts.}$
 \Rightarrow $v_c(0) = 100 \text{ Volts}$



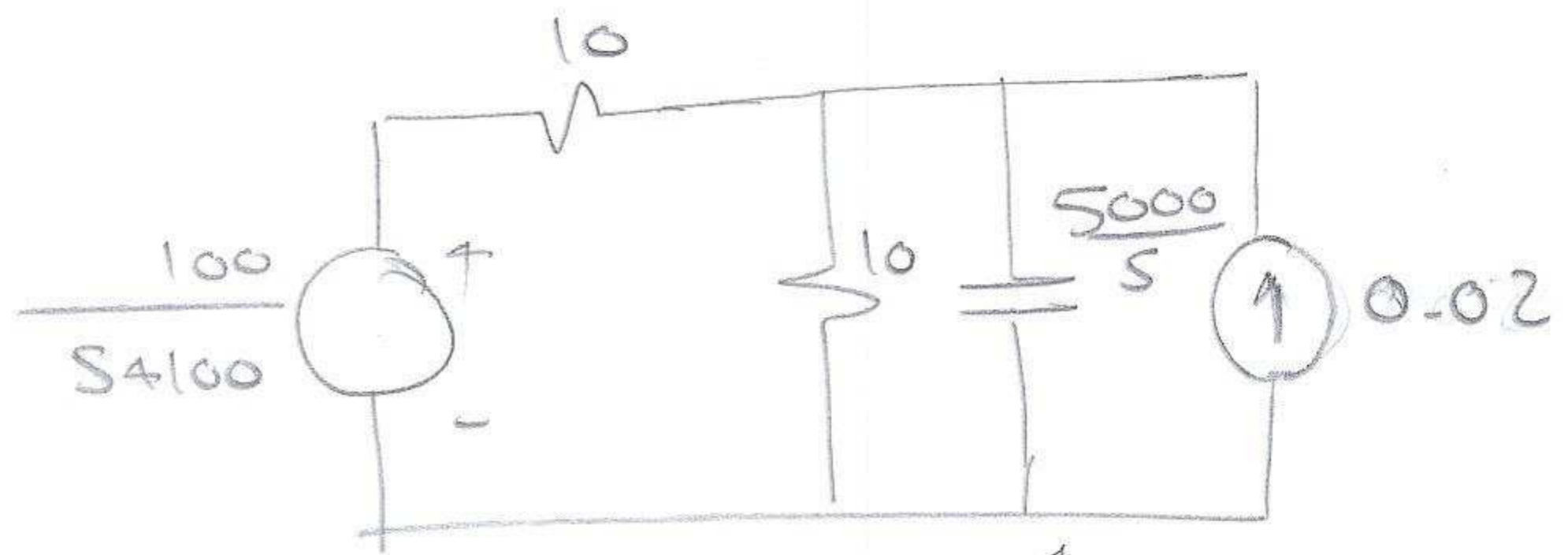
$$\begin{aligned}
 Z_p &= \frac{\frac{5 \times 10^4}{s}}{10 + \frac{5000}{s}} \\
 &= \frac{5 \times 10^4}{10s + 5000} \\
 &= \frac{5000}{s + 500}
 \end{aligned}$$



Z_p


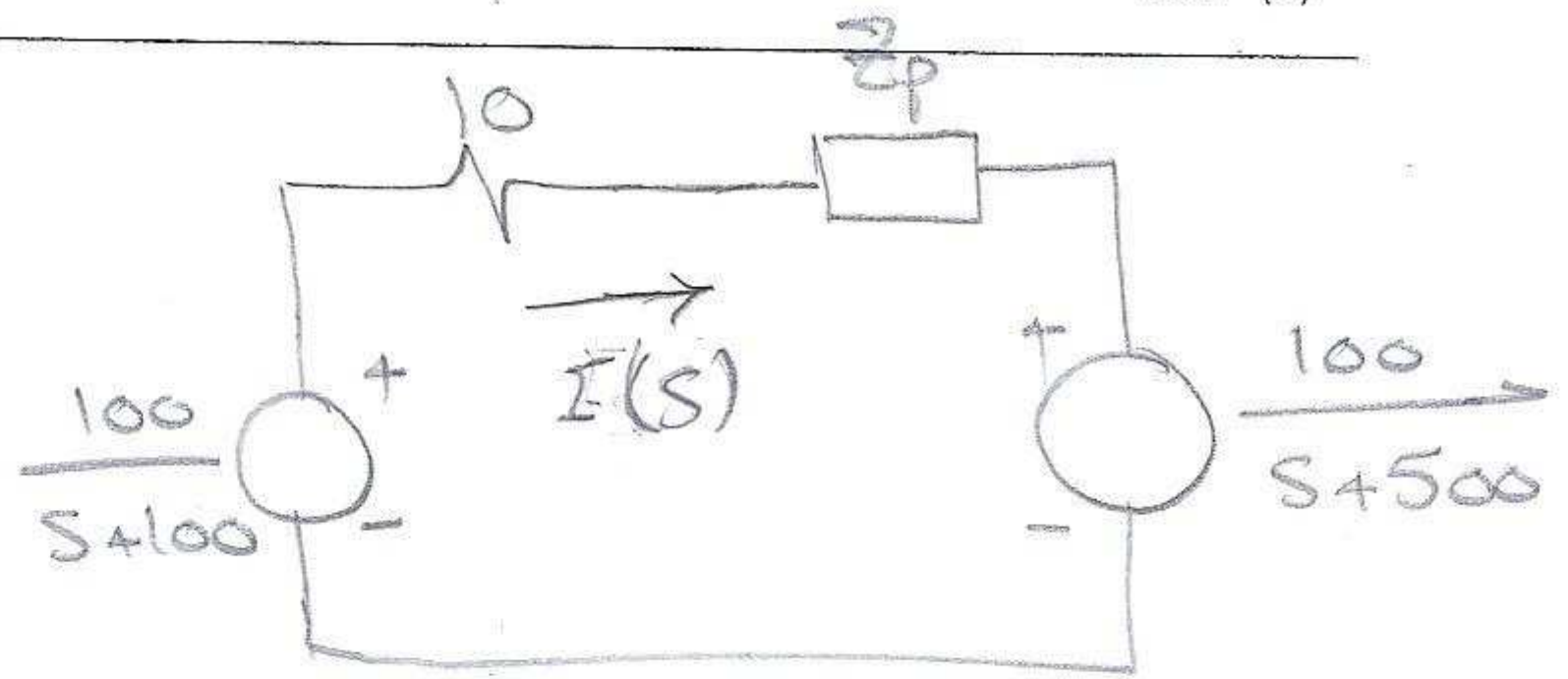
$$I(s) = \frac{\frac{100}{s+100} - \frac{100}{s+500}}{10 + \frac{5000}{s+500}}$$



$$= \frac{10(s+500) - 10(s+100)}{(s+100)(s+500) + 5000(s+100)}$$

$$= \frac{4000}{(s+100)(s+500) + 5000(s+100)}$$

$$= \frac{4000}{s^2 + 1100s + 10^5} = \frac{4000}{(s+100)(s+1000)}$$

$$= \frac{40/g}{s+100} - \frac{40/g}{s+1000}$$

$$\therefore i(t) = \frac{40}{g} (e^{-100t} - e^{-1000t}) u(t)$$





$i(t), t > 0$	$\frac{40}{9} (e^{-100t} - e^{-1000t}) u(t)$
---------------	--


Table (10)





Question[11]: Answer of Question 14

For the circuit shown in figure, calculate the node potentials $v_1(t)$ and $v_2(t)$. Using the initial and final value theorems, calculate $v_1(0)$, $v_2(0)$, $v_1(\infty)$ and $v_2(\infty)$.

Insert your results in Table 11.

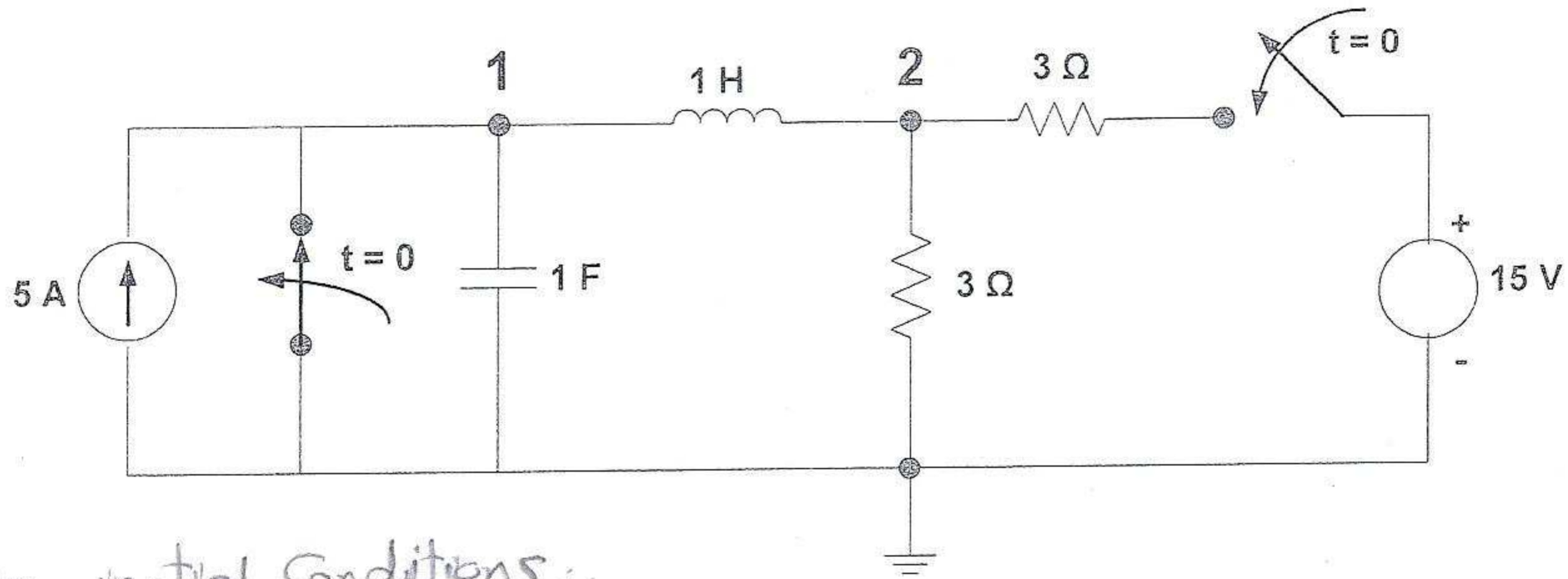

⇒ no-initial conditions.

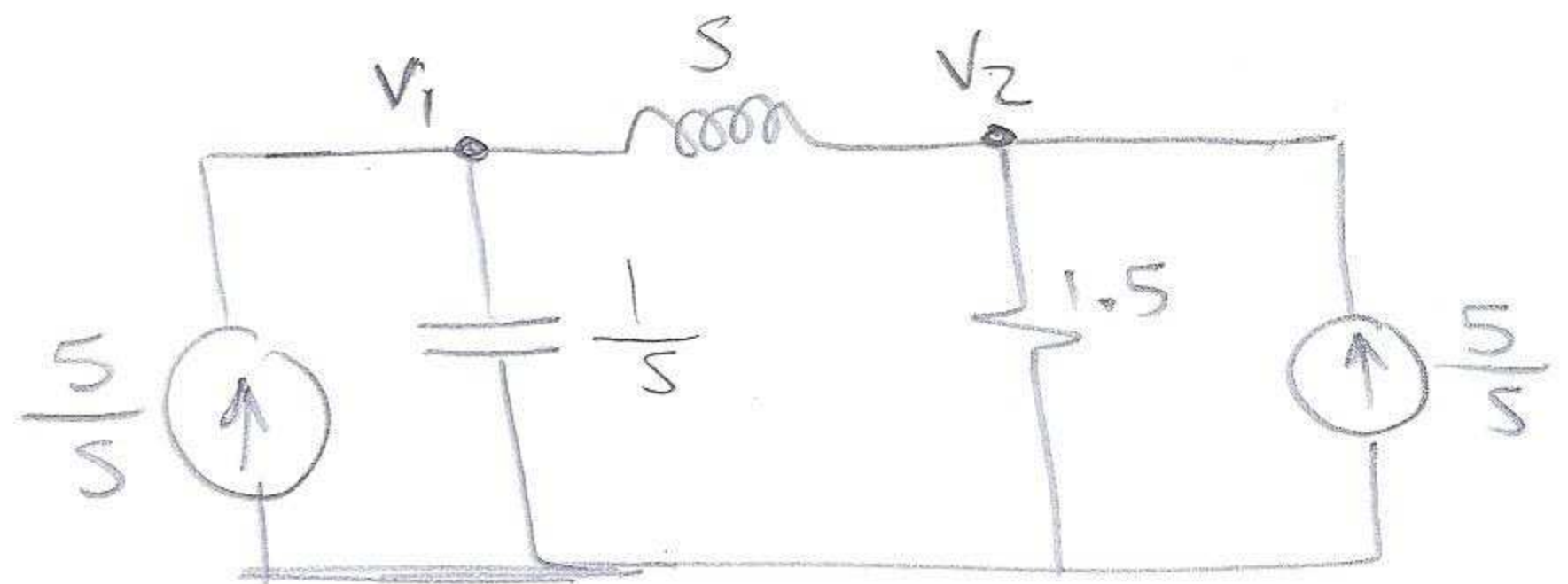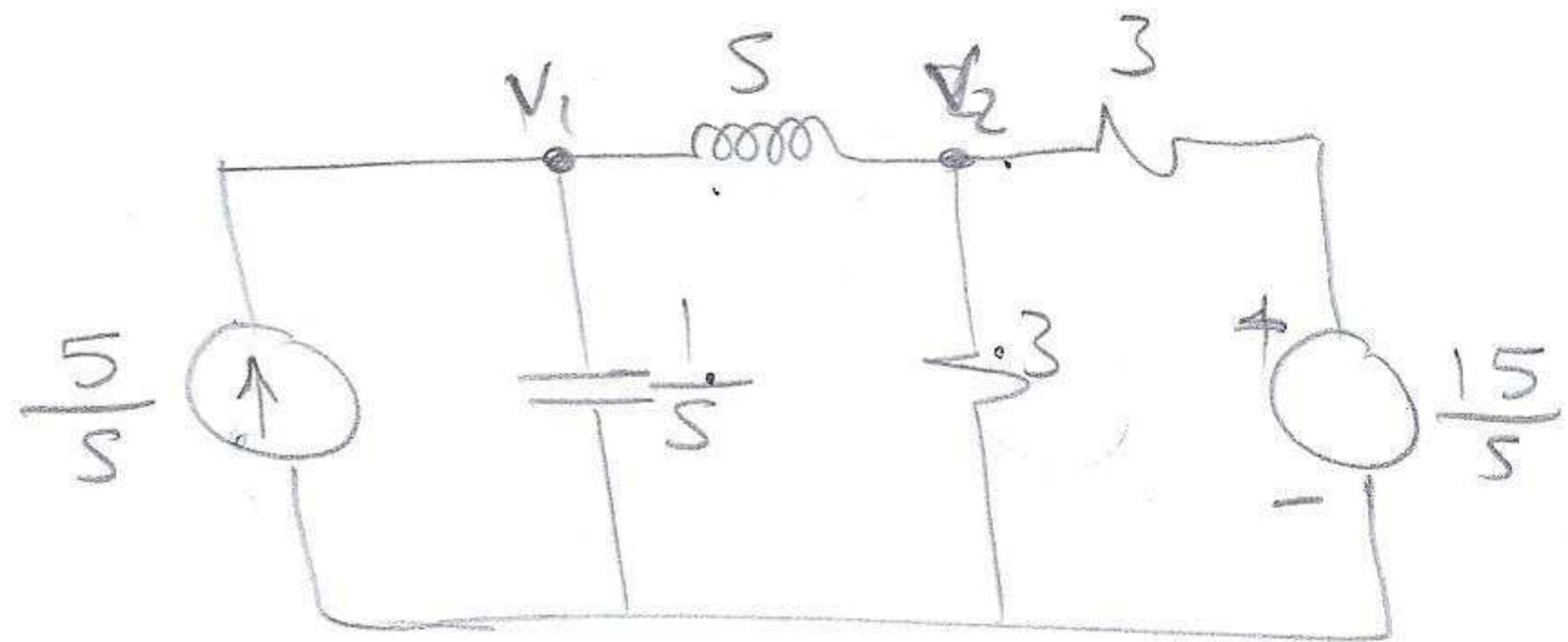

$$\begin{bmatrix} s + \frac{1}{s} & -\frac{1}{s} \\ -\frac{1}{s} & \frac{1}{s} + \frac{2}{3} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} \frac{5}{s} \\ \frac{5}{s} \end{bmatrix}$$



$$\begin{bmatrix} \frac{s^2+1}{s} & -\frac{1}{s} \\ -\frac{1}{s} & \frac{2s+3}{3s} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{5}{s} \\ \frac{5}{s} \end{bmatrix}$$

$$\Delta = \frac{(2s+3)(s^2+1)}{3s^2} - \frac{1}{s^2} = \frac{2s^3 + 3s^2 + 2s + 3 - 3}{3s^2}$$

$$\therefore \Delta = \frac{2s^2 + 3s + 2}{3s}$$

$$\Delta_1 = \begin{vmatrix} \frac{5}{s} & -\frac{1}{s} \\ \frac{5}{s} & \frac{2s+3}{3s} \end{vmatrix} = \frac{10s+15}{3s^2} + \frac{5}{s^2}$$

$$= \frac{10s+30}{3s^2} = \frac{10(s+3)}{3s^2}$$

$$\Delta_2 = \begin{vmatrix} \frac{s^2+1}{s} & \frac{5}{s} \\ -\frac{1}{s} & \frac{5}{s} \end{vmatrix} = \frac{5s^2+5+5}{s^2} = \frac{5(s^2+2)}{s^2}$$

$$V_1(s) = \frac{\Delta_1}{\Delta} = \frac{10(s+3)}{3s^2} \times \frac{3s}{2s^2+3s+2} = \frac{5(s+3)}{s(s^2+1.5s+1)}$$

$$= \frac{5(s+3)}{s(s + \frac{3}{4} - j\frac{\sqrt{7}}{4})(s + \frac{3}{4} + j\frac{\sqrt{7}}{4})}$$

$$= \frac{15}{s} + \frac{k_1}{s + \frac{3}{4} - j\frac{\sqrt{7}}{4}} + \frac{k_1^*}{s + \frac{3}{4} + j\frac{\sqrt{7}}{4}}$$



$$k_1 = 8.86 \angle 147.8^\circ$$

$$\therefore u_1(t) = 15 + 17.72 e^{-\frac{3}{4}t} \cos\left(\frac{\sqrt{7}}{4}t + 147.8^\circ\right) \text{ Volts.}$$

$$V_2(s) = \frac{5(s^2+2)}{s^2} * \frac{38}{2s^2+3s+2}$$

$$= \frac{7.5(s^2+2)}{s(s+\frac{3}{4}-j\frac{\sqrt{7}}{4})(s+\frac{3}{4}+j\frac{\sqrt{7}}{4})}$$

$$= \frac{15}{s} + \frac{k_2}{s+\frac{3}{4}-j\frac{\sqrt{7}}{4}} + \frac{k_2^*}{s+\frac{3}{4}+j\frac{\sqrt{7}}{4}}$$

$$k_2 = 13.3 \angle 106.38^\circ$$

$$\therefore u_2(t) = 15 + 26.6 e^{-\frac{3}{4}t} \cos\left(\frac{\sqrt{7}}{4}t + 106.38^\circ\right)$$

$$u_1(0) = \lim_{s \rightarrow \infty} \frac{5(s+3)}{s^2 + \frac{3}{2}s + 1} = 0$$

$$u_1(\infty) = \lim_{s \rightarrow 0} \frac{5(s+3)}{s^2 + \frac{3}{2}s + 1} = 15 \text{ Volts.}$$

$$u_2(0) = \lim_{s \rightarrow \infty} \frac{7.5(s^2+2)}{s^2 + \frac{3}{2}s + 1} = 7.5 \text{ Volts.}$$

$$u_2(\infty) = \lim_{s \rightarrow \infty} \frac{7.5(s^2+2)}{s^2 + \frac{3}{2}s + 1} = 15 \text{ Volts.}$$



$v_1(t)$	$15 + 17.72 e^{-\frac{3}{4}t} \cos\left(\frac{\sqrt{7}}{4}t + 147.8^\circ\right)$
$v_2(t)$	$15 + 26.6 e^{-\frac{3}{4}t} \cos\left(\frac{\sqrt{7}}{4}t + 106.38^\circ\right)$
$v_1(0)$	0
$v_2(0)$	7.5 Volts.
$v_1(\infty)$	15 Volts.
$v_2(\infty)$	15 Volts.

Table 11



Question[12]: Answer of Question 17

Find the Z-parameters of the two-port network shown in Fig.a . If the same network is used in Fig.b, calculate $i_2(t)$ for $t > 0$.

Insert your results in Table 12 .

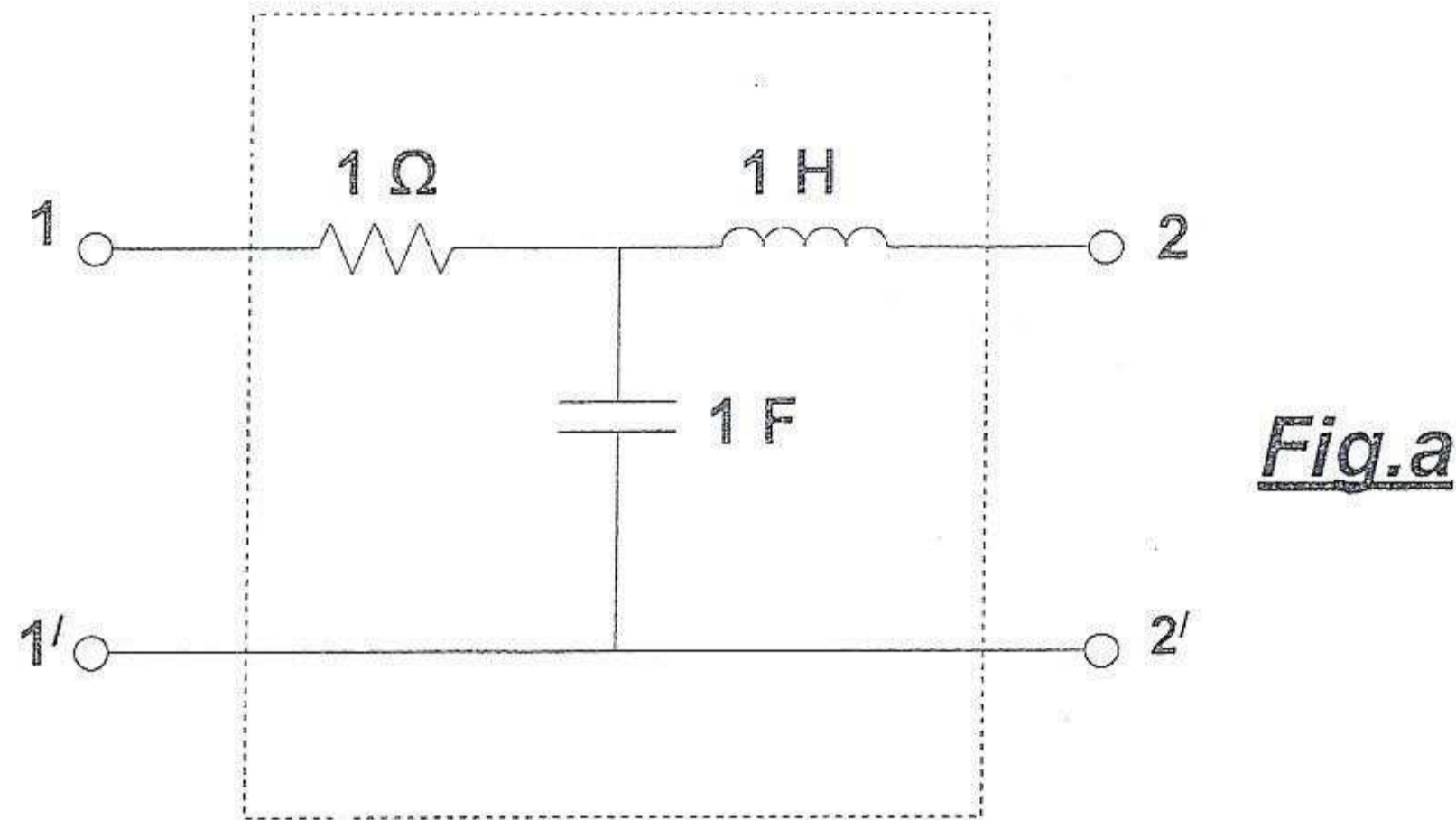


Fig.a


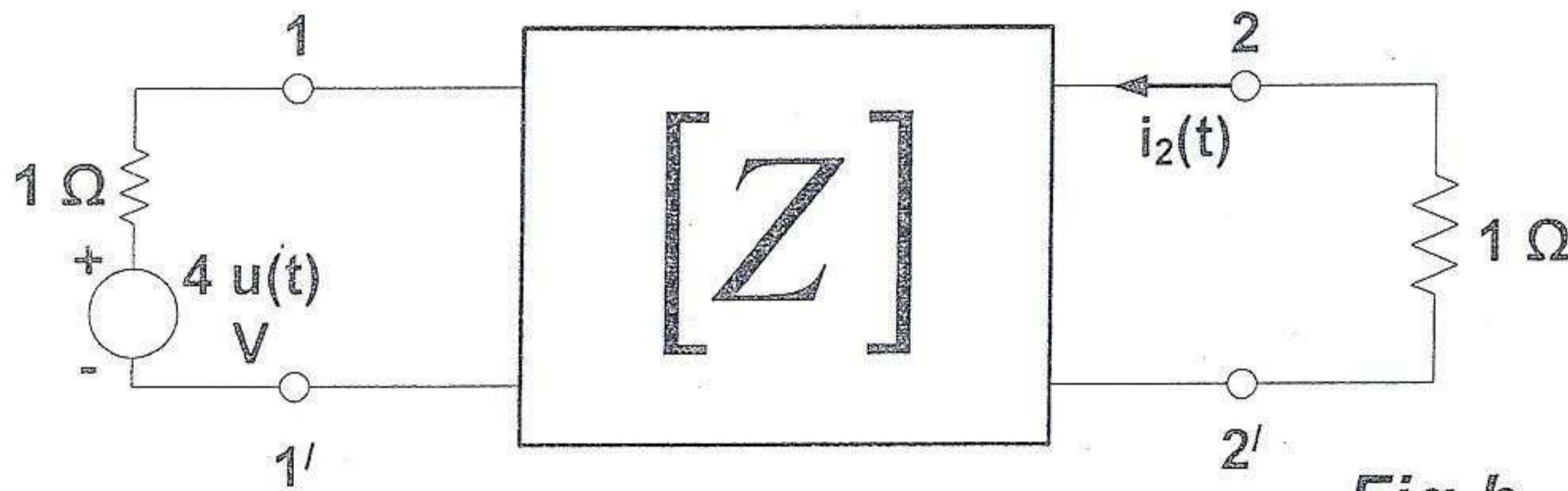


Fig.b

in Fig.a

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

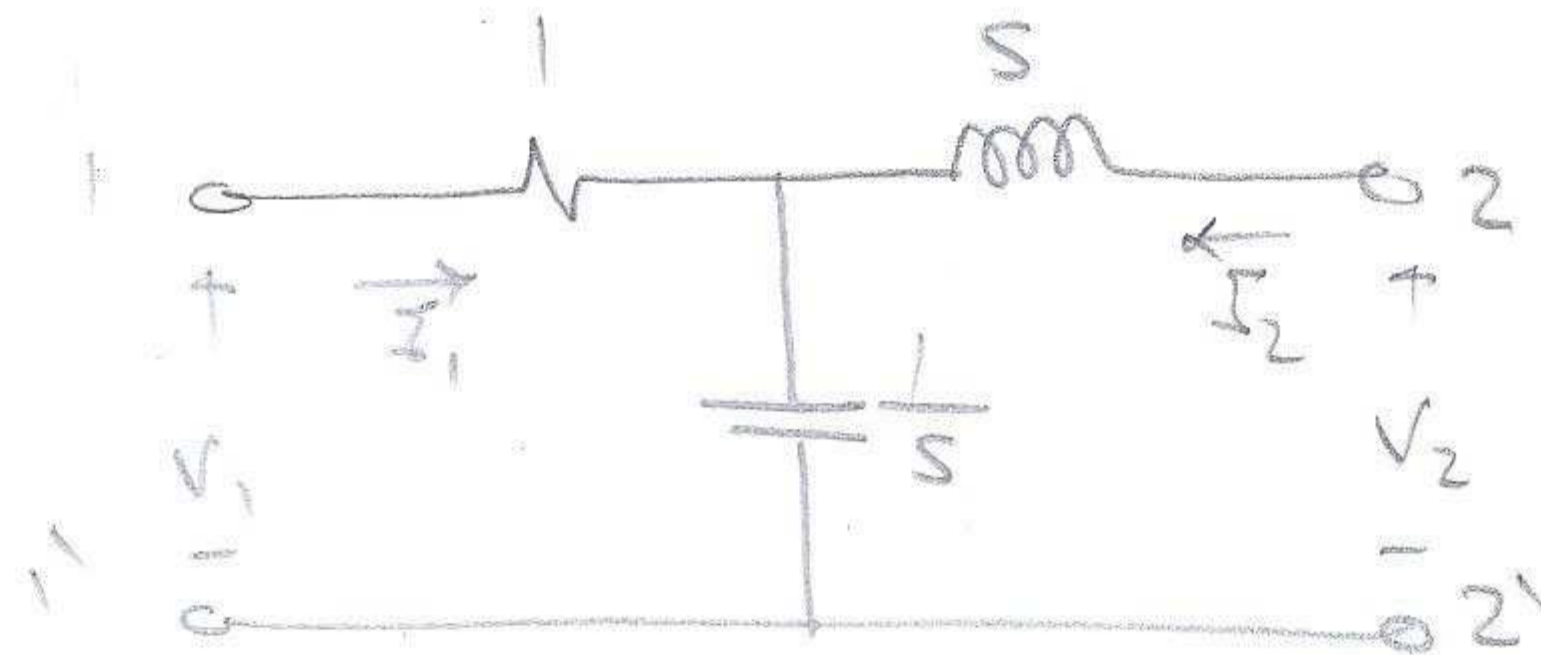

$$\Rightarrow \text{Let } I_2 = 0 \quad \therefore V_1 = Z_{11} I_1, \quad V_2 = Z_{21} I_1$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{(1 + \frac{1}{s}) I_1}{I_1} \Rightarrow \boxed{Z_{11} = \frac{s+1}{s}}$$



$$V_2 = \frac{1}{s} I_2 \quad \therefore Z_{21} = \frac{1}{s}$$

\therefore the system is reciprocal

$$\therefore Z_{21} = Z_{12} = \frac{1}{s}$$

② Let $I_1 = 0$

$$\therefore V_2 = Z_{22} I_2$$

$$V_2 = \left(s + \frac{1}{s}\right) I_2$$

$$\therefore Z_{22} = \frac{s^2 + 1}{s}$$

$$\therefore [Z] = \begin{bmatrix} \frac{s+1}{s} & \frac{1}{s} \\ \frac{1}{s} & \frac{s^2+1}{s} \end{bmatrix}$$


in Fig. b

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \leftarrow \textcircled{1}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \leftarrow \textcircled{2}$$

$$V_1 = -I_1 + \frac{4}{s} \quad \leftarrow \textcircled{3}$$
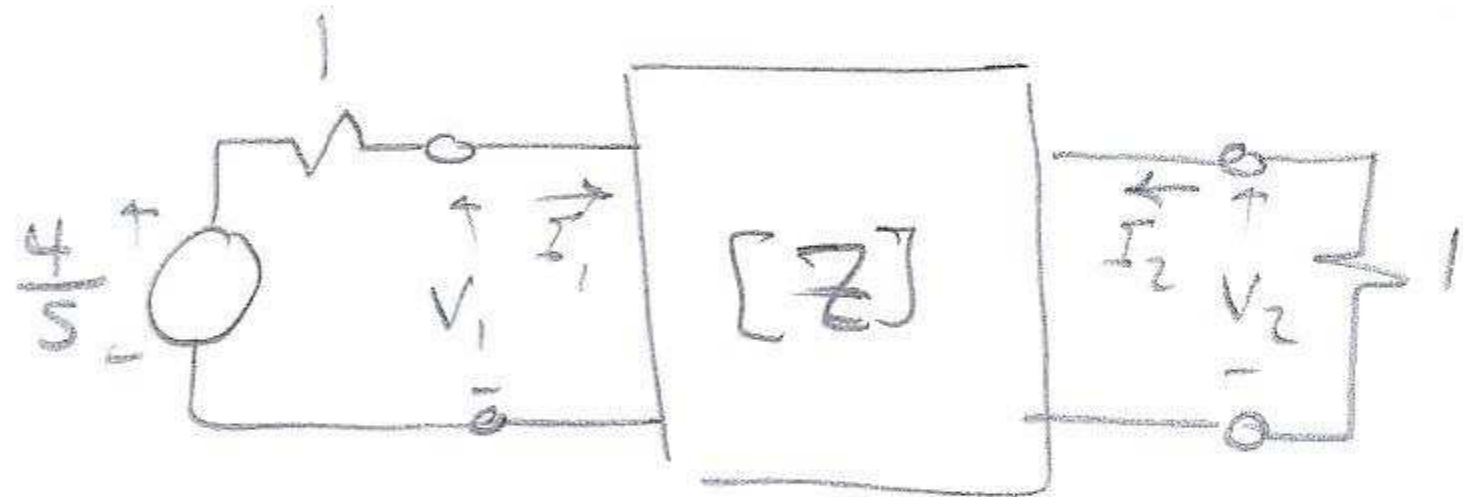
$$V_2 = -I_2 \quad \leftarrow \textcircled{4}$$



sub. $\textcircled{4}$ in $\textcircled{2}$

$$-I_2 = Z_{21} I_1 + Z_{22} I_2$$

$$\therefore -(1 + Z_{22}) I_2 = Z_{21} I_1$$

$$\therefore I_1 = \frac{-(1 + Z_{22}) I_2}{Z_{21}}$$

$$-I_1 + \frac{4}{s} = Z_{11} I_1 + Z_{12} I_2$$

$$\frac{4}{s} = (Z_{11} + 1) I_1 + Z_{12} I_2$$



$$\therefore \left(\frac{-(1+z_{11})(1+z_{22})}{z_{21}} + z_{12} \right) I_2 = \frac{4}{s}$$

$$I_2 = \frac{4z_{21}}{z_{12}z_{21} - (1+z_{11})(1+z_{22})}$$

$$I_2 = \frac{4/s}{\frac{1}{s^2} - \left(1 + \frac{s+1}{s}\right)\left(1 + \frac{s^2+1}{s}\right)}$$

$$= \frac{4/s}{\frac{1}{s^2} - \frac{2s^3 + 5s^2 + 4s + 1}{s^2}} = \frac{4s}{-(2s^3 + 5s^2 + 4s)}$$

$$= \frac{-5 + \sqrt{25-32}}{4} = \frac{-5 + j\sqrt{7}}{4}$$

$$I_2 = \frac{-2}{s^2 + 2.5s + 2} = \frac{-2}{\left(s + \frac{5}{4} - j\frac{\sqrt{7}}{4}\right)\left(s + \frac{5}{4} + j\frac{\sqrt{7}}{4}\right)}$$

$$= \frac{k}{s + \frac{5}{4} - j\frac{\sqrt{7}}{4}} + \frac{k^*}{s + \frac{5}{4} + j\frac{\sqrt{7}}{4}}$$

$$k = 1.512 \angle 90^\circ$$

$$\therefore i_2(t) = \left\{ 3.024 e^{-\frac{5}{4}t} \cos\left(\frac{\sqrt{7}}{4}t + 90^\circ\right) \right\} u(t)$$



$[Z]$	$\begin{bmatrix} 1 + \frac{1}{s} & \frac{1}{s} \\ \frac{1}{s} & s + \frac{1}{s} \end{bmatrix}$
$i_2(t)$	$\left\{ 3.024 e^{-\frac{5}{4}t} \cos\left(\frac{\sqrt{7}}{4}t + 90^\circ\right) \right\} u(t)$


Table 12



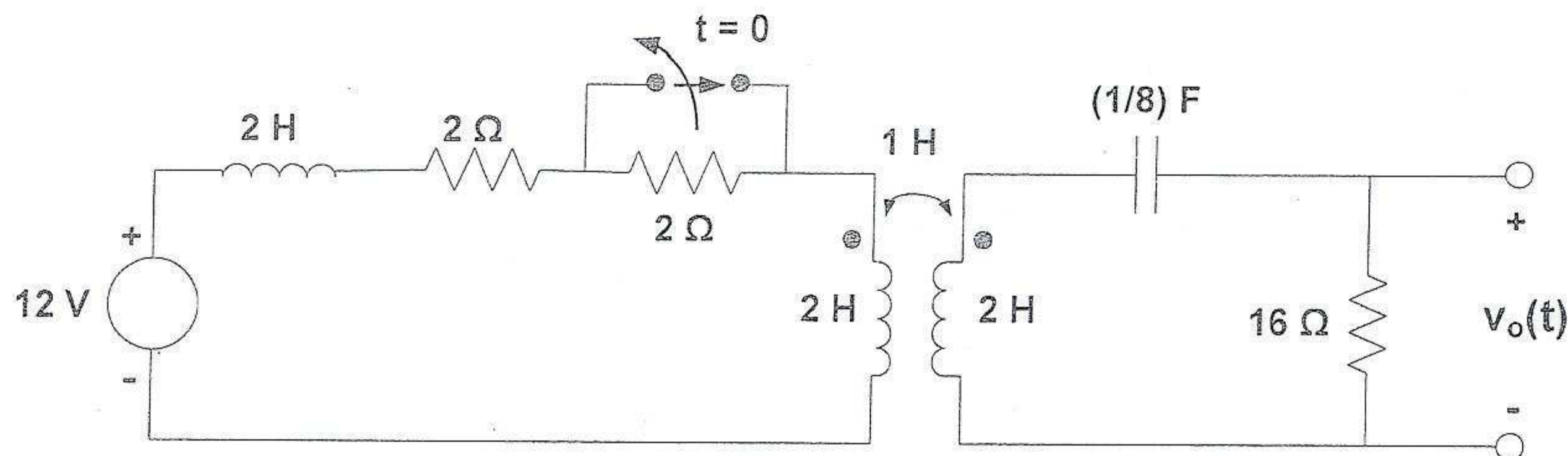Question[13]: Answer of Question 18

In the circuit shown in figure, derive an expression for the voltage $v_o(t)$ for $t > 0$ and sketch its value in volts against time in seconds.



Insert your results in Table 13 and sketch a.



$$i_{L_1}(0) = 6A$$

$$i_{L_2}(0) = 0$$

$$v_c(0) = 0$$

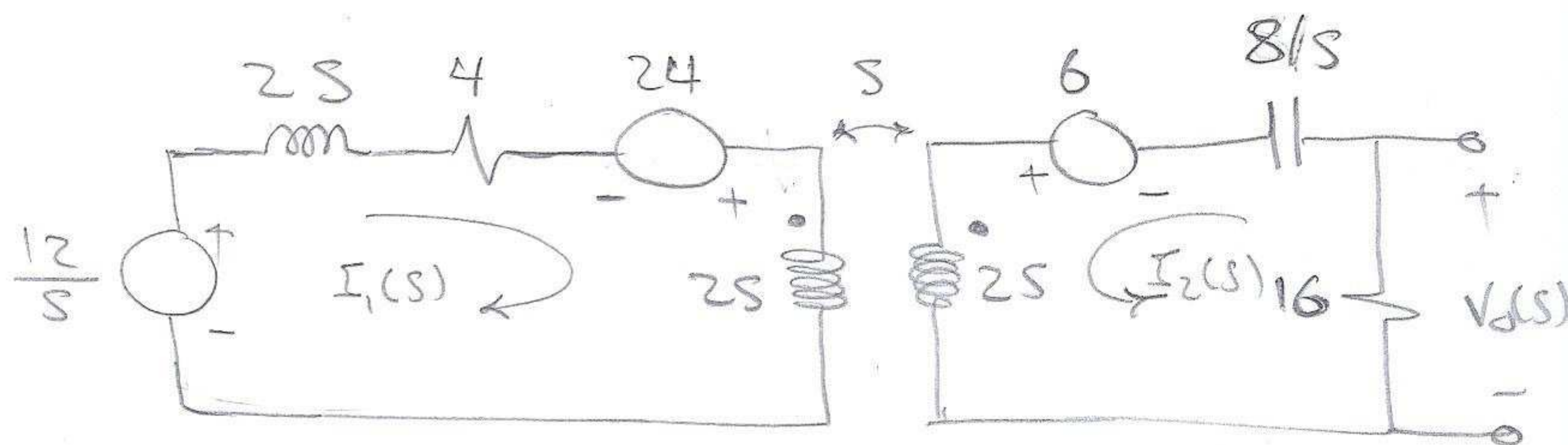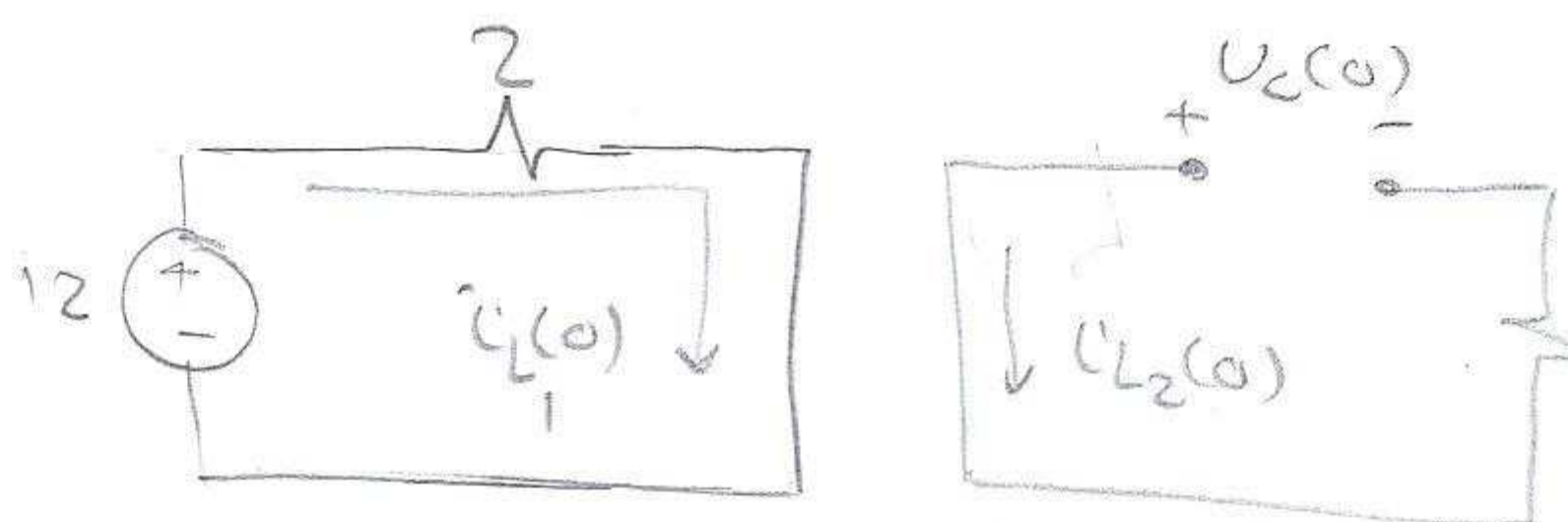

$$\frac{12}{s} + 24 = (4s + 4)I_1(s) + sI_2(s) \quad \rightarrow \textcircled{1}$$

$$6 = sI_1(s) + \left(\frac{8}{s} + 2s + 16\right)I_2(s) \quad \rightarrow \textcircled{2}$$

$$\begin{bmatrix} 4s+4 & s \\ s & \frac{2s^2+16s+8}{s} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{24s+12}{s} \\ 6 \end{bmatrix}$$



$$\Delta = \frac{8(s+1)(s^2+8s+4)}{s} - s^2$$

$$= \frac{7s^3 + 72s^2 + 96s + 32}{s}$$

$$\Delta_2 = \begin{vmatrix} 4(s+1) & \frac{12(2s+1)}{s} \\ s & 6 \end{vmatrix} = 24(s+1) - 12(2s+1) = 12$$


$$I_2 = \frac{\Delta_2}{\Delta} = \frac{12s}{7s^3 + 72s^2 + 96s + 32}$$

$$V_o(s) = -16 I_2 = \frac{-192s}{7(s+8.78)(s+0.542)(s+0.96)}$$

$$= \frac{3.7}{s+8.78} + \frac{4.317}{s+0.542} - \frac{0.035}{s+0.96}$$
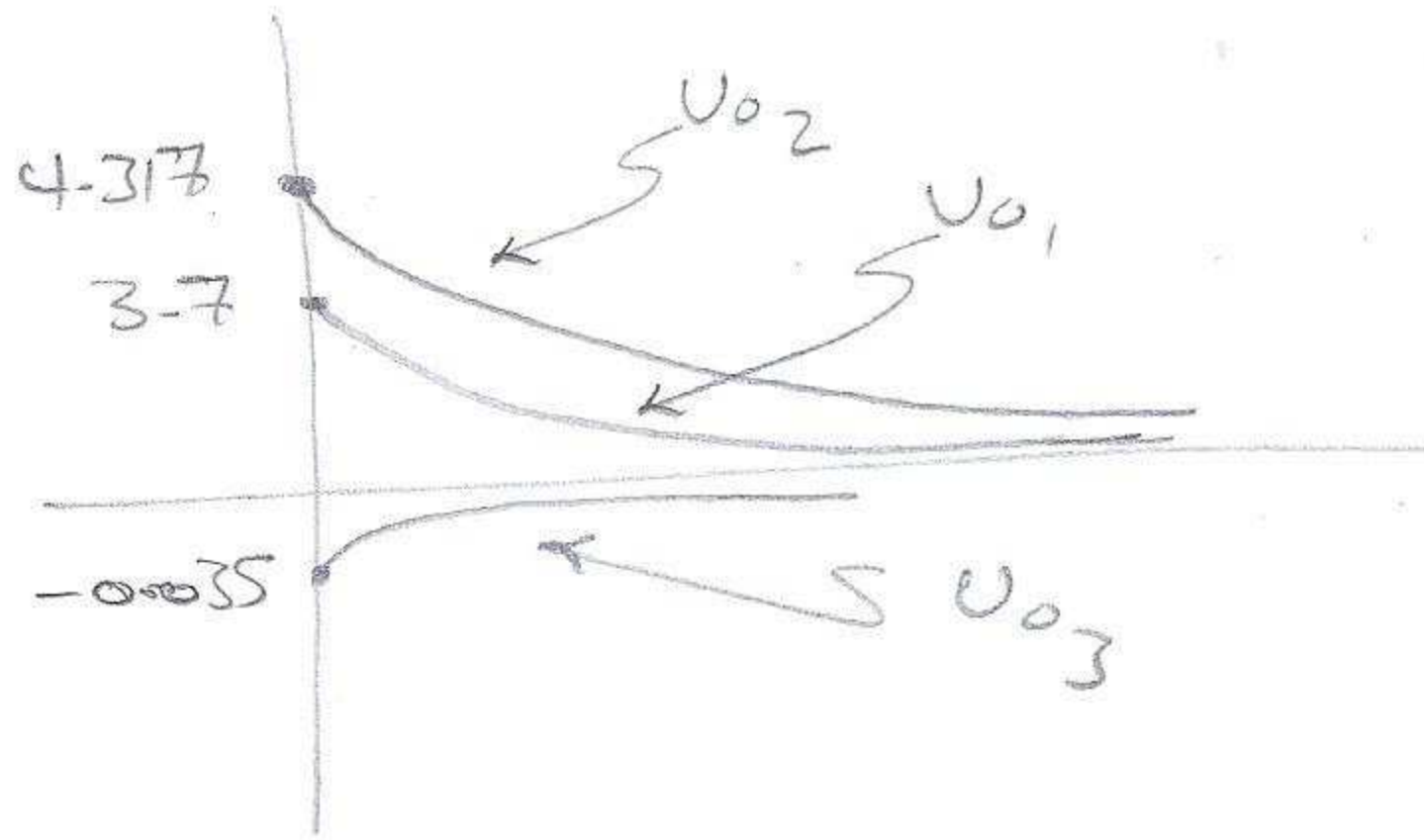
$$\therefore v_o(t) = \left(3.7 e^{-8.78t} + 4.317 e^{-0.542t} - 0.035 e^{-0.96t} \right) u(t)$$






$$v_o(t) = \left(\underset{v_{o1}}{3.7} e^{-8.78t} + \underset{v_{o2}}{4.317} e^{-0.542t} - \underset{v_{o3}}{0.035} e^{-0.96t} \right) u(t).$$

$v_o(t)$	
----------	--

Table 13

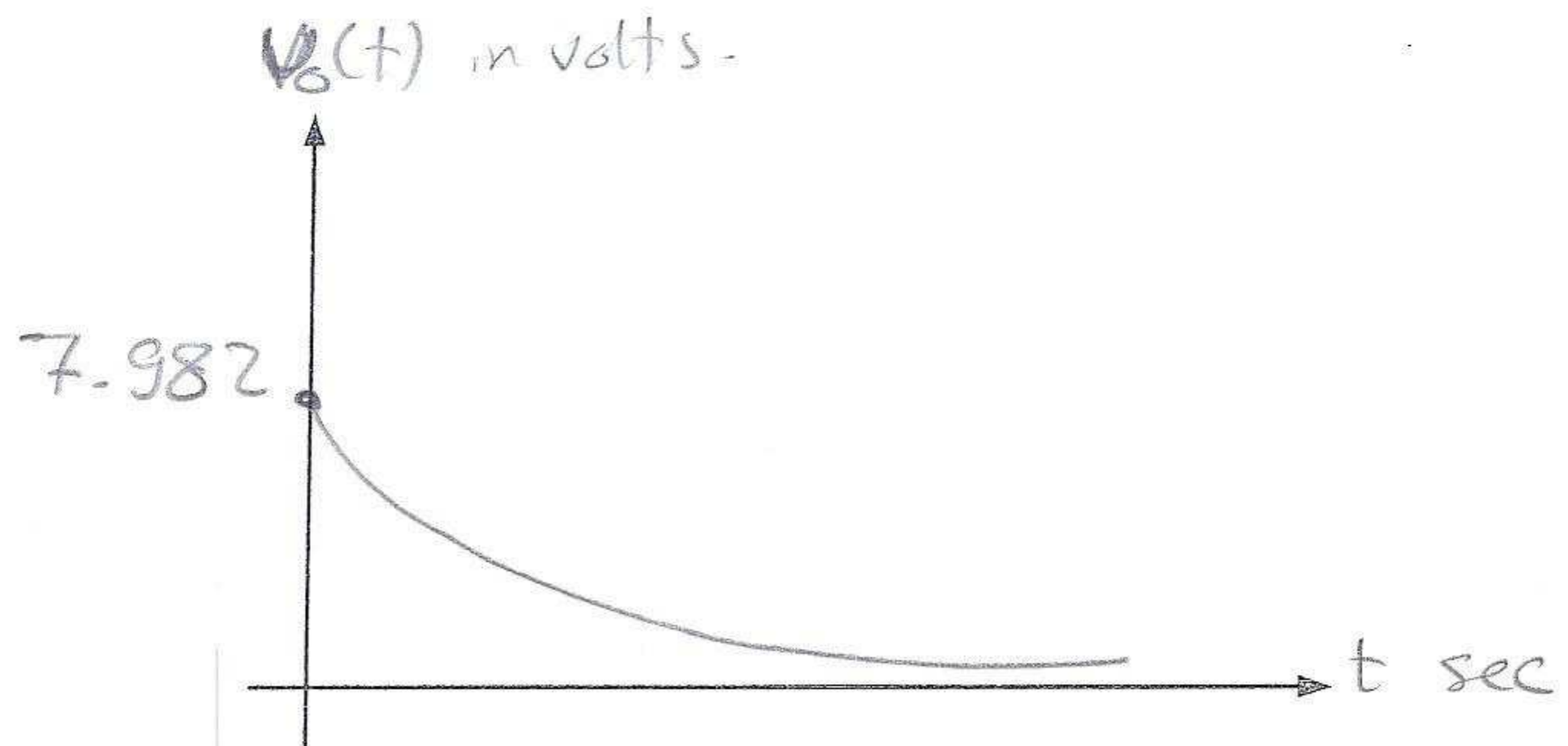

Sketch a






Question[14]: Answer of Question 19

Derive an expression of the output voltage $v_o(t)$ for the circuit shown in Fig.a if the input is the voltage $v(t)$ shown in :

i) Fig.b .

ii) Fig.c .

Insert your result in Table 14 .

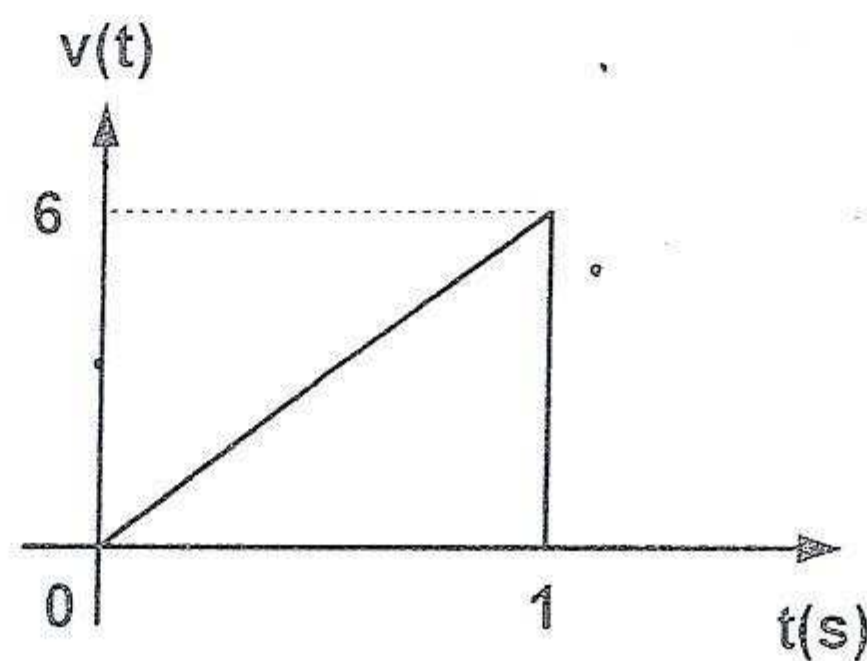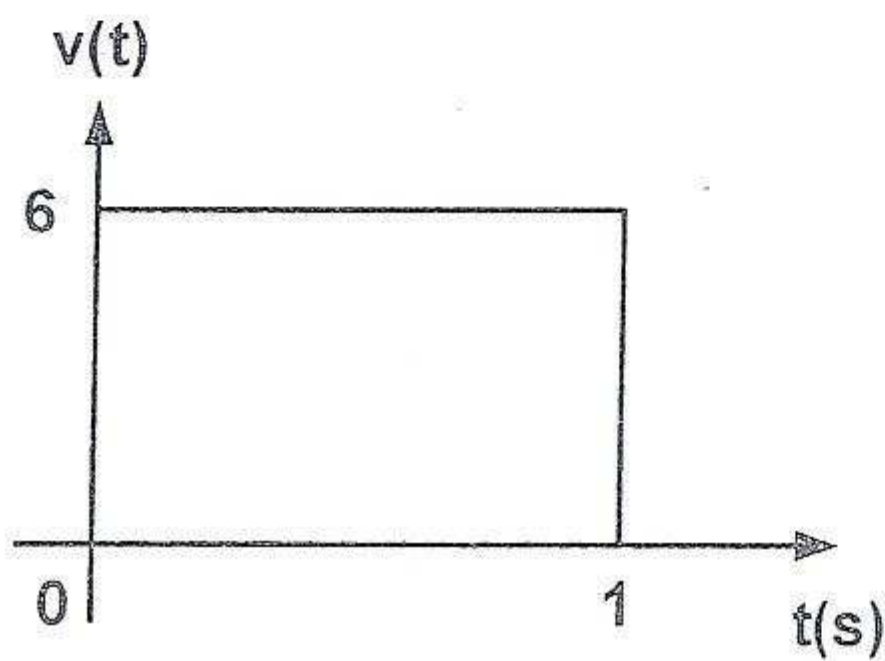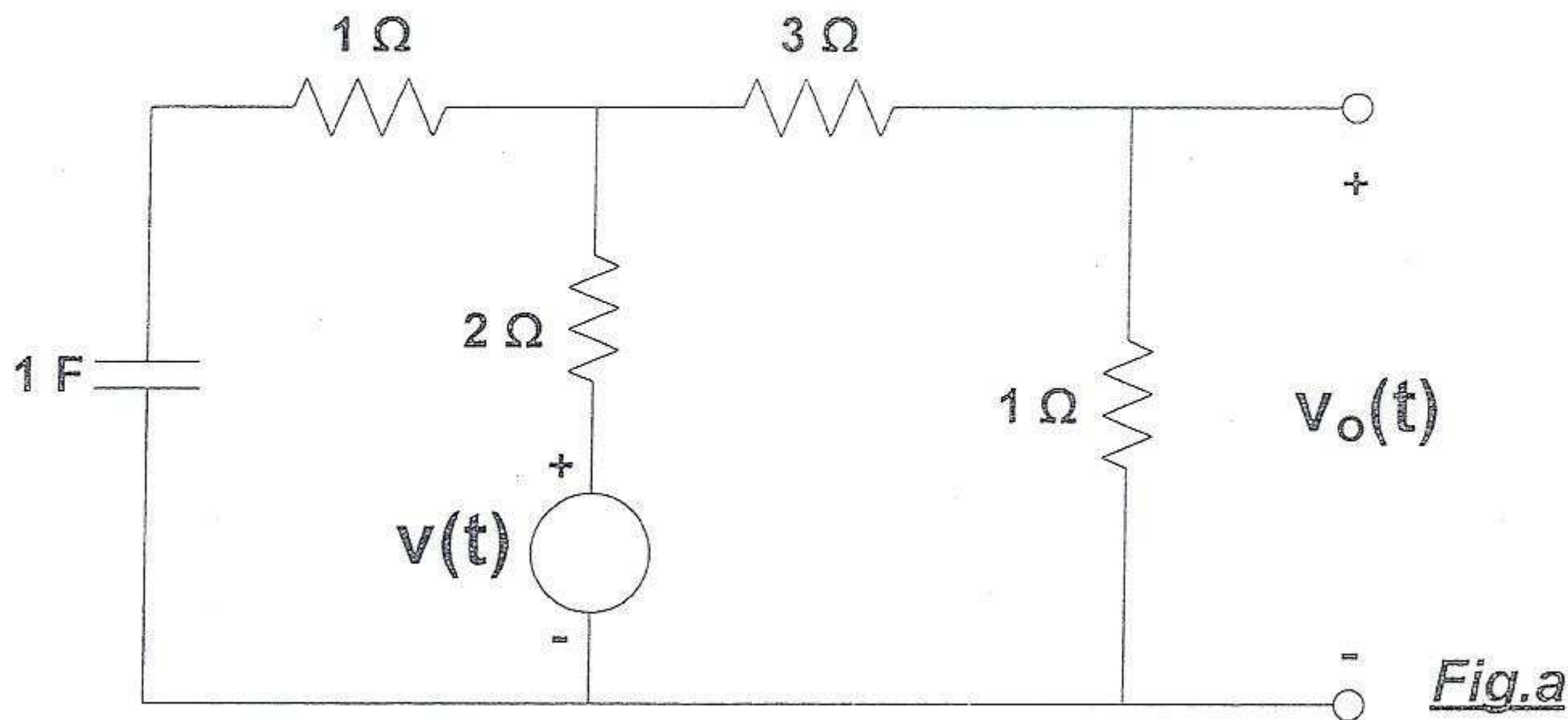

* For Fig. a


$$v(t) = 6(u(t) - u(t-1))$$

at $t=0$ $v(t) = 6\text{Volts}$.

$$V_c(0) = 6 - 2I$$



$$= 6 - 2 * \frac{6}{6}$$

$$\therefore V_c(0) = 4\text{Volts}$$

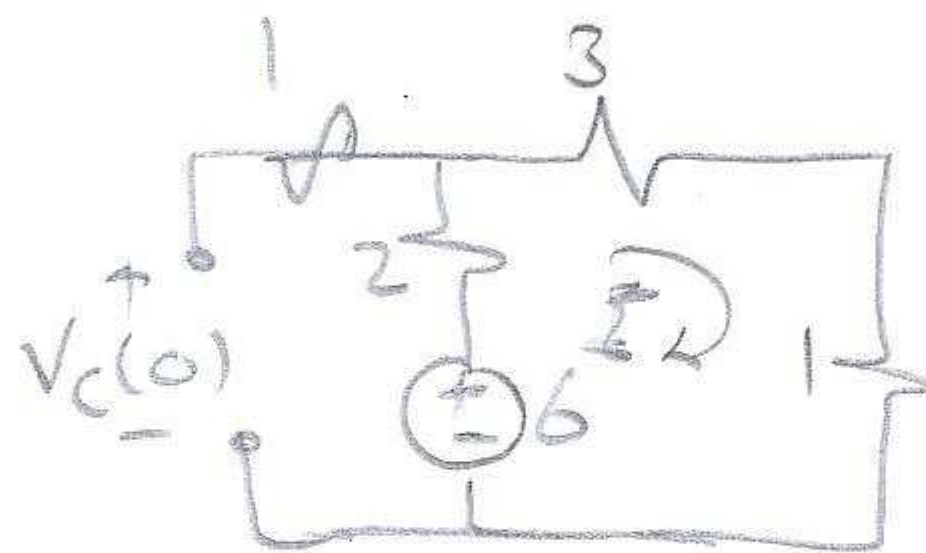



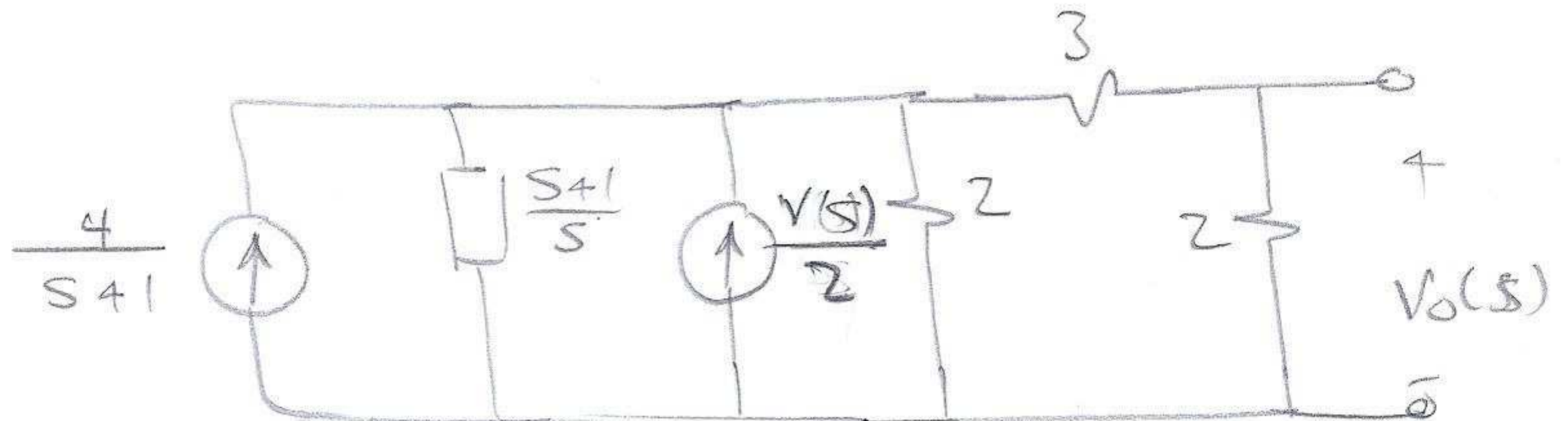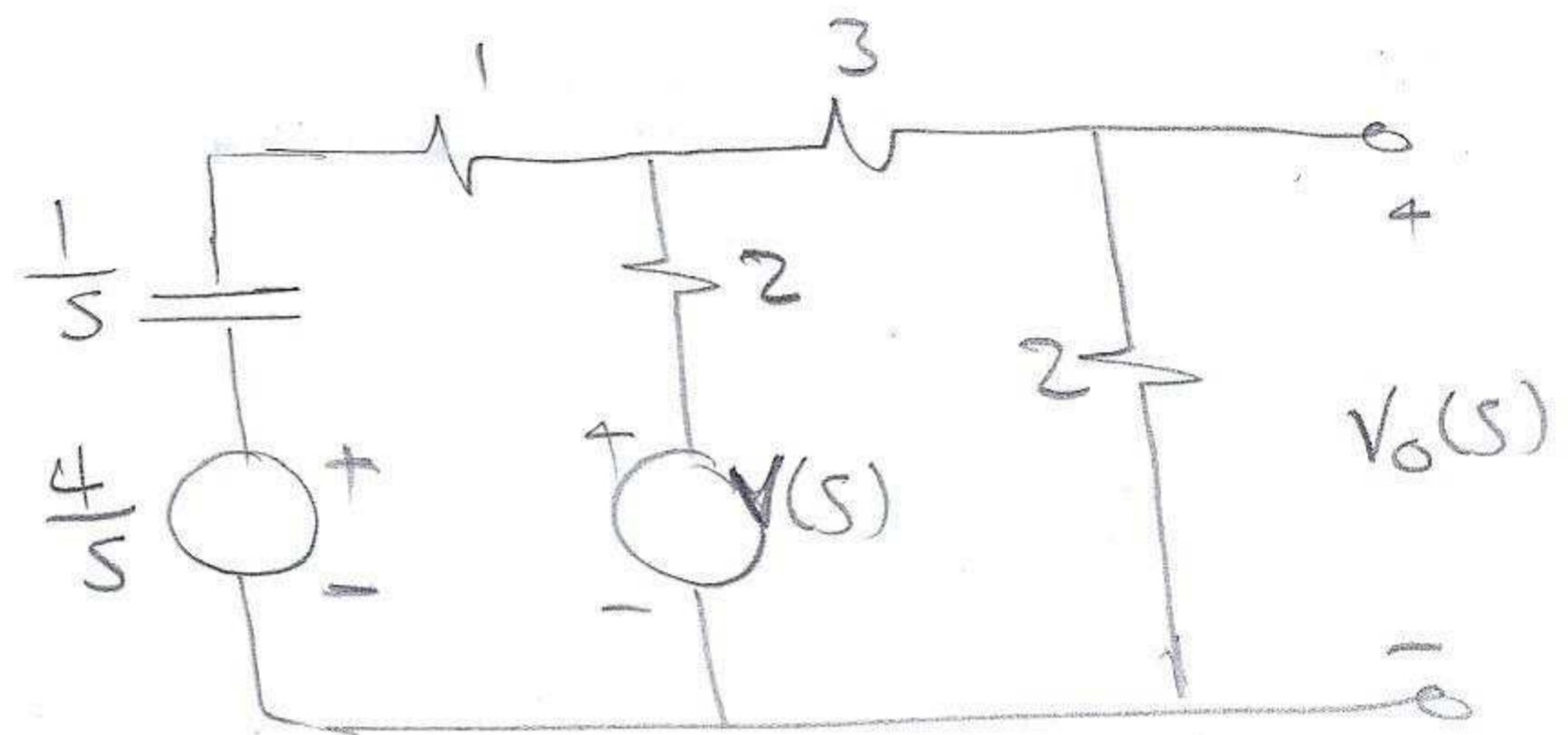
$$Z_p = \frac{2 * \frac{s+1}{s}}{2 + \frac{s+1}{s}} = \frac{2(s+1)}{3s+1}$$


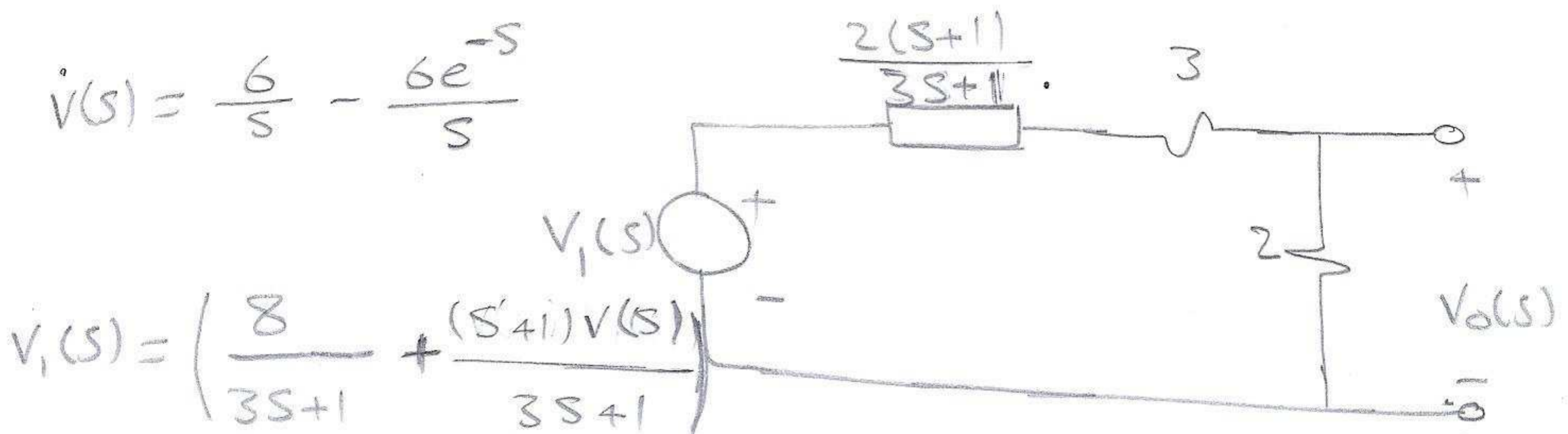
$$V(s) = \frac{6}{s} - \frac{6e^{-s}}{s}$$



$$V_1(s) = \left(\frac{8}{3s+1} + \frac{(s+1)V(s)}{3s+1} \right)$$

$$V_o(s) = V_1(s) * \frac{2}{5 + \frac{2(s+1)}{3s+1}} = \frac{8 + (s+1)V(s)}{3s+1} * \frac{2}{5 + \frac{2(s+1)}{3s+1}}$$

$$V_o(s) = \frac{16 + 2(s+1)V(s)}{17s+7} = \frac{12(8 + (s+1)(1 - e^{-s}))}{s(17s+7)}$$

$$= \frac{96}{17s(s + \frac{7}{17})} + \frac{12(1 - e^{-s})}{17(s + \frac{7}{17})} + \frac{12(1 - e^{-s})}{17s(s + \frac{7}{17})}$$



$$V_o(s) = \frac{96/7}{s} - \frac{96/7}{s + \frac{7}{17}} + \frac{12/7}{s + \frac{7}{17}} - \frac{12/7 e^{-s}}{(s + \frac{7}{17})}$$

$$+ \frac{12/7}{s} - \frac{12/7}{s + \frac{7}{17}} - \frac{12/7 e^{-s}}{s} + \frac{12/7 e^{-s}}{s + \frac{7}{17}}$$

$$\therefore V_o(t) = \left(\frac{96}{7} - \frac{96}{7} e^{-\frac{7}{17}t} + \frac{12}{17} e^{-\frac{7}{17}t} + \frac{12}{7} - \frac{12}{7} e^{-\frac{7}{17}t} \right) u(t)$$

$$+ \left(\frac{12}{17} e^{-\frac{7}{17}(t-1)} - \frac{12}{7} + \frac{12}{7} e^{-\frac{7}{17}(t-1)} \right) u(t-1)$$

$$V_o(t) = \left(\frac{108}{7} - 14.722 e^{-\frac{7}{17}t} \right) u(t)$$

$$+ \left(\frac{-12}{7} + 2.42 e^{-\frac{7}{17}(t-1)} \right) u(t-1)$$


in Fig.b



no-initial conditinal as $u(t) = 6t \{u(t) - u(t-1)\} = 0 \Big|_{t=0}$

$$u(t) = 6t u(t) - 6(t-1) u(t-1) - 6 u(t-1)$$

$$V(s) = \frac{6}{s^2} - \frac{6e^{-s}}{s^2} - \frac{6e^{-s}}{s} \cdot \frac{1}{s}$$
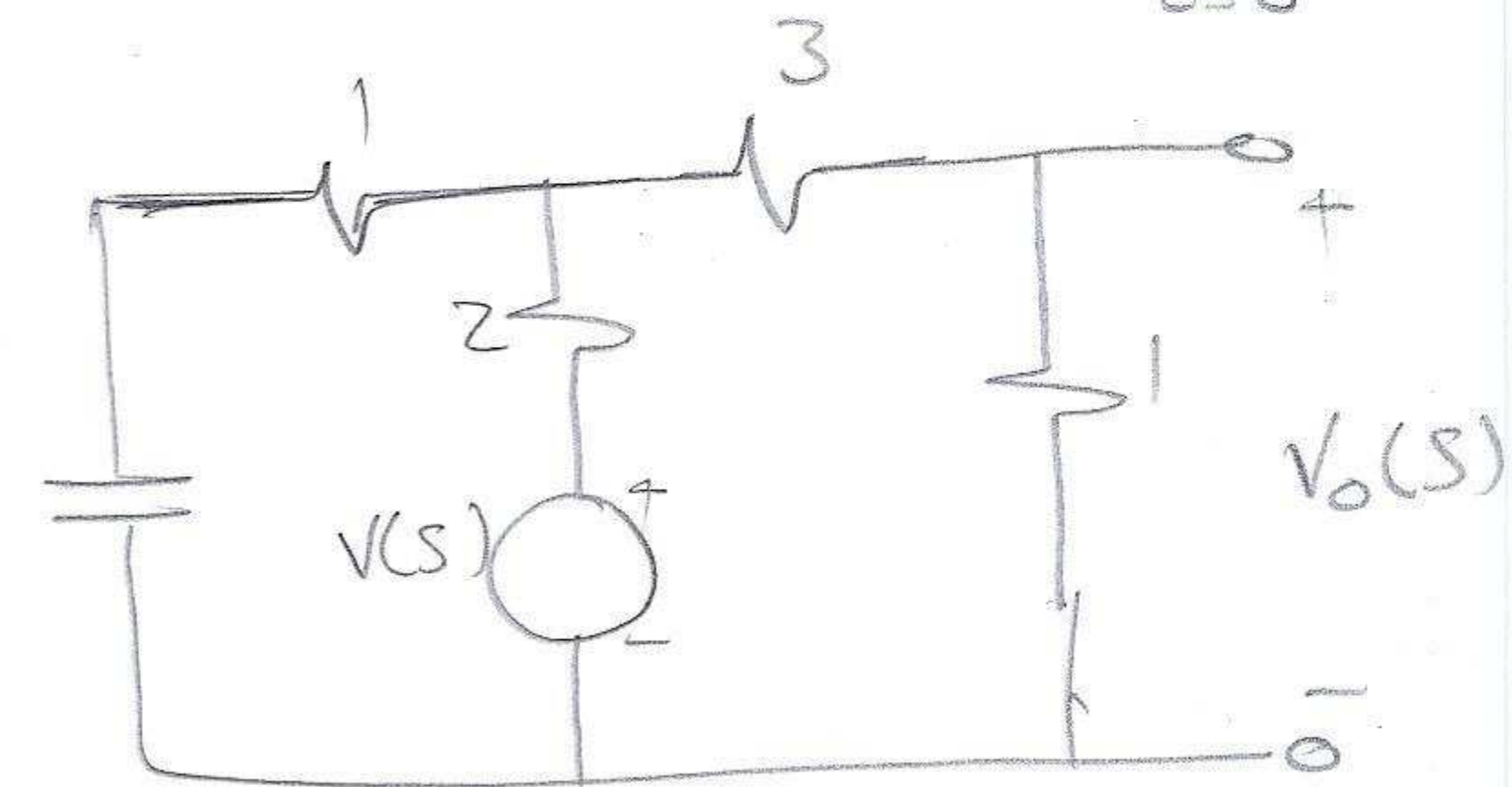
$$V(s) = \frac{6(1 - e^{-s} - se^{-s})}{s^2}$$



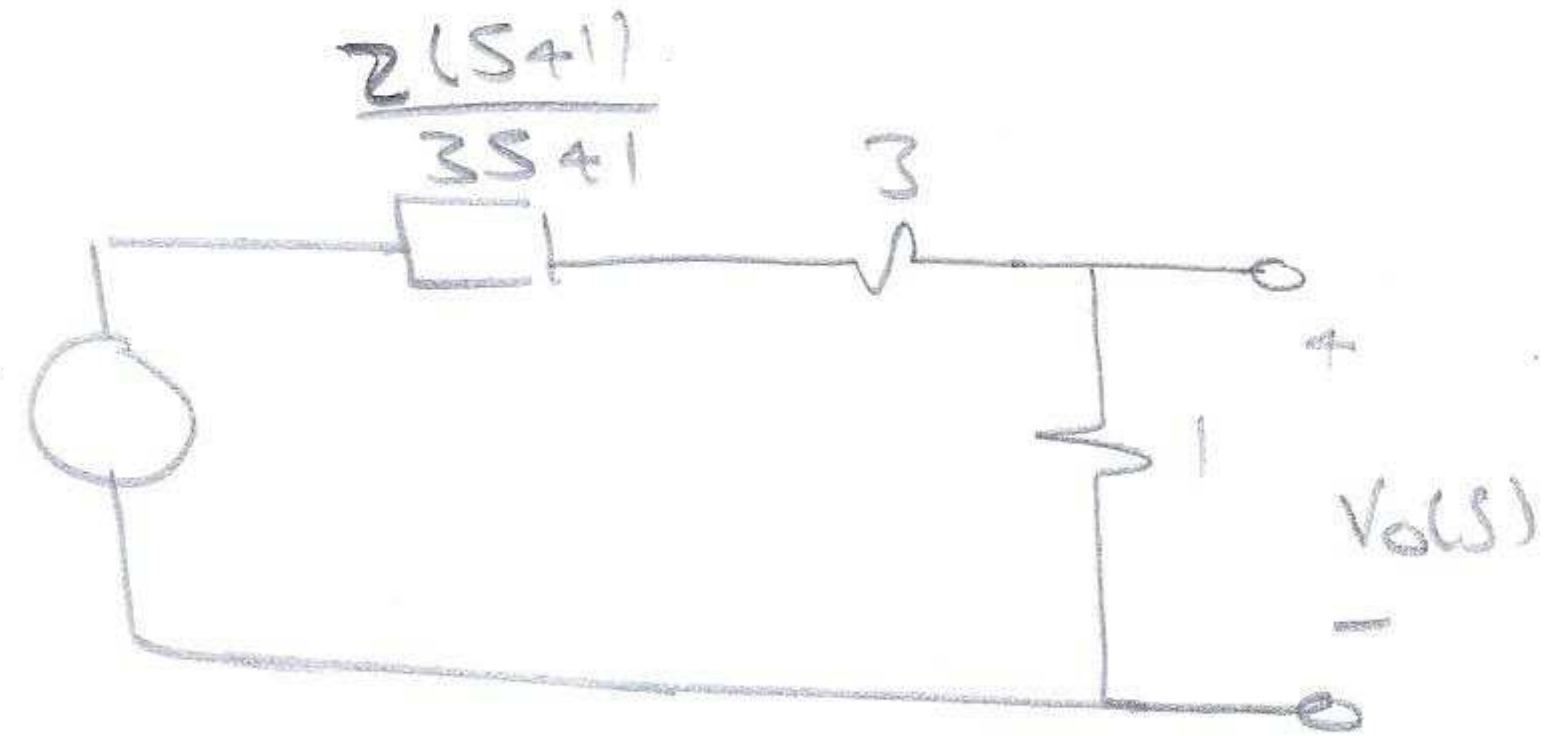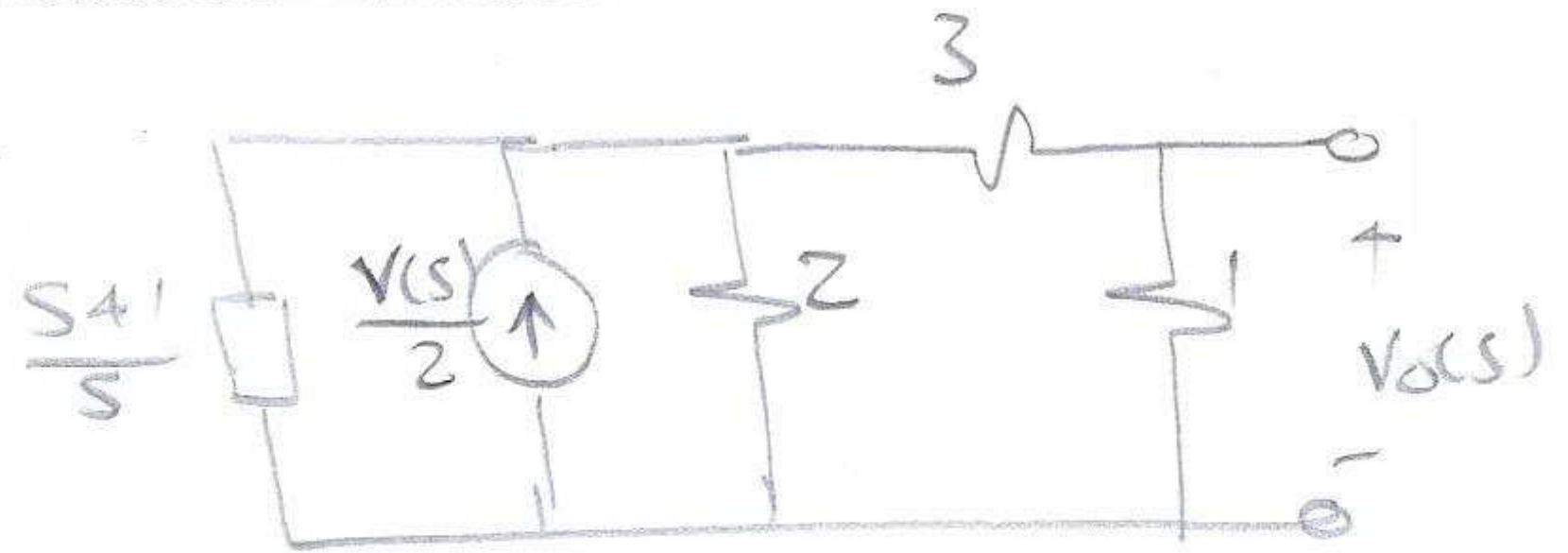

$$V_o(s) = \frac{(S+1)V(s)}{3S+1} + \frac{(S+1)V(s)}{3S+1} \cdot \frac{2(S+1)}{3S+1}$$

$$V_o(s) = \frac{(S+1)V(s)}{14S+6}$$

a) $v_o(t)$	$\frac{10e^{-t}}{7} - 3e^{-2t}$
b) $v_o(t)$	

Table 14