



[1] Determine the O.C. Z-parameters for the network shown in Fig. 1. Sketch its Z-parameters' equivalent circuits.

[2] Determine the S.C. Y-parameters for the network shown in Fig. 2. Sketch the two forms of its equivalent circuit.

[3] Calculate the Hybrid H-parameters for the network given in Fig. 1 and sketch its equivalent circuit.

[4] For the Hybrid equivalent circuit shown in Fig. 3, calculate the current gain  $A_i$  and the voltage gain  $A_v$ .

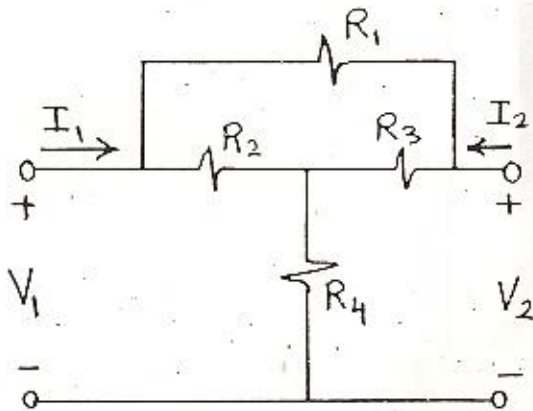


Fig.1

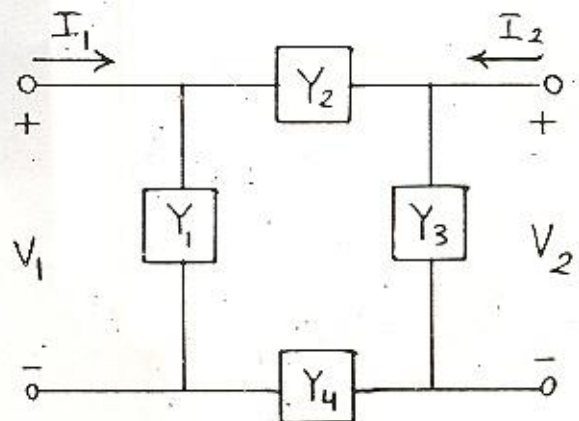


Fig.2


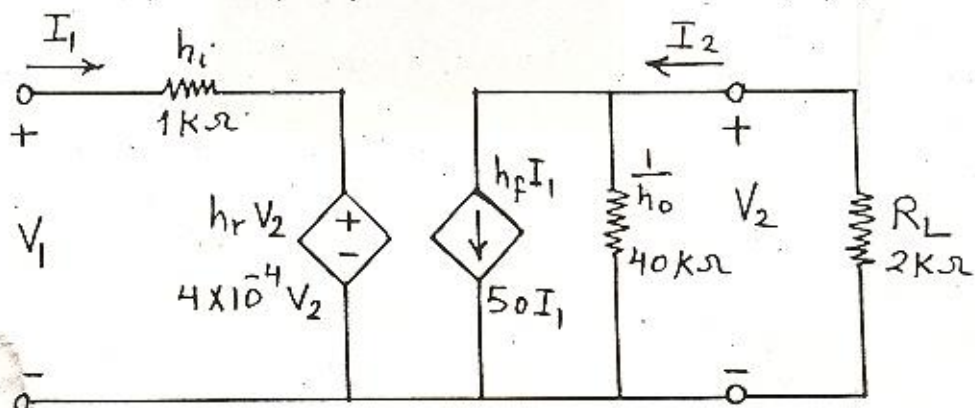
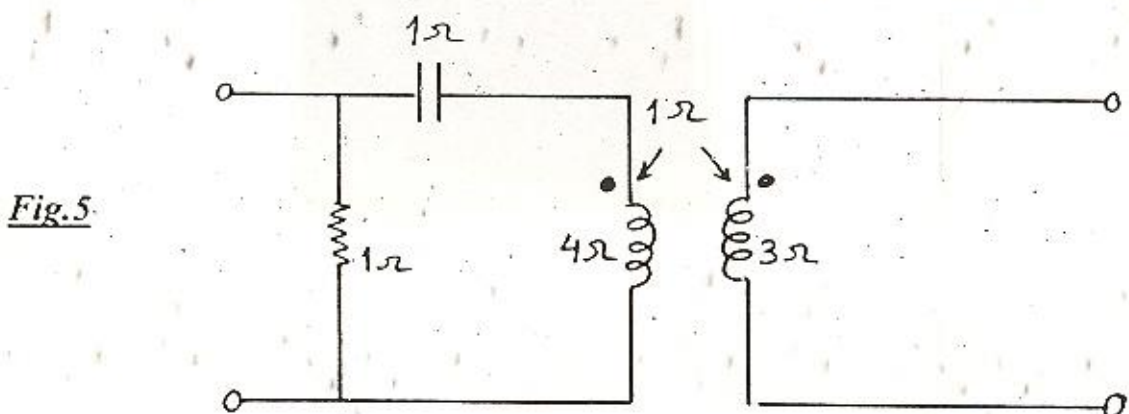


Fig.3

[5] For the Z-parameter equivalent circuit shown in Fig. 4, calculate the input and output impedances.

[6] The Hybrid H-parameters of a network are given by:  $h_{11} = 1 \text{ K}\Omega$ ,  $h_{12} = 0.0002$ ,  $h_{21} = 100$  and  $h_{22} = 20 \mu \text{ mho}$ . Calculate the H-parameters of two of such network connected in: a) series. b) parallel.

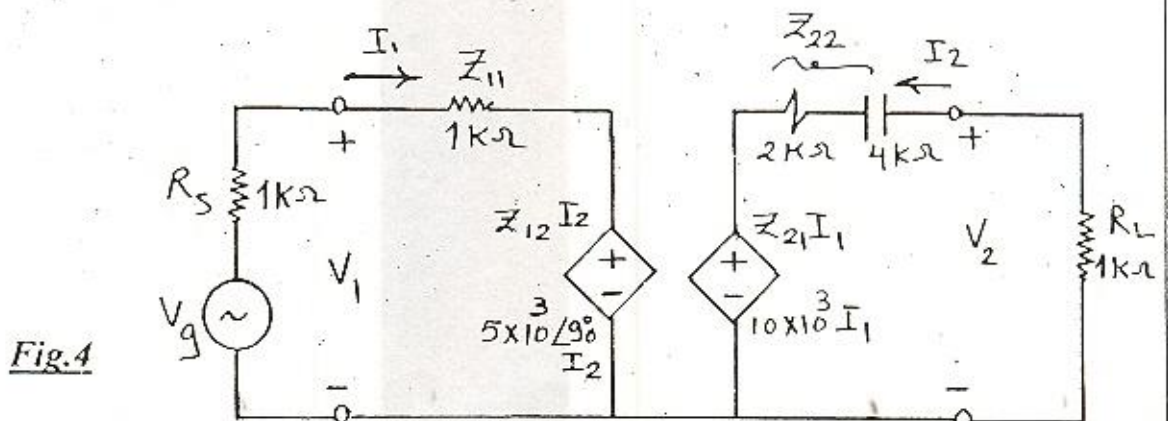[7] Determine the transmission-parameters for the network shown in Fig. 5 and write its 2-port equations in the A-form.



[8] Find the Z-parameters for the 2-port network shown in Fig. 6 and calculate the voltage gain of the entire circuit with a  $4\text{ K}\Omega$  load attached to the output.

[9] Find the transmission-parameters for the 2-port network shown in Fig. 7.

[10] Simplify the network shown in Fig. 8 into two 2-port networks connected in parallel. Hence, calculate the Y-parameters' matrix of the whole network.

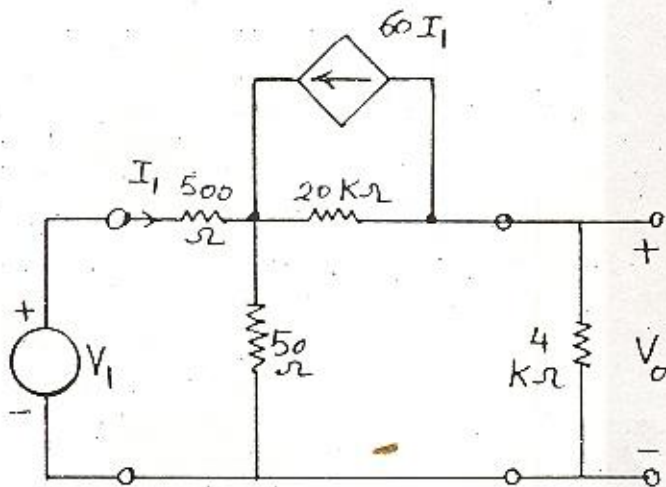


Fig.6

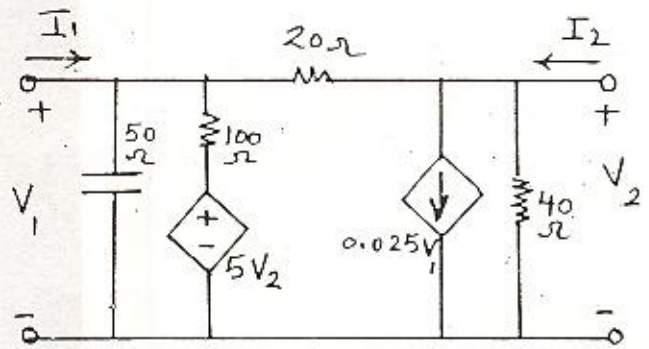


Fig.7

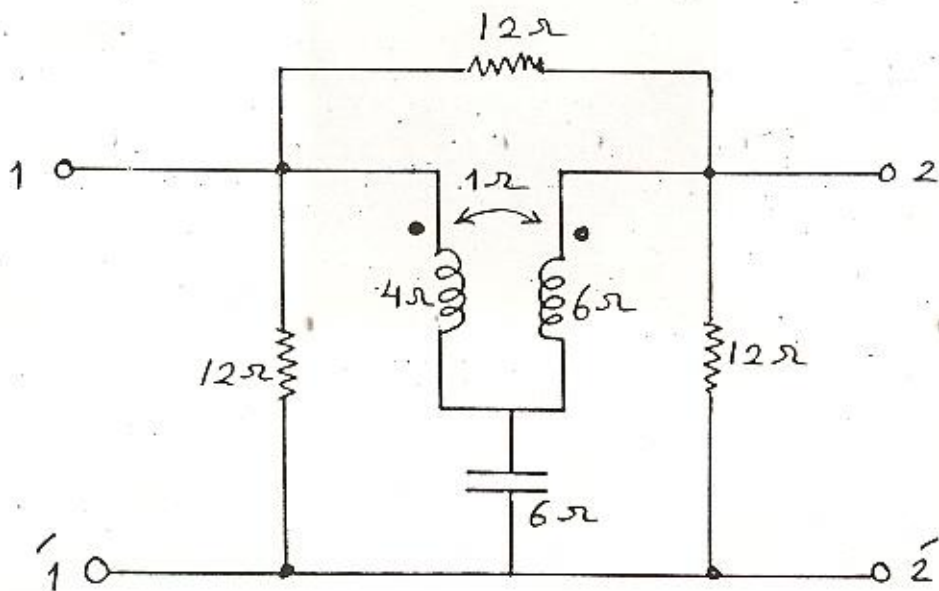


Fig.8

[11] Using the  $Z$ -parameters find Thevenin's equivalent circuit with respect to port 2 for the 2-port network shown in Fig. 9.




[12] The networks  $D$  and  $E$  in the circuit shown in Fig. 10 are reciprocal and symmetrical networks.  $D$  has  $a_{11} = 5$  and  $a_{12} = 24 \Omega$ . The impedance  $Z_0$  is adjusted for maximum average power transfer. Find  $Z_0$  if  $Z_g = 5 \Omega$ .

[13] a) Derive an expression of the input and output impedances of the two-port network shown in Fig. 11 in terms of the  $H$ -parameters of the network, the internal impedance of the source  $Z_g$  and the load impedance  $Z_L$ .

b) If  $h_{11} = 1500 \Omega$ ,  $h_{12} = 10^{-3}$ ,  $h_{21} = 50$ ,  $h_{22} = 50 \mu \text{ mho}$ , the internal impedance of the source is  $Z_g = 1500 \Omega$  and the source voltage  $V_g = 250 \angle 0^\circ$ , calculate:

i) The maximum average power delivered to the load.

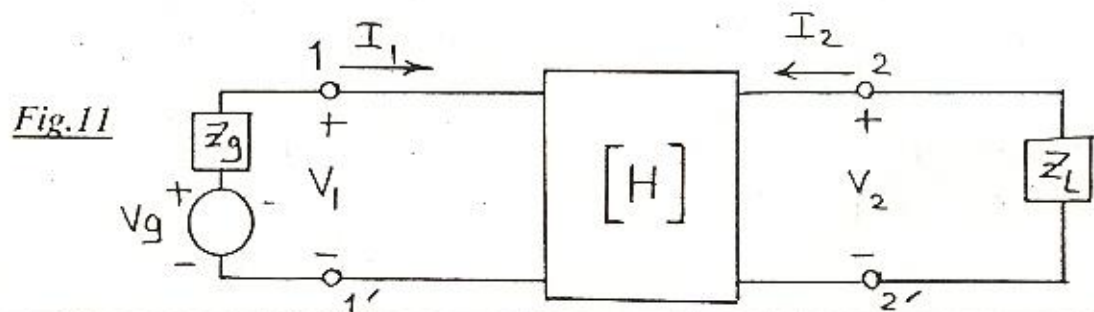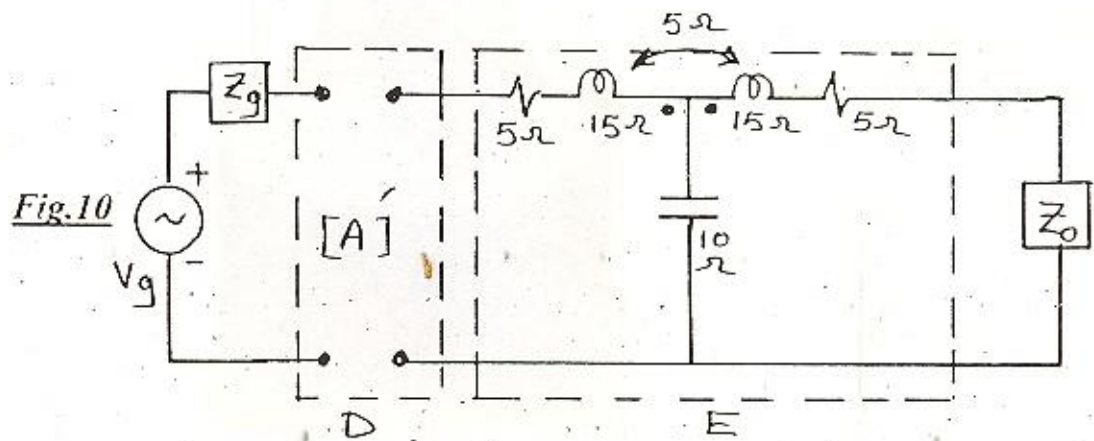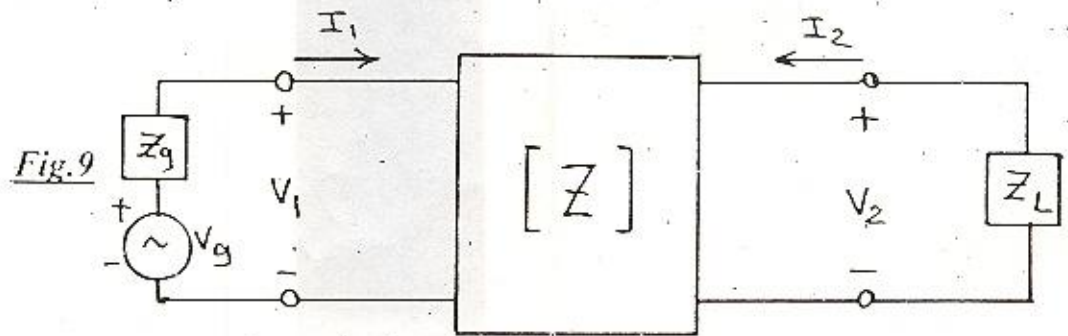ii) The average power delivered to the input port of the network at the condition of maximum power transfer to the load.



[14] The H-parameters of a two-port network are given by the matrix :

$$[H] = \begin{bmatrix} 2 \Omega & 0.2 \\ -4 & 0.1 \text{ mho} \end{bmatrix}$$



- Check the conditions of symmetry and reciprocity for the network.
- Sketch its equivalent circuit.
- If two resistors of  $2\Omega$  and  $5\Omega$  are added to the network as shown in Fig.12, calculate the H-parameters of the total network :

[15] a) Calculate the transmission A-parameters of a two-port network as a function of its Hybrid H-parameters.

- The amplifier circuit shown in Fig.13 is formed of two identical stages each having the Hybrid H-parameters given by :

$$[H] = \begin{bmatrix} 1 \text{ K}\Omega & 0.001 \\ 100 & 0.1 \text{ m.mho} \end{bmatrix}$$

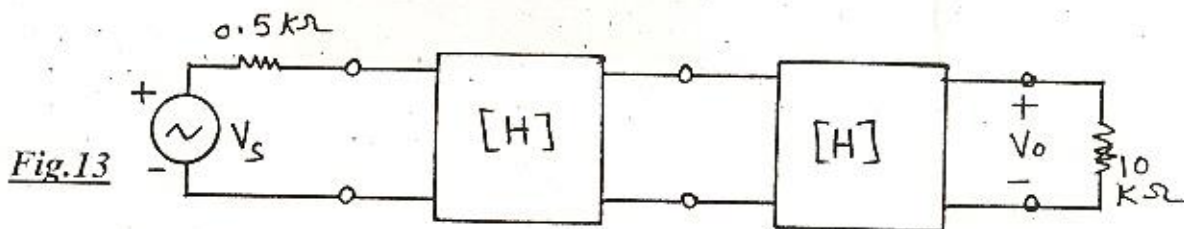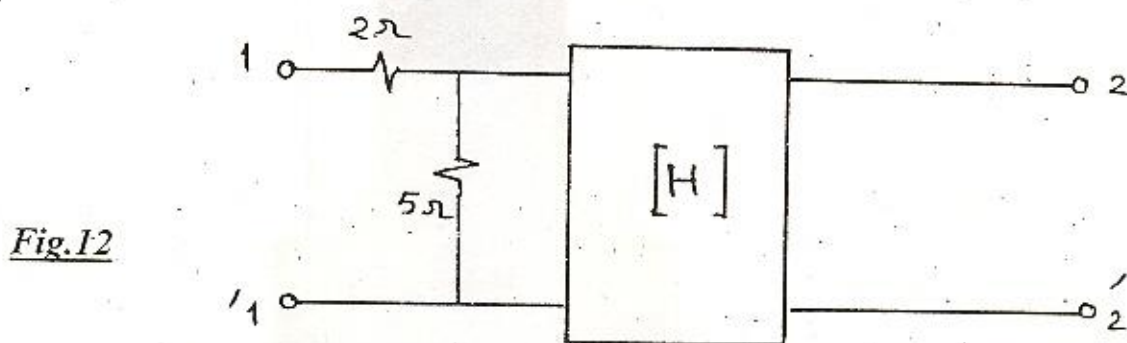What is the value of the input voltage  $V_s$  required to obtain an output voltage  $V_o$  of 25 volts ?



[16(a)] Two sets of measurements were made on the two-port network  $N$  shown in Fig. 14. The results were as follows:

Measurement 1

$$V_1 = 20 \text{ mV}$$

$$I_1 = 20 \text{ } \mu\text{A}$$

$$V_2 = 40 \text{ V}$$

$$I_2 = 0$$

Measurement 2

$$V_1 = 4 \text{ V}$$

$$I_1 = 5 \text{ mA}$$

$$V_2 = 0$$

$$I_2 = -200 \text{ mA}$$

Find the H-parameters representing the two-port network.

b) Using the H-parameters, calculate the value of the variable resistance  $R_o$  when adjusted to receive maximum power and find the value of this power.

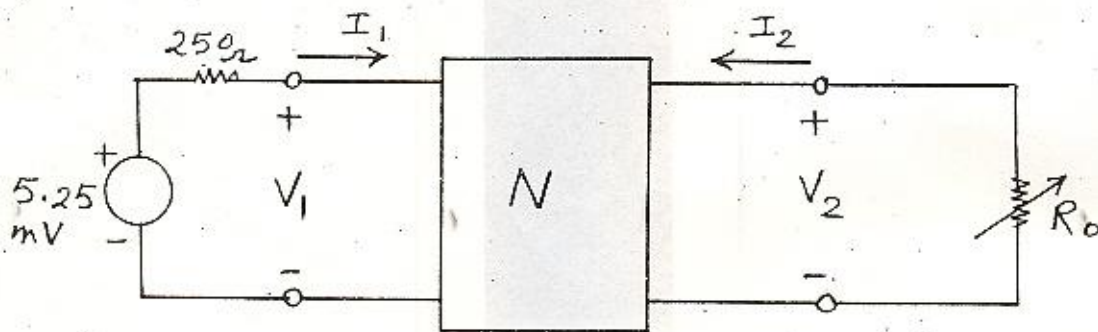


Fig.14




**Question/1/:**

a) Determine the O.C. Z-parameters for the network shown in figure and sketch its Z-parameters' equivalent circuits.

b) Calculate the Hybrid H-parameters of the same network and sketch its equivalent circuit.

Insert your results in Table 1 .

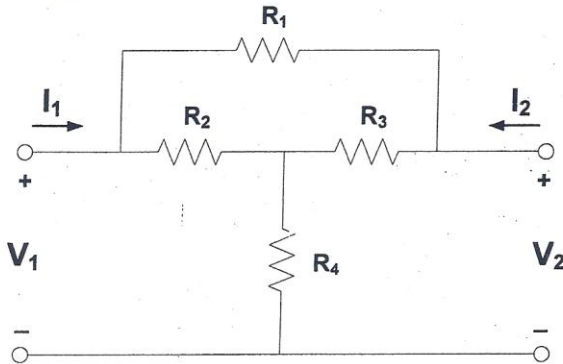

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$


@  $I_2 = 0$

$$V_1 = Z_{11} I_1, \quad V_2 = Z_{21} I_1$$

$$V_1 = R_2 I_1 + \frac{R_1 + R_3}{R_1 + R_2 + R_3} I_1 + I_1 R_4$$

$$V_1 = \left[ R_4 + (R_2 \parallel (R_1 + R_3)) \right] I_1$$
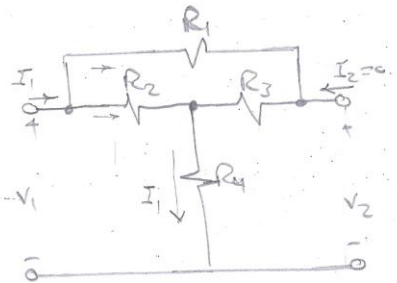
$$\therefore Z_{11} = R_4 + (R_2 \parallel (R_1 + R_3))$$






$$V_2 = R_4 I_1 + R_3 * I_1 * \frac{R_2}{R_1 + R_2 + R_3}$$

$$\therefore Z_{21} = R_4 + \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

the network is reciprocal so  $\Rightarrow Z_{12} = Z_{21} = R_4 + \frac{R_2 R_3}{R_1 + R_2 + R_3}$

at  $I_1 = 0$
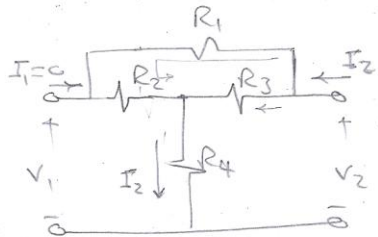
$$V_1 = Z_{12} I_2 \quad , \quad V_2 = Z_{22} I_2$$



$$V_2 = I_2 R_4 + R_3 * I_2 * \frac{R_1 + R_2}{R_1 + R_2 + R_3}$$

$$\therefore Z_{22} = \frac{V_2}{I_2} \Rightarrow Z_{22} = R_4 + (R_3 \parallel (R_1 + R_2))$$

$$\therefore [Z] = \begin{bmatrix} R_4 + (R_2 \parallel (R_1 + R_3)) & R_4 + \frac{R_2 R_3}{R_1 + R_2 + R_3} \\ R_4 + \frac{R_2 R_3}{R_1 + R_2 + R_3} & R_4 + (R_3 \parallel (R_1 + R_2)) \end{bmatrix}$$

\* For H-Parameters

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$

\* For Z-Parameters

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned}$$



at  $I_1 = 0$

$$V_1 = h_{12} V_2$$

$$I_2 = h_{22} V_2$$

$$V_1 = Z_{12} I_2$$

$$V_2 = Z_{22} I_2$$

$$h_{12} = \frac{V_1}{V_2} = \frac{Z_{12}}{Z_{22}}$$

$$h_{22} = \frac{I_2}{V_2} = \frac{1}{Z_{22}}$$

∴ the network is reciprocal ∴  $h_{12} = -h_{21}$

$$\therefore h_{21} = -\frac{Z_{12}}{Z_{22}}$$

at  $V_2 = 0$

$$V_1 = h_{11} I_1$$

$$I_2 = h_{21} I_1$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$0 = Z_{21} I_1 + Z_{22} I_2 \rightarrow -Z_{21} I_1 = Z_{22} I_2$$

$$V_1 = Z_{11} I_1 + Z_{12} \left( \frac{-Z_{21}}{Z_{22}} \right) I_1$$

$$\therefore h_{11} = \frac{V_1}{I_1} = \frac{|Z_{11}|}{Z_{22}}$$

$$\therefore [H] = \begin{bmatrix} \frac{|Z_{11}|}{Z_{22}} & \frac{Z_{12}}{Z_{22}} \\ -\frac{Z_{12}}{Z_{22}} & \frac{1}{Z_{22}} \end{bmatrix}$$



	$\begin{bmatrix} R_4 + (R_2 \parallel (R_1 + R_3)) & R_4 + \frac{R_2 R_3}{R_1 + R_2 + R_3} \\ R_4 + \frac{R_2 R_3}{R_1 + R_2 + R_3} & R_4 + (R_3 \parallel (R_1 + R_2)) \end{bmatrix}$
	$\begin{bmatrix} \frac{Z_{11}}{Z_{22}} & \frac{Z_{12}}{Z_{22}} \\ -\frac{Z_{21}}{Z_{22}} & \frac{1}{Z_{22}} \end{bmatrix}$


Table 1



**Question[2]:**

Determine the S.C. Y-parameters for the network shown in figure and sketch the two forms of its equivalent circuit.

Insert your results in Table 2.

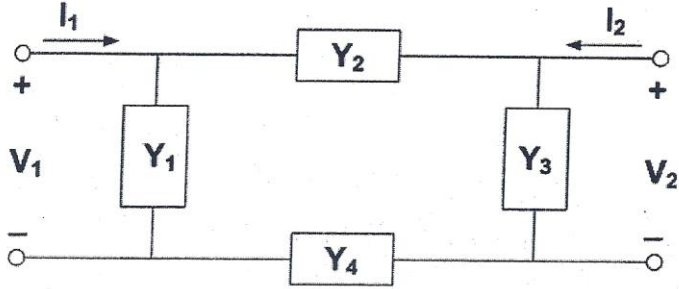

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

at  $V_2 = 0$

$$I_1 = Y_{11} V_1$$

$$I_2 = Y_{21} V_1$$


$$V_1 = \frac{1}{Y_1} * I_1 * \frac{Y_1}{Y_1 + (Y_2 // Y_4)}$$

$$V_1 = \frac{I_1}{Y_1 + (Y_2 // Y_4)}$$

$$\therefore Y_{11} = Y_1 + (Y_2 // Y_4)$$

$$V_1 = \frac{-I_2}{(Y_2 // Y_4)}$$

$$\therefore Y_{21} = -(Y_2 // Y_4)$$

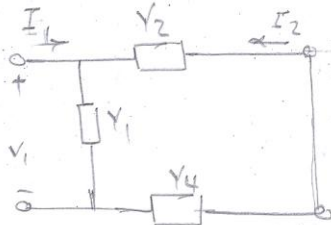



at  $V_1 = 0$

$$I_1 = Y_{12} V_2$$

$$I_2 = Y_{22} V_2$$


$$V_2 = \frac{1}{Y_3} \times I_2 \times \frac{Y_3}{Y_3 + (Y_2 // Y_4)} = \frac{I_2}{Y_3 + (Y_2 // Y_4)}$$

$$\Rightarrow Y_{22} = Y_3 + (Y_2 // Y_4)$$

the network is reciprocal  $\Rightarrow Y_{12} = Y_{21} = -(Y_2 // Y_4)$


$$\therefore [Y] = \begin{bmatrix} Y_1 + (Y_2 // Y_4) & -(Y_2 // Y_4) \\ -(Y_2 // Y_4) & Y_3 + (Y_2 // Y_4) \end{bmatrix}$$

1<sup>st</sup> equivalent circuit

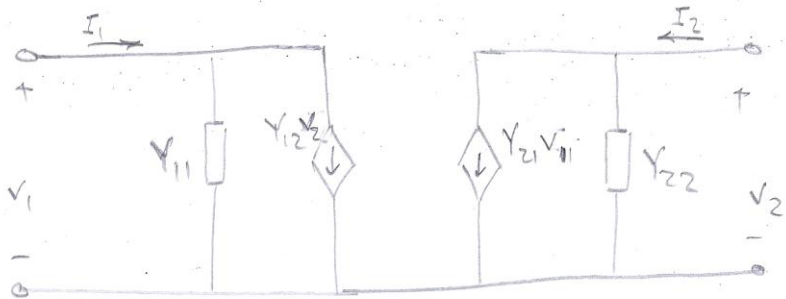



2<sup>nd</sup> equivalent circuit

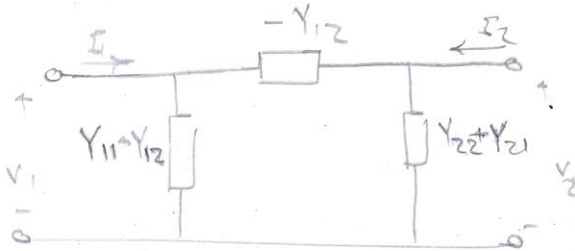



	$\begin{bmatrix} Y_1 + (Y_2 // Y_4) & -(Y_2 // Y_4) \\ -(Y_2 // Y_4) & Y_3 + (Y_2 // Y_4) \end{bmatrix}$


Table 2



**Question/3/:**

For the Hybrid equivalent circuit shown in figure, calculate the current gain  $A_i$  and the voltage gain  $A_v$ .

Insert your results in Table 3.

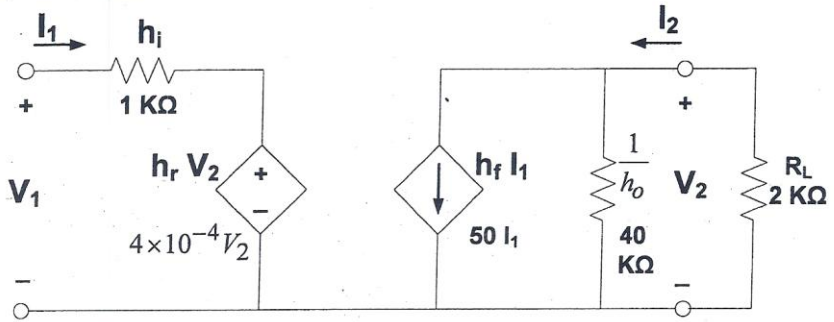

$$V_1 = h_i I_1 + h_r V_2 \quad \rightarrow \textcircled{1}$$

$$I_2 = h_f I_1 + h_o V_2 \quad \rightarrow \textcircled{2}$$

$$V_2 = -I_2 R_L \quad \rightarrow \textcircled{3}$$

Sub From  $\textcircled{3}$  in  $\textcircled{2}$

$$I_2 = h_f I_1 + h_o (-I_2 R_L)$$

$$\therefore I_2 (1 + h_o R_L) = h_f I_1$$

$$A_i = \frac{I_2}{I_1} = \frac{h_f}{1 + h_o R_L}$$

$$\therefore A_i = 47.619$$



$$V_1 = h_i \left( \frac{1+h_o R_L}{h_f} \right) I_2 + h_r V_2$$

$$V_1 = h_i \left( \frac{1+h_o R_L}{h_f} \right) \left( \frac{-V_2}{R_L} \right) + h_r V_2$$

$$V_1 = V_2 \left[ \frac{h_r h_f R_L - h_i (1+h_o R_L)}{h_f R_L} \right]$$

$$A_v = \frac{V_2}{V_1} = \frac{h_f R_L}{h_r h_f R_L - h_i (1+h_o R_L)}$$

$$A_v \approx -99$$





	47.619
	-99.0099


Table 3



**Question[4]:**

For the Z-parameters' equivalent circuit shown in figure, calculate the input and output impedances.

Insert your results in Table 4.

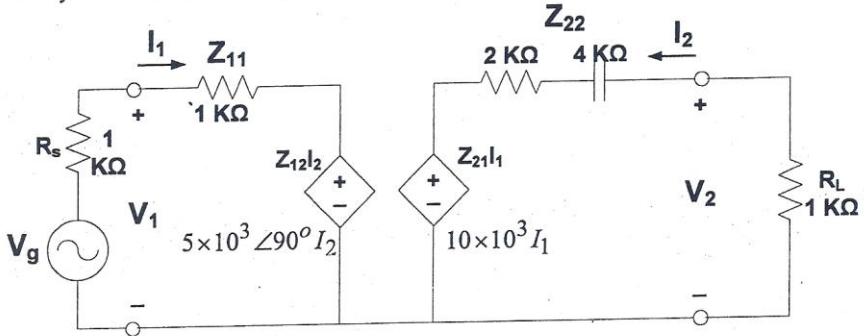

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow \text{①}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow \text{②}$$

$$V_1 = V_g - I_1 R_s \rightarrow \text{③}$$

$$V_2 = -I_2 R_L \rightarrow \text{④}$$

$$Z_{11} = 1 \text{ k}\Omega$$

$$Z_{12} = 5 \text{ j k}\Omega$$

$$Z_{21} = 10 \text{ k}\Omega$$

$$Z_{22} = (2 - \text{j}4) \text{ k}\Omega$$

From ④ → ②

$$-I_2 R_L = Z_{21} I_1 + Z_{22} I_2$$

$$-I_2 (R_L + Z_{22}) = Z_{21} I_1 \quad \therefore I_2 = \frac{-Z_{21}}{R_L + Z_{22}} I_1$$

Sub. in ①

$$V_1 = Z_{11} I_1 + Z_{12} * \frac{-Z_{21}}{R_L + Z_{22}} I_1$$



$$Z_{in} = \frac{V_1}{I_1} = Z_{11} - \frac{Z_{12} Z_{21}}{R_L + Z_{22}}$$

$$\boxed{Z_{in} = (9 - 6j) \text{ k}\Omega}$$

$$Z_0 = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

at  $V_1 = 0$

$$\therefore V_1 = -I_1 R_S$$

$$\therefore -I_1 R_S = Z_{11} I_1 + Z_{12} I_2$$

$$-I_1 (R_S + Z_{11}) = Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + \frac{-Z_{12}}{R_S + Z_{11}} I_2 + Z_{22} I_2$$

$$\therefore Z_0 = Z_{22} - \frac{Z_{12} Z_{21}}{R_S + Z_{11}}$$

$$\boxed{Z_0 = (2 - j29) \text{ k}\Omega}$$





$Z_{in}$	$(9 - j6) \text{ k}\Omega$
$Z_{out}$	$(2 - j29) \text{ k}\Omega$

**Table 4**



**Question [5]:**

The Hybrid H-parameters of a network are given by the following matrix:

$$[H] = \begin{bmatrix} 1 \text{ K}\Omega & 0.0002 \\ 100 & 20 \mu \text{ mho} \end{bmatrix}$$

Calculate the H-parameters of two of such network connected in:

a) Series.

b) Parallel.

Insert your results in Table 5.

$$|H| = 0$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

at  $I_1 = 0$

$$Z_{12} = \frac{V_1}{I_2} = \frac{h_{12}}{h_{22}} = 10$$

$$Z_{22} = \frac{V_2}{I_2} = \frac{1}{h_{22}} = 50 \text{ k}\Omega$$

$$V_1 = h_{12} V_2$$

$$I_2 = h_{22} V_2$$

at  $I_2 = 0$

$$Z_{11} = \frac{V_1}{I_1}$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$-h_{21} I_1 = h_{22} V_2$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{-h_{21}}{h_{22}} = -5 \text{ M}\Omega$$

$$\therefore V_1 = h_{11} I_1 + h_{12} \left( \frac{-h_{21}}{h_{22}} \right) I_1$$

$$\frac{V_1}{I_1} = Z_{11} = \frac{|H|}{h_{22}} = 0$$

$$\therefore [Z] = \begin{bmatrix} 0 & 10 \Omega \\ -5 \text{ M}\Omega & 50 \text{ k}\Omega \end{bmatrix}$$



$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

at  $V_2 = 0$

$$Y_{11} = \frac{I_1}{V_1} = \frac{1}{h_{11}} = 1 \text{ m}\Omega, \quad Y_{21} = \frac{I_2}{V_1} = \frac{h_{21}}{h_{11}} = 0.1 \text{ S}$$

at  $V_1 = 0$

$$Y_{12} = \frac{I_1}{V_2}, \quad Y_{22} = \frac{I_2}{V_2}$$

$$-h_{11} I_1 = h_{12} V_2$$

$$\therefore Y_{12} = \frac{-h_{12}}{h_{11}} = -2 \mu\text{S}$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$I_2 = \frac{-h_{12} h_{21}}{h_{11}} V_2 + h_{22} V_2 \quad \therefore Y_{22} = \frac{1 \text{ H}}{h_{11}} = 0$$

$$\therefore [Y] = \begin{bmatrix} 1 \text{ m}\Omega & -2 \mu\text{S} \\ 0.1 \text{ S} & 0 \end{bmatrix}$$

(a) Series Connection

$$[Z_{eq}] = [Z_1] + [Z_2] = 2[Z] \quad \therefore [Z_{eq}] = \begin{bmatrix} 0 & 20 \Omega \\ -10 \text{ m}\Omega & 100 \text{ k}\Omega \end{bmatrix}$$

(b) Parallel Connection

$$[Y_{eq}] = [Y_1] + [Y_2] = \begin{bmatrix} 2 \text{ m}\Omega & -4 \mu\text{S} \\ 0.2 \text{ S} & 0 \end{bmatrix}$$



$$Z_{22} = \frac{1}{h_{22}} \quad \therefore h_{22} = \frac{1}{Z_{22}} = 10 \mu\text{S}$$

$$Z_{12} = \frac{h_{12}}{h_{22}} \quad \therefore h_{12} = h_{22} Z_{12} = 0.0002$$

$$Z_{21} = \frac{-h_{21}}{h_{22}} \quad \therefore h_{21} = -h_{22} Z_{21} = 100$$

$$Z_{11} = \frac{h_{11}}{h_{22}} = 0 \quad h_{11} h_{22} = h_{12} h_{21} \quad \therefore h_{11} = 2 \text{ k}\Omega$$

$\therefore$  in series connection

$$[H] = \begin{bmatrix} 2 \text{ k}\Omega & 0.0002 \\ 100 & 10 \mu\text{S} \end{bmatrix}$$

$$Y_{11} = \frac{1}{h_{11}} \quad \therefore h_{11} = \frac{1}{Y_{11}} = 500 \Omega$$

$$Y_{21} = \frac{h_{21}}{h_{11}} \quad \therefore h_{21} = 100$$

$$Y_{12} = \frac{-h_{12}}{h_{11}} \quad \therefore h_{12} = -h_{11} Y_{12} = 0.0002$$

$$Y_{22} = \frac{h_{22}}{h_{11}} = 0.4 \text{ mS} \quad \therefore h_{11} h_{22} = h_{12} h_{21} \quad \therefore h_{22} = 0.4 \text{ mS}$$

$\therefore$  in parallel connection

$$[H] = \begin{bmatrix} 500 \Omega & 0.0002 \\ 100 & 0.4 \text{ mS} \end{bmatrix}$$



Series connection	$\begin{bmatrix} 2k\Omega & 0.0002 \\ 100 & 10\mu\text{V} \end{bmatrix}$
Parallel connection	$\begin{bmatrix} 500\Omega & 0.002 \\ 100 & 0.4\text{mV} \end{bmatrix}$


Table 5



**Question[6]:**

Determine the transmission A-parameters for the network shown in figure and write its 2-port equations in the A-form.

Insert your results in Table 6.

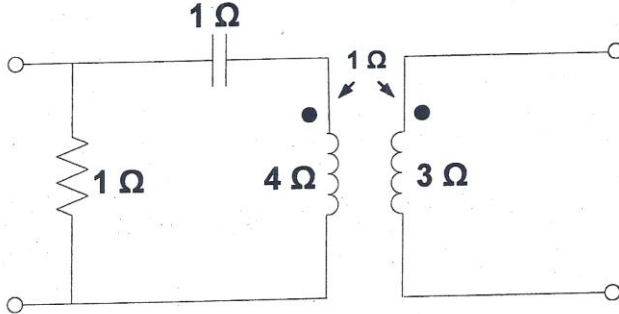

$$V_1 = a_{11} V_2 - a_{12} I_2$$

$$I_1 = a_{21} V_2 - a_{22} I_2$$

ⓐ  $I_2 = 0$

$$V_1 = a_{11} V_2 \quad , \quad I_1 = a_{21} V_2$$


$$V_1 = I_1 * \frac{j3}{1+j3} \rightarrow \textcircled{1}$$

$$V_1 = j2 * I_1 * \frac{1}{1+j3} + V_2$$

$$V_1 = V_1 * \frac{(1+j3)}{j3} * \frac{j2}{(1+j3)} + V_2$$

$$\therefore \frac{V_1}{3} = V_2$$
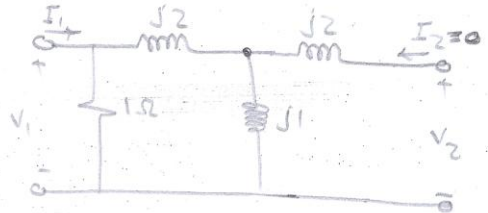
$$\boxed{\therefore a_{11} = \frac{V_1}{V_2} = 3}$$





in eqn ①

$$V_1 = I_1 * \frac{J3}{1+J3}$$

$$3V_2 = I_1 * \frac{J3}{1+J3}$$


$$a_{21} = \frac{I_1}{V_2} = \frac{1+J3}{J}$$

$$\therefore a_{21} = (3-J) \text{ mho}$$

②  $V_2 = 0$

$$V_1 = -a_{12} I_2$$

$$I_1 = -a_{22} I_2$$

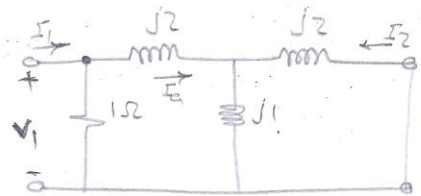

$$I_a = I_1 * \frac{1}{1+J\frac{8}{3}}$$

$$I_a = \frac{3I_1}{3+J8}$$

$$I_2 = -I_a * \frac{J1}{J3} = \frac{-I_a}{3}$$

$$\therefore -I_2 = \frac{-I_1}{3+J8}$$

$$a_{22} = \frac{-I_1}{I_2}$$

$$\therefore a_{22} = 3+J8$$

$$V_1 = J\frac{8}{3} I_a = -J8 I_2$$

$$a_{12} = \frac{-V_1}{I_2} = J8$$

$$\therefore a_{12} = J8 \Omega$$



$$\therefore [A] = \begin{bmatrix} 3 & j8 \\ 3-j & 3+j8 \end{bmatrix}$$




	$\begin{bmatrix} 3 & j8 \\ 3-j & 3+j8 \end{bmatrix}$
	$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 3 & j8 \\ 3-j & 3+j8 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$

Table 6



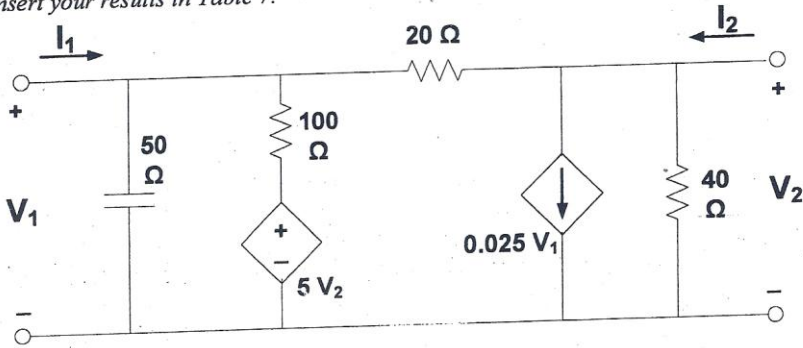**Question[7]:**

For the 2-port network shown in figure, find the transmission A-parameters.  
Insert your results in Table 7.




$$V_1 = a_{11}V_2 - a_{12}I_2$$

$$I_1 = a_{21}V_2 - a_{22}I_2$$

at  $V_2 = 0$

$$V_1 = -a_{12}I_2$$

$$I_1 = -a_{22}I_2$$

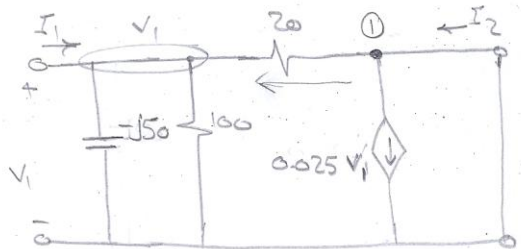

kd at ①

$$I_2 = 0.025V_1 + \frac{0 - V_1}{20} \Rightarrow I_2V_1 = -0.025V_1$$

$$\frac{-V_1}{I_2} = a_{12} \quad \boxed{\therefore a_{12} = 40 \Omega} \quad \Rightarrow V_1 = -40I_2$$

$$V_1 = I_1(20 \parallel 100 \parallel -j50) = I_1(15 - j5)$$

$$-40I_2 = I_1(15 - j5)$$


$$a_{22} = \frac{-I_1}{I_2} = \frac{40}{15 - j5} \Rightarrow \boxed{a_{22} = 2.4 + j0.8}$$



at  $I_2 = 0$

$$V_1 = a_{11} V_2$$

$$I_1 = a_{21} V_2$$

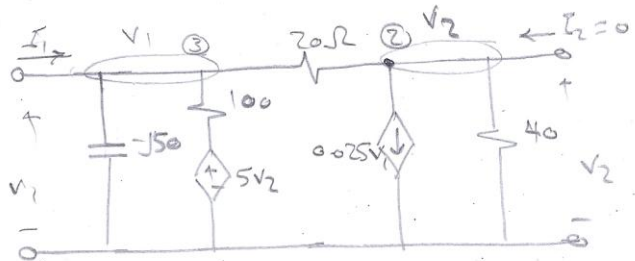

Kcl at point ②

$$\frac{V_2}{40} + 0.025V_1 + \frac{V_2 - V_1}{20} = 0$$

$$\frac{3V_2}{40} = \frac{V_1}{40}$$

$$\therefore V_1 = 3V_2$$

$$\boxed{\therefore a_{11} = 3}$$

Kcl at ③

$$I_1 = \frac{V_1}{-j50} + \frac{V_1 - 5V_2}{100} + \frac{V_1 - V_2}{20}$$

$$I_1 = V_1 \left( \frac{3}{50} + \frac{j}{50} \right) - 0.1V_2$$

$$I_1 = V_2 \left( \frac{9}{50} + \frac{j3}{50} \right) - 0.1V_2$$

$$I_1 = V_2 (0.08 + j0.06)$$

$$\boxed{\therefore a_{21} = (0.08 + j0.06) \Omega}$$



$$2-[A] = \begin{bmatrix} 3 & 40 \\ 0.08 + j0.06 & 2.4 + j0.8 \end{bmatrix}$$





	$\begin{bmatrix} 3 & 40 \\ 0.08 + j0.06 & 24 + j0.8 \end{bmatrix}$
--	--

Table 7




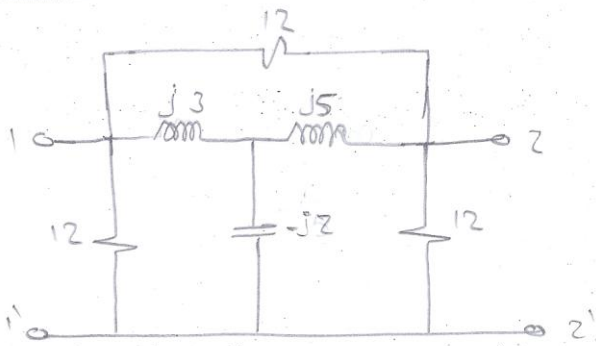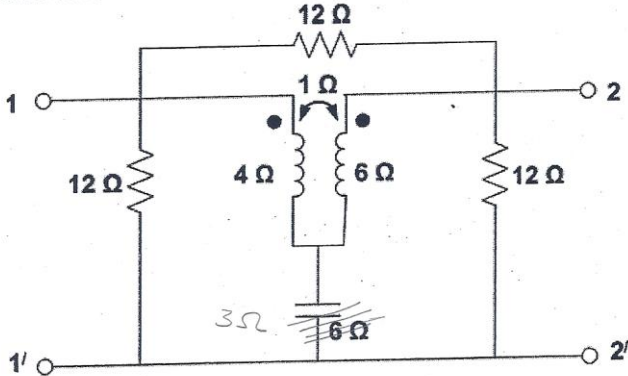**Question[8]:**

Simplify the network shown in figure into two 2-port networks connected in parallel. Hence, calculate the Y-parameters' matrix of the whole network. Insert your results in Table 8.




$$[Y_{eq}] = [Y_1] + [Y_2]$$

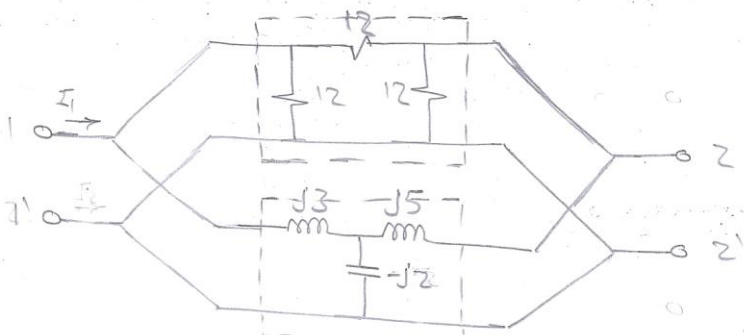



$$I_1 = Y_{11} V_1 + Y_{12} V_2$$


$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

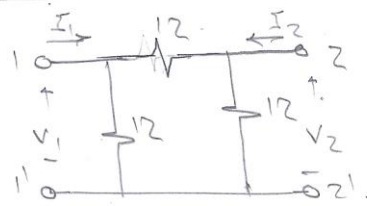

cut  $V_2 = 0$

$$I_1 = Y_{11} V_1$$

$$I_2 = Y_{21} V_1$$

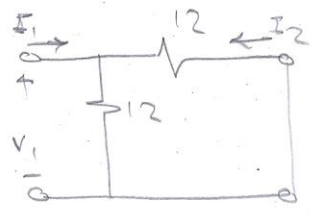

$$V_1 = 12 * I_1 * \frac{12}{24}$$

$$V_1 = 6 I_1 \quad \boxed{\therefore Y_{11} = \frac{1}{6} \text{ S}}$$

$$V_1 = -12 I_2 \quad \boxed{\therefore Y_{21} = \frac{-1}{12} \text{ S}}$$

the network is symmetrical and reciprocal

$$\therefore Y_{11} = Y_{22} = \frac{1}{6} \text{ S}$$

$$Y_{12} = Y_{21} = \frac{-1}{12} \text{ S}$$

$$\therefore [Y_1] = \begin{bmatrix} \frac{1}{6} & \frac{-1}{12} \\ \frac{-1}{12} & \frac{1}{6} \end{bmatrix}$$



$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

@  $V_2 = 0$

$$I_1 = Y_{11} V_1$$

$$I_2 = Y_{21} V_1$$

$$V_1 = j3 * I_1 - j2 * I_1 * \frac{j5}{j5 - j2} = \frac{1}{3j} I_1$$

$$\therefore Y_{11} = 3j$$

$$V_1 = (j3 * I_1) + (j5 * (-I_2))$$

$$V_1 = \left(\frac{3j}{2} - j5\right) I_2 \quad \therefore Y_{21} = 2j$$

the network is reciprocal  $\Rightarrow Y_{12} = Y_{21} = 2j$

at  $V_1 = 0$

$$I_1 = Y_{12} V_2$$


$$I_2 = Y_{22} V_2$$

$$V_2 = j5 I_2 - j2 * I_2 * \frac{j3}{j}$$

$$V_2 = -j I_2$$

$$\therefore Y_{22} = j$$

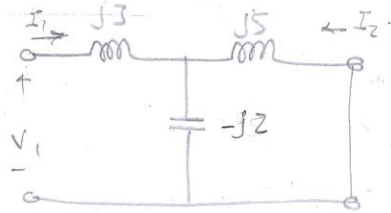
$$\therefore [Y_2] = \begin{bmatrix} 3j & 2j \\ 2j & j \end{bmatrix}$$



$$I_2 = -I_1 * \frac{-j2}{j5 - j2}$$

$$I_2 = \frac{2I_1}{3}$$

$$\therefore I_1 = \frac{3I_2}{2}$$

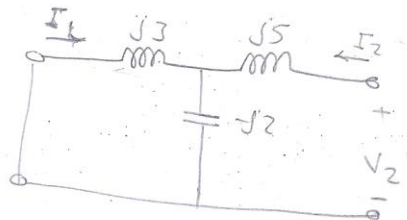



$$\therefore [Y_{eq}] = \begin{bmatrix} \frac{1}{8} + 3j & \frac{-1}{12} + 2j \\ \frac{-1}{12} + 2j & \frac{1}{8} + j \end{bmatrix}$$

	$\begin{bmatrix} (\frac{1}{8} + 3j) & (\frac{-1}{12} + 2j) \\ (\frac{-1}{12} + 2j) & (\frac{1}{8} + j) \end{bmatrix}$
--	---


Table 8



**Question 9:**

Using the Z-parameters, find Thevenin's equivalent circuit with respect to port 2 for the 2-port network shown in figure.

Insert your results in Table 9.

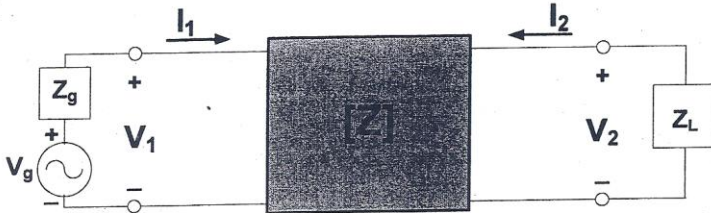

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_1 = V_g - I_1 Z_g$$

$$V_2 = -I_2 Z_L$$

$$V_{Th} = V_2 \Big|_{I_2 = 0}$$

$$\Rightarrow \text{at } I_2 = 0 \Rightarrow$$

$$V_1 = Z_{11} I_1$$

$$V_2 = Z_{21} I_1$$

$$V_1 = V_g - I_1 Z_g$$

$$\therefore V_g - I_1 Z_g = Z_{11} I_1$$

$$V_g = I_1 (Z_{11} + Z_g)$$

$$\therefore I_1 = \frac{V_g}{Z_{11} + Z_g}$$

$$V_2 = Z_{21} I_1 = \frac{Z_{21} V_g}{Z_{11} + Z_g}$$

$$\therefore V_{Th} = \left( \frac{Z_{21}}{Z_{11} + Z_g} \right) V_g$$



$$Z_{Th} = \frac{V_2}{I_2} \Big|_{V_g=0}$$

$$V_1 = -I_1 Z_g$$

$$\therefore -I_1 Z_g = Z_{11} I_1 + Z_{12} I_2$$

$$-I_1 (Z_{11} + Z_g) = Z_{12} I_2$$

$$\therefore I_1 = \frac{-Z_{12}}{Z_{11} + Z_g} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$= \left( \frac{-Z_{12} Z_{21}}{Z_{11} + Z_g} + Z_{22} \right) I_2$$

$$\therefore Z_{Th} = Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11} + Z_g}$$






	$\left( \frac{Z_{21}}{Z_{11} + Z_g} \right) V_g$
	$Z_{22} = \frac{Z_{12} Z_{21}}{Z_{11} + Z_g}$

Table 9



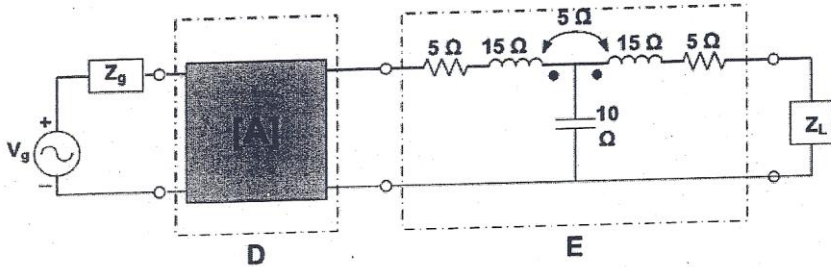**Question[10]:**

The networks **D** and **E** in the circuit shown in figure are reciprocal and symmetrical networks. **D** has  $a_{11}=5$  and  $a_{12}=24 \Omega$ . The impedance  $Z_L$  is adjusted for maximum average power transfer. Find  $Z_L$  if  $Z_g=5 \Omega$ .  
Insert your results in Table 10.



For network D

Symm.  $\Rightarrow a_{11} = a_{22} = 5$


reciprocal  $\Rightarrow a_{11}a_{22} - a_{12}a_{21} = 1 \quad \therefore a_{12} = 12$

$$\therefore [A_D] = \begin{bmatrix} 5 & 24\Omega \\ 12 & 5 \end{bmatrix}$$

For network E

$$V_1 = a_{11}V_2 - a_{12}I_2$$

$$I_1 = a_{21}V_2 - a_{22}I_2$$

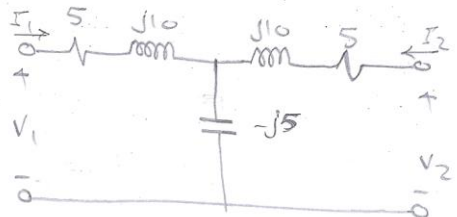

@  $I_2 = 0$

$$V_1 = a_{11}V_2$$

$$I_1 = a_{21}V_2$$

$$V_2 = V_1 \times \frac{-j5}{5+j5}$$

$$\therefore a_{11} = -1+j$$



$$V_1 = (5 + j10)I_1 + V_2$$

$$(-1 + j)V_2 = (5 + j10)I_1 + V_2$$

$$\therefore (-2 + j)V_2 = (5 + j10)I_1$$

$$\therefore a_{21} = 0.2j \Omega$$

the network is symm.  $\Rightarrow a_{11} = a_{22} = (-1 + j)$

reciprocal  $\Rightarrow a_{11}a_{22} - a_{12}a_{21} = 1$


$$\therefore a_{12} = (-10 + j5) \Omega$$

$$\therefore [A_E] = \begin{bmatrix} -1 + j & -10 + j5 \\ 0.2j & -1 + j \end{bmatrix}$$

$$[A] = [A_0][A_E]$$

$$= \begin{bmatrix} 5 & 24 \\ 1 & 5 \end{bmatrix} \begin{bmatrix} -1 + j & -10 + j5 \\ 0.2j & -1 + j \end{bmatrix}$$
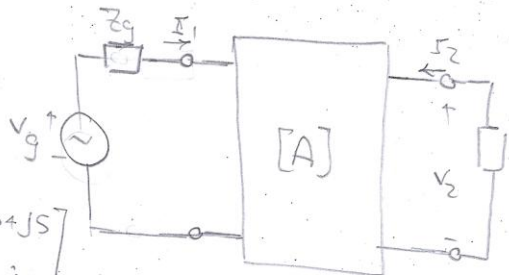
$$[A] = \begin{bmatrix} (-5 + 9.8j) & (-74 + 49j) \\ (-1 + 2j) & (-15 + 10j) \end{bmatrix}$$





$$V_1 = a_{11}V_2 - a_{12}I_2$$

$$I_1 = a_{21}V_2 - a_{22}I_2$$

$$V_1 = V_g - I_1 Z_g$$

$$V_2 = -I_2 Z_L$$

$$Z_{th} = \left. \frac{V_2}{I_2} \right|_{V_g=0}$$

at  $V_g=0 \quad \therefore V_1 = -I_1 Z_g$

$$\therefore -I_1 Z_g = a_{11}V_2 - a_{12}I_2$$

$$\therefore -Z_g (a_{21}V_2 - a_{22}I_2) = a_{11}V_2 - a_{12}I_2$$

$$-(Z_g a_{21} + a_{11}) V_2 = -(Z_g a_{22} + a_{12}) I_2$$

$$\frac{V_2}{I_2} = \frac{Z_g a_{22} + a_{12}}{Z_g a_{21} + a_{11}}$$

$$\therefore Z_{th} = \frac{Z_g a_{22} + a_{12}}{Z_g a_{21} + a_{11}}$$

to receive max. power  $Z_L = Z_{th}^*$

$$Z_{th} = 8.06 \angle 29.6^\circ \Omega$$

$$\therefore Z_L = 8.06 \angle -29.6^\circ \Omega$$



**Question [1]:**

a) Derive an expression of the input and output impedances of the two-port network shown in figure in terms of the H-parameters of the network, the internal impedance of the source  $Z_g$  and the load impedance  $Z_L$ .

b) If the network parameters are given by :

$$[H] = \begin{bmatrix} 1500\Omega & 10^{-3} \\ 50 & 50\mu \text{ mho} \end{bmatrix}$$

$$Z_g = 1500 \Omega$$


$$V_g = 250 \angle 0^\circ \text{ V}$$

Calculate:

i) The maximum average power delivered to the load.

ii) The average power delivered to the input port of the network at the condition of maximum power transfer to the load.

Insert your results in Table 1.

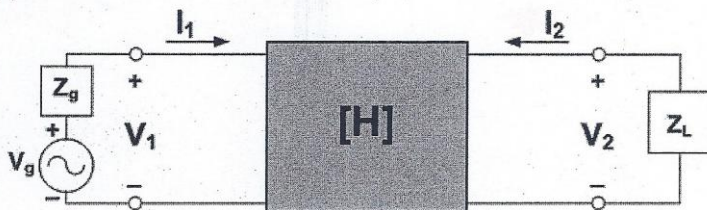

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \rightarrow \textcircled{1}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \rightarrow \textcircled{2}$$

$$V_1 = V_g - I_1 Z_g \quad \rightarrow \textcircled{3}$$

$$V_2 = -I_2 Z_L \quad \rightarrow \textcircled{4}$$

From  $\textcircled{4} \rightarrow \textcircled{2}$


$$I_2 = h_{21} I_1 - h_{22} Z_L I_2$$

$$I_2 = \frac{h_{21} I_1}{1 + h_{22} Z_L}$$

$$I_2 = h_{21} I_1 - h_{22} Z_L I_2 \rightarrow \textcircled{5}$$

in eq.  $\textcircled{1}$   $V_1 = h_{11} I_1 - \frac{h_{12} h_{21} Z_L}{1 + h_{22} Z_L} I_1$

$$\therefore Z_{in} = \frac{V_1}{I_1} = h_{11} - \frac{h_{12} h_{21} Z_L}{1 + h_{22} Z_L}$$

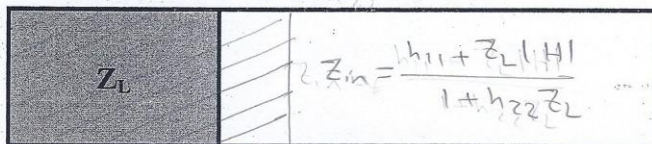

**Table 10**



$$Z_0 = \left. \frac{V_2}{I_2} \right|_{V_g=0}$$

$$\text{at } V_g=0 \Rightarrow V_1 = -I_1 Z_g$$

in equation ①

$$-I_1 Z_g = h_{11} I_1 + h_{12} V_2$$

$$\therefore I_1 = \frac{-h_{12}}{h_{11} + Z_g} V_2$$

in equation ②

$$I_2 = \frac{-h_{12} h_{21}}{h_{11} + Z_g} V_2 + h_{22} V_2$$

$$I_2 = \left( \frac{|H| + h_{22} Z_g}{h_{11} + Z_g} \right) V_2$$


$$\therefore Z_0 = \frac{h_{11} + Z_g}{|H| + h_{22} Z_g}$$

$$Z_0 = Z_L \quad \text{at max Power transfer}$$

$$\therefore Z_L = 30k\Omega$$

$$\therefore Z_{in} \Big|_{\text{max Power}} = 900\Omega$$
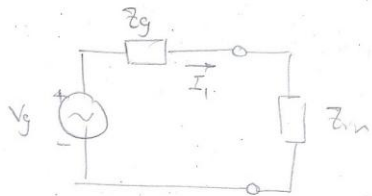
$$I_1 = \frac{V_g}{Z_g + Z_{in}} = 0.104 \text{ A}$$



From equation ⑤

$$V_2 = \frac{-h_{21} Z_L I_1}{1 + h_{22} Z_L}$$

$$\therefore V_2 = -62400 \text{ Volts}$$

$$P_{L \text{ max}} = \frac{|V_2|^2}{Z_L} = 130 \text{ Kwatts}$$



$$P_{in} = |I_1|^2 Z_{in}$$
$$= 9.7344 \text{ watts}$$



$Z_{in}$	$\frac{h_{11} + Z_L  h_1 }{1 + h_{22} Z_L}$
$Z_{out}$	$\frac{h_{11} + Z_g}{ h_1  + h_{22} Z_g}$
$P_L$	130 $\mu$ watts
$P_{in}$	9.7344 watts

Table 1




**Question[2]:**

The H-parameters of a two-port network are given by the matrix :

$$[H] = \begin{bmatrix} 2\ \Omega & 0.2 \\ -4 & 0.1\ \text{mho} \end{bmatrix}$$

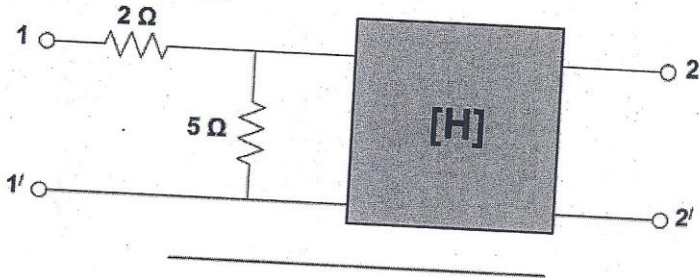
- Check the conditions of symmetry and reciprocity of the network.
- Sketch its equivalent circuit.
- If two resistors of  $2\ \Omega$  and  $5\ \Omega$  are added to the network as shown in figure, calculate the H-parameters of the total network. Insert your results in Table 2.



a) For reciprocity  $h_{12} = -h_{21} \Rightarrow$  not satisfied  
 $\therefore$  the network is not reciprocal.

For symmetry  $|H| = 1 \Rightarrow 2 \times 0.1 + 0.2 \times 4 = 1$  satisfied  
 $\therefore$  the network is symmetric

b)

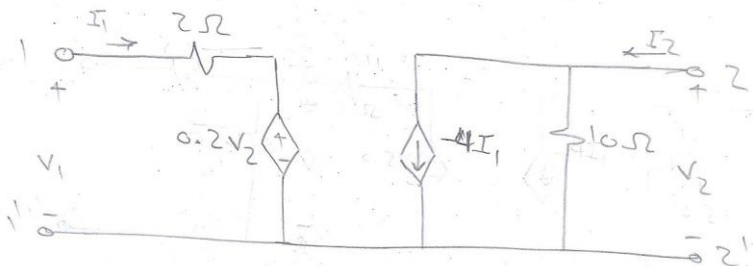


$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$



(C)

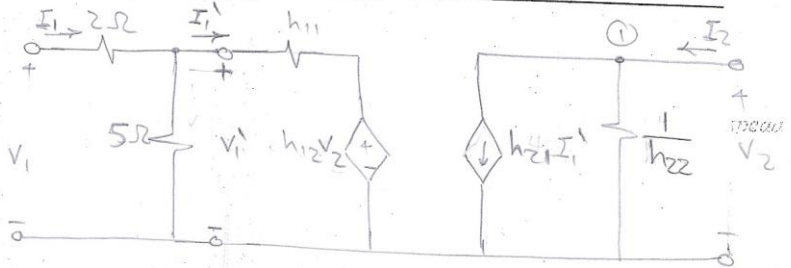

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

① at  $I_1 = 0$

$$V_1 = h_{12} V_2$$

$$I_2 = h_{22} V_2$$

$$V_1 = V_1'$$

$$V_1 = h_{12} V_2 * \frac{5}{5+h_{11}}$$

$$\Rightarrow h_{12} = \frac{V_1}{V_2} = \frac{5 \cdot h_{12}}{5+h_{11}}$$

$$\boxed{h_{12} = \frac{1}{7}}$$

kel at node ①

$$I_2 = h_{22} V_2 + h_{21} I_1'$$

$$I_1' = \frac{-h_{12} V_2}{5+h_{11}}$$

$$\therefore I_2 = \left( h_{22} - \frac{h_{12} h_{21}}{5+h_{11}} \right) V_2$$

$$\Rightarrow h_{22} = \frac{I_2}{V_2}$$

$$\therefore h_{22} = h_{22} - \frac{h_{12} h_{21}}{5+h_{11}}$$


$$\boxed{h_{22} = \frac{3}{14} \Omega}$$



at  $v_2 = 0$

$$V_1 = h_{11} I_1$$

$$I_2 = h_{21} I_1$$

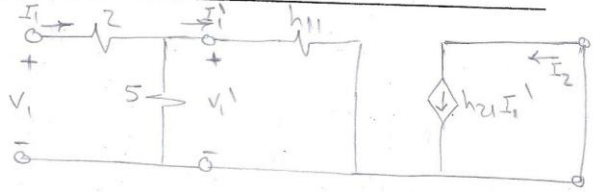

$$V_1 = I_1 * [Z + (5 // h_{11})]$$

$$h_{11} = \frac{V_1}{I_1}$$

$$\therefore h_{11} = 2 + (5 // h_{11})$$

$$\Rightarrow h_{11} = \frac{24}{7} \Omega$$

$$I_2 = h_{21} I_1'$$

$$I_1' = I_1 * \frac{5}{5 + h_{11}}$$

$$\therefore I_2 = I_1 * \frac{5 h_{21}}{5 + h_{11}}$$

$$h_{21} = \frac{I_2}{I_1}$$

$$\therefore h_{21} = \frac{5 h_{21}}{5 + h_{11}}$$

$$\Rightarrow h_{21} = \frac{-20}{7}$$



<i>Is the net. sym. ?</i>	yes
<i>Is the net. recip. ?</i>	no
<i>Equivalent Circuit</i>	
[H]	$\begin{bmatrix} \frac{24}{7} & \frac{1}{7} \\ -\frac{20}{7} & \frac{3}{14} \end{bmatrix}$

Table 2



**Question[3]:**

a) Calculate the transmission A-parameters of a two-port network as a function of its Hybrid H-parameters.


b) The amplifier circuit shown in figure is formed of two identical stages each having the Hybrid H-parameters given by :

$$[H] = \begin{bmatrix} 1 \text{ K}\Omega & 0.001 \\ 100 & 0.1 \text{ m.mho} \end{bmatrix}$$

$$|H| = 0$$

What is the value of the input voltage  $V_s$  required to obtain an output voltage  $V_o$  of 25 volts ?

Insert your results in Table 3.

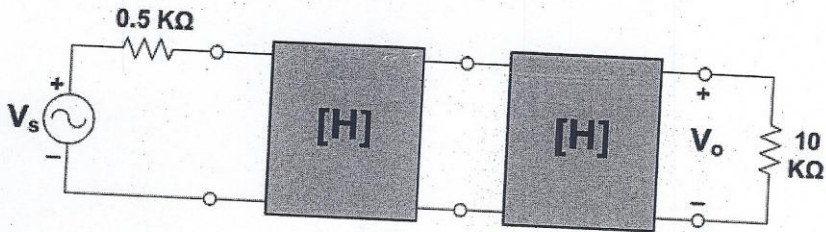

$$\begin{aligned} V_1 &= a_{11} V_2 - a_{12} I_2 \\ I_1 &= a_{21} V_2 - a_{22} I_2 \end{aligned}$$

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$

at  $V_2 = 0$

$$\begin{aligned} V_1 &= h_{11} I_1 \\ I_2 &= h_{21} I_1 \end{aligned}$$

$$\begin{aligned} a_{12} &= \frac{-V_1}{I_2} = \frac{-h_{11} I_1}{h_{21} I_1} = \frac{-h_{11}}{h_{21}} \\ a_{22} &= \frac{-I_1}{I_2} = \frac{-1}{h_{21}} \end{aligned}$$

at  $I_2 = 0$

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ h_{21} I_1 &= -h_{22} V_2 \end{aligned}$$

$$a_{21} = \frac{I_1}{V_2} = \frac{-h_{22}}{h_{21}}$$




$$v_1 = 1 - \frac{h_{11} h_{22}}{h_{21}} v_2 + h_{12} v_2 = \frac{-1 \text{ H}}{h_{21}} v_2$$

$$a_{11} = \frac{v_1}{v_2} = \frac{-1 \text{ H}}{h_{21}}$$

$$\therefore [A] = \begin{bmatrix} 0 & -10 \\ -10^{-6} & -0.01 \end{bmatrix}$$
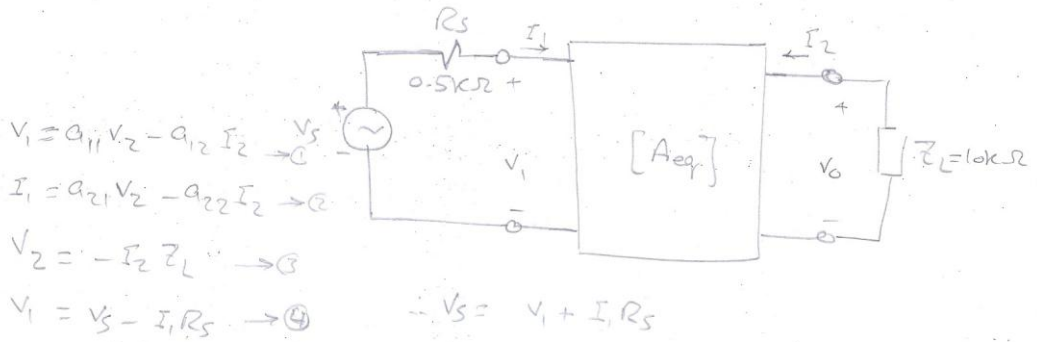
$$[A_{eq}] = [A][A] = \begin{bmatrix} 10^{-5} & 0.1 \\ 10^{-8} & 1.1 \times 10^{-4} \end{bmatrix}$$



sub. from eq  $\textcircled{3}$  in eq  $\textcircled{1}$ ,  $\textcircled{2}$

$$v_1 = a_{11} v_2 + \frac{a_{12}}{Z_L} v_2 \quad \therefore v_1 = \left( a_{11} + \frac{a_{12}}{Z_L} \right) v_2$$

$$v_1 = 5 \times 10^{-4} \text{ volts}$$



$$I_1 = a_{21} V_2 + \frac{a_{22}}{Z_2} V_2$$

$$-I_1 = \left( a_{21} + \frac{a_{22}}{Z_2} \right) V_2$$

$$-I_1 = 5.25 \times 10^{-7} \text{ A}$$

$$V_S = V_1 + I_1 R_S$$

$$V_S = 7.625 \times 10^{-4} \text{ Volts}$$



[A]	$\begin{bmatrix} \frac{-1h1}{h21} & \frac{-h11}{h21} \\ \frac{-h22}{h21} & \frac{-1}{h21} \end{bmatrix}$
$V_s$	$7.625 \times 10^{-4} \text{ Volts}$

Table 3



**Question[4]:**

a) Two sets of measurements were made on the two-port network  $N$  shown in figure. The results were as follows:

Measurement 1

$V_1 = 20 \text{ mV}$

$I_1 = 20 \mu\text{A}$

$V_2 = 40 \text{ V}$

$I_2 = 0$

Measurement 2

$V_1 = 4 \text{ V}$


$I_1 = 5 \text{ mA}$

$V_2 = 0$

$I_2 = -200 \text{ mA}$

Find the H-parameters representing the two-port network.

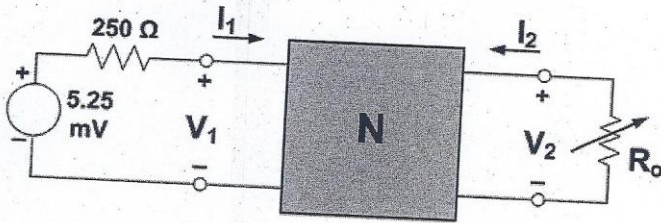b) Using the H-parameters, calculate the value of the variable resistance  $R_o$  when adjusted to receive maximum power and find the value of this power. Insert Your results in Table 4.



$V_1 = h_{11} I_1 + h_{12} V_2$

$I_2 = h_{21} I_1 + h_{22} V_2$

For Measurement 2

$V_2 = 0$

$\therefore V_1 = h_{11} I_1$

$I_2 = h_{21} I_1$

$h_{11} = \frac{V_1}{I_1} = 800 \Omega$

$h_{21} = \frac{I_2}{I_1} = \frac{-200}{5} = -40$

For Measurement 1

$I_2 = 0$

$V_1 = h_{11} I_1 + h_{12} V_2$

$h_{21} I_1 = -h_{22} V_2$

$h_{12} = \frac{V_1 - h_{11} I_1}{V_2} = 10^{-4}$

$h_{22} = \frac{-h_{21} I_1}{V_2} = 2 \times 10^{-5}$



$$\therefore [H] = \begin{bmatrix} 800 \Omega & 10^{-4} \\ -40 & 2 \times 10^{-5} \Omega \end{bmatrix}$$

$$\text{[b]} \quad V_1 = h_{11} I_1 + h_{12} V_2 \quad \rightarrow \text{①}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \rightarrow \text{②}$$

$$V_2 = -I_2 Z_L \quad \rightarrow \text{③}$$

$$V_1 = V_g - I_1 Z_g \quad \rightarrow \text{④}$$

to receive Maximum Power  $Z_L = Z_{Th}^*$

$$Z_{Th} = \left. \frac{V_2}{I_2} \right|_{V_g=0} \quad \text{at } V_g=0 \Rightarrow V_1 = -I_1 Z_g$$

$$\text{at equation ①} \quad -I_1 Z_g = h_{11} I_1 + h_{12} V_2$$

$$-I_1 (Z_g + h_{11}) = h_{12} V_2$$

$$\therefore I_1 = \frac{-h_{12} V_2}{h_{11} + Z_g}$$

at equation ②

$$I_2 = \frac{-h_{12} h_{21} V_2}{h_{11} + Z_g} + h_{22} V_2$$

$$I_2 = \left( \frac{h_{11} h_{22} - h_{12} h_{21} + h_{22} Z_g}{h_{11} + Z_g} \right) V_2 = \left( \frac{|H| + h_{22} Z_g}{h_{11} + Z_g} \right) V_2$$

$$Z_{Th} = \frac{V_2}{I_2} = \frac{h_{11} + Z_g}{|H| + h_{22} Z_g} = 42 \text{ k}\Omega$$



$$\therefore R_0 = 42 \text{ k}\Omega$$

$$V_{th} = V_2 \Big|_{I_2=0} \quad \therefore h_{21} I_1 = -h_{22} V_2$$

$$\therefore I_1 = \frac{-h_{22}}{h_{21}} V_2$$

in equation ①  $V_1 = h_{11} I_1 + h_{12} V_2$

$$V_g - I_1 Z_g = h_{11} I_1 + h_{12} V_2$$

$$V_g = I_1 (h_{11} + Z_g) + h_{12} V_2$$

$$V_g = V_2 \left[ h_{12} - \frac{h_{22} (h_{11} + Z_g)}{h_{21}} \right]$$

$$V_g = V_2 \left[ \frac{h_{12} h_{21} - h_{22} h_{11} - h_{22} Z_g}{h_{21}} \right]$$

$$V_g = -V_2 \left[ \frac{|H| + h_{22} Z_g}{h_{21}} \right]$$

$$\therefore V_2 = \frac{-h_{21} V_g}{|H| + h_{22} Z_g} = 8.4 \text{ volts}$$

$\therefore V_{th} = 8.4 \text{ volts}$

$$P_{max} = \frac{1}{4} \frac{V_{th}^2}{R_{th}} = \frac{(8.4)^2}{4 \times 42 \times 10^3} = 4.2 \times 10^{-4} \text{ watts}$$



$[H]$	$\begin{bmatrix} 800 \Omega & 10^{-4} \\ -40 & 2 \times 10^{-5} \end{bmatrix}$
$R_o$	$42 \text{ k}\Omega$
$P_{max}$	$4.2 \times 10^{-4} \text{ watts}$

**Table 4**