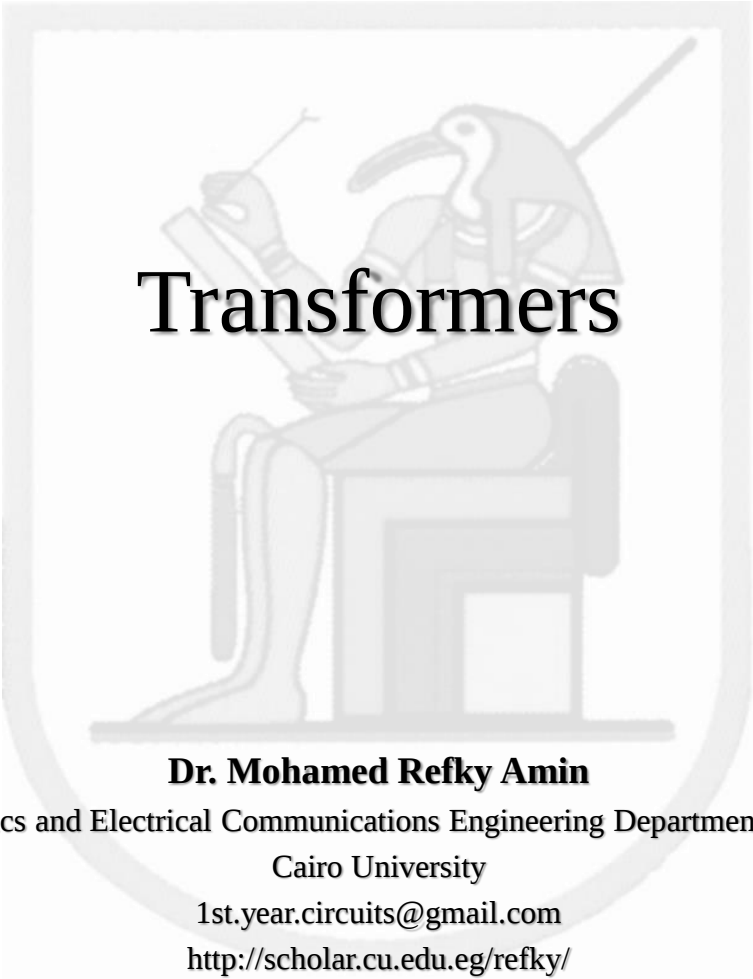




Transformers

Dr. Mohamed Refky Amin

Electronics and Electrical Communications Engineering Department (EECE)

Cairo University

1st.year.circuits@gmail.com

<http://scholar.cu.edu.eg/refky/>

Outline of This Lecture

- Introduction
- Linear Transformer
- Ideal Transformer

Transformers

Introduction

A transformer is a magnetic device that takes advantage of the phenomenon of mutual inductance.

A transformer is generally a four-terminal device comprising two magnetically coupled coils.




Transformers

Linear Transformer

A transformer is linear if the coils are wound on a magnetically linear material (has a constant magnetic permeability).

Most materials are magnetically linear (air, plastic, Bakelite, and wood).

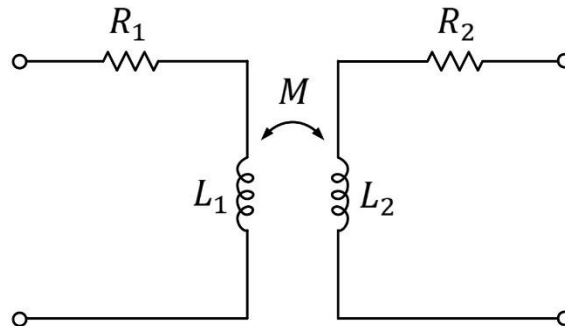Linear transformers are used in radio and TV sets.




Transformers

Linear Transformer

The coil that is directly connected to the voltage source is called the primary coil.

The coil connected to the load is called the secondary coil.

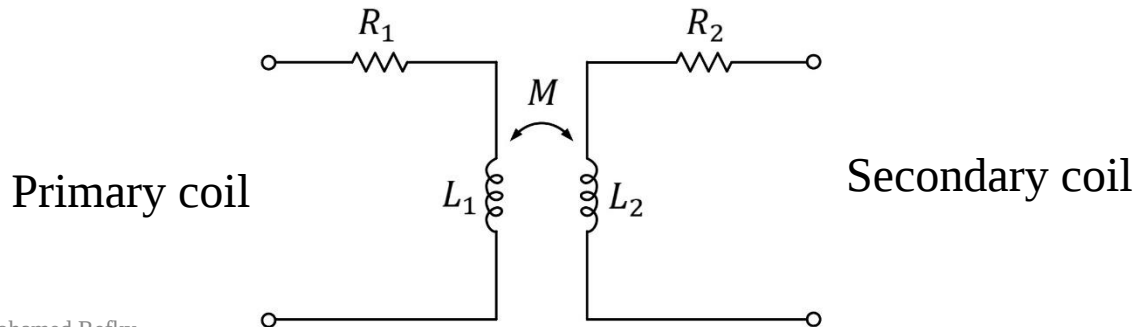R_1 and R_2 are included to account for the power dissipation in the coils.




Transformers

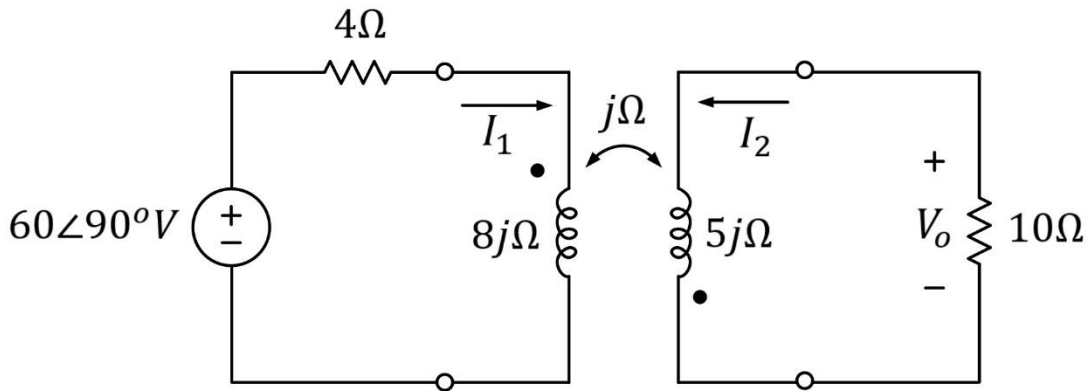Example (1)

For the linear transformer shown below, find I_1 , I_2 , and V_o using

- The direct solution method
- the T-equivalent circuit



Transformers


Linear Transformer

Input Impedance & Reflected Impedance

$$V_1 = I_1(R_1 + j\omega L_1) \pm j\omega M I_2$$

$$0 = I_2(R_2 + Z_L + j\omega L_2) \pm j\omega M I_1$$

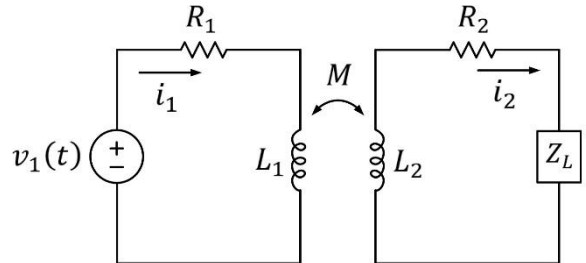Z_{in} governs the behavior of the primary circuit.



$$Z_{in} = \frac{V_1}{I_1} = (R_1 + j\omega L_1) \pm j\omega M \frac{I_2}{I_1}$$

Form the second equation


$$I_2 = \frac{\mp j\omega M I_1}{R_2 + Z_L + j\omega L_2} = \frac{\mp j\omega M I_1}{Z_{Secondary}}$$

Transformers

Linear Transformer

Input Impedance & Reflected Impedance
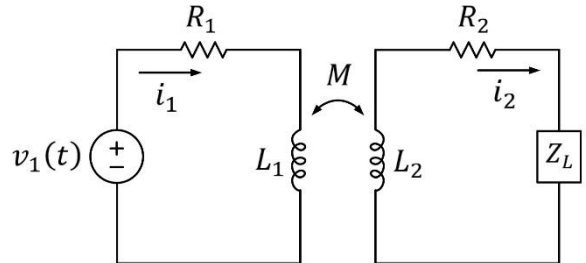
$$\begin{aligned} Z_{in} &= (R_1 + j\omega L_1) + \frac{\omega^2 M^2}{Z_{Secondary}} \\ &= Z_{Primary} + \frac{\omega^2 M^2}{Z_{Secondary}} \\ &= Z_{Primary} + Z_{Reflected} \end{aligned}$$



Transformers


Ideal Transformer

Ideal transformer is the limiting case of the two coupled ideal inductors ($R_1 = R_2 = 0$) and the coupling is perfect ($k = 1$).

Because $k = 1$, when a sinusoidal voltage is applied, the same magnetic flux goes through both coils.

According to Faraday's law, the voltage across the primary coil is given by

$$v_1(t) = N_1 \frac{d\phi}{dt}$$

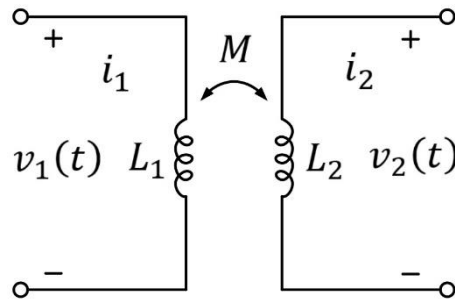

Transformers

Ideal Transformer

According to Faraday's law, the voltage across the secondary coil is given by


$$v_2(t) = N_2 \frac{d\phi}{dt}$$

$$\frac{v_1(t)}{v_2(t)} = \frac{V_1}{V_2} = \frac{N_1}{N_2} = a$$

From the conservation of power

$$S_1 = S_2 \rightarrow V_1 I_1^* = V_2 I_2^*$$
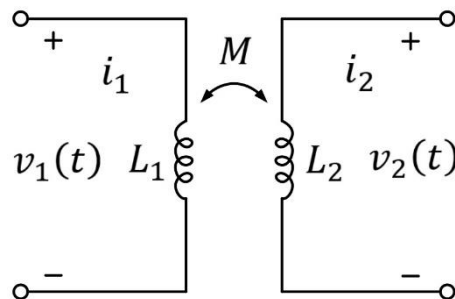
$$\frac{I_2}{I_1} = \frac{V_1}{V_2} = a$$



Transformers


Ideal Transformer

The assumptions of the ideal transformer are

- The coils are lossless (resistance of the cables are zero).
- The coils are perfectly coupled ($k = 1$).
- $L_1, L_2, M \rightarrow \infty$

An ideal transformer is a unity-coupled, lossless transformer in which the primary and secondary coils have infinite self-inductances.

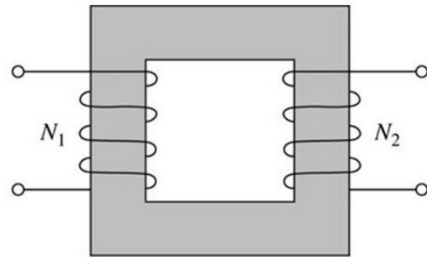Iron-core transformers are close approximations to ideal transformers.




Transformers

Ideal Transformer

The assumptions of the ideal transformer are

- The coils are lossless (resistance of the cables are zero).
- The coils are perfectly coupled ($k = 1$).
- $L_1, L_2, M \rightarrow \infty$

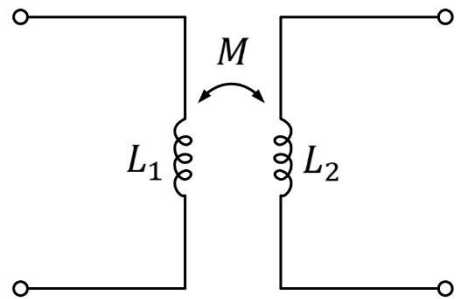The vertical lines between the coils indicate an iron core as distinct from the air core used in linear transformers.



Transformers

Ideal Transformer

Step-up and Step-down Transformer

A step-up transformer is one whose secondary voltage is greater than its primary voltage

$$V_2 > V_1 \rightarrow a < 1 \rightarrow N_1 < N_2 \rightarrow I_2 < I_1$$

A step-down transformer is one whose secondary voltage is less than its primary voltage

$$V_2 < V_1 \rightarrow a > 1 \rightarrow N_1 > N_2 \rightarrow I_2 > I_1$$


Transformers

Ideal Transformer

Voltages Polarity and Currents Direction

If V_1 and V_2 are both positive or both negative at the dotted terminals, the ratio is positive. Otherwise, the ratio is negative.

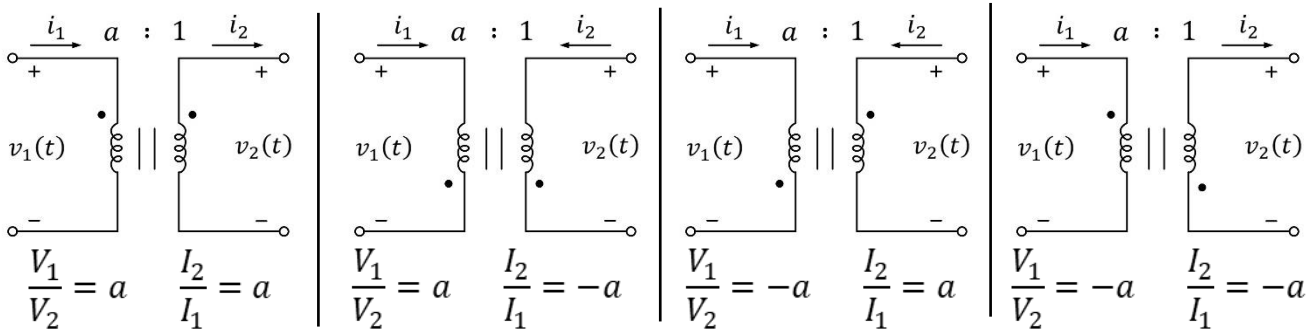If I_1 and I_2 both enter into or both leave the dotted terminals, the ratio is negative. Otherwise, the ratio is positive.




Transformers

Ideal Transformer

Referred Impedance – Refer to Primary
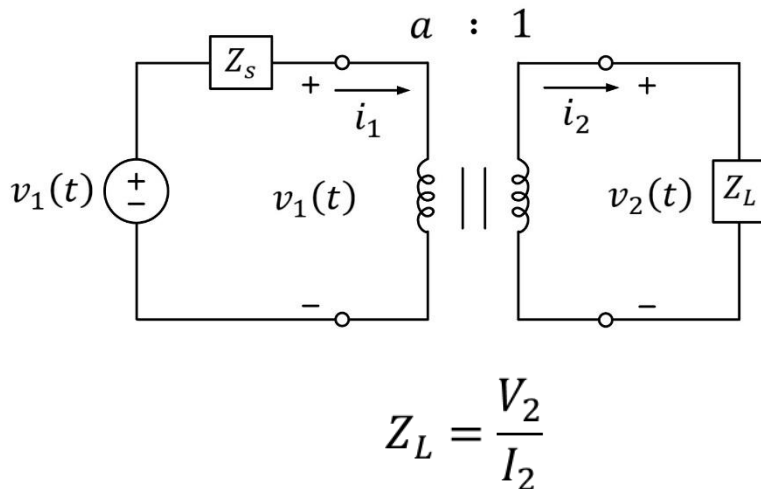
$$\begin{aligned} Z_{in} &= \frac{V_1}{I_1} \\ &= \frac{a \times V_2}{I_2/a} \\ &= a^2 \frac{V_2}{I_2} \\ &= a^2 Z_L \end{aligned}$$



Z_L appears in the primary circuit as $a^2 Z_L$


Transformers

Ideal Transformer

Referred Impedance – Refer to Primary

In refer to primary, the primary and the secondary are connected as one circuit and the secondary elements are replaced as
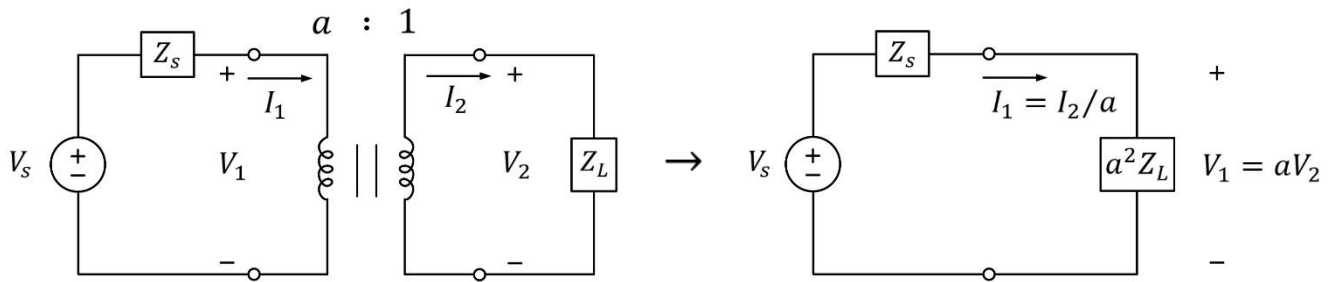
$$Z_L \rightarrow a^2 Z_L, \quad V_2 \rightarrow V_1 = aV_2, \quad I_2 \rightarrow I_1 = I_2/a$$




Transformers

Ideal Transformer

Referred Impedance – Refer to Primary

Load power is given by

$$P_{Z_L} = |I_2|^2 \times \operatorname{Re}\{Z_L\} = |I_1|^2 \times \operatorname{Re}\{a^2 Z_L\}$$

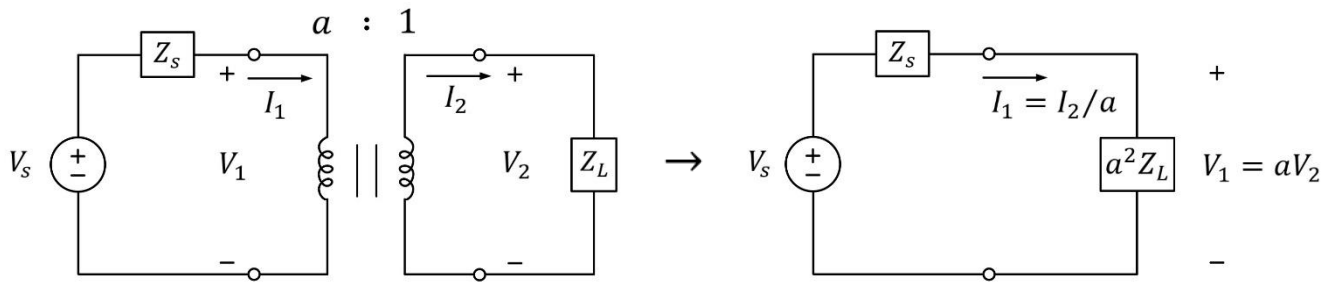


Transformers

Ideal Transformer

Referred Impedance – Refer to Secondary

$$\begin{aligned} Z_{th} &= \left. \frac{V_2}{I_2} \right|_{V_s=0, Z_L=\infty} \\ &= \frac{V_1/a}{a \times I_1} \\ &= \frac{1}{a^2} \frac{V_1}{I_1} \\ &= Z_s/a^2 \end{aligned}$$

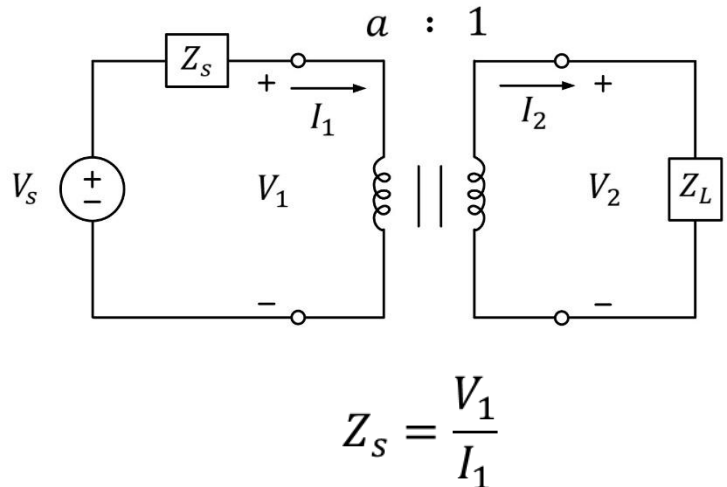

Z_s appears in the secondary circuit as Z_s/a^2

Transformers

Ideal Transformer


Referred Impedance – Refer to Secondary

$$V_{th} = V_2 \Big|_{I_2=0}$$

$$I_2 = 0 \rightarrow I_1 = 0$$

$$V_1 = V_s$$

$$V_2 = \frac{V_1}{a} = \frac{V_s}{a}$$

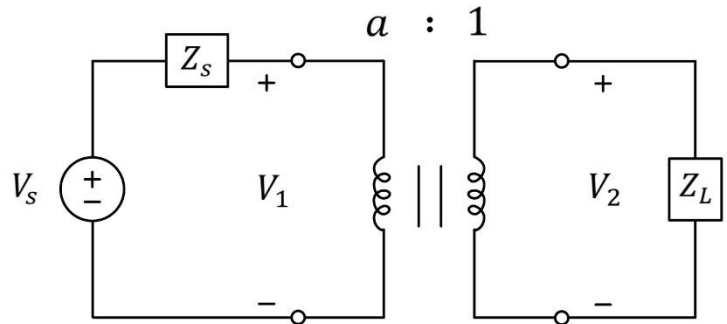

V_s appears in the secondary circuit as V_s/a


Transformers

Ideal Transformer

Referred Impedance – Refer to Secondary

In refer to secondary, the primary and the secondary are connected as one circuit and the secondary elements are replaced as
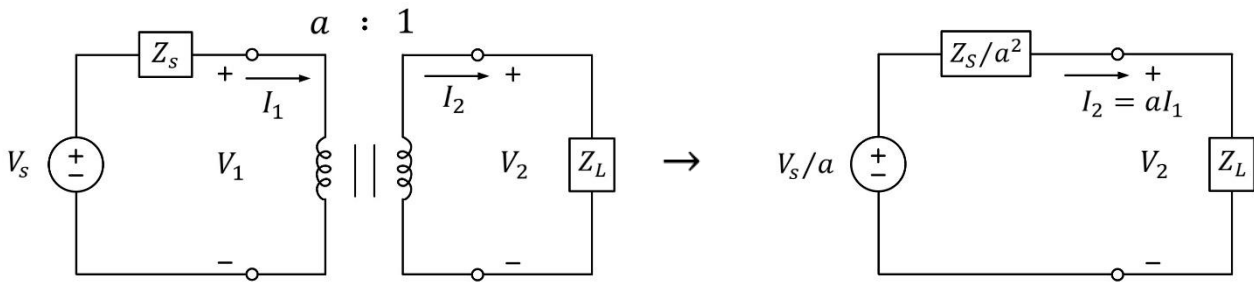
$$Z_S \rightarrow Z_S/a^2, \quad V_S \rightarrow V_S/a, \quad I_1 \rightarrow I_2 = a \times I_1$$




Transformers

Ideal Transformer

Referred Impedance

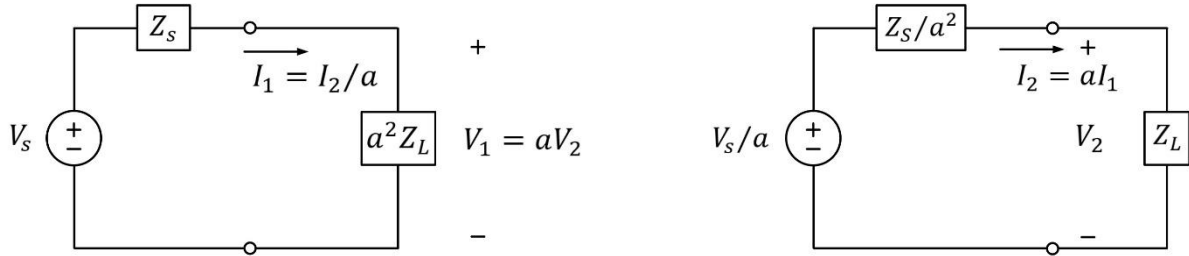
Referred impedance (either refer to primary or refer to secondary) simplifies the solution of the transformer circuit and simplifies the maximum power transform calculations.



Transformers

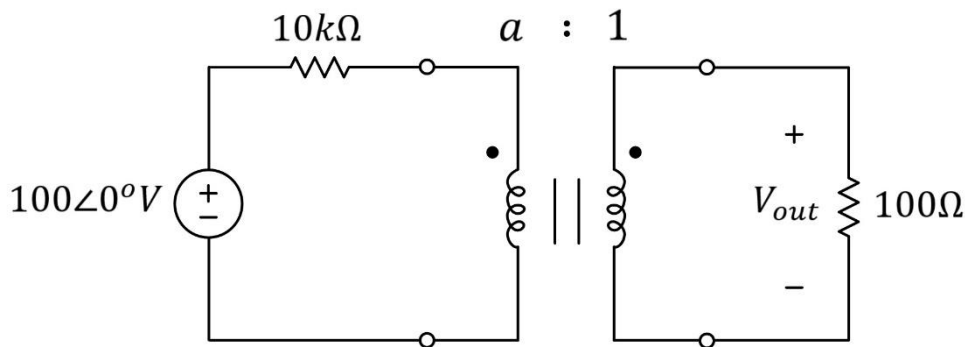Example (2)


For the circuit shown below, find a , P_{max} , and V_{out} to get a maximum power for the load 100Ω .



Transformers

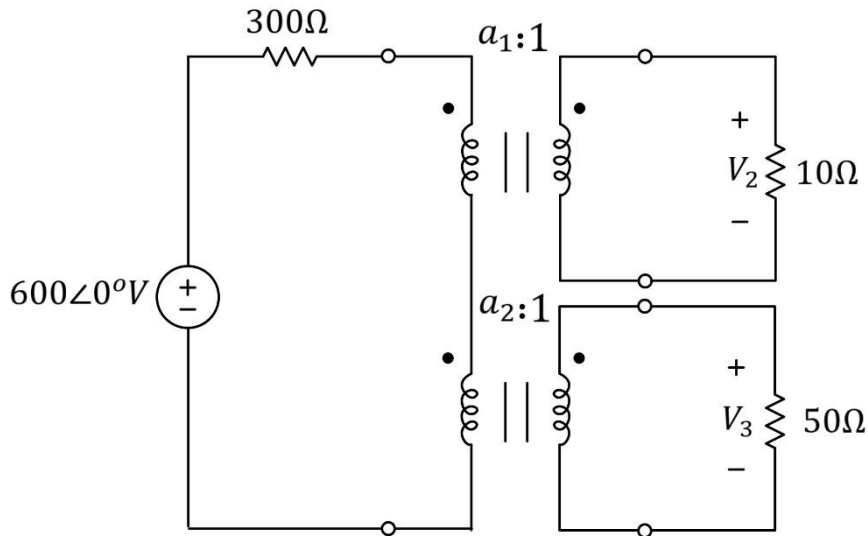Example (3)

For the circuit shown below, find a_1 , and a_2 , such that $P_{10\Omega} = 5P_{50\Omega}$ using matching transform. Then, get V_2 and V_3 .



Transformers

Example (4)

For the circuit shown below, find a_1 , and a_2 , such that Z_L get maximum power. Then, get V_1 and V_4 .

