



- [1] Find the Exponential Fourier Series representation for the signal $f(t)=2t$ over the interval $(0,1)$.
- [2] Represent the signal $f(t) = e^{-t}$ over the interval $(0,1)$ using :
- The Exponential Fourier Series .
 - The Trigonometric Fourier Series .
- Compare your results .
- [3] Find the Exponential and Trigonometric Fourier Series representation for :
- The symmetric square wave shown in Fig.1 .
 - The waveform shown in Fig.2 .
- [4] Determine the average power of the signal $f(t) = 2 \cos(200t)$ and draw its single and double-sided amplitude and phase spectra .
- [5] A periodic gate signal , $f(t)$, is applied to the input of a system having the transfer function shown in Fig.3 . If the input signal is given by :
- $$f(t) = \sum_{n=-\infty}^{\infty} (A\tau/T) \left| \frac{\sin(n\omega_0\tau/2)}{(n\omega_0\tau/2)} \right| e^{jn\omega_0 t}$$
- Where τ is the pulse width and T is the period of the signal . Calculate the output of the System .
- [6] The system $H(\omega) = -\omega^2/(1+\omega^2)$ is used to filter the signal shown in Fig.4 . Determine the series expression for the output signal and calculate the output power contained in the first three components .
- [7] A given amplifier is tested with a sinusoidal input signal of 500 Hz having 2mV peak amplitude . If the output was found to be the symmetrical square wave with unit peak amplitude shown in Fig.1 . Calculate the Total Harmonic Distortion (T.H.D.) and the Linear Gain of the amplifier .
- [8] The output of a simple rectifier circuit with a smoothing capacitor and a resistive load is shown in Fig.5 :
- Find the Exponential Fourier Series for this waveform .
 - Sketch its amplitude and phase spectra (for $n \leq 5$) .
 - Calculate the percentage of the total average power contained in the fundamental .

- [9] A voltage signal $v(t)$ supplies a circuit containing a series connection of a resistance R of 100Ω , a coil L of $0.5H$ and a condenser C of $12.5\mu F$. If the voltage signal is :
 $v(t) = 100 \sin(200t) + 50 \sin(400t) + 30 \sin(600t)$ V
 a) Calculate the expression of the current in the time domain $i(t)$.
 b) Sketch the amplitude and phase spectra of the current.
 c) Find the effective values of the current and voltage.




- [10] The single-sided amplitude and phase spectra of a periodic function $f(t)$ are shown in Fig. 6a, b. Determine the time domain expression of the function if $T=0.1$ sec and sketch its double-sided amplitude and phase spectra.

- [11] Determine and sketch the first four terms of the amplitude and phase spectra of the periodic voltage signal given by :
 $v(t) = (1-t^2) \quad -1 \leq t \leq 1$

- [12] The current in a $10mH$ inductance has the waveform shown in Fig. 7. Obtain the Trigonometric Fourier Series of the voltage across the inductance given that $\omega = 500$ rad./sec. Sketch the voltage waveform.

- [13] A voltage signal $v(t)$ is applied to the terminals of a passive network resulting in a current $i(t)$. If the current and voltage are given by :
 $v(t) = 50 + 25 \sin(500t) + 10 \sin(1500t) + 5 \sin(2500t)$ V
 $i(t) = 5 + 2.23 \sin(500t - 26.6^\circ) + 0.556 \sin(1500t - 56.3^\circ) + 0.186 \sin(2500t - 68.2^\circ)$ A
 Calculate the effective values of the voltage and current and the average power dissipated in the network.

- [14] Determine the steady state response of the current $i_o(t)$ in the circuit shown in Fig. 8a if the input voltage of the circuit $v(t)$ is described by the waveform shown in Fig. 8b.

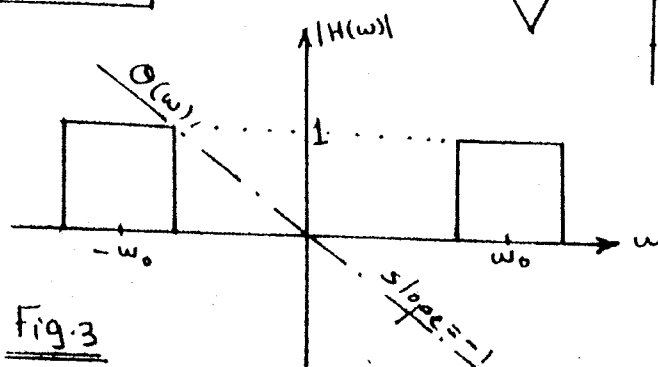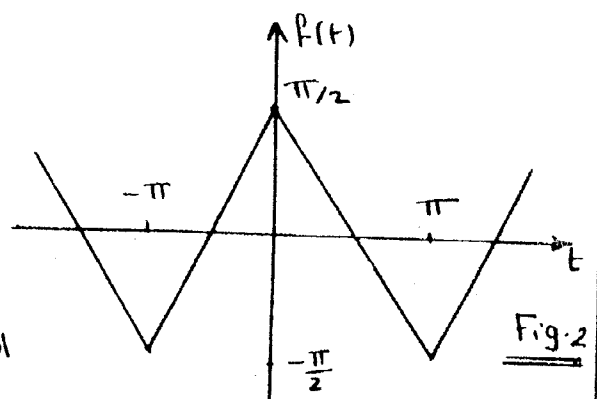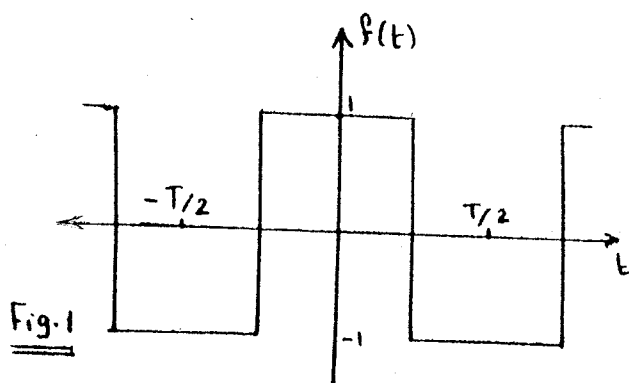

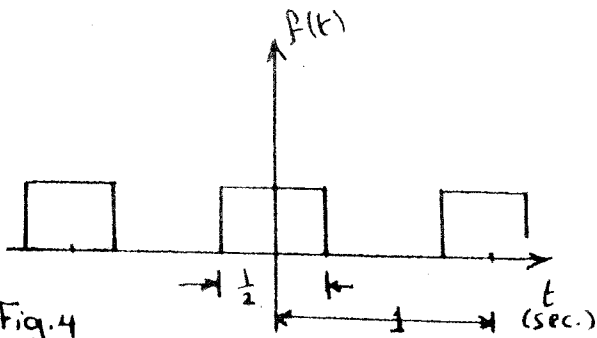


Fig. 4

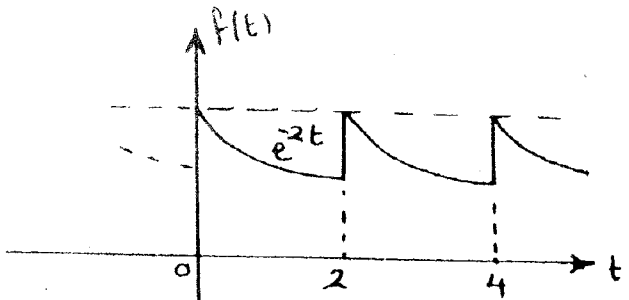


Fig. 5

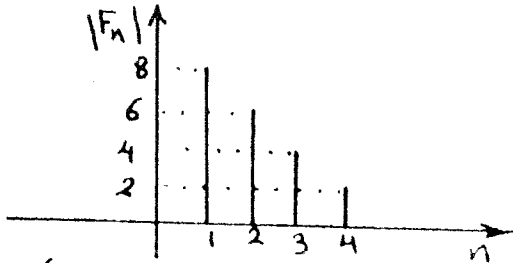


Fig. 6a

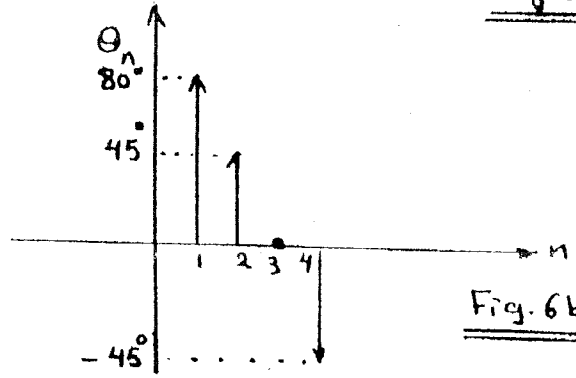


Fig. 6b

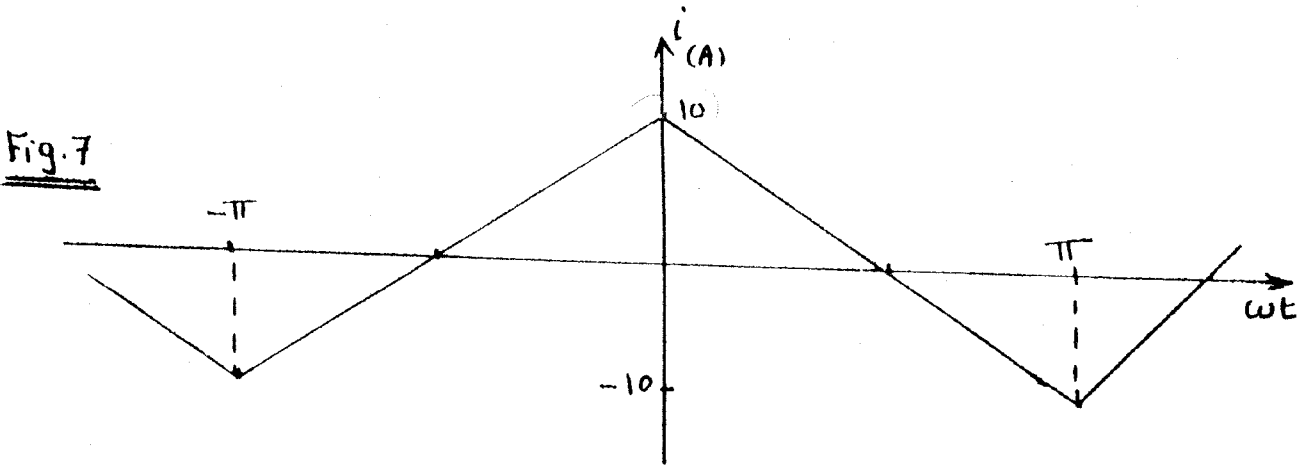


Fig. 7

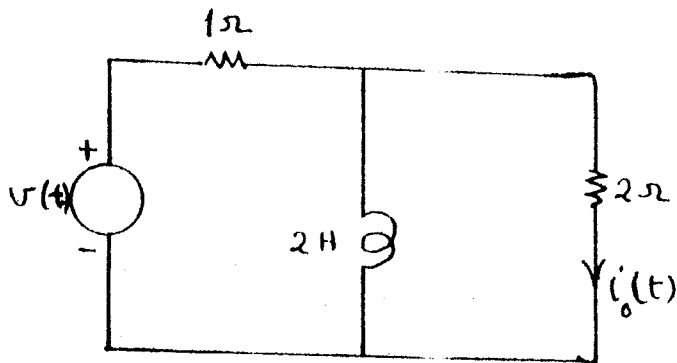


Fig. 8a

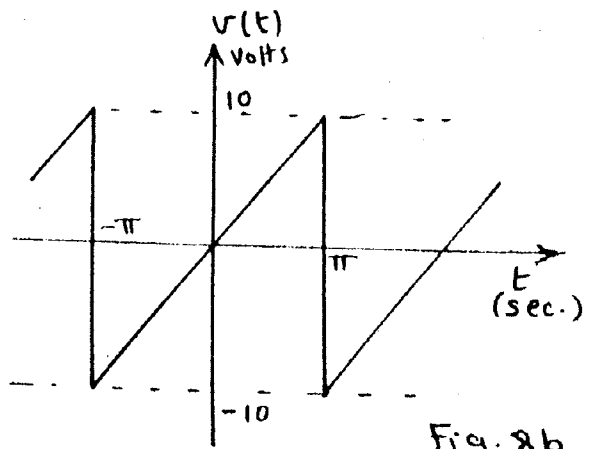


Fig. 8b