



- [1] Draw the normalized resonance curves for the current in a series resonance circuit having a quality factor $Q_s = 20$ in the narrow band near resonance (for $\delta = +1\%$, $+2\%$,, $+5\%$). Plot the phase angle of the current in the same band and show the effect of increasing Q_s .
- [2] In a series resonance circuit $L = 65 \text{ mH}$, $C = 1.56 \text{ nF}$ and $R = 5.1 \Omega$, calculate the resonance frequency, the quality factor of the circuit, the bandwidth and the impedance of the circuit at frequencies 1% and 10% above resonance.
- [3] For the circuit shown in Fig. 1, calculate the frequency at which series resonance occurs (the input impedance is real). At what value of the conductance G will it be impossible to obtain resonance?
- [4] A generator is connected to a series oscillating circuit has a frequency of 250 KHz. The oscillating circuit has a constant $L = 600 \mu\text{H}$, $R = 30 \Omega$ and a variable capacitor C . For which value of the capacitor C will the circuit be at resonance? and for which value of frequency will the current flowing through the circuit decrease to one fourth of its value at resonance.
- [5] The cutoff frequencies of a series resonance circuit are 5600 and 6000 Hz :
- Calculate the B.W. of the circuit and Q_s .
 - If the resistance of the circuit is 2Ω , calculate X_L , X_C , L and C at resonance.
- [6] A series resonance circuit has a resonance frequency of 10 KHz. The resistance of the circuit is 5Ω and X_C at resonance is 200Ω , find :
- The Bandwidth and the cutoff frequencies.
 - Q_s of the circuit.
 - The voltage across the coil and the capacitor at resonance and at a frequency 10% below resonance if the input voltage is $30 \angle 0^\circ$.
 - The power dissipated in the circuit at resonance and at a frequency 4% above resonance.
- [7] Design a series resonance circuit with an input voltage $5 \angle 0^\circ \text{ V}$ to have the following specifications :
- A peak current of 500 mA.
 - A Bandwidth of 120 Hz.
 - A resonance frequency of 8400 Hz.

Handwritten notes and scribbles on the right side of the page, including the word "Xc" and some illegible symbols.

Calculate the circuit elements and the cutoff frequencies .

18] A series resonance circuit of L, C and R is required to be at resonance at a frequency of 1 MHz . Its Bandwidth is 5 KHz and its input impedance at resonance is 50Ω . Calculate L, C and R .

19] Make the necessary derivations to sketch the magnitude of the current I shown in Fig.2 in amperes against frequency in Hertz showing its value at the resonance frequency F_s and the cutoff frequencies F_1 and F_2 , hence , prove that : $F_s = \sqrt{F_1 F_2}$.

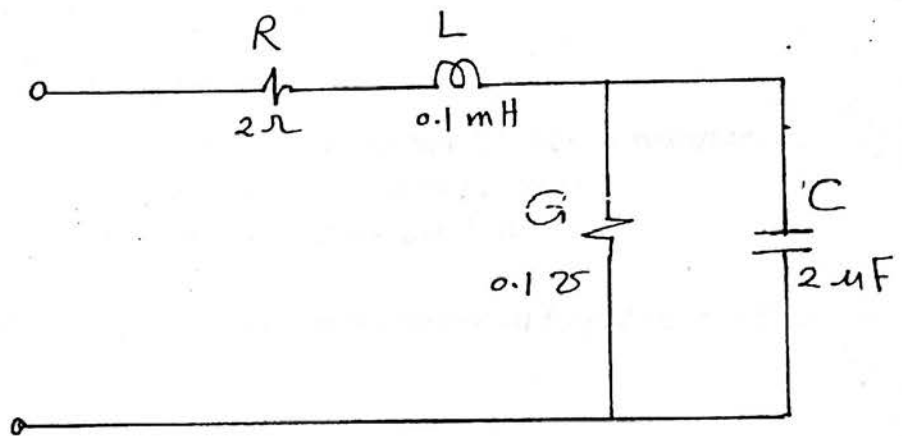


Fig.1

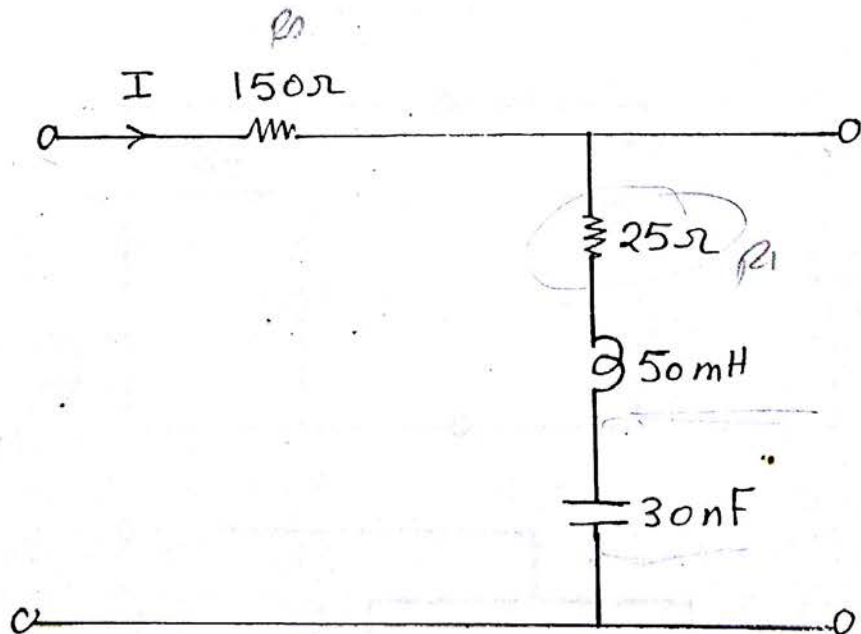


Fig.2