



ELECTRICAL MACHINES

Elective Course – EPM332

Course Grading System

2

100 Marks

70

Final Exam

30

Semester Work

- **15 Mid-term**
- **10 Quizzes**
- **5 Assignments**

Course Schedule

3

- Lecture: Tuesday 12:15 - 1:45 pm
- Office Hours: Tuesday 2-3 pm
- Quizzes: W6 – W12
- Mid-term: W8 (29 March-3 April)
- Email: tamer.m.abdo@gmail.com
- Scholar page: <https://goo.gl/ymLdll>

Course ILOs

4

- 1. Explain the construction, types, principle of operation, equivalent circuit and tests of the 1-phase transformer**
- 2. Define the principle of pulsating and rotating fields**
- 3. Explain the construction, types, principle of operation and equivalent circuit of the 3-phase induction machines.**
- 4. Explain the theory of operation of single-phase induction motor**
- 5. Discuss the different types of 1-phase induction motors and their performance**
- 6. Calculate the basic quantities concerning the operation of the transformer and induction machines.**
- 7. Solve performance problems of transformer and induction machines**
- 8. Compare different types of single-phase induction motors and different starting methods**
- 9. Explain the construction, types and theory of operation of the stepper motor.**

Course Contents

5

- Basic Principles
- Transformers
- Induction Machines
 1. Three-phase induction motors.
 2. Two-phase induction motors (AC Servo).
 3. Single-phase induction motors.
- Stepper Motors

Revision: Basic Principles

6

- AC Circuits
- Three-phase Circuits
- Magnetic Fields
- Time-varying Fields: Faraday's Law
- Magnetic Circuits


Revision: Basic Principles

7

AC Circuits

Sinusoidal Voltage Supply

$$v = V_m \sin(\omega t)$$

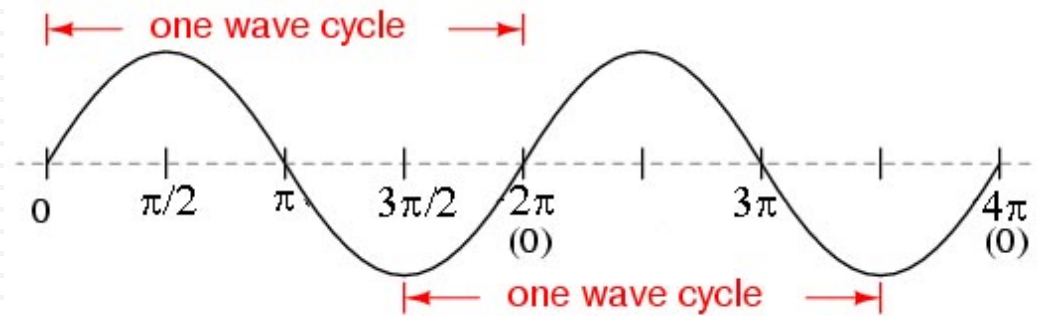

Time of one cycle = Period = T

$$\boxed{2\pi = \omega T} \Rightarrow \boxed{T = \frac{2\pi}{\omega}} \text{ (sec)} \Rightarrow \boxed{f = \frac{\omega}{2\pi}} \text{ (Hz)} \Rightarrow \boxed{\omega = 2\pi f} \text{ (rad/sec)}$$

No. of cycles/sec = Frequency = $1/T$

Revision: Basic Principles

8

AC Circuits

Phase Shift


$$v_1 = V_m \sin(\omega t)$$

$$v_2 = V_m \sin(\omega t + \phi)$$

$$v_3 = V_m \sin(\omega t - \phi)$$

v_1 lags v_2 but leads v_3

v_3 lags v_1 and lags v_2

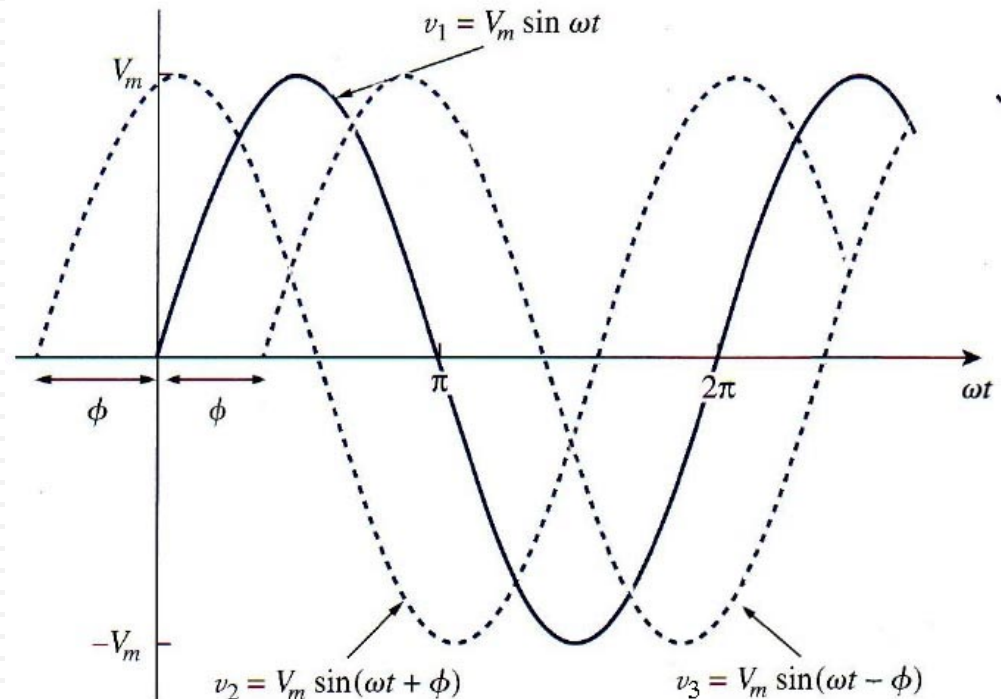

The terms lag and lead are used to describe phase shift between sinusoidal waveforms of same frequency


Revision: Basic Principles

9


AC Circuits

Phasor Representation

$$v_1 = V_m \sin(\omega t)$$

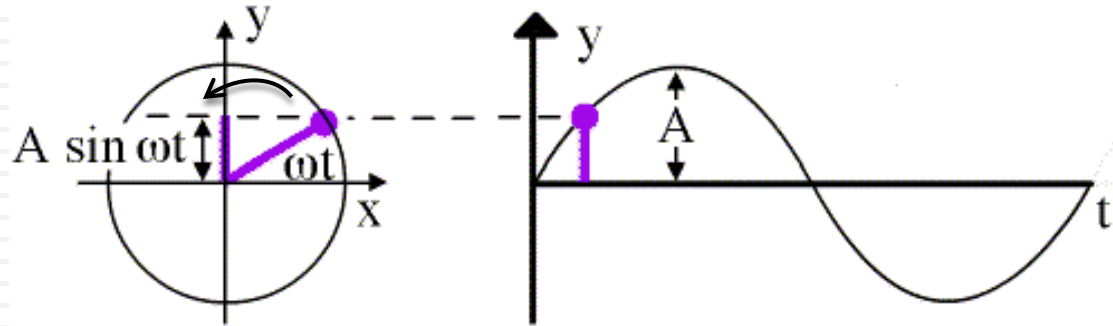

$$v_2 = V_m \sin(\omega t + \theta_o)$$

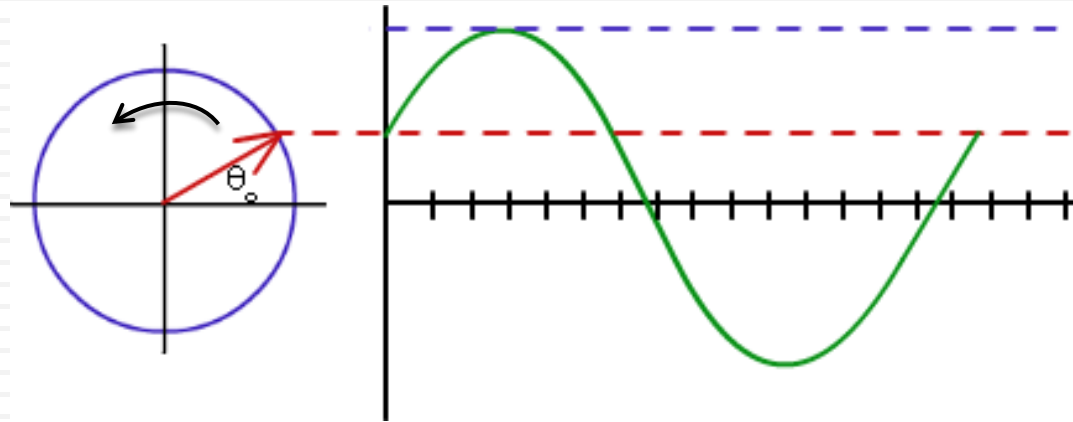


Revision: Basic Principles

10


AC Circuits

Phasor Representation

$$V_1 = V_{rms} \angle 0$$

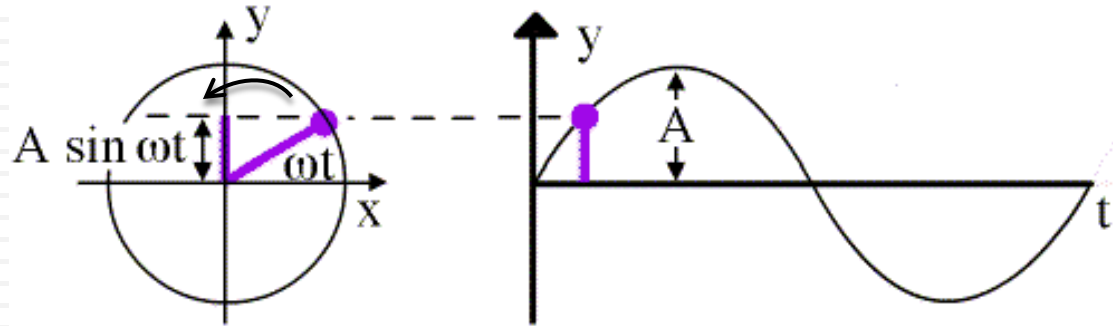

$$V_2 = V_{rms} \angle \theta_o$$

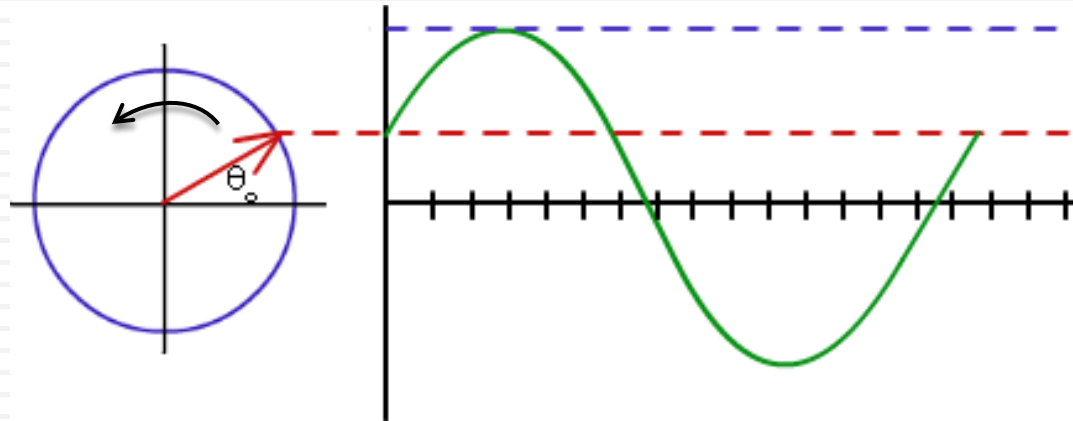

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

Revision: Basic Principles


11

AC Circuits

Phasor Representation

$$V_1 = V_1 \angle 0$$

$$V_2 = V_2 \angle \theta_o$$

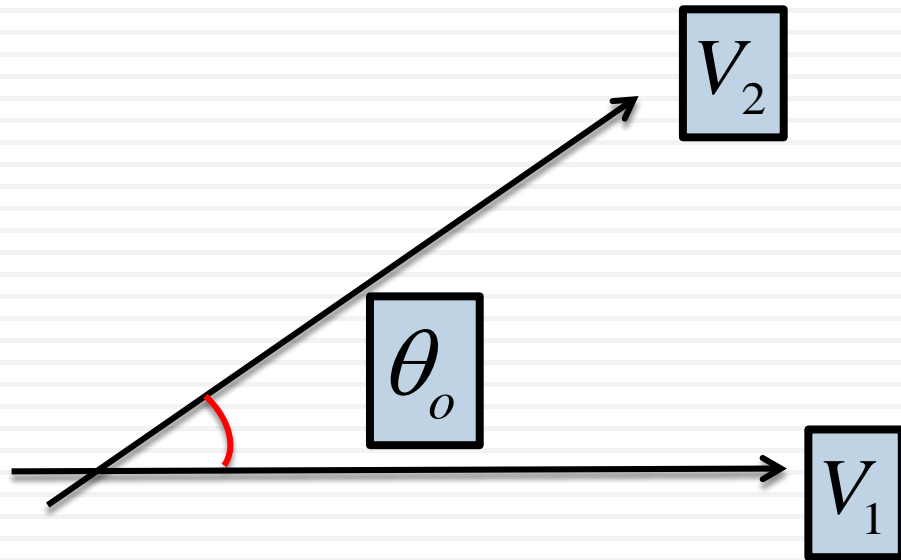


Phasor Diagram

Revision: Basic Principles

12

AC Circuits

Phasor Representation

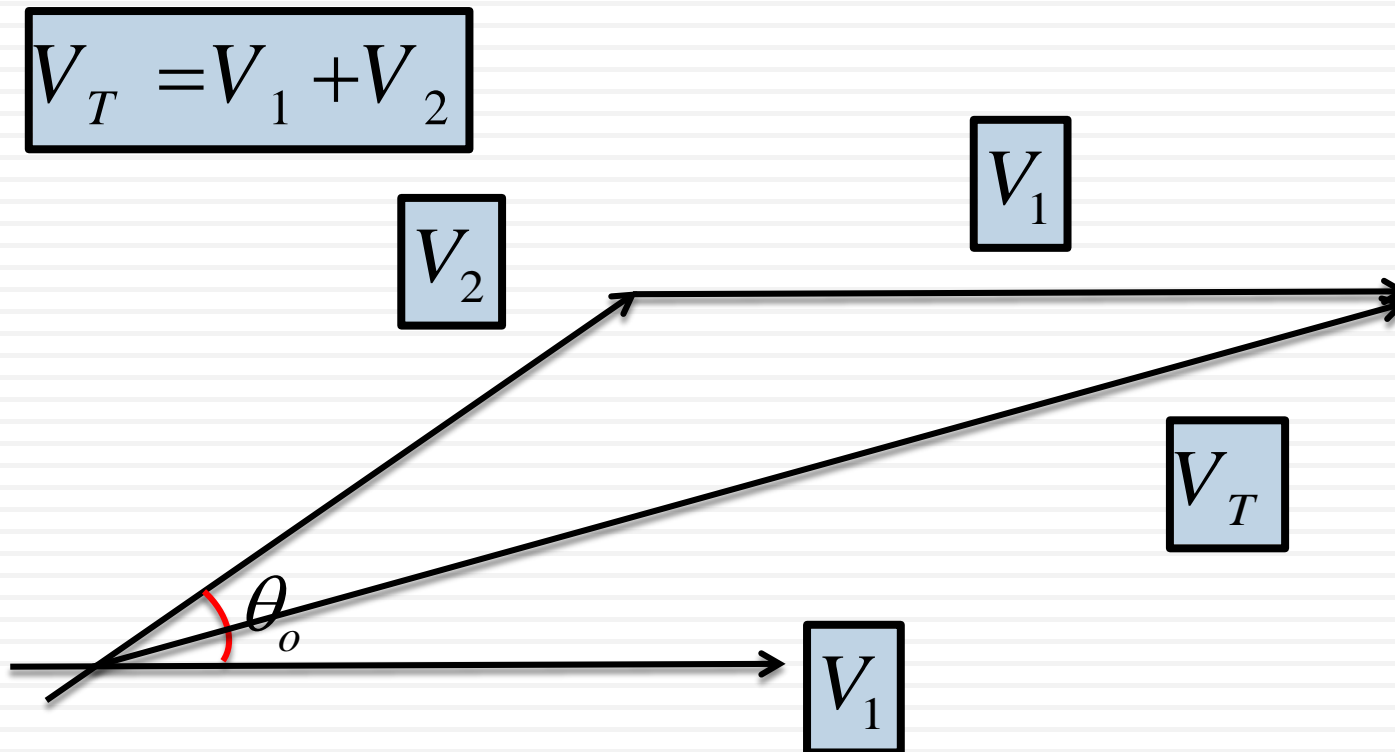


Revision: Basic Principles

13

AC Circuits

Phasor Representation

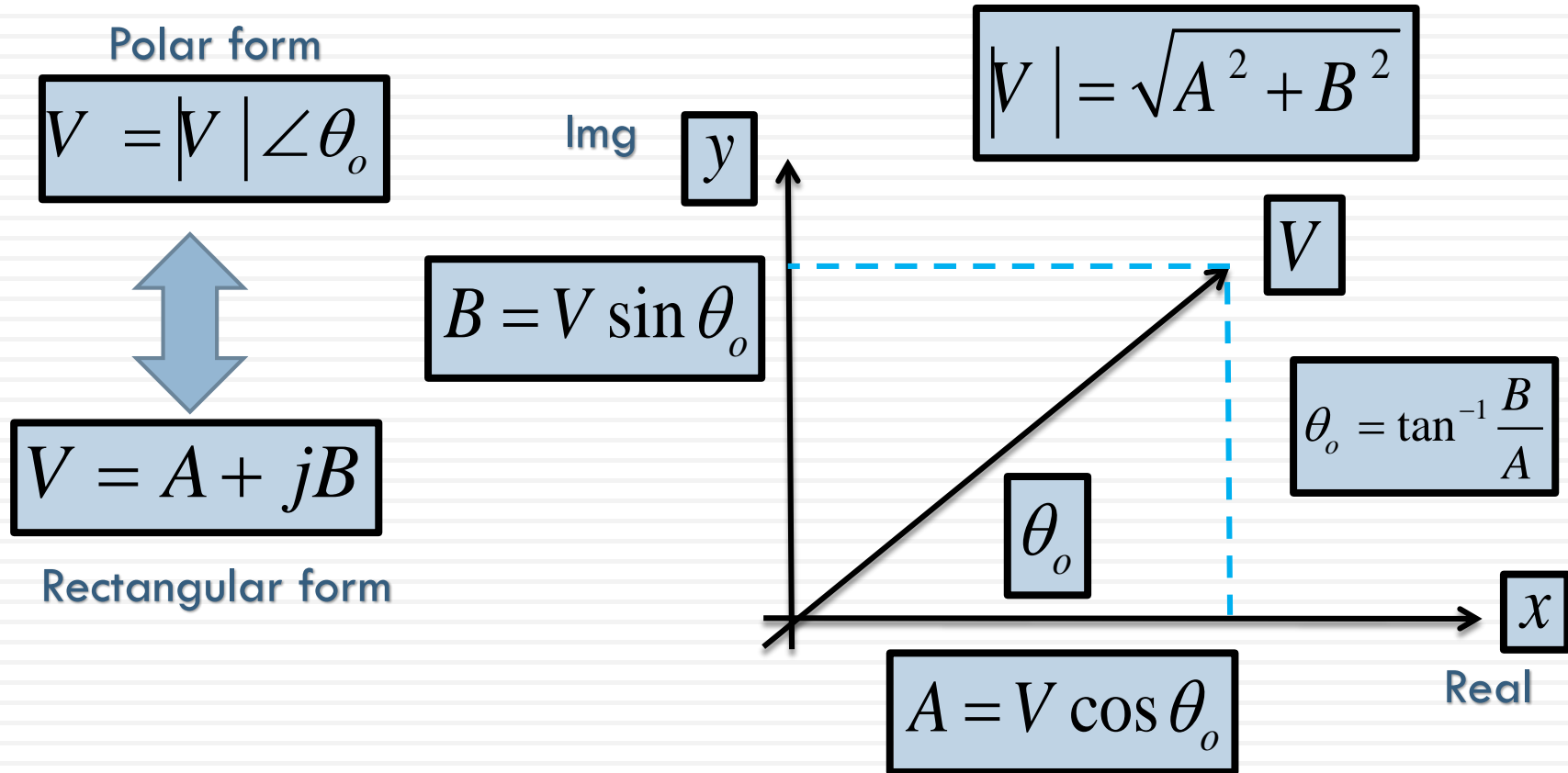

Revision: Basic Principles

14

AC Circuits

Phasor Representation

$$V_1 = A_1 + jB_1 \iff V_1 = |V_1| \angle \theta_1 \quad V_2 = A_2 + jB_2 \iff V_2 = |V_2| \angle \theta_2$$

$$V_T = V_1 \pm V_2$$

$$V_T = (A_1 \pm A_2) + j(B_1 \pm B_2)$$

$$V_T = |V_T| \angle \theta_T$$

$$|V_T| = \sqrt{(A_1 \pm A_2)^2 + (B_1 \pm B_2)^2}$$

$$\theta_T = \tan^{-1} \frac{B_1 \pm B_2}{A_1 \pm A_2}$$

Revision: Basic Principles

15

AC Circuits

Phasor Representation

$$V_1 = A_1 + jB_1 \leftrightarrow V_1 = |V_1| \angle \theta_1 \quad V_2 = A_2 + jB_2 \leftrightarrow V_2 = |V_2| \angle \theta_2$$

$$V_T = V_1 \times V_2$$

$$V_T = [|V_1| \angle \theta_1] \times \text{or} \div [|V_2| \angle \theta_2] \quad V_T = |V_1| \times \text{or} \div |V_2| \angle \theta_1 \pm \theta_2$$

$$V_T = |V_T| \angle \theta_T$$

$$|V_T| = |V_1| \times \text{or} \div |V_2|$$

$$\theta_T = \theta_1 \pm \theta_2$$

Revision: Basic Principles

16

AC Circuits

Loads: Resistive Load

$$v(t) = V_m \sin(\omega t) = \sqrt{2}V \sin(\omega t)$$


$$V = V \angle 0$$

$$i(t) = \frac{v(t)}{R} = \sqrt{2} \frac{V}{R} \sin(\omega t)$$

$$i(t) = \sqrt{2}I \sin(\omega t)$$

$$I = I \angle 0$$

$$V = IR$$

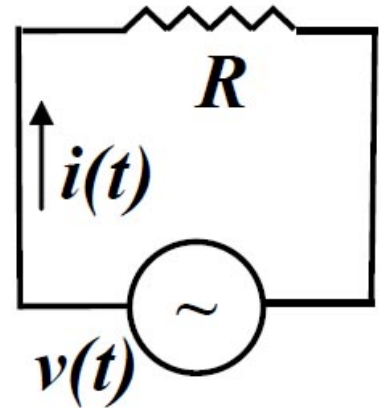

Revision: Basic Principles

17


AC Circuits

Loads: Resistive Load

$$V = IR$$



Phasor Diagram

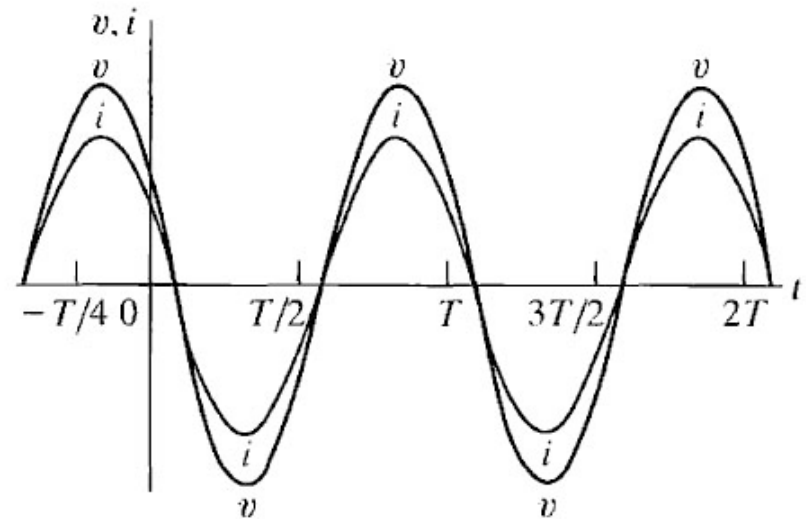

Voltage and current are in-phase

Revision: Basic Principles

18

AC Circuits


Loads: Inductive Load

$$v = N \frac{d\phi}{dt} = L \frac{di}{dt}$$

$$v(t) = \sqrt{2}V \sin(\omega t)$$

$$i(t) = \frac{1}{L} \int v(t) dt = -\sqrt{2} \frac{V}{\omega L} \cos(\omega t)$$
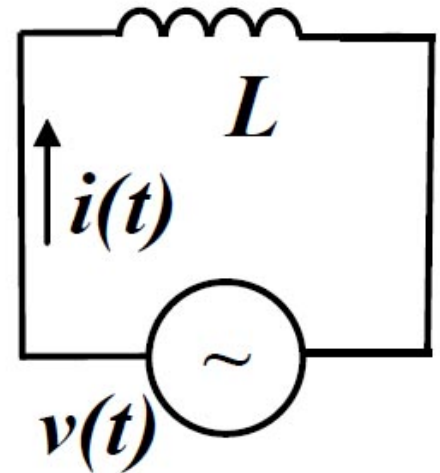
$$i(t) = \sqrt{2} \frac{V}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right)$$



Revision: Basic Principles

19

AC Circuits


Loads: Inductive Load

$$I = -j \frac{V}{\omega L}$$

$$V = j(\omega L)I$$

$$V = jX_L I$$

Inductive reactance (Ω)

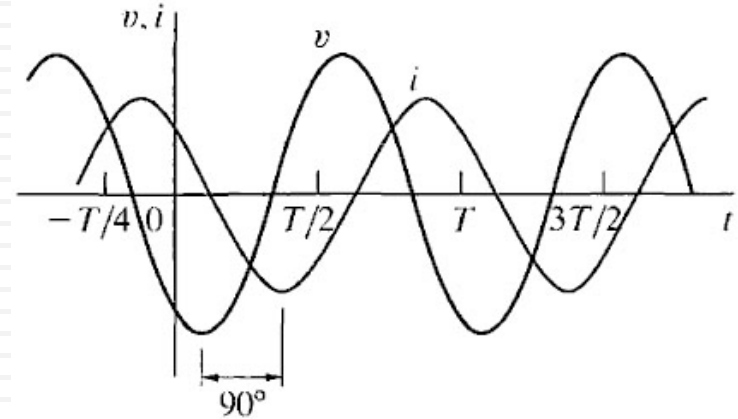

current lags voltage by 90°



Revision: Basic Principles

20

AC Circuits


Loads: Capacitive Load

$$i = C \frac{dv}{dt}$$

$$v(t) = \sqrt{2}V \sin(\omega t)$$

$$i(t) = \sqrt{2}\omega CV \cos(\omega t)$$
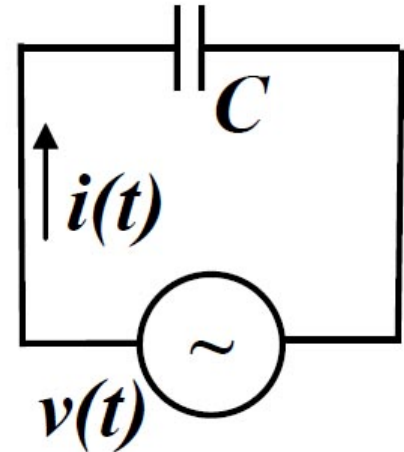
$$i(t) = \sqrt{2}\omega CV \sin\left(\omega t + \frac{\pi}{2}\right)$$



Revision: Basic Principles

21


AC Circuits

Loads: Capacitive Load

$$I = j(\omega C)V$$

$$V = -j\left(\frac{1}{\omega C}\right)I$$
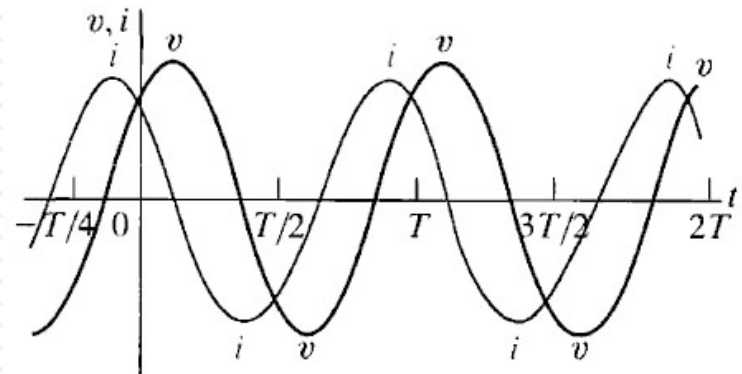
$$V = -jX_C I$$
 Capacitive reactance (Ω)



current leads voltage by 90°

Revision: Basic Principles

22

AC Circuits

Loads: R-L Load

$$V = I(R + j\omega L)$$


$$V = I(R + jX_L)$$

$$V = IZ \quad \text{Impedance}$$

$$Z = R + jX_L = Z \angle \Phi$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$\Phi = \tan^{-1} \frac{\omega L}{R}$$

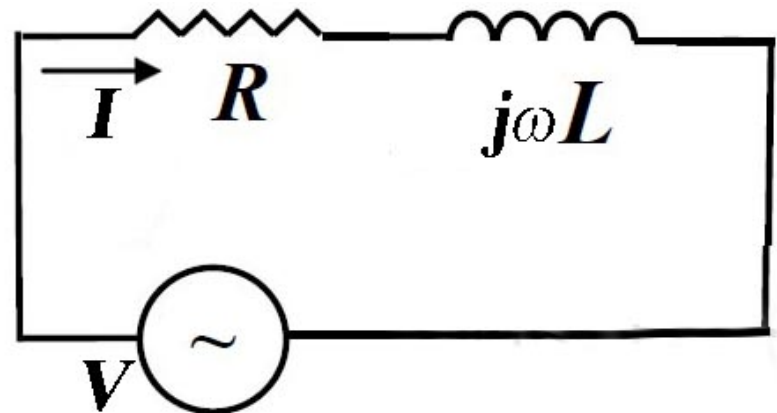

$$I = \frac{V \angle 0}{Z \angle \Phi} = \frac{V}{Z} \angle -\Phi$$


current lags voltage

Revision: Basic Principles

23

AC Circuits

Loads: R-L Load

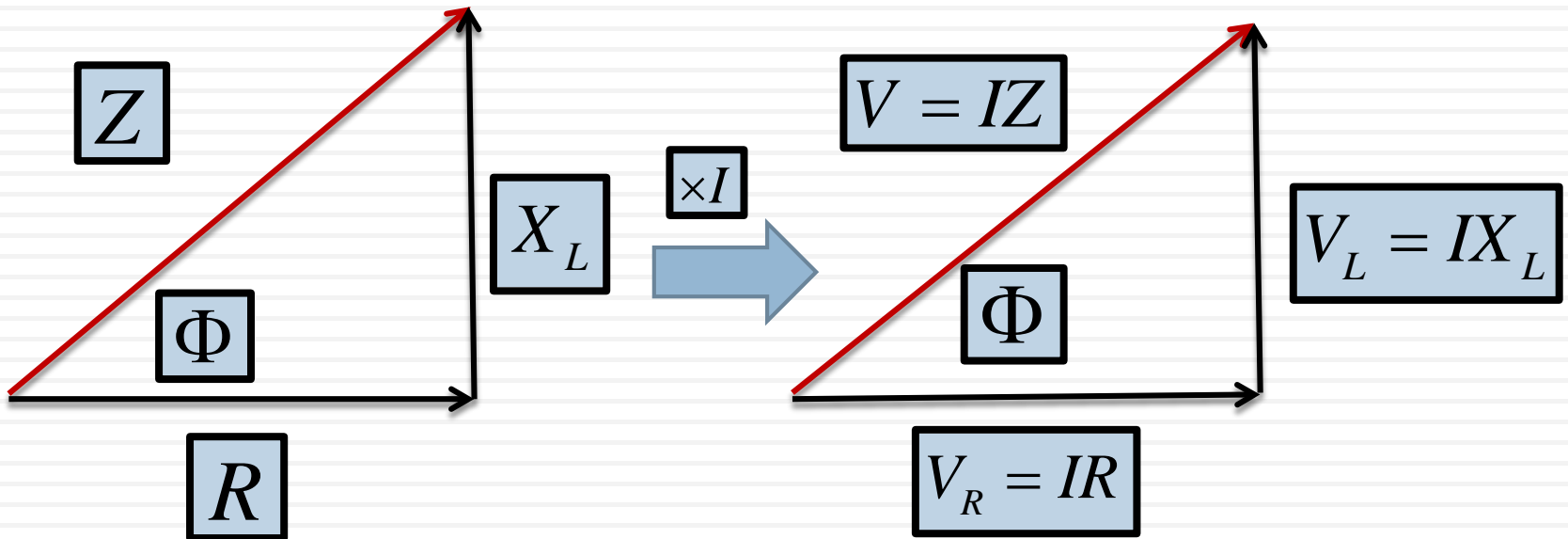

Revision: Basic Principles

24

AC Circuits

Loads: R-C Load

$$V = I\left(R - j\frac{1}{\omega C}\right)$$

$$V = I(R - jX_C)$$


$$Z = R - jX_C = Z \angle -\Phi$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$\Phi = \tan^{-1} \frac{1/\omega C}{R}$$

$$I = \frac{V \angle 0}{Z \angle -\Phi} = \frac{V}{Z} \angle \Phi$$

current **leads** voltage

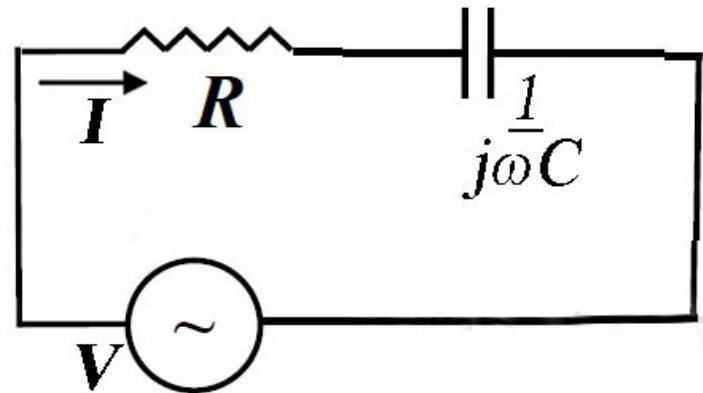


Revision: Basic Principles

25

AC Circuits

Loads: R-C Load

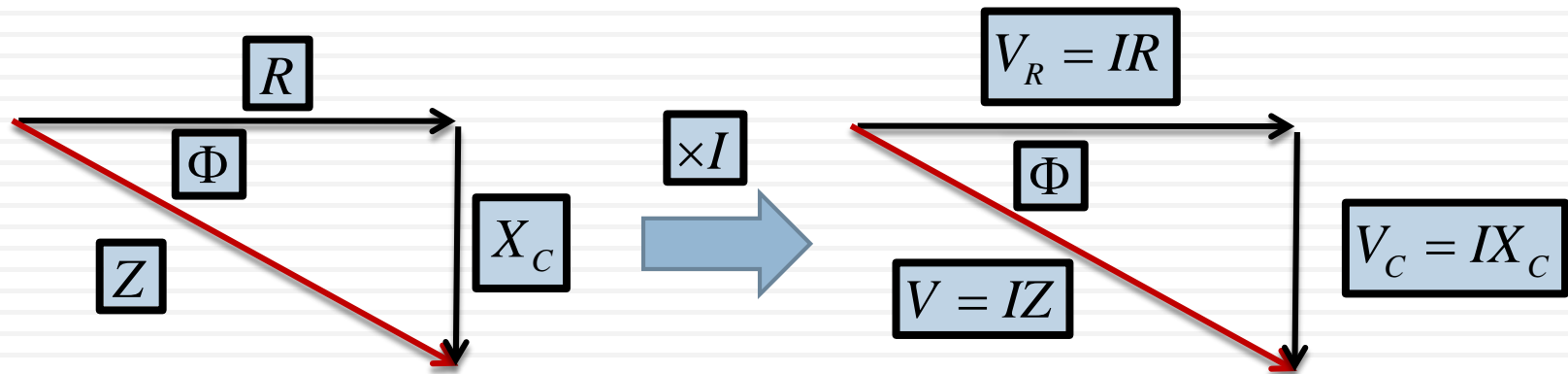

Revision: Basic Principles


26

AC Circuits

Loads: R-L-C Load

$$V = I[R + j(X_L - X_C)]$$

$$Z = R + j(X_L - X_C) = Z \angle \Phi$$

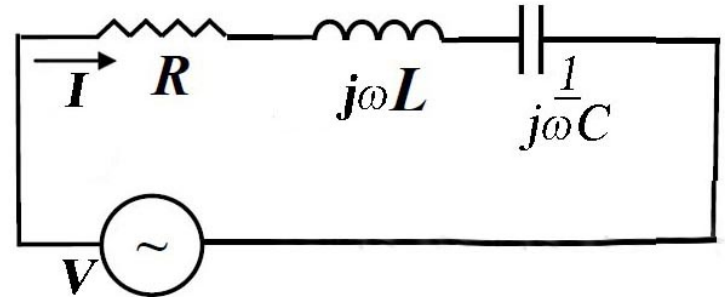

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\Phi = \tan^{-1} \frac{X_L - X_C}{R}$$

$$X_L > X_C$$

$$\Phi = +ve$$

inductive load

$$X_L < X_C$$

$$\Phi = -ve$$

capacitive load


$$I = \frac{V \angle 0}{Z \angle \pm \Phi} = \frac{V}{Z} \angle \mp \Phi$$

Revision: Basic Principles


27

AC Circuits


Loads

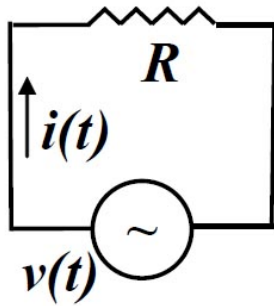


Resistive load

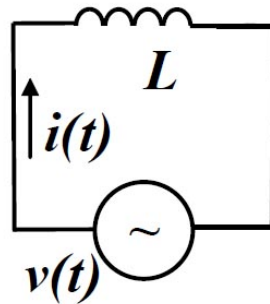


Pure inductive load

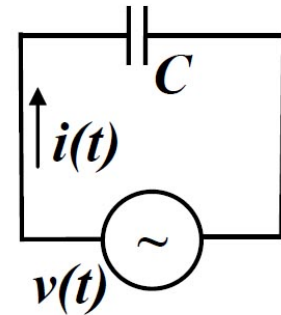


Pure capacitive load

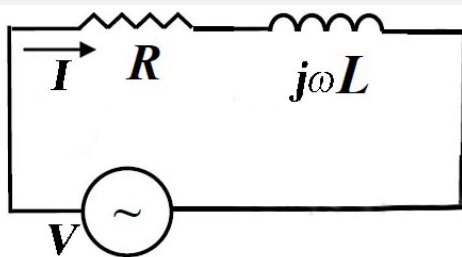

inductive load

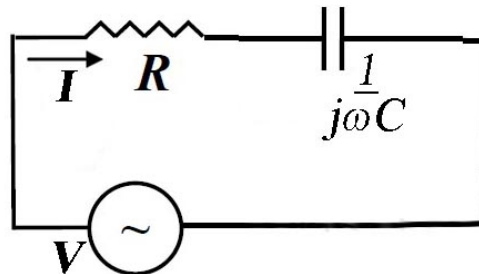

capacitive load

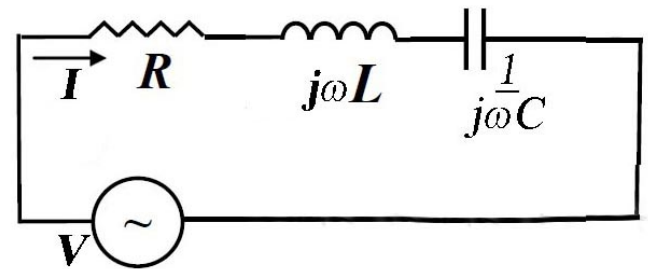

$$X_L > X_C$$

inductive load

$$X_L < X_C$$

capacitive load

Revision: Basic Principles

28

AC Circuits

AC Power


$$p(t) = v(t) \times i(t)$$

$$v(t) = \sqrt{2}V \sin(\omega t)$$

$$i(t) = \sqrt{2}I \sin(\omega t \pm \Phi)$$

$$p(t) = VI[\cos(\Phi) - \cos(2\omega t \pm \Phi)]$$
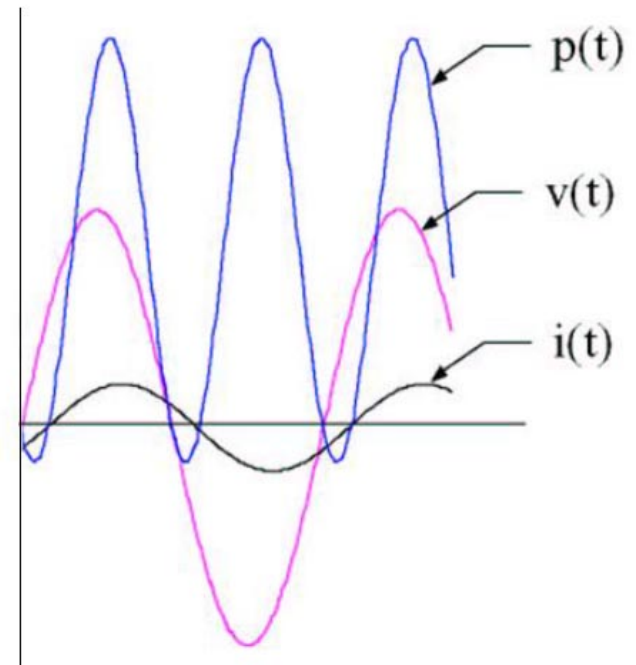
$$P_{avg} = VI \cos \Phi \quad \text{Active Power (W)}$$



Revision: Basic Principles

29

AC Circuits

Active and Reactive Power


$$p(t) = VI[\cos(\Phi) - \cos(2\omega t \pm \Phi)]$$

For pure resistive load:

$$\Phi = 0$$

$$p(t) = VI[1 - \cos(2\omega t)]$$

$$P_{avg} = VI$$

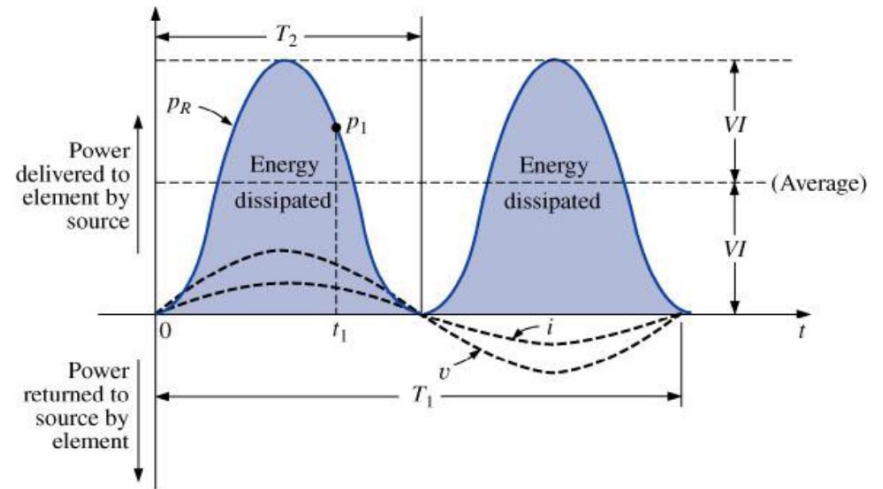

Revision: Basic Principles

30

AC Circuits

Active and Reactive Power

$$p(t) = VI[\cos(\Phi) - \cos(2\omega t \pm \Phi)]$$


For pure inductive load:

$$\Phi = -90^\circ$$

$$p(t) = VI \cos(2\omega t - 90^\circ)$$

$$p(t) = VI \sin(2\omega t)$$

$$P_{avg} = \text{zero}$$

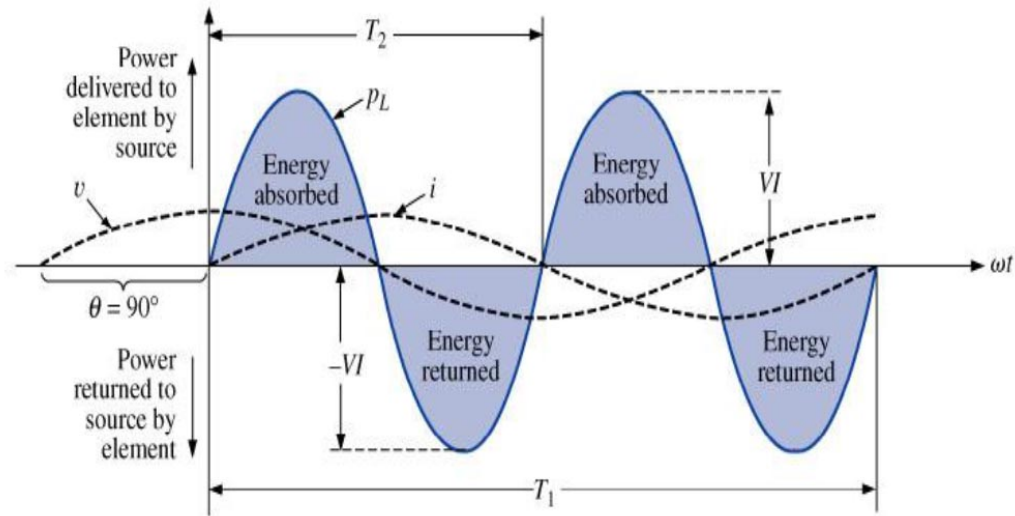

Revision: Basic Principles

31

AC Circuits

Active and Reactive Power

$$p(t) = VI[\cos(\Phi) - \cos(2\omega t \pm \Phi)]$$


For pure capacitive load:

$$\Phi = 90^\circ$$

$$p(t) = VI \cos(2\omega t + 90^\circ)$$

$$p(t) = -VI \sin(2\omega t)$$

$$P_{avg} = zero$$

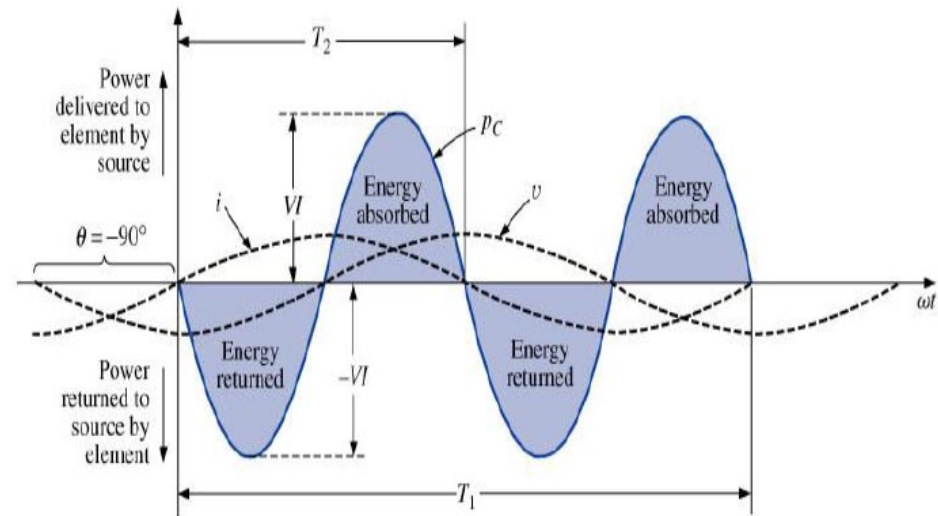


Revision: Basic Principles

32

AC Circuits

AC Power: Inductive Load

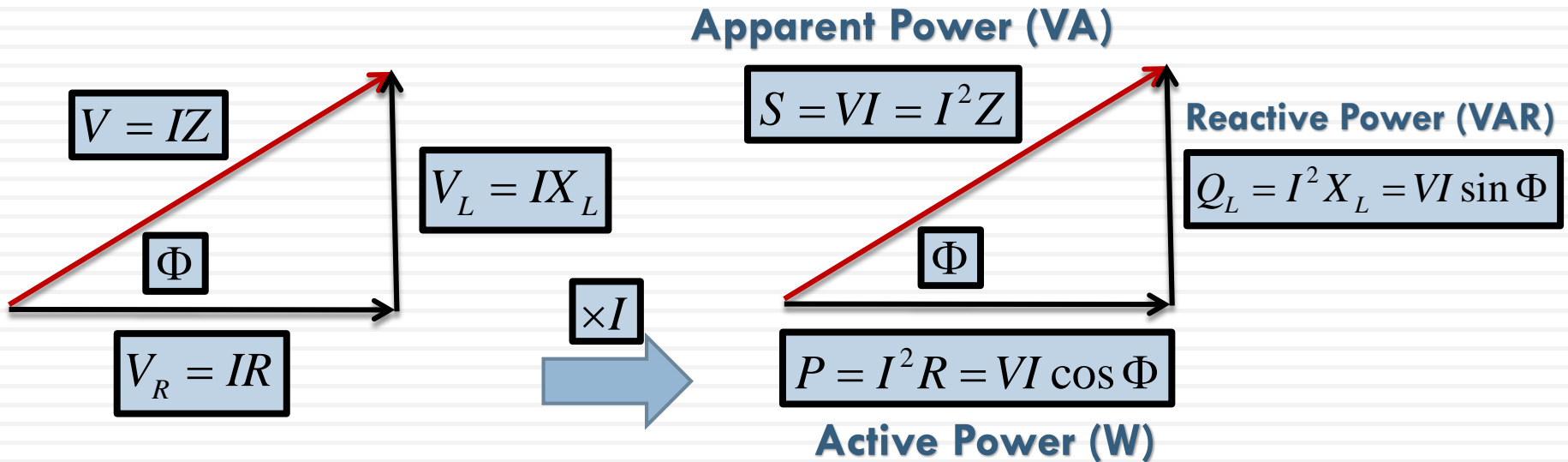


Revision: Basic Principles

33

AC Circuits

AC Power: Capacitive Load

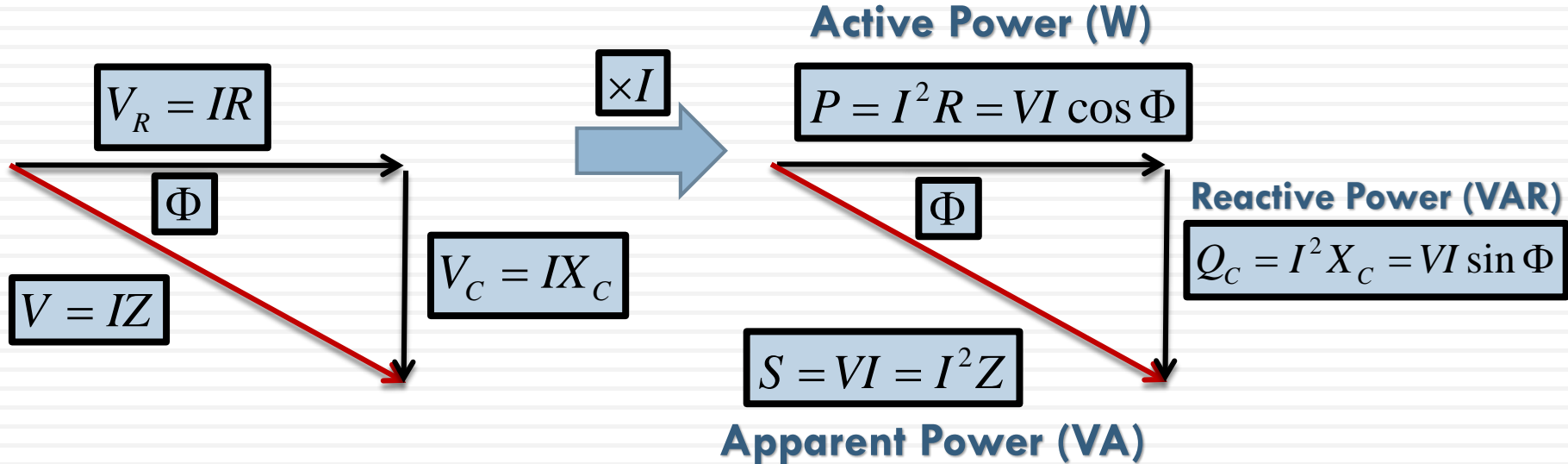

Revision: Basic Principles

34

AC Circuits


Complex Power & Power Factor

$$S = P \pm jQ = VI^*$$

$$I^* = (I \angle \mp \Phi)^* = I \angle \pm \Phi$$

$$S = VI \cos \phi \pm jVI \sin \phi$$
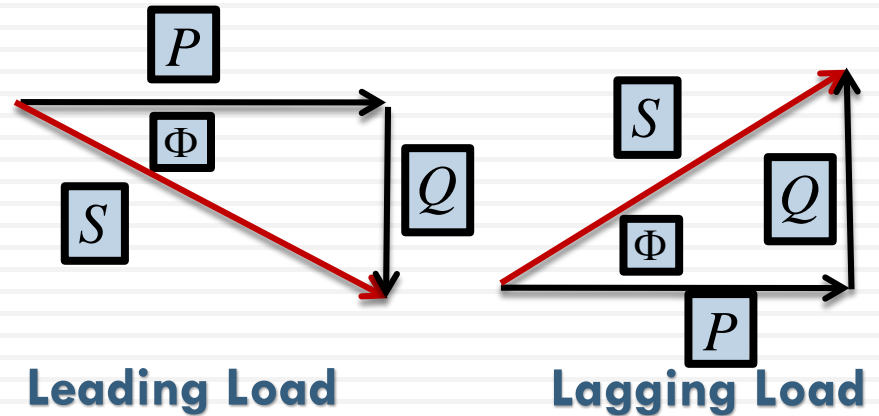
$$\text{power factor} = \frac{P}{S} = \cos \Phi$$




Revision: Basic Principles

35

AC Circuits

$$\text{Power Factor} = \frac{P}{S}$$

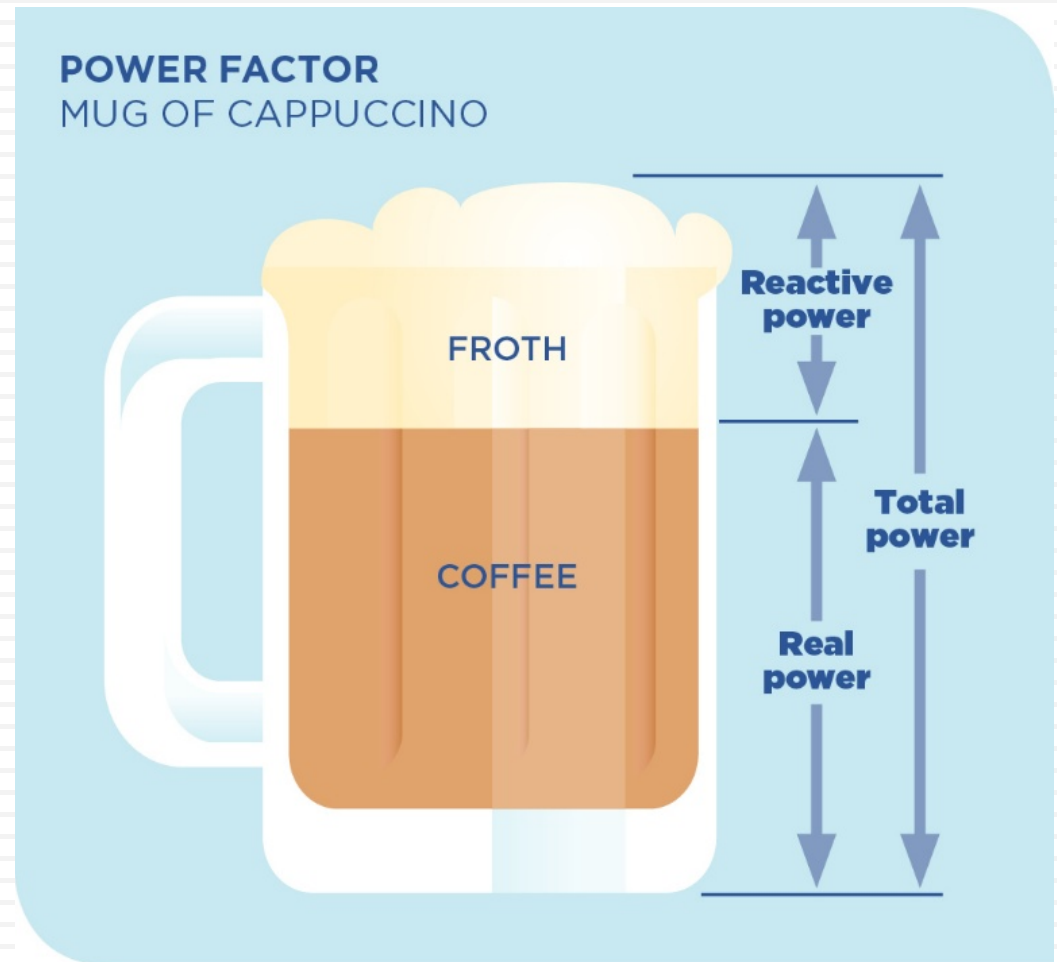


Revision: Basic Principles


36

AC Circuits

Before compensation

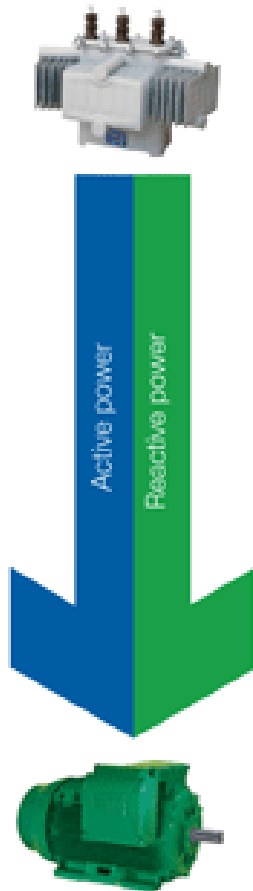

After compensation

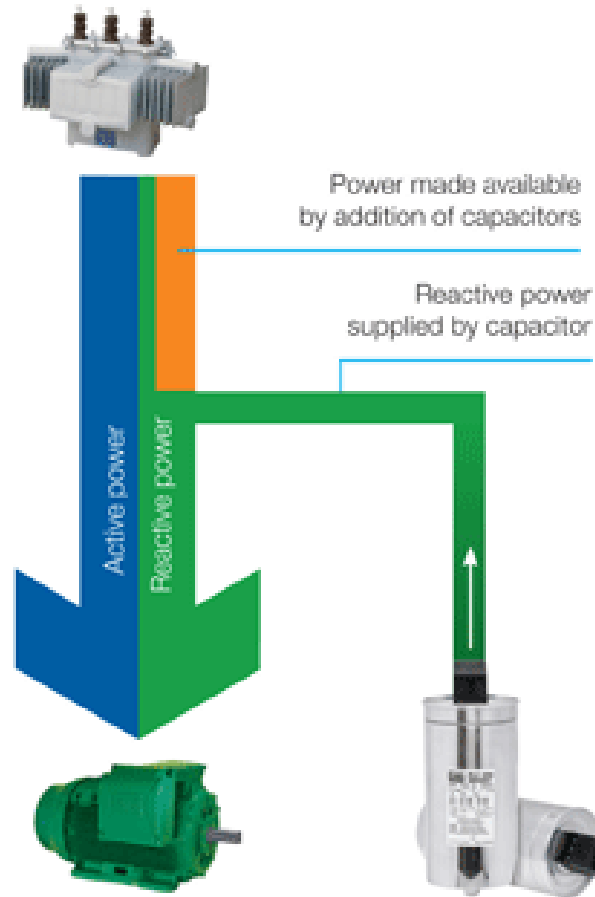


Revision: Basic Principles

37

3-phase AC Circuits

3-phase AC Supply

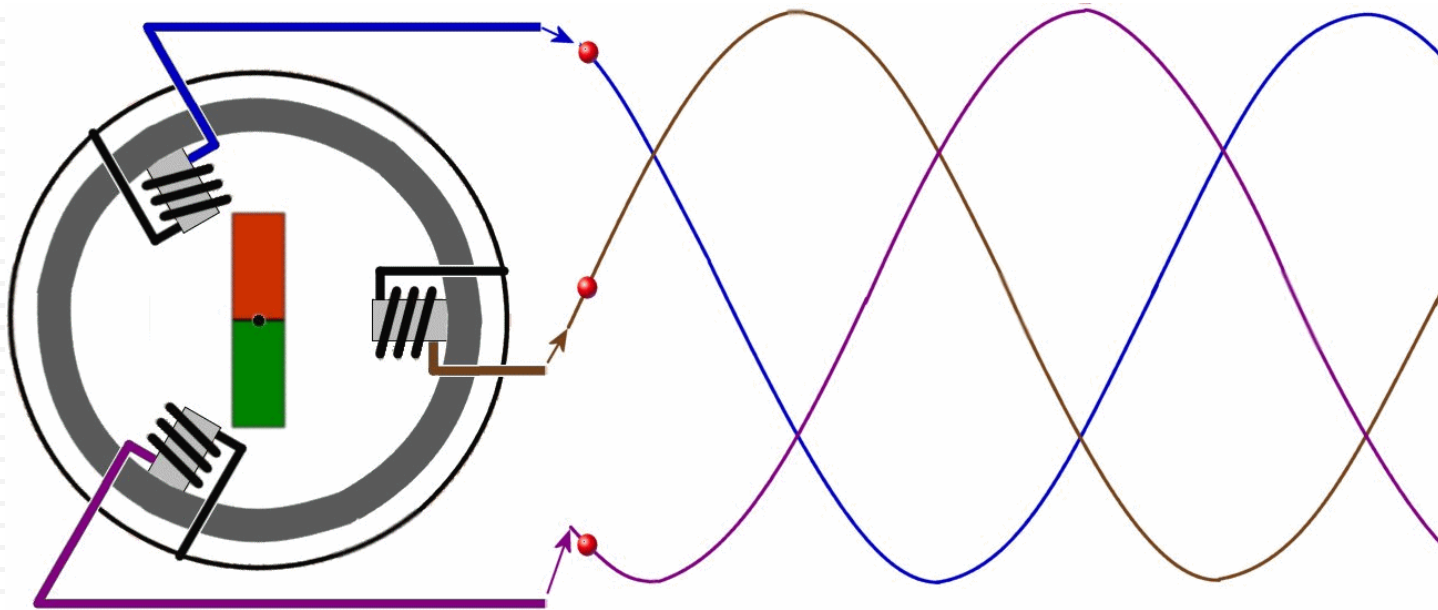

Revision: Basic Principles

38

3-phase AC Circuits

The three-phases are called: *A-B-C* or *R-S-T* or *R-Y-B*

$$v_a = V_m \sin(\omega t)$$

$$V_a = V \angle 0$$


$$v_b = V_m \sin(\omega t - 120^\circ)$$

$$V_b = V \angle -120$$

$$v_c = V_m \sin(\omega t - 240^\circ)$$

$$V_c = V \angle 120$$

$$v_c = V_m \sin(\omega t + 120^\circ)$$

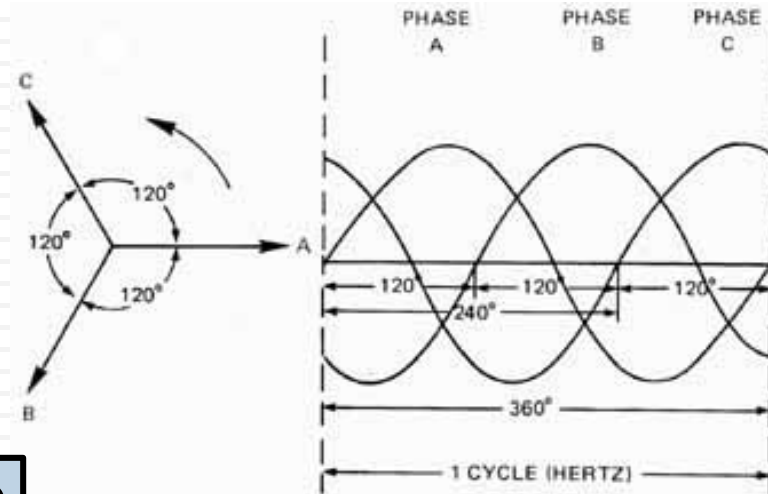


Balanced 3-phase supply: the three voltages are equal in magnitude and are 120° out of phase.

Revision: Basic Principles


39

3-phase AC Circuits

A-B-C

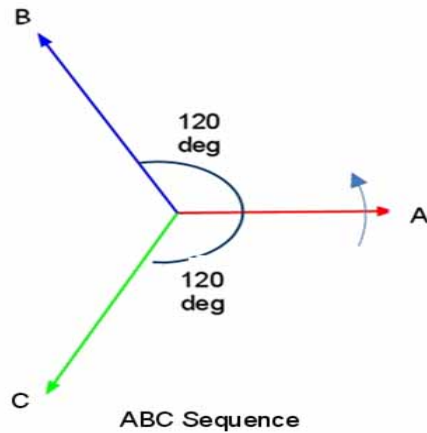

A-C-B

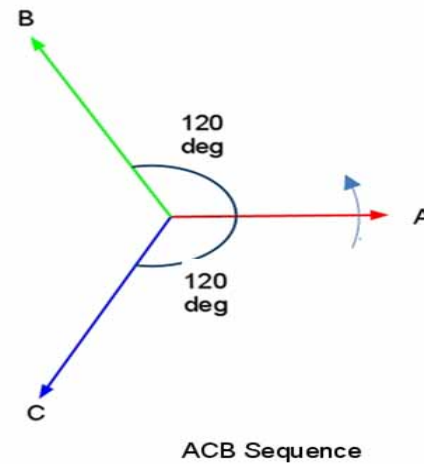

Positive sequence

$$V_a = V \angle 0$$

$$V_b = V \angle -120$$

$$V_c = V \angle 120$$

Negative sequence

$$V_a = V \angle 0$$


$$V_b = V \angle 120$$

$$V_c = V \angle -120$$

Revision: Basic Principles

40

3-phase AC Circuits

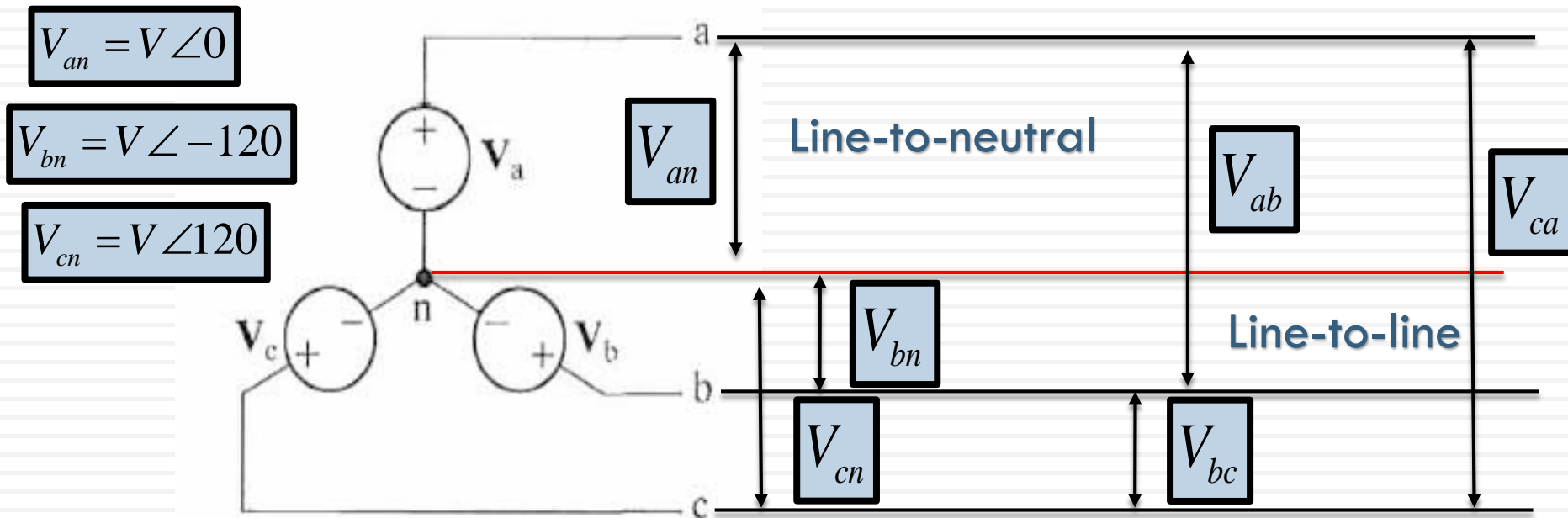

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{bc} = V_{bn} - V_{cn}$$

$$V_{ca} = V_{cn} - V_{an}$$

Revision: Basic Principles

41


3-phase AC Circuits

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3}V \angle 30^\circ$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3}V \angle -90^\circ$$

$$V_{ca} = V_{cn} - V_{an} = \sqrt{3}V \angle 150^\circ$$

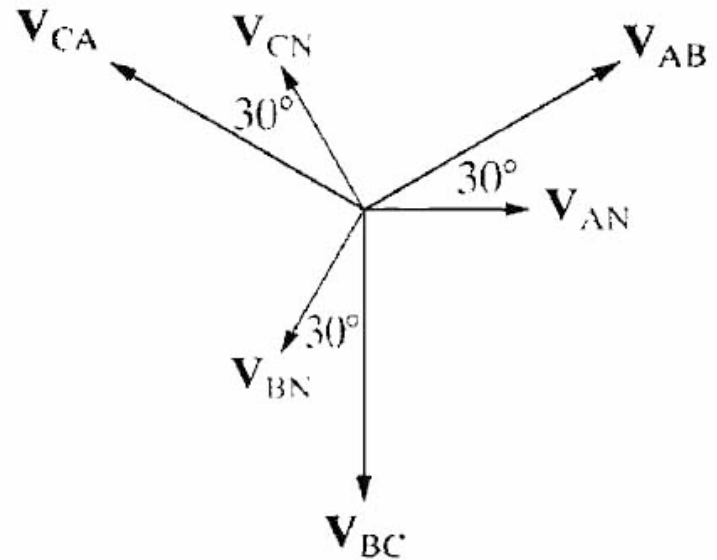
$$V_{LL} = \sqrt{3}V_{Ln} \angle (\theta + 30^\circ)$$



Revision: Basic Principles

42

3-phase AC Circuits

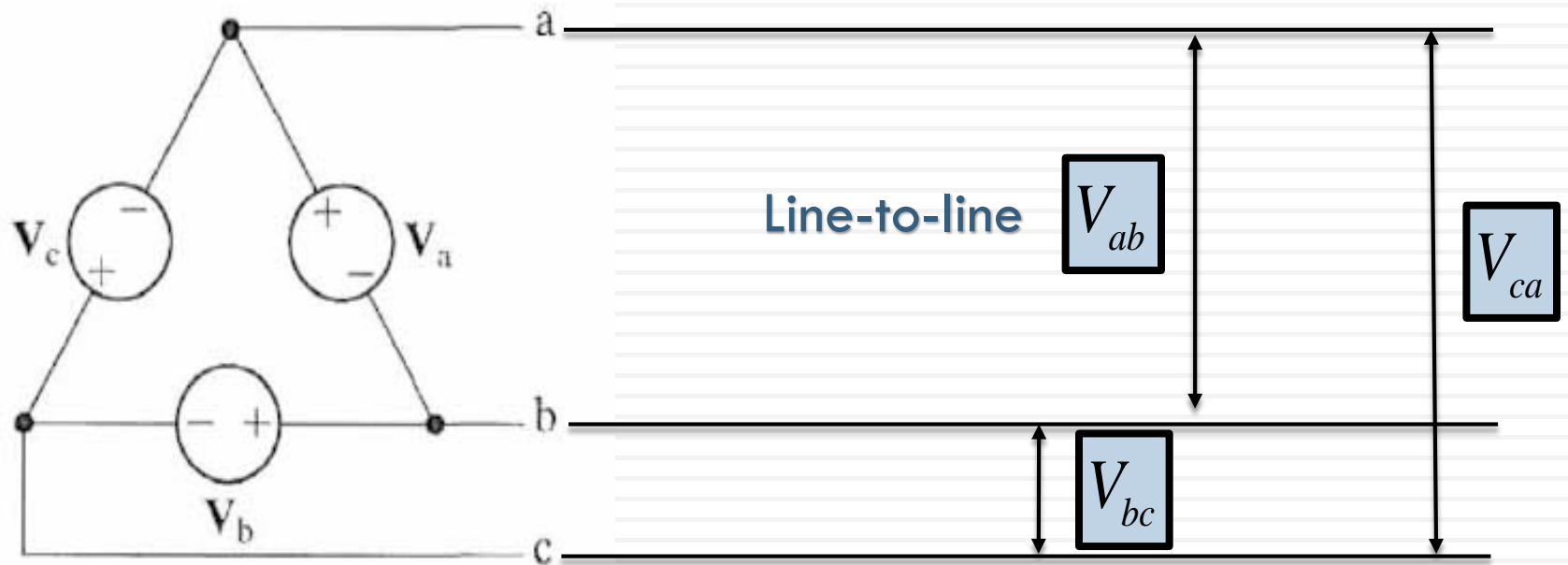

$$V_{ab} = V \angle 0$$

$$V_{bc} = V \angle -120$$


$$V_{ca} = V \angle 120$$

Revision: Basic Principles

43

3-phase AC Circuits

Balanced Star Load ($Z_A = Z_B = Z_C$)

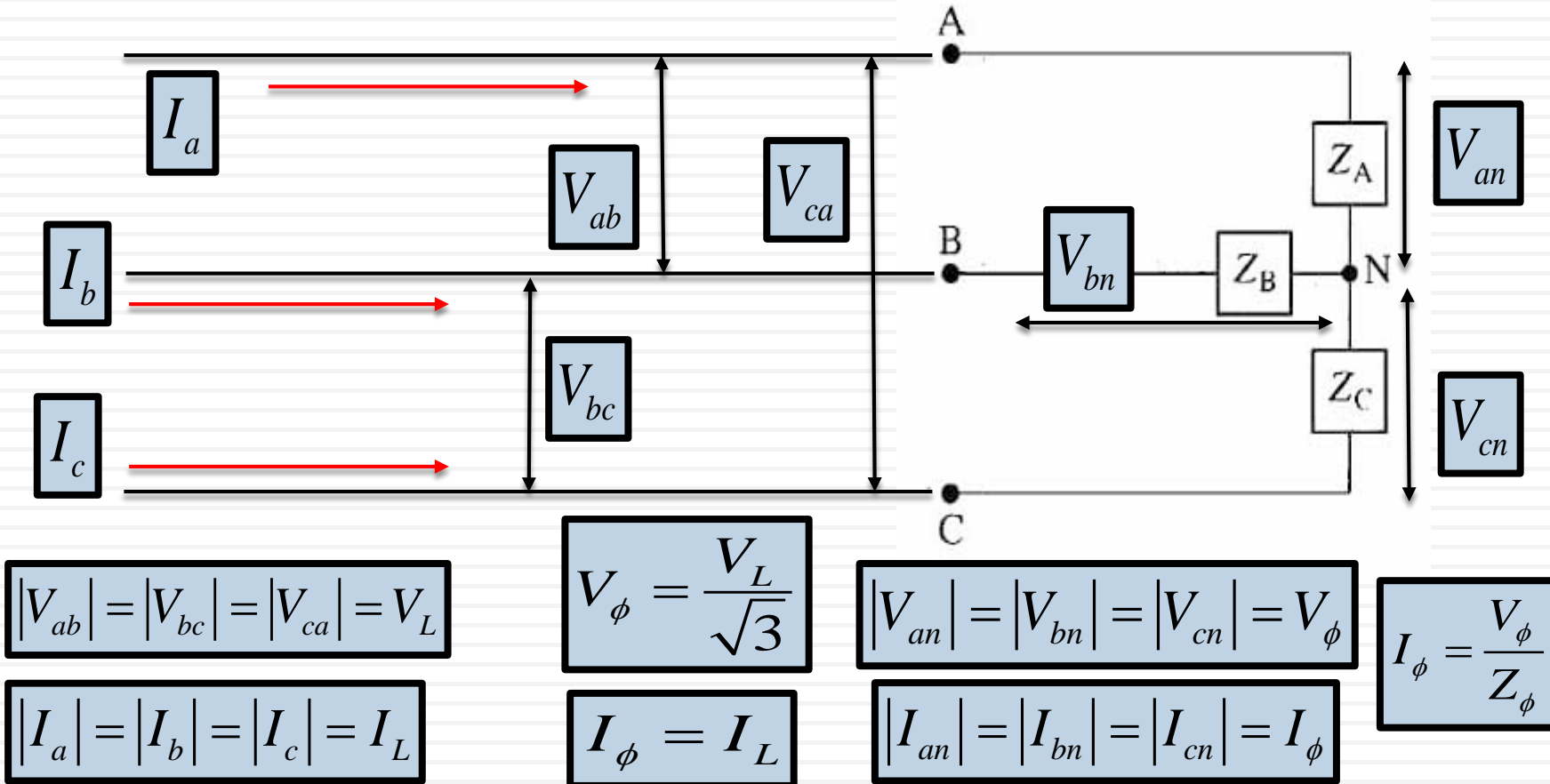


Revision: Basic Principles

44

3-phase AC Circuits

Balanced Delta Load ($Z_A = Z_B = Z_C$)

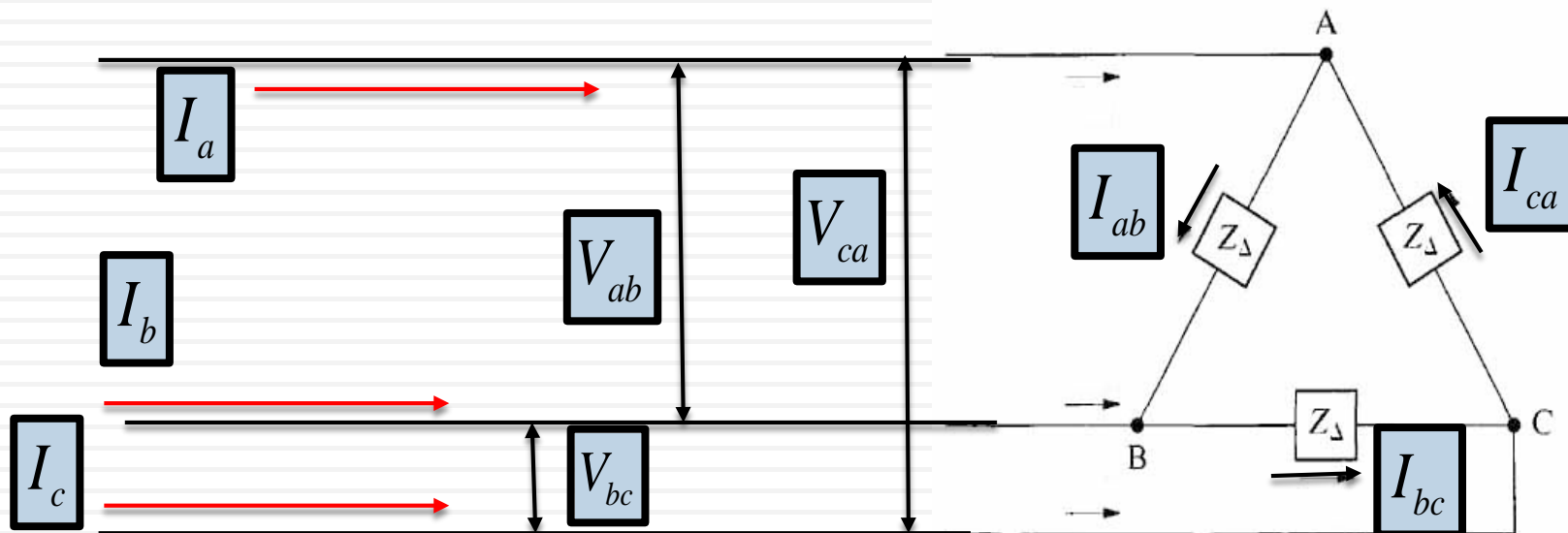

$$|V_{ab}| = |V_{bc}| = |V_{ca}| = V_L$$

$$V_\phi = V_L$$


$$|I_a| = |I_b| = |I_c| = I_L$$

$$|I_{ab}| = |I_{bc}| = |I_{ca}| = I_\phi$$

Revision: Basic Principles

45


3-phase AC Circuits

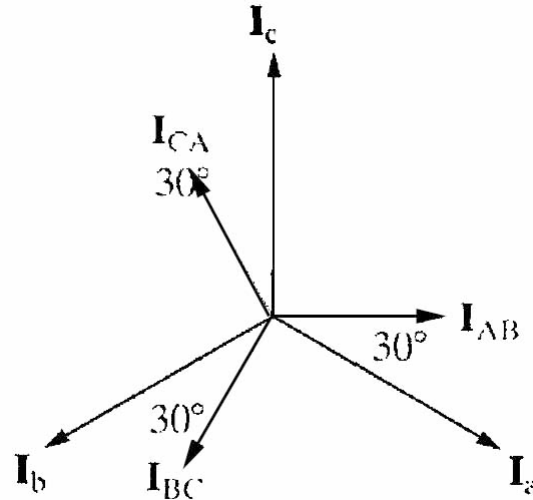

$$I_a = I_{ab} - I_{ca} = \sqrt{3}I_\phi \angle -30^\circ$$

$$I_b = I_{bc} - I_{ab}$$

$$I_c = I_{ca} - I_{bc}$$

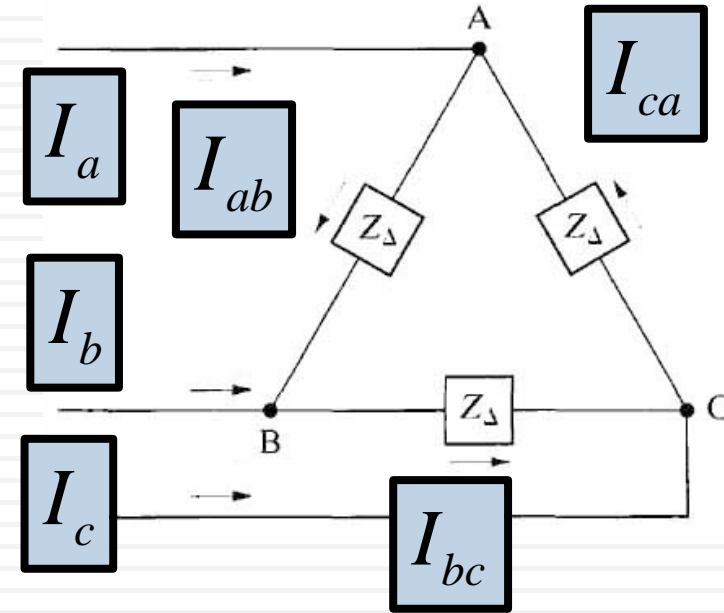

$$|I_{ab}| = |I_{bc}| = |I_{ca}| = I_\phi$$

$$|I_a| = |I_b| = |I_c| = I_L = \sqrt{3}I_\phi$$

Revision: Basic Principles

46

3-phase AC Circuits

Star

$$V_L = \sqrt{3}V_\phi$$

$$I_\phi = I_L$$

Delta

$$V_L = V_\phi$$

$$I_L = \sqrt{3}I_\phi$$

3-phase power = 3 x per phase power

$$P = 3V_\phi I_\phi \cos \Phi = \sqrt{3}V_L I_L \cos \Phi$$

Active Power (W)

$$Q = 3V_\phi I_\phi \sin \Phi = \sqrt{3}V_L I_L \sin \Phi$$

Reactive Power (VAR)

$$S = 3V_\phi I_\phi = \sqrt{3}V_L I_L$$

Apparent Power (VA)

$$\text{Power Factor} = \frac{P}{S}$$