

TRANSFORMERS

Electrical Machines – Elective Course for ELC

Transformer

1

- Construction
- Theory of Operation
- Equivalent Circuit
- Transformer Rating
- Efficiency
- Voltage Regulation
- Tests
- Applications

Transformer: Introduction

3

What's a transformer?

*It's a stationary electric device used to transfer electric energy from one circuit to another (mostly of different voltage levels but with the same frequency). The two circuits are electrically isolated and the energy transfer occurs through **magnetic induction** between the two circuits.*

It is not an energy conversion device.



Transformer: Introduction

4

What's a transformer?

video

Transformer: Introduction


5

Transformer Applications

1. *In power transmission and distribution systems.*
2. *When the required voltage is different from the supply voltage.*
3. *To provide electrical isolation for circuits.*
4. *For matching circuits to change the impedance.*
5. *In measuring and control instruments (current and potential transformers)*

Transformer: Introduction

6 Transformer Applications

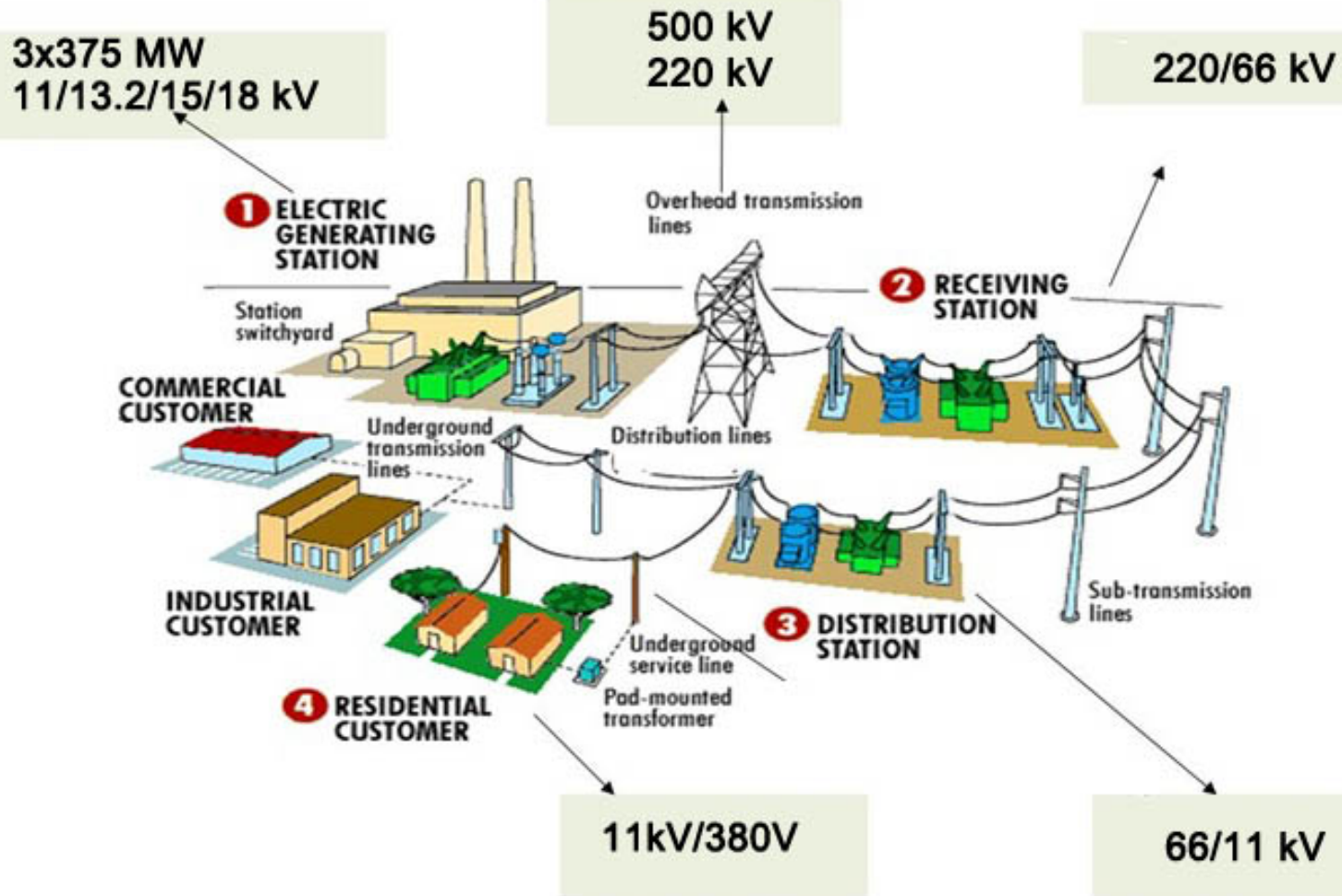

Transformer: Construction

7

- *It consists of two or more coils of wire (windings) wrapped around a common ferromagnetic core.*
- *The winding connected to the supply is called the Primary Winding, while the winding connected to the load is called Secondary Winding.*
- *The transformer windings wires are made of high conductivity copper.*
- *The transformer core is made of insulated steel laminations.*

Transformer

8


Single-phase transformer



Transformer

9

Construction


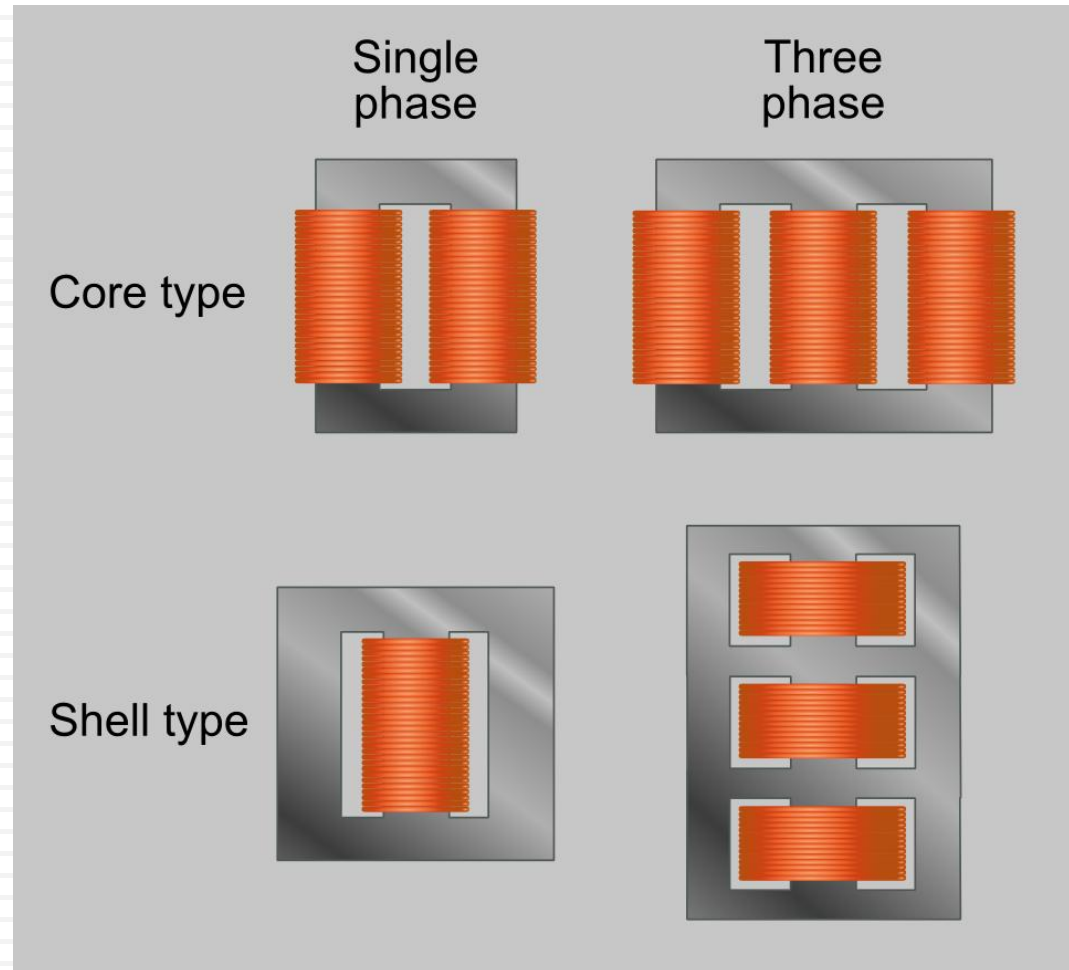


Transformer

10

Construction


Silicon-Steel Laminated core

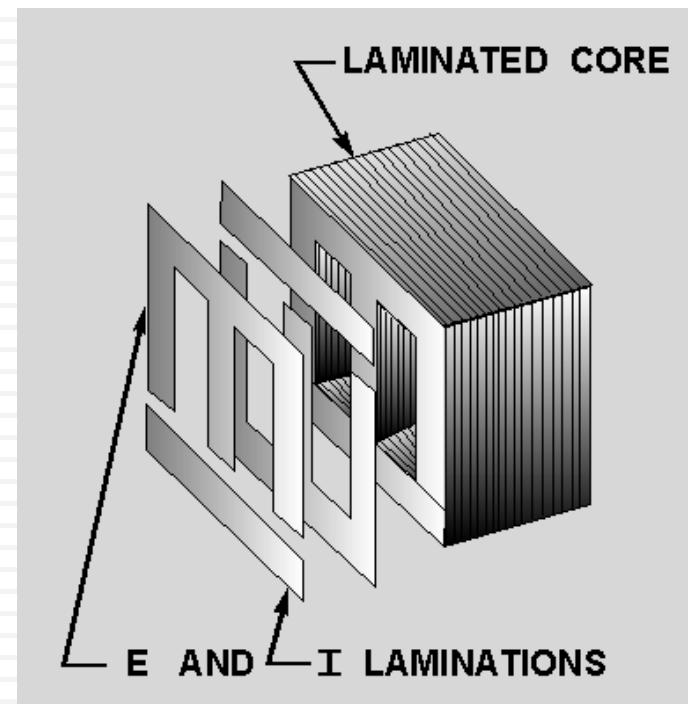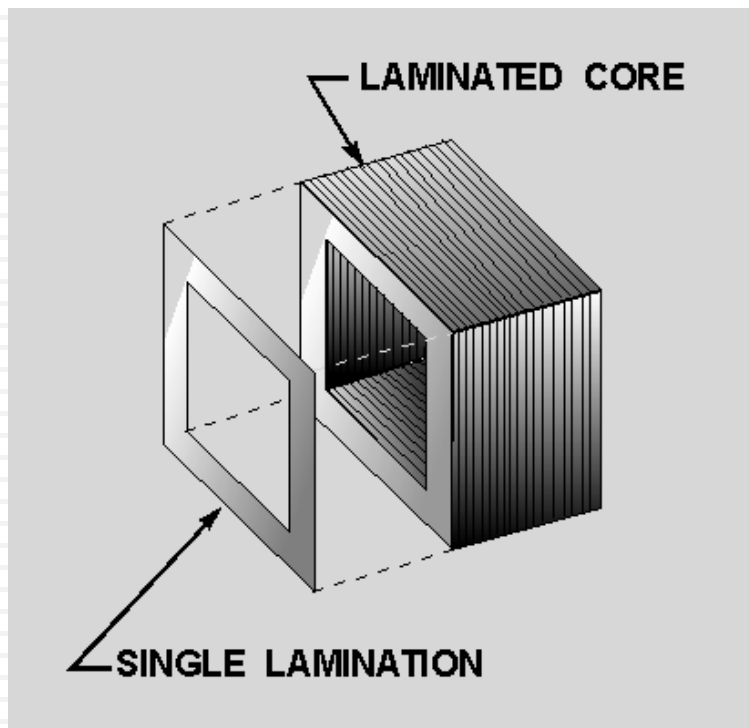

Transformer


11

Single-phase transformer

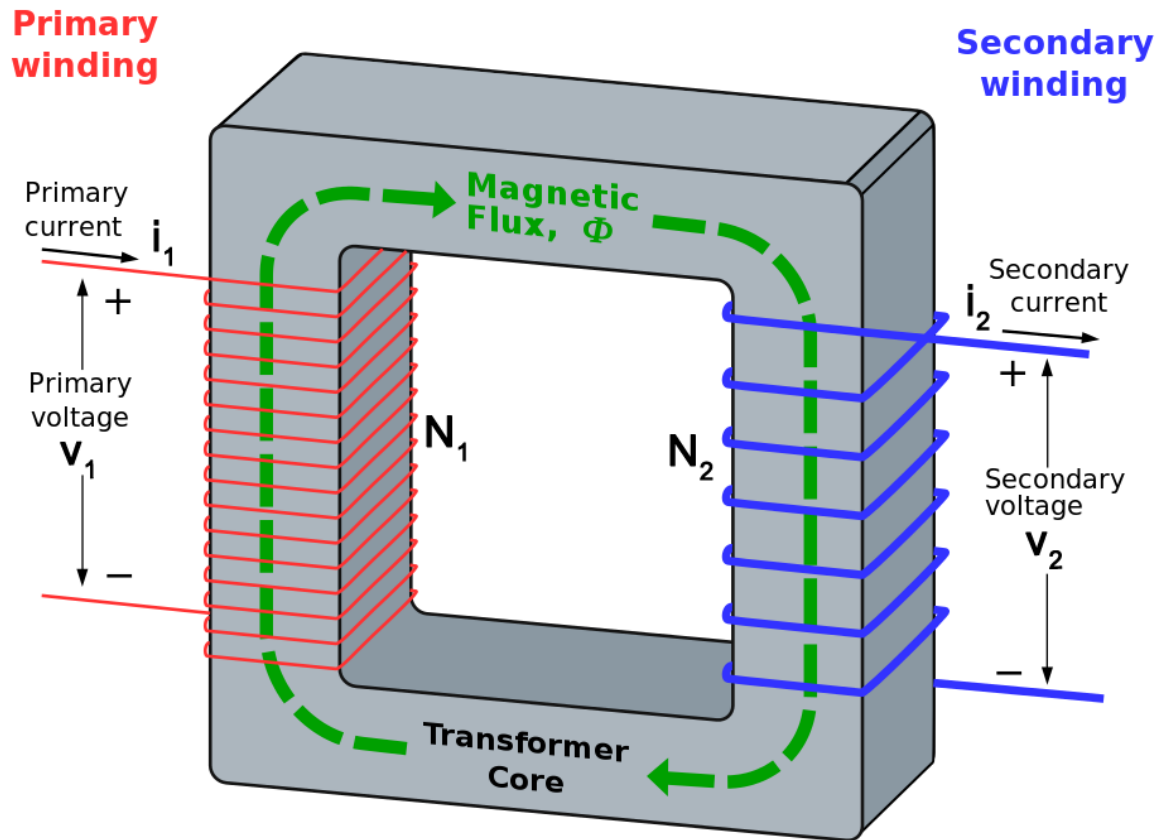

Transformer

12

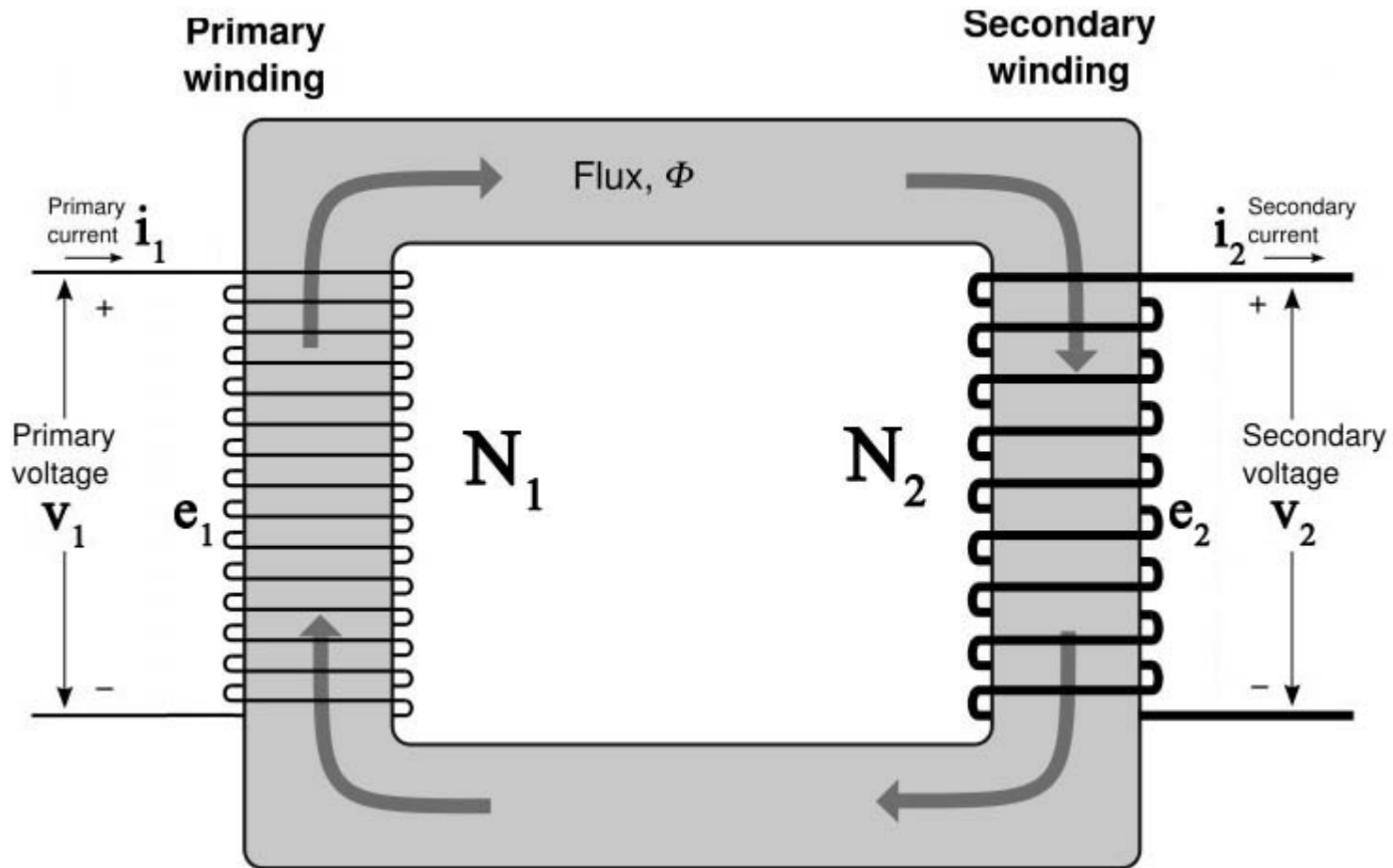

Transformer

13

Ideal Transformer

- $R_{\text{coil}} = \text{zero}$

- $\mu \rightarrow \infty$

- No leakage flux

- No core losses

$$v_1 = N_1 \frac{d\phi_1}{dt}$$

$$v_2 = N_2 \frac{d\phi_2}{dt}$$

Since no leakage

$$\phi_1 = \phi_2$$

$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$

$$\frac{e_1}{e_2} = \frac{N_1}{N_2}$$

Transformer

14

Ideal Transformer

$$V_{1m} \sin(\omega t) = N_1 \frac{d\phi}{dt}$$



$$\phi = \frac{V_{1m}}{\omega N_1} \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$\phi_m = \frac{V_{1m}}{\omega N_1}$$



$$V_{1rms} = \frac{2\pi f N_1 \phi_m}{\sqrt{2}}$$

$$V_1 = 4.44 f \phi_m N_1$$

$$V_2 = 4.44 f \phi_m N_2$$

$$E_1 = 4.44 f \phi_m N_1$$

$$E_2 = 4.44 f \phi_m N_2$$

Transformer


15

Ideal Transformer



$$N_1 i_1 - N_2 i_2 = \phi \mathcal{R}$$

Since $\mu \rightarrow \infty$

$$\mathcal{R} = \text{zero}$$

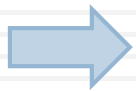

$$\frac{N_1}{N_2} = \frac{i_2}{i_1}$$

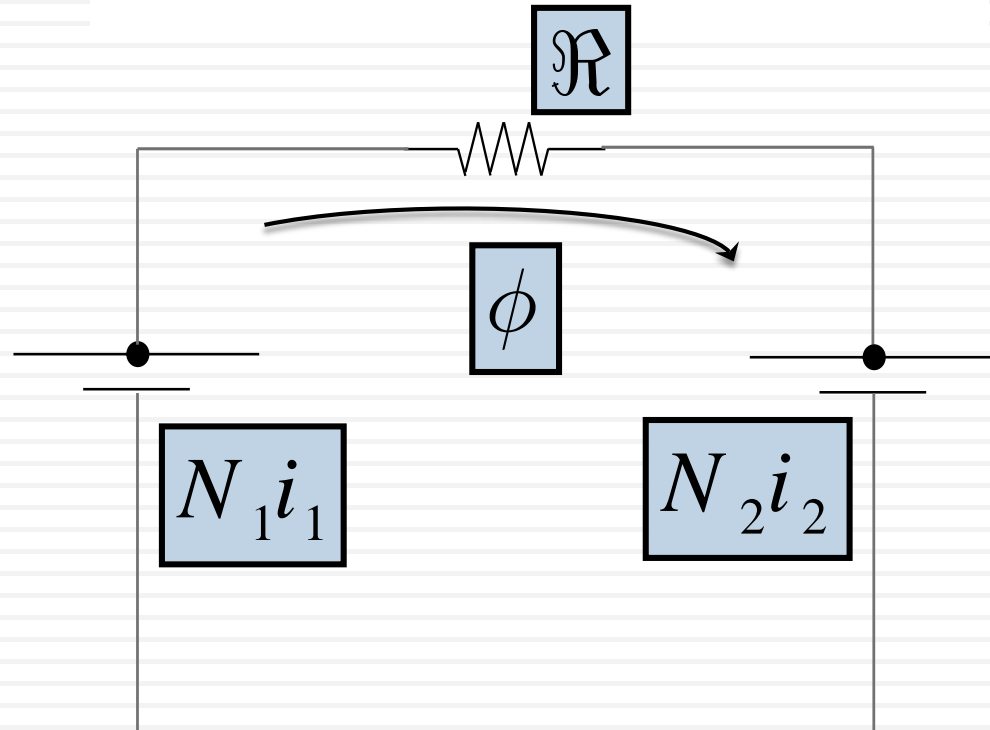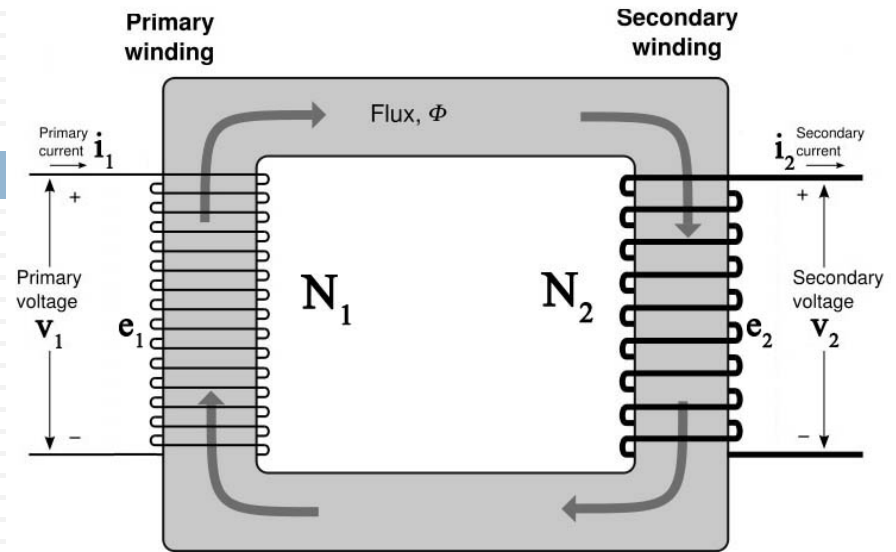

Transformer


16

Ideal Transformer

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2}$$

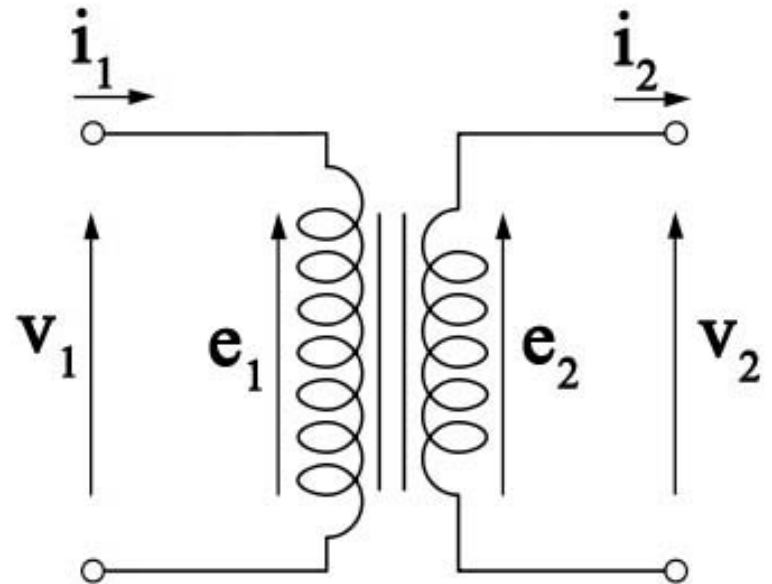

Transformer

17

Ideal Transformer

$$S = V_1 I_1 = V_2 I_2$$


$$S = V_2 I_2 = I_2^2 Z_L$$

$$V_2 = I_2 Z_L$$

$$V_1 \frac{N_2}{N_1} = I_1 \frac{N_1}{N_2} Z_L$$

$$V_1 = I_1 Z_L \left(\frac{N_1}{N_2} \right)^2$$
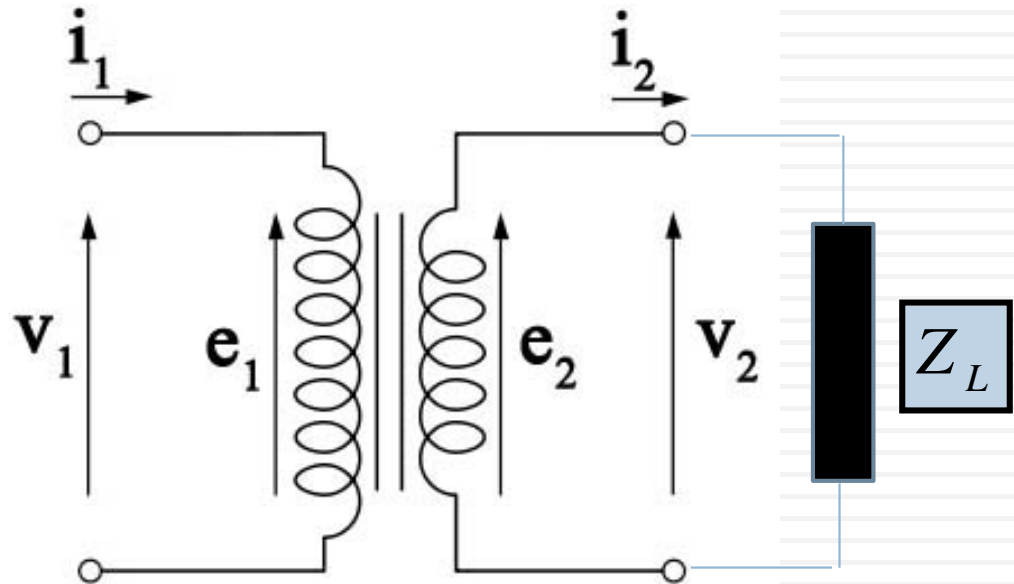
$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \quad \frac{I_2}{I_1} = \frac{N_1}{N_2}$$




Transformer

18

Ideal Transformer

$$V_1 = I_1 Z_L \left(\frac{N_1}{N_2} \right)^2$$

$$V_1 = I_1 Z_L'$$

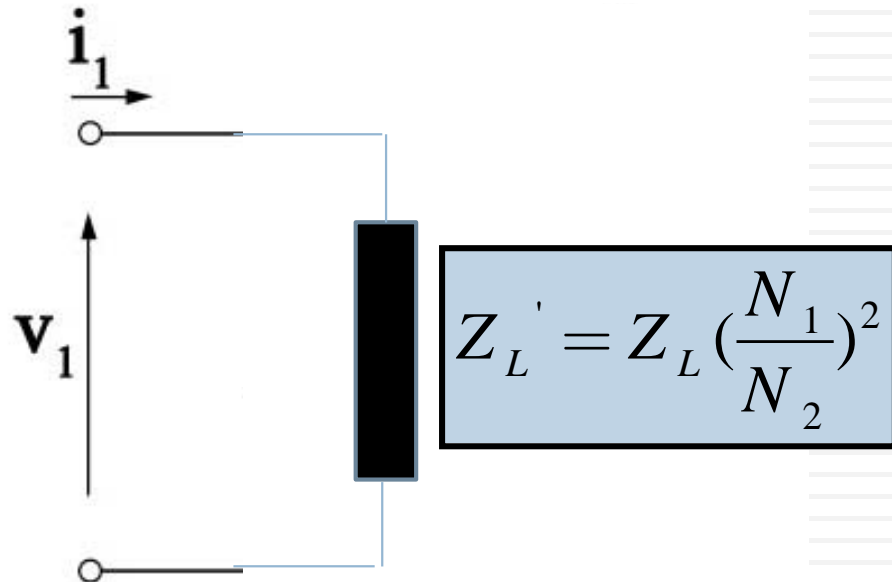

Load referred to the primary

Transformer: Equivalent Circuit

19

Case B: - $R_{\text{coil}} = \text{zero}$

- $\mu \neq \infty$

- No leakage flux

- No core losses


At No-load: ($i_2 = \text{zero}$)

$$N_1 i_\mu = \phi \mathfrak{R}$$

From Faraday's Law

$$\phi = \frac{V_{1m}}{\omega N_1} \sin\left(\omega t - \frac{\pi}{2}\right)$$
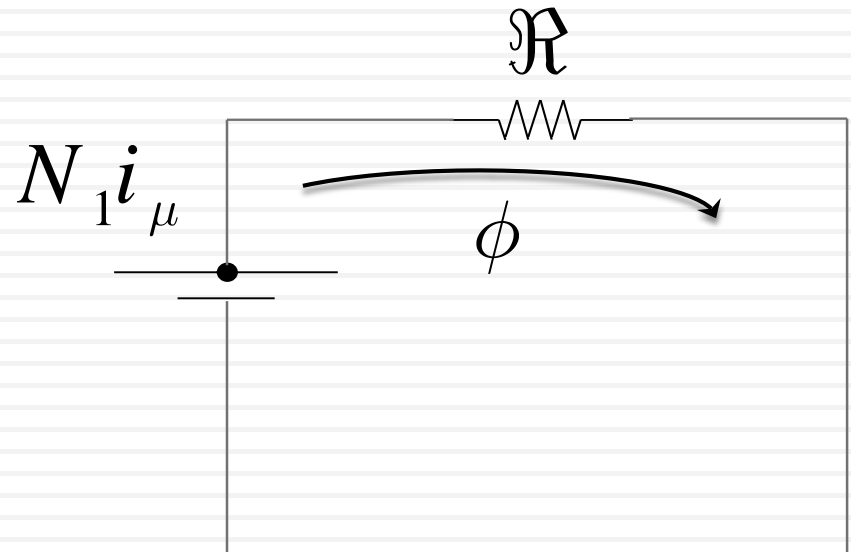
$$i_\mu = \frac{V_{1m}}{\omega N_1^2 \mathfrak{R}} \sin\left(\omega t - \frac{\pi}{2}\right)$$



Transformer: Equivalent Circuit

20

$$i_{\mu} = \frac{V_{1m}}{\omega L_{core}} \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$I_{\mu} = \frac{V_1}{j\omega L_{core}}$$




$$X_{\mu} = \omega L_{core}$$

If the transformer is loaded:

$$N_1 i_1 - N_2 i_2 = \phi \mathcal{R}$$

$$N_1 i_1 - N_2 i_2 = N_1 i_{\mu}$$

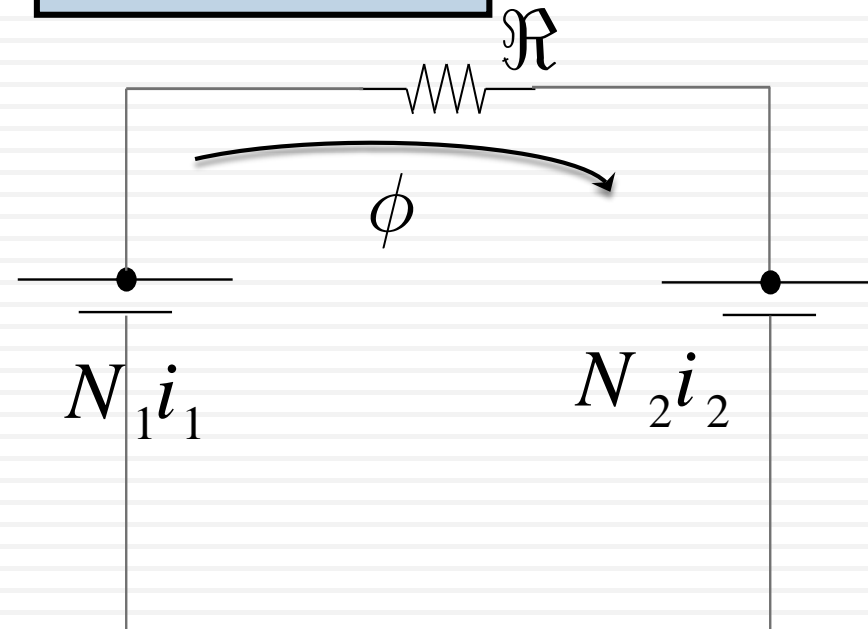


Transformer: Equivalent Circuit

21

$$i_{\mu} = i_1 - \frac{N_2}{N_1} i_2$$

$$i_1 = i_{\mu} + \frac{N_2}{N_1} i_2$$

$$i_2' = \frac{N_2}{N_1} i_2$$

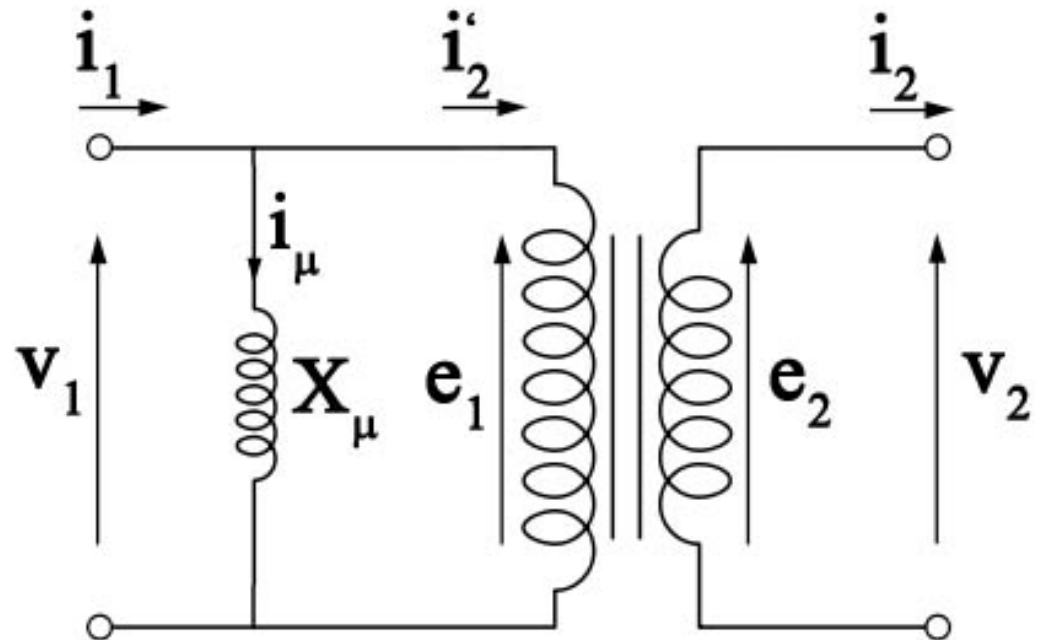

Transformer: Equivalent Circuit

22

Case C: - $R_{\text{coil}} = \text{zero}$



- $\mu \neq \infty$

- No leakage flux

- core losses exist.

Core (iron) losses

1. Eddy Current Losses

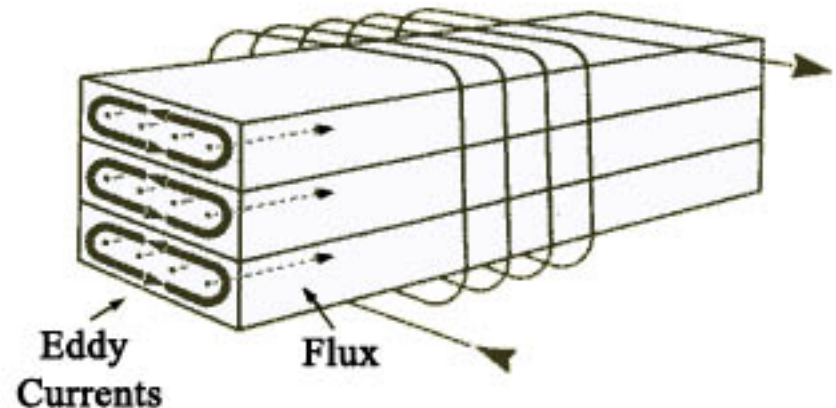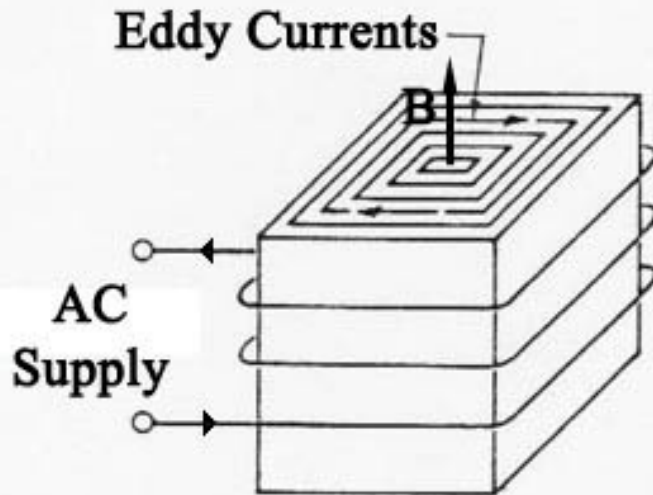

$$P_e \propto B_m^2 f^2 (\text{thickness})^2$$

$$P_e = k_e B_m^2 f^2 (\text{thickness})^2$$


$$W/m^3$$

Transformer: Equivalent Circuit


23

Case C:

2. Hysteresis Losses

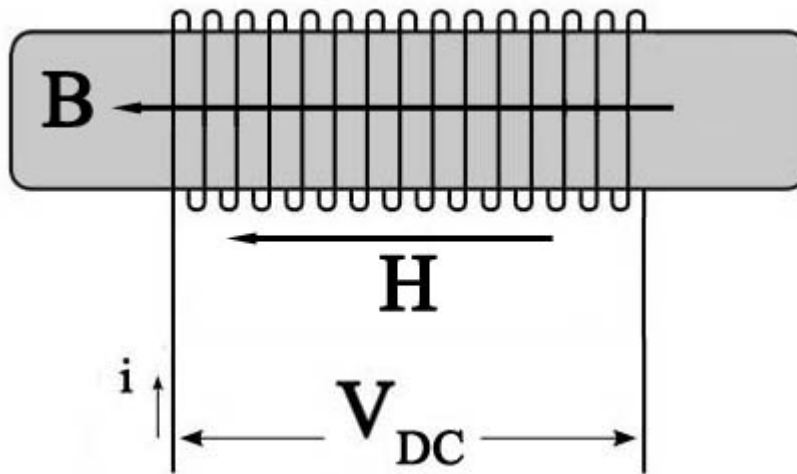

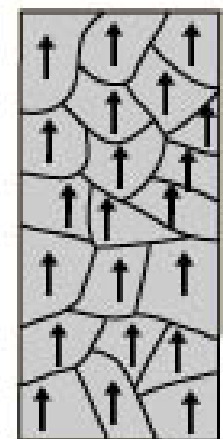In bulk material the domains usually cancel, leaving the material unmagnetized.




Externally applied magnetic field.

Transformer: Equivalent Circuit

24

Case C:

2. Hysteresis Losses

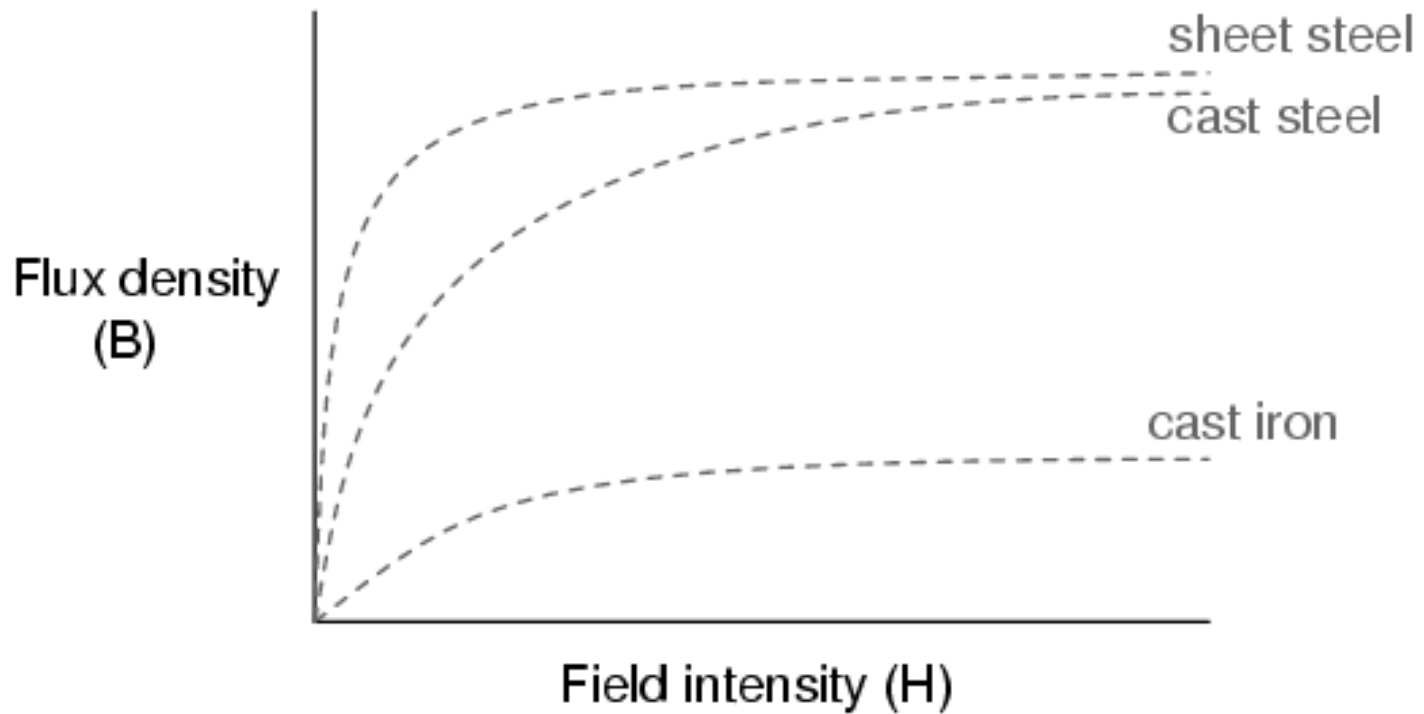




BH Curve (Magnetization Curve)

Transformer: Equivalent Circuit

25

Case C:

2. Hysteresis Losses

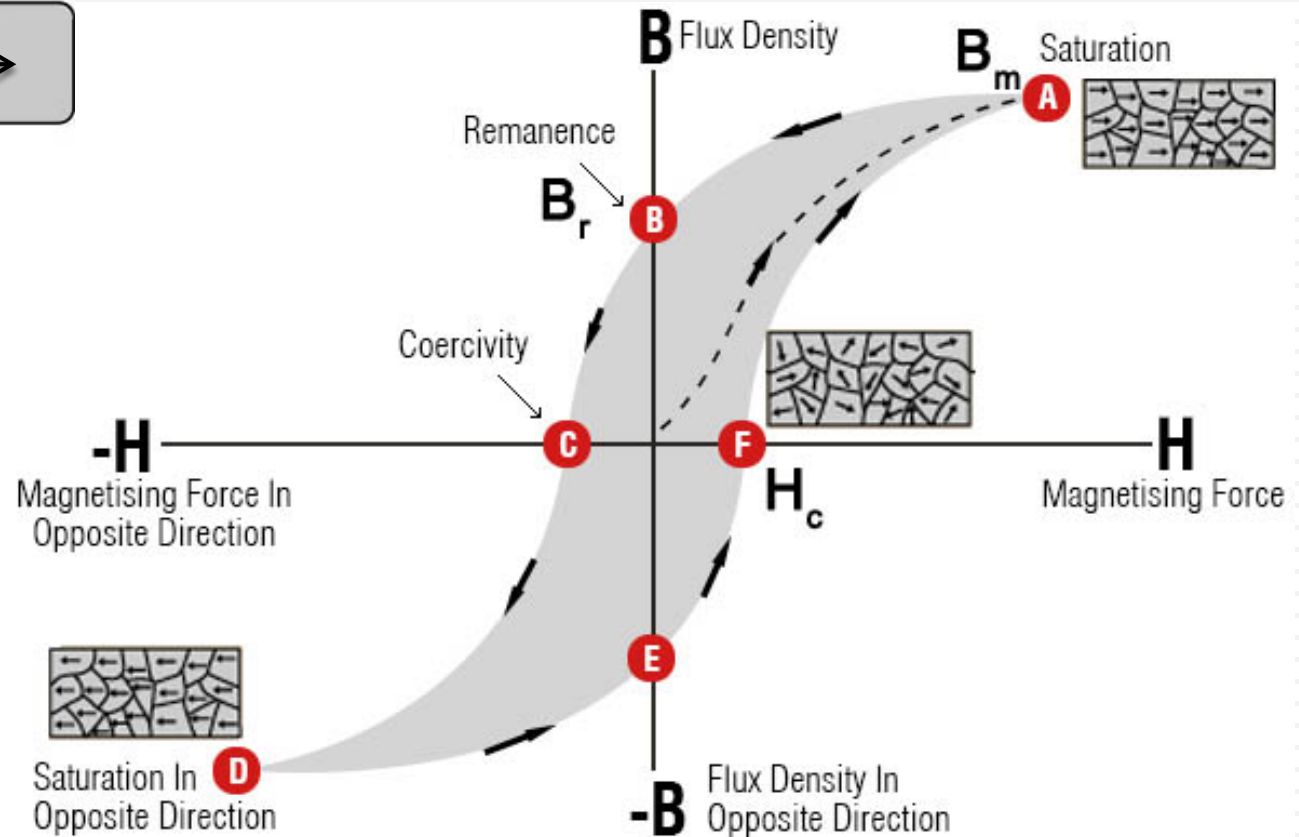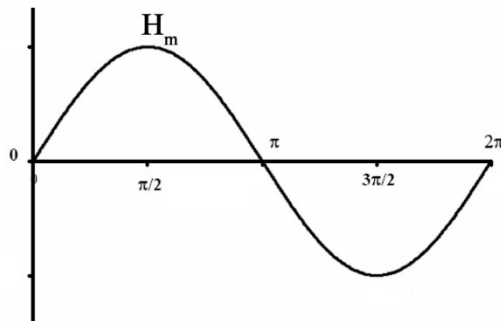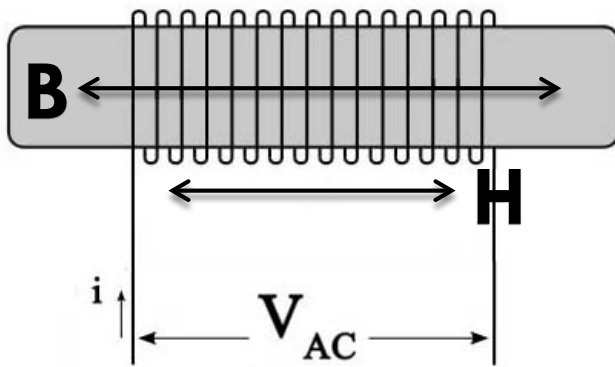

Transformer: Equivalent Circuit

26


Case C:

2. Hysteresis Losses

$$w_1 = \int_{-B_r}^{B_m} \underline{H} \underline{dB}$$

$$w_2 = \int_{B_m}^{-B_r} \underline{H} \underline{dB}$$
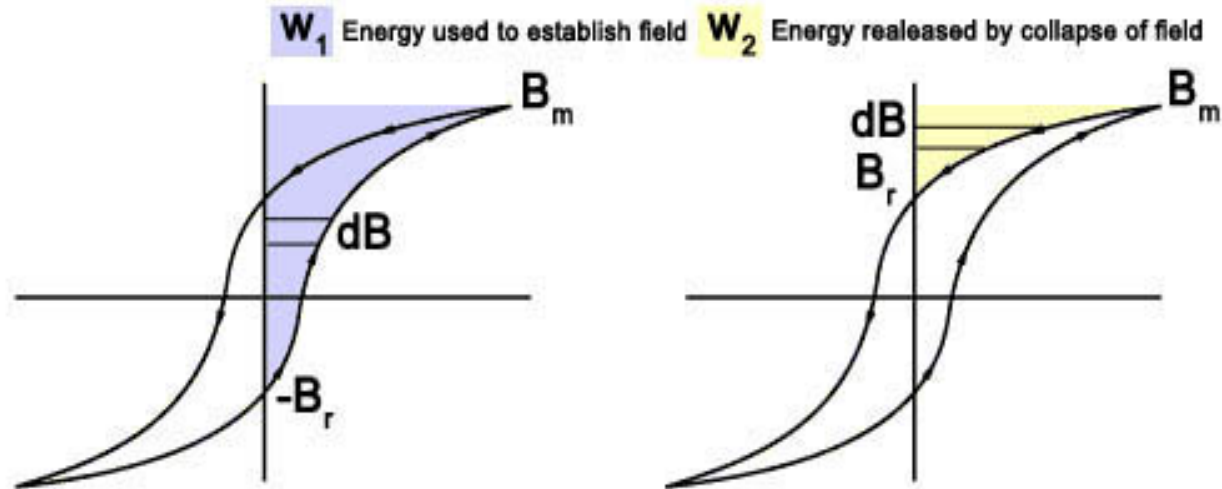
$$H \text{ (A.m}^{-1}\text{)} \times B \text{ (T = J.A}^{-1}\text{.m}^{-2}\text{)} = \text{J.m}^{-3}$$



Energy lost /unit volume/cycle = $2(w_1 - w_2)$ = area of the loop

Transformer: Equivalent Circuit

27

Case C:

2. Hysteresis Losses

$$P_h \propto B^n f (\text{volume})$$

$$P_h = k_h B^n f \quad \boxed{W/m^3}$$

n depends on the material (1.6 – 2.4)

Total core losses:

$$P_c = k_e B^2 f^2 (\text{thickness})^2 + k_h B^n f \quad \boxed{W/m^3}$$

Since f is usually constant


$$\begin{aligned} \Rightarrow & \boxed{P_c \propto B^2} \Rightarrow \boxed{P_c \propto \phi^2} \Rightarrow \boxed{P_c \propto V^2} \end{aligned}$$

Transformer: Equivalent Circuit

28

Case C:

$$P_c = \frac{V_1^2}{R_c}$$

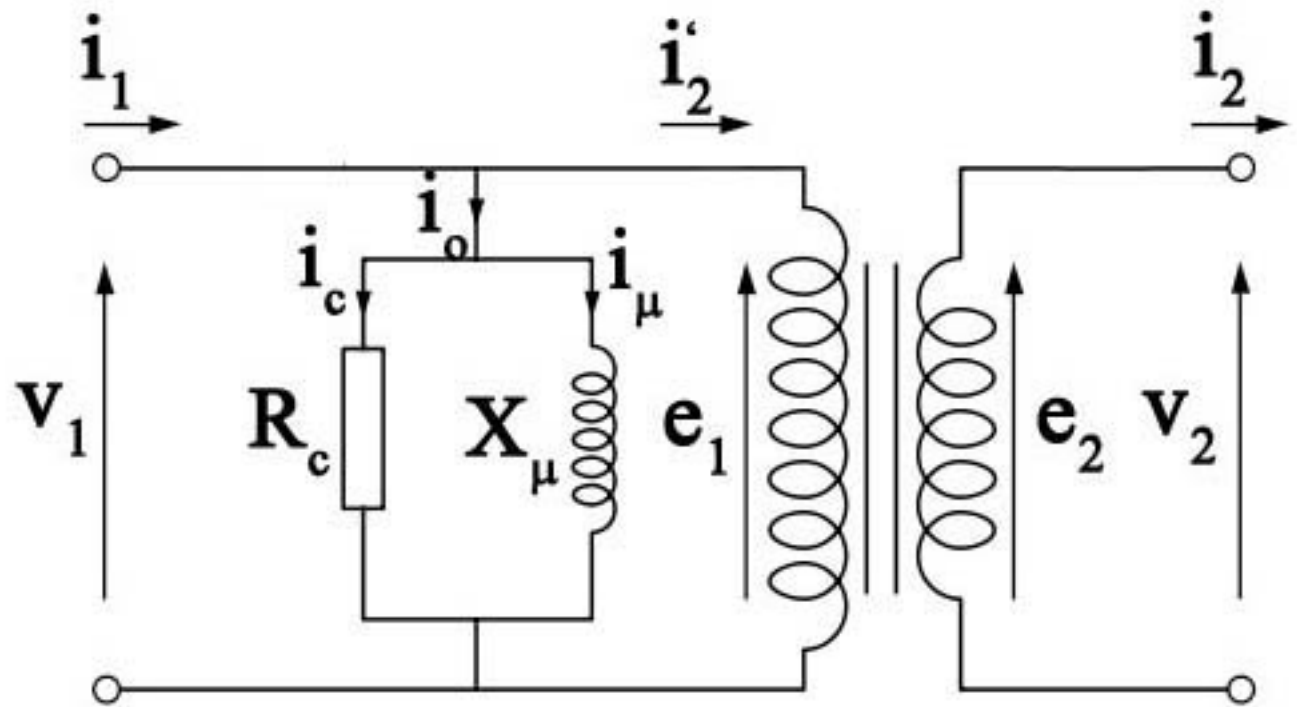

Transformer: Equivalent Circuit


29

Case D: - $R_{\text{coil}} = \text{zero}$

- $\mu \neq \infty$

- Leakage flux exists.

- core losses exist.

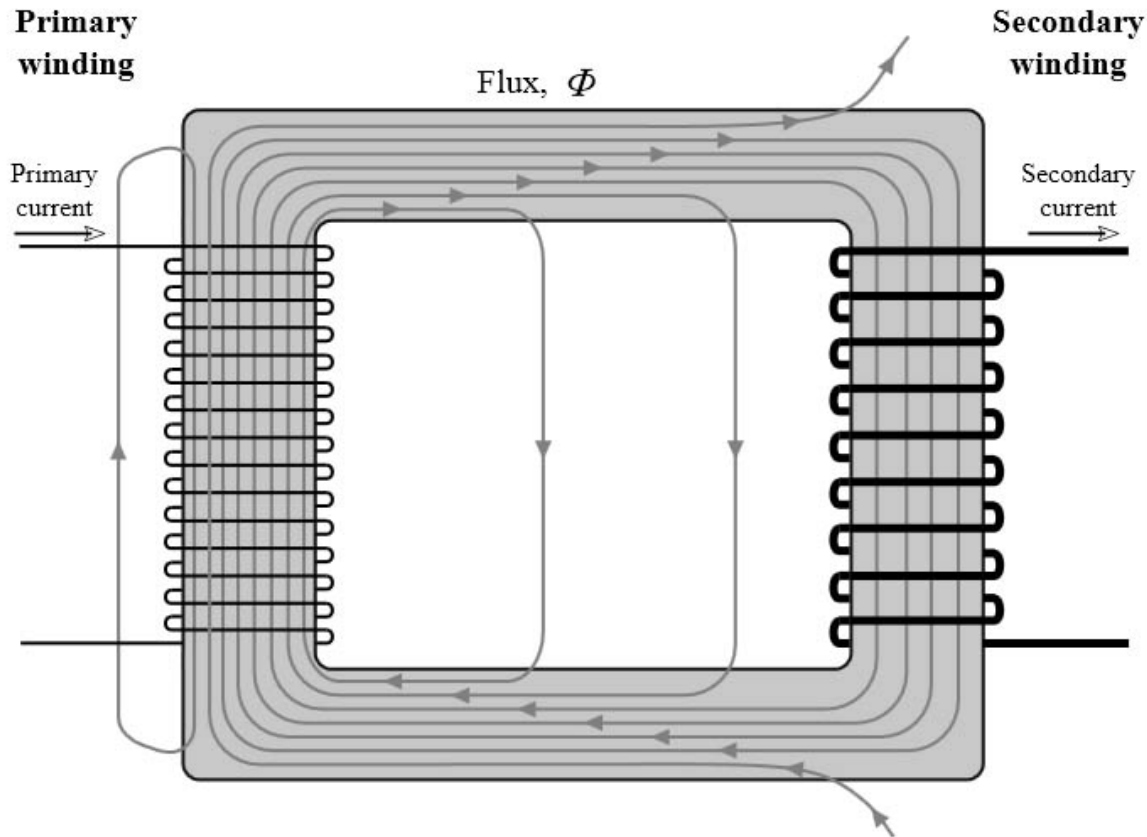

Transformer: Equivalent Circuit

30


Case D:

$$\phi_1 = \phi + \phi_{l1} \quad (1)$$

$$\phi_2 = \phi - \phi_{l2} \quad (2)$$

$$N_1 i_1 = \phi_{l1} \mathcal{R}_{l1} \quad (3)$$
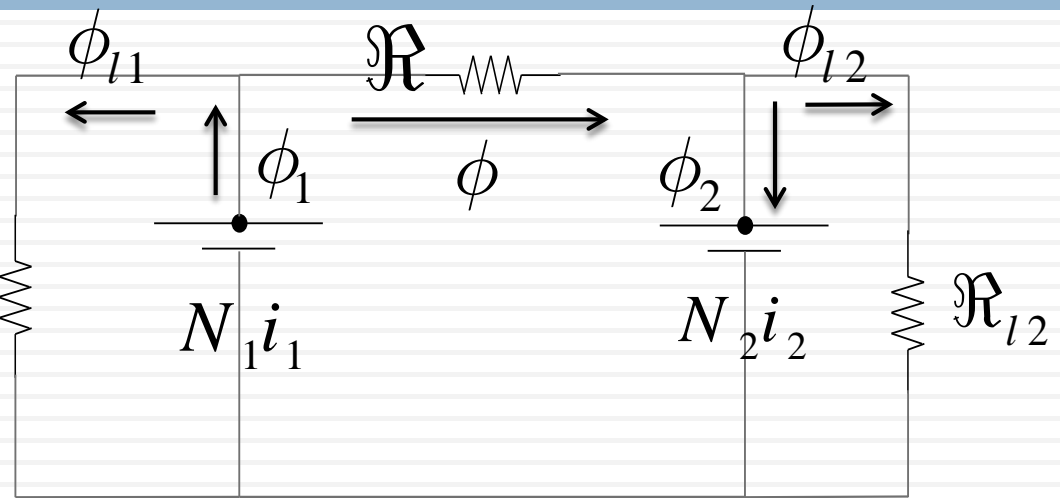
$$N_2 i_2 = \phi_{l2} \mathcal{R}_{l2} \quad (4)$$



From (1) & (3)

$$N_1 \frac{d\phi_1}{dt} = N_1 \frac{d\phi}{dt} + N_1 \frac{d\phi_{l1}}{dt}$$




$$v_{l1} = N_1 \frac{d\phi_{l1}}{dt} = \frac{N_1^2}{R_{l1}} \frac{di_1}{dt}$$

Transformer: Equivalent Circuit

31

Case D:

From (2) & (4)

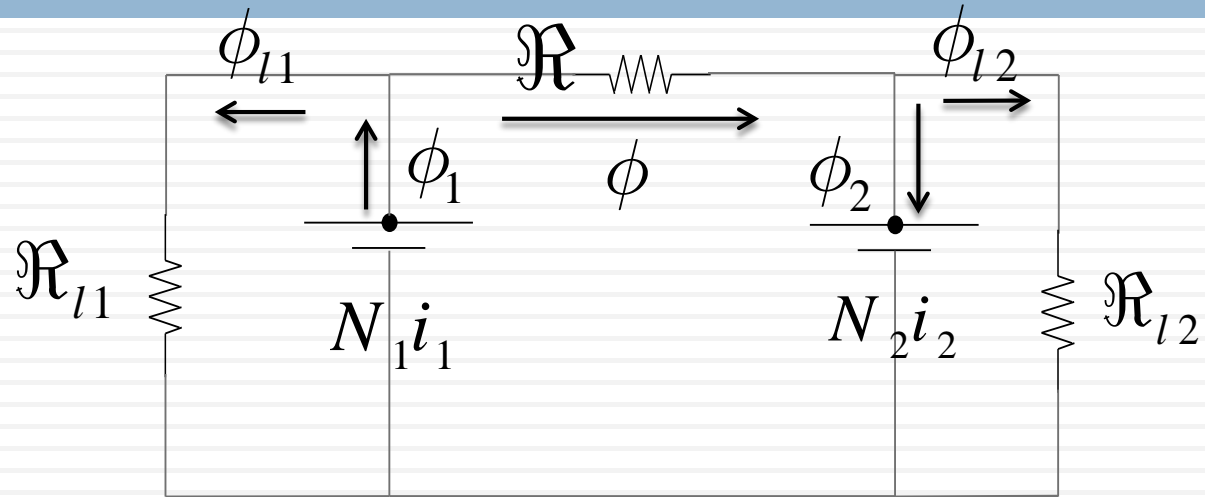

$$N_2 \frac{d\phi_2}{dt} = N_2 \frac{d\phi}{dt} - N_2 \frac{d\phi_{l2}}{dt}$$



$$v_{l2} = N_2 \frac{d\phi_{l2}}{dt} = \frac{N_2^2}{R_{l2}} \frac{di_2}{dt}$$

From Faraday's law

$$v_1 = N_1 \frac{d\phi_1}{dt}$$

$$v_2 = N_2 \frac{d\phi_2}{dt}$$

Transformer: Equivalent Circuit

32

Case D:

let


$$e_1 = N_1 \frac{d\phi}{dt}$$

$$e_2 = N_2 \frac{d\phi}{dt}$$



$$v_1 = e_1 + v_{l1}$$

$$v_2 = e_2 - v_{l2}$$

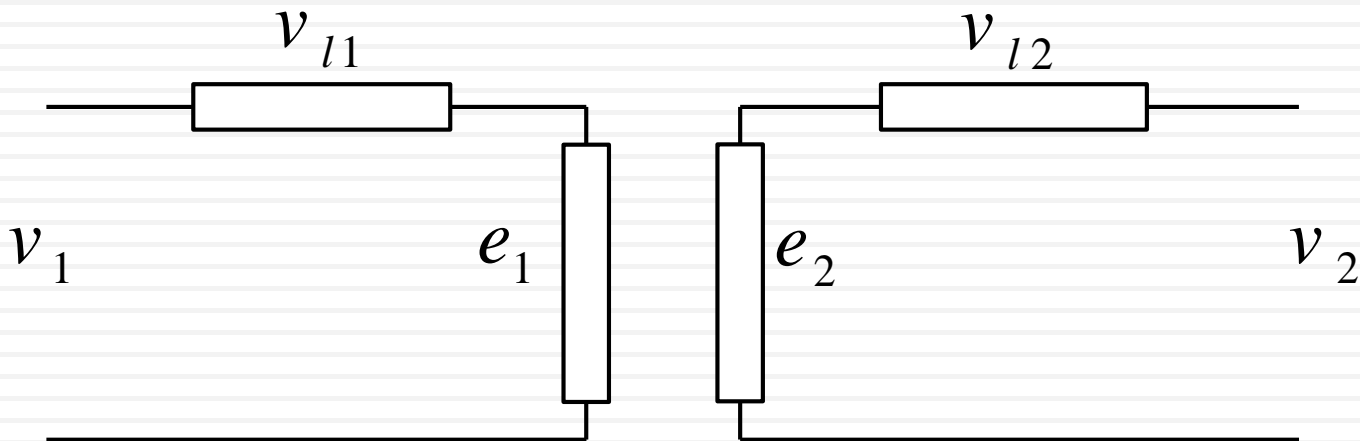

Transformer: Equivalent Circuit

33

Case D:

$$v_{l1} = \frac{N_1^2}{R_{l1}} \frac{di_1}{dt}$$

$$v_{l1} = L_{l1} \frac{di_1}{dt}$$

$$v_{l2} = \frac{N_2^2}{R_{l2}} \frac{di_2}{dt}$$

$$v_{l2} = L_{l2} \frac{di_2}{dt}$$

$$V_{l1} = j\omega L_{l1} I_1$$

$$V_{l2} = j\omega L_{l2} I_2$$

$$V_{l1} = jX_{l1} I_1$$

$$V_{l2} = jX_{l2} I_2$$

$$L_{l1} = \frac{N_1^2}{R_{l1}}$$

$$L_{l2} = \frac{N_2^2}{R_{l2}}$$


Transformer: Equivalent Circuit

34

Case D:

$$V_{l1} = jX_{l1}I_1$$


$$V_{l2} = jX_{l2}I_2$$

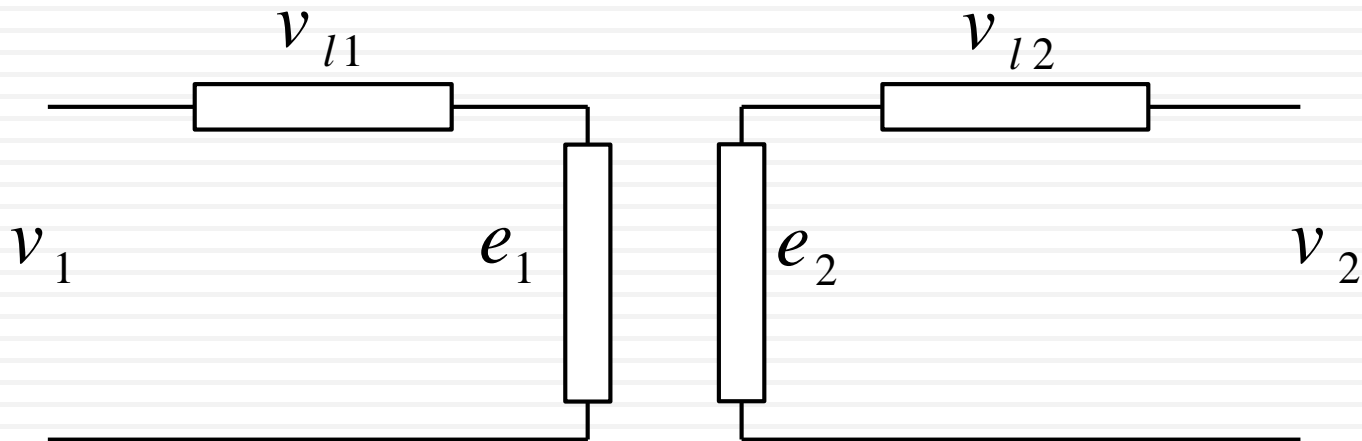

Transformer: Equivalent Circuit

35

Case D:

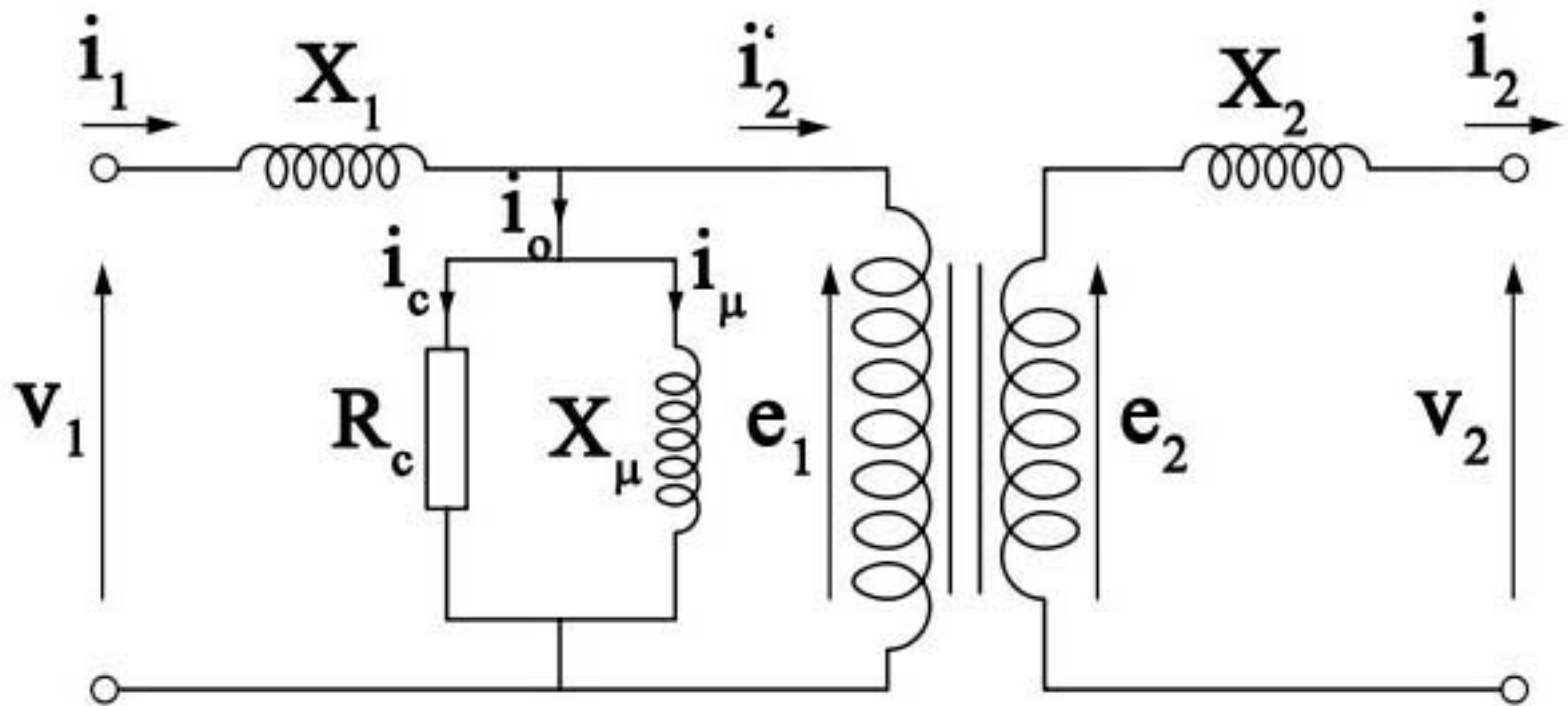

Transformer: Equivalent Circuit


36

Case E: - $R_{\text{coil}} \neq \text{zero}$

- $\mu \neq \infty$


- Leakage flux exists.

- core losses exist.

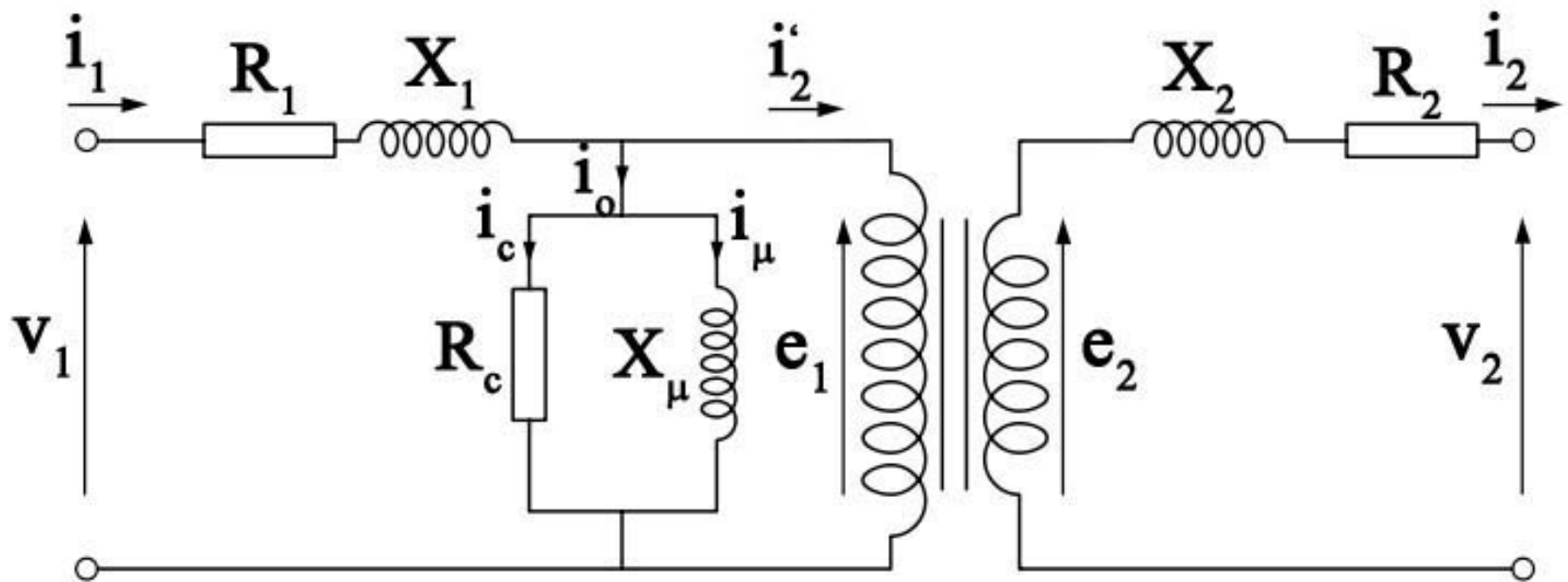

Exact Equivalent Circuit of the Transformer

Transformer: Equivalent Circuit

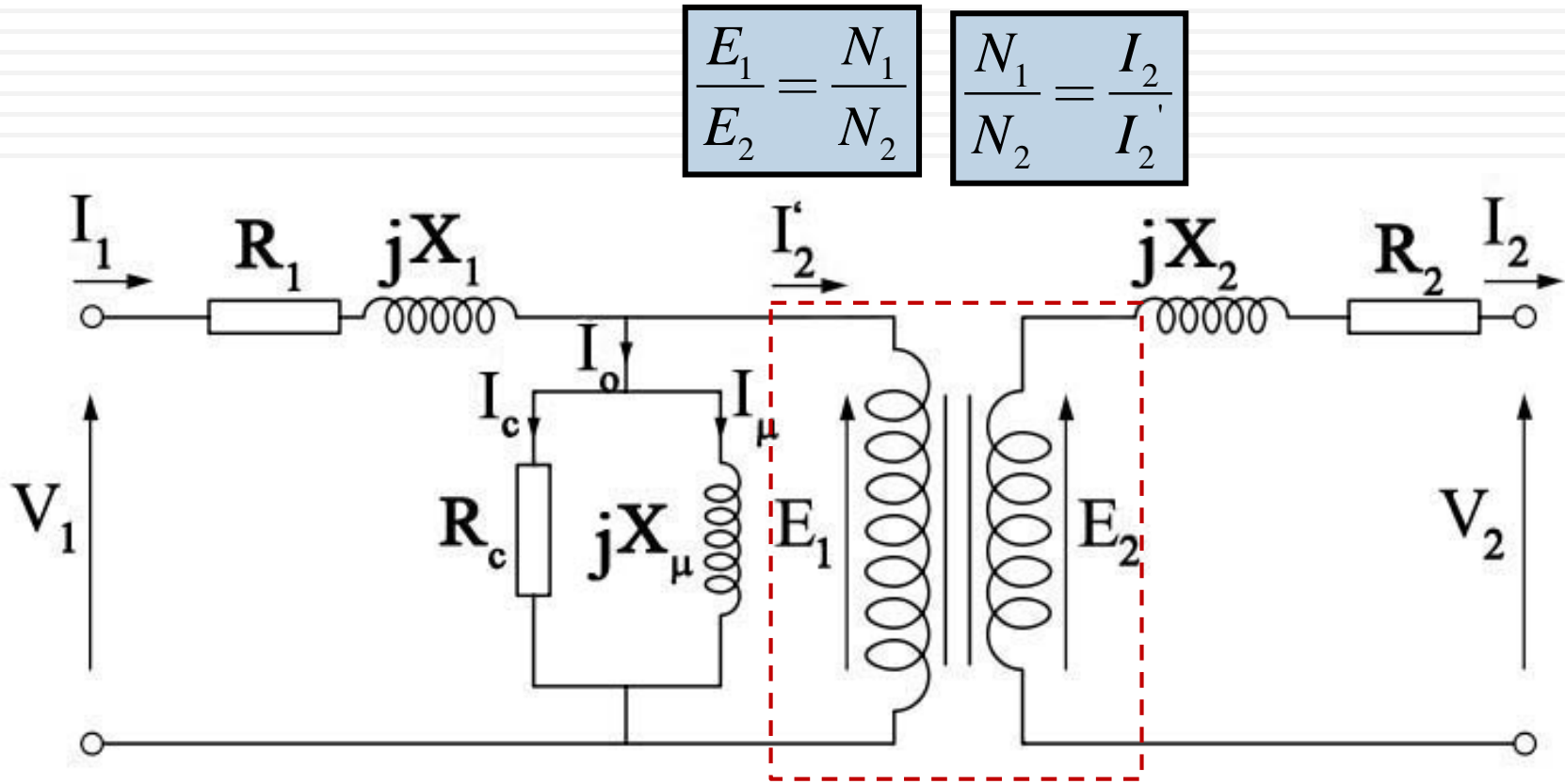

Exact Equivalent Circuit of the Transformer

Transformer: Equivalent Circuit

R_1 = Resistance of the primary winding

R_2 = Resistance of the secondary winding

X_1 = Leakage Reactance of the primary winding


X_2 = Leakage Reactance of the secondary winding

R_C = Resistance representing the core (iron) losses


X_μ = reactance representing the main flux path

$$R_C \gg X_\mu$$
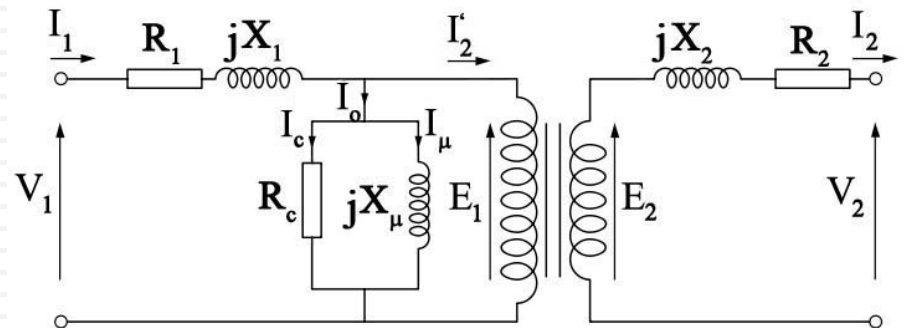
$$R_C \ \& \ X_\mu \gg R_1, X_1 \ \& \ R_2, X_2$$



Transformer: Equivalent Circuit

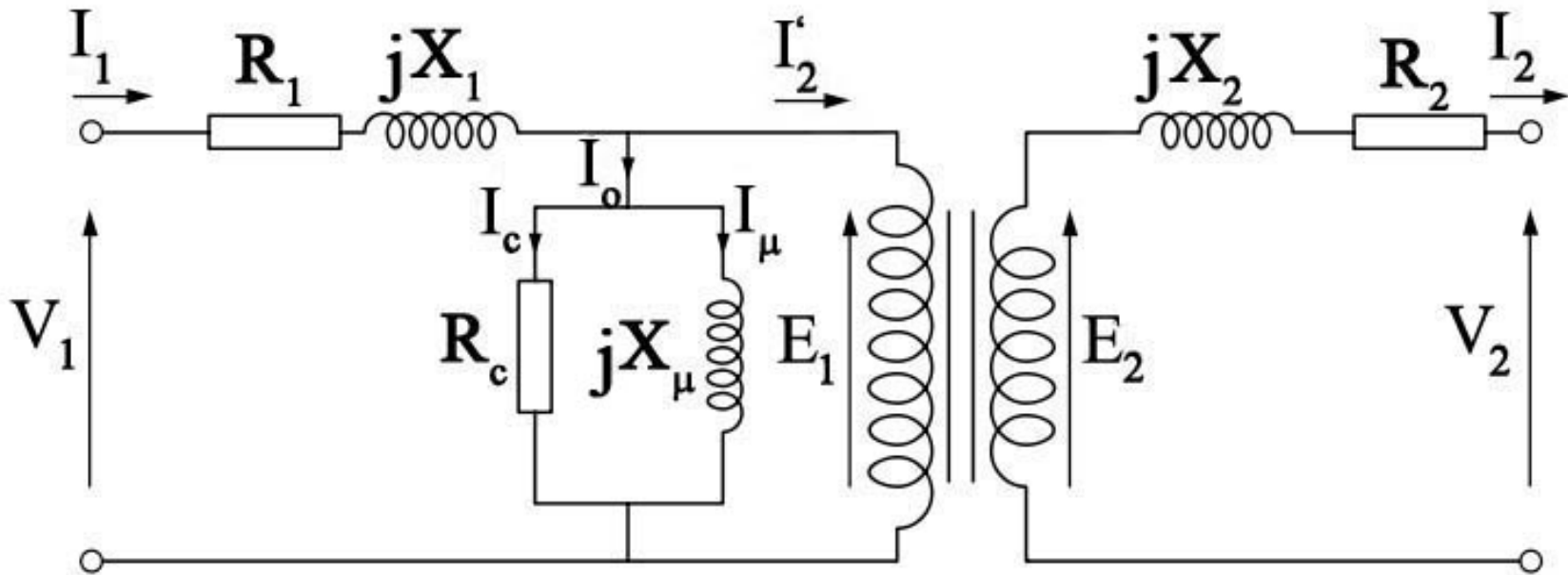

$$E_1 = 4.44 f \phi_m N_1$$

$$E_2 = 4.44 f \phi_m N_2$$

Transformer: Equivalent Circuit

At No-load:

$$I_2 = 0 \quad \longrightarrow \quad I_2' = 0 \quad \longrightarrow \quad E_2 = V_2$$

$$I_1 = I_o \quad I_o = 2 - 5\% I_{FL}$$


$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\frac{N_1}{N_2} = \frac{I_2'}{I_2}$$

$$\longrightarrow I_o (R_1 + jX_1) \quad \text{Small Voltage Drop}$$

$$\longrightarrow V_1 \cong E_1$$
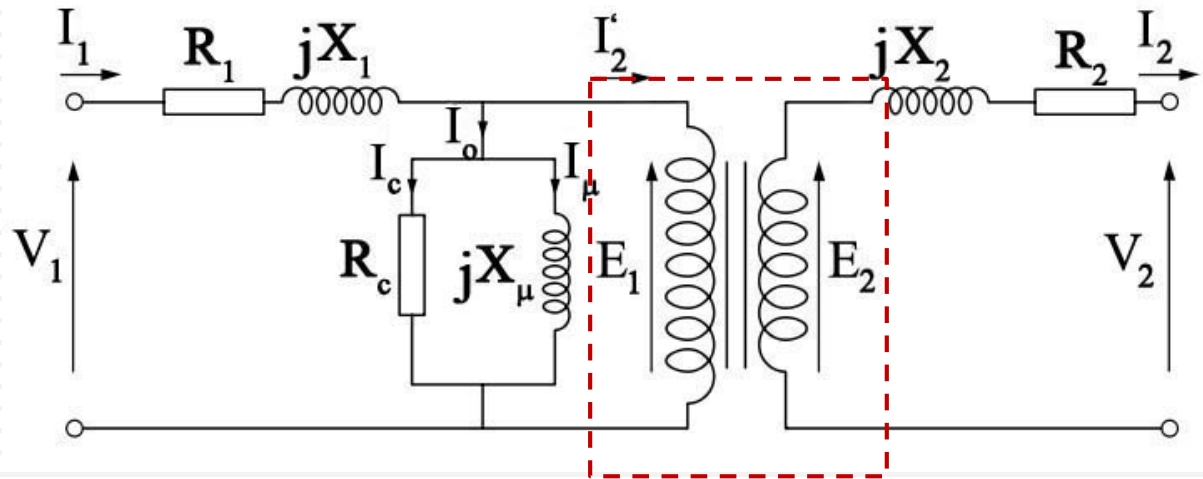
$$\longrightarrow \frac{V_1}{V_2} = \frac{E_1}{E_2} = \frac{N_1}{N_2}$$




Transformer: Equivalent Circuit

At loading:

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\frac{N_1}{N_2} = \frac{I_2}{I_2'}$$

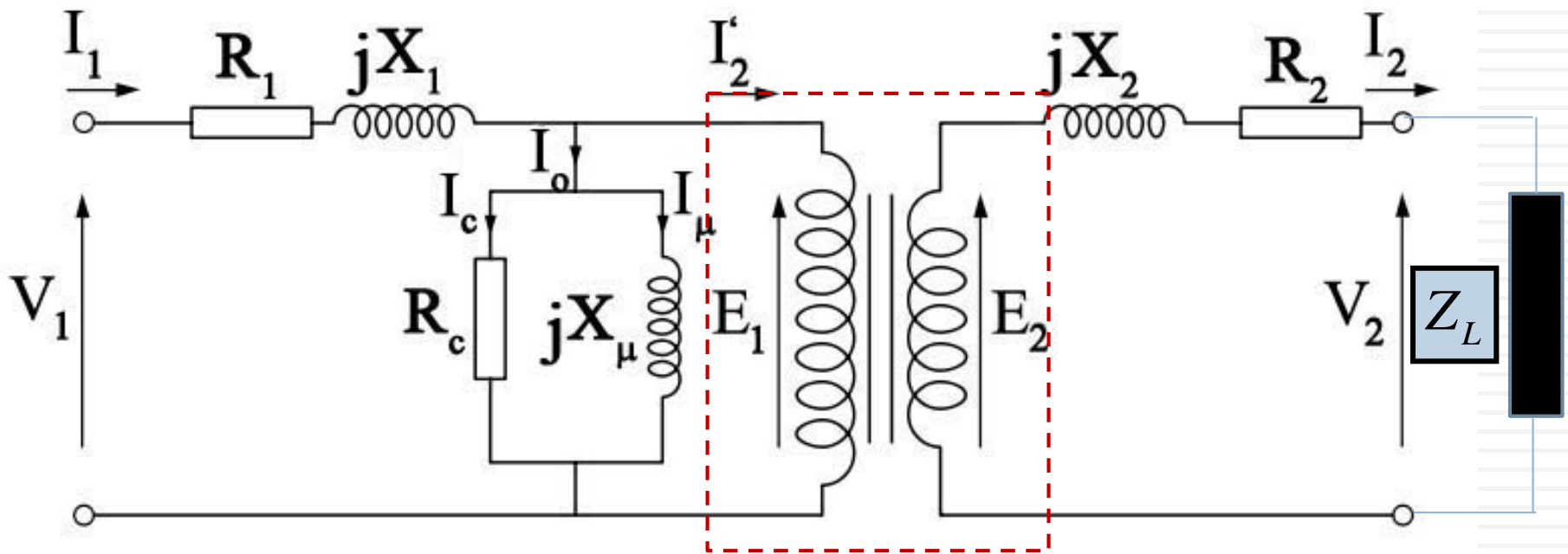

Transformer: Equivalent Circuit


At loading:

$$E_2 = V_2 + I_2(R_2 + jX_2)$$

$$E_1 \frac{N_2}{N_1} = V_2 + I_2' \frac{N_1}{N_2} (R_2 + jX_2)$$

$$E_1 = V_2 \left(\frac{N_1}{N_2} \right) + I_2' \left(\frac{N_1}{N_2} \right)^2 (R_2 + jX_2)$$

$$E_1 = V_2' + I_2' (R_2' + jX_2')$$

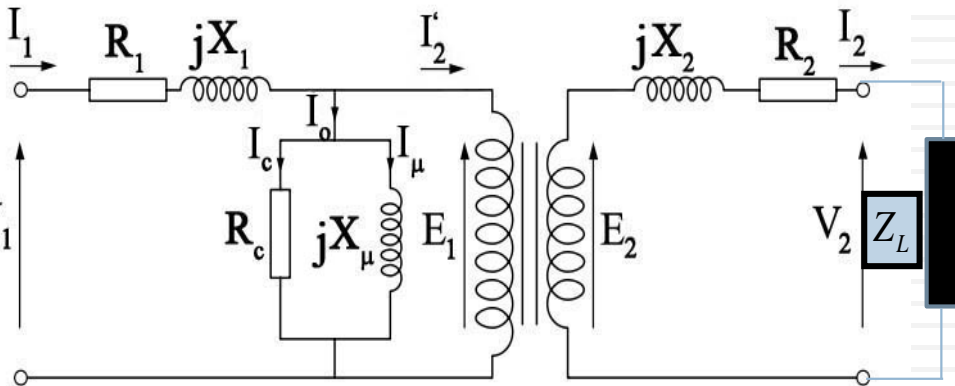

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\frac{N_1}{N_2} = \frac{I_2}{I_2'}$$

$$\frac{V_2'}{V_2} = \frac{N_1}{N_2}$$

$$R_2' = R_2 \left(\frac{N_1}{N_2} \right)^2$$

$$X_2' = X_2 \left(\frac{N_1}{N_2} \right)^2$$


Transformer: Equivalent Circuit

$$E_1 = V_2' + I_2'(R_2' + jX_2')$$

$$\frac{V_2'}{V_2} = \frac{N_1}{N_2}$$

$$R_2' = R_2 \left(\frac{N_1}{N_2}\right)^2$$
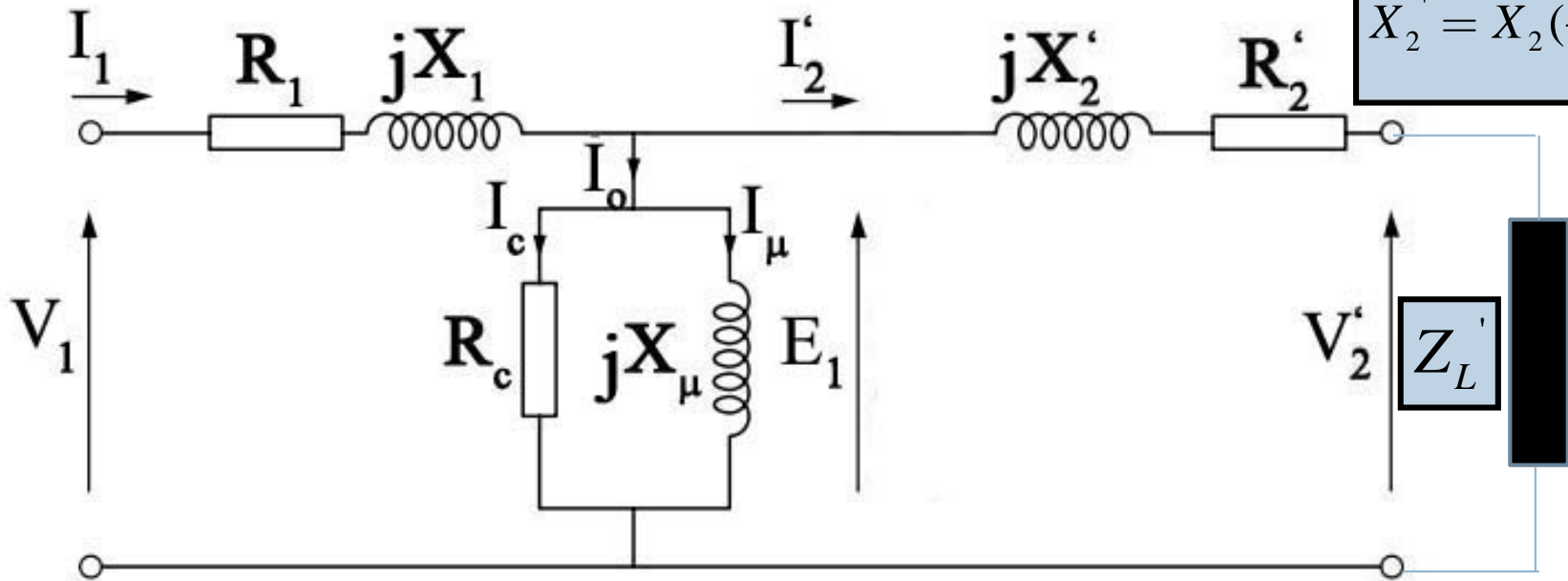
$$X_2' = X_2 \left(\frac{N_1}{N_2}\right)^2$$



Exact Equivalent Circuit referred to Primary

Transformer: Equivalent Circuit

$$\frac{V_1'}{V_1} = \frac{N_2}{N_1}$$


$$\frac{I_1'}{I_1} = \frac{N_1}{N_2}$$

$$R_c' = R_c \left(\frac{N_2}{N_1}\right)^2$$

$$X_{\mu}' = X_{\mu} \left(\frac{N_2}{N_1}\right)^2$$


$$R_1' = R_1 \left(\frac{N_2}{N_1}\right)^2$$
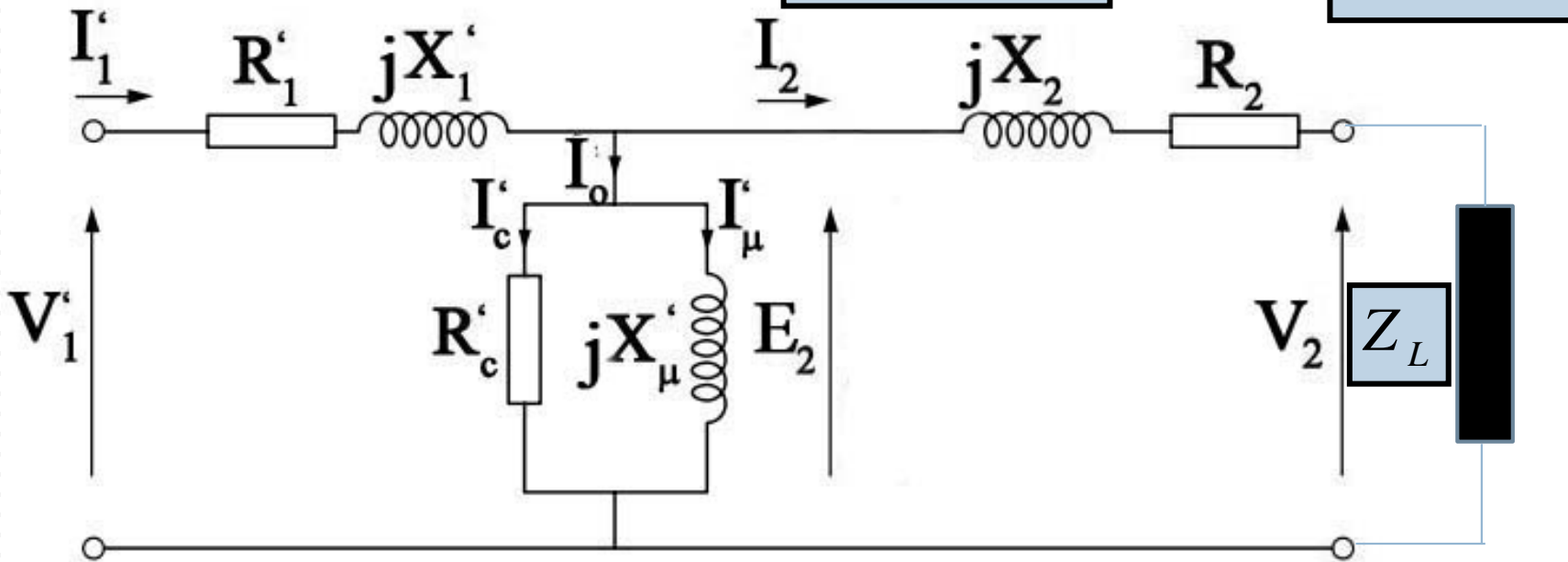
$$X_1' = X_1 \left(\frac{N_2}{N_1}\right)^2$$



Exact Equivalent Circuit referred to Secondary


Transformer: Equivalent Circuit

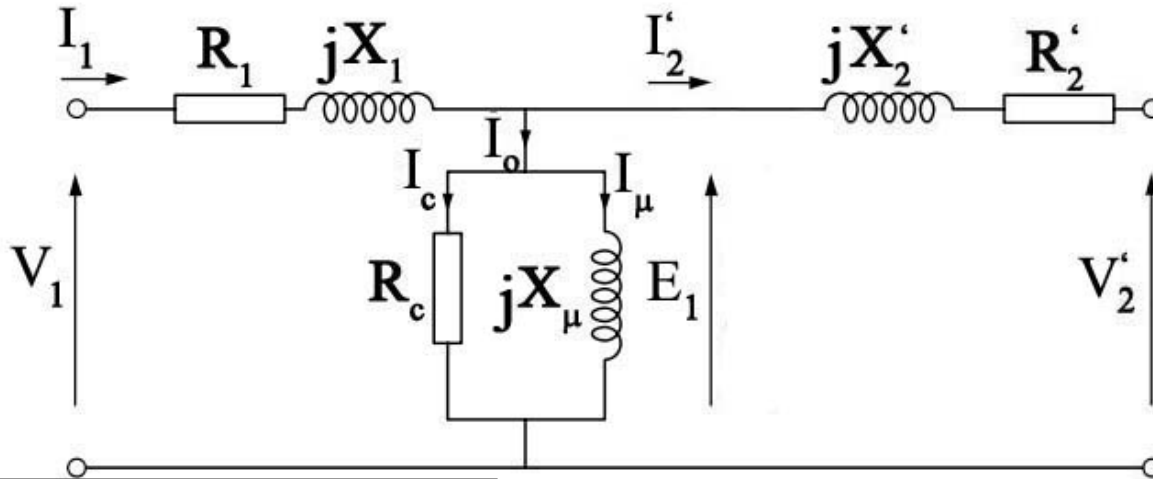


$$V_1 = E_1 + I_1(R_1 + jX_1)$$

$$I_1 = I_o + I_2'$$

$$V_1 = E_1 + (I_o + I_2')(R_1 + jX_1)$$

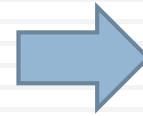

$$E_1 = V_2' + I_2'(R_2' + jX_2')$$

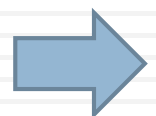


$$V_1 = V_2' + I_o(R_1 + jX_1) + I_2'[(R_1 + jX_1) + (R_2' + jX_2')]$$

Small Voltage Drop

Transformer: Equivalent Circuit
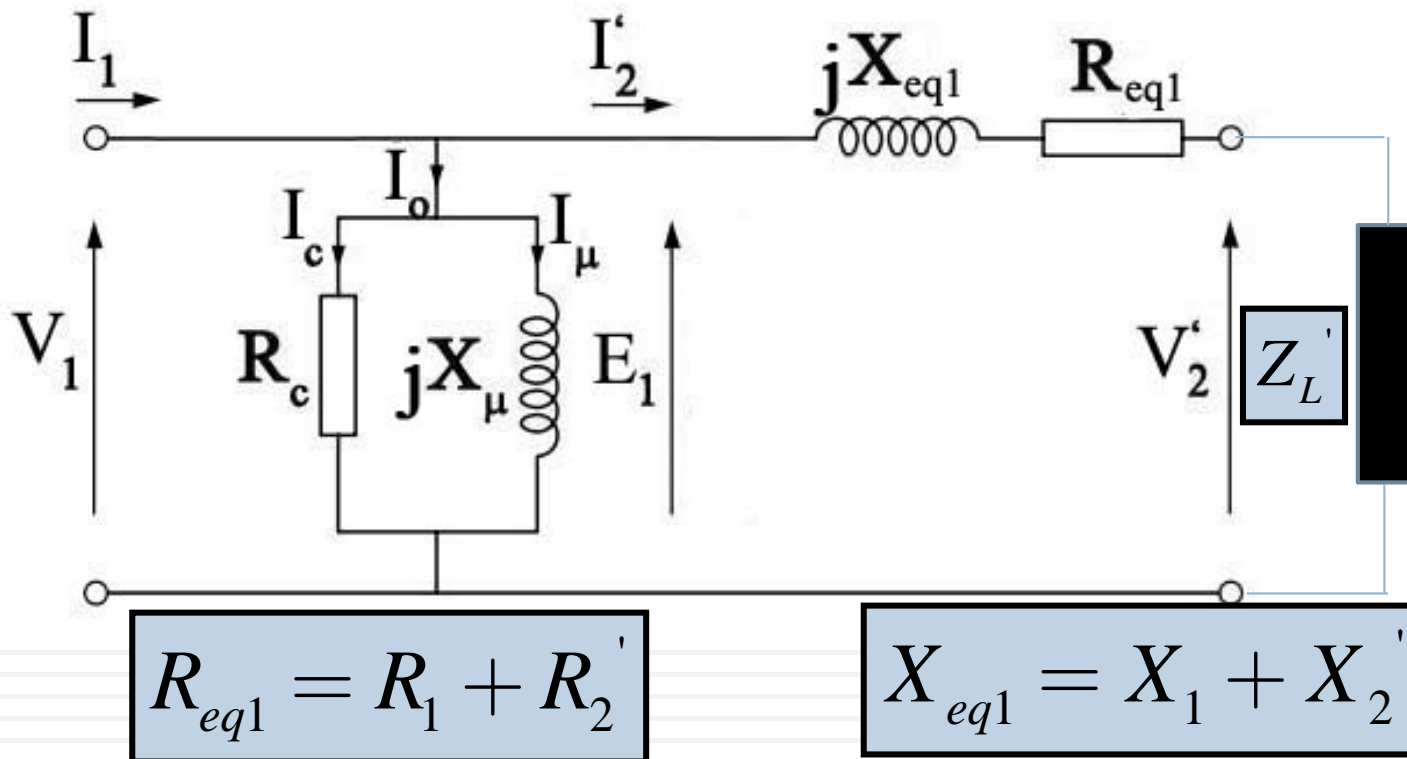
$$V_1 \cong V_2' + I_2'[(R_1 + jX_1) + (R_2' + jX_2')]$$




Equivalent resistance referred to the primary

Equivalent leakage reactance referred to the primary

Approximate Eq. Ct. referred to Primary

Transformer: Equivalent Circuit

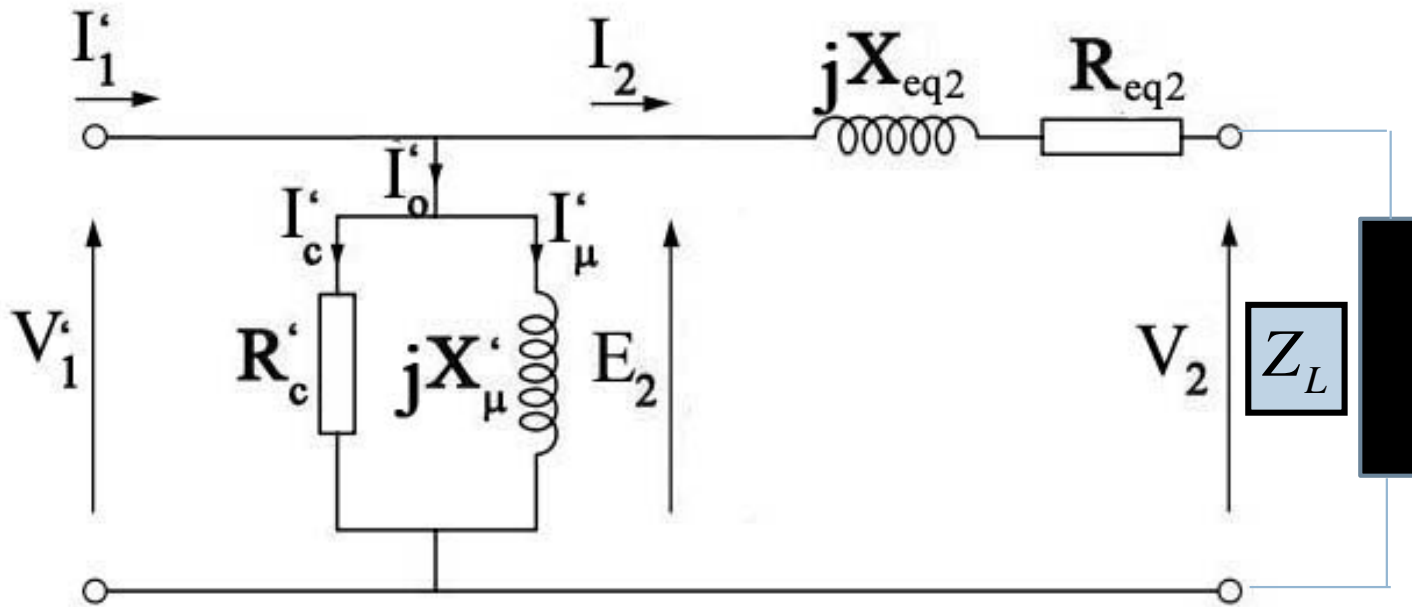

$$R_{eq2} = R_1' + R_2$$


Equivalent resistance referred to the secondary

$$X_{eq2} = X_1' + X_2$$

Equivalent leakage reactance referred to the secondary


Approximate Eq. Ct. referred to Secondary

Transformer: Equivalent Circuit

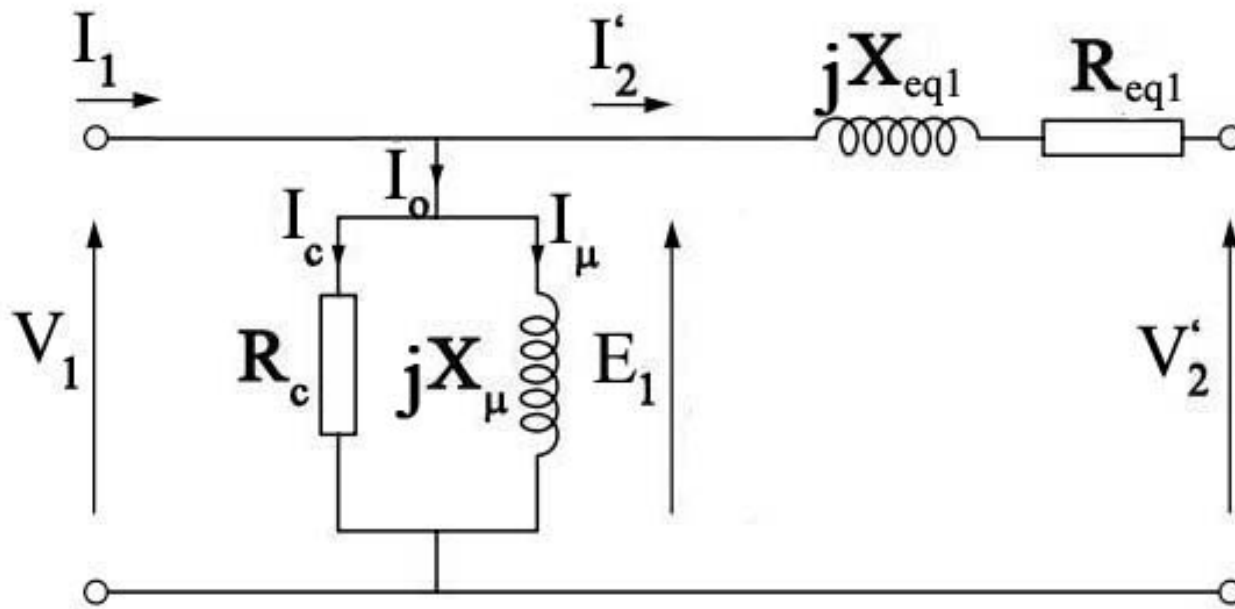


Eq. Ct. for small transformers (up to 100 kVA)

Transformer: Equivalent Circuit

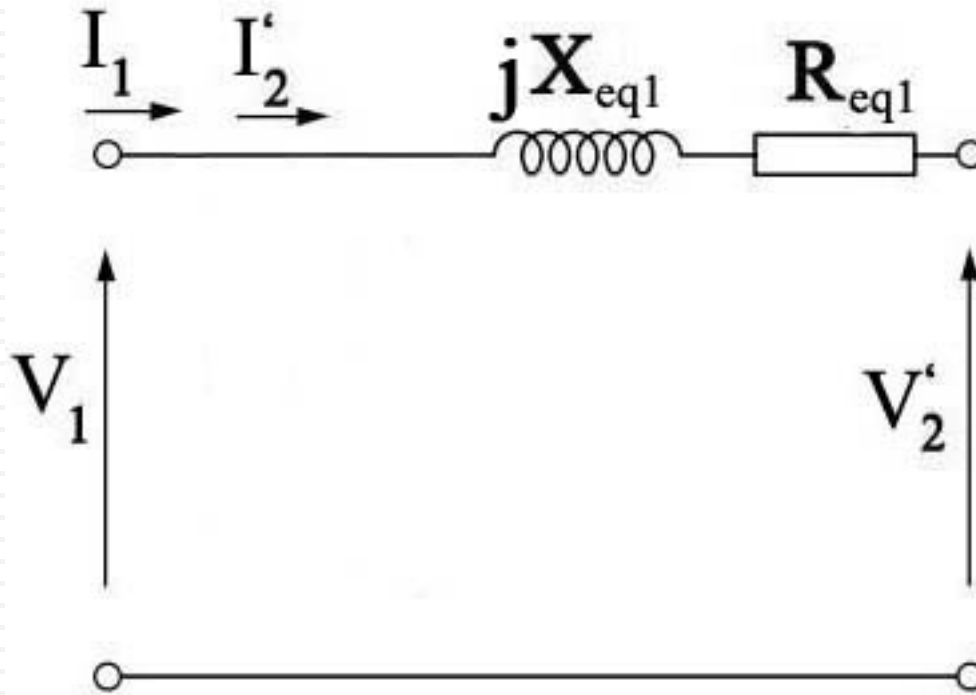

Eq. Ct. for transformers (100-500 kVA)

Transformer: Equivalent Circuit

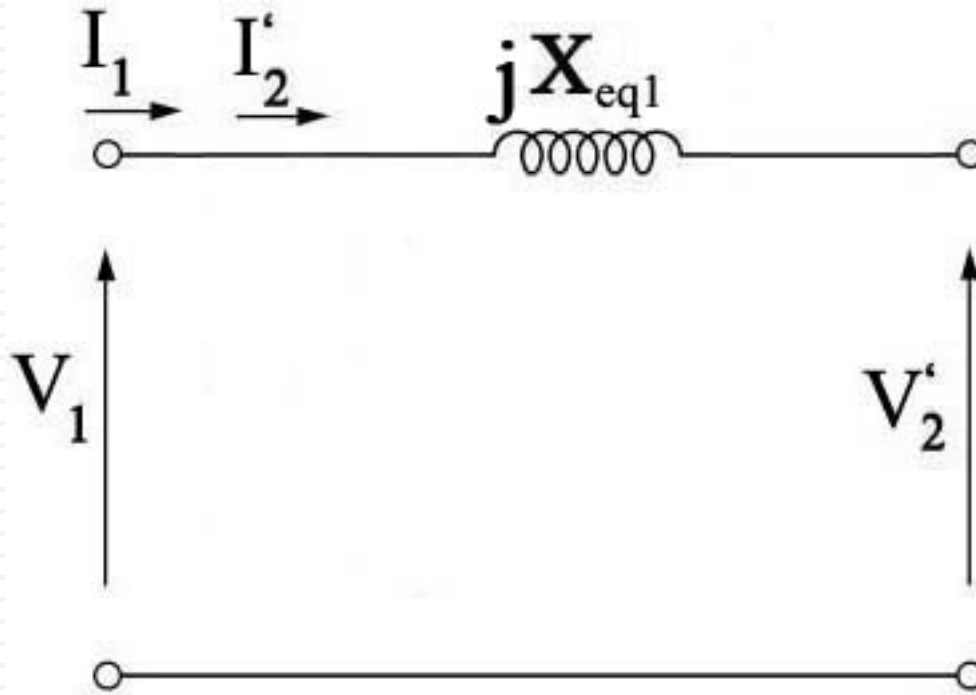

Eq. Ct. for large transformers (larger than 500 kVA)

Transformer: Equivalent Circuit

TABLE 10A ACTUAL TRANSFORMER VALUES

S_n	kVA	1	10	100	1000	400000
E_{np}	V	2400	2400	12470	69000	13800
E_{ns}	V	460	347	600	6900	424000
I_{np}	A	0.417	4.17	8.02	14.5	29000
I_{ns}	A	2.17	28.8	167	145	943
R_1	Ω	58.0	5.16	11.6	27.2	0.0003
R_2	Ω	1.9	0.095	0.024	0.25	0.354
X_{r1}	Ω	32	4.3	39	151	0.028
X_{r2}	Ω	1.16	0.09	0.09	1.5	27
X_m	Ω	200000	29000	150000	505000	460
R_m	Ω	400000	51000	220000	432000	317
I_o	A	0.0134	0.0952	0.101	0.210	52.9