

Induction Machines: 1-phase Induction Motors

1

- Principle of Operation
- Equivalent Circuit
- Power and Torque
- Starting Methods and Types
- Testing

Induction Machines: 1-phase Induction Motors



- Video

Induction Machines: 1-phase Induction Motors

3



Magnetic Field Production & Distribution

$$\oint_c \underline{H} \cdot \underline{dl} = I_{en}$$

$$\oint_c \underline{H} \cdot \underline{dl} = Ni$$

$$H \times g + H \times g \simeq Ni$$

$$H_g g = \frac{Ni}{2} = M$$


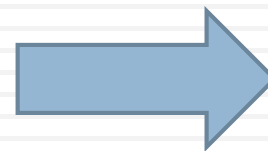
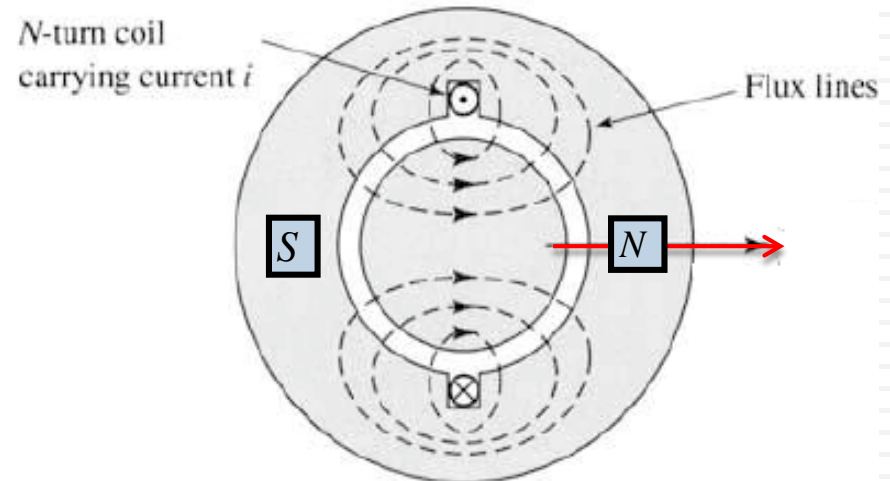


$$M = \frac{Ni}{2p}$$


Induction Machines: 1-phase Induction Motors

4

Magnetic Field Production & Distribution

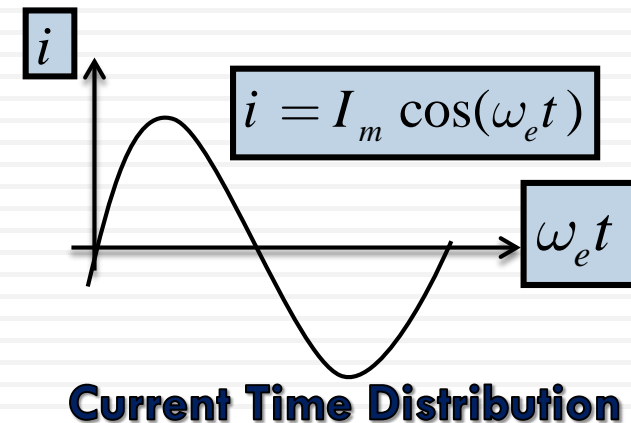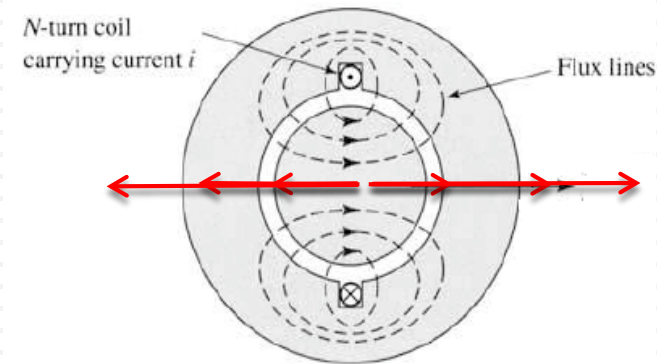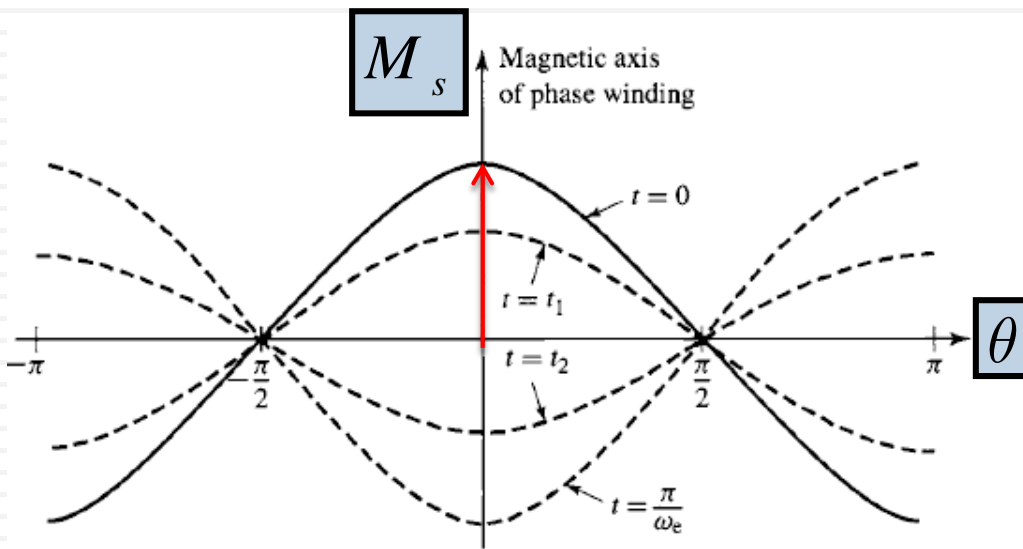

MMF Space Distribution

AC Current  Pulsating Field

Current Time Distribution

Induction Machines: 1-phase Induction Motors

5


Rotor Reaction

At standstill, the rotor field will always be shifted by 180° from the stator field at all instances.

$$T = k B_s B_r \sin \gamma$$

$$T = k B_s B_r \sin 180^\circ$$

$$T = \text{zero}$$

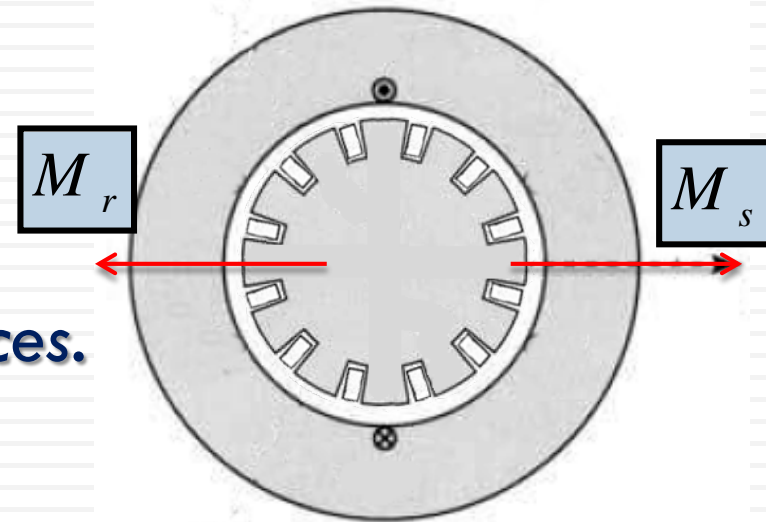

Induction Machines: 1-phase Induction Motors

6


Double Rotating Field Theory

$$I = I_m \cos(\omega_e t)$$

$$M = kNI \cos \theta$$

$$M = kNI_m \cos(\omega_e t) \cos p\theta$$
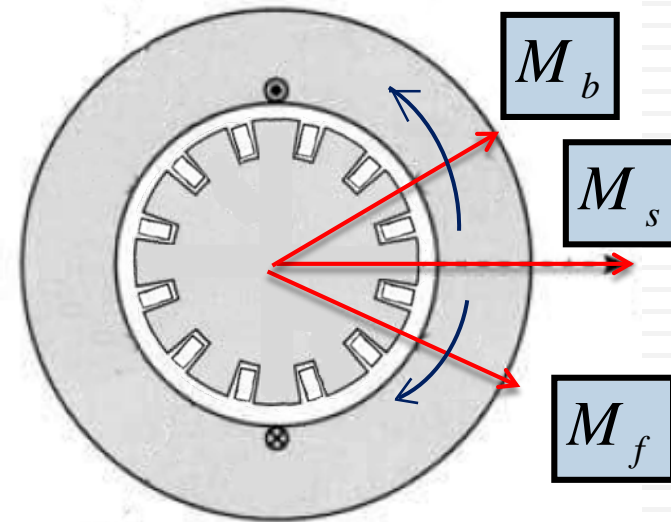
$$M = kN \frac{I_m}{2} [\cos(\omega_e t - p\theta) + \cos(\omega_e t + p\theta)]$$



$$M_f = kN \frac{I_m}{2} \cos(\omega_e t - p\theta)$$

Speed of
Rotation

$$n_s = \frac{60f}{p}$$

Forward
Field

$$M_b = kN \frac{I_m}{2} \cos(\omega_e t + p\theta)$$

Speed of
Rotation

$$-n_s = -\frac{60f}{p}$$


Backward
Field

Induction Machines: 1-phase Induction Motors

7


Double Rotating Field Theory

**Forward
Field**

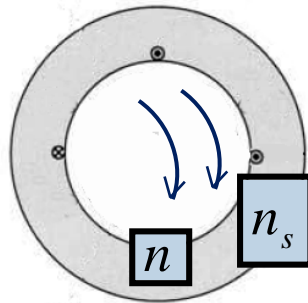


$$s_1 = \frac{n_s - n}{n_s} = s$$


**Backward
Field**

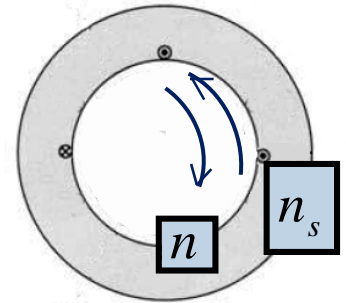

$$s_2 = \frac{n_s + n}{n_s} = 2 - s$$

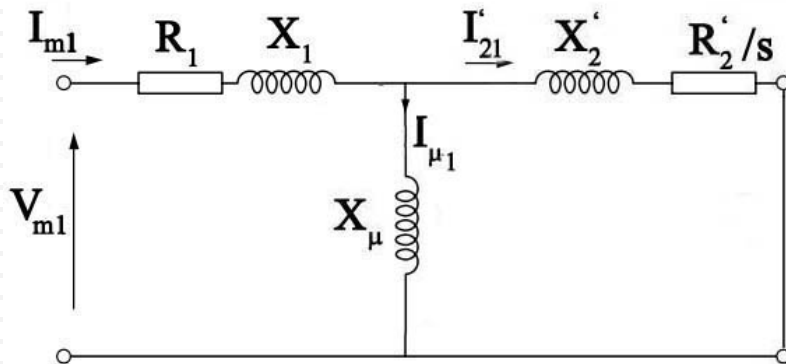

Forward

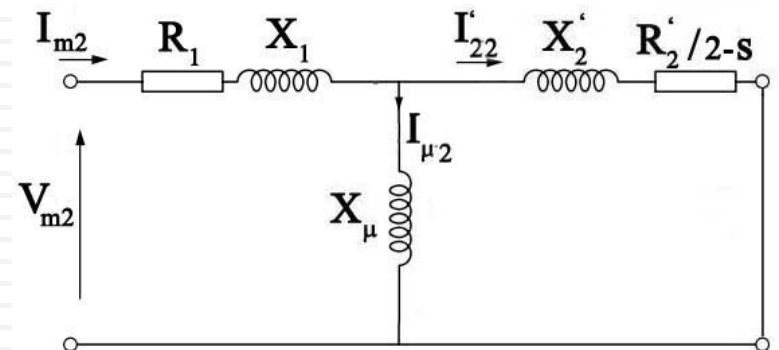


Backward


Induction Machines: 1-phase Induction Motors

8

Double Rotating Field Theory

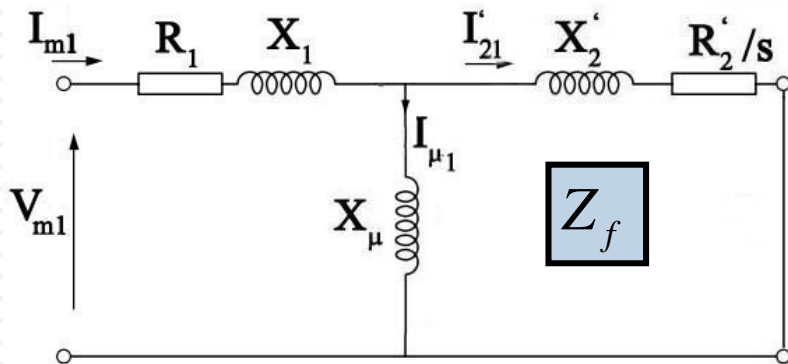

Forward

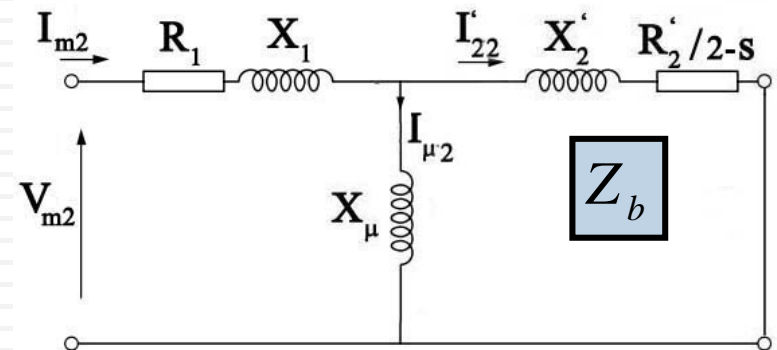

Backward

$$\begin{bmatrix} V_{m1} \\ V_{m2} \end{bmatrix} = \frac{1}{2} \begin{bmatrix} 1 & j \\ 1 & -j \end{bmatrix} \begin{bmatrix} V_m \\ V_c \end{bmatrix}$$

$$V_{m1} = V_{m2} = \frac{1}{2} V_m$$

At $s = 1$

$$Z_f = Z_b = Z$$

$$I_{m1} = I_{m2}$$

$$P_{g1} = P_{g2}$$


$$T_1 = T_2$$

$$T_{net} = T_1 - T_2 = \text{zero}$$

Induction Machines: 1-phase Induction Motors

9



Torque-Speed Characteristics

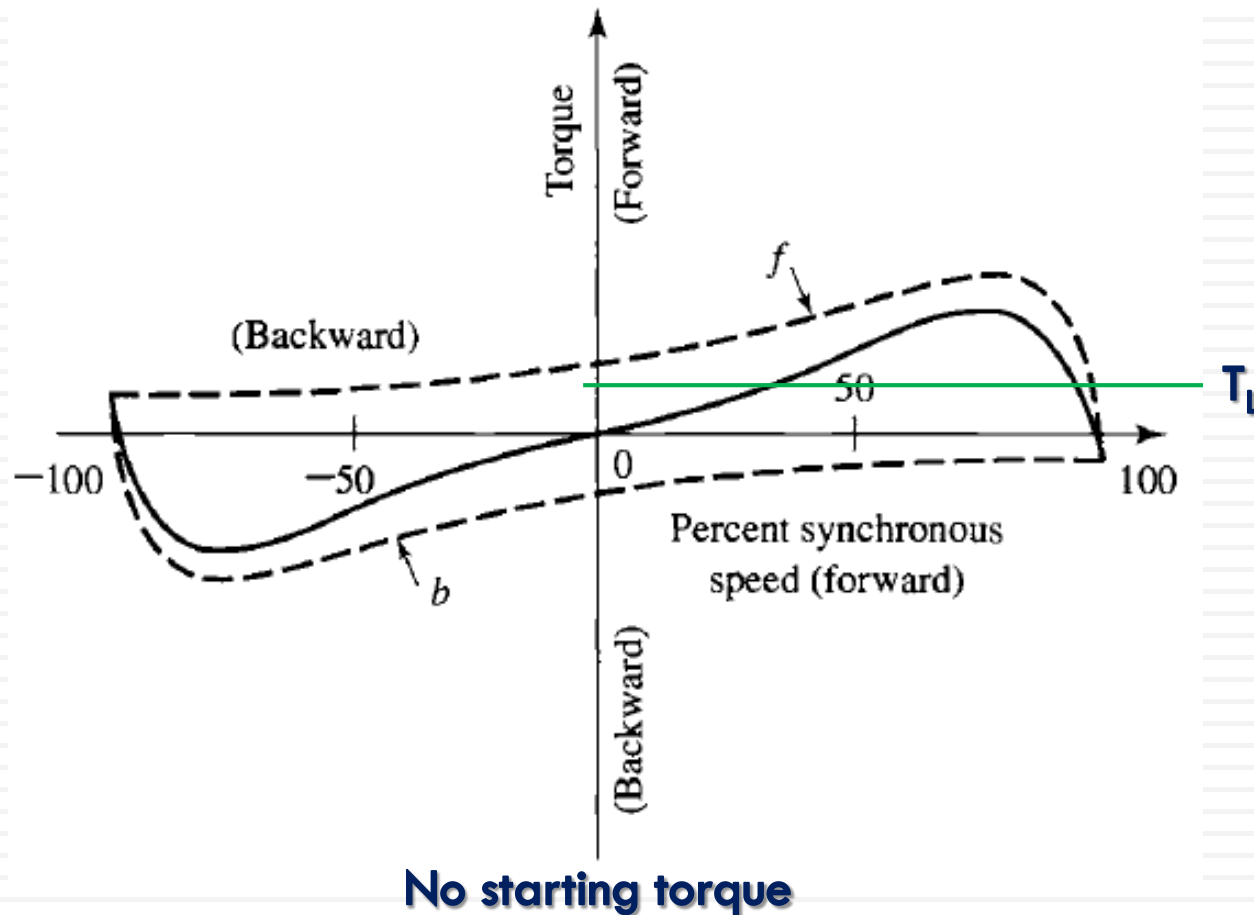

Induction Machines: 1-phase Induction Motors

10

Motor Starting

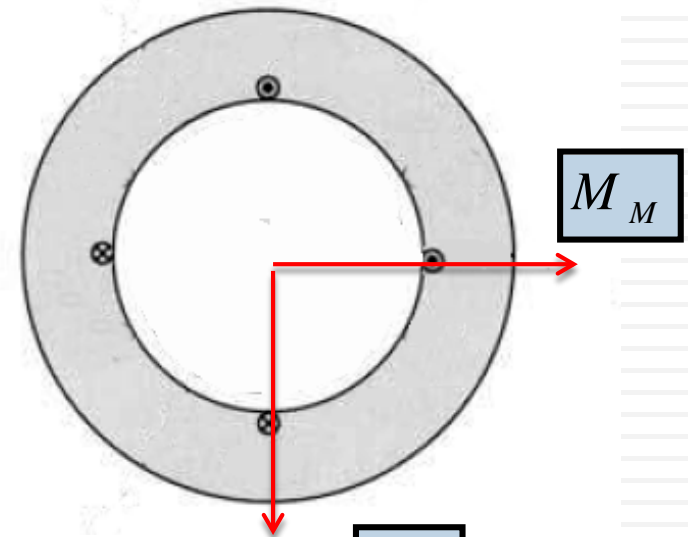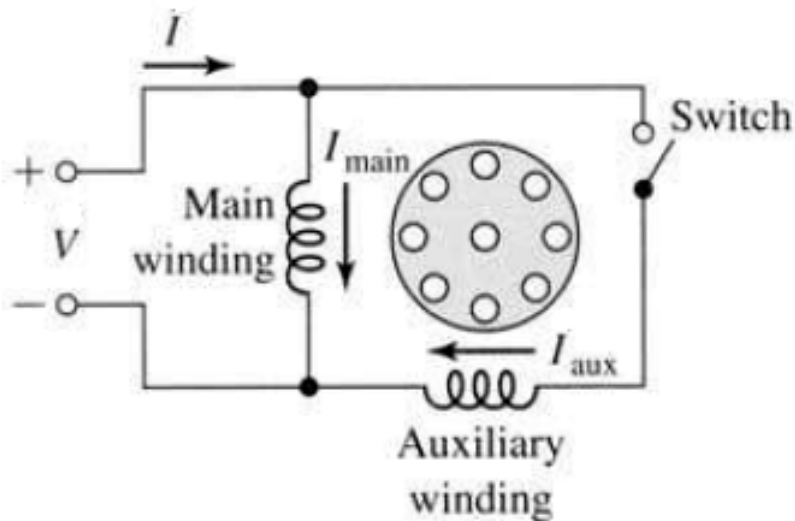

$$N_M > N_A$$


$$X_M > X_A$$

$$A_{cM} > A_{cA}$$

$$R_M < R_A$$

$$\frac{R_A}{X_A} > \frac{R_M}{X_M}$$

$$T_{st} \propto I_M I_A \sin \alpha$$

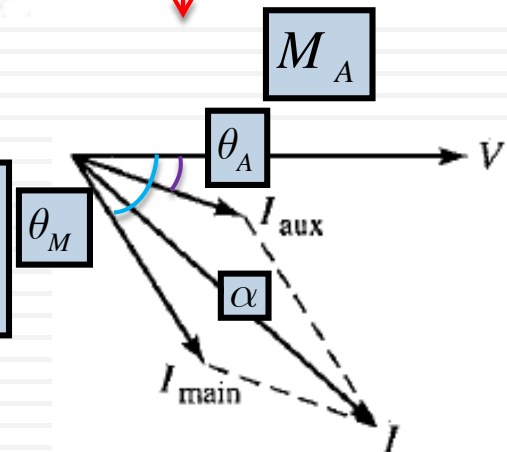

Induction Machines: 1-phase Induction Motors

11

Motor Starting

$$I_M = I_{Mm} \cos(\omega_e t)$$


$$M_M = kN_M I_M \cos \theta$$

$$M_M = kN_M I_{Mm} \cos(\omega_e t) \cos p\theta$$

$$I_A = I_{Am} \cos(\omega_e t + \alpha)$$

$$M_A = kN_A I_A \cos(\theta + 90^\circ)$$
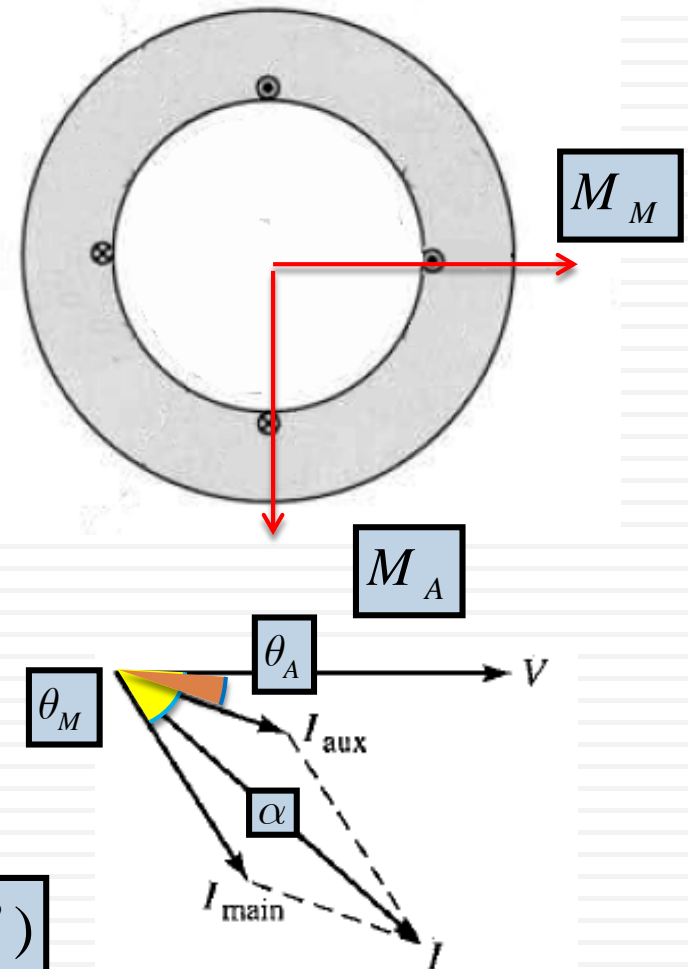
$$M_A = kN_A I_{Am} \cos(\omega_e t + \alpha) \cos(p\theta + 90^\circ)$$



Induction Machines: 1-phase Induction Motors

12

Motor Starting

$$M_t = kN_M I_{Mm} \cos(\omega_e t) \cos p\theta - kN_A I_{Am} \cos(\omega_e t + \alpha) \sin p\theta]$$

$$M_t = k[N_M I_{Mm} \cos(\omega_e t) \cos p\theta - N_A I_{Am} \sin p\theta [\cos(\omega_e t) \cos(\alpha) - \sin(\omega_e t) \sin(\alpha)]]$$

$$M_t = \frac{kN_M I_{Mm}}{2} [\cos(\omega_e t - p\theta) + \cos(\omega_e t + p\theta)] - \frac{kN_A I_{Am}}{2} \cos(\alpha) [\sin(\omega_e t + p\theta) - \sin(\omega_e t - p\theta)] \\ + \frac{kN_A I_{Am}}{2} \sin(\alpha) [\cos(\omega_e t - p\theta) - \cos(\omega_e t + p\theta)]$$

$$M_t = \frac{k}{2} [N_M I_{Mm} + N_A I_{Am} \sin(\alpha)] [\cos(\omega_e t - p\theta)] + \frac{kN_A I_{Am}}{2} \cos(\alpha) \sin(\omega_e t - p\theta) \\ + \frac{k}{2} [N_M I_{Mm} - N_A I_{Am} \sin(\alpha)] [\cos(\omega_e t + p\theta)] - \frac{kN_A I_{Am}}{2} \cos(\alpha) \sin(\omega_e t + p\theta)$$



Induction Machines: 1-phase Induction Motors

13

Equivalent Circuit at running conditions

$$\begin{bmatrix} I_{m1} \\ I_{m2} \end{bmatrix} = \frac{1}{2} \begin{bmatrix} 1 & j \\ 1 & -j \end{bmatrix} \begin{bmatrix} I_m \\ I/a \end{bmatrix}$$

$$I_{m1} = I_{m2} = \frac{1}{2} I_m$$

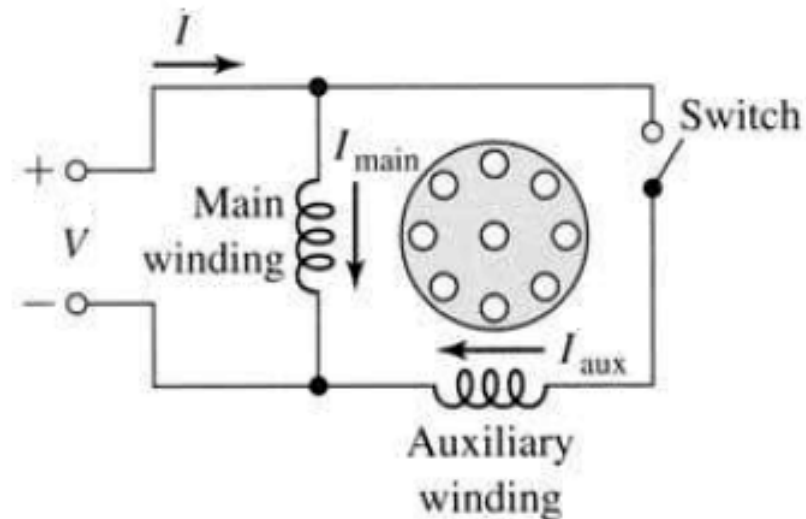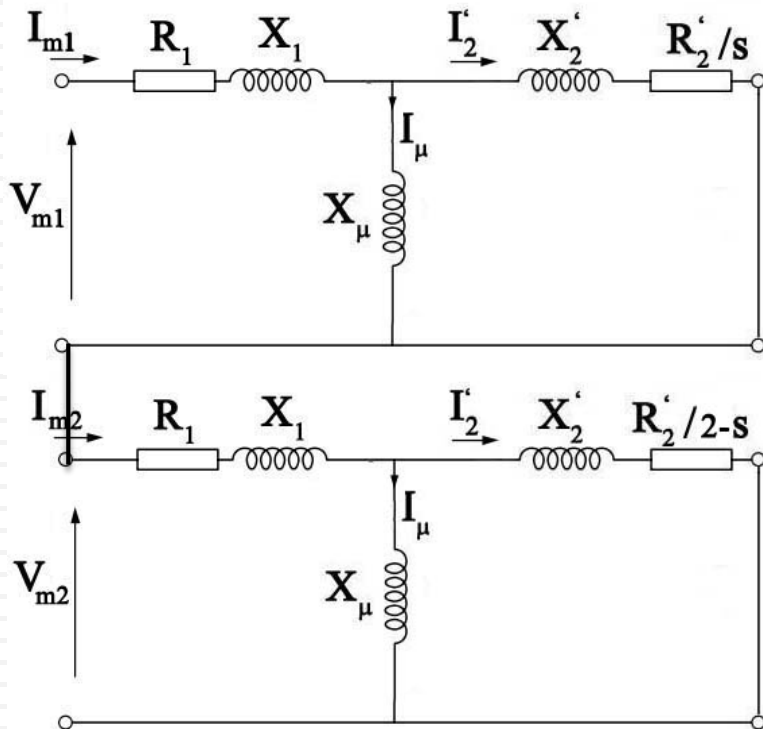



$$I_a = \text{zero}$$

$$V_{m1} = V_{m2} = \frac{1}{2} V_m$$

Induction Machines: 1-phase Induction Motors

14

Equivalent Circuit at running conditions

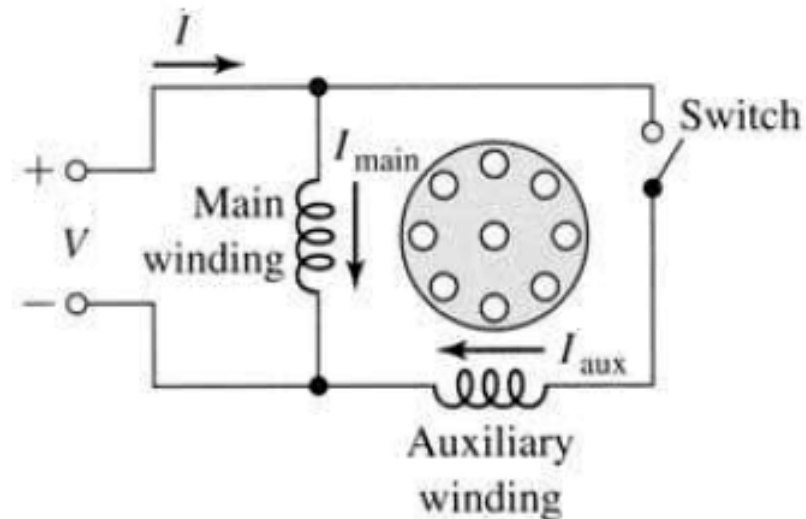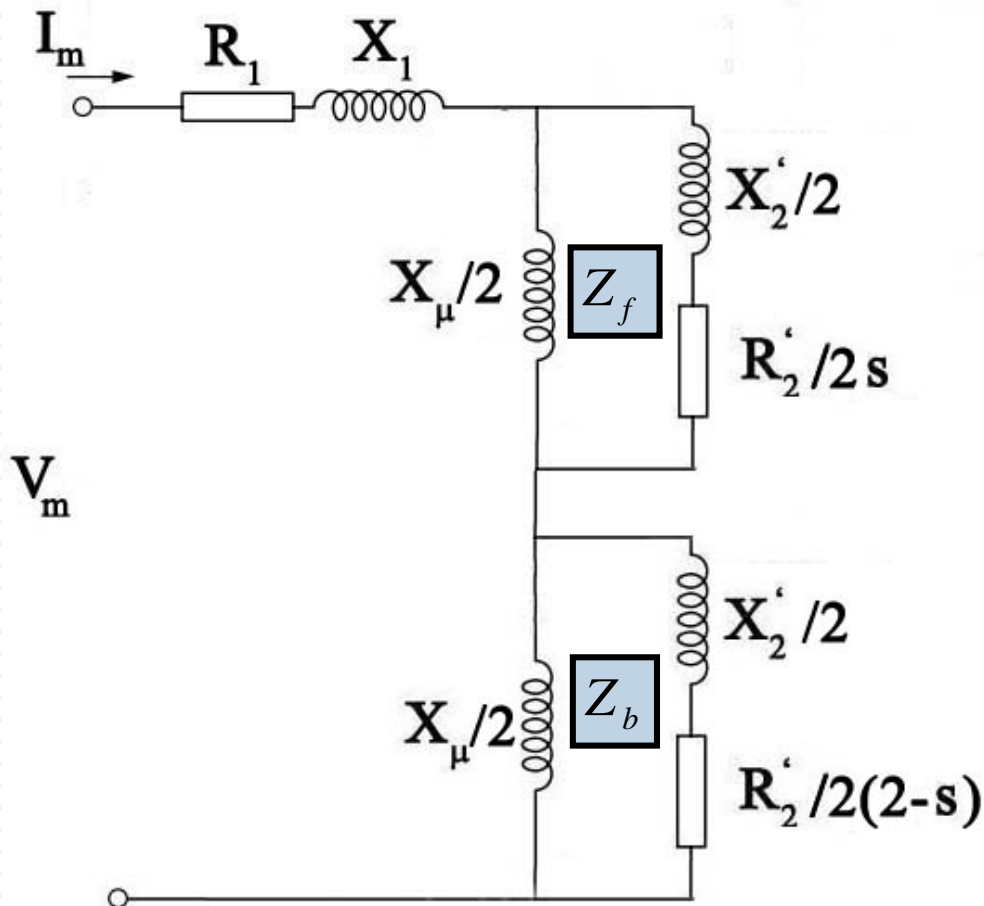


$$I_a = \text{zero}$$

$$I_m = \frac{V_m}{R_1 + jX_1 + Z_f + Z_b}$$

Induction Machines: 1-phase Induction Motors

15

Power Flow

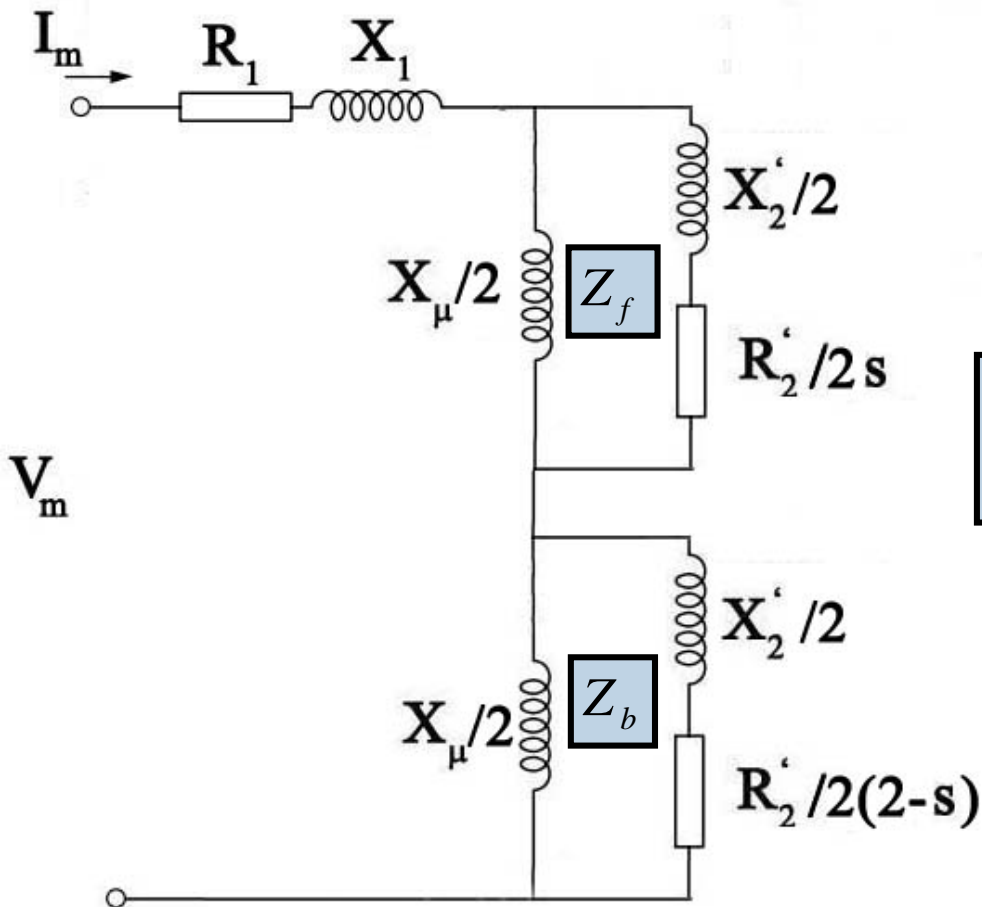

$$P_{in} = V_m I_m \cos \phi_m$$

$$P_{cu1} = I_m^2 R_1$$

$$P_{gf} = I_m^2 R_f$$

$$P_{gb} = I_m^2 R_b$$

$$P_{gf} : P_{cuf2} : P_{df} \\ 1 : s : (1-s)$$

$$P_{gb} : P_{cub2} : P_{db} \\ 1 : 2-s : (1-(2-s))$$

$$P_{cu2} = P_{cu2f} + P_{cu2b}$$

$$P_d = P_{df} + P_{db} = (1-s)(P_{gf} - P_{gb})$$

$$P_{out} = P_d - P_{mech}$$




$$T_{out} = \frac{P_{out}}{\omega}$$

Induction Machines: 1-phase Induction Motors

16

Motor Types

1. Split-phase (resistance-start) Motor

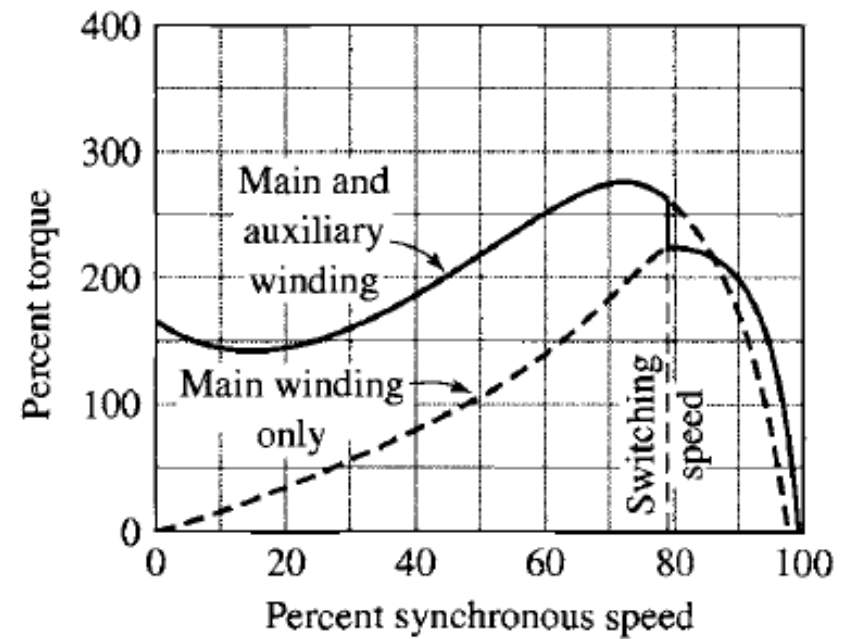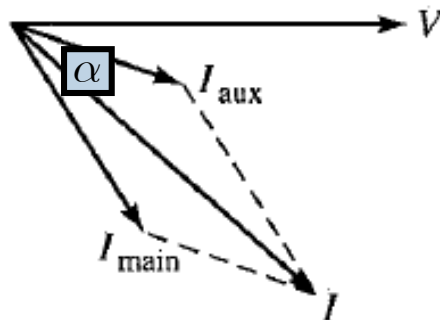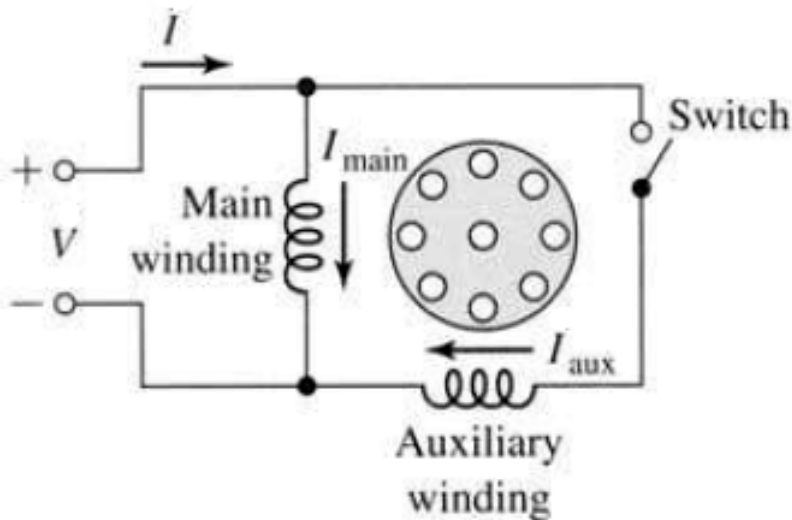


Induction Machines: 1-phase Induction Motors

17

Motor Types

1. Split-phase (resistance-start) Motor

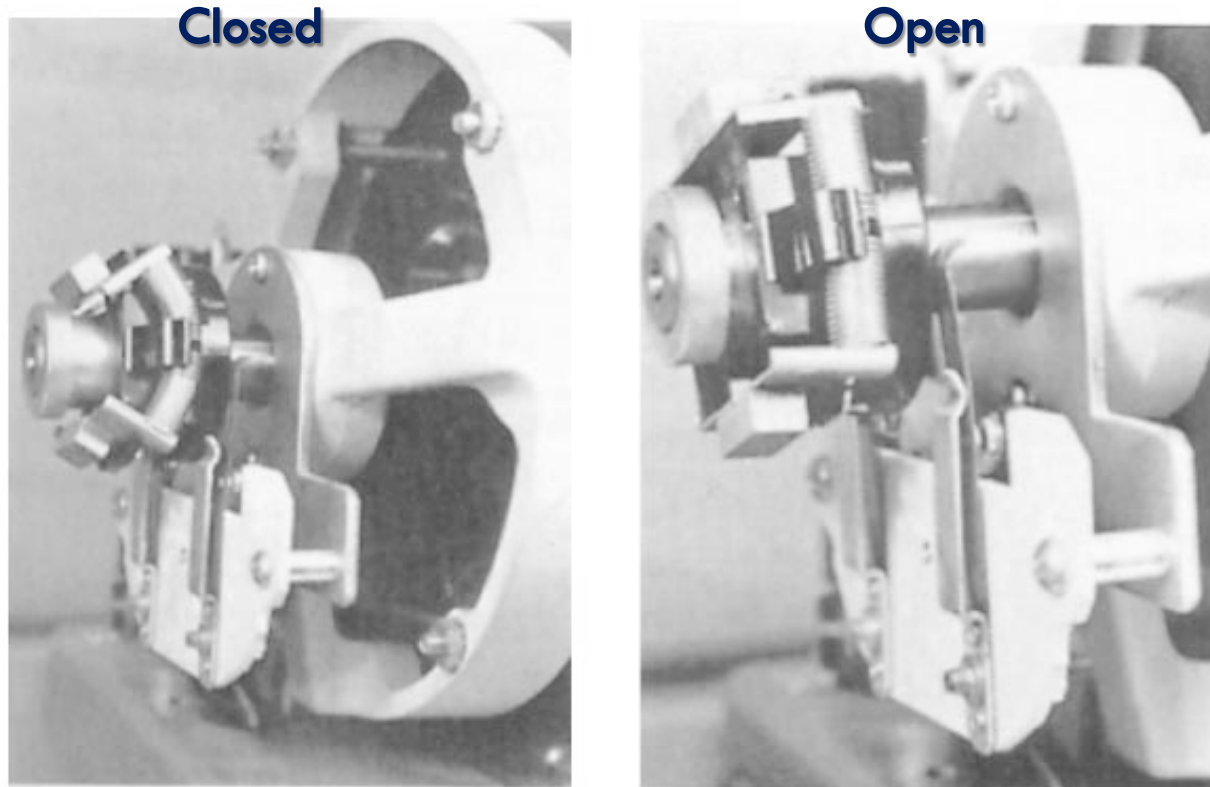




Centrifugal Switch

Induction Machines: 1-phase Induction Motors

18

Motor Types

2. Capacitor-Start Motor

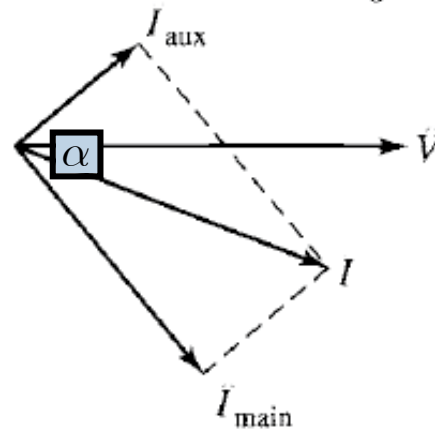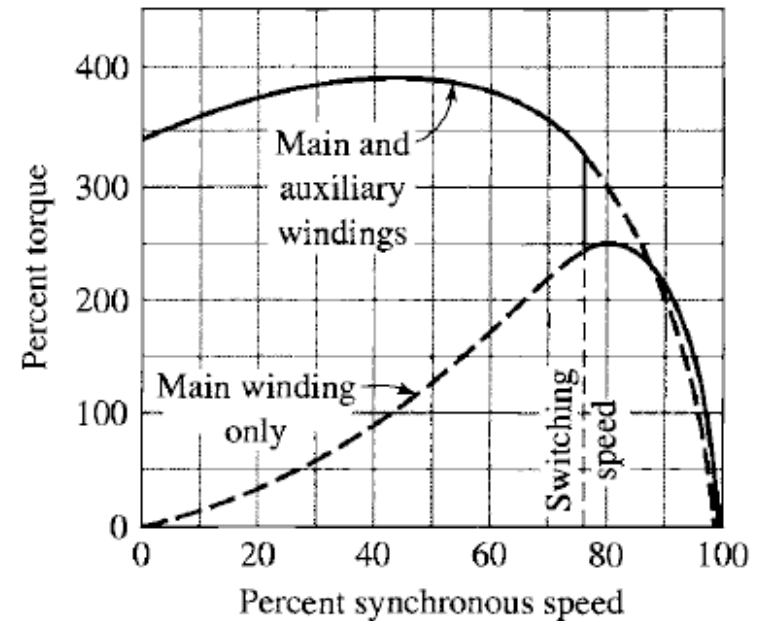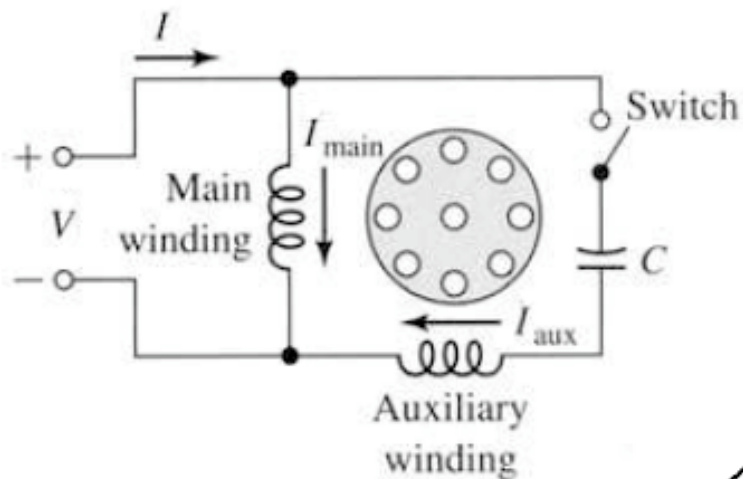


Induction Machines: 1-phase Induction Motors

19

Motor Types

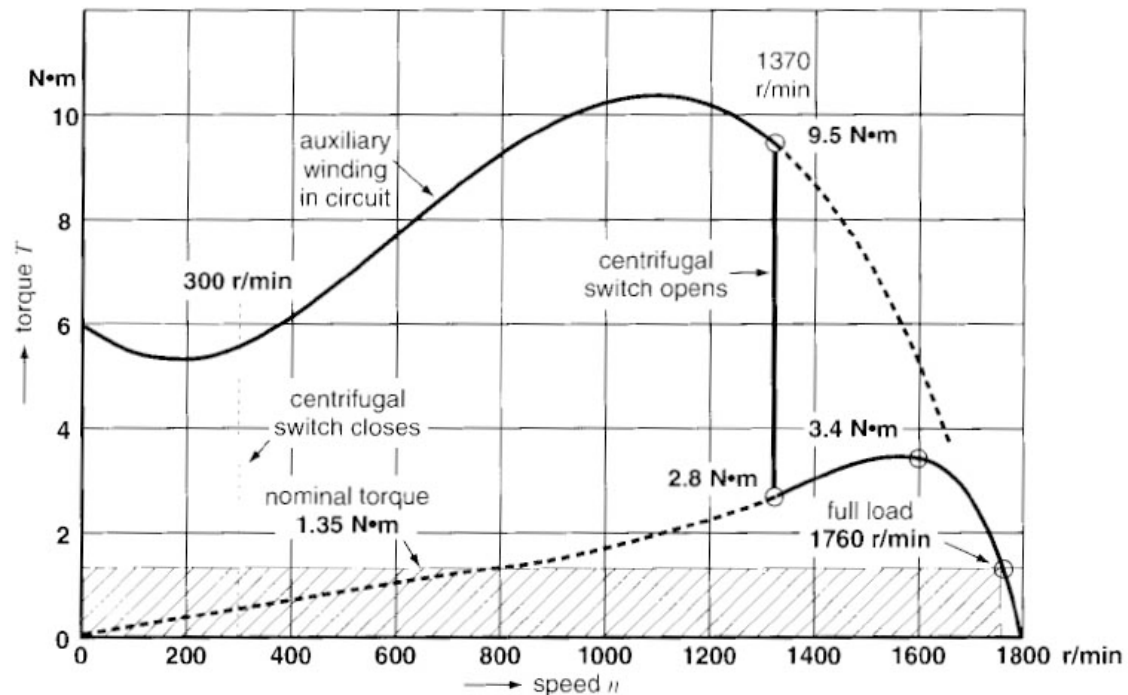2. Capacitor-Start Motor

250 W (1/3 hp) motor, 4-poles, 110 V, 60 Hz





Induction Machines: 1-phase Induction Motors

20

Motor Types

3. Capacitor-Run Motor

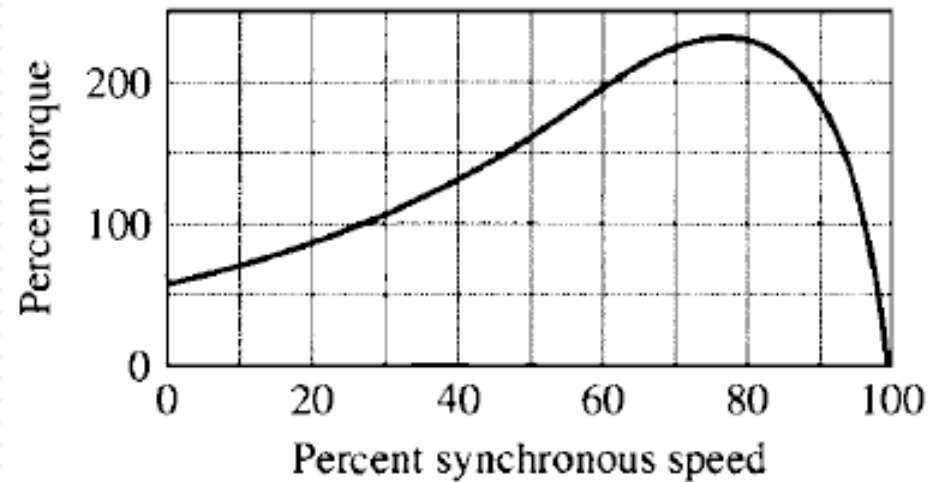
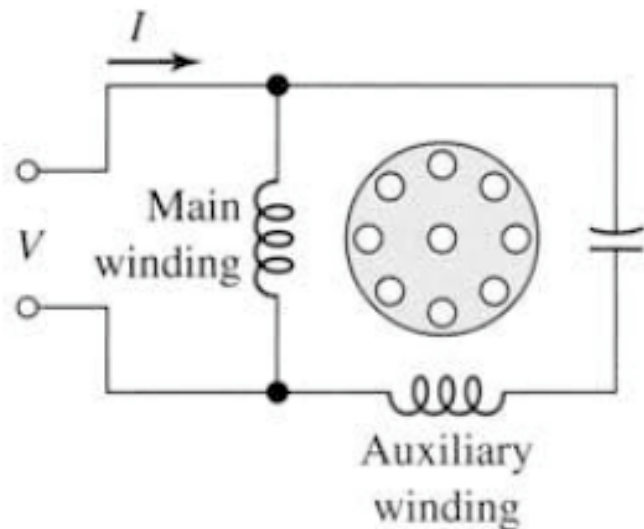


Induction Machines: 1-phase Induction Motors

21

Motor Types

4. Capacitor-Start, Capacitor-Run Motor

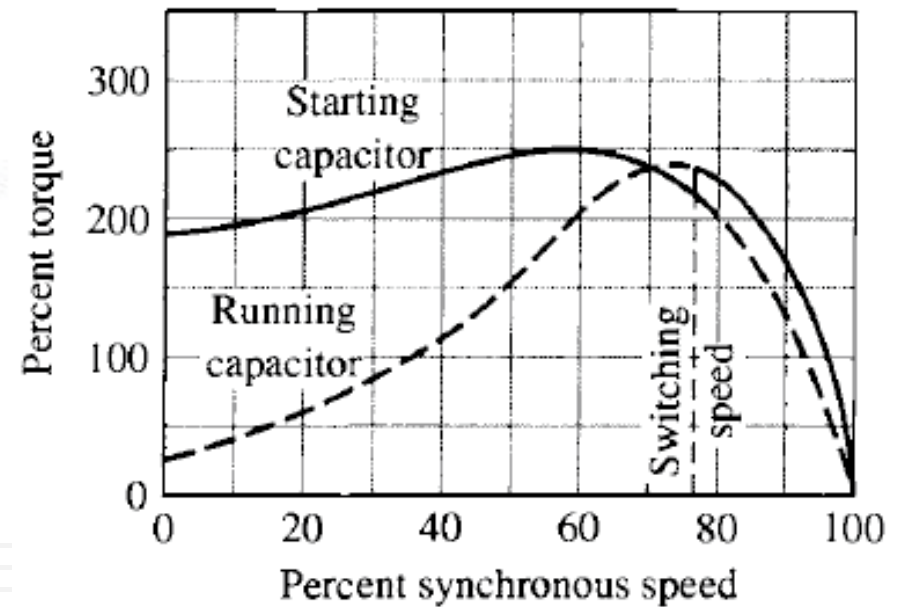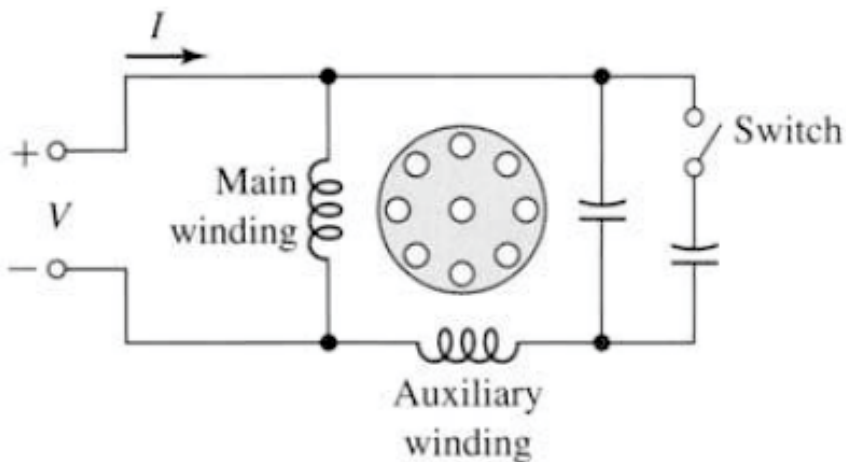


Induction Machines: 1-phase Induction Motors

22

Starting Winding Design

At starting ($n=0, s=1$)


Split-phase (resistance start)

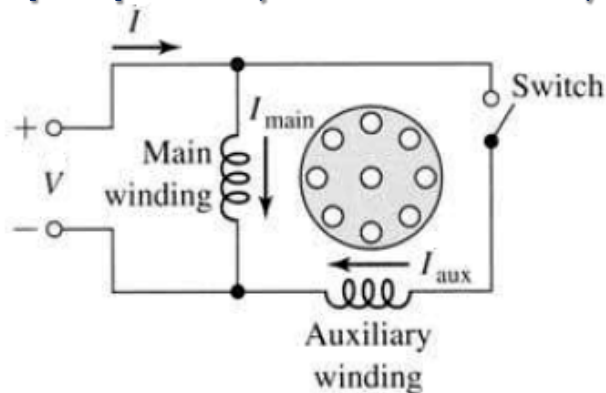

$$I_M = \frac{V}{Z_M}$$

$$I_A = \frac{V}{Z_A}$$

Capacitor-start

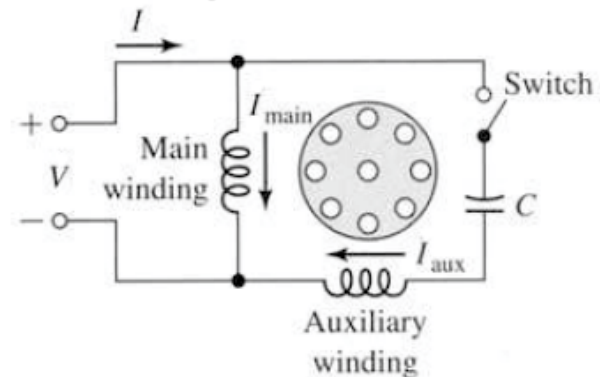

$$I_M = \frac{V}{Z_M}$$

$$I_A = \frac{V}{Z_A - jX_C}$$

$Z_M =$ standstill impedance of the main winding



$Z_A =$ standstill impedance of the auxiliary winding

Induction Machines: 1-phase Induction Motors



23

Starting Winding Design

Split-phase (resistance start)

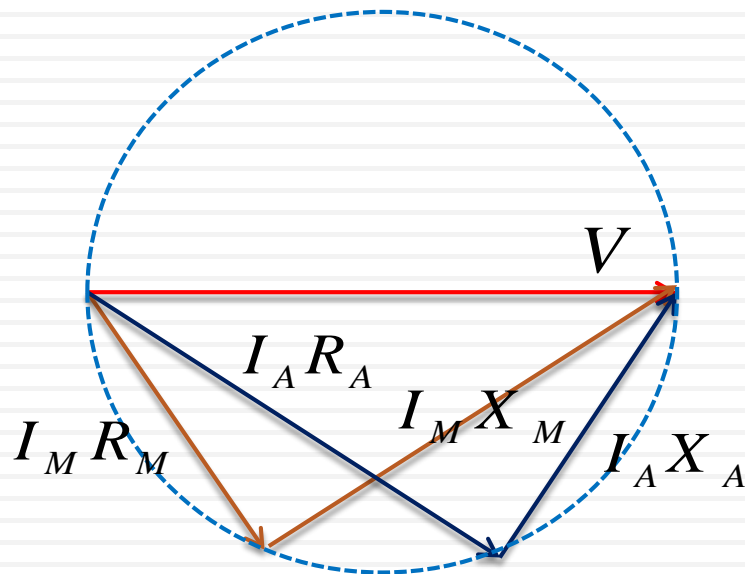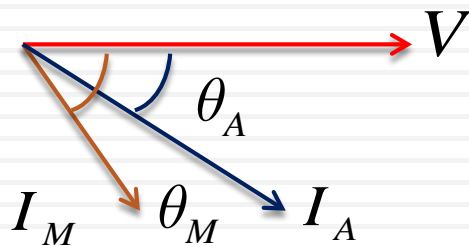

Capacitor-start

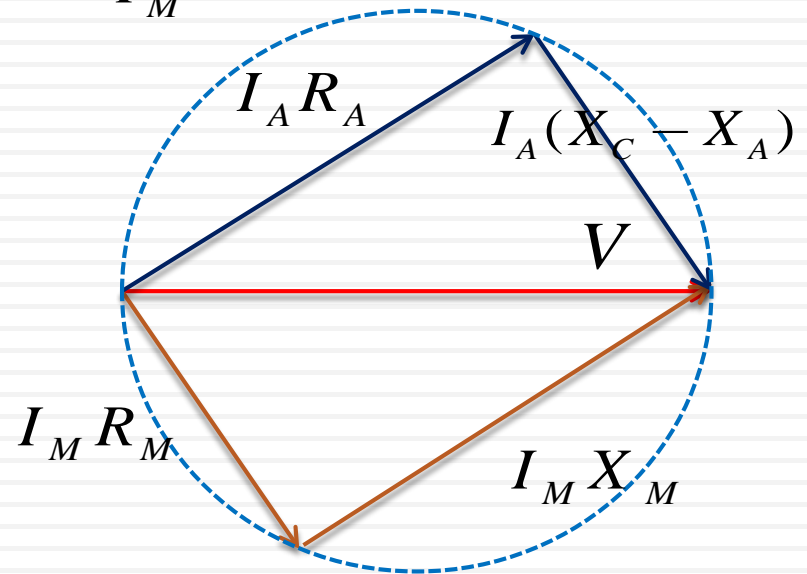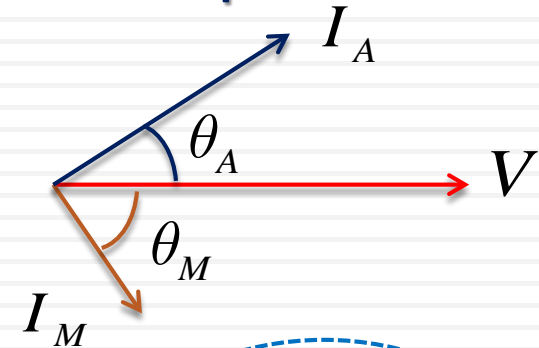

Induction Machines: 1-phase Induction Motors

24


Starting Winding Design

1. Design of Resistance-Start Motors

$$T_{st} \propto I_A \sin \alpha$$

For max. starting torque:
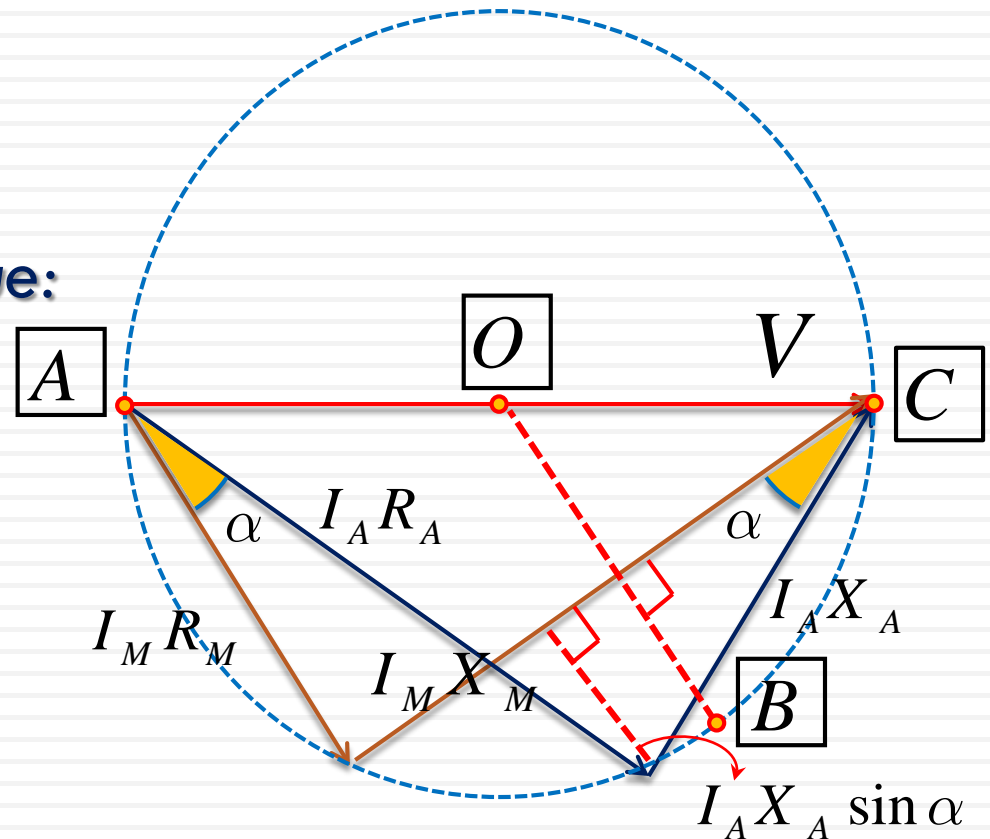
$$\frac{AB}{BC} = \frac{R_A + R_{Add}}{X_A}$$



Induction Machines: 1-phase Induction Motors

25


Starting Winding Design

2. Design of Capacitor-Start Motors

$$T_{st} \propto I_A \sin \alpha$$

For max. starting torque:
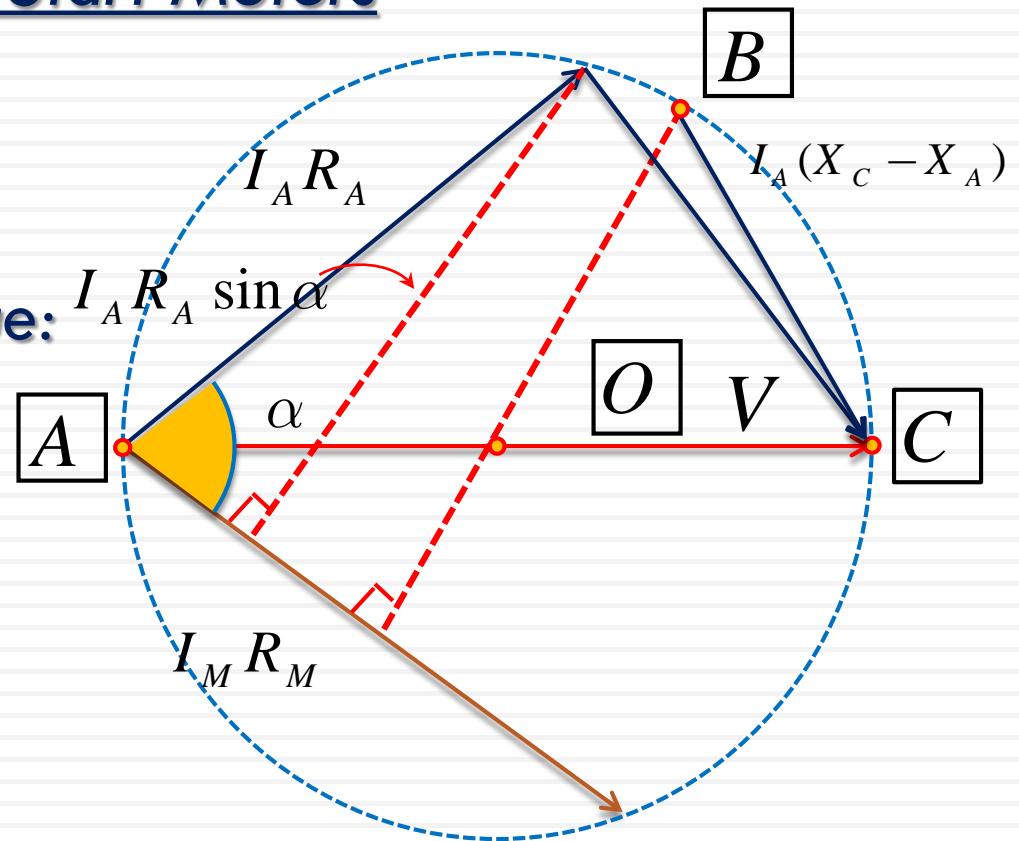
$$\frac{BC}{AB} = \frac{X_C - X_A}{R_A}$$



Induction Machines: 1-phase Induction Motors


26

Testing: 1. Locked Rotor (Standstill) Test

Voltage is adjusted such that stator current \leq full load current

Main winding only is connected

Reduced
Voltage

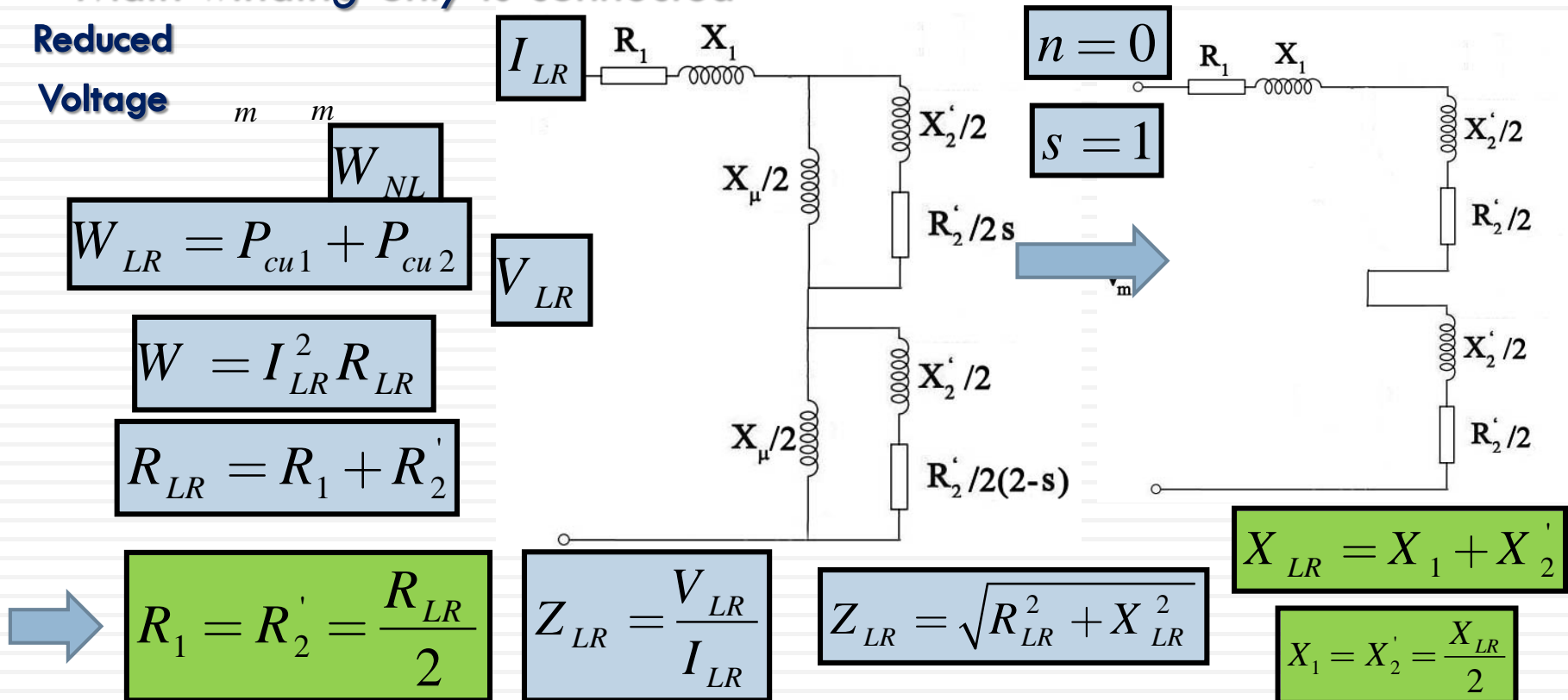


Induction Machines: 1-phase Induction Motors

27

Testing: 1. Locked Rotor (Standstill) Test

To get the standstill impedances of the main and auxiliary windings, this test is performed on each winding individually.

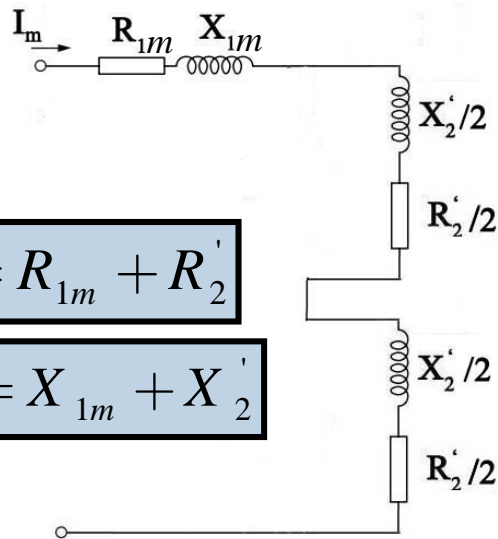Main Winding only connected to the supply




$$R_M = R_{1m} + R_2'$$

$$X_M = X_{1m} + X_2'$$

$$Z_M = R_M + jX_M$$

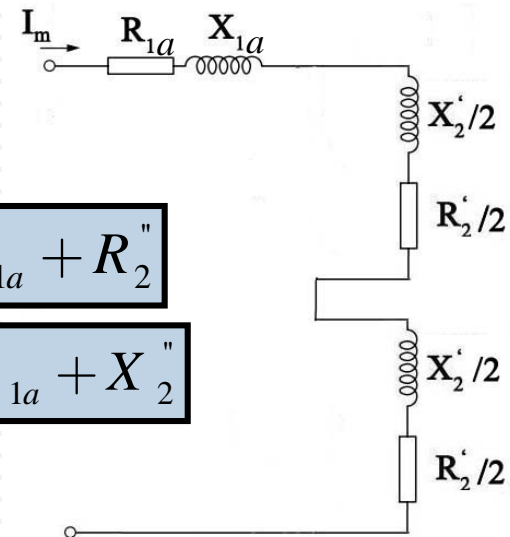Aux. Winding only connected to the supply



$$R_A = R_{1a} + R_2''$$

$$X_A = X_{1a} + X_2''$$

$$Z_A = R_A + jX_A$$

Induction Machines: 1-phase Induction Motors

28

Testing: 2. No-Load Test

$$W_{NL} = P_{mech} + P_{cu1}$$

$$W_{NL}$$

$$P_{cu1} = I_{NL}^2 \left(R_1 + \frac{R_2'}{4} \right)$$

V_{NL} **Rated Voltage**


$$P_{mech}$$

$$Z_{NL} = \frac{V_{NL}}{I_{NL}}$$

$$Z_{NL} = \sqrt{R_{NL}^2 + X_{NL}^2}$$

$$X_{NL} = X_1 + \frac{X_2'}{2} + \frac{X_\mu}{2}$$

$s \approx 0$

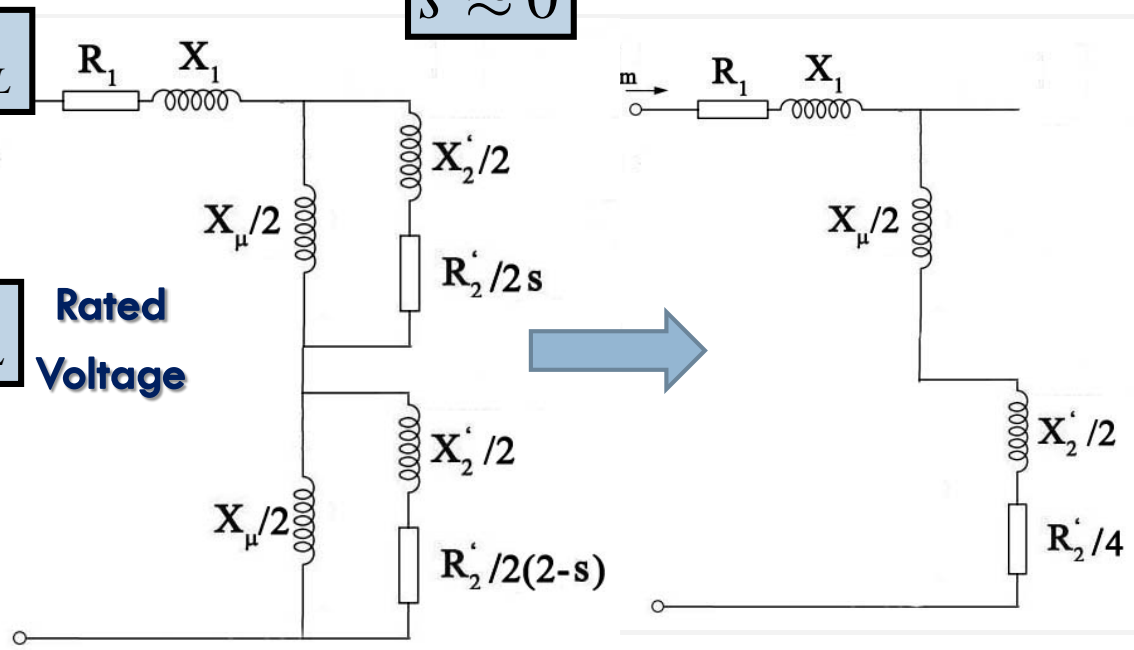

$$X_\mu = 2 \times \left(X_{NL} - X_1 - \frac{X_2'}{2} \right)$$