

# Induction Machines: 1-phase Induction Motors

1

- Construction
- Principle of Operation
- Equivalent Circuit
- Power and Torque
- Motor Types
- Starting Winding Design
- Testing

# Induction Machines: 1-phase Induction Motors

2




□ Video

# Induction Machines: 1-phase Induction Motors

3

## Motor Types
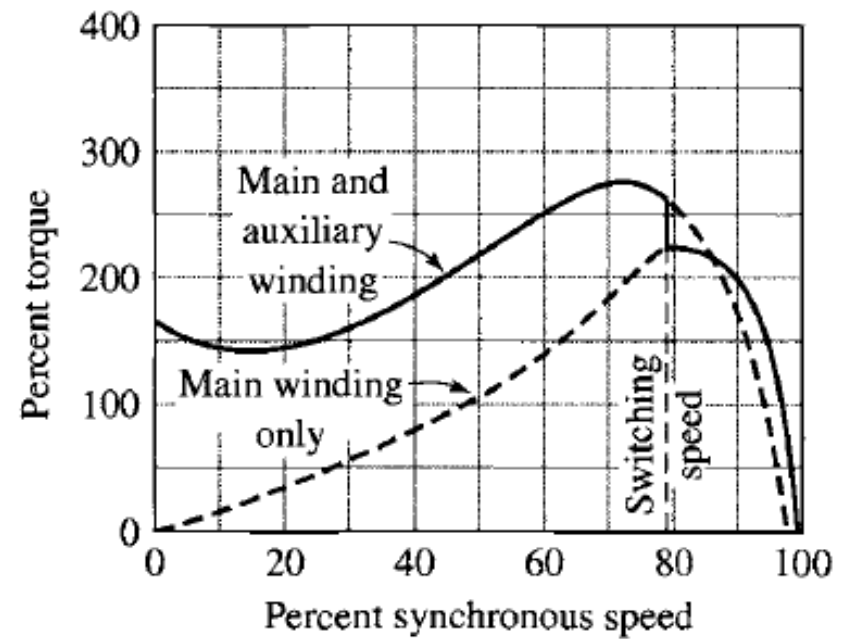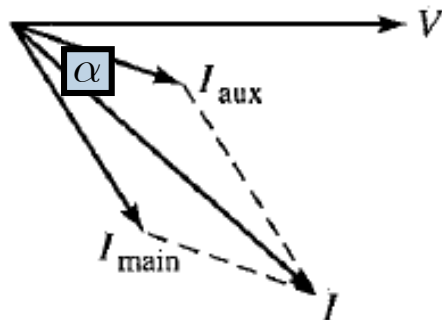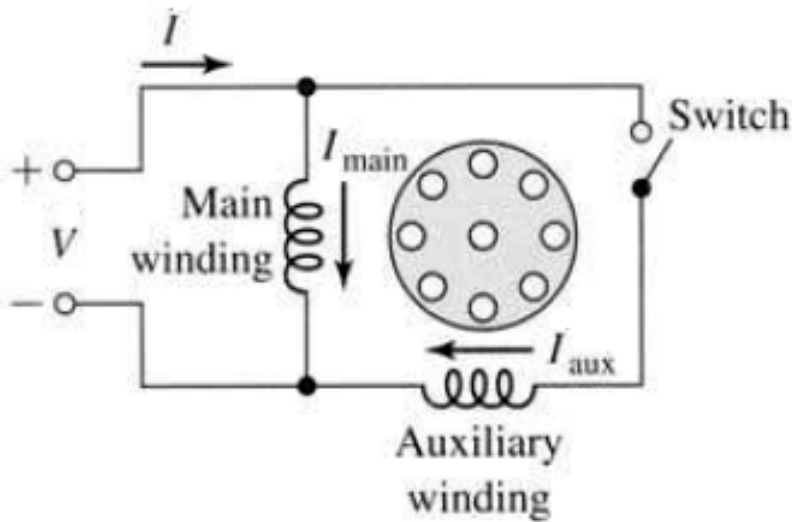
### 1. Split-phase (resistance-start) Motor




# Induction Machines: 1-phase Induction Motors

4

## Motor Types
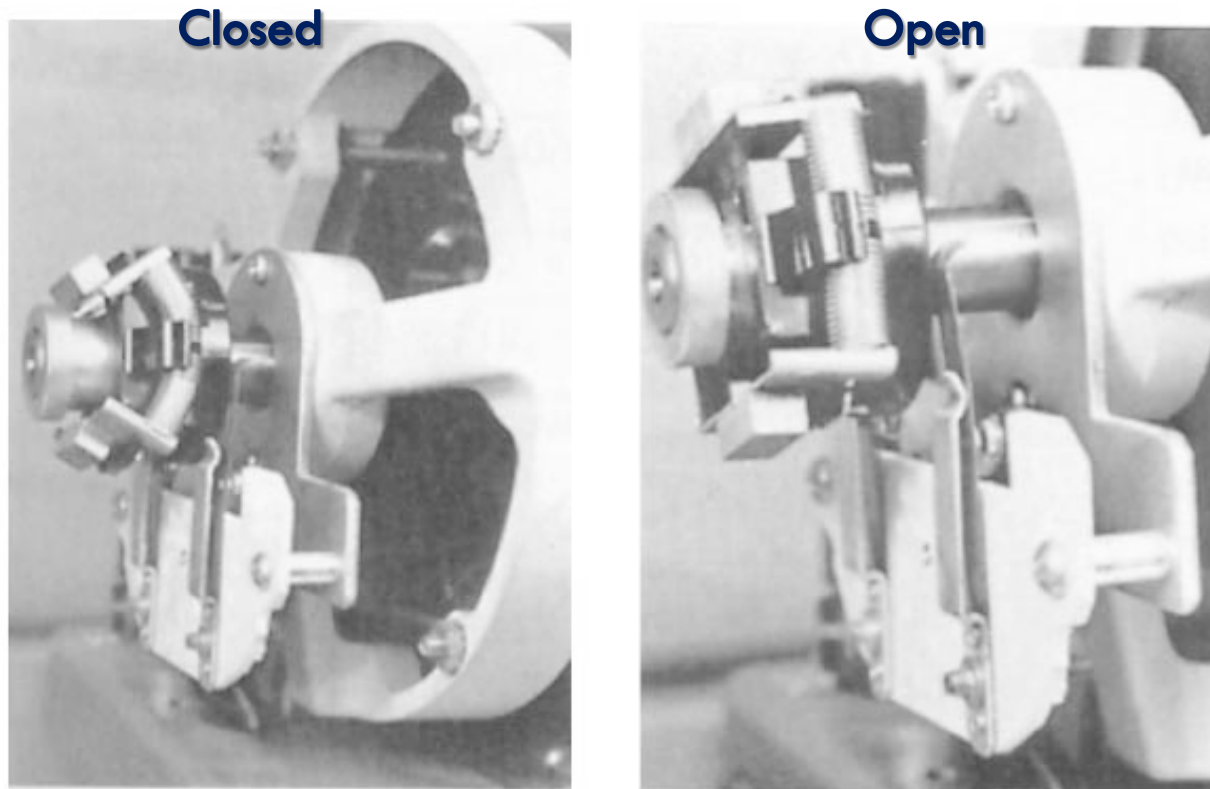
### 1. Split-phase (resistance-start) Motor






**Centrifugal Switch**

# Induction Machines: 1-phase Induction Motors

5

## Motor Types

### 2. Capacitor-Start Motor

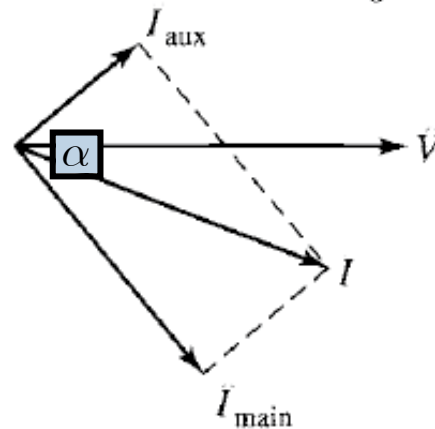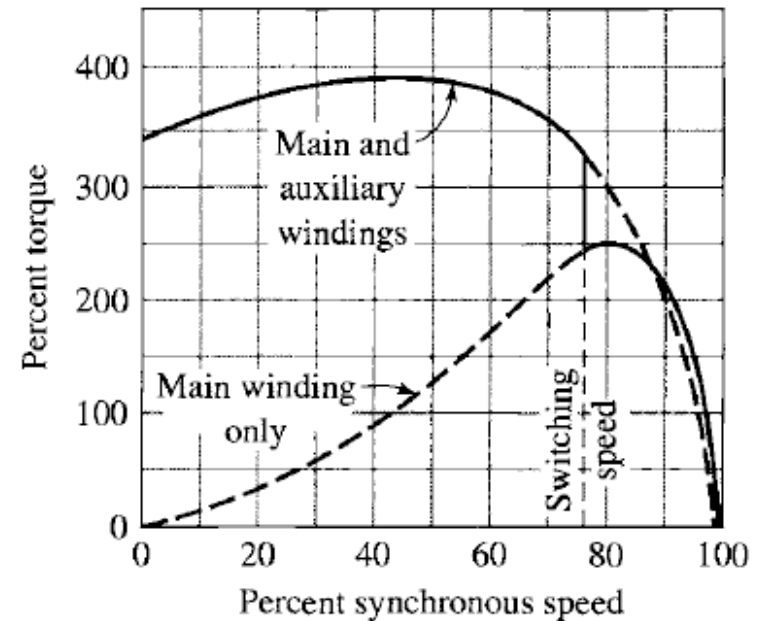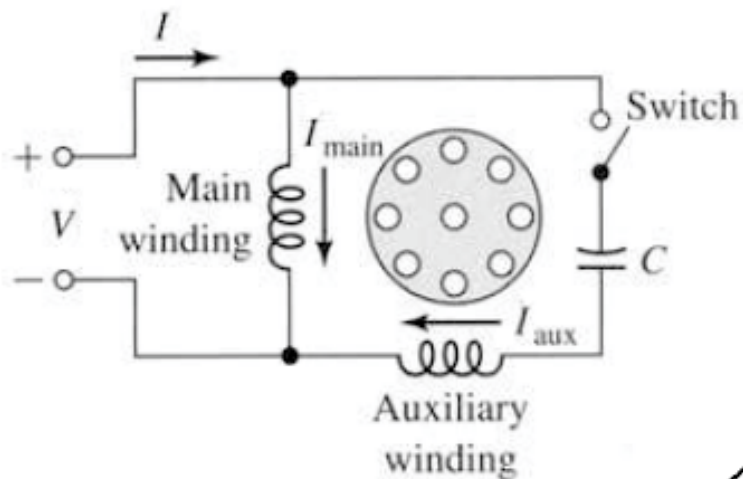


# Induction Machines: 1-phase Induction Motors

6

## Motor Types
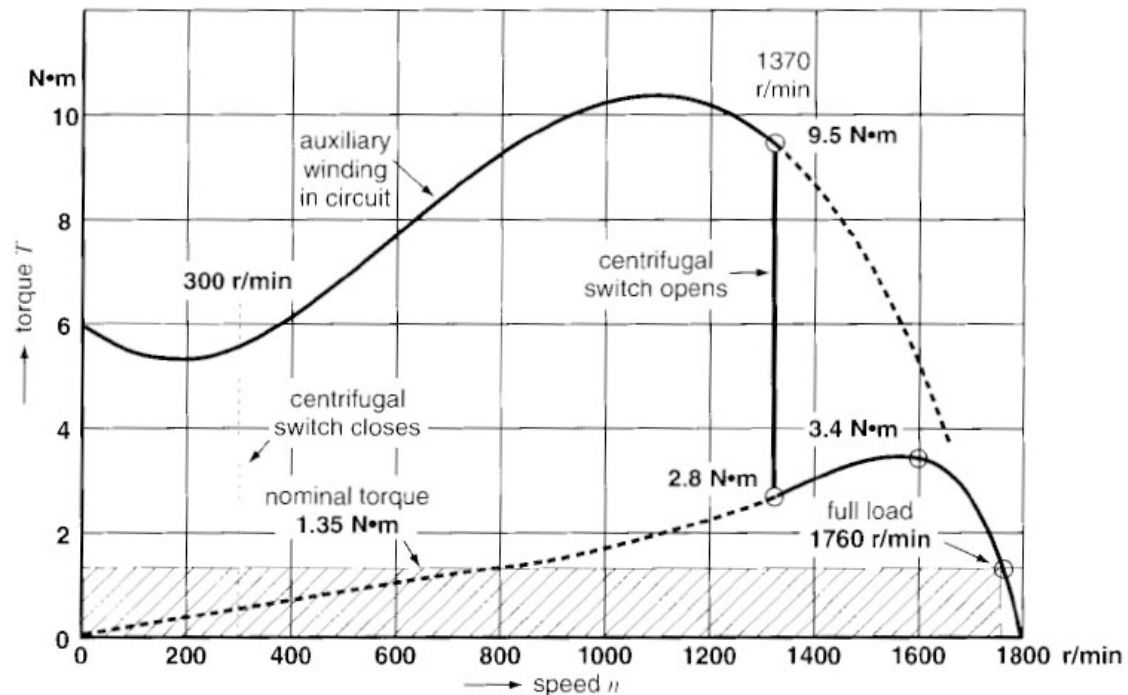
### 2. Capacitor-Start Motor

250 W (1/3 hp) motor, 4-poles, 110 V, 60 Hz





# Induction Machines: 1-phase Induction Motors

7

## Motor Types

### 3. Capacitor-Run Motor

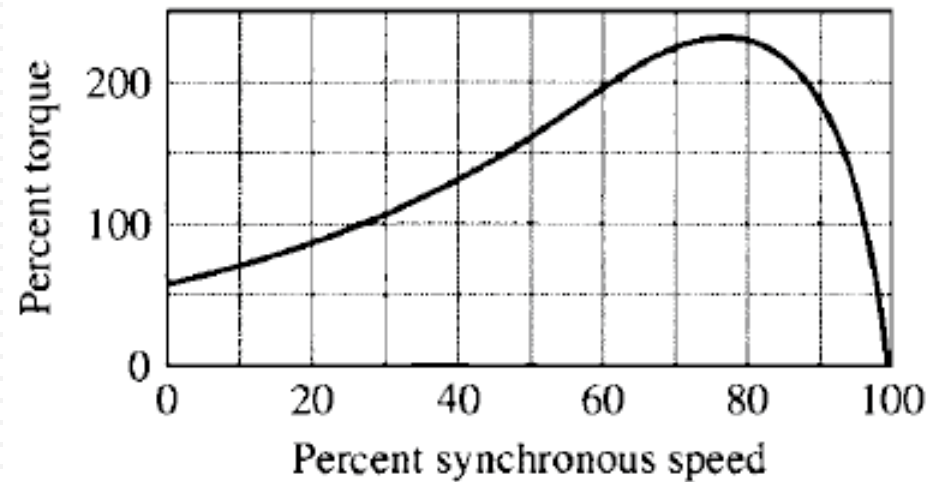
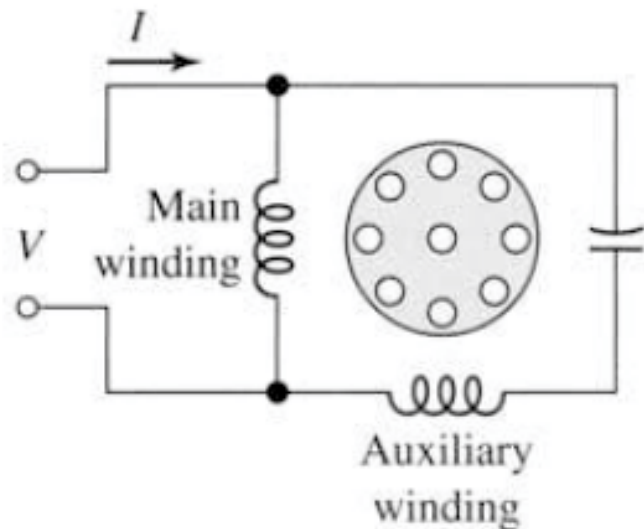


# Induction Machines: 1-phase Induction Motors

8

## Motor Types
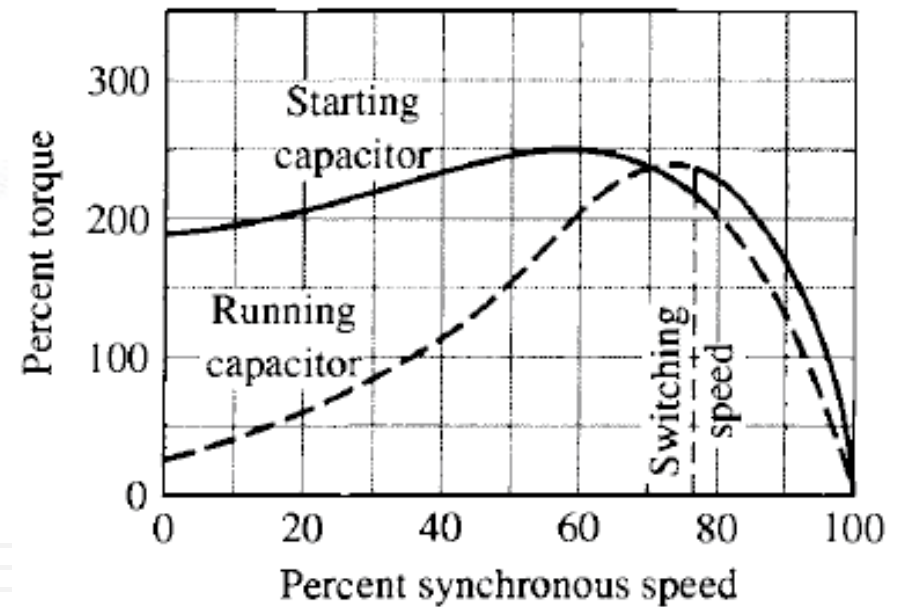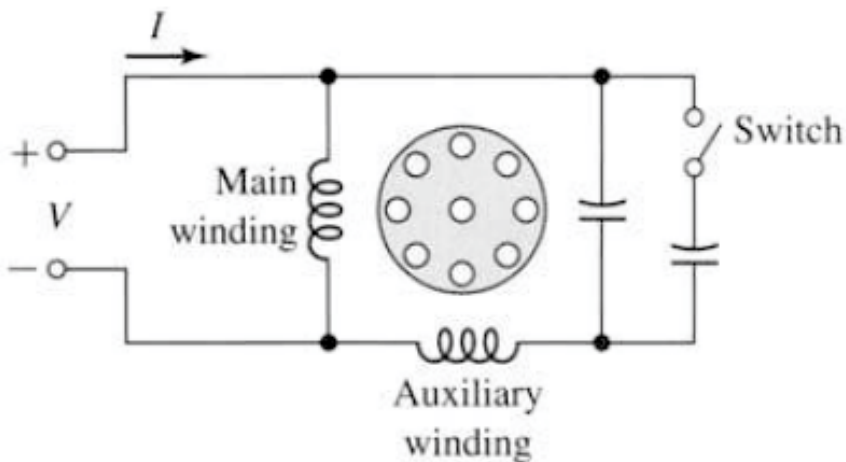
### 4. Capacitor-Start, Capacitor-Run Motor





# Induction Machines: 1-phase Induction Motors

9

## Motor Types

### 5. Shaded-pole Motor

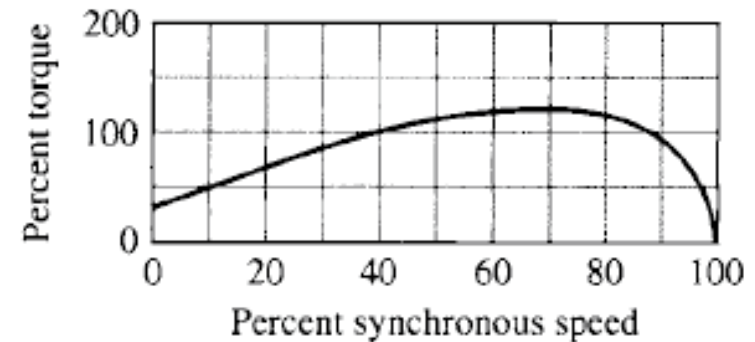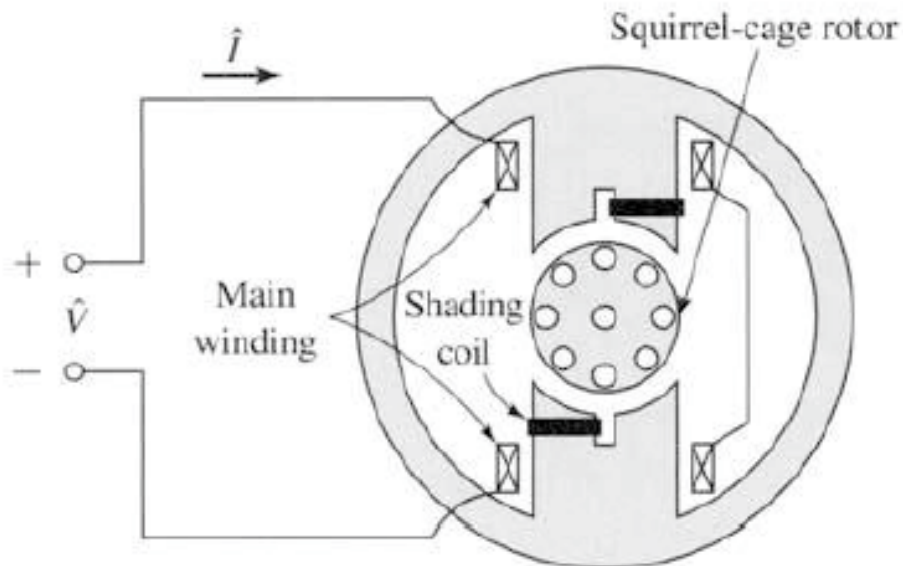


# Induction Machines: 1-phase Induction Motors


10

## Motor Types

### 5. Shaded-pole Motor

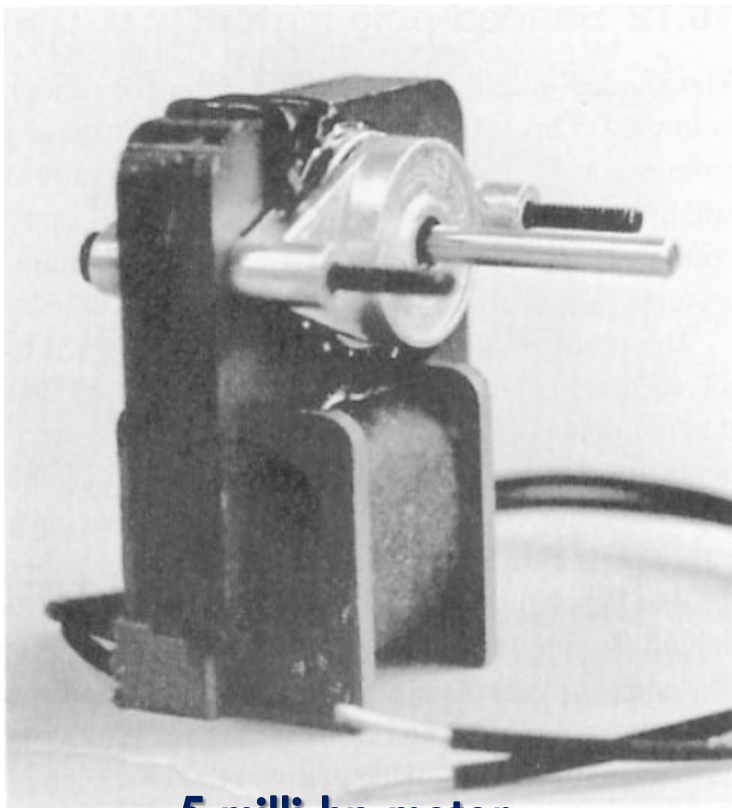

**5 milli-hp motor**

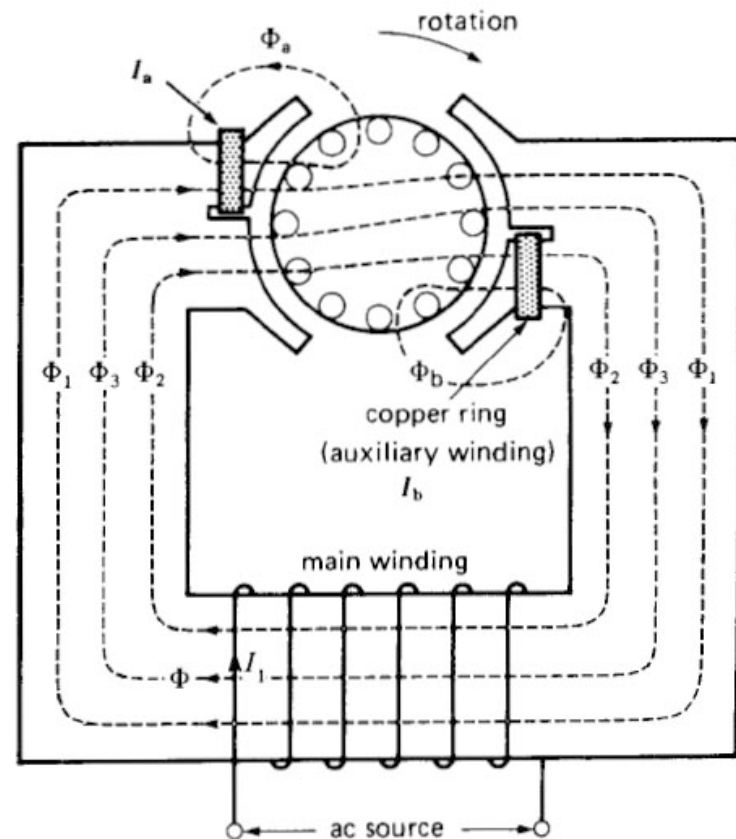


# Induction Machines: 1-phase Induction Motors

11

## Starting Winding Design

At starting ( $n=0, s=1$ )


**Split-phase (resistance start)**

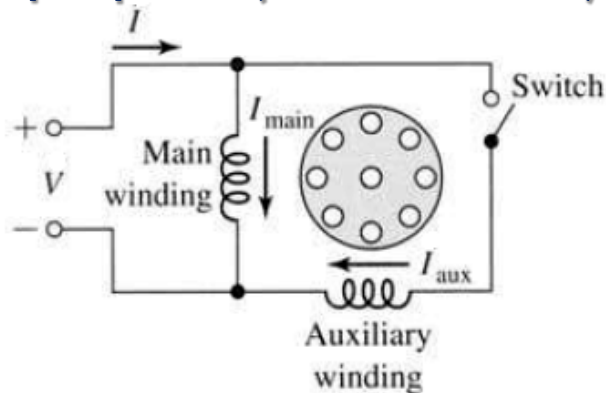

$$I_M = \frac{V}{Z_M}$$

$$I_A = \frac{V}{Z_A + R_{add}}$$

**Capacitor-start**

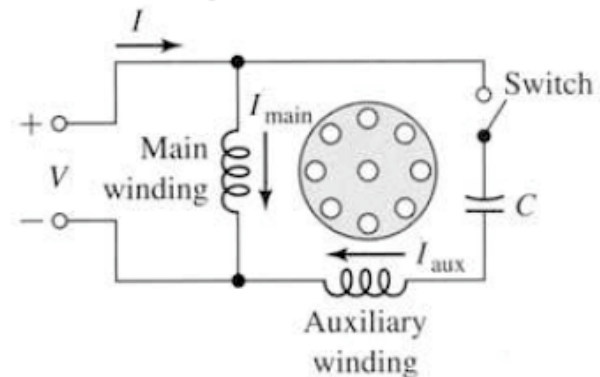

$$I_M = \frac{V}{Z_M}$$

$$I_A = \frac{V}{Z_A - jX_C}$$

$Z_M$  = standstill impedance of the main winding


$Z_A$  = standstill impedance of the auxiliary winding

# Induction Machines: 1-phase Induction Motors


12

## Starting Winding Design

### Split-phase (resistance start)

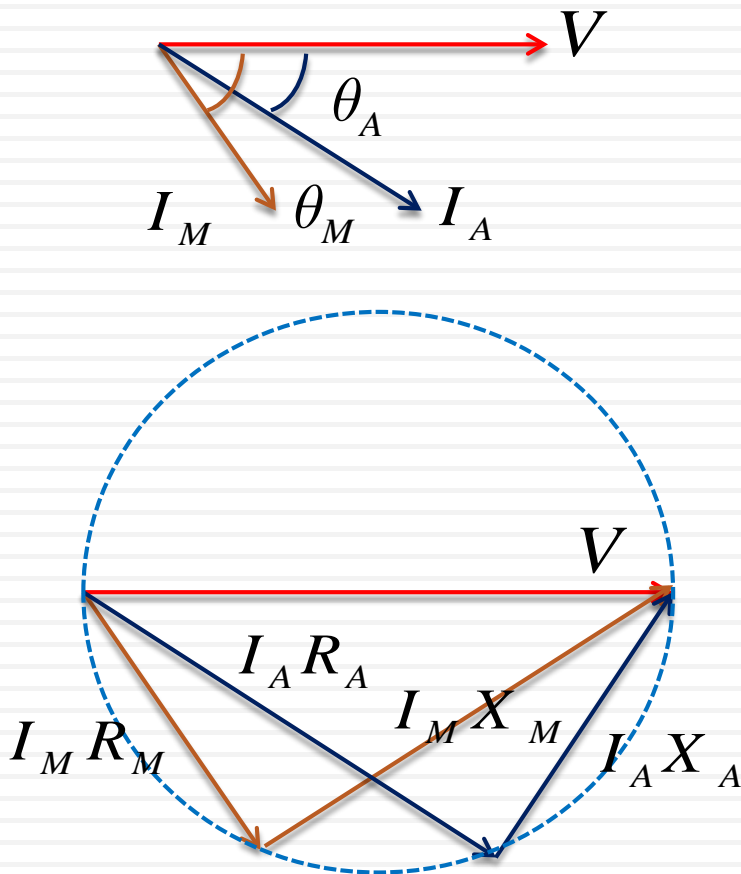

### Capacitor-start

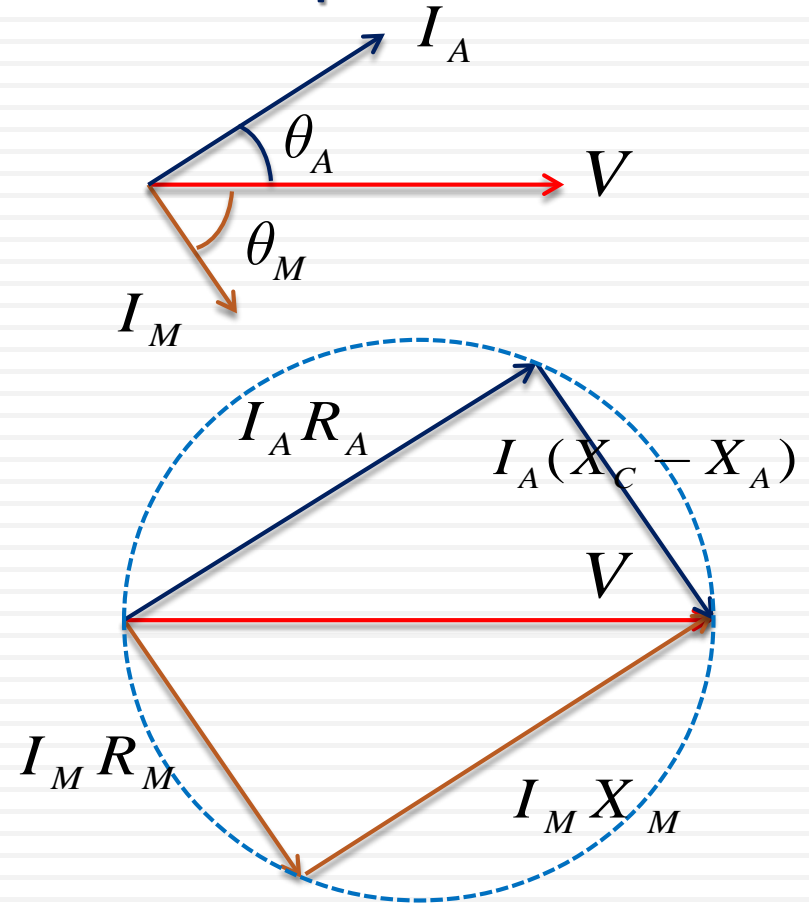





# Induction Machines: 1-phase Induction Motors

15

## Testing: 1. Locked Rotor (Standstill) Test

Voltage is adjusted such that stator current  $\leq$  full load current

Main winding only is connected

Reduced  
Voltage

$$W_{LR}$$

$$W_{LR} = P_{cu1} + P_{cu2}$$

$$W = I_{LR}^2 R_{LR}$$

$$R_{LR} = R_1 + R_2'$$

$$R_1 = R_2' = \frac{R_{LR}}{2}$$


$$V_{LR}$$

$$Z_{LR} = \frac{V_{LR}}{I_{LR}}$$

$$Z_{LR} = \sqrt{R_{LR}^2 + X_{LR}^2}$$

$$X_{LR} = X_1 + X_2'$$

$$X_1 = X_2' = \frac{X_{LR}}{2}$$

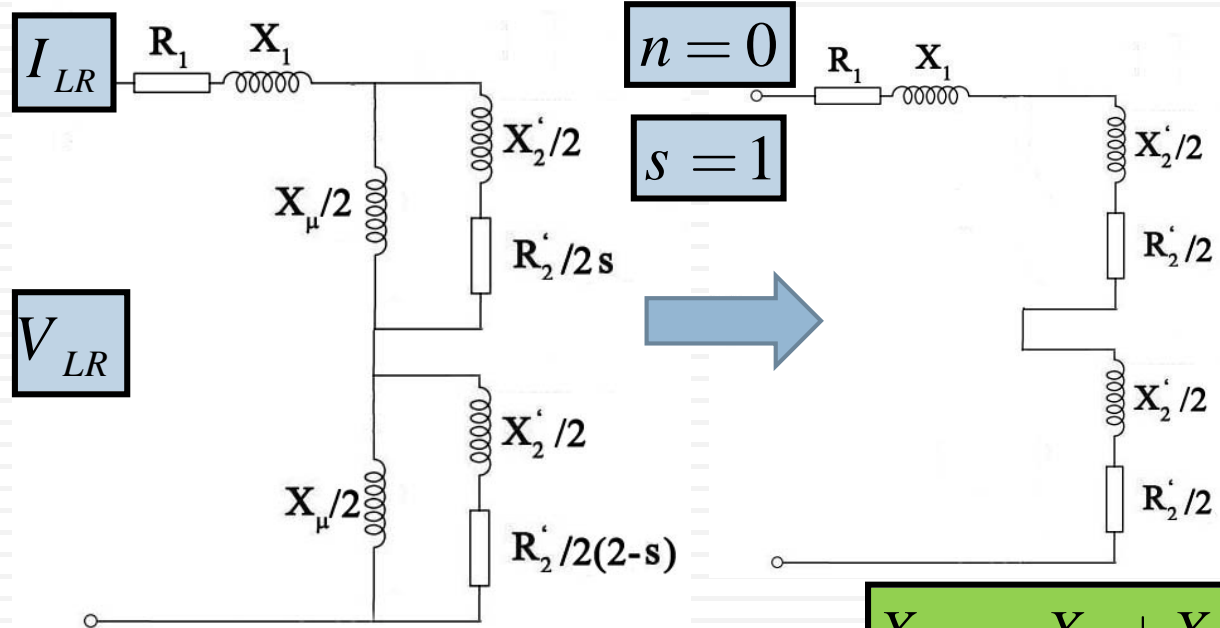


# Induction Machines: 1-phase Induction Motors

16

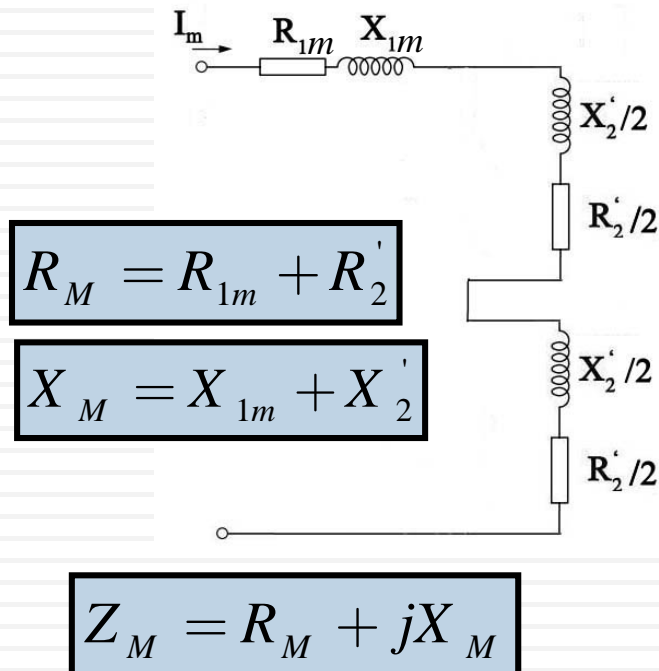
## Testing: 1. Locked Rotor (Standstill) Test

To get the standstill impedances of the main and auxiliary windings, this test is performed on each winding individually.

*Main Winding only connected to the supply*



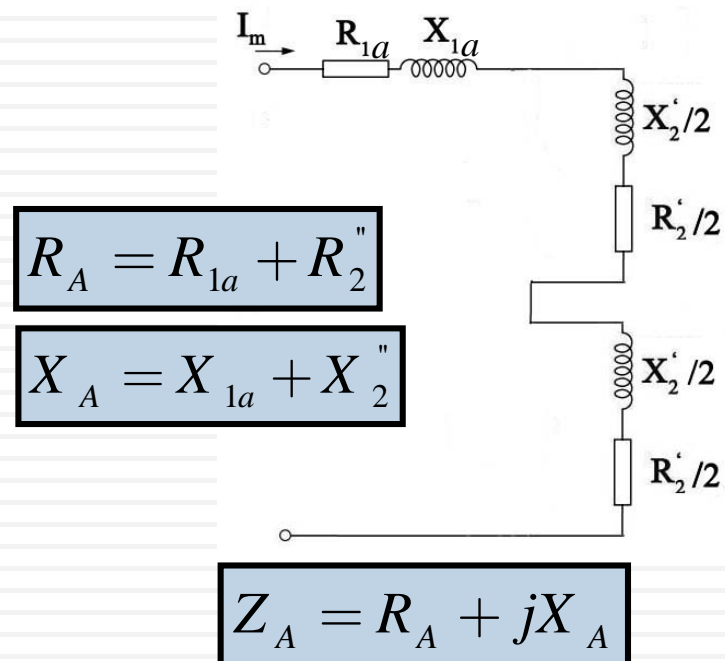*Aux. Winding only connected to the supply*



# Induction Machines: 1-phase Induction Motors

## Testing: 2. No-Load Test

$$W_{NL} = P_{mech} + P_{cu1}$$

$$W_{NL}$$

$$P_{cu1} = I_{NL}^2 \left( R_1 + \frac{R_2'}{4} \right)$$

$V_{NL}$  **Rated Voltage**


$$P_{mech}$$

$$Z_{NL} = \frac{V_{NL}}{I_{NL}}$$

$$Z_{NL} = \sqrt{R_{NL}^2 + X_{NL}^2}$$

$$X_{NL} = X_1 + \frac{X_2'}{2} + \frac{X_\mu}{2}$$

$s \approx 0$

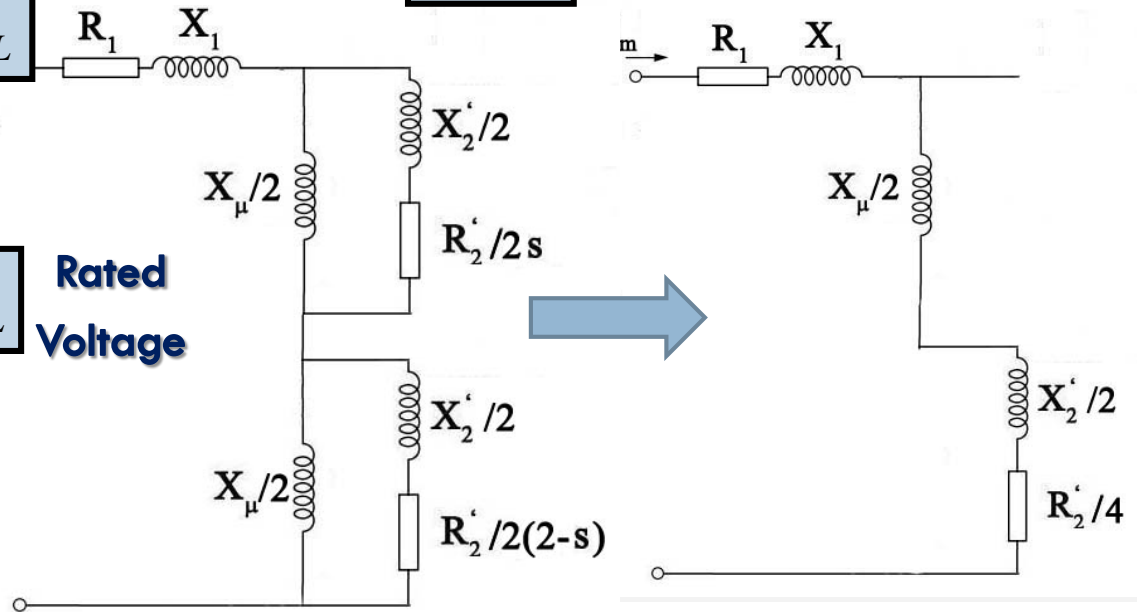

$$X_\mu = 2 \times \left( X_{NL} - X_1 - \frac{X_2'}{2} \right)$$