
Circuits I

Lecture 3-5: Methods of DC Solutions

Dr. Hassan Mostafa

hmostafa@uwaterloo.ca

Cairo University

Modified from Dr. Mohamed Fathy Slides

Fall 2019

Methods of solution of DC circuits

- **Definition :**


The problem of solution of DC circuits is finding the **response** (voltage, current, power) in any circuit element due to **input excitation** (voltage and/or current sources).

Methods of solution of DC circuits


- Method 1: Branch Method : KCL & KVL
- Circuit Topology
 - N** Nodes **L** Loops **B=N+L-1** Branches
 - Write **N-1** equations at (**N-1 nodes**) using KCL
 - Write **L** equations at (**L independent Loops**) using KVL
 - Solve the **N+L-1** equations to find all **branch currents**.

50

Example

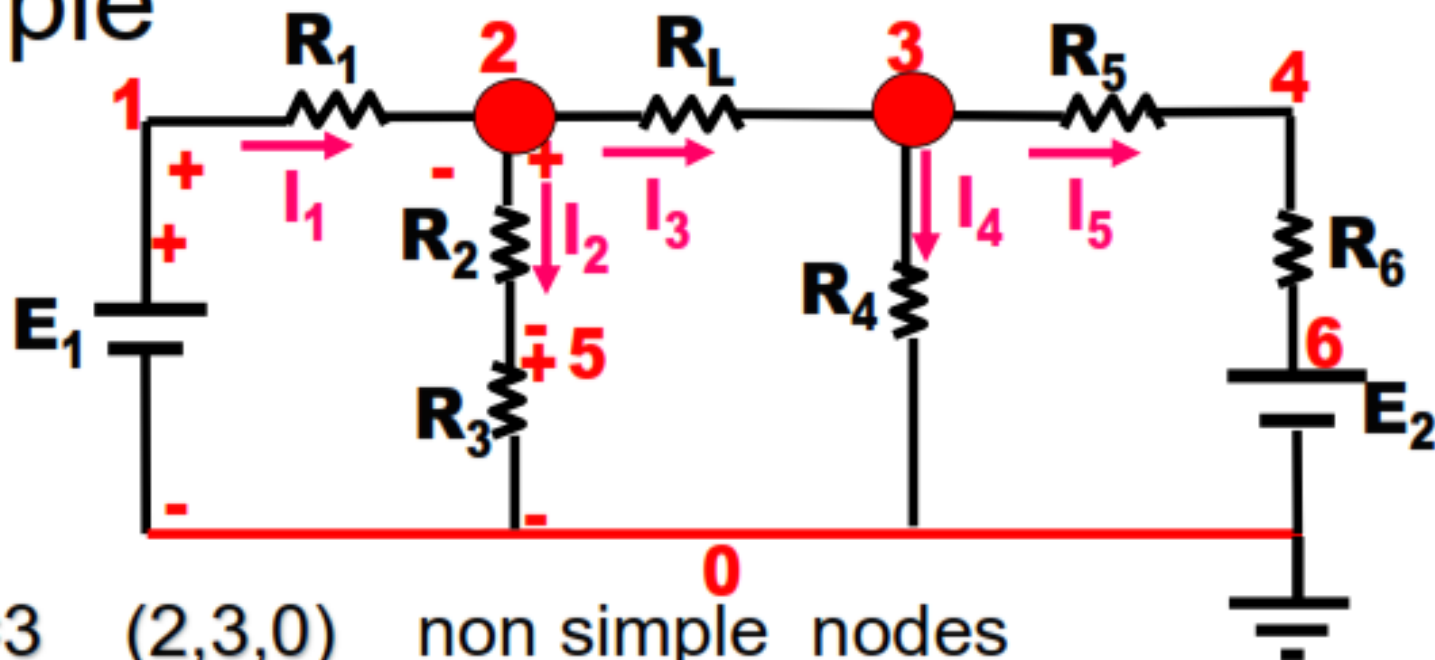

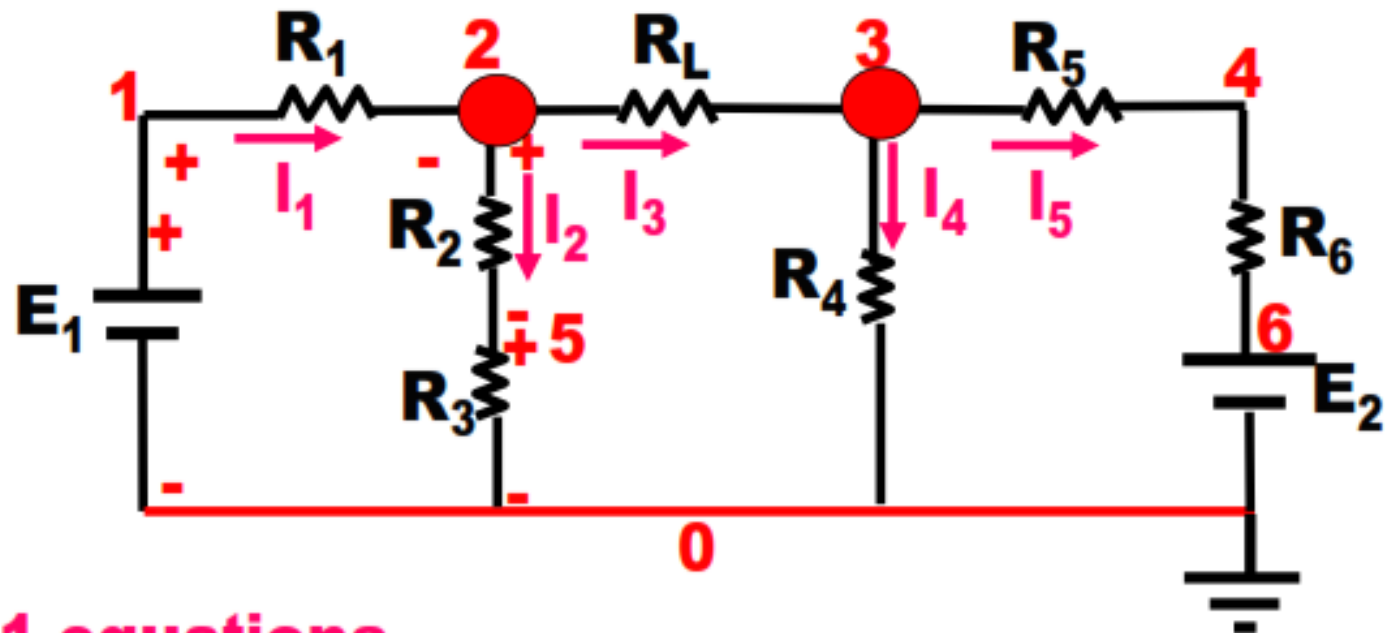
- Nodes: $N=3$ (2,3,0) non simple nodes
- Loops: $L=3$ independent loops 12501, 23052, 34603
- Branches $B=5$ 012, 250, 23, 30, 3460
- $B=N+L-1$



✓ Write $N-1$ equations
using KCL (usually node 0 is excluded)

Node 2

Node 3

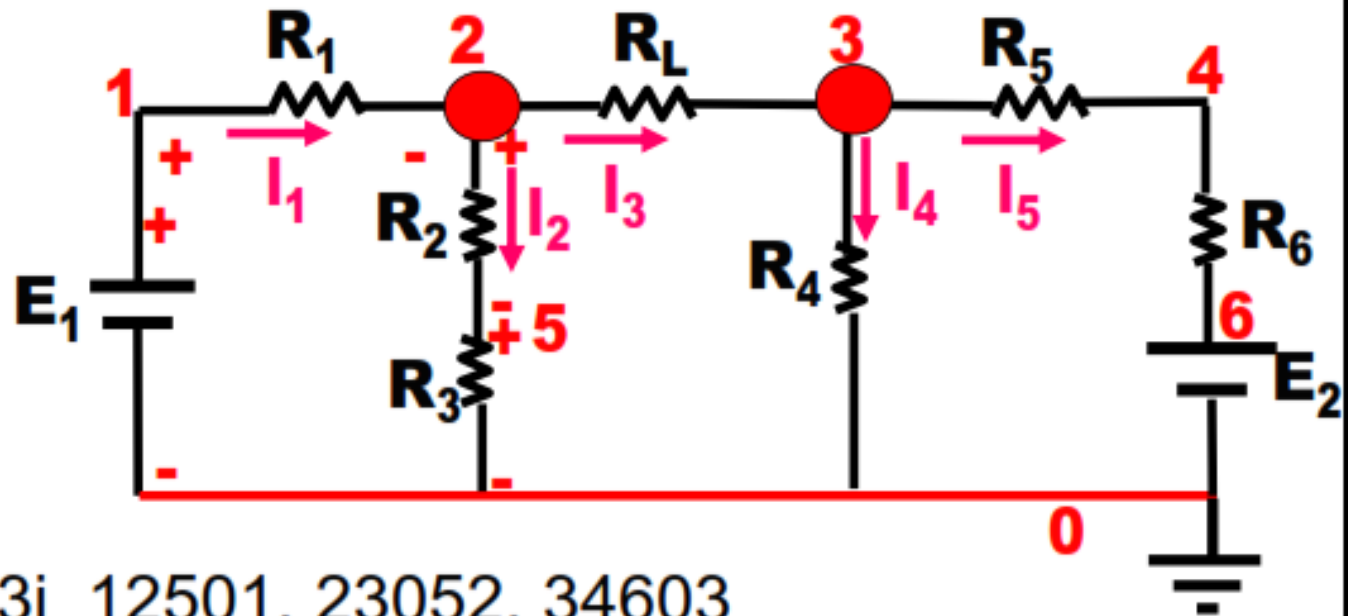


- Loops: $L=3i$ 12501, 23052, 34603

✓ **Write L equations using KVL**

Loop 12501

$$V_{12} + V_{25} + V_{50} + V_{01} = 0$$

✓ Write L equations using KVL

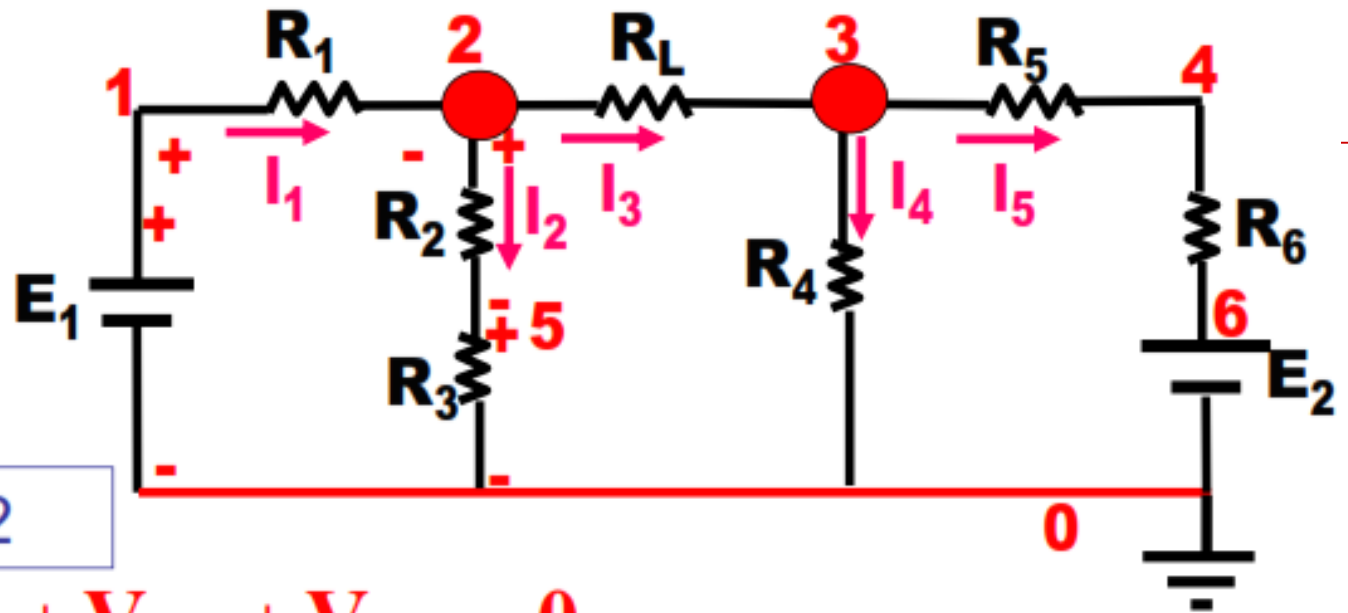

Loop 23052

$$V_{23} + V_{30} + V_{05} + V_{52} = 0$$

Loop 34603

$$V_{34} + V_{46} + V_{60} + V_{03} = 0$$

Example

$$\mathbf{I}_1 - \mathbf{I}_2 - \mathbf{I}_3 = 0 \quad (1)$$

$$\mathbf{I}_3 - \mathbf{I}_4 - \mathbf{I}_5 = 0 \quad (2)$$


$$\mathbf{I}_1 \mathbf{R}_1 + \mathbf{I}_2 \mathbf{R}_2 + \mathbf{I}_2 \mathbf{R}_3 - \mathbf{E}_1 = 0 \quad (3)$$

$$\mathbf{I}_3 \mathbf{R}_L + \mathbf{I}_4 \mathbf{R}_4 - \mathbf{I}_2 \mathbf{R}_3 - \mathbf{I}_2 \mathbf{R}_2 = 0 \quad (4)$$

$$\mathbf{I}_5 \mathbf{R}_5 + \mathbf{I}_5 \mathbf{R}_6 + \mathbf{E}_2 - \mathbf{I}_4 \mathbf{R}_4 = 0 \quad (5)$$

How to put Equations in a matrix form?

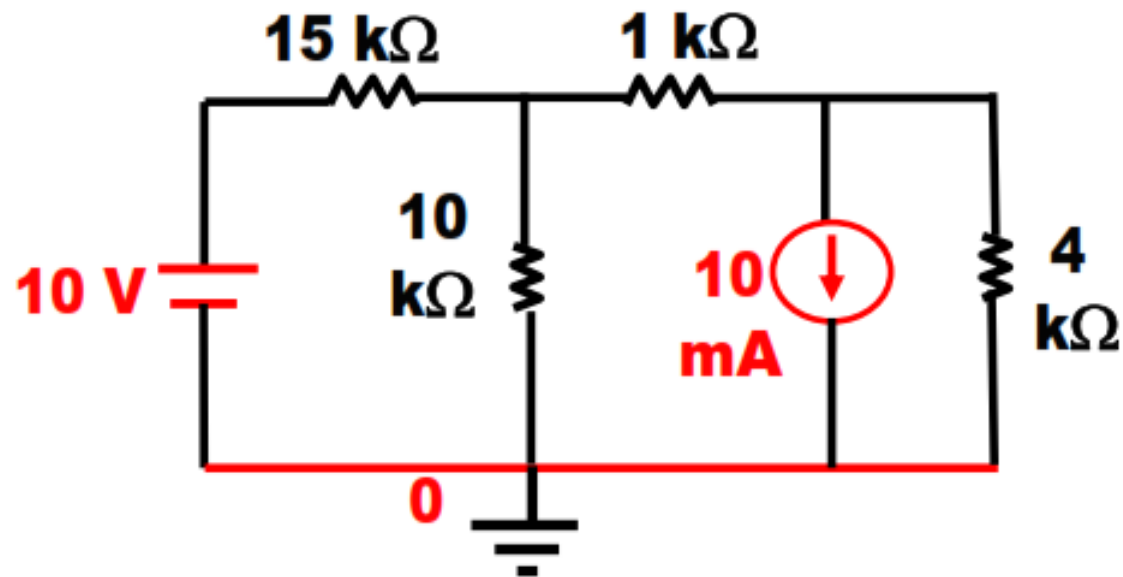
For the shown circuit, find all branch currents and check the power balance



N=

L=

B=

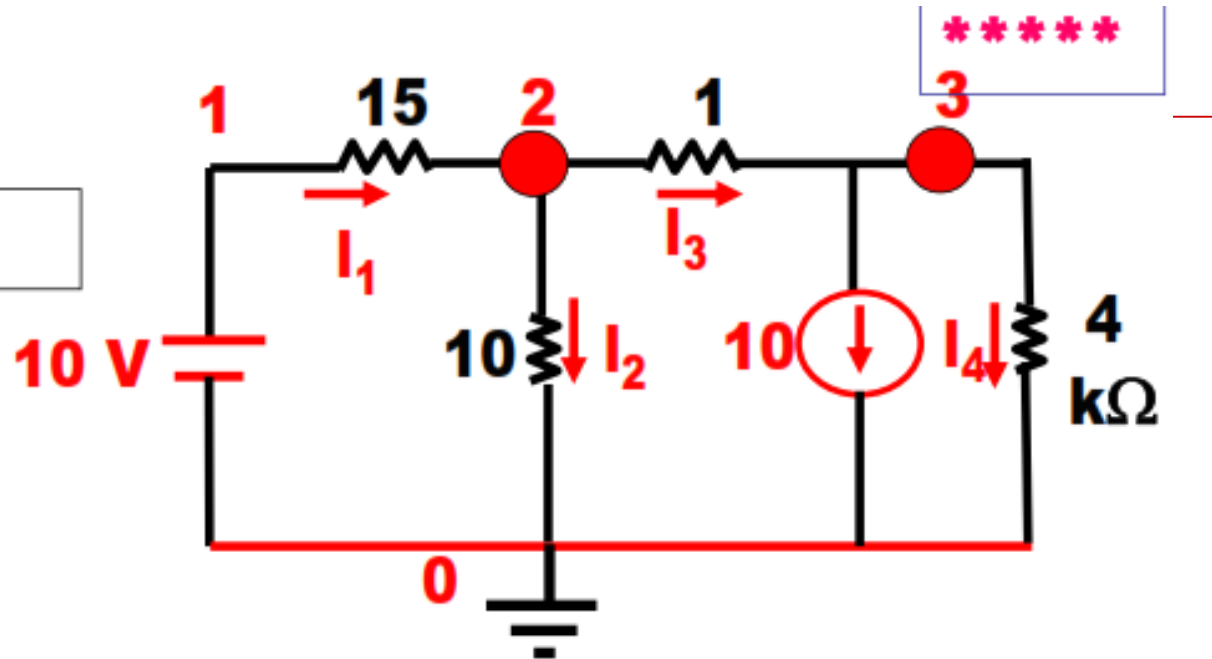


KCL Node 2

KCL Node 3

KVL loop 1201

KVL loop 2302

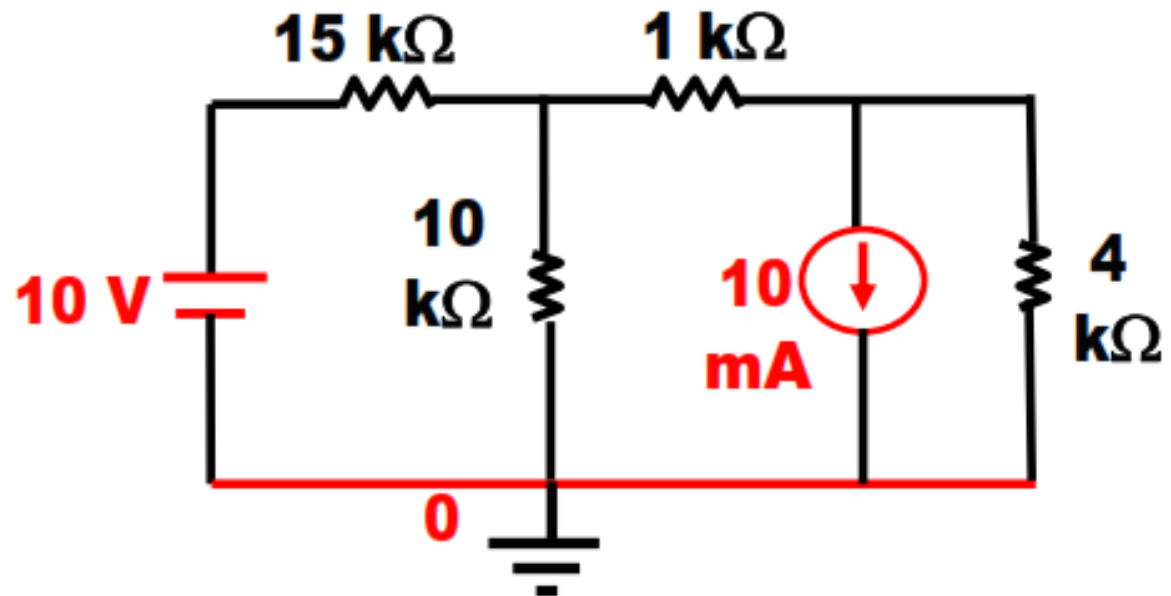For the shown circuit, find all branch currents and check the power balance




Solve equations 1-4 to get:

$$\mathbf{I_1=2} \quad \mathbf{I_2=-2} \quad \mathbf{I_3=4} \quad \mathbf{I_4=-6}$$

Power balance

R k Ω	Power (mw) I^2R
15	
10	
1	
4	
Total	

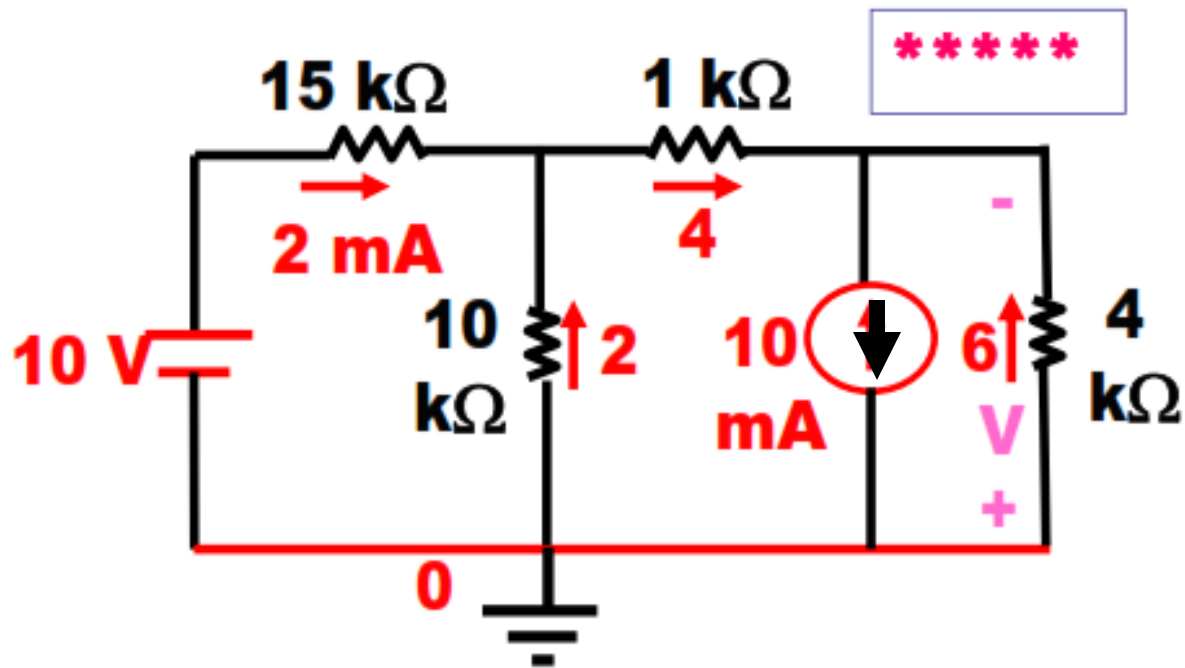

Source	Power (mw)
10 V	
10 mA	
Total	

59

BEAT QUESTION

Two random students are selected and keep asking questions till one beats the other...

Fourth row, second student from the left wall

third row, fourth student from the right wall

Punishment: Read the following:

سبع لحاليح استلحلحناهم من عند المستلحلحين تقدر يا ملحلح يا
مستلحلح تستلحلحنا سبع لحاليح زى ما استلحلحناهم من عند
المستلحلحين

Methods of solution of DC circuits


- **Method 2 Step by Step Simplification**
 - 1. Transforming current sources into equivalent voltage sources or visa versa**
 - 2. Combination of active elements**
 - 3. Replacing series and parallel resistors by its equivalent (All resistors are assumed linear)**
 - 4. Star-Delta or Delta-Star transformation**

Method 2

Step by Step Simplification

- **Source Equivalence**
- **Combination of active elements**

Solution

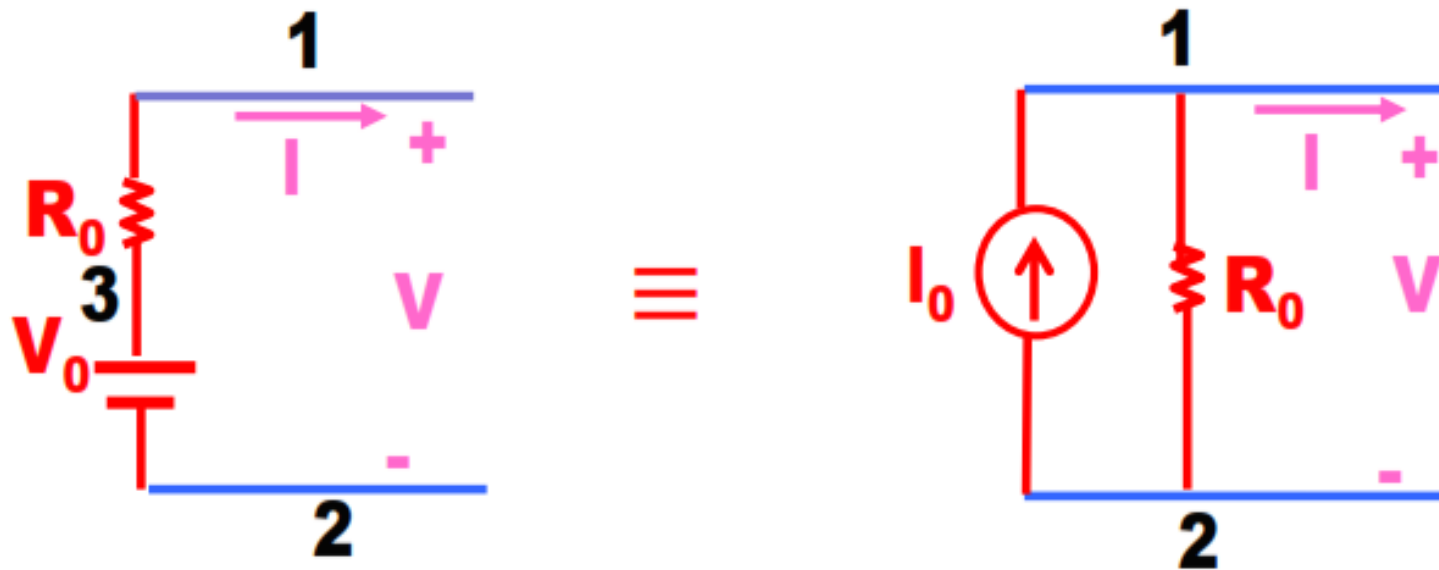

$$V = V_{12} = V_{13} + V_{32} = -IR_0 + V_0$$


$$I_0 = I + \frac{V}{R_0}$$

$$V = V_0 - IR_0$$


$$V = I_0 R_0 - IR_0$$

$$V_0 = I_0 R_0$$

$$V = V_0 - IR_0$$

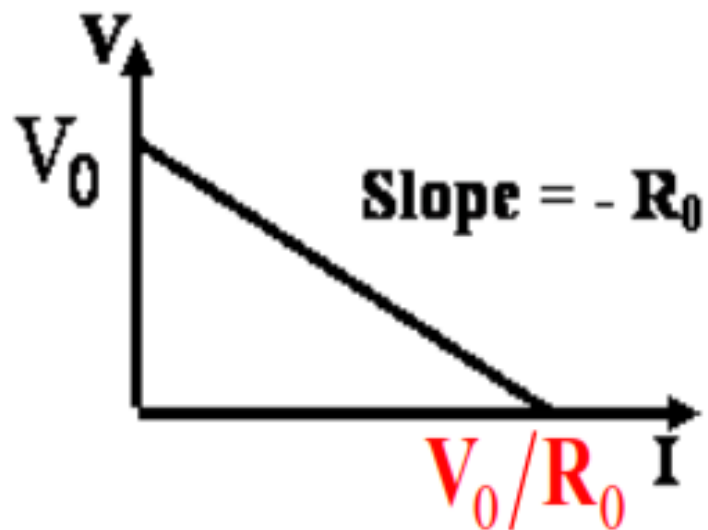


$$V = I_0 R_0 - IR_0$$

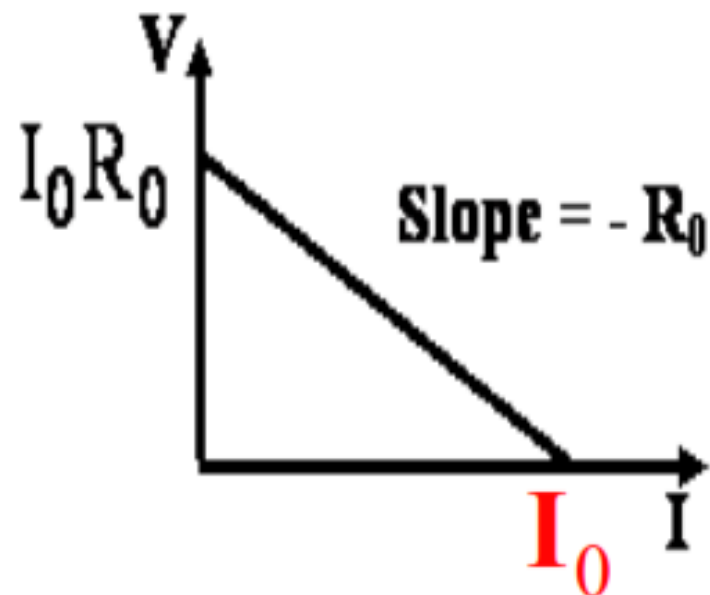

$$V_0 = I_0 R_0$$

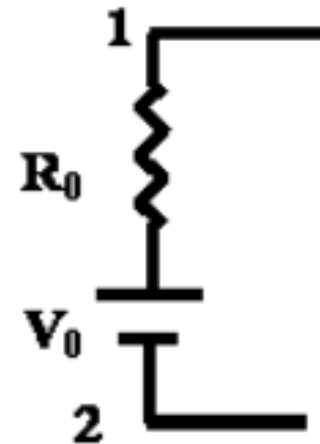
Example

- Convert the shown voltage source ($V_0 = 3\text{V}$ & $R_0 = 100\Omega$) into its equivalent current source.




Solution
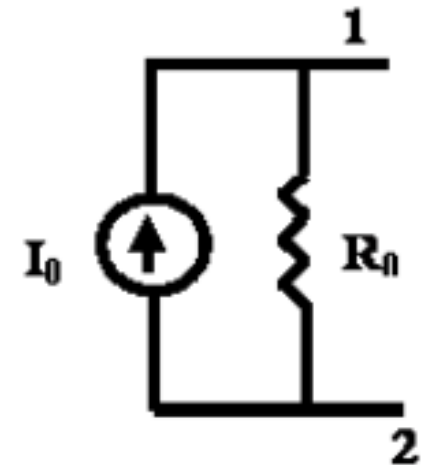
$$I_0 = \frac{V_0}{R_0} = \frac{3}{0.1} = 30\text{mA}$$



Combination of active elements


i) Series Connection

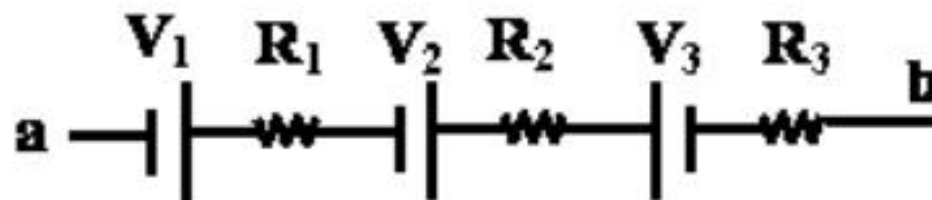

$\equiv$



$$V_0 = V_1 + V_2 - V_3$$

$$R_0 = R_1 + R_2 + R_3$$

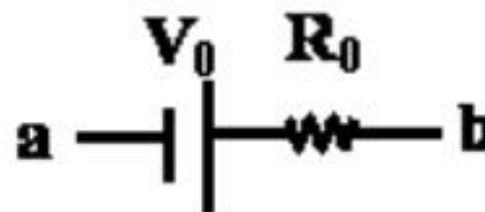

Combination of active elements

ii) Parallel Connection

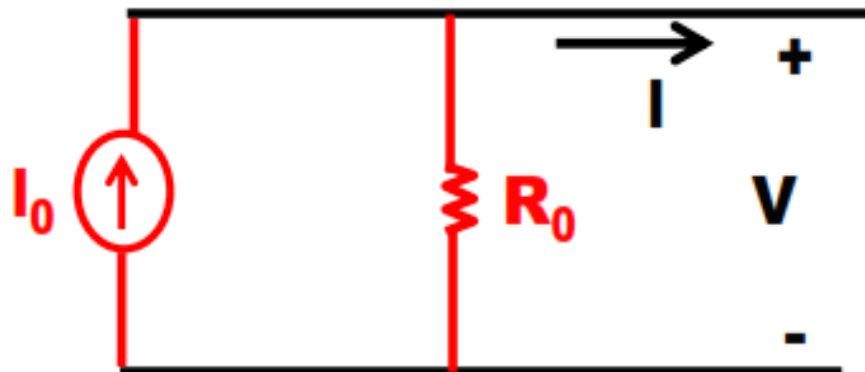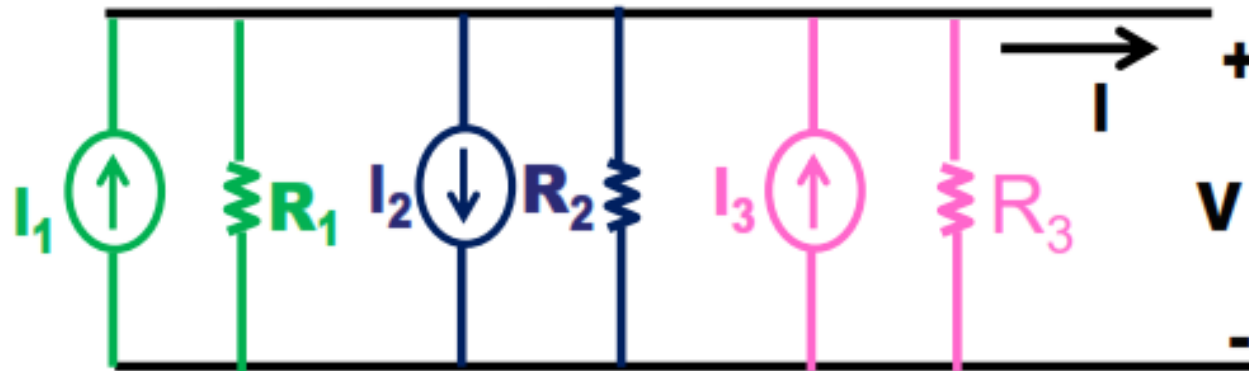


$$I_0 =$$

$$\frac{1}{R_{eq}} =$$




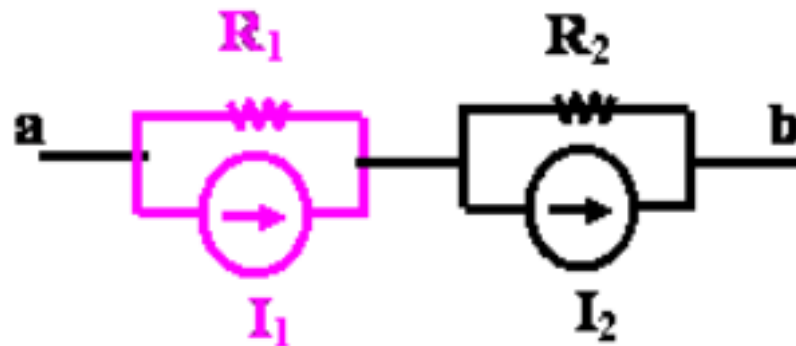
Example

- Convert the shown current sources ($I_1 = 100 \text{ mA}$, $R_1 = 50 \Omega$, $I_2 = 200 \text{ mA}$, and $R_2 = 50 \Omega$) into one equivalent current source.



Solution

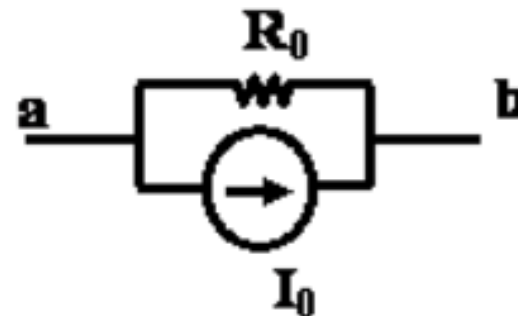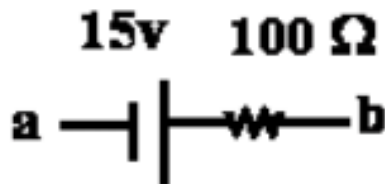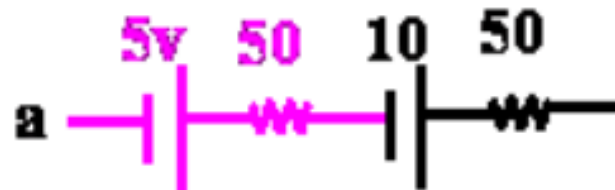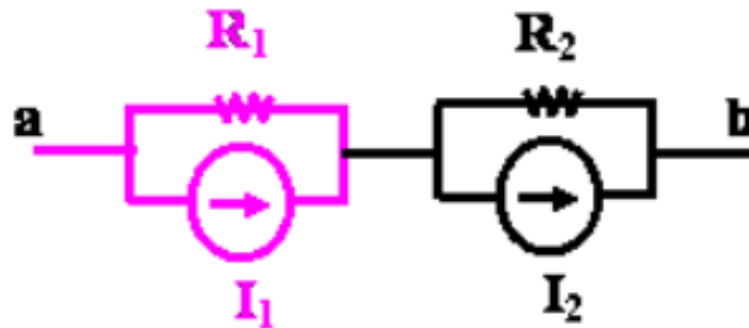($I_1 = 100 \text{ mA}$, $R_1 = 50 \Omega$, $I_2 = 200 \text{ mA}$, and $R_2 = 50 \Omega$)




$I_0 =$



$R_0 =$


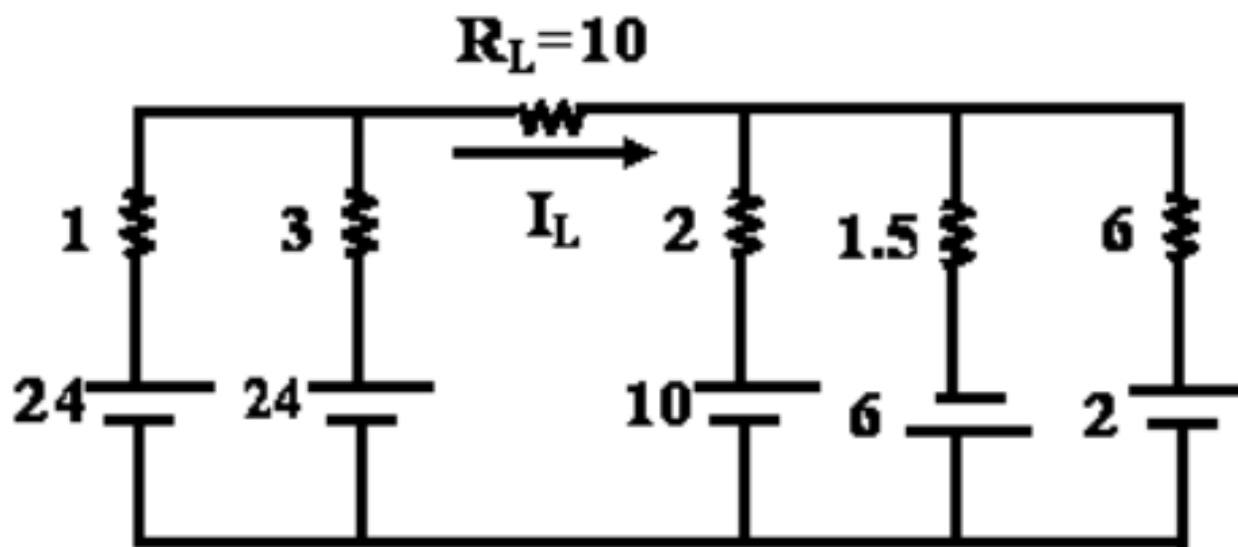
Example

- For the shown circuit, use simplification method to find the load current I_L . (All voltages are in Volts & all resistors are in $k\Omega$).




Solution

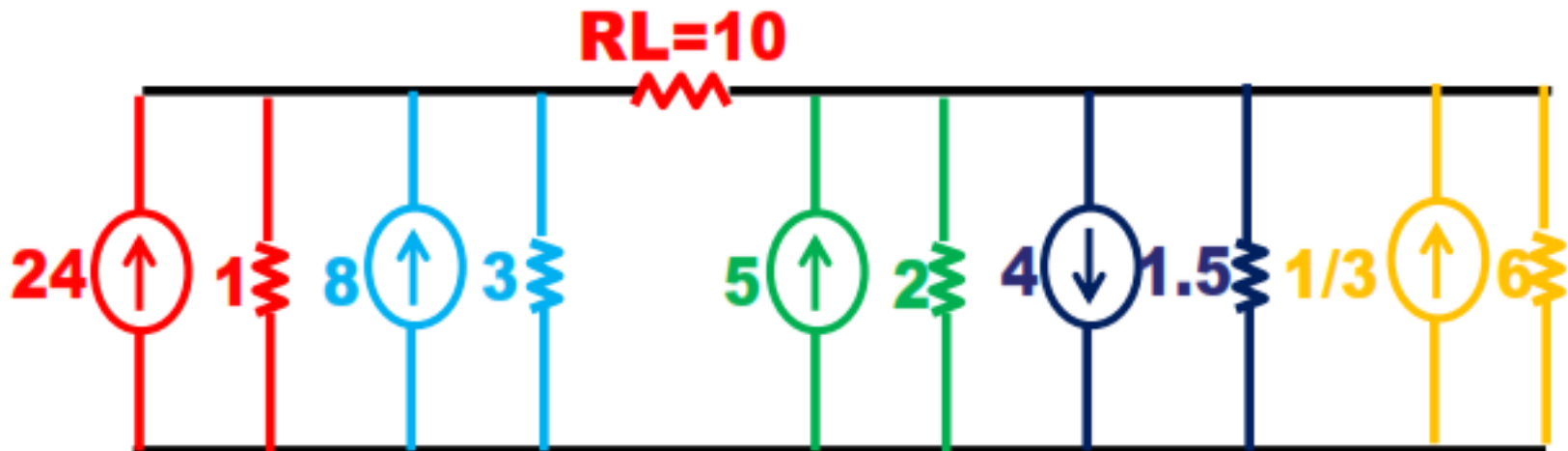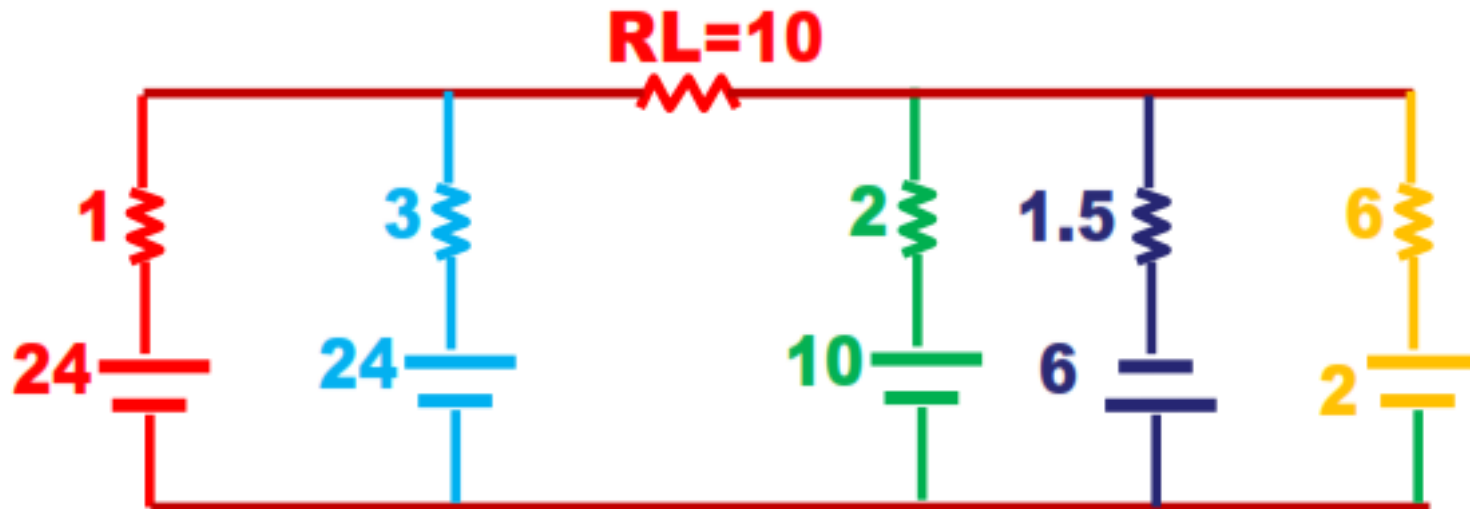

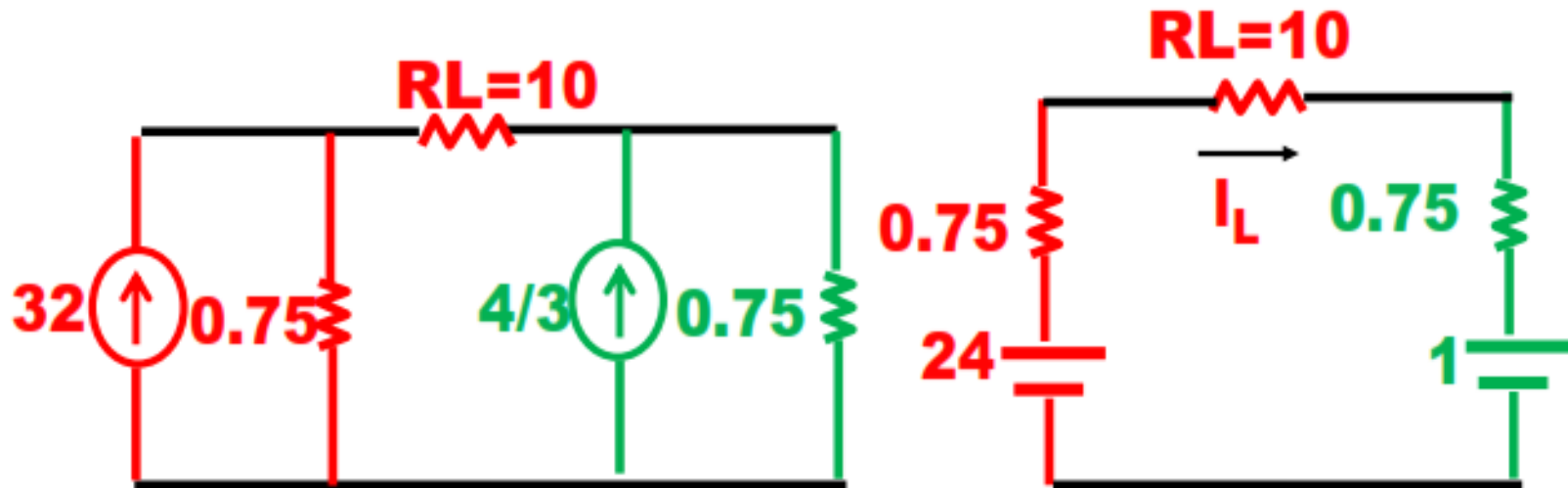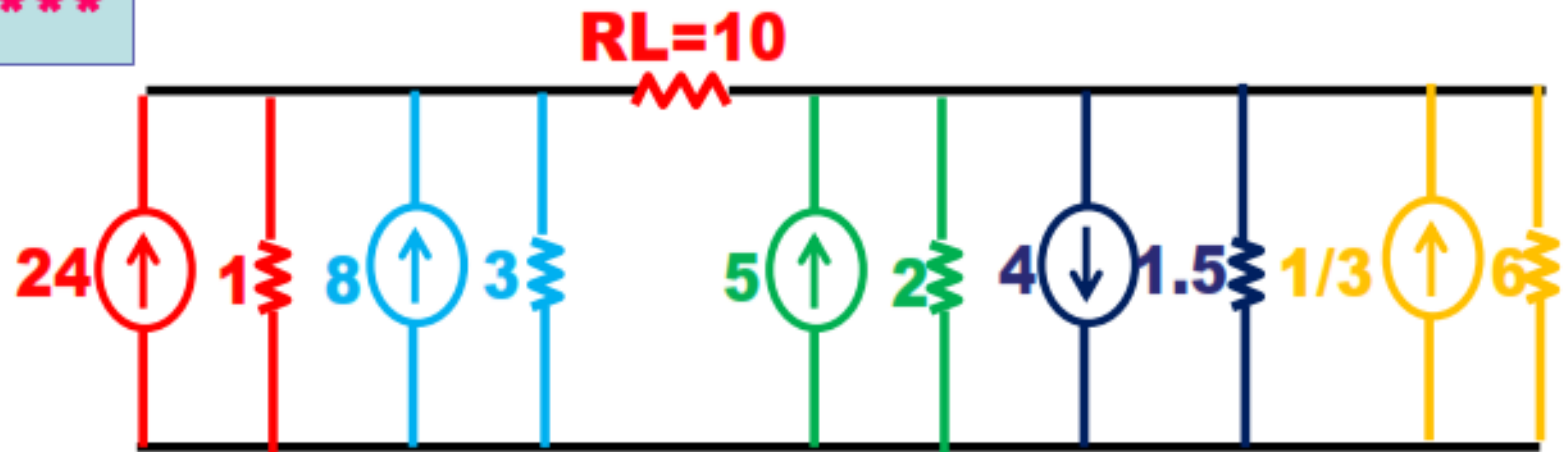


$$I_L =$$

Star - Delta Transformation

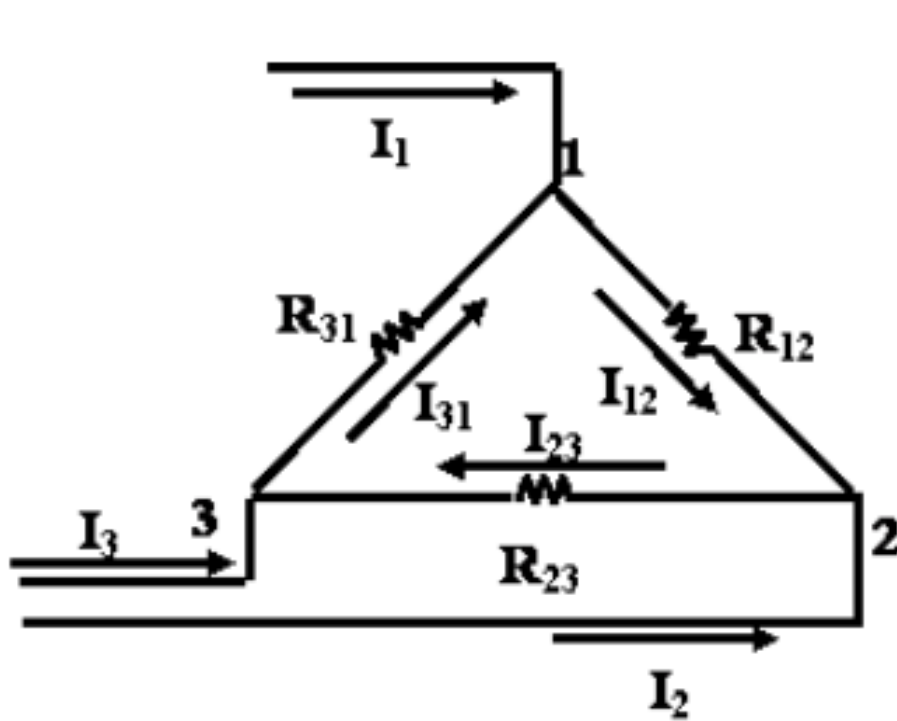


Delta (Pi or π)

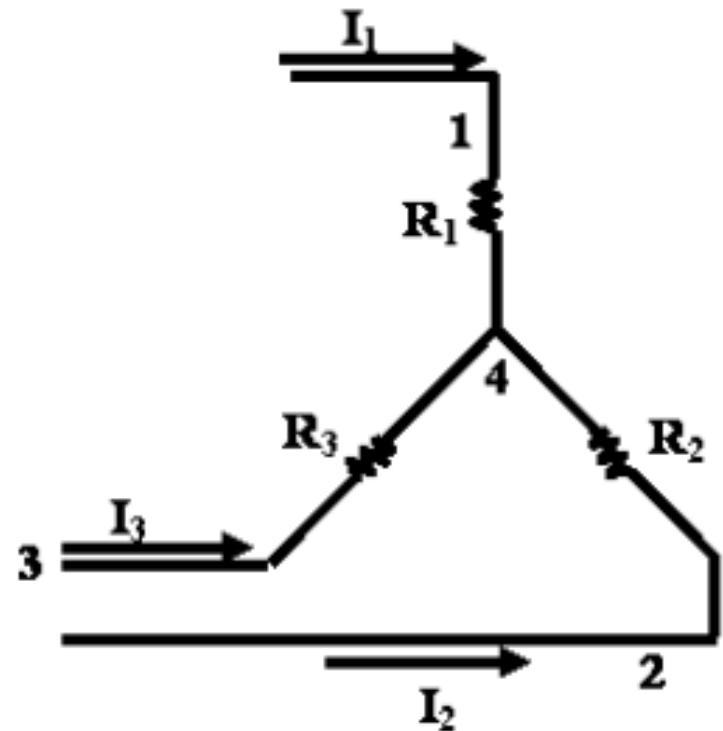

Star (Y or T)

Δ to Y Transformation

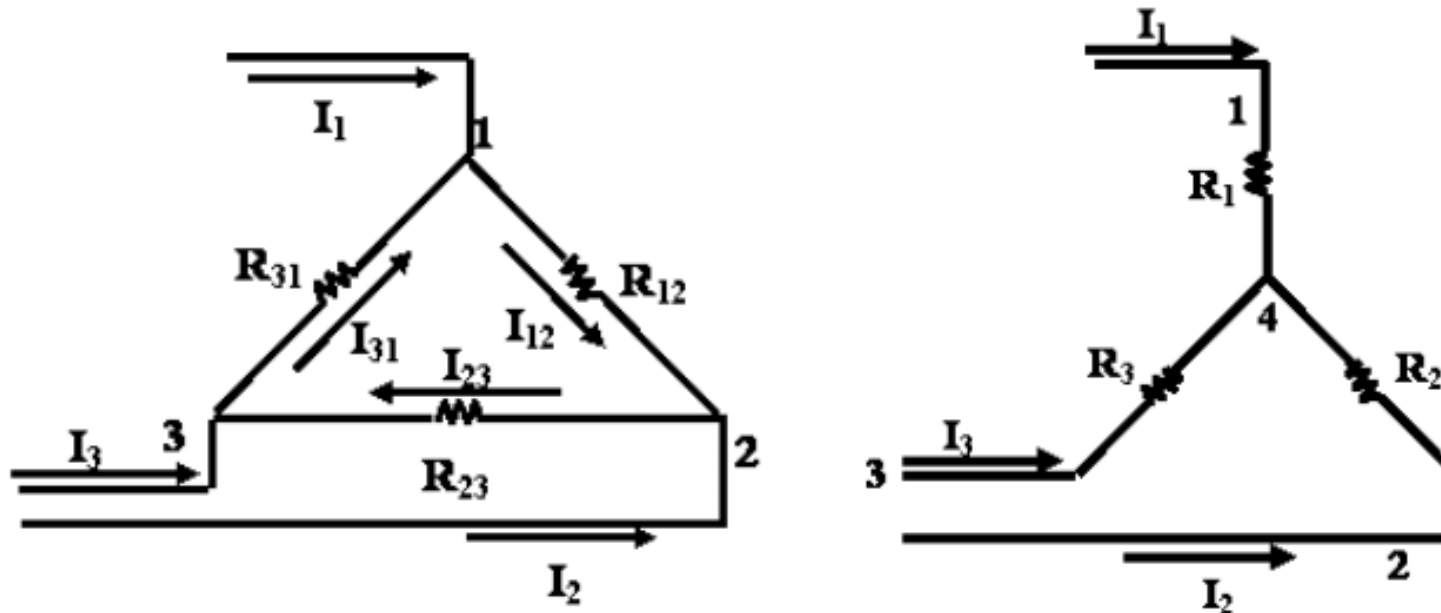

$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{23}R_{12}}{R_{12} + R_{23} + R_{31}}$$



$$R_3 = \frac{R_{31}R_{23}}{R_{12} + R_{23} + R_{31}}$$

Special case

$$R_{12} = R_{23} = R_{31} = R$$

$$R_1 = R_2 = R_3 = \frac{R}{3}$$

Y - Δ Transformation

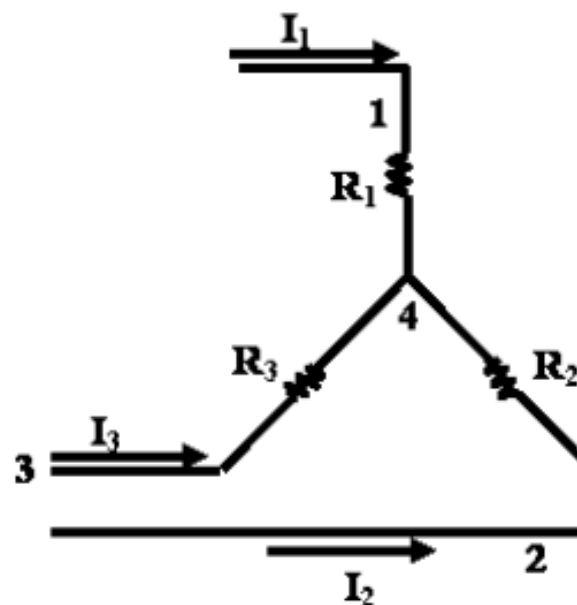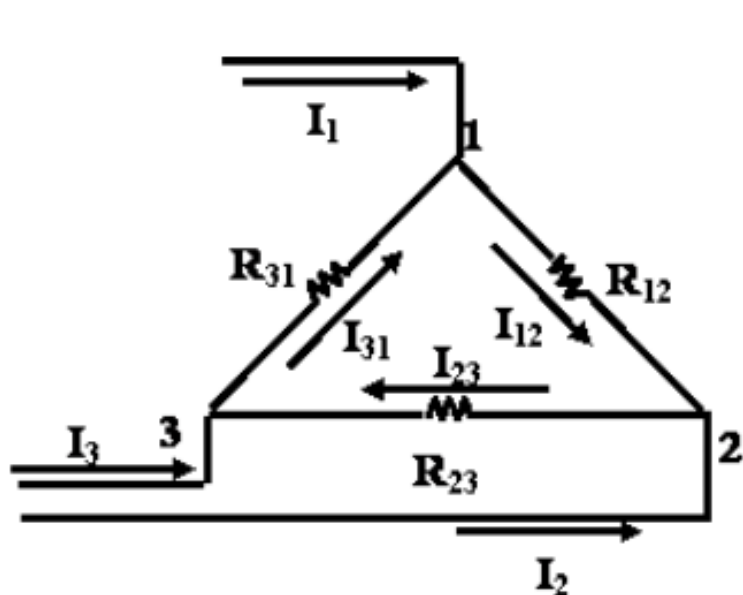

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$

Special case

$$R_1 = R_2 = R_3 = R$$

$$R_{12} = R_{23} = R_{31} = 3R$$

Assignment 1

(Deadline Oct. 27, 2019)

You are required to prove the previous relationships between Delta-Y transformations and Y-Delta transformations

Submit a hard copy assignment showing the proof

You are required to write a online program that takes on the values of the Delta branch resistors and produce the values of the Y branch resistors And vice versa. You can use whatever language but the program should be online

You should make an acceptable GUI for the program

Send your program link to

hmostafa@staff.cu.edu.eg with subject:


CMP_Assignment1_DeltaY_Your_Full_Name

Example

For the shown circuit , Find:


a) The input resistance between the two terminals 1 and 3



b) V_{23}

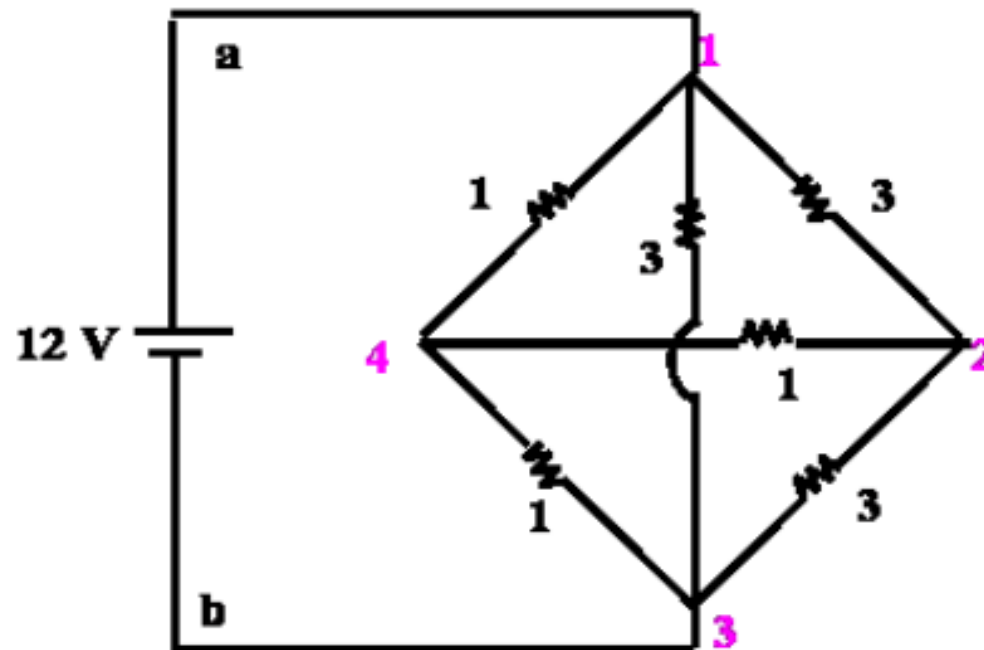

Solution 1

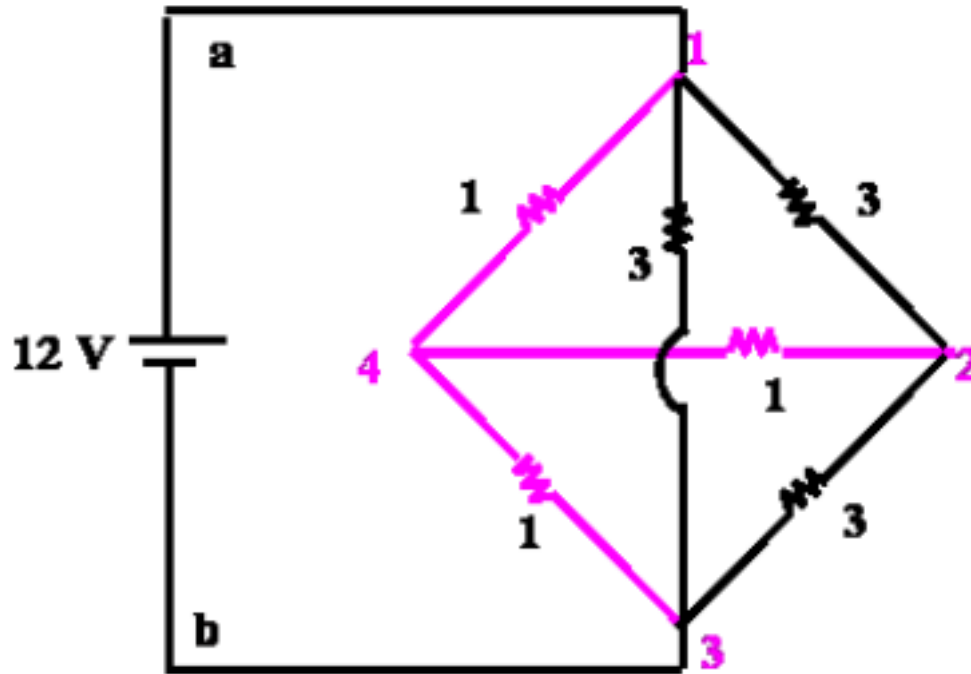By converting Y 123-4 $\Rightarrow$ Δ 123





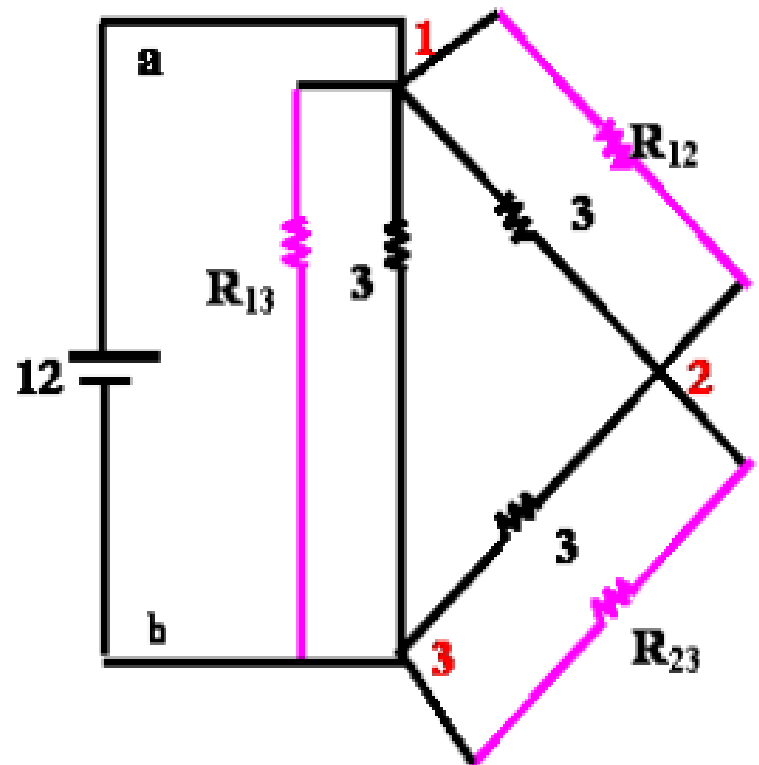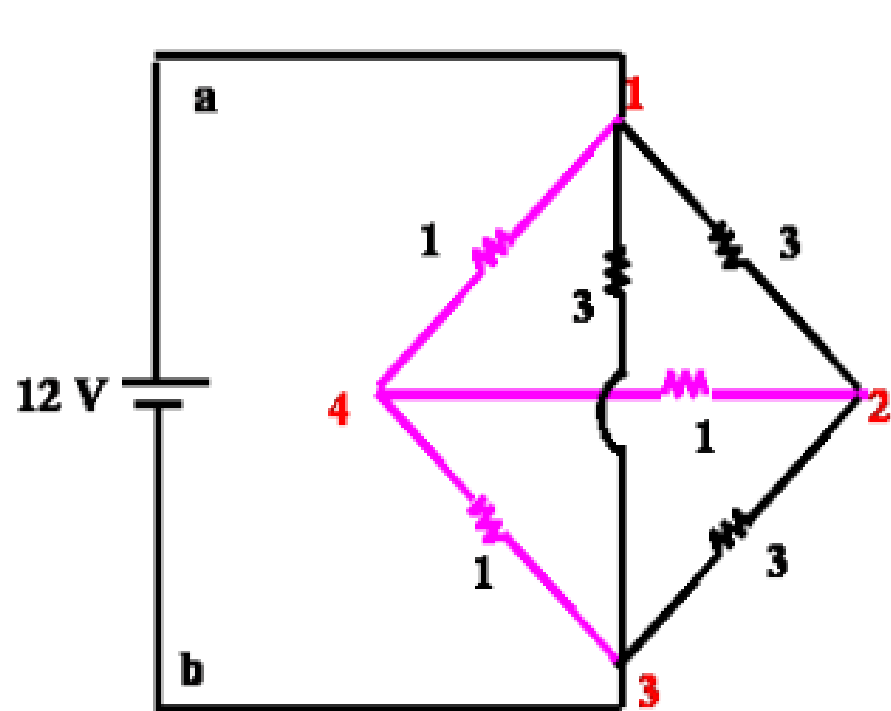

Special case

$$R_1 = R_2 = R_3 = R$$

$$R_{12} = R_{23} = R_{31} = 3R$$

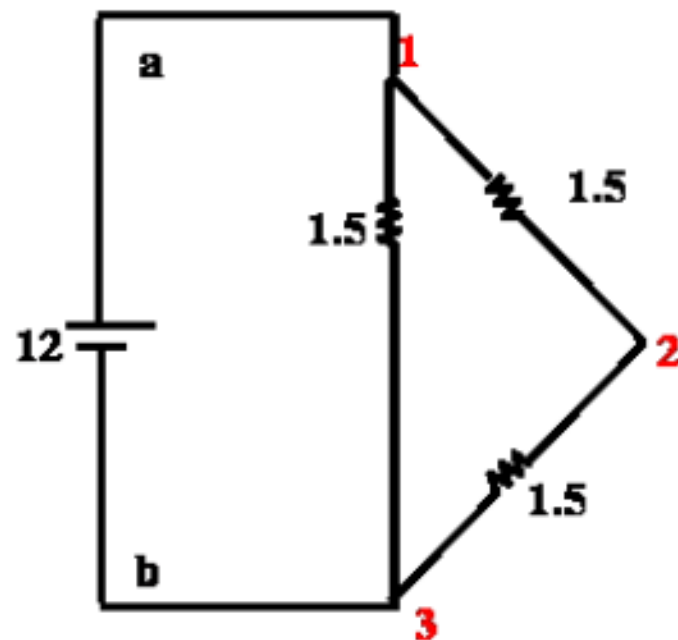
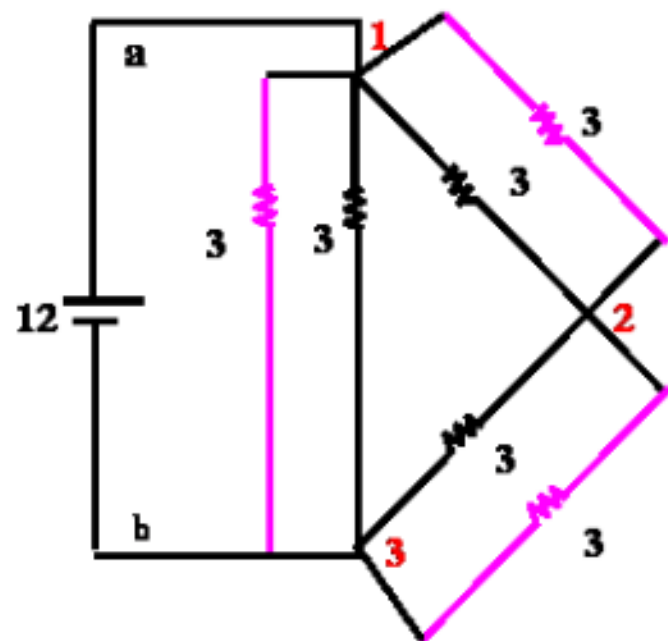


$$R_{13} =$$

$$V_{23} =$$

Solution 2

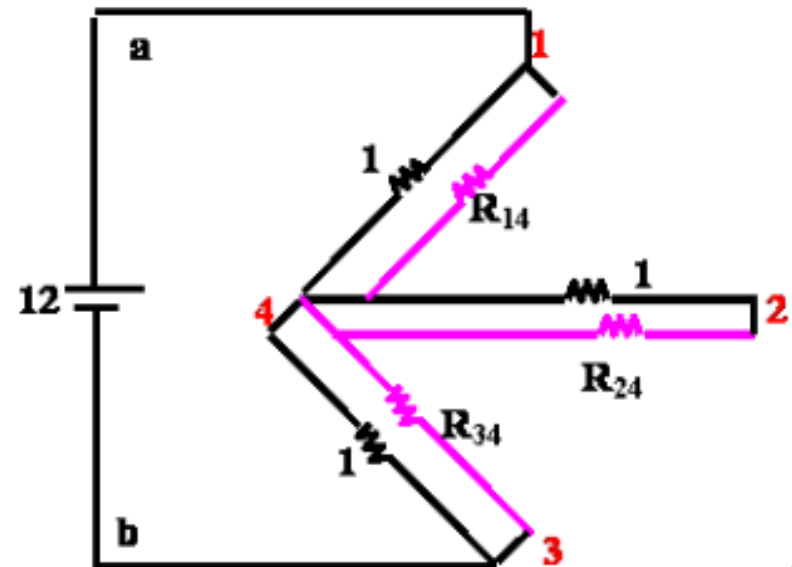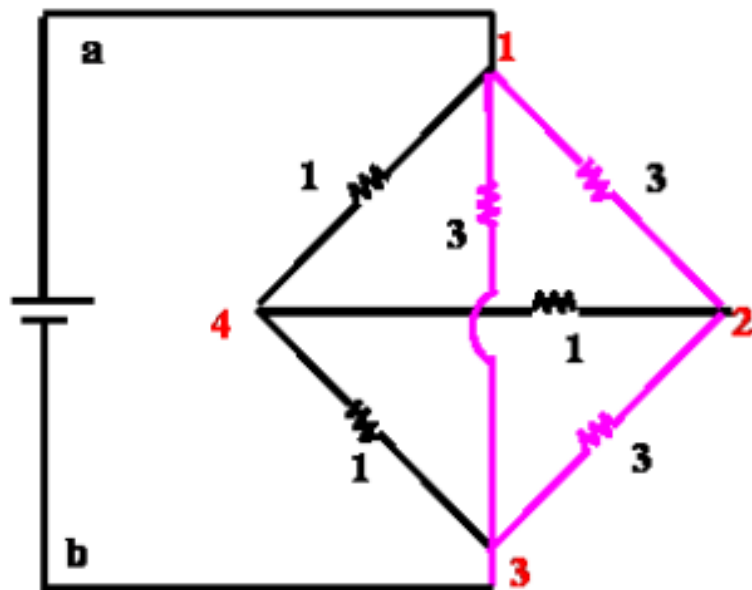By converting $\Delta 123 \Rightarrow Y 123-4$




Special case

$$R_{12} = R_{23} = R_{31} = R$$

$$R_1 = R_2 = R_3 = \frac{R}{3}$$

Solution 2

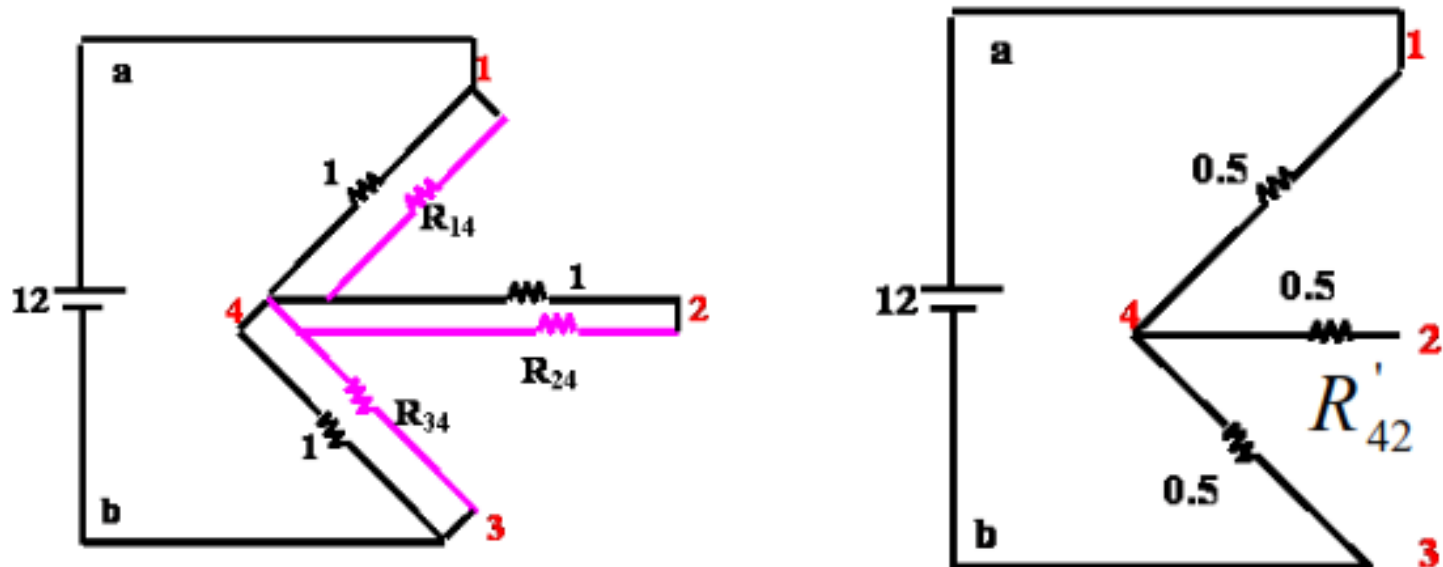By converting $\Delta 123 \Rightarrow Y 123-4$



Note that R'_{42} has no effect

$$R_{13} =$$

$$V_{23} =$$

IQ

Find five consecutive numbers in the list below that total 21.

5823639472165834259423

IQ

Find five consecutive numbers in the list below that total 21.

5823639472165834259423

Answer: 72165


Methods of solution of DC circuits (Cont.)

Method 3: Loop Analysis

Methods of solution of DC circuits

- **Method 3** Loop Current Method (Loop Analysis)
 - 1-Convert independent current sources into equivalent voltage sources
 - 2- Identify the number of independent loop (L) on the circuit
 - 3- Label a loop current on each loop (Clock wise direction).
 - 4- Write an expression for the KVL around each loop.
 - 5- Solve the resultant system of algebraic equations to find the L loop currents.

$L=3$;

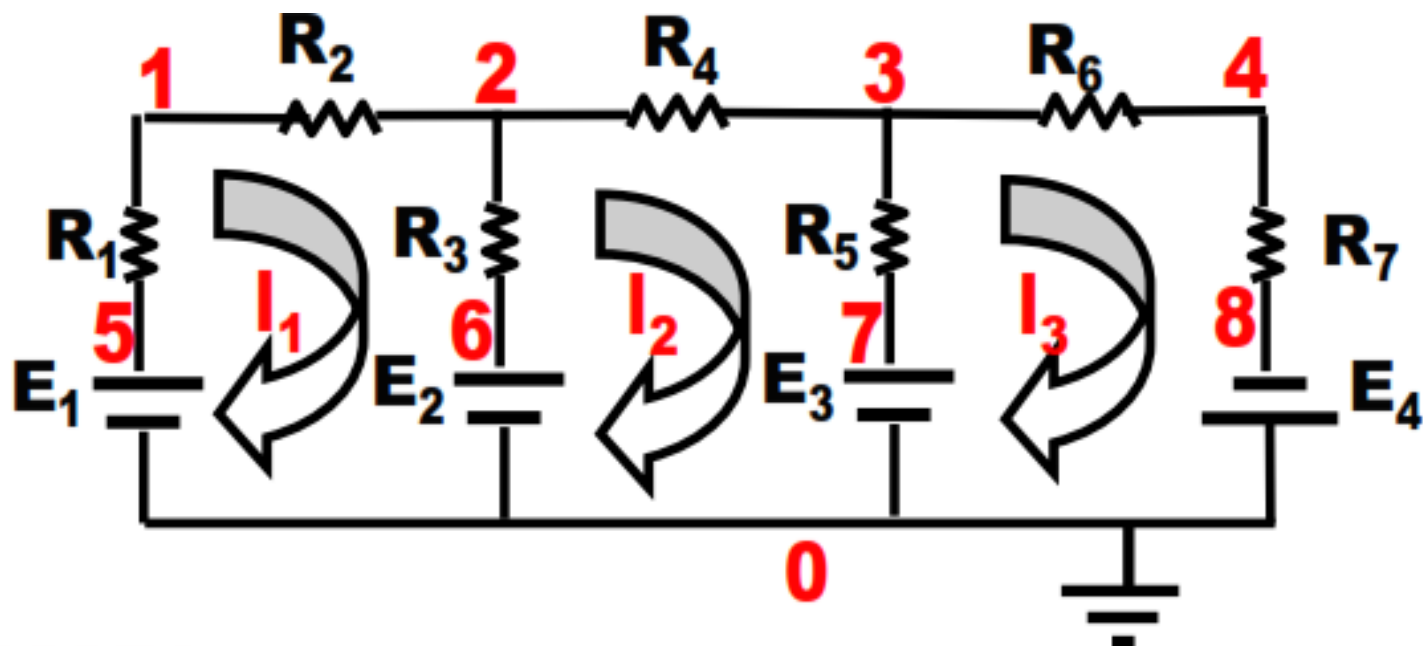


• **Loop 126051 :**

$$V_{12} + V_{26} + V_{60} + V_{05} + V_{51} = 0$$

$$I_1 R_2 + (I_1 - I_2) R_3 + E_2 - E_1 + I_1 R_1 = 0$$
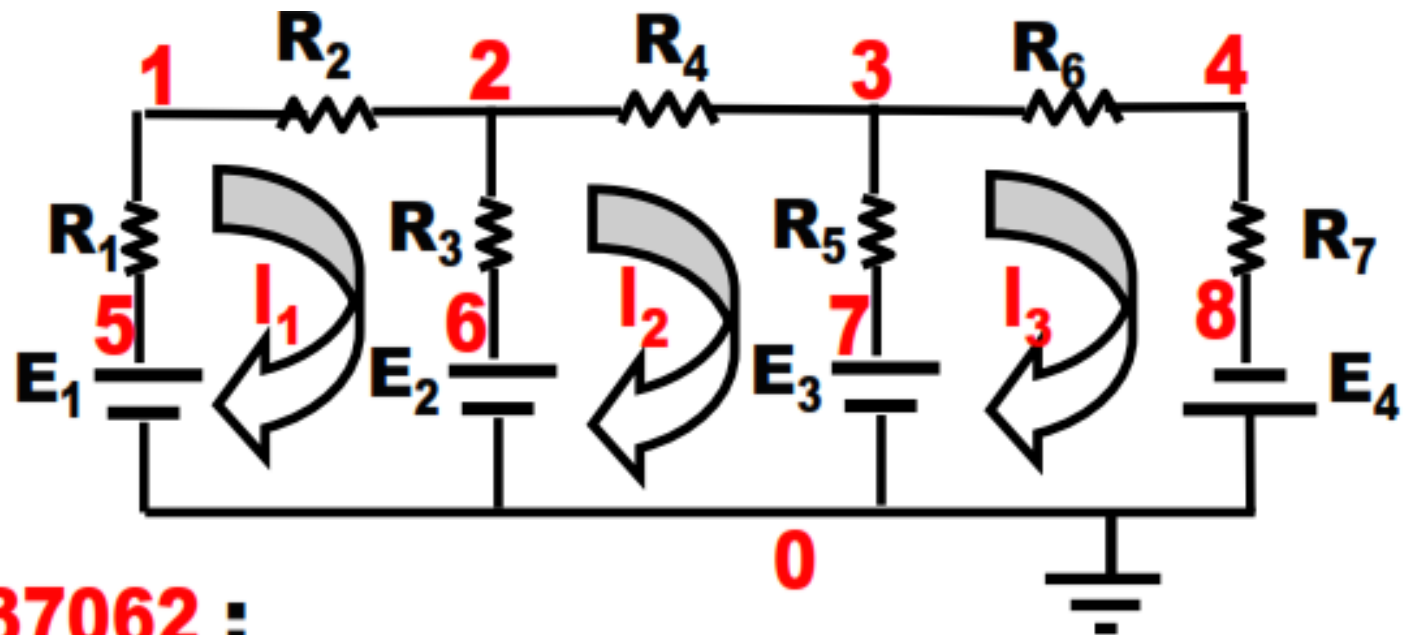
$$I_1 (R_1 + R_2 + R_3) - I_2 R_3 - I_3 (0) = E_1 - E_2 \quad (1)$$




• **Loop 237062 :**

$$V_{23} + V_{37} + V_{70} + V_{06} + V_{62} = 0$$

$$I_2 R_4 + (I_2 - I_3) R_5 + E_3 - E_2 + (I_2 - I_1) R_3 = 0$$
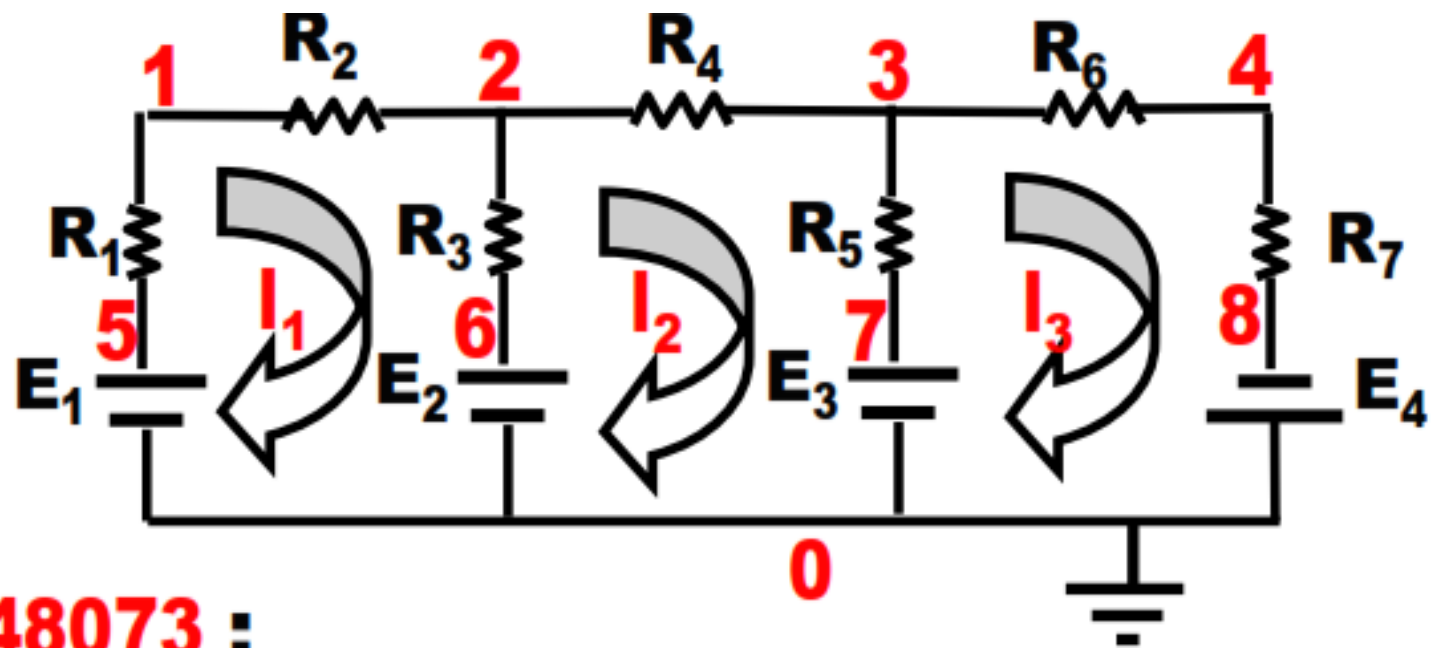
$$-I_1 R_3 + I_2 (R_3 + R_4 + R_5) - I_3 R_5 = E_2 - E_3 \quad (2)$$




• **Loop 348073 :**

$$V_{34} + V_{48} + V_{80} + V_{07} + V_{73} = 0$$

$$I_3 R_6 + I_3 R_7 - E_4 - E_3 + (I_3 - I_2) R_5 = 0$$
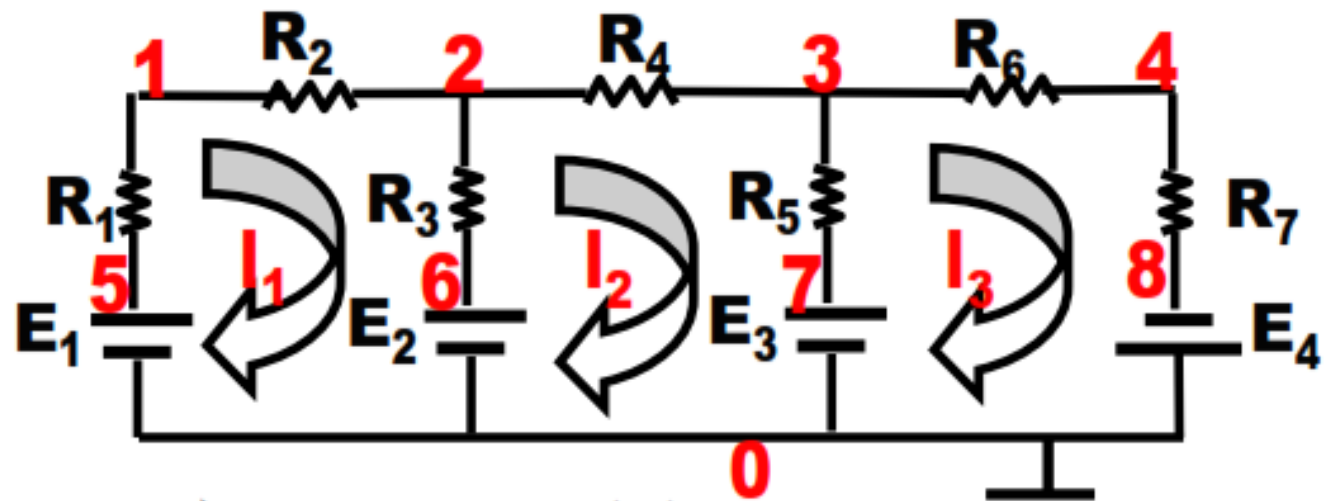
$$I_1 (0) - I_2 R_5 + I_3 (R_5 + R_6 + R_7) = E_3 + E_4 \quad (3)$$



$$I_1(R_1 + R_2 + R_3) - I_2 R_3 - I_3(0) = E_1 - E_2 \quad (1)$$

$$-I_1 R_3 + I_2(R_3 + R_4 + R_5) - I_3 R_5 = E_2 - E_3 \quad (2)$$

$$-I_1(0) - I_2 R_5 + I_3(R_5 + R_6 + R_7) = E_3 + E_4 \quad (3)$$

$$\begin{pmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix}$$

$$\begin{pmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix}$$

$$\begin{pmatrix} \mathbf{R} \end{pmatrix} \begin{pmatrix} \mathbf{I} \end{pmatrix} = \begin{pmatrix} \mathbf{V} \end{pmatrix}$$


$R_{ii} = \sum$ Resistance in loop i $\equiv$ Self resistance of loop i

$R_{ij} = R_{ji} = \sum$ Common Resistance between loops i & j

$V_i = \sum$ voltage sources in loop i

- A voltage source is assumed +ve if it pushes current in the loop direction and –ve otherwise.

98

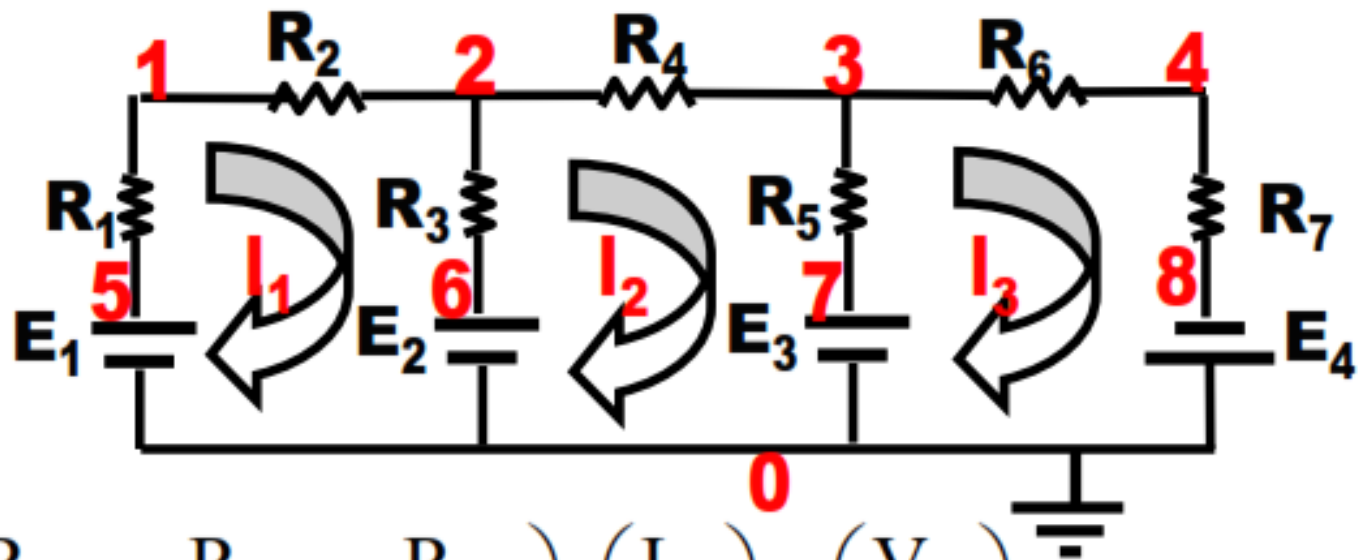

$$\begin{pmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix}$$

$$R_{11} = (R_1 + R_2 + R_3) \quad R_{12} = R_3 \quad R_{13} = 0 \quad V_1 = E_1 - E_2$$

$$R_{21} = R_3 \quad R_{22} = (R_3 + R_4 + R_5) \quad R_{23} = R_5 \quad V_2 = E_2 - E_3$$

$$R_{31} = 0 \quad R_{32} = R_5 \quad R_{33} = R_5 + R_6 + R_7 \quad V_3 = E_3 + E_4$$

$$\begin{pmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta} \quad \text{where, } \Delta = \begin{vmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{12} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{vmatrix}$$

and

$$\Delta_1 = \begin{vmatrix} V_1 & -R_{12} & -R_{13} \\ V_2 & R_{22} & -R_{23} \\ V_3 & -R_{32} & R_{33} \end{vmatrix}$$

$$\begin{pmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{12} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix}$$


$$I_2 = \frac{\Delta_2}{\Delta}$$

$$\Delta_2 = \begin{vmatrix} R_{11} & V_1 & -R_{13} \\ -R_{12} & V_2 & -R_{23} \\ -R_{31} & V_3 & R_{33} \end{vmatrix}$$

$$I_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta_3 = \begin{vmatrix} R_{11} & -R_{12} & V_1 \\ -R_{12} & R_{22} & V_2 \\ -R_{31} & -R_{32} & V_3 \end{vmatrix}$$


Lecture Pause

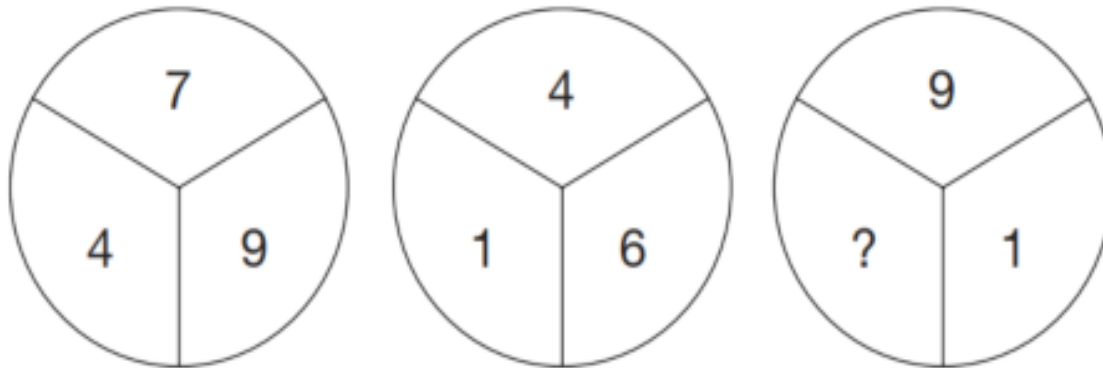

What number should replace the question mark?

Answer:

Lecture Pause

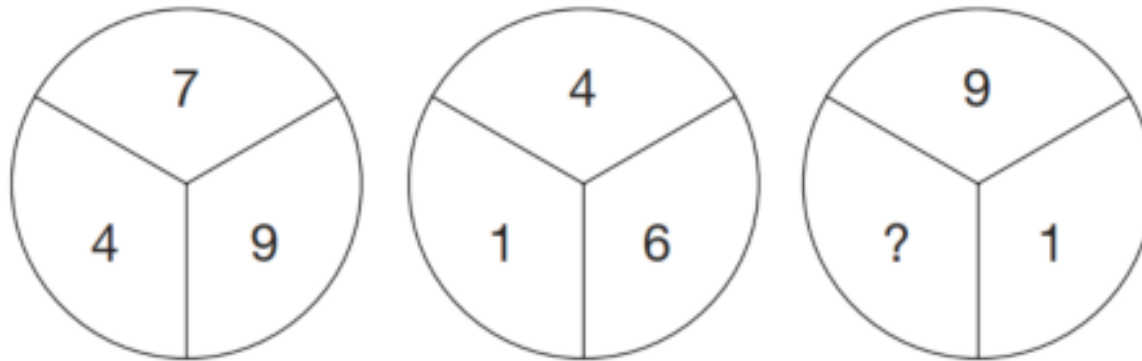

What number should replace the question mark?


Answer:

8


Example

For the shown circuit, **use loop analysis to:**

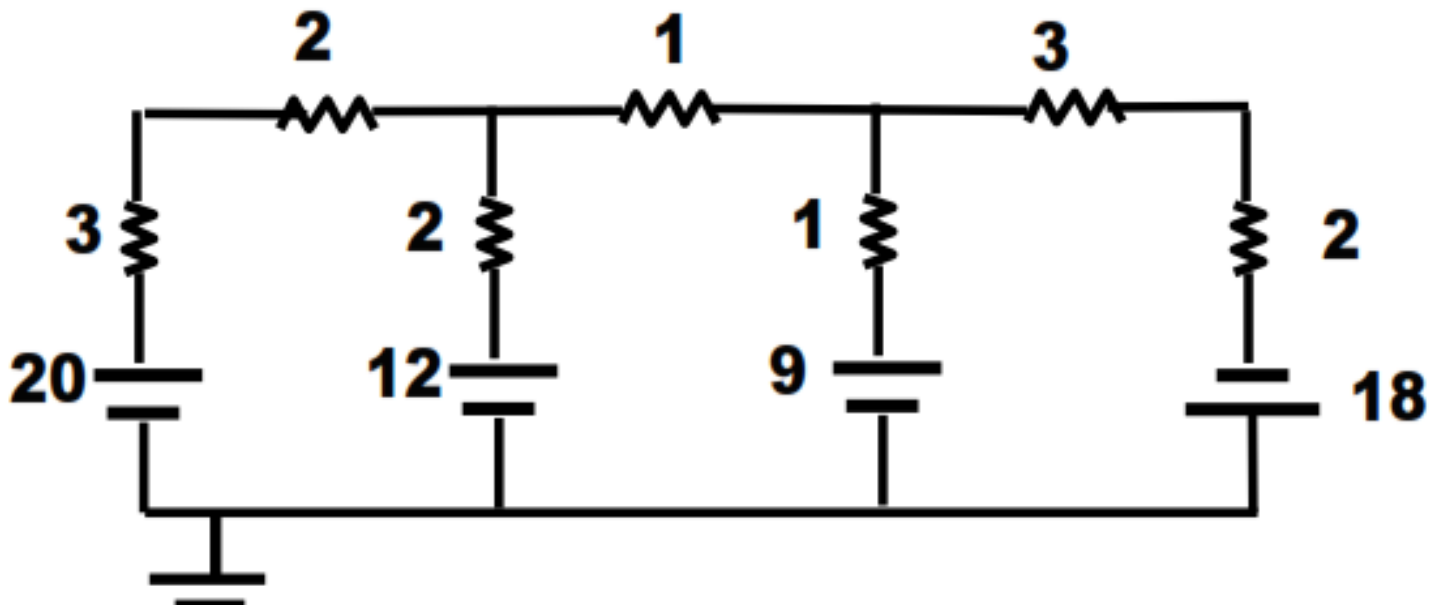
- a) Find the branch currents
- b) Check the power balance of the circuit.



Solution

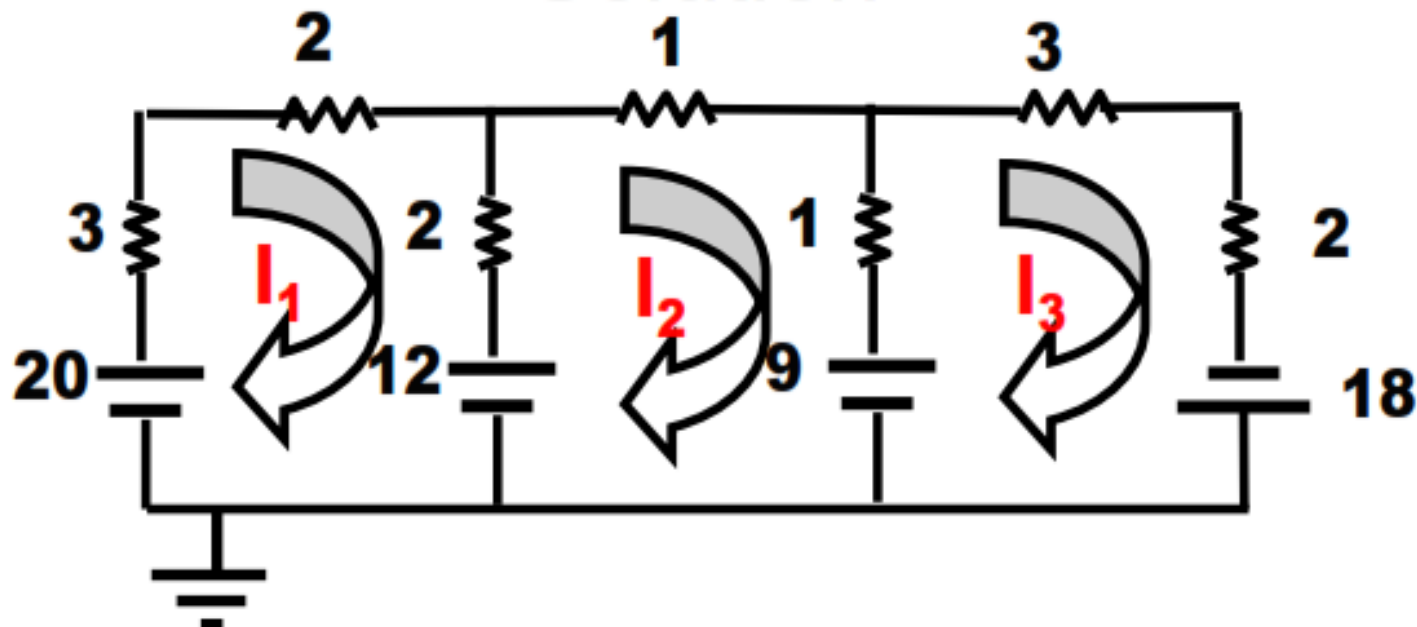

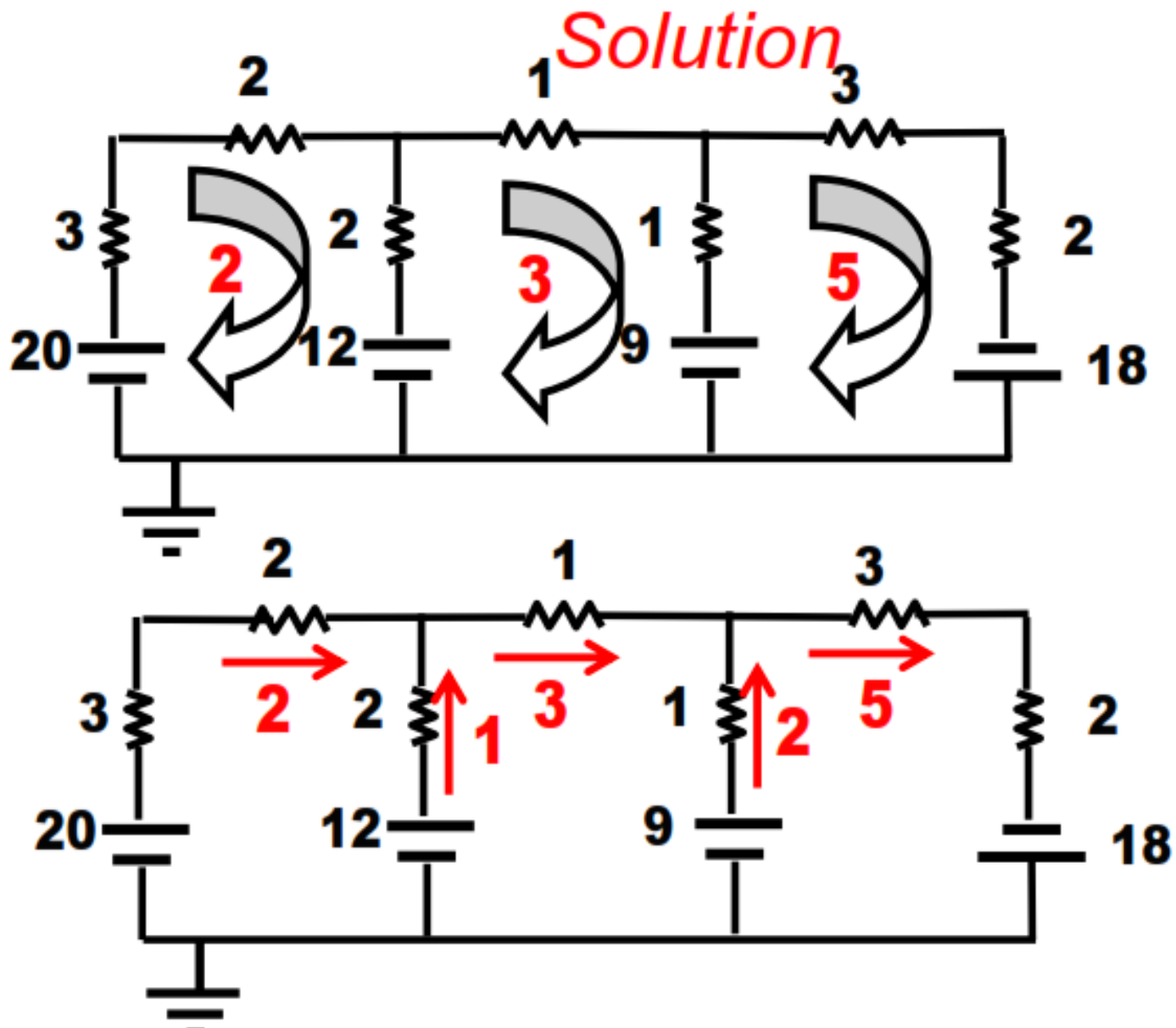
$$\begin{pmatrix} \\ \\ \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} \\ \\ \end{pmatrix} \begin{matrix} I_1 = 2 \text{ mA} \\ I_2 = 3 \text{ mA} \\ I_3 = 5 \text{ mA} \end{matrix}$$



power dissipated by resistors


Resistance	Power (mw) I^2R
R15	
R12	
R26	
R23	
R37	
R34	
R48	
Total	160

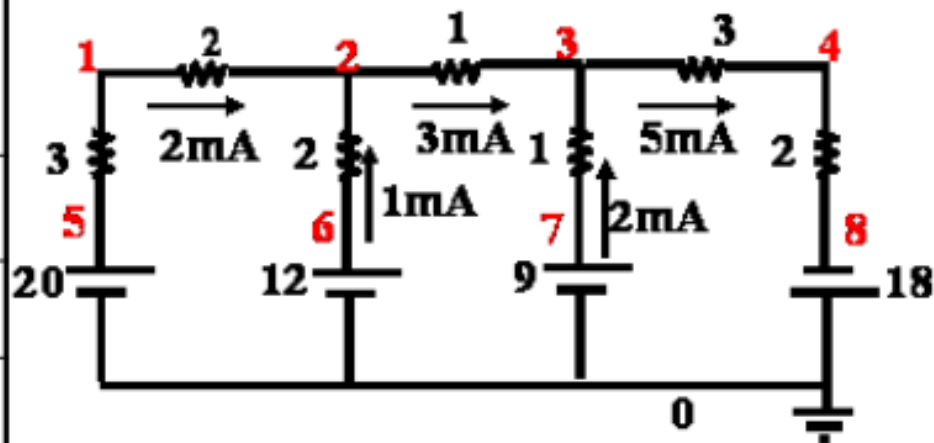

105

power delivered by sources

Source	Power (mw) $E \cdot I$
E20	
E12	
E9	
E18	
Total	160

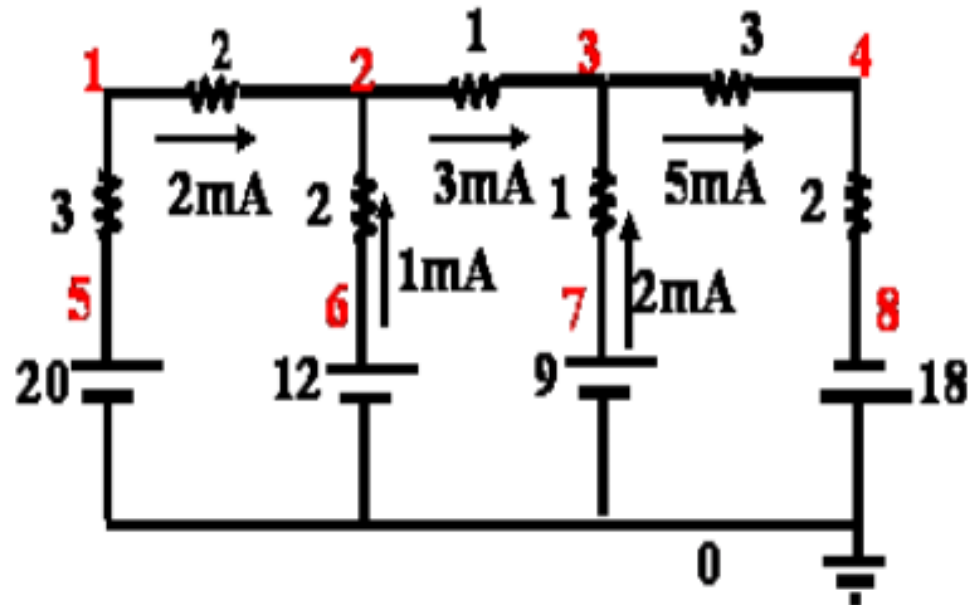

Power balance


$$\Sigma \text{ Power delivered by sources} \\ = \Sigma \text{ Power dissipated by resistors} = 160 \text{ mw}$$


106

Example


For the circuit shown, **use loop analysis** to find:

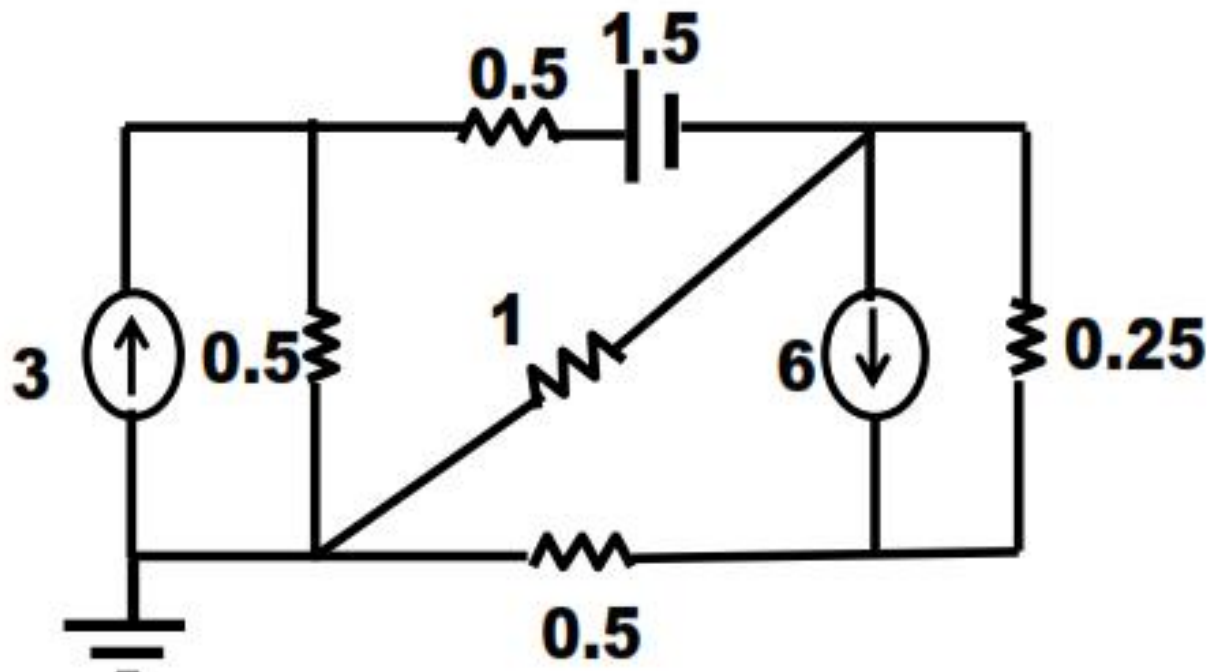- a) The branch currents
- b) Check the power balance



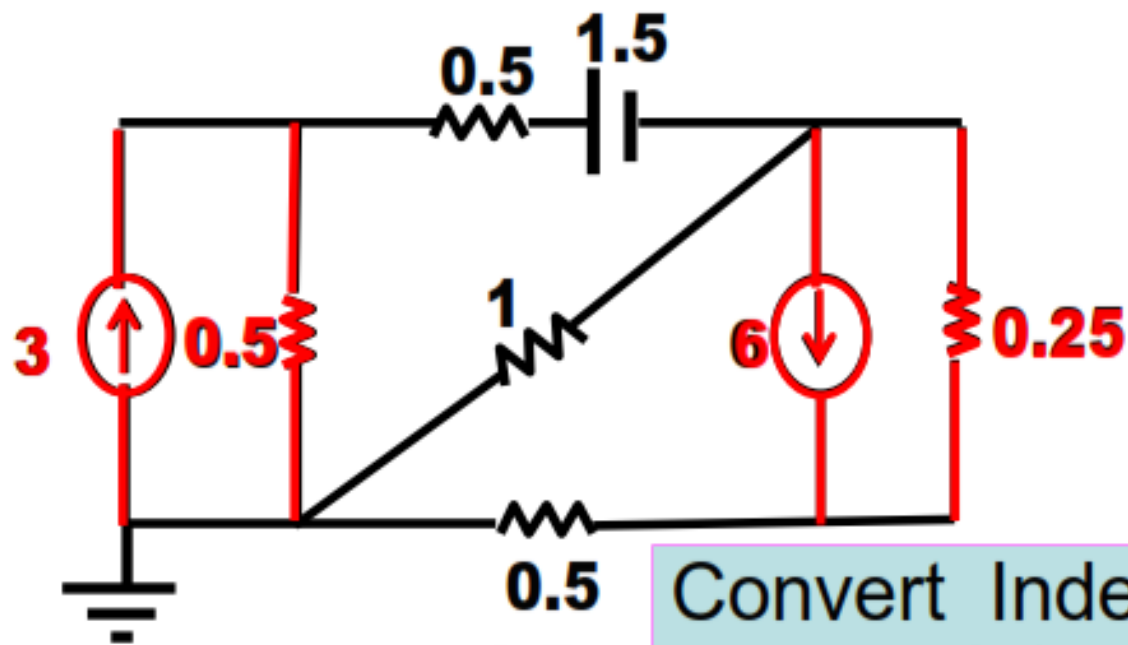

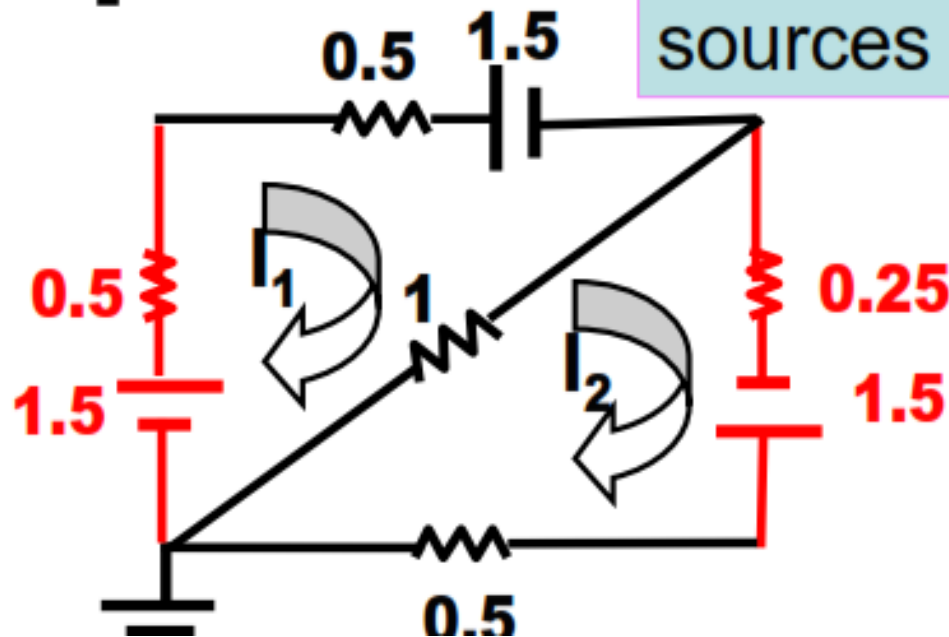
Convert Independent Current sources into voltage sources



$$\begin{pmatrix} R \end{pmatrix} \begin{pmatrix} I \end{pmatrix} = \begin{pmatrix} V \end{pmatrix}$$

108
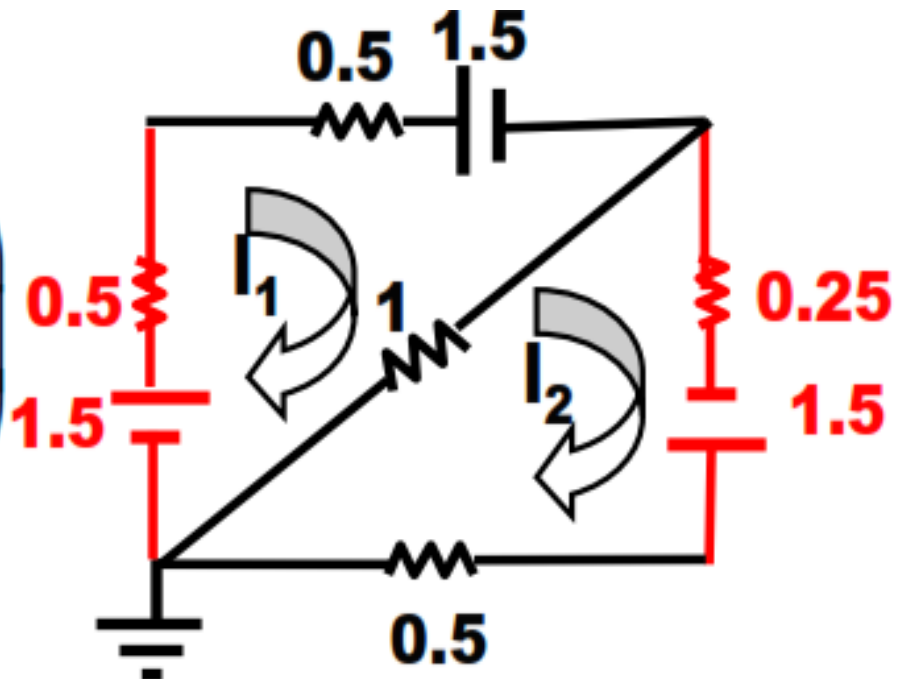
$$\begin{pmatrix} R_{11} & -R_{12} \\ -R_{21} & R_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$



$$\begin{pmatrix} \\ \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} \\ \end{pmatrix}$$


$$I_1 = 0.6\text{ mA}$$

$$I_2 = 1.2\text{ mA}$$

a) Branch Currents

$$I_1 = 0.6 \text{ mA} \quad I_2 = 1.2 \text{ mA}$$

b) Nodal Voltages

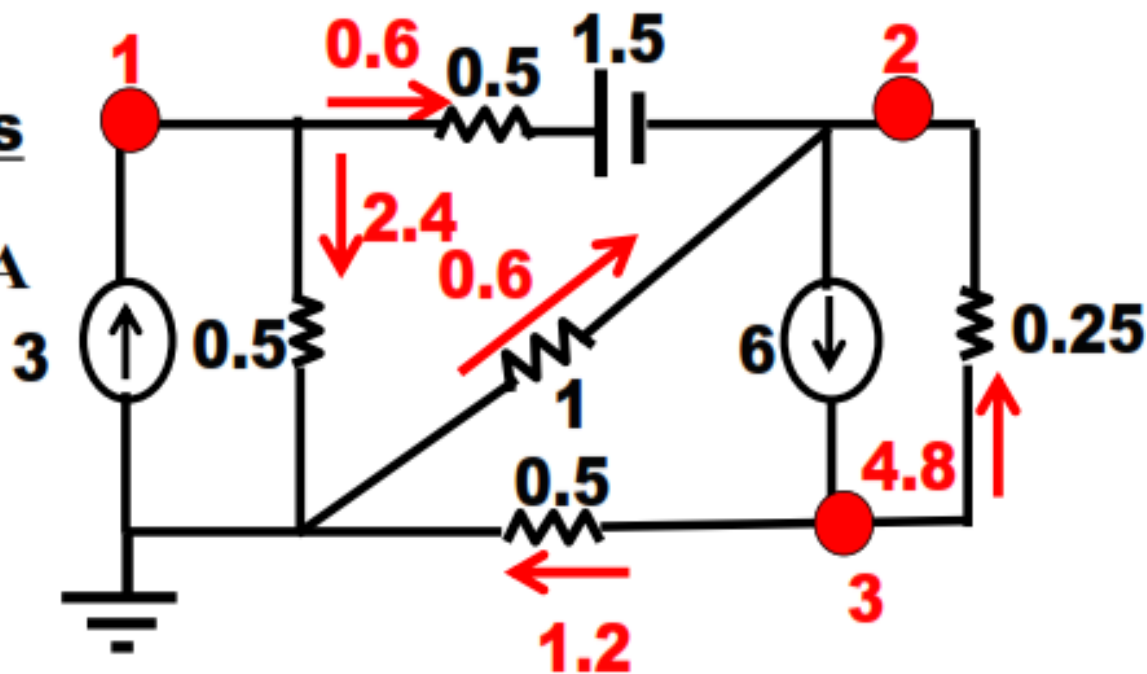


$V_1 =$

$V_2 =$


$V_3 =$

Power dissipated by resistors

R	Dissipated power (mw)
R_{10}	
R_{32}	
R_{12}	
R_{30}	
R_{02}	
Total	9.9

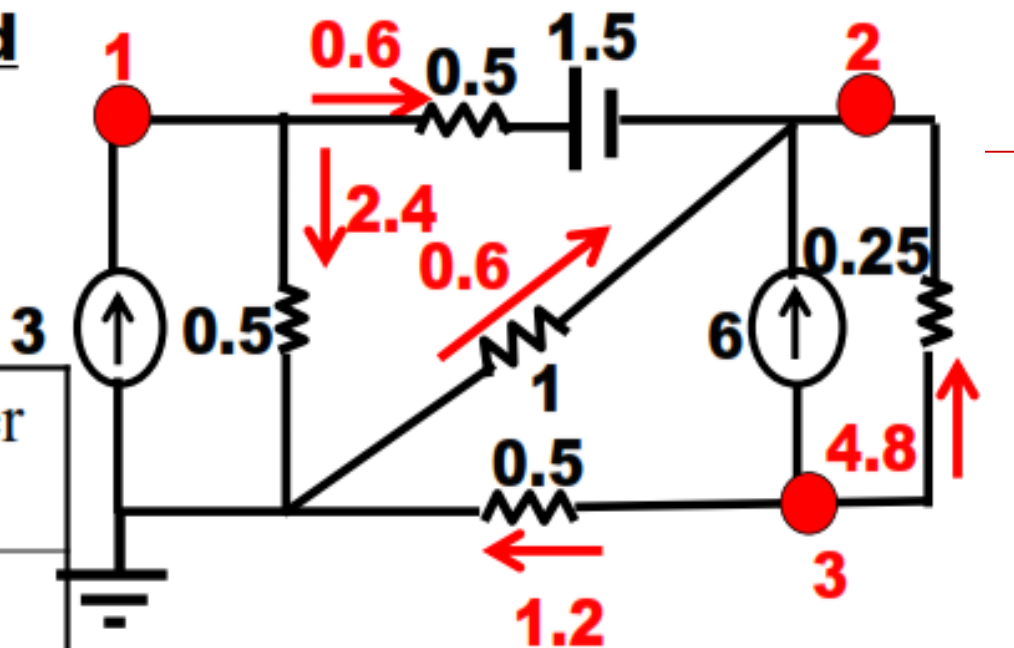

Power supplied by each source

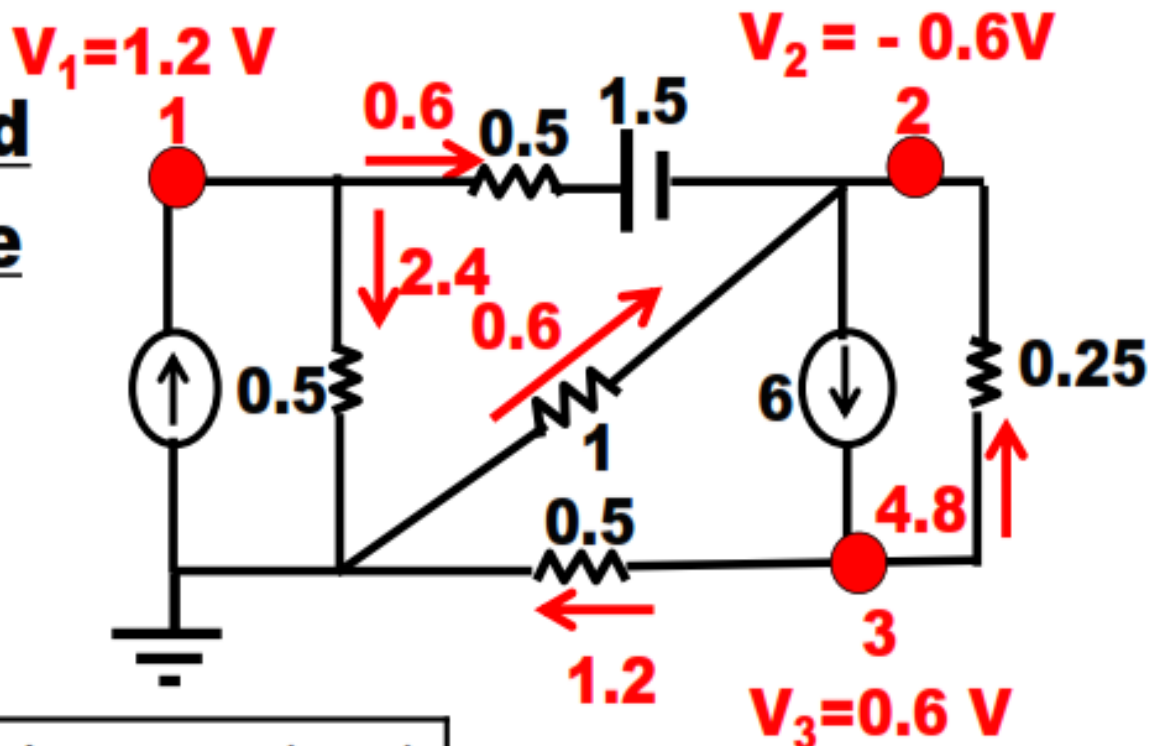

Source	Delivered power (mw)
1.5 V	
3 mA	
6 mA	
Total	9.9 mw

112

Loop Analysis With an Ideal Current Source


CASE 1: When an ideal current source exists in one loop

Write loop equation
for loop 1

• For loop 2,


$$I_2 =$$

$$\therefore I_1 =$$

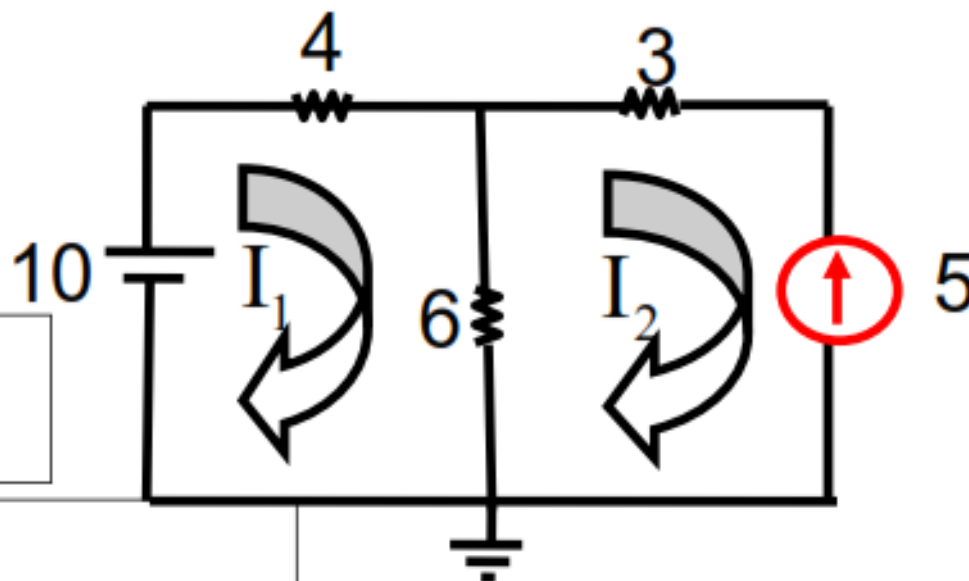

Loop Analysis With Current Source

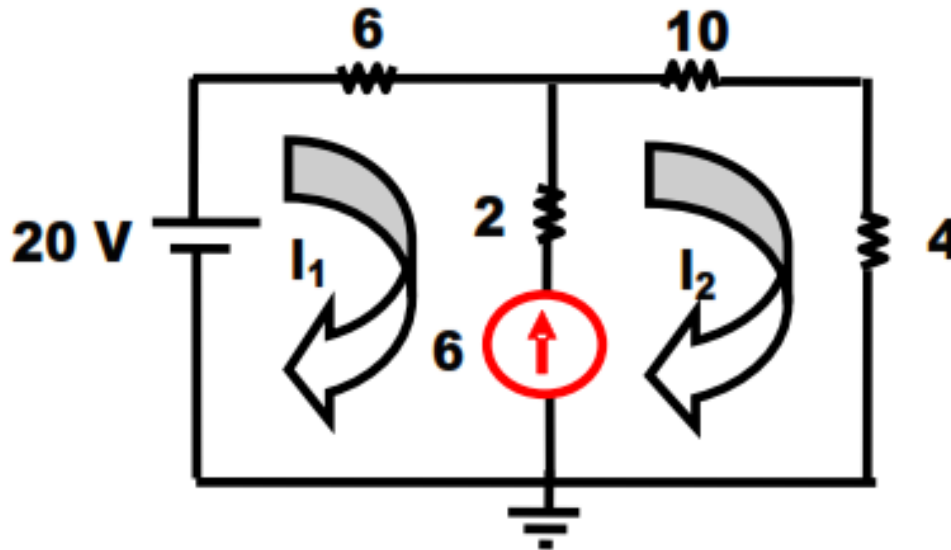CASE 2: When an ideal current source exists between two loops




(1)

114

Loop Analysis With Current Source

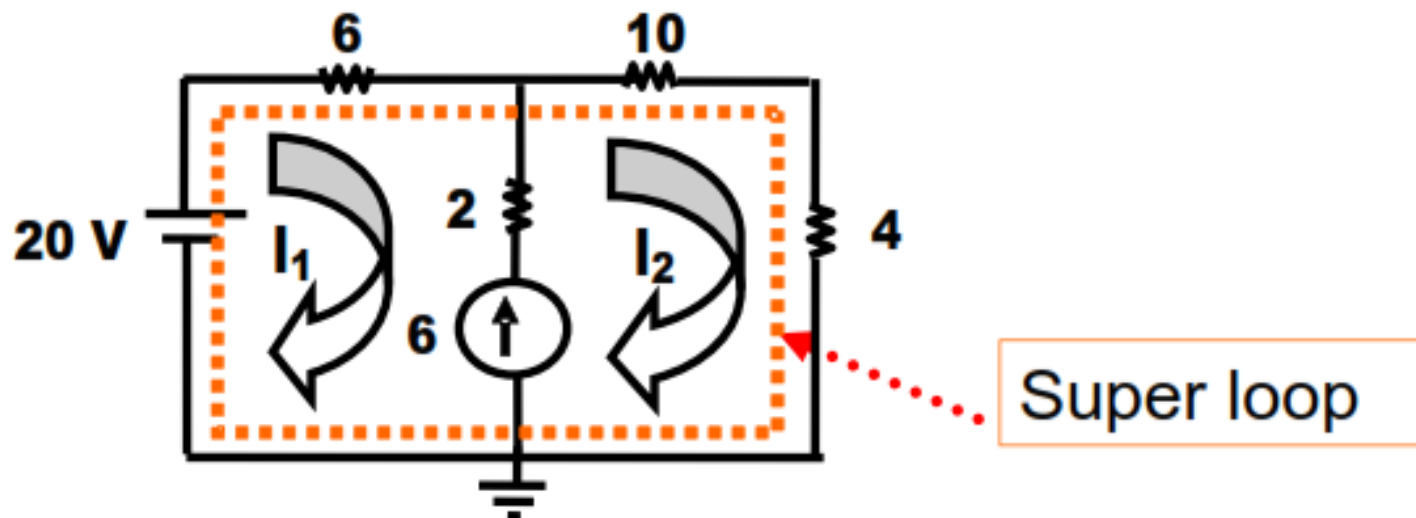
Super loop: A loop consisting of 2 or more loops.



(2)

From (1), (2), $I_1 = -3.2 \text{ mA}$ $I_2 = 2.8 \text{ mA}$

Loop Analysis With Dependent Sources

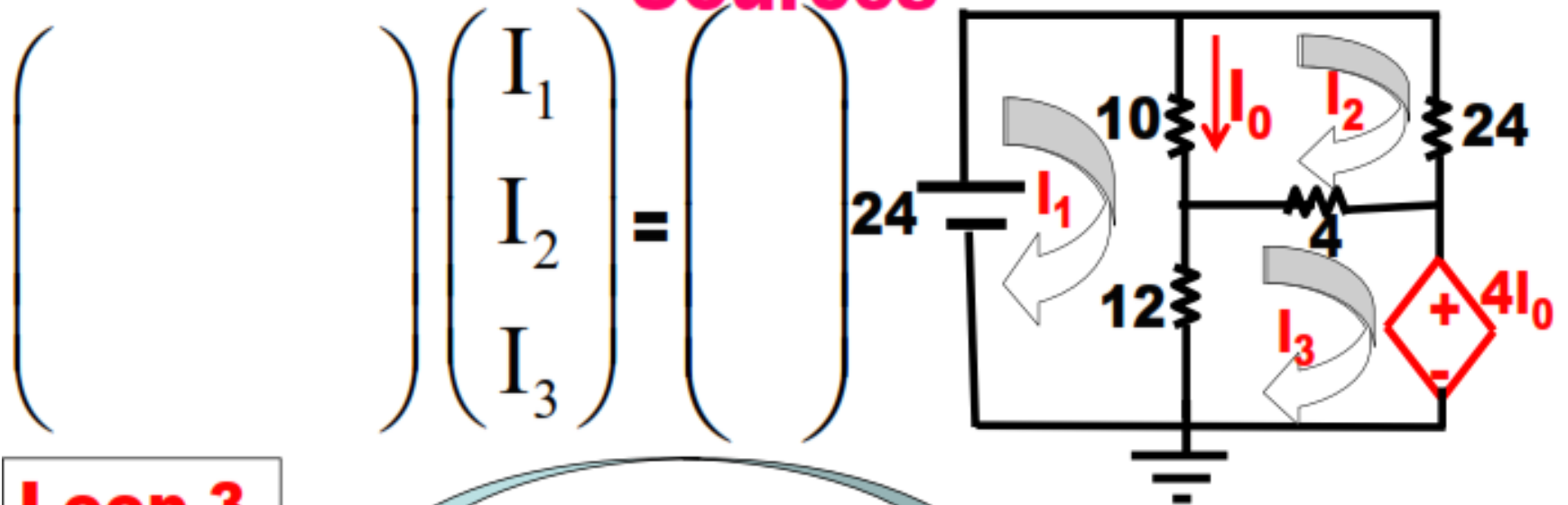


Loop 3

$$I_0 = I_1 - I_2$$

$$I_1 = 2.25 \text{ mA} \quad I_2 = 0.75 \text{ mA} \quad I_3 = 1.5 \text{ mA}$$

Loop Analysis With Dependent Sources

$$\begin{pmatrix} \\ \\ \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} \\ \\ \end{pmatrix}$$

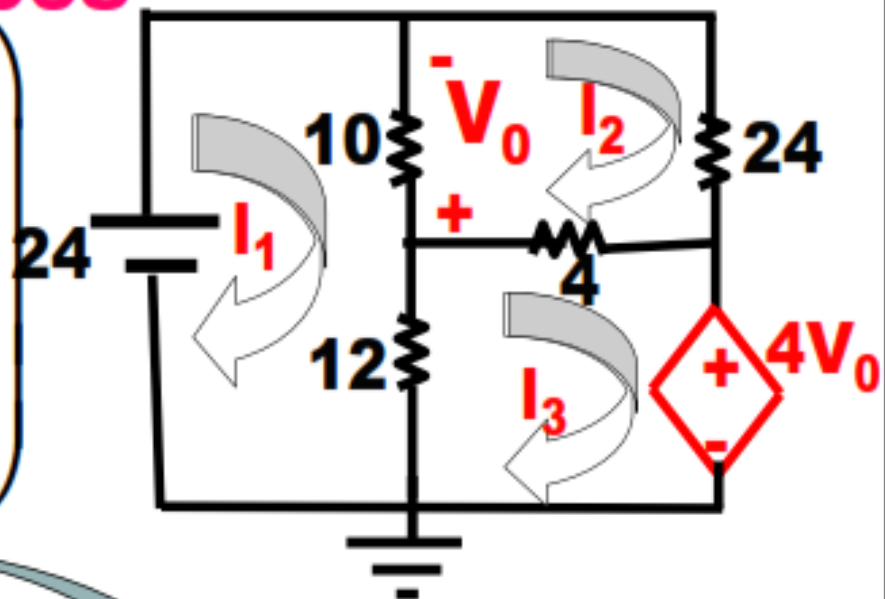


Loop 3

$$V_0 = 10(I_2 - I_1)$$

Loop Analysis With Dependent Sources

$$\begin{pmatrix} \\ \\ \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} \\ \\ \end{pmatrix}$$

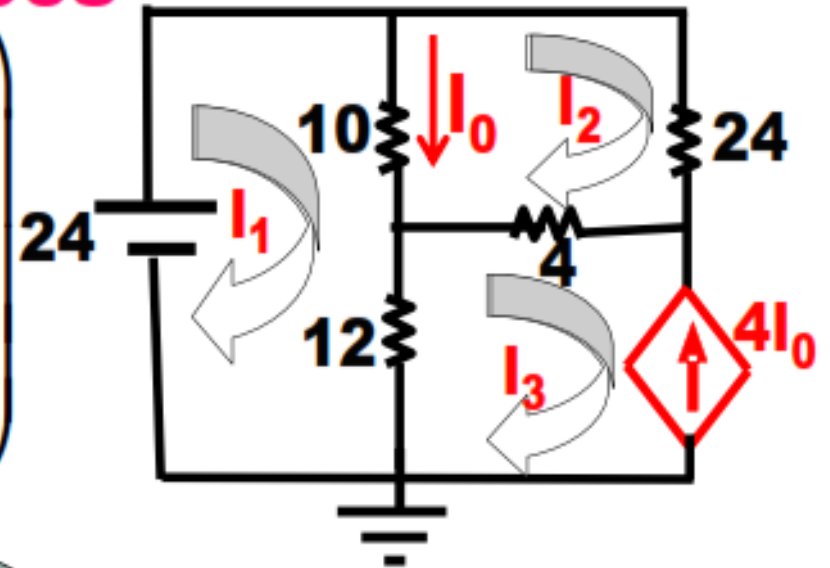

Loop 3


$$I_0 = I_1 - I_2$$

Important Applications Using Loop Analysis

Balanced bridge

- For the bridge to be balanced $I = 0$
- $V_2 = V_4$ Hence,
- $V_{12} = V_{14}$
- $I_{12} R_1 = I_{14} R_4$ (1)
- $V_{23} = V_{43}$
- $I_{23} R_2 = I_{43} R_3$ (2)
- Since $I = 0$, $I_{12} = I_{23}$
& $I_{14} = I_{43}$
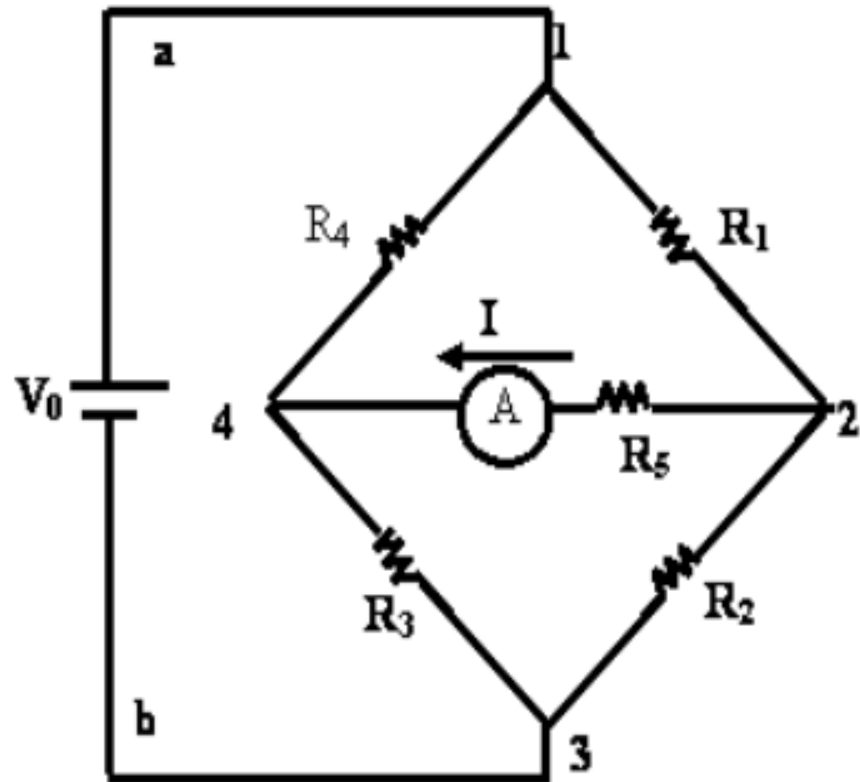
$$\frac{(1)}{(2)} \Rightarrow \frac{R_1}{R_2} = \frac{R_4}{R_3} \quad \text{Hence, } R_1 R_3 = R_2 R_4$$




119

Input Resistance

$$R_i = \frac{V_i}{I_i} \Big|_{\text{all circuit sources are cancelled}}$$


- Voltage sources are SC & current sources are OC

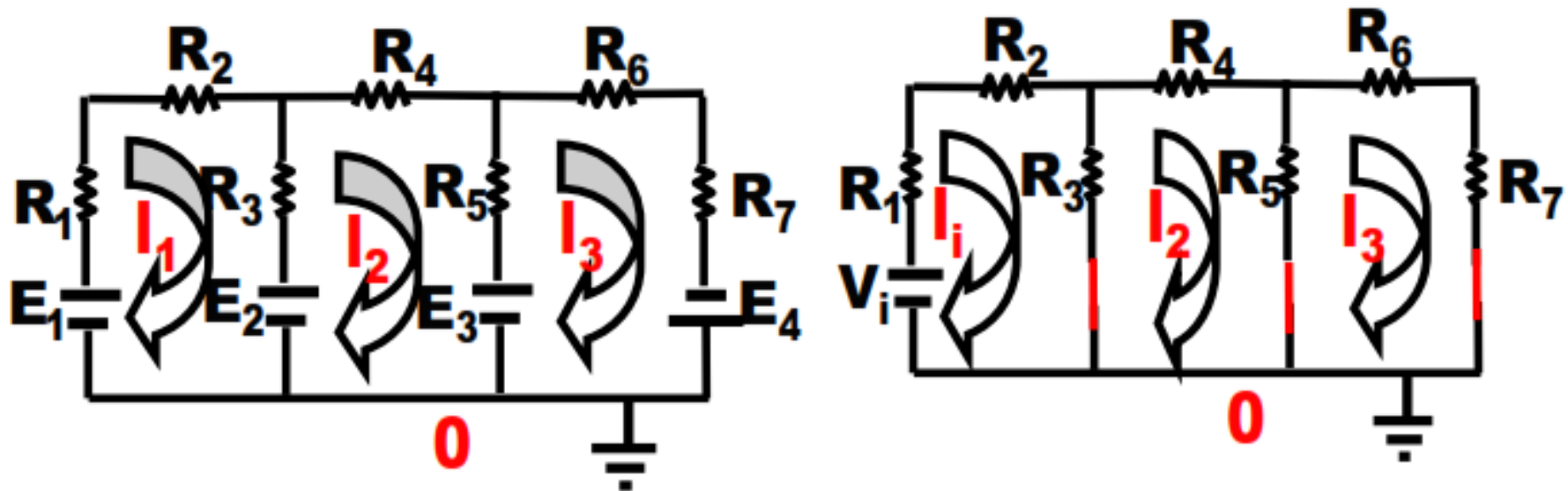1- Resistance Seen by a source in one Loop (e.g. E_1)



Input Resistance

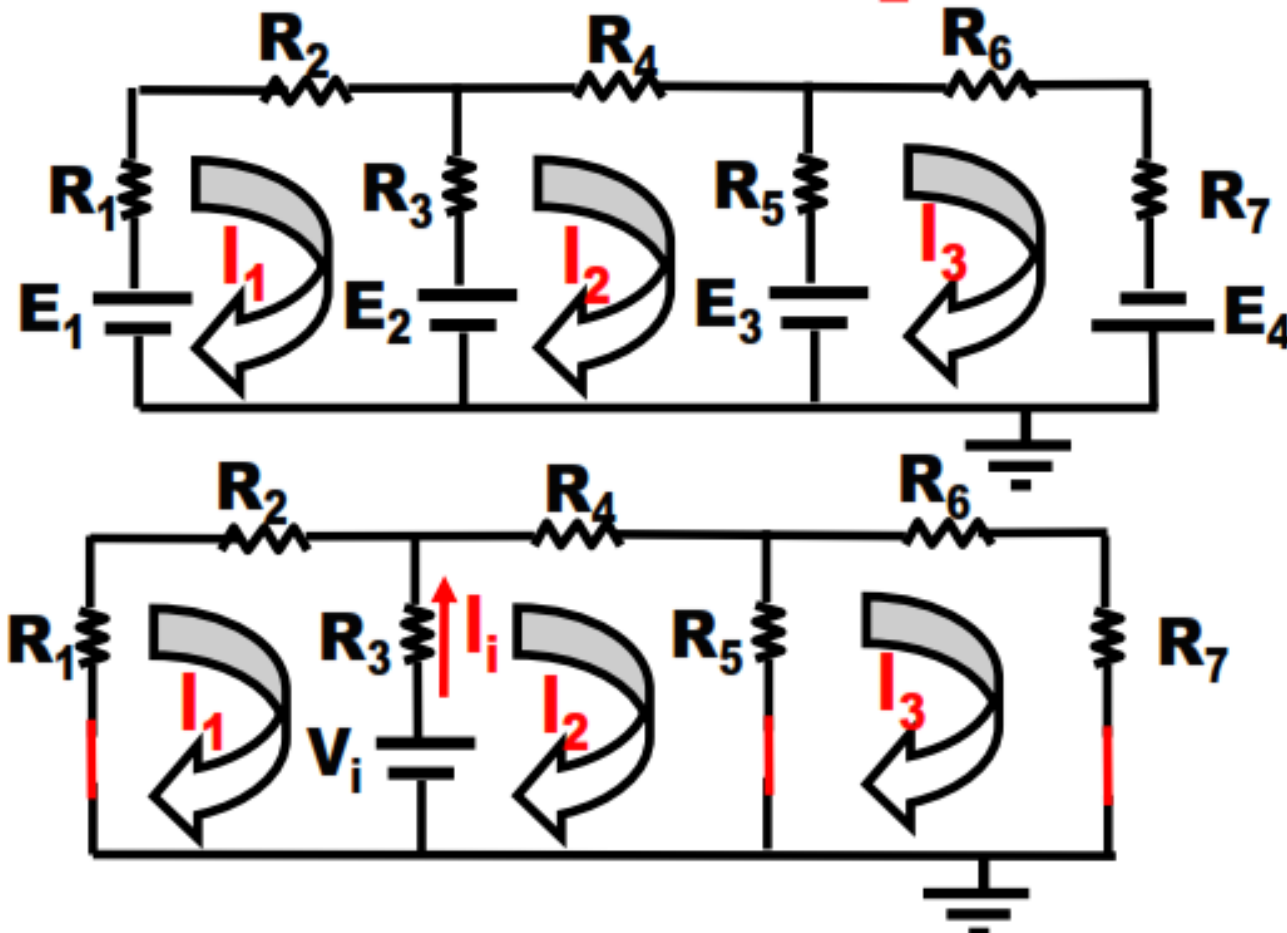2- Resistance Seen by a source common between two Loops (e.g. E_2)



4. Nodal Analysis


Method 4 Nodal Analysis

- Steps of solution:
 - 1- Convert independent voltage sources into equivalent current sources
 - 2- Identify the number of nodes (N) of the circuit
 - 3- Write an expression for the KCL at $N-1$ nodes (Exclude the ground node).
 - 4- Solve the resultant system of algebraic equations to find the node voltages.

100, 1, 91.5, 9.5, 83, 18, 74.5, 26.5, ?, ?

What two numbers come next?

Answer:

 

100, 1, 91.5, 9.5, 83, 18, 74.5, 26.5, ?, ?

What two numbers come next?


Answer:



66, 35

Explanation:


There are two interwoven sequences. Start at 100 and deduct 8.5. Start at 1 and add 8.5.

Example

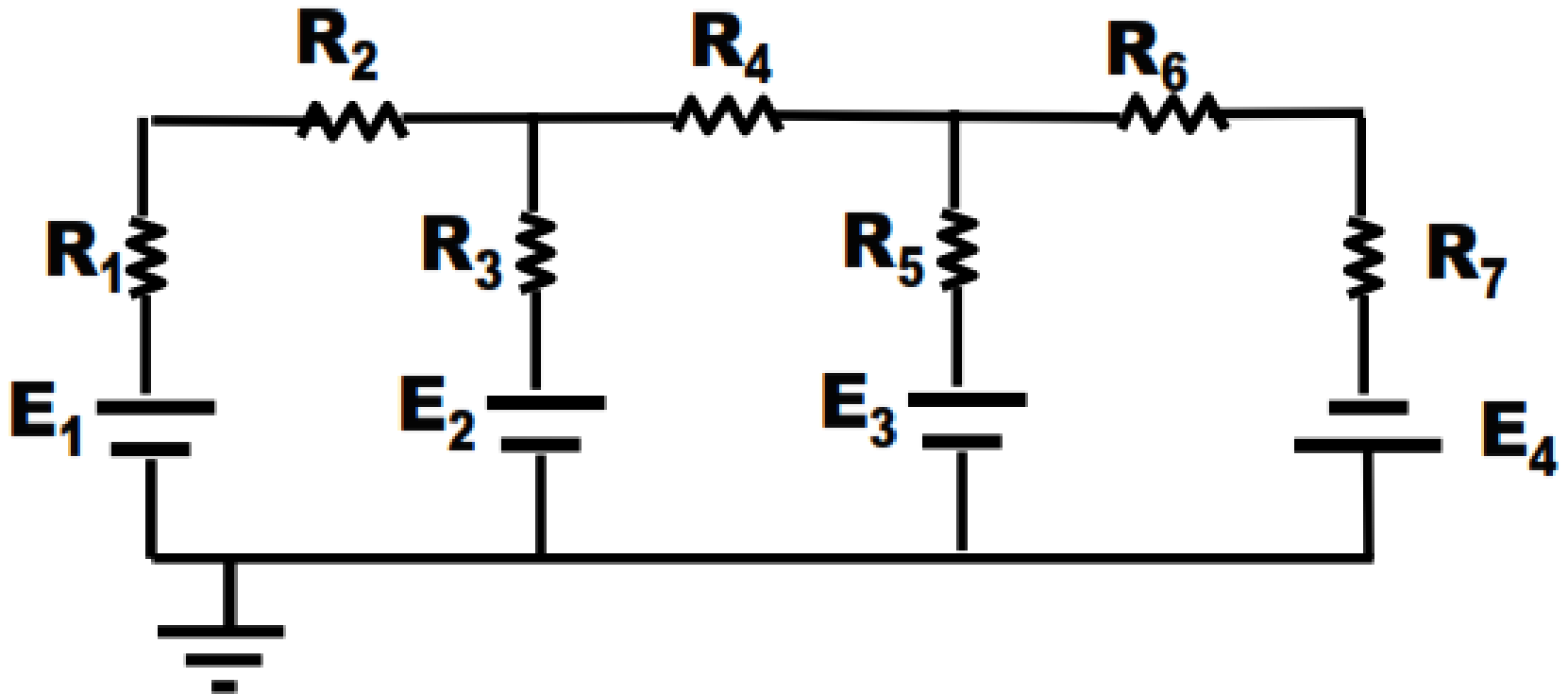


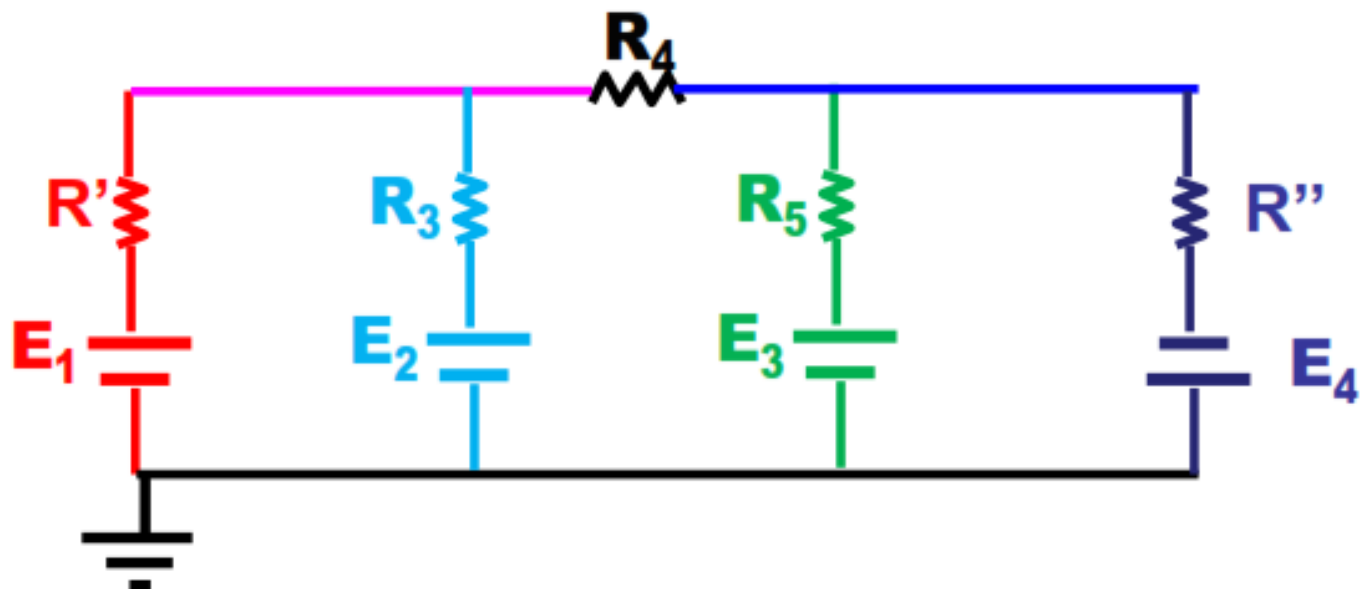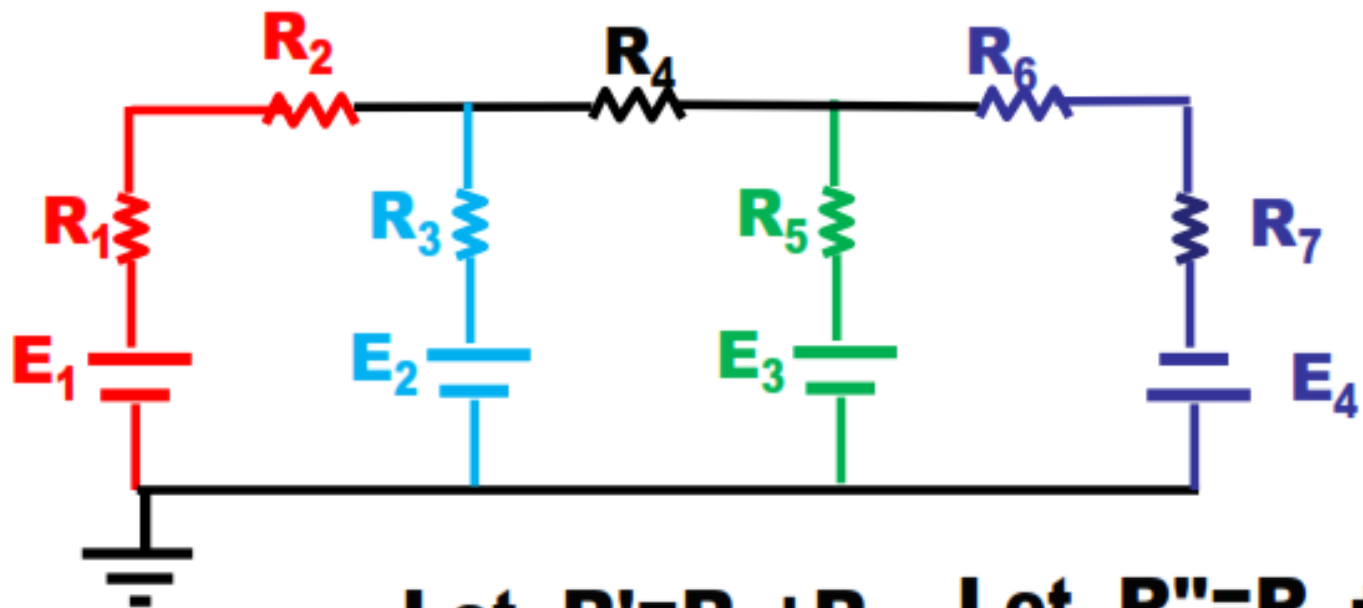

137

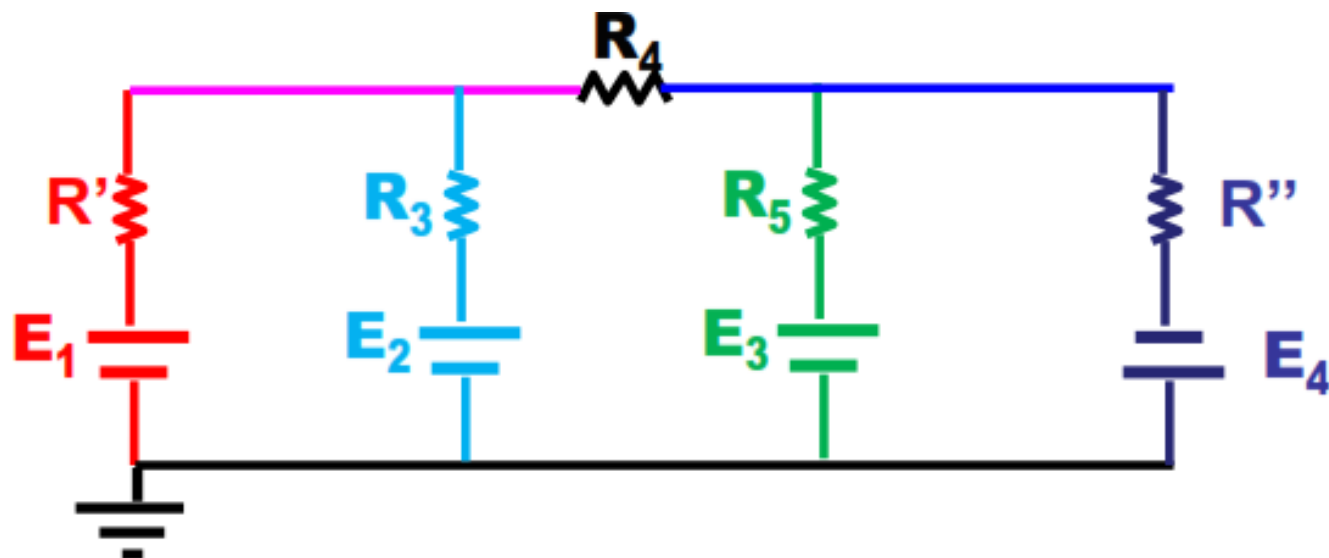


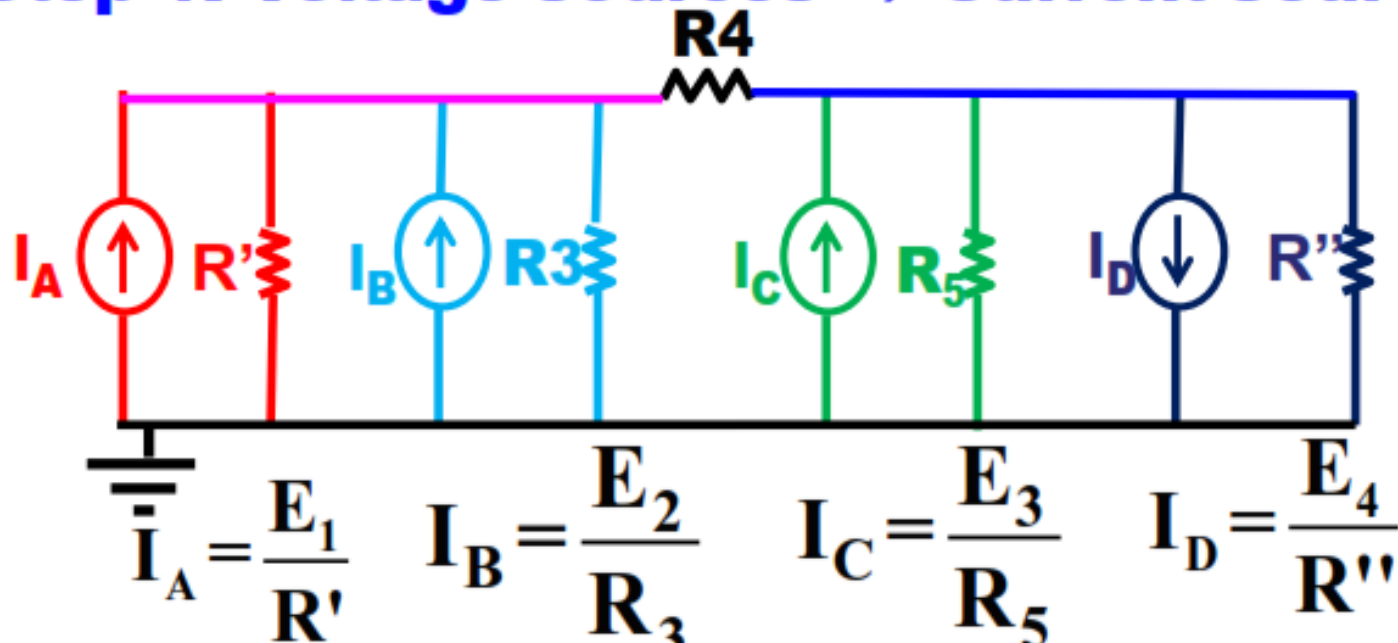Step 1: Voltage sources $\Rightarrow$ Current sources




- **Step 2 : N=3**

- **Step 3: KCL at each node** $\sum \mathbf{I}_{\text{out}} = \mathbf{0}$

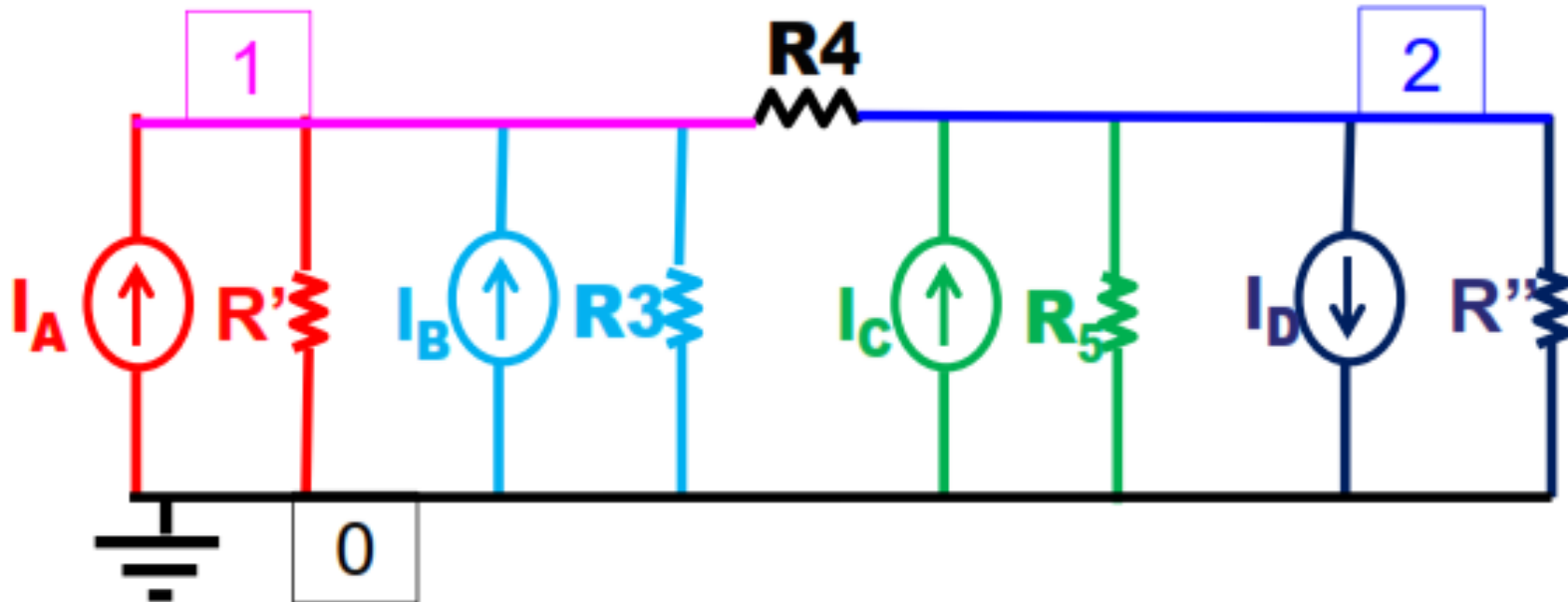

Node 1
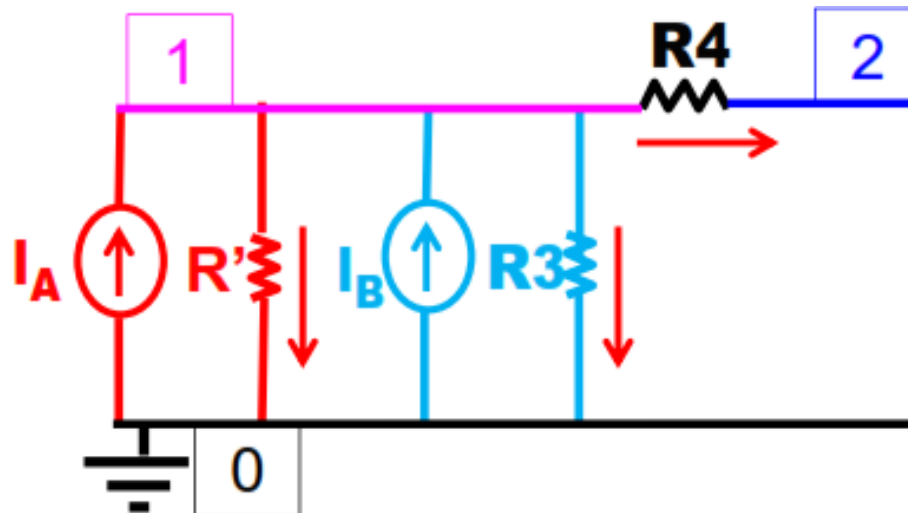
$$\sum \mathbf{I}_{\text{out}} = \mathbf{0}$$



$$\mathbf{I}_{R'} + \mathbf{I}_{R3} + \mathbf{I}_{R4} - \mathbf{I}_A - \mathbf{I}_B = \mathbf{0}$$

$$\frac{\mathbf{V}_1}{\mathbf{R}'} + \frac{\mathbf{V}_1}{\mathbf{R}_3} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{\mathbf{R}_4} - \mathbf{I}_A - \mathbf{I}_B = \mathbf{0}$$


$$\mathbf{G}' \mathbf{V}_1 + \mathbf{G}_3 \mathbf{V}_1 + \mathbf{G}_4 (\mathbf{V}_1 - \mathbf{V}_2) - \mathbf{I}_A - \mathbf{I}_B = \mathbf{0}$$

$$(\mathbf{G}' + \mathbf{G}_3 + \mathbf{G}_4) \mathbf{V}_1 - \mathbf{G}_4 \mathbf{V}_2 = \mathbf{I}_A + \mathbf{I}_B \quad (1)$$

140

Node 2

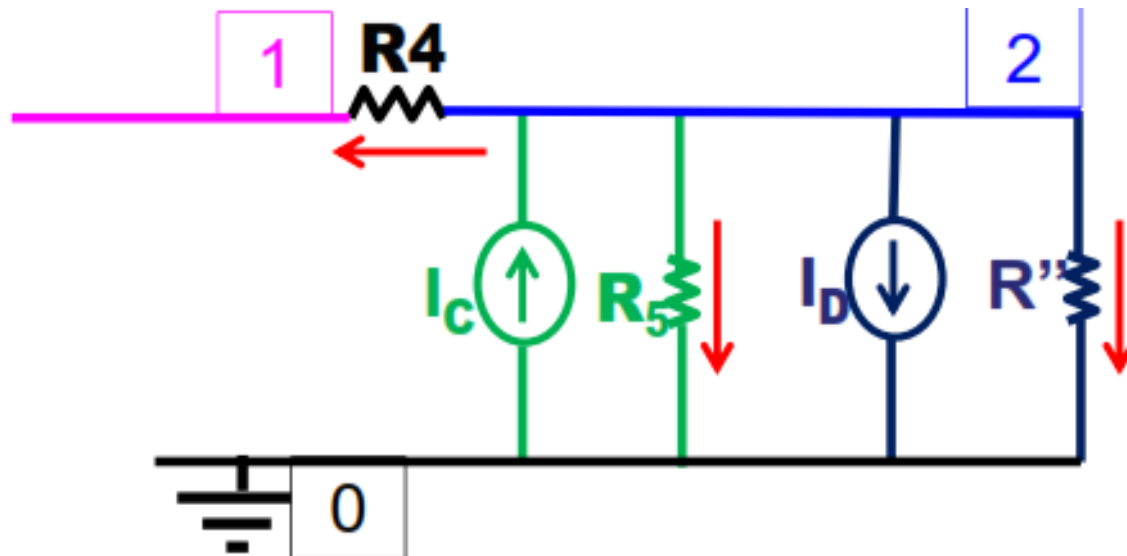
$$\sum \mathbf{I}_{\text{out}} = \mathbf{0}$$



$$\mathbf{I}_{R4} + \mathbf{I}_{R5} + \mathbf{I}_{R''} - \mathbf{I}_C + \mathbf{I}_D = 0$$

$$\mathbf{G}_4 (\mathbf{V}_2 - \mathbf{V}_1) + \mathbf{G}_5 \mathbf{V}_2 + \mathbf{G}'' \mathbf{V}_2 = \mathbf{I}_C - \mathbf{I}_D$$
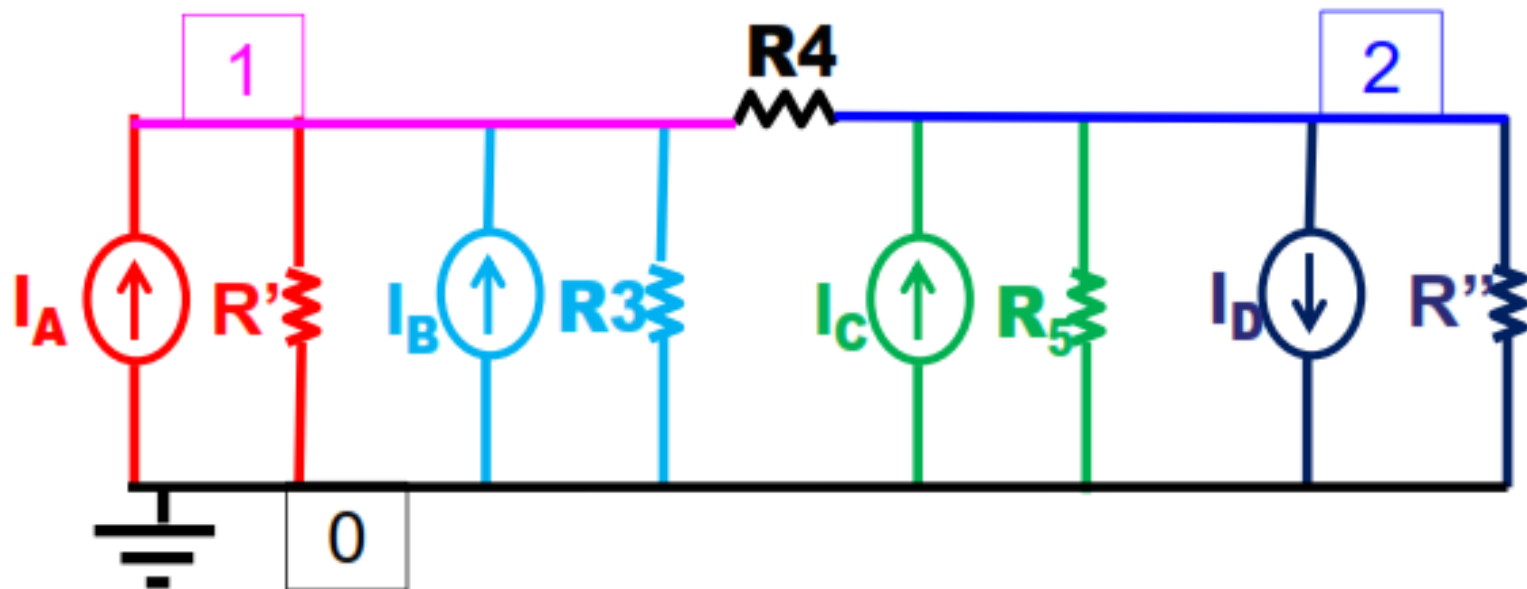
$$-\mathbf{G}_4 \mathbf{V}_1 + (\mathbf{G}_4 + \mathbf{G}_5 + \mathbf{G}'') \mathbf{V}_2 = \mathbf{I}_C - \mathbf{I}_D \quad (2)$$



- Equations**

$$(G' + G_3 + G_4) V_1 - G_4 V_2 = I_A + I_B \quad (1)$$

$$-G_4 V_1 + (G_4 + G_5 + G'') V_2 = I_C - I_D \quad (2)$$

$$\begin{pmatrix} G_{11} & -G_{12} \\ -G_{21} & G_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$G_{ii} = \sum \text{Conductance of node } i \equiv \text{Self conductance of node } i$

$G_{ij} = G_{ji} = \sum \text{Common conductances between nodes } i \& j$

$I_i = \sum \text{Currents sources at node } i$

A current source is assumed +ve if it pushes current toward the node direction and –ve otherwise.


143

$$\begin{pmatrix} \mathbf{G} \end{pmatrix} \begin{pmatrix} \mathbf{V} \end{pmatrix} = \begin{pmatrix} \mathbf{I} \end{pmatrix}$$



- $\mathbf{G} \equiv$ Conductance Matrix
- $\mathbf{V} \equiv$ Unknown nodal voltages
- $\mathbf{I} \equiv$ Current Vector

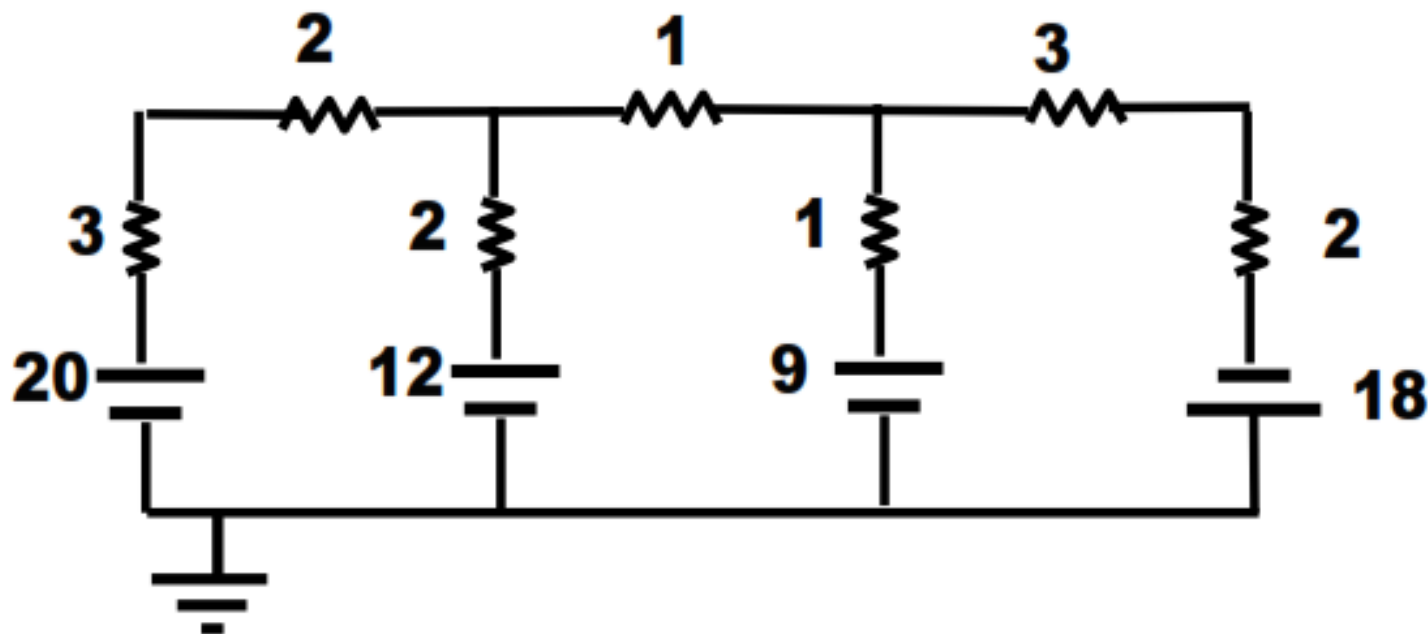
Example

For the shown circuit, **Use node method** to find the nodal voltages & the branch currents



Solution

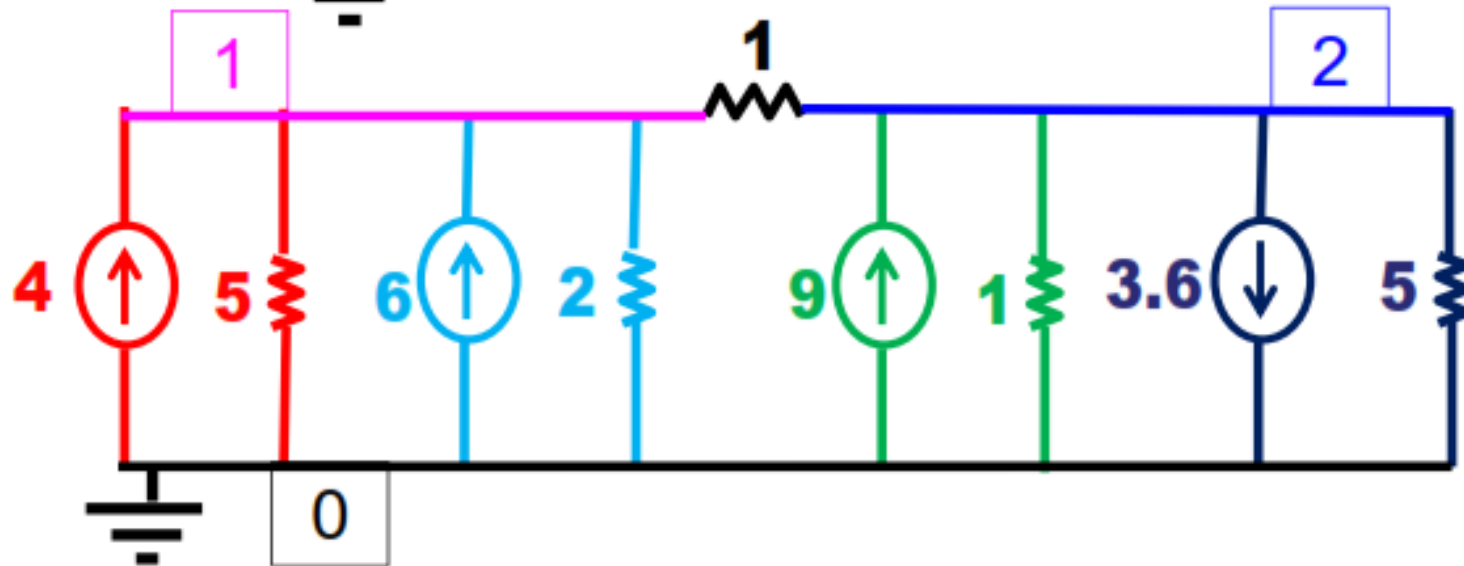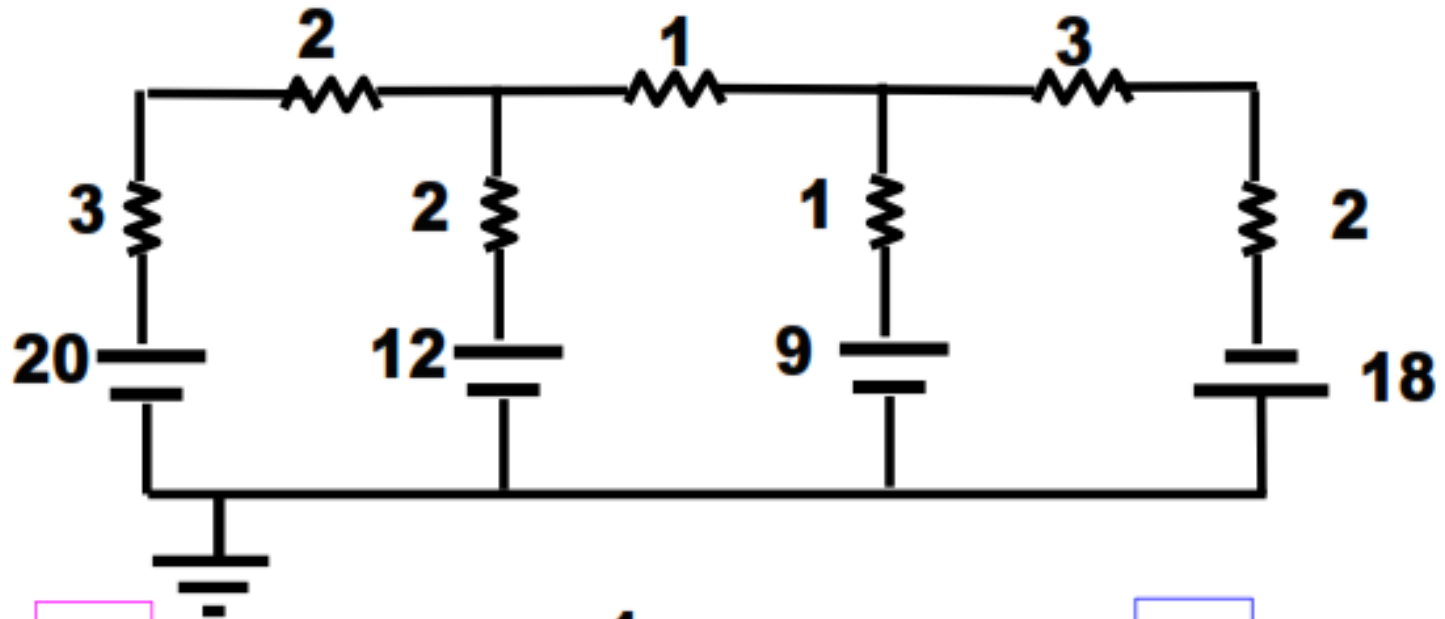

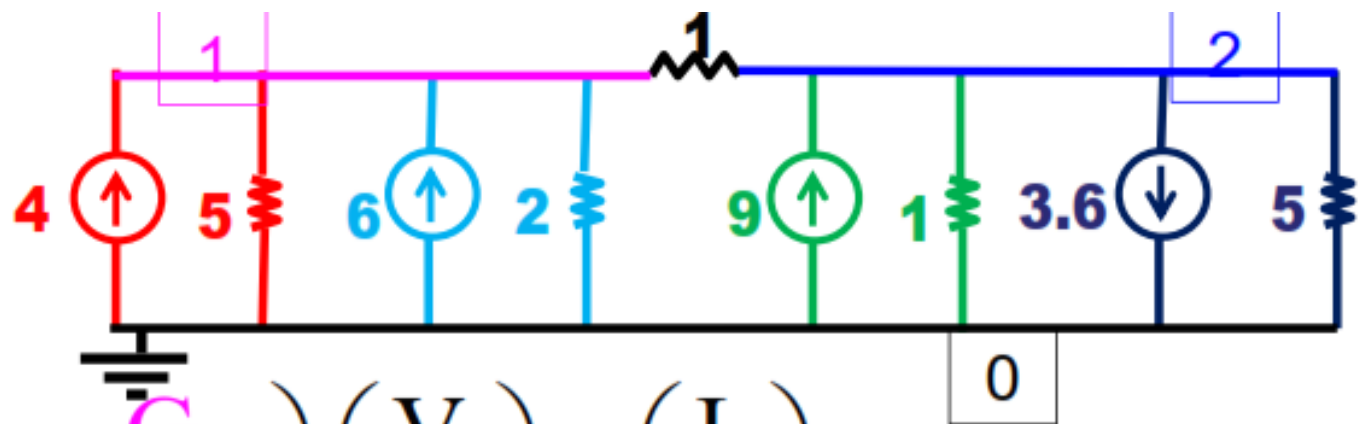

$$\begin{pmatrix} G_{11} & -G_{12} \\ -G_{21} & G_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$


$$\begin{pmatrix} \phantom{G_{11}} & \phantom{-G_{12}} \\ \phantom{-G_{21}} & \phantom{G_{22}} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} \\ \end{pmatrix}$$

$$\begin{pmatrix} \phantom{G_{11}} & \phantom{-G_{12}} \\ \phantom{-G_{21}} & \phantom{G_{22}} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} \\ \end{pmatrix}$$

$$V_1 = 10 \text{ V}$$

$$V_2 = 7 \text{ V}$$

150

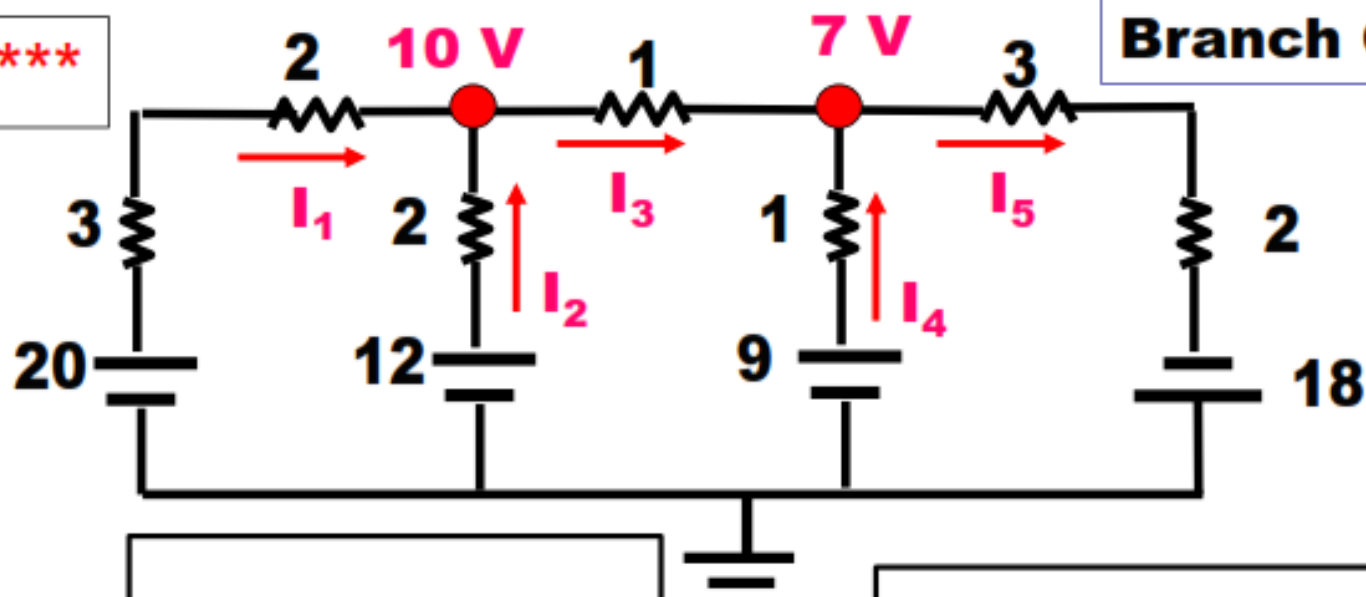

Branch Currents

$I_1 =$

$I_2 =$

$I_3 =$

Check KCL at node 1

$I_4 =$


$I_5 =$

Check KCL at node 2

151

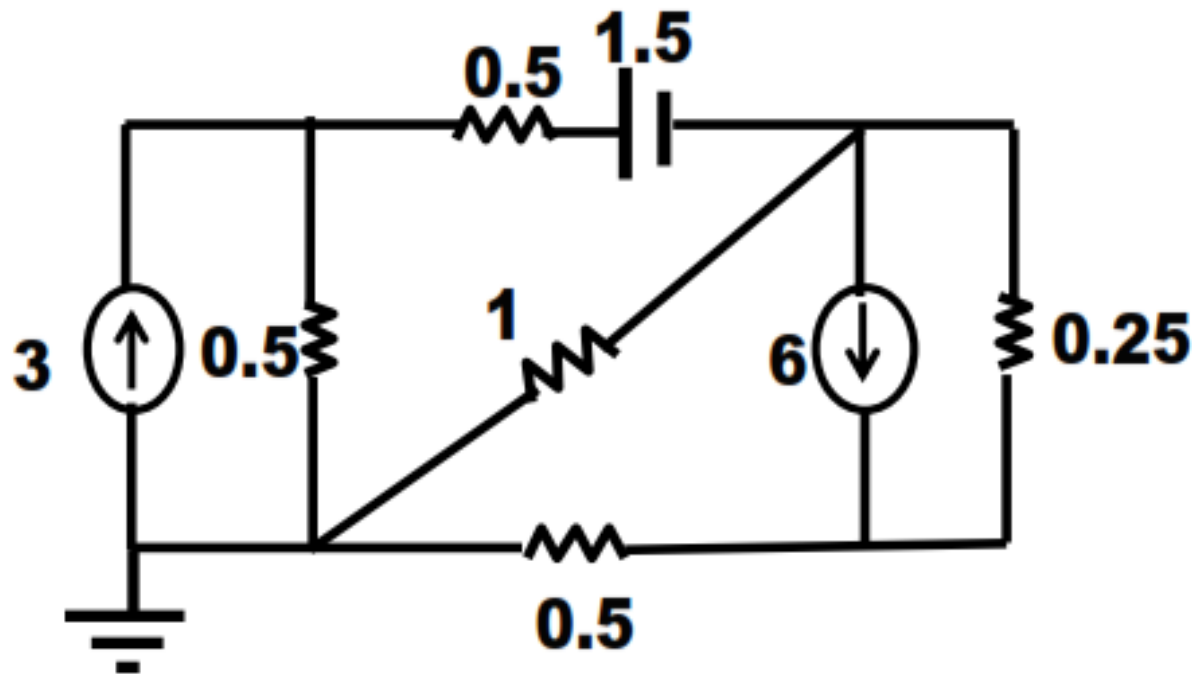
Example

- For the circuit shown, use node analysis to find:




- The nodal voltages and the branch currents
- Check the power balance

Sol.

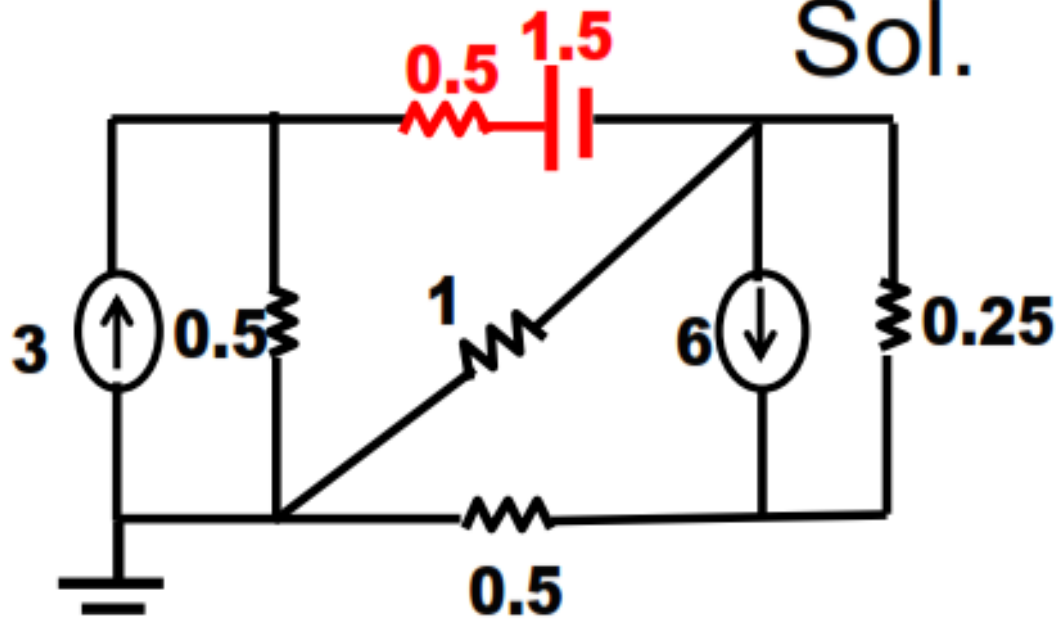


**Independent
VS $\Rightarrow$ CS**

N=4

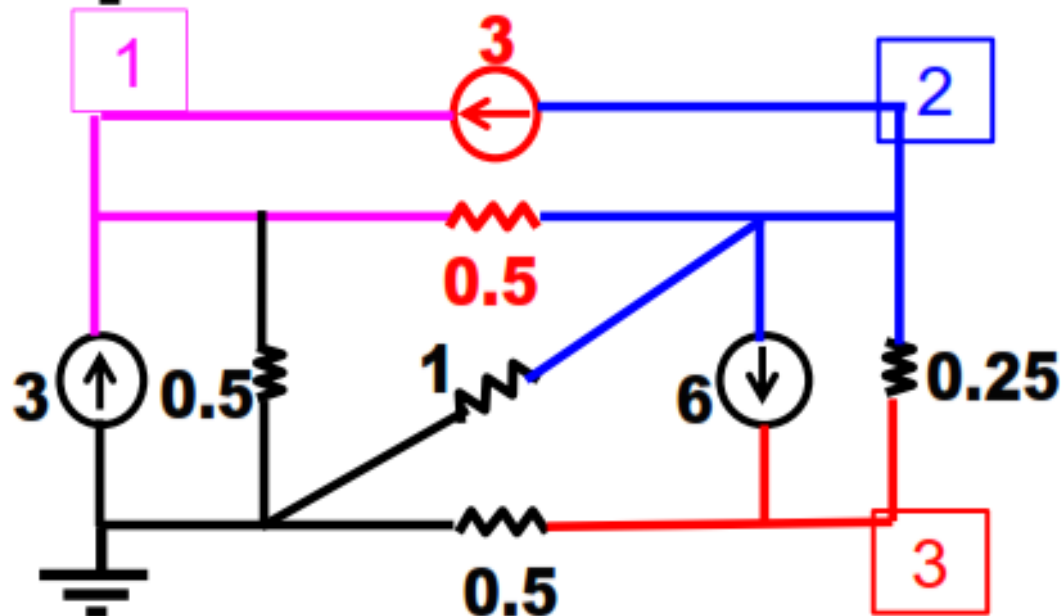


$$\begin{pmatrix} G \end{pmatrix} \begin{pmatrix} V \end{pmatrix} = \begin{pmatrix} I \end{pmatrix}$$

153

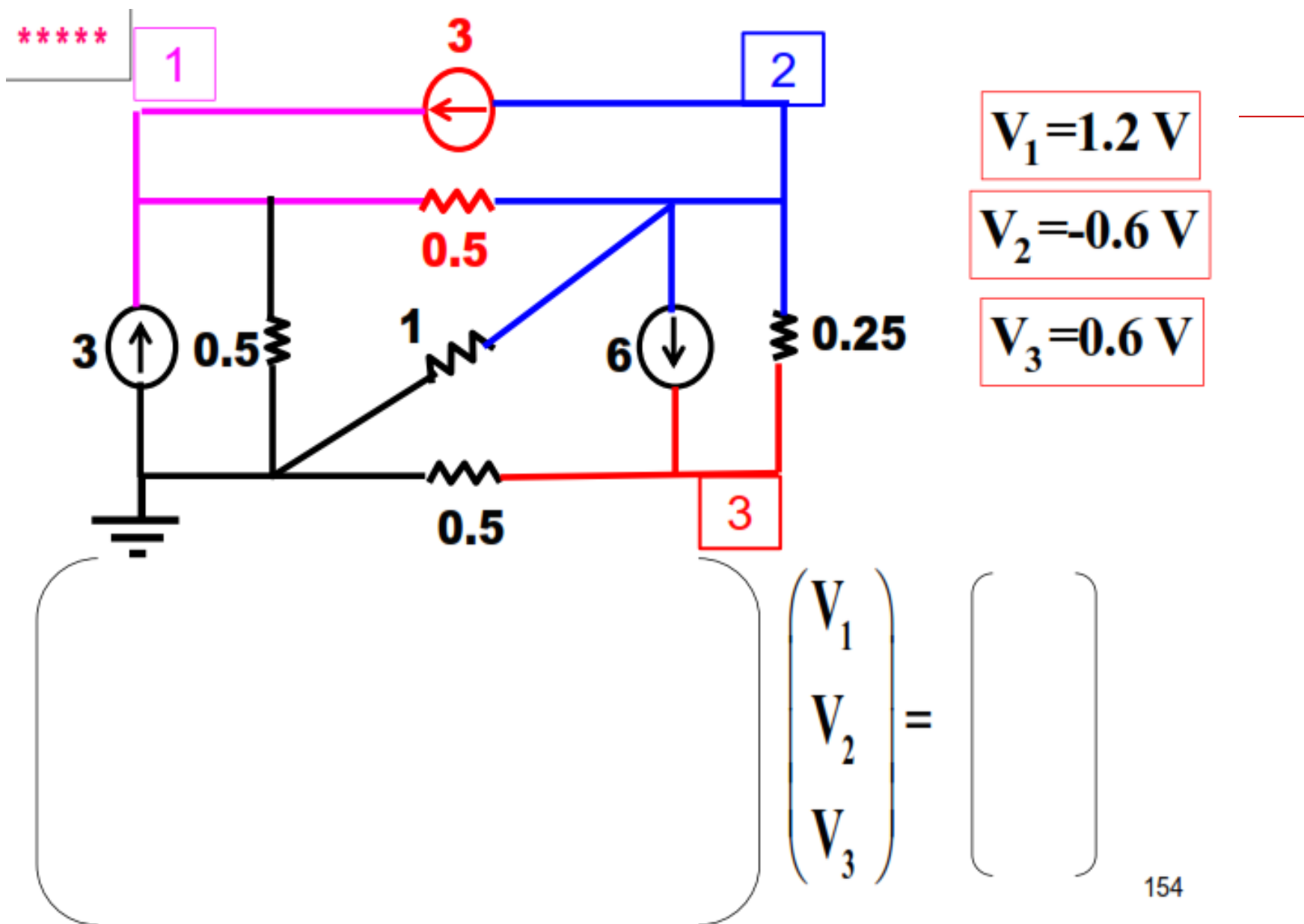

154

Branch Currents

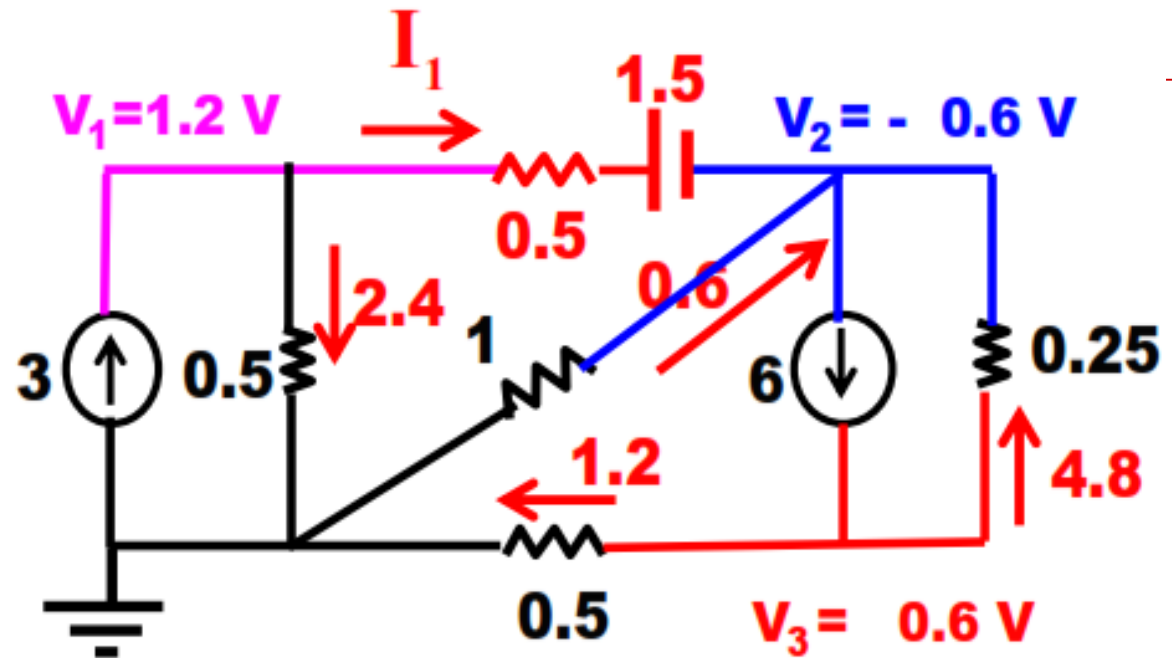

$V_{12} =$

$I_1 =$ Check **KCL** t node 1


Check **KCL** at node 2

Check **KCL** at node 3

Node Analysis With Voltage Source

CASE 1: When a voltage source exists between one node and the reference node

$$V_1 = 10 \text{ V} \quad (1)$$

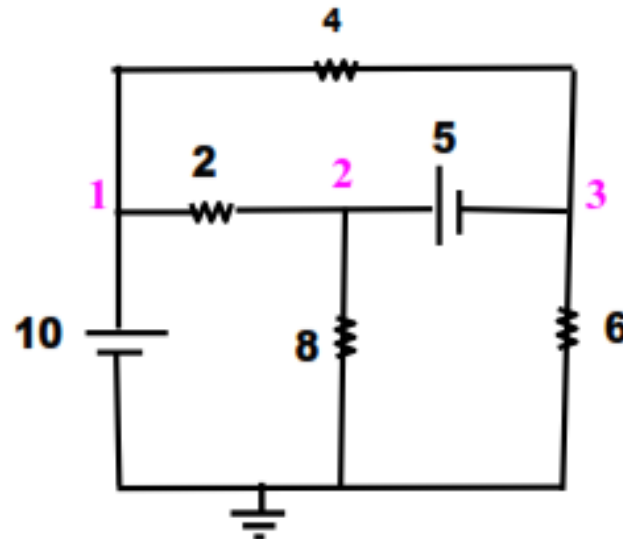

Node Analysis With Voltage Source

CASE 2: When a voltage source exists between two non-reference nodes


A super node is formed by enclosing a (dependent or independent) voltage source connected between two non-reference nodes

and any elements in parallel with it.

$$\text{KVL} \quad V_2 - V_3 = 5 \text{ V} \quad (2)$$

$$\text{KCL} \quad I_1 + I_2 + I_3 + I_4 = 0$$

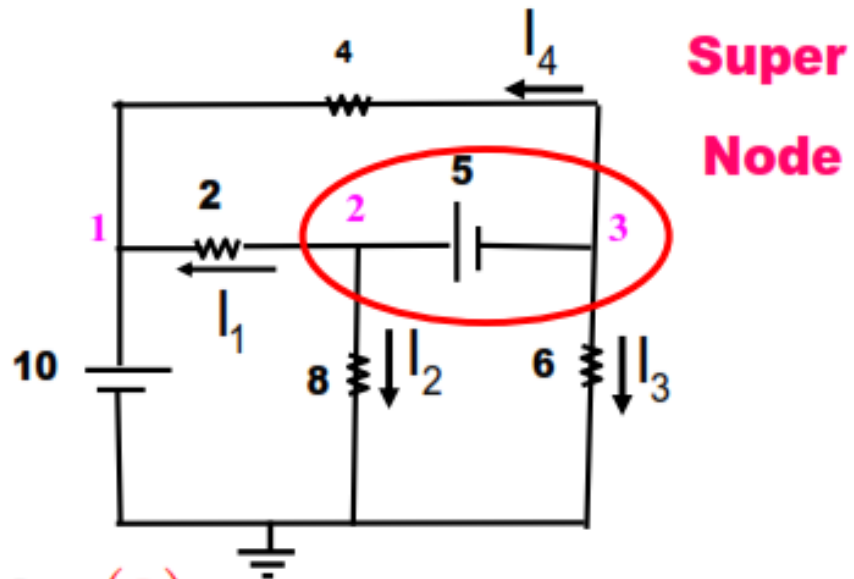
$$\frac{V_2 - V_1}{2} + \frac{V_2}{8} + \frac{V_3}{6} + \frac{V_3 - V_1}{4} = 0 \quad (3)$$



157

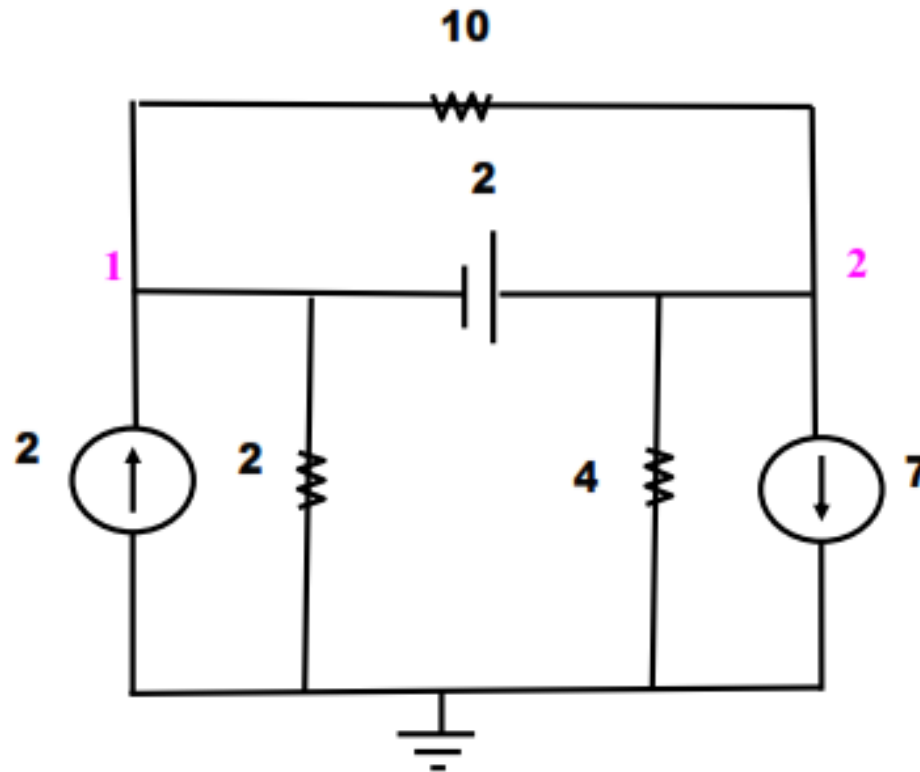Example

Find the node voltages for the circuit shown.



Example


KVL $V_2 - V_1 = 2 \text{ V} \quad (1)$

KCL $I_1 + I_2 + 7 - 2 = 0$

$$\frac{V_1}{2} + \frac{V_2}{4} = -5 \quad (2)$$


From 1, 2
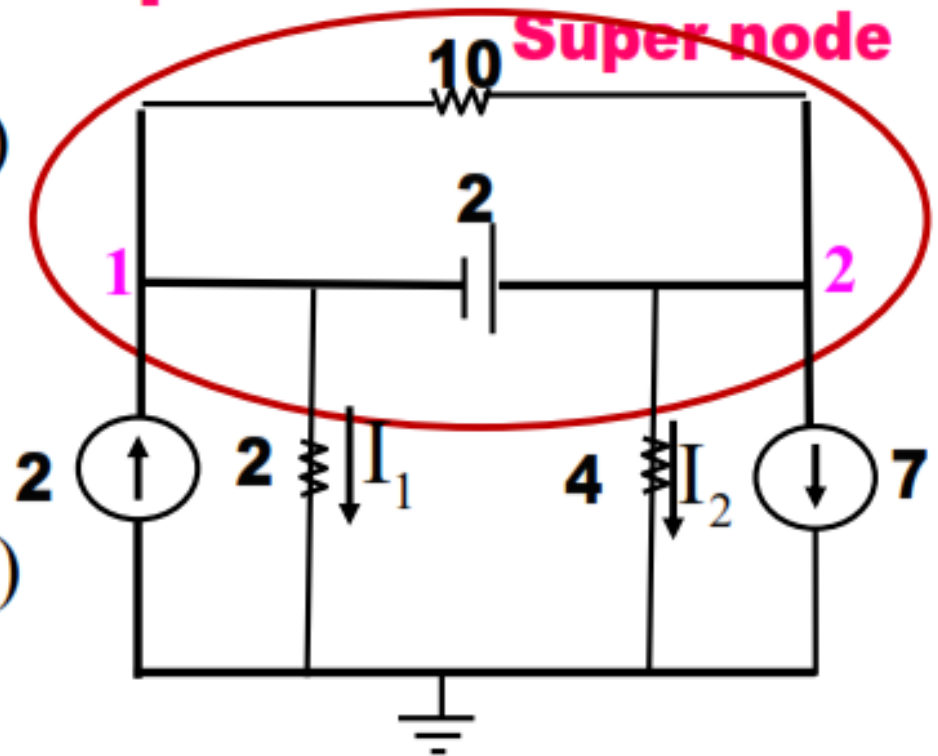
$$V_1 = -\frac{22}{3} \text{ V} \quad V_2 = -\frac{16}{3} \text{ V}$$



Node Analysis With Dependent Sources

$$\begin{pmatrix} \\ \\ \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} \\ \\ \end{pmatrix}$$

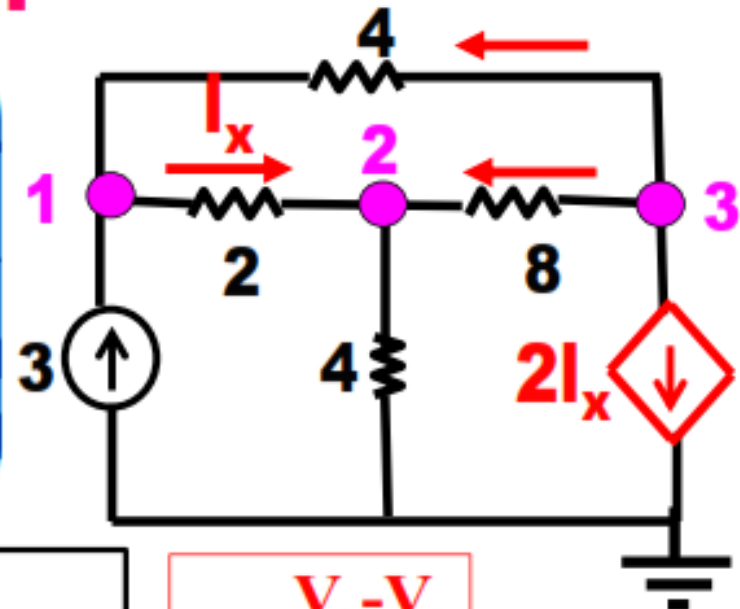

Node 3:

$$I_x = \frac{V_1 - V_2}{2}$$

$$\sum I_{out} = 0$$

$$V_1 = 4.8V \quad V_2 = 2.4V \quad V_3 = -2.4V$$


160

Node Analysis With Dependent Sources

$$\begin{pmatrix} 3/4 & -1/2 & -1/4 \\ -1/2 & 7/8 & -1/8 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 3 \\ 0 \\ 0 \end{pmatrix}$$

Node 3:


$$\sum I_{\text{out}} = 0$$

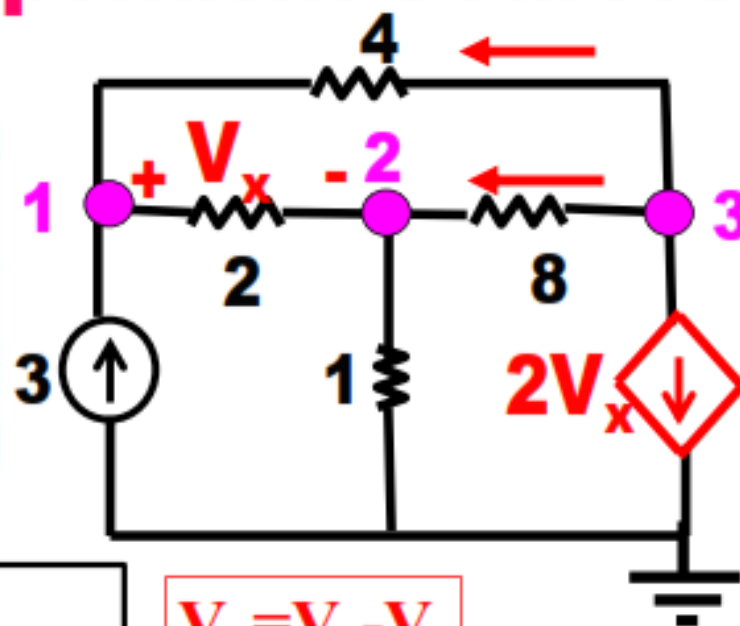

$$V_x = V_1 - V_2$$

Node Analysis With Dependent Sources

$$\begin{pmatrix} 3/4 & -1/2 & -1/4 \\ -1/2 & 7/8 & -1/8 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 3 \\ 0 \\ 0 \end{pmatrix}$$

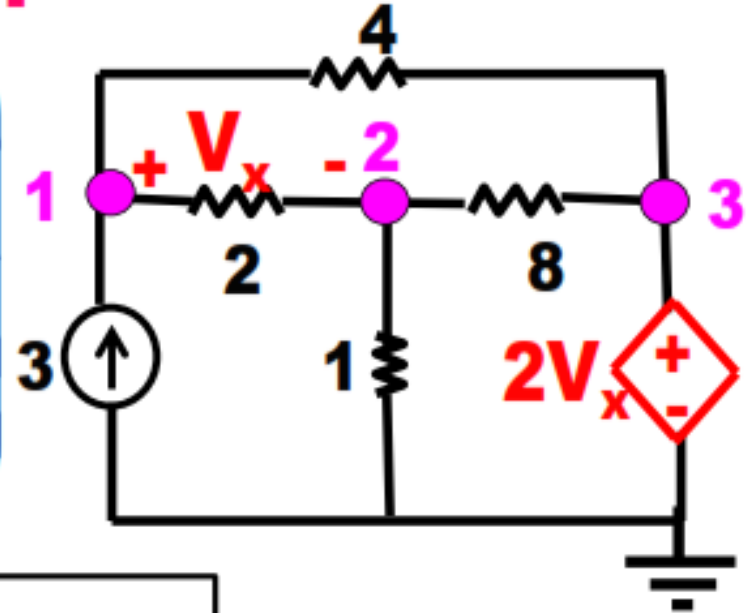


Node 3:

Node Analysis With Dependent Sources


$$\begin{pmatrix} 3/4 & -1/2 & -1/4 \\ -1/2 & 7/8 & -1/8 \\ 1 & -1 & -1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 3 \\ 0 \\ 0 \end{pmatrix}$$

Node 3:

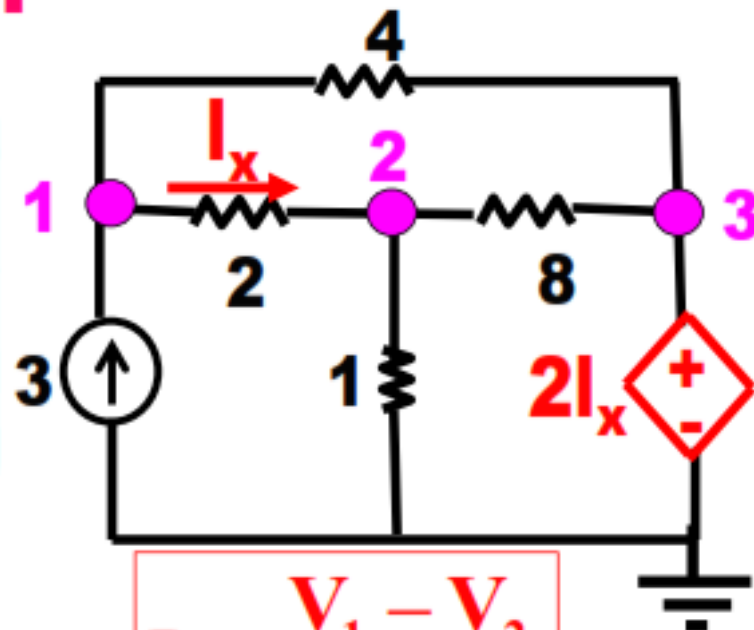

$$I_x = \frac{V_1 - V_2}{2}$$

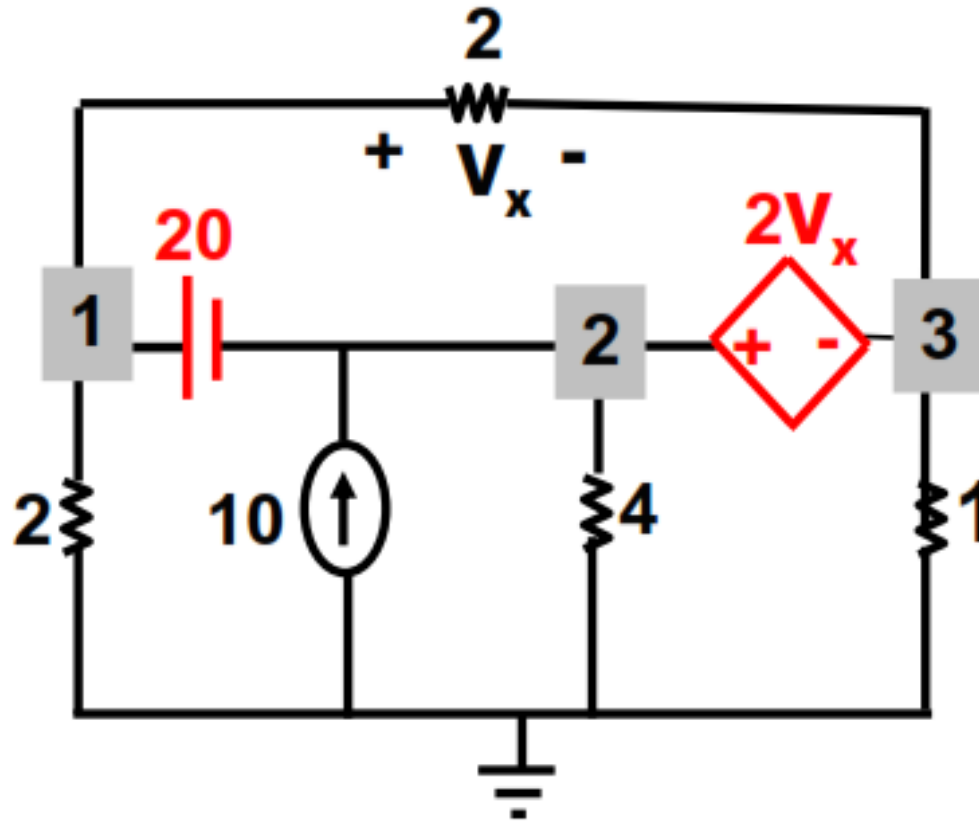Use **node analysis** to find **the node voltages** for the circuit shown.



Solution

