



# Lecture 7 – Feedback Amplifier

## Part II

**Dr. Mohamed Refky Amin**

Electronics and Electrical Communications Engineering Department (EECE)

Cairo University

[elcn201.eng@gmail.com](mailto:elcn201.eng@gmail.com)

<http://scholar.cu.edu.eg/refky/>

# Outline of this Lecture

---

- Previously on ELCN 201
- Shunt-Shunt Feedback Topology
- Shunt-Series Feedback Topology

# Previously on ELCN 201

---

## Feedback Amplifier

Amplifiers are usually classified into two groups: open-loop amplifiers and closed-loop (feedback) amplifiers

In amplifier design, feedback is usually applied to achieve one or more of the following goals:

- Make the value of the gain less sensitive to variations in the values of circuit components.
- Extend the Bandwidth
- Modify the input and output resistances

# Previously on ELCN 201

---


## General Feedback Structure

The closed-loop gain of the feedback amplifier  $A_f$ , is given by

$$A_f = \frac{x_o}{x_i} = \frac{A}{1 + A\beta}$$

The quantity  $A\beta$  is called the **loop gain**

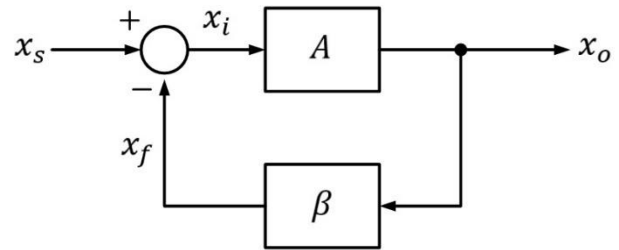The quantity  $1 + A\beta$  is called the **amount of feedback**



$$x_o = Ax_i$$

$$x_f = \beta x_o$$

$$x_i = x_s - x_f$$

$$x_o/A = x_s - \beta x_o$$

$$x_o(1 + A\beta) = Ax_s$$

# Previously on ELCN 201

---

## Feedback Amplifier Types

Based on the input signal to be amplified and on the desired form of output signal, feedback amplifiers are classified into four categories:

Amplifier Type	Input signal $x_s, x_i, x_f$	Output signal $x_o$
Voltage Amplifier	Voltage	Voltage
Current Amplifier	Current	Current
Transconductance Amplifier	Voltage	Current
Transresistance Amplifier	Current	Voltage

# Previously on ELCN 201

---


## Feedback Amplifier Types

Voltage signals are added or subtracted (mixed) in **series** fashion

Current signals are mixed in **parallel (shunt)** fashion





Voltage is sampled in a **parallel (shunt)** fashion

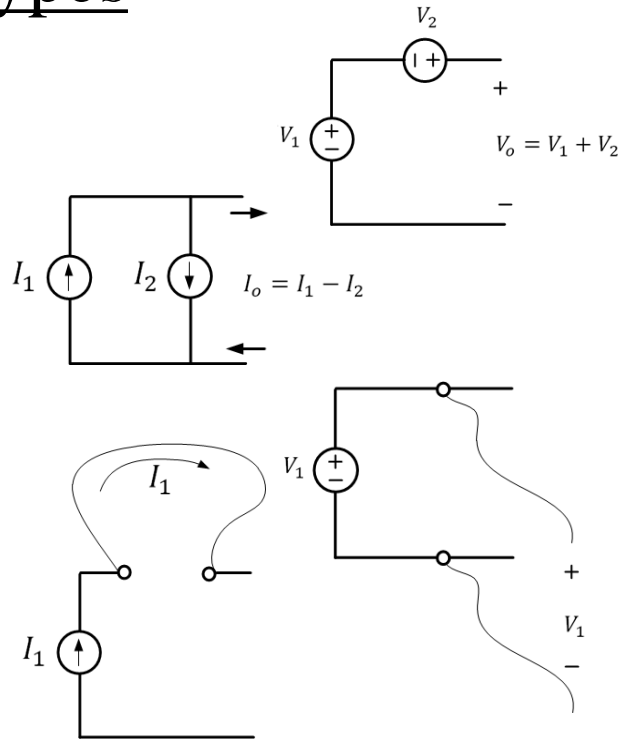Current is sampled in a **series** fashion




# Previously on ELCN 201

## Feedback Amplifier Types

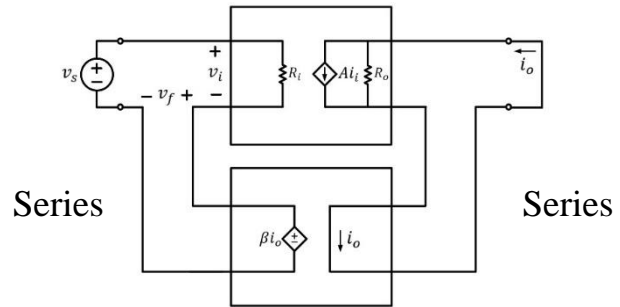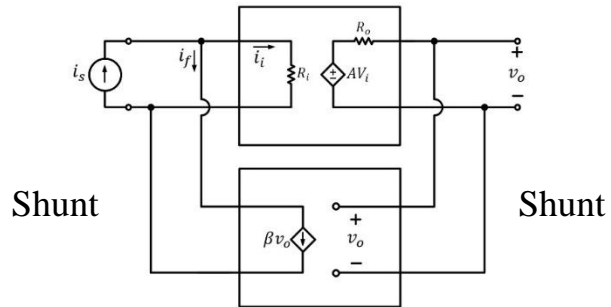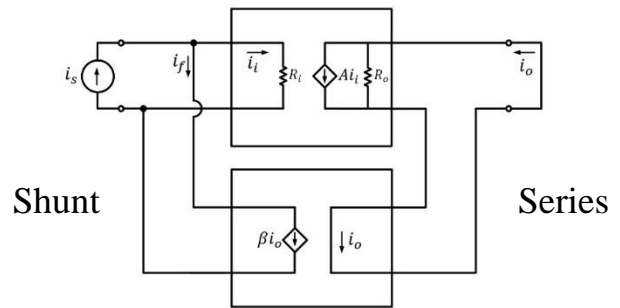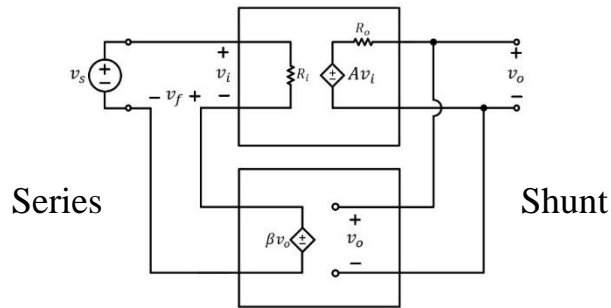


# Transresistance Amplifier

## Shunt-Shunt Feedback Topology

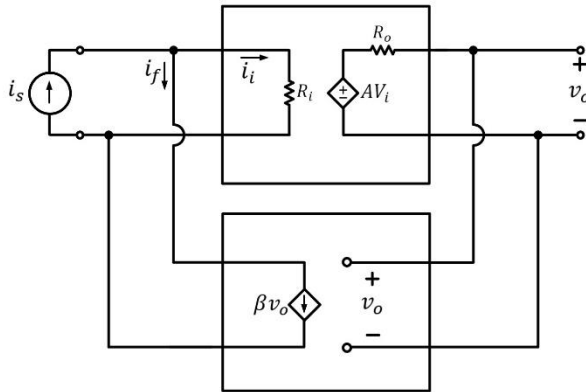

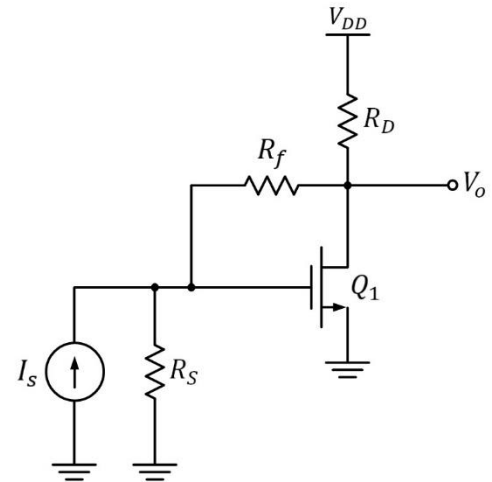For the feedback to be negative,  $i_f$  must be of the **same** polarity as  $i_s$





# Transresistance Amplifier



## Shunt-Shunt Feedback Topology

### The Ideal Case

In the ideal case, the feedback network has an **infinite** input resistance and **infinite** output resistance

The feedback network **does not** load the basic amplifier
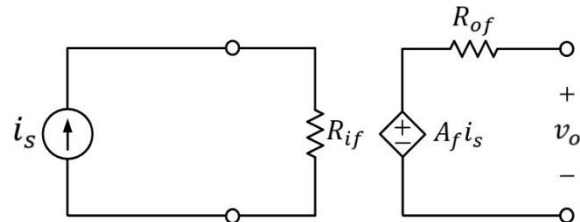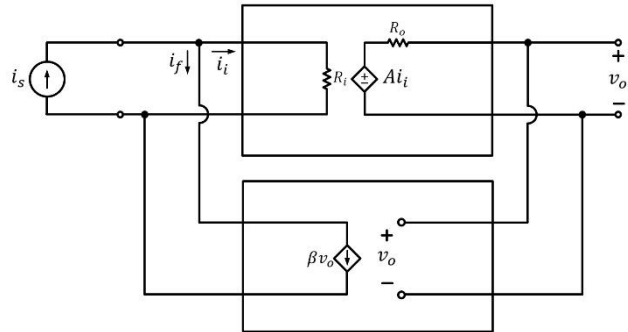
$$A_f = \frac{v_o}{i_s} = \frac{A}{1 + \beta A}$$



# Transresistance Amplifier

## Shunt-Shunt Feedback Topology



### The Ideal Case

Due to the shunt connection at the input, the input resistance is given by

$$R_{if} = \frac{R_i}{1 + A\beta}$$

Due to the shunt connection at the output, the output resistance is given by

$$R_{of} = \frac{R_o}{1 + A\beta}$$

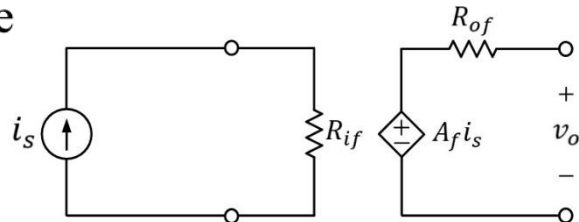
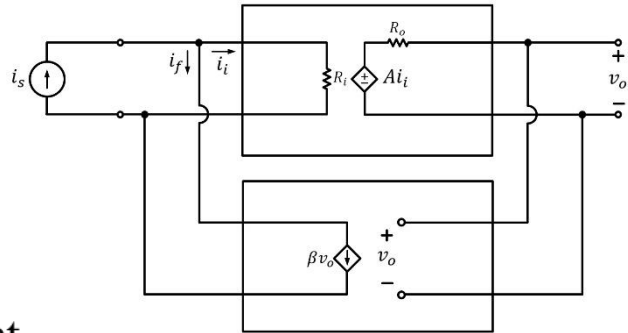


# Transresistance Amplifier

## Shunt-Shunt Feedback Topology
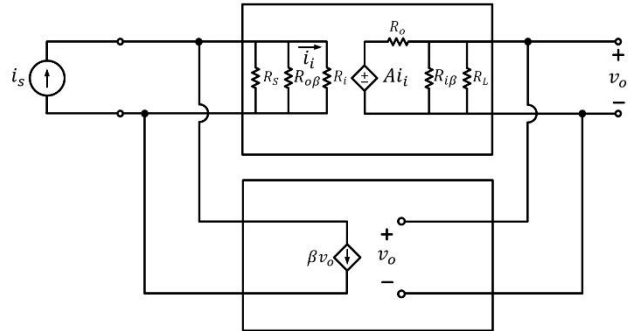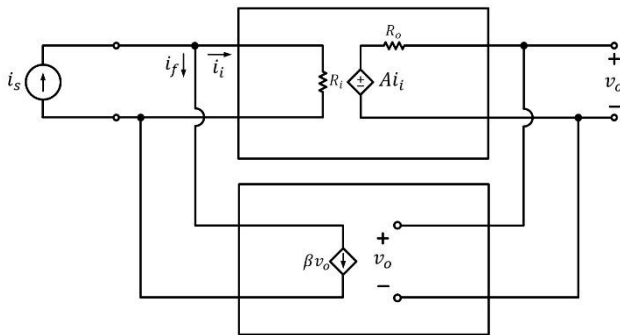
### The Practical Case

In the practical case, the feedback network loads the basic amplifier and affects the values of  $A$ ,  $R_i$ , and  $R_o$ .



The finite source and load resistances also affect the values of  $A$ ,  $R_i$ , and  $R_o$ .

# Transresistance Amplifier

## Shunt-Shunt Feedback Topology



### The Practical Case

The gain of the feedback network is given by

$$\beta = \frac{i_f}{v_o} \bigg|_{v_f=0}$$

The input resistance of the feedback network is given by

$$R_{i\beta} = \frac{v_o}{i_o} \bigg|_{v_f=0}$$

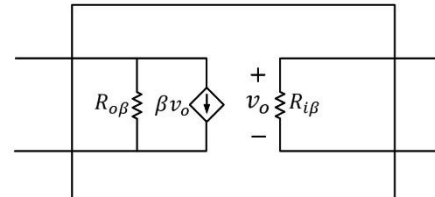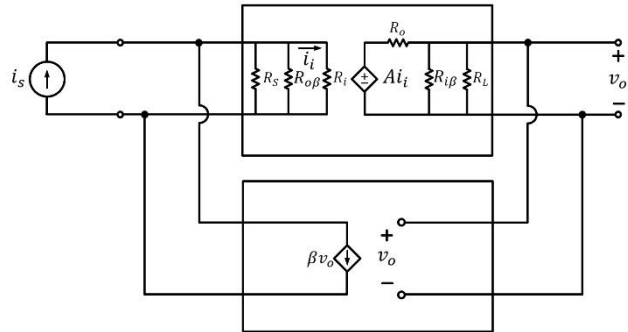



# Transresistance Amplifier

## Shunt-Shunt Feedback Topology

### The Practical Case

The output resistance of the feedback network is given by

$$R_{o\beta} = \left. \frac{v_x}{i_x} \right|_{v_o=0}$$

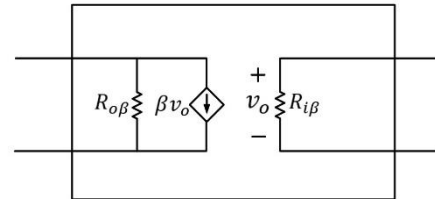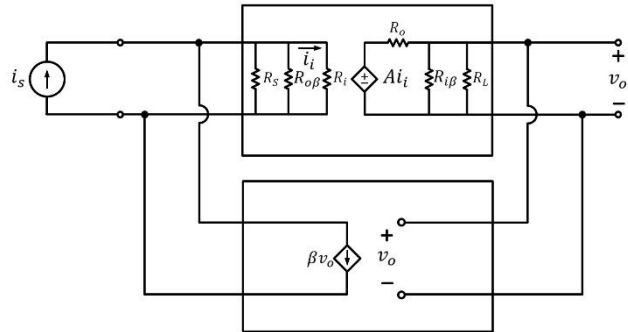

# Transresistance Amplifier

## Shunt-Shunt Feedback Topology



### The Practical Case

The gain of the modified basic amplifier is given by

$$A_m = \frac{v_o}{i_i'}$$

$R_{im}$  and  $R_{om}$  are determined from the modified basic amplifier circuit

$$R_{im} = \frac{v_i}{i_i} \quad R_{om} = \frac{v_o}{i_o} \bigg|_{i_i' = 0}$$

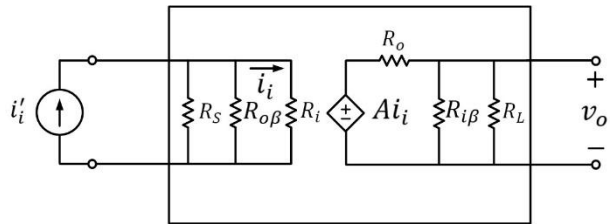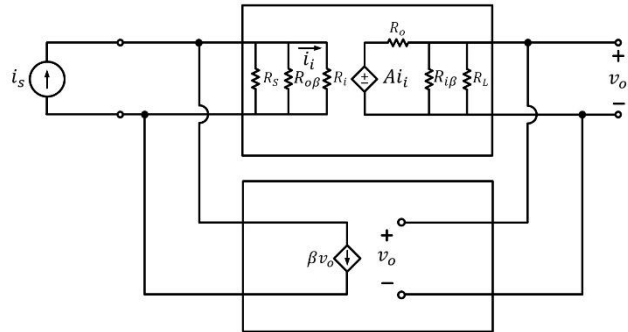

# Transresistance Amplifier

## Shunt-Shunt Feedback Topology


### The Practical Case

The overall gain of the feedback amplifier is given by

$$A_f = \frac{A_m}{1 + A_m \beta}$$

The input resistance with feedback is given by
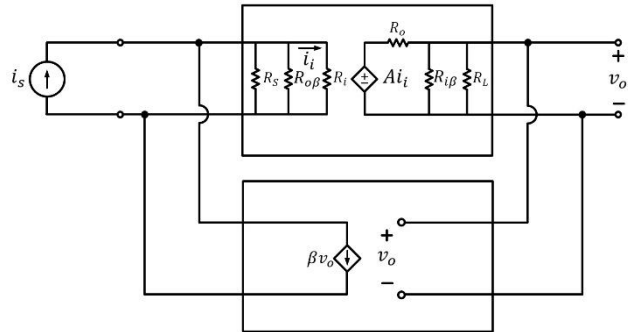
$$R_{if} = \frac{R_{im}}{1 + A_m \beta}$$



The output resistance with feedback is given by

$$R_{of} = \frac{R_{om}}{1 + A_m \beta}$$

# Transresistance Amplifier

## Shunt-Shunt Feedback Topology



### The Practical Case

The actual input resistance of the feedback amplifier is given by

$$R_{in} = 1 / \left( \frac{1}{R_{if}} - \frac{1}{R_s} \right)$$

The actual output resistance of the feedback amplifier is given by
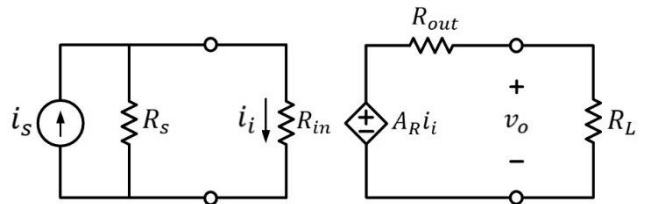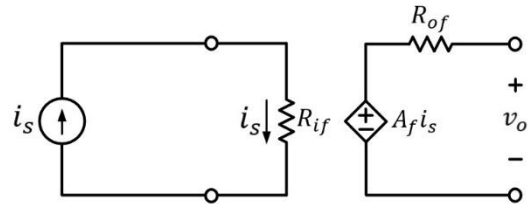
$$R_{out} = 1 / \left( \frac{1}{R_{of}} - \frac{1}{R_L} \right)$$



$$R_{of} = R_{out} // R_L$$




# Transresistance Amplifier

---

## Example (1)


Analyze the shown amplifier obtain its gain, input resistance, and output resistance. Assume  $R_S \gg R_f$

---

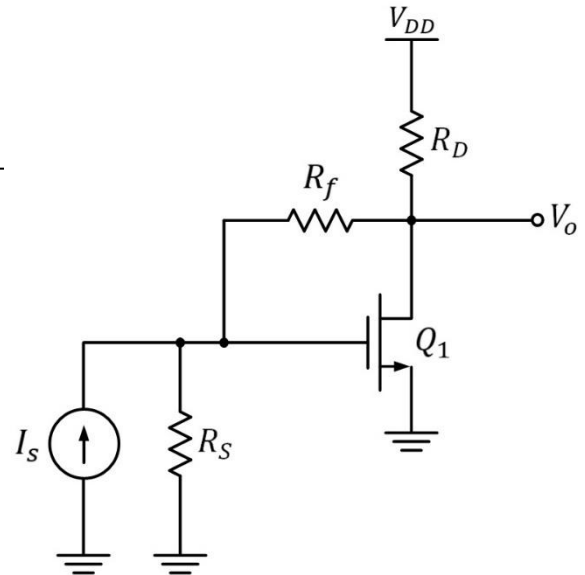


# Current Amplifier

## Shunt-Series Feedback Topology

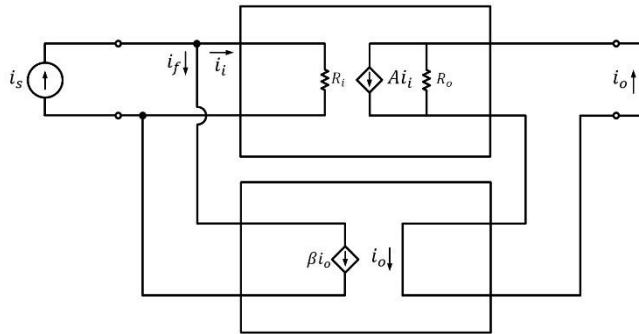

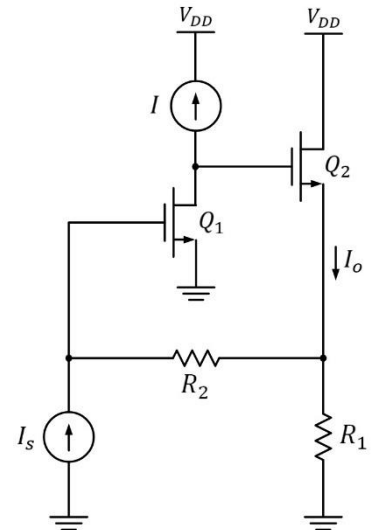For the feedback to be negative,  $i_f$  must be of the **same** polarity as  $i_s$




# Current Amplifier

## Shunt-Series Feedback Topology

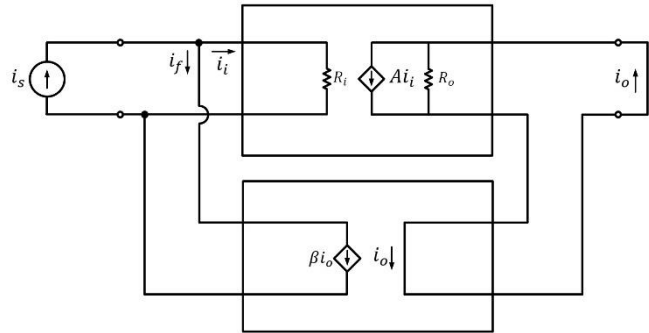
### The Ideal Case

In the ideal case, the feedback network has an **zero** input resistance and **infinite** output resistance

The feedback network **does not** load the basic amplifier


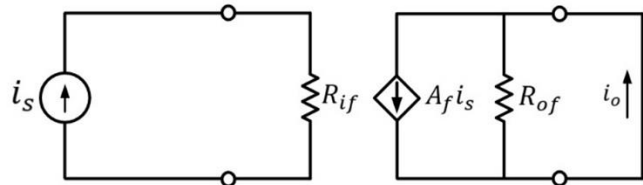
$$A_f = \frac{i_o}{i_s} = \frac{A}{1 + \beta A}$$



# Current Amplifier

## Shunt-Series Feedback Topology



### The Ideal Case

Due to the shunt connection at the input, the input resistance is given by

$$R_{if} = \frac{R_i}{1 + A\beta}$$

Due to the series connection at the output, the output resistance is given by

$$R_{of} = R_o(1 + A\beta)$$

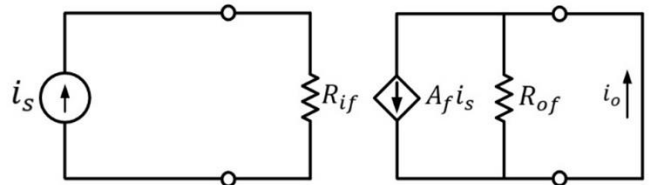
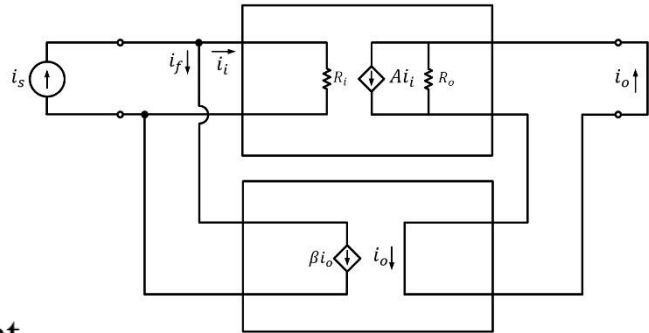


# Current Amplifier

## Shunt-Series Feedback Topology
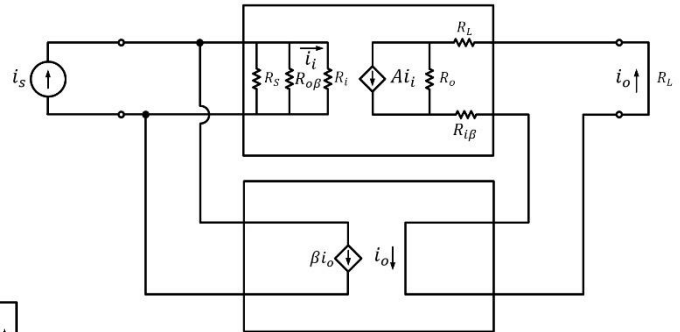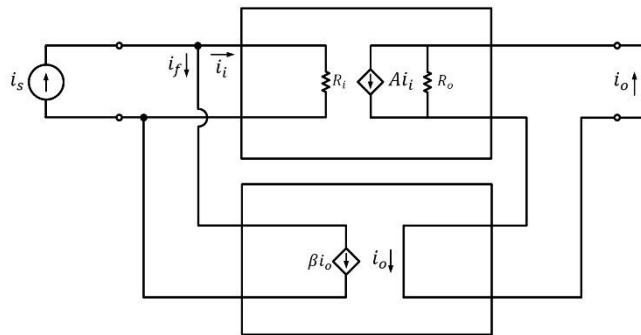
### The Practical Case

In the practical case, the feedback network loads the basic amplifier and affects the values of  $A$ ,  $R_i$ , and  $R_o$ .



The finite source and load resistances also affect the values of  $A$ ,  $R_i$ , and  $R_o$ .

# Current Amplifier

## Shunt-Series Feedback Topology



### The Practical Case

The gain of the feedback network is given by

$$\beta = \left. \frac{i_f}{i_o} \right|_{v_f=0}$$

The input resistance of the feedback network is given by

$$R_{i\beta} = \left. \frac{v_o}{i_o} \right|_{v_f=0}$$

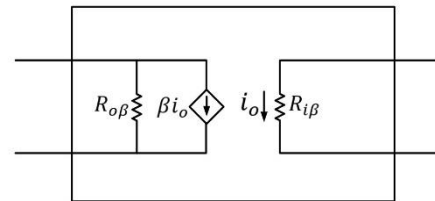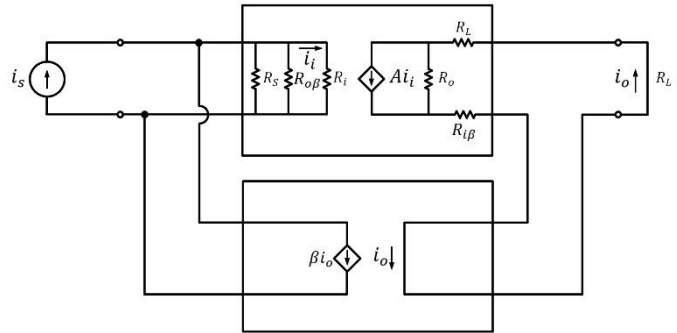



# Current Amplifier

## Shunt-Series Feedback Topology

### The Practical Case

The output resistance of the feedback network is given by

$$R_{o\beta} = \left. \frac{v_f}{i_f} \right|_{i_o=0}$$

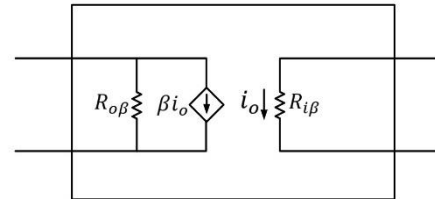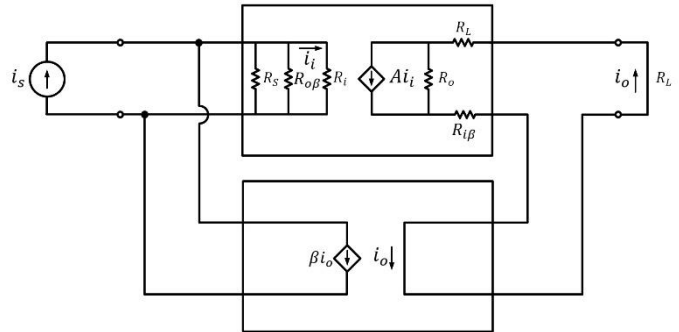





# Current Amplifier

## Shunt-Series Feedback Topology


### The Practical Case

The overall gain of the feedback amplifier is given by

$$A_f = \frac{A_m}{1 + A_m \beta}$$

The input resistance with feedback is given by
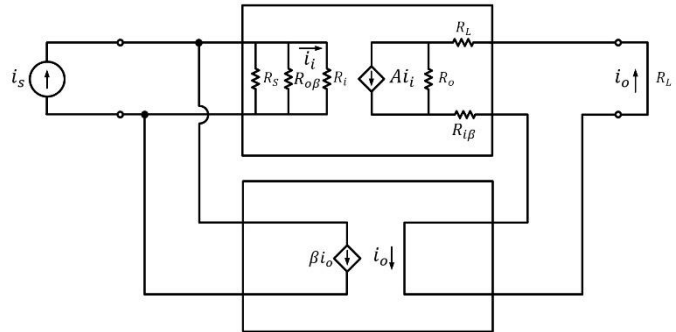
$$R_{if} = \frac{R_{im}}{1 + A_m \beta}$$



The output resistance with feedback is given by

$$R_{of} = R_{om}(1 + A_m \beta)$$

# Current Amplifier

## Shunt-Series Feedback Topology


### The Practical Case

The actual input resistance of the feedback amplifier is given by

$$R_{in} = 1 / \left( \frac{1}{R_{if}} - \frac{1}{R_s} \right)$$

The actual output resistance of the feedback amplifier is given by

$$R_{out} = R_{of} - R_L$$

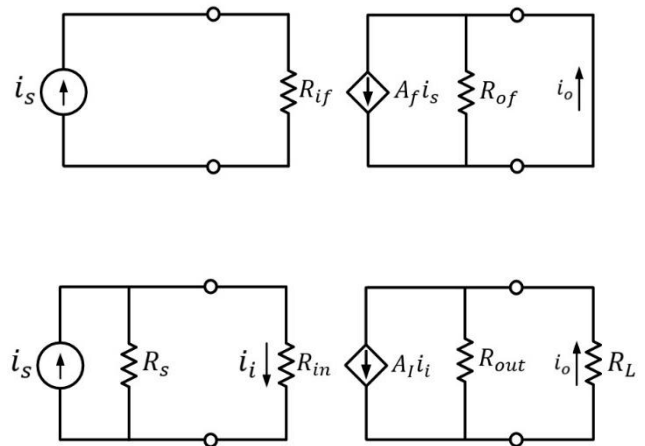

$$R_{of} = R_{out} + R_L$$

# Current Amplifier

---

## Example (2)

Analyze the shown amplifier obtain its gain, input resistance, and output resistance.

---

