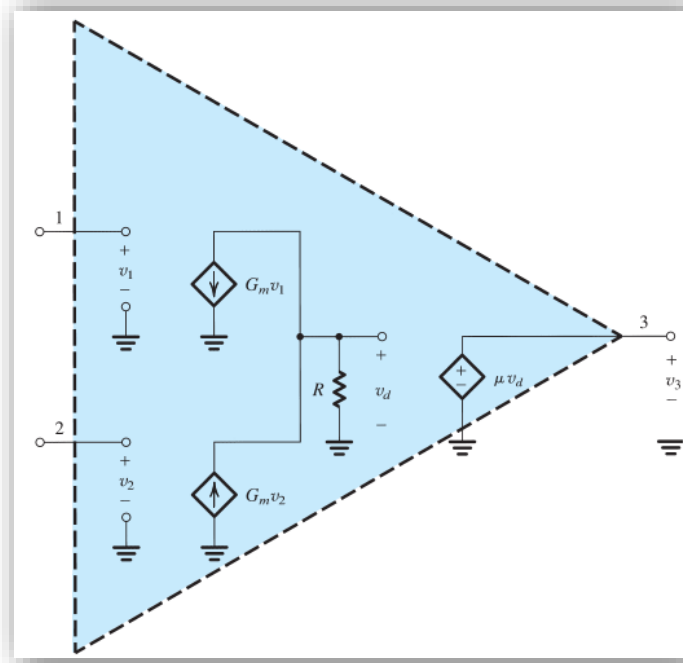






Operational Amplifier

- 1- For the Op-Amp shown in figure, express the output v_3 as a function of v_1 and v_2 .
For $G_m = 10 \text{ mA/V}$, $R = 10 \text{ k}\Omega$, and $\mu = 100$, find the value of the open-loop gain A



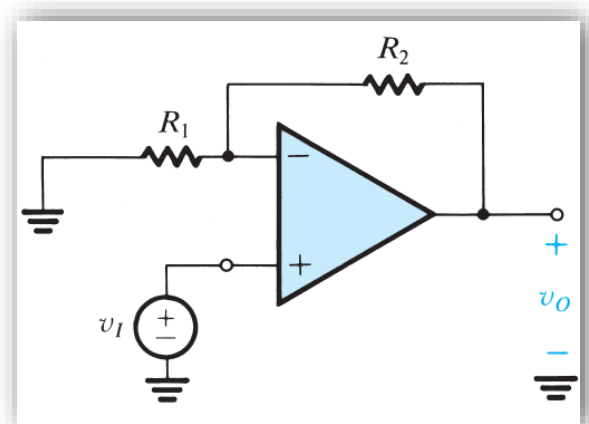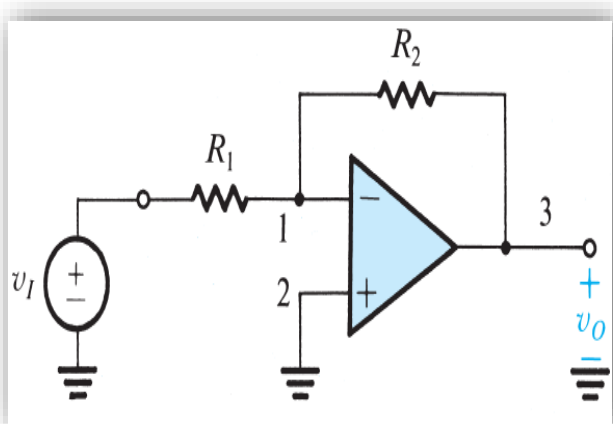- 2- Find the closed-loop gain, G , for both the inverting and non-inverting Op-Amp configurations, assuming that the open-loop gain, A , is finite.







Operational Amplifier

3- For each of the following circuits:

Determine all the indicated branch currents and node voltages.

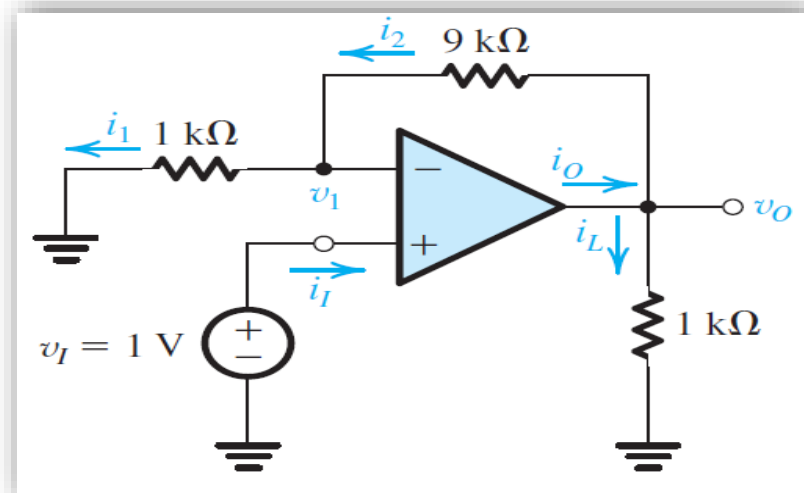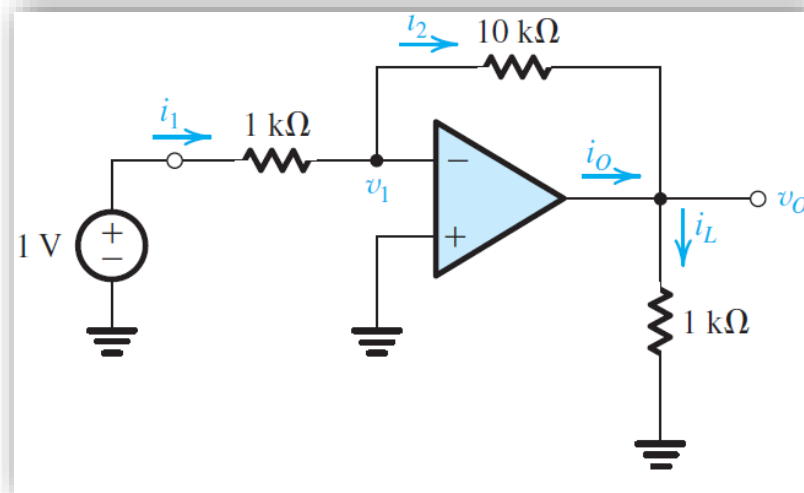
Find the voltage gain, v_o/v_i , the current gain, i_L/i_I , and the power gain, P_o/P_i





Operational Amplifier

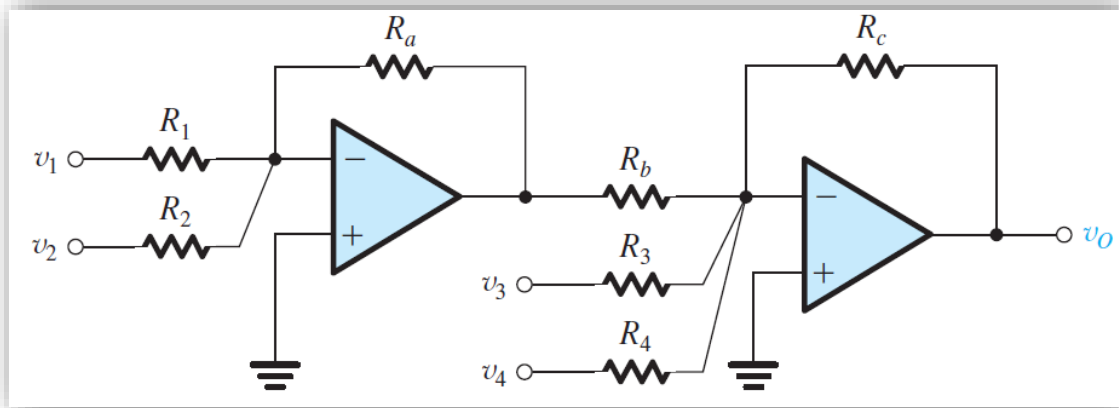- 4- Find the relation between the output voltage and the input voltages.
Assume ideal Op-Amp.



- 5- Find the relation between the output voltage and the input voltages.
Assume ideal Op-Amps.

