

# Electronic and Digital Circuits (ELC 225a)

Samy S. Soliman

Electronics and Electrical Communication Engineering Department  
Cairo University, Egypt

**Email:** *samy.soliman@cu.edu.eg*

**Website:** <http://scholar.cu.edu.eg/samysoliman>

November 25, 2015

## 1 Bipolar Junction Transistor

- Introduction
- Device Structure and Physical Operation
- Current-Voltage Characteristics
- DC Operation
- Small-Signal Operation
- Applications: Basic BJT Amplifier Circuits

## Bipolar Junction Transistor

- 1 One of the main building blocks in electronic systems
- 2 Three terminal device that can be used for both analog and digital circuits
- 3 Incorporate two back-to-back PN junctions
- 4 Can be used as a control device
- 5 Control is generally due to electric current (flow of charge carriers), i.e. the current flow in one terminal controls the current between the other two terminals



# BJT Circuit Symbols

## Three Terminals Device


- Base (B)  $\Rightarrow$  Control terminal
- Emitter (E)
- Collector (C)

## Two Types


- npn Type
- pnp Type

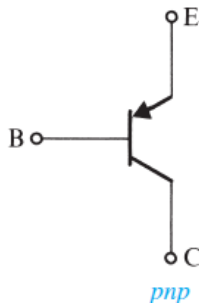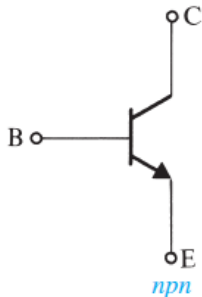


# Terminology

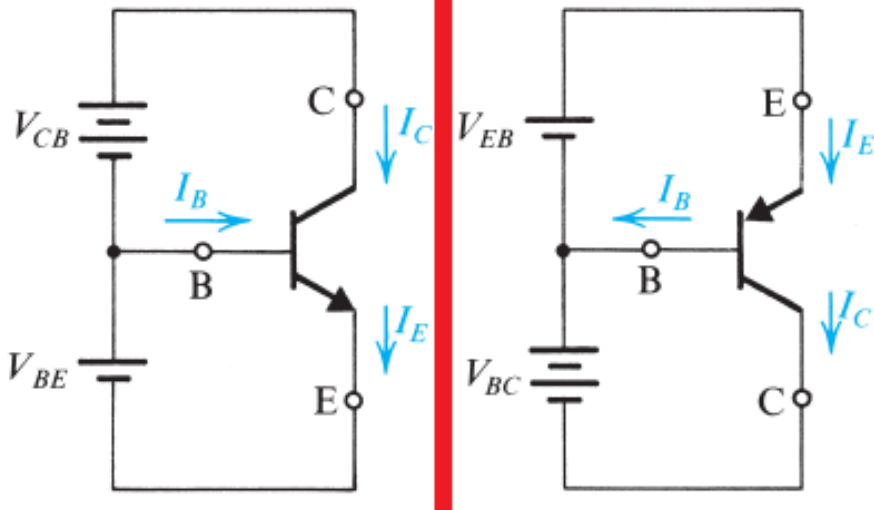

# Device Structure: npn Type

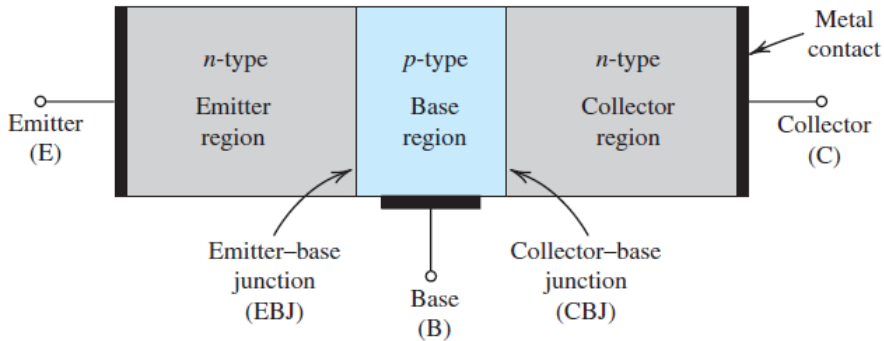

# Device Structure: pnp Type

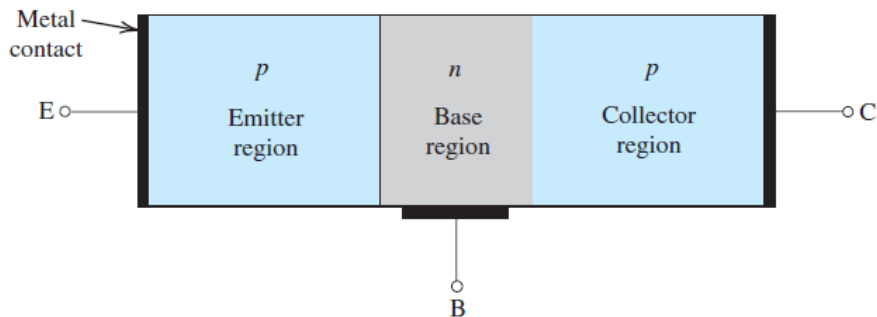


## BJT Modes of Operation

Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward



# Physical Operation: npn Type BJT

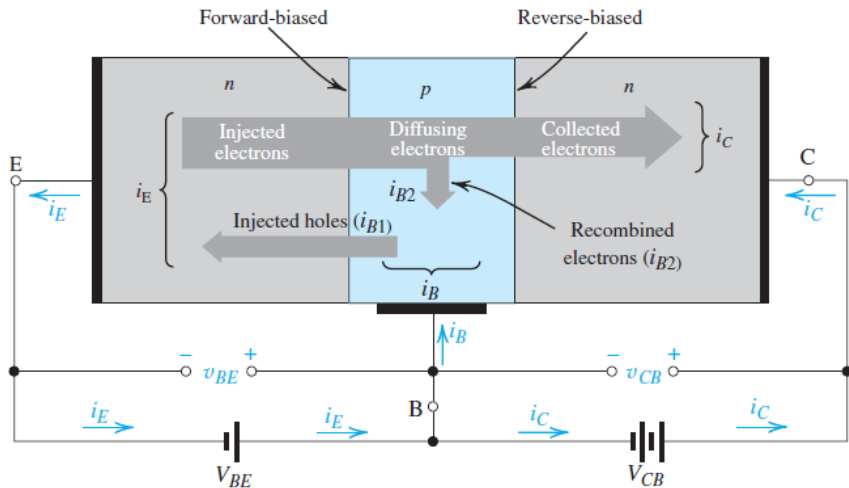



# Physical Operation: npn Type BJT

- Collector is normally more positive than the Emitter
- $V_{CE}$  might be a few volts
- The device resembles two back-to-back diodes

## With positive $V_{BE}$

- This forward biases the Base-Emitter junction
- The base region is lightly doped and very thin
- Because it is lightly doped, the current produced is mainly electrons flowing from the emitter to the base
- Because the base region is thin, most of the electrons entering the base get swept across the Base-Collector junction into the collector
- This produces a collector current that is much larger than the base current
- This gives current amplification


## Input-Output Relations

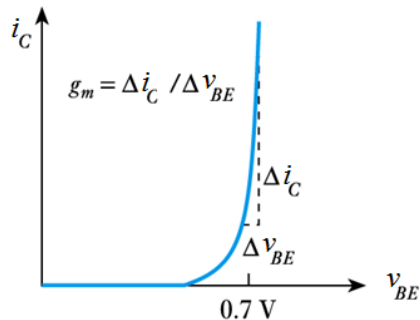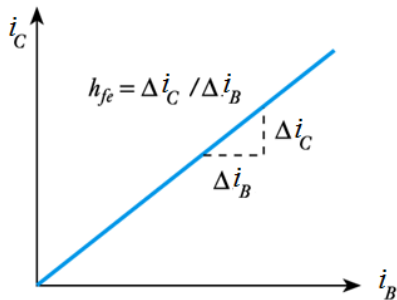

# Current-Current ( $i_C - i_B$ ) Characteristics

## Collector Current - Base Current Relation

$$i_C = \beta i_B$$

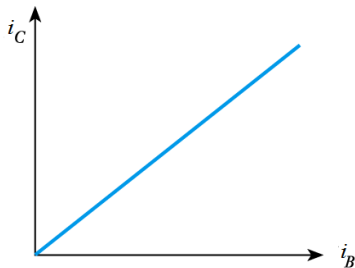


- 1 Characteristic is approximately linear
- 2 Magnitude of collector current is generally many times that of the base current
- 3 The device provides current gain  $\beta$

# Current-Voltage ( $i_C - v_{BE}$ ) Characteristics
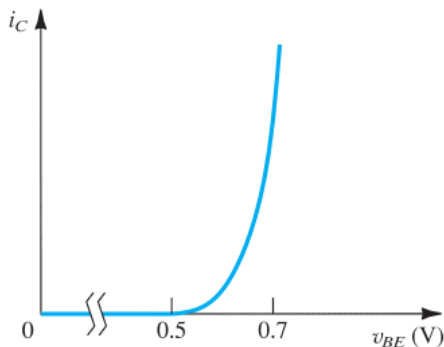
## Collector Current - Base-Emitter Voltage Relation

$$i_C = I_S \exp \left[ \frac{v_{BE}}{V_T} \right]$$

**Note:** Both  $I_S$  and  $V_T$  are temperature dependent.



## Current-Voltage Relationships in the Active Mode

$$i_C = I_S e^{v_{BE}/V_T}$$

$$i_B = \frac{i_C}{\beta} = \left(\frac{I_S}{\beta}\right) e^{v_{BE}/V_T}$$

$$i_E = \frac{i_C}{\alpha} = \left(\frac{I_S}{\alpha}\right) e^{v_{BE}/V_T}$$

*Note:* For the *pnp* transistor, replace  $v_{BE}$  with  $v_{EB}$ .


$$i_C = \alpha i_E \qquad i_B = (1 - \alpha)i_E = \frac{i_E}{\beta + 1}$$

$$i_C = \beta i_B \qquad i_E = (\beta + 1)i_B$$


$$\beta = \frac{\alpha}{1 - \alpha} \qquad \alpha = \frac{\beta}{\beta + 1}$$

$$V_T = \text{thermal voltage} = \frac{kT}{q} \approx 25 \text{ mV at room temperature}$$

# Current-Voltage Characteristics

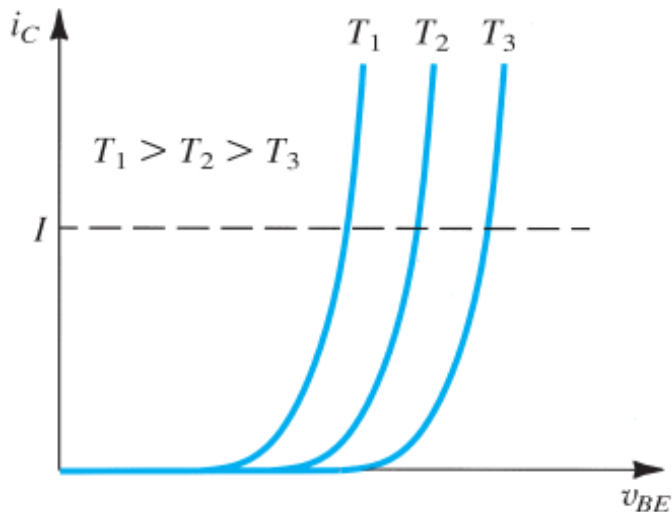
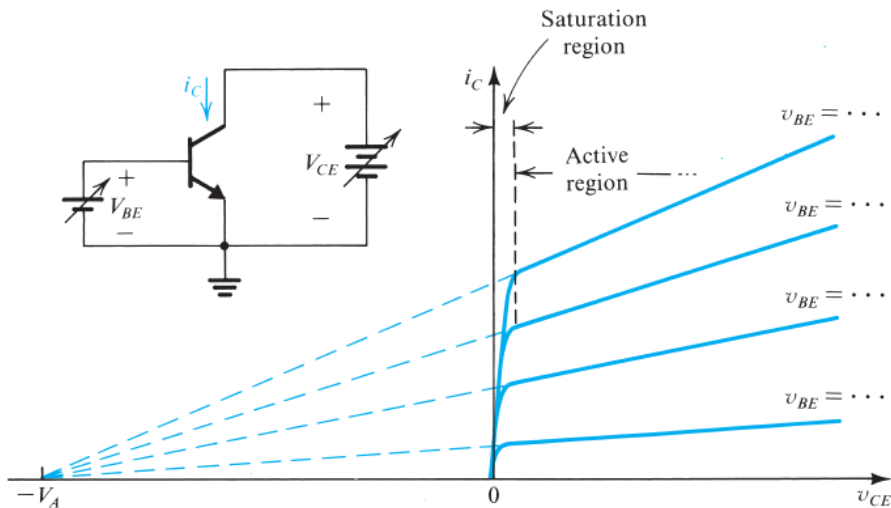
# Common-Emitter Characteristics - Early Voltage






# DC Operation: Example 1

$$\beta = 100$$

$$v_{BE} = 0.7 \text{ V at } i_C = 1 \text{ mA}$$

Design the circuit so that a current of  $2 \text{ mA}$  flows through the collector and a voltage of  $+5 \text{ V}$  appears at the collector.

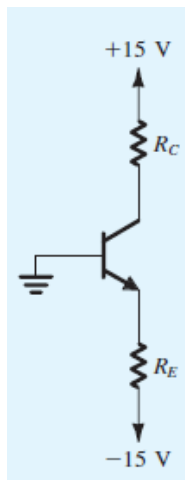Design the circuit  $\Leftarrow$  Find the values of  $R_C$  and  $R_E$



# DC Operation: Example 1

Given;

$$I_C = 2 \text{ mA}$$

$$V_C = 5 \text{ V}$$


Then;

$$① R_C = \frac{+15 - V_C}{I_C}$$

$$② I_E = \frac{\beta + 1}{\beta} I_C$$

$$③ V_{BE} = v_{BE} + V_T \ln \left( \frac{I_C}{i_C} \right)$$

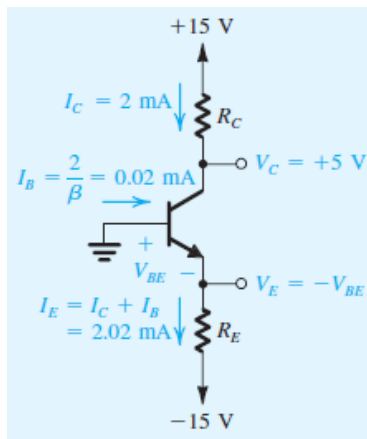
$$④ R_E = \frac{(0 - V_{BE}) - (-15)}{I_E}$$



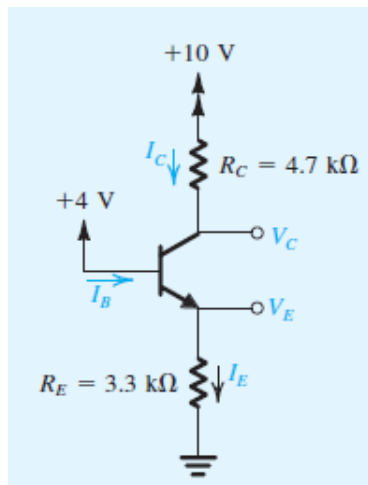
## DC Operation: Example 2

$$\beta = 100$$

Analyze this circuit to determine all node voltages and branch currents




## DC Operation: Example 2

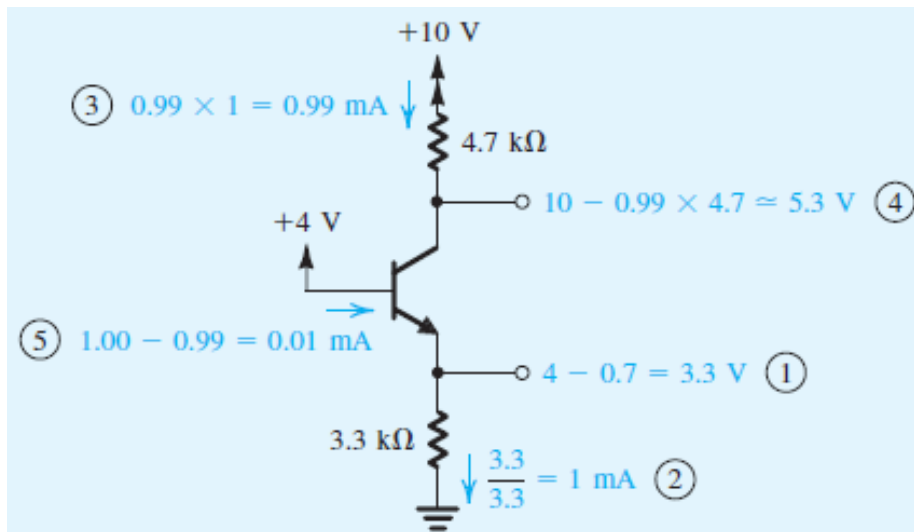

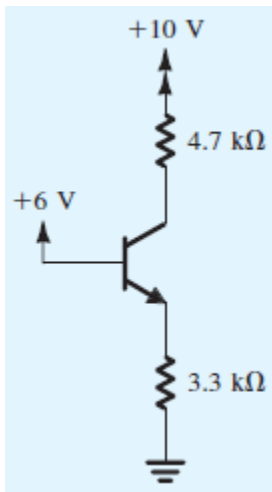
# DC Operation: Example 3

$$\beta = 50$$


Analyze this circuit to determine all node voltages and branch currents



# DC Operation: Example 3

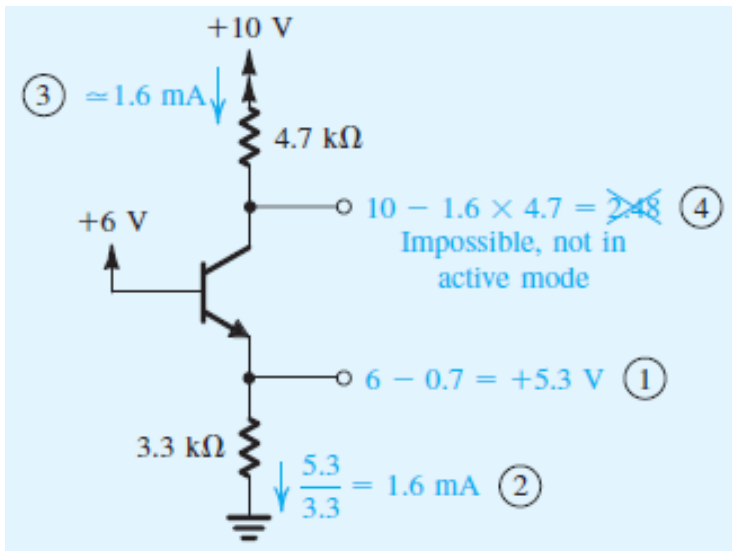


# DC Operation: Example 3

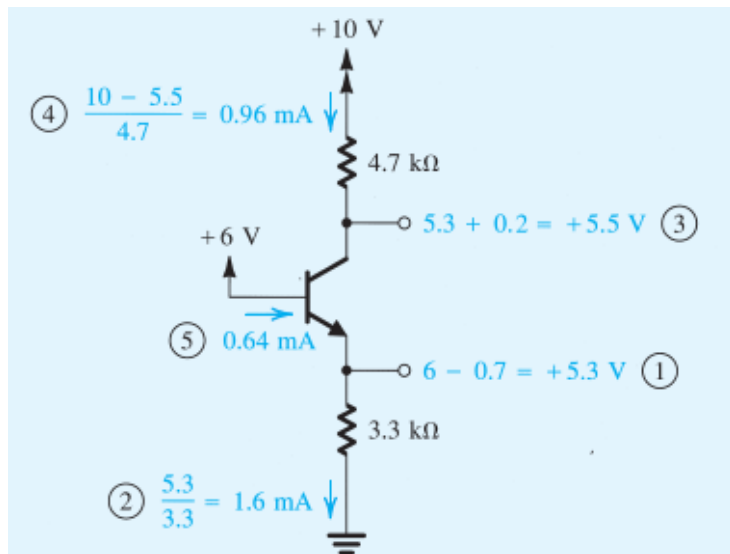
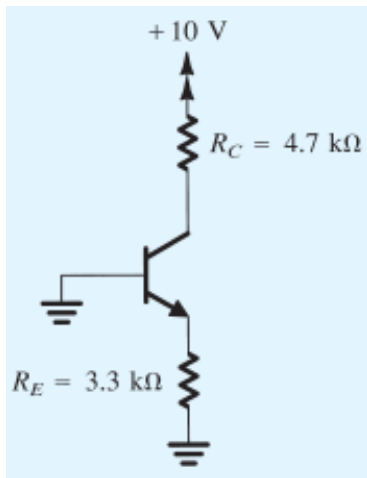
# DC Operation: Example 4


$$\beta = 100$$

Analyze this circuit to determine all node voltages and branch currents






# DC Operation: Example 4

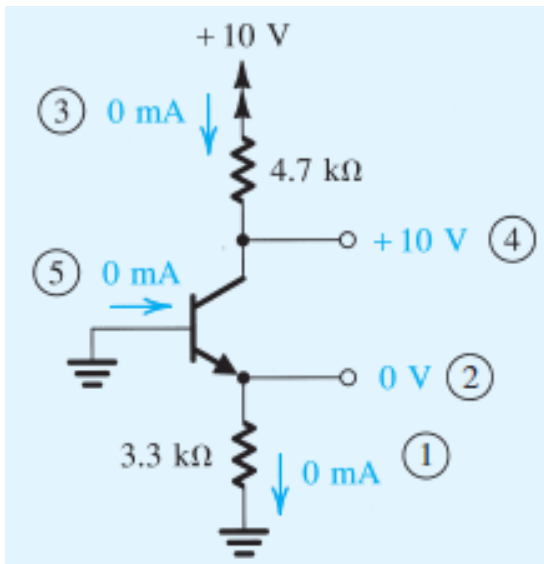

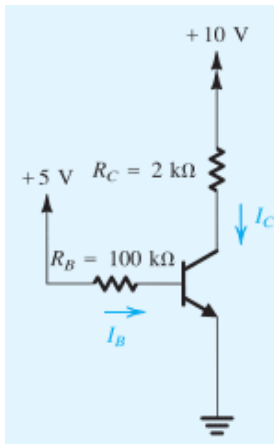
# DC Operation: Example 5

$$\beta = 50$$

Analyze this circuit to determine all node voltages and branch currents



# DC Operation: Example 5

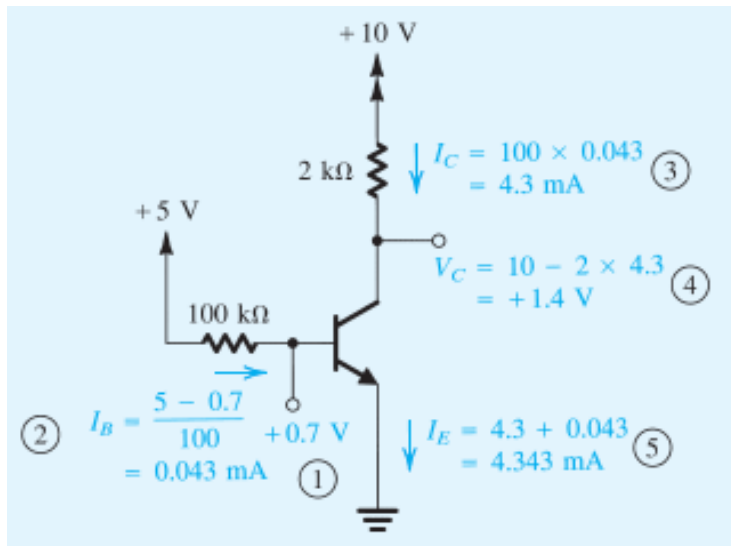



Sedra/Smith

Microelectronic Circuits, 6th Edition.

*Oxford University Press.*

# Thank You

Questions ?

samy.soliman@cu.edu.eg

<http://scholar.cu.edu.eg/samysoliman>