



ELC2020

Electronics II

CS/CD/CG Amplifiers

Dr. Omar Bakry

omar.bakry.eece@cu.edu.eg

Department of Electronics and Electrical Communications

Faculty of Engineering

Cairo University



Fall 2023




Amplifiers Review



- Large capacitors help to separate AC signal from DC bias
 - Since capacitors are large, they are considered short circuit during AC analysis ($Z_C = \frac{1}{j\omega C}$)
- DC Analysis:
 - At DC, caps are open circuit
 - Since gate current = 0, R_G will not impact V_G , DC analysis is very similar to basic common source amplifier (for this example)
 - After solving the DC analysis, calculate the small signal parameters (g_m, r_o)
- AC Analysis:
 - At AC, caps are short circuit
 - DC voltage sources are short circuit
 - DC current sources are open circuit
 - Draw small signal model and calculate G_m, Z_{out} , and A_v .

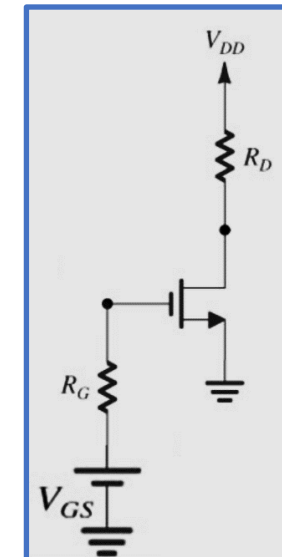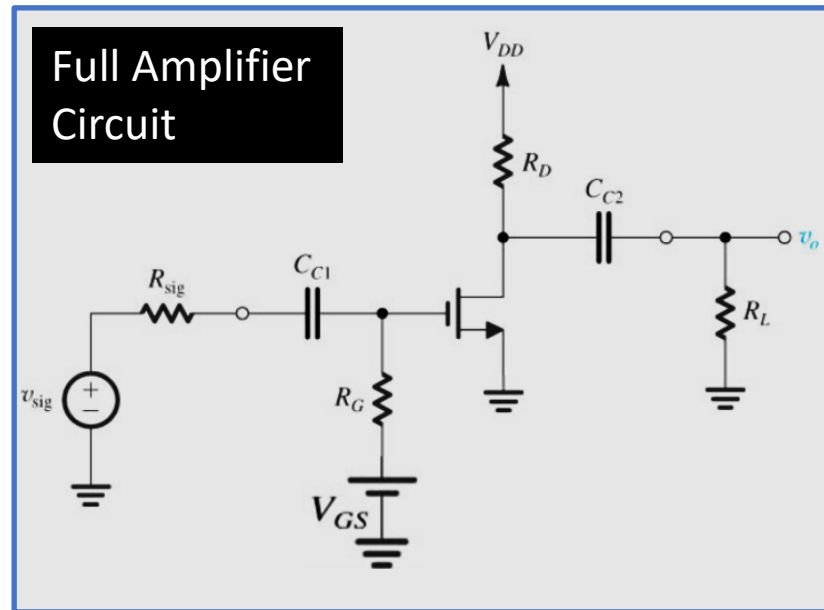

DC Analysis

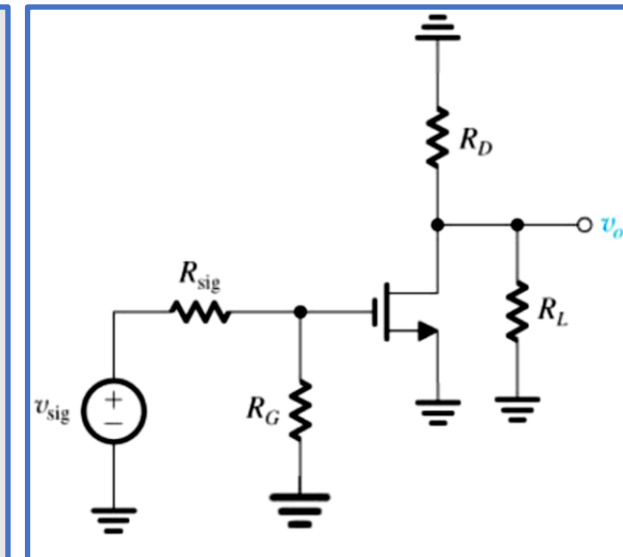


AC Analysis



Single-Ended Amplifier Summary




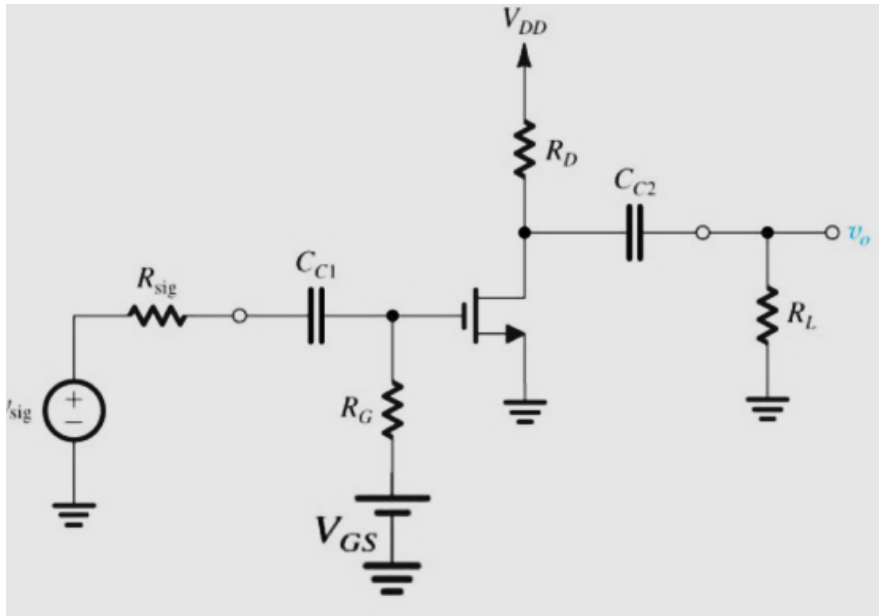- Common source amplifier: input at gate, output at drain ($r_o = \infty$)



C_c is a large cap

- S.C. for AC
- O.C. for DC

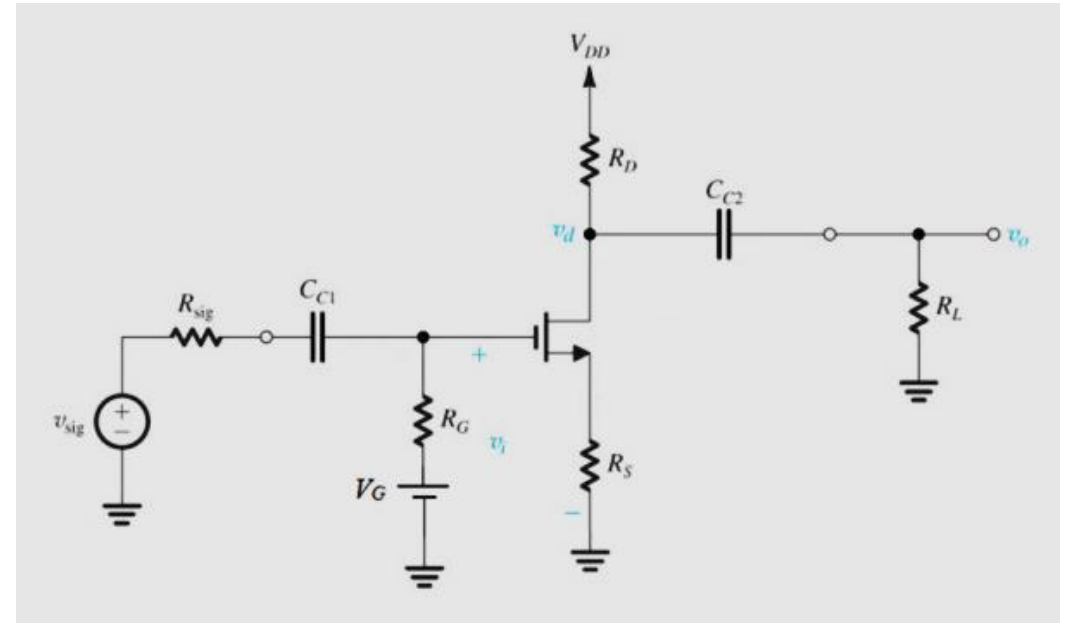

- $R_{in} = R_G$
- $R_{out} = R_D$
- $G_m = -\frac{g_m}{1+g_m R_S}$
- $A_v = -\frac{g_m R_D}{1+g_m R_S}$
- $Gain_{tot} = -\left(\frac{R_G}{R_G+R_{sig}}\right) \frac{g_m}{1+g_m R_S} (R_L || R_D)$

- $R_{in} = R_G$
- $R_{out} = R_D$
- $G_m = -g_m$
- $A_v = -g_m R_D$


$$Gain_{tot} = -\left(\frac{R_G}{R_G+R_{sig}}\right) g_m (R_D || R_L)$$



Single-Ended Amplifier Summary




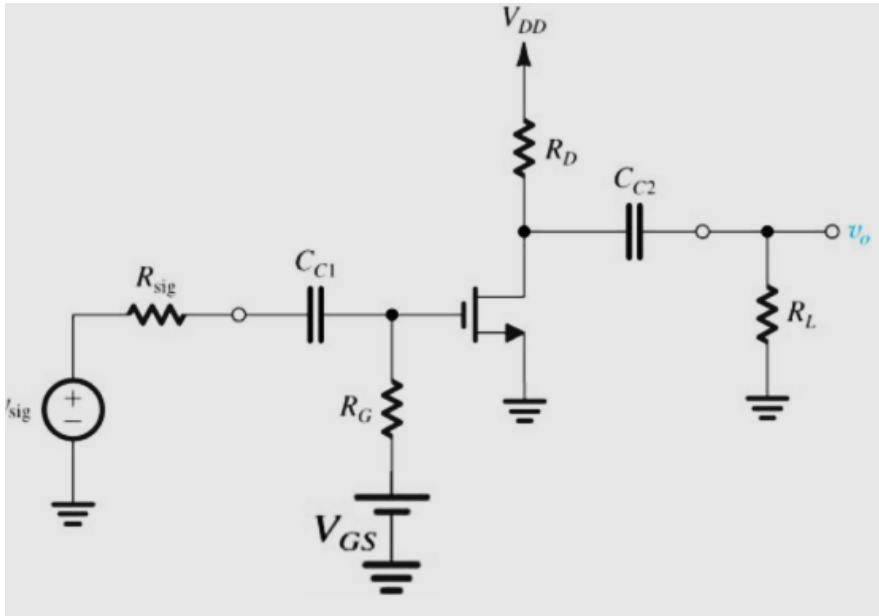- Common source amplifier: input at gate, output at drain ($r_o \neq \infty$)



C_c is a large cap

- S.C. for AC
- O.C. for DC

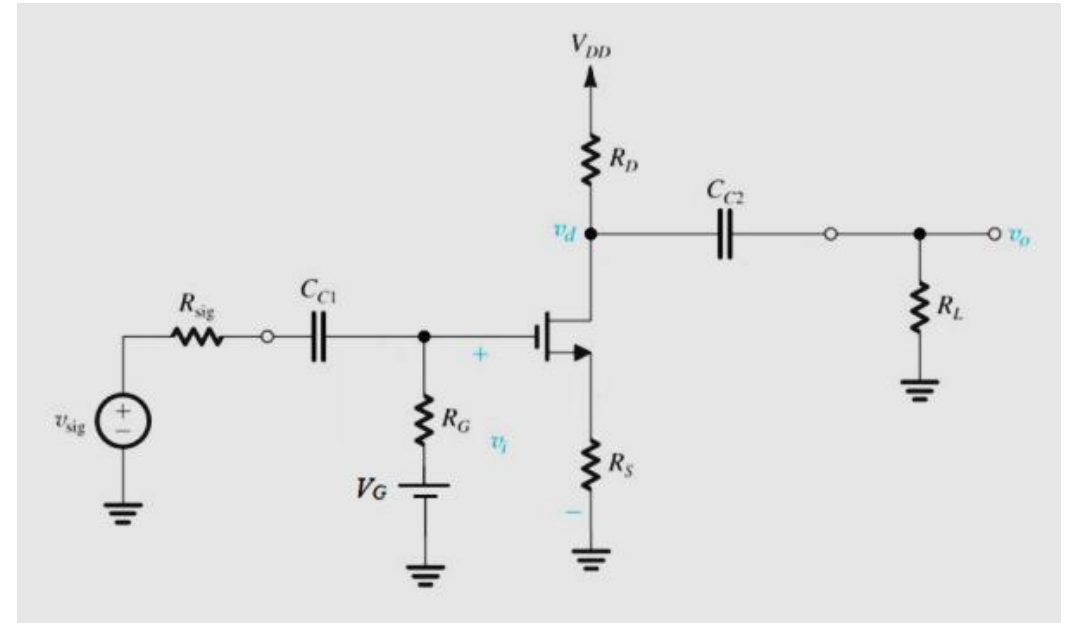

- $R_{in} = R_G$
- $R_{out} = R_D || r_o$
- $G_m = -g_m$
- $A_v = -g_m(R_D || r_o)$
- $Gain_{tot} = -\left(\frac{R_G}{R_G + R_{sig}}\right) g_m(R_D || r_o || R_L)$


- $R_{in} = R_G$
- $R_{out} = R_D || (r_o + (1 + g_m r_o) R_S)$
- $G_m = -\frac{g_m}{1 + g_m R_S}$
- $A_v = -\frac{g_m}{1 + g_m R_S} [R_D || (r_o + (1 + g_m r_o) R_S)]$
- $Gain_{tot} = -\left(\frac{R_G}{R_G + R_{sig}}\right) \frac{g_m}{1 + g_m R_S} [R_L || R_D || (r_o + (1 + g_m r_o) R_S)]$



Single-Ended Amplifier Summary



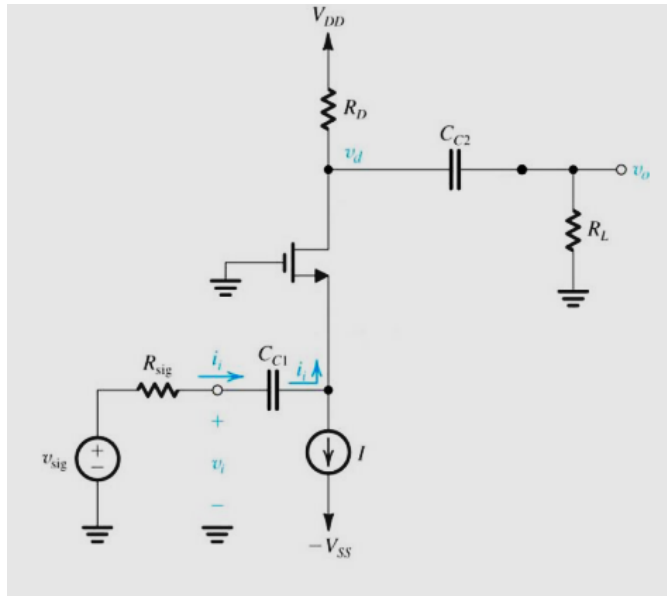- Common gate amplifier: input at source, output at drain ($r_o = \infty$)




C_c is a large cap

- S.C. for AC
- O.C. for DC

- $R_{in} = 1/g_m$
- $R_{out} = R_D$
- $G_m = g_m$
- $A_v = g_m R_D$
- $Gain_{tot} = \left(\frac{1/g_m}{1/g_m + R_{sig}} \right) g_m (R_D || R_L)$

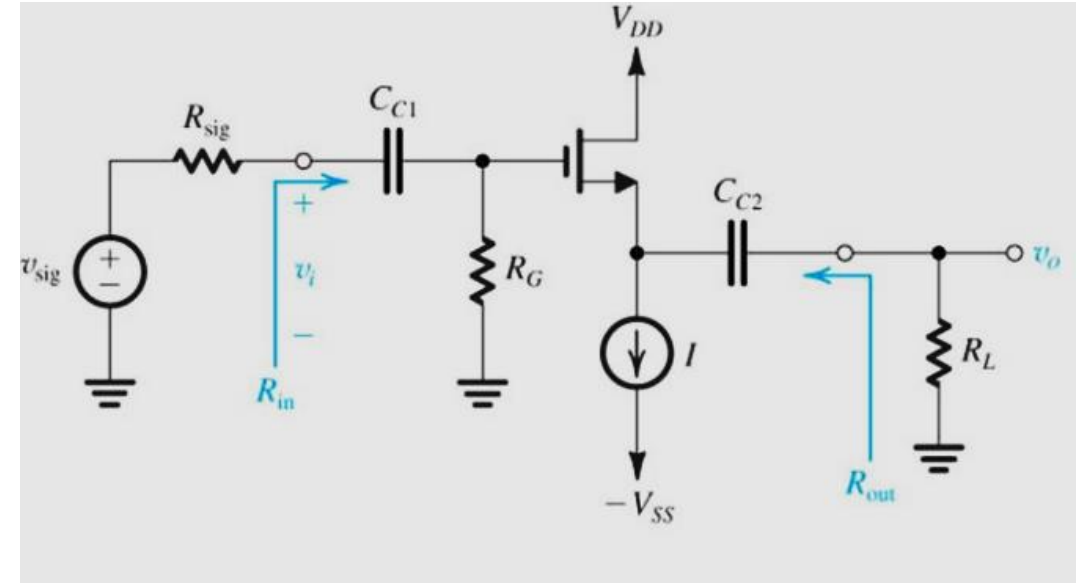- Common drain amplifier (source follower): input at gate, output at source ($r_o = \infty$)



- $R_{in} = R_G$
- $R_{out} = 1/g_m$
- $G_m = g_m$
- $A_v = \frac{g_m}{g_m} = 1$
- $Gain_{tot} = \left(\frac{R_G}{R_G + R_{sig}} \right) g_m \left(R_L || \frac{1}{g_m} \right) = \left(\frac{R_G}{R_G + R_{sig}} \right) \frac{g_m R_L}{1 + g_m R_L}$



Example 1




- Calculate amplifier gain given that:

$$K' = \frac{0.2mA}{V^2}, V_{TH} = 0.5V, V_{DD} = 2V, V_{GS} = 1V, R_D = 4k\Omega, \frac{W}{L} = 10$$

- Solution:

- $I_D = \frac{k}{2} (V_{GS} - V_t)^2 = 0.25mA$
- $V_D = V_{DD} - I_D R_L = 1V > V_{GS} - V_t$ (sat region)
- $g_m = K(V_{GS} - V_t) = 1mA/V$
- $Gain = -g_m R_L = -4$

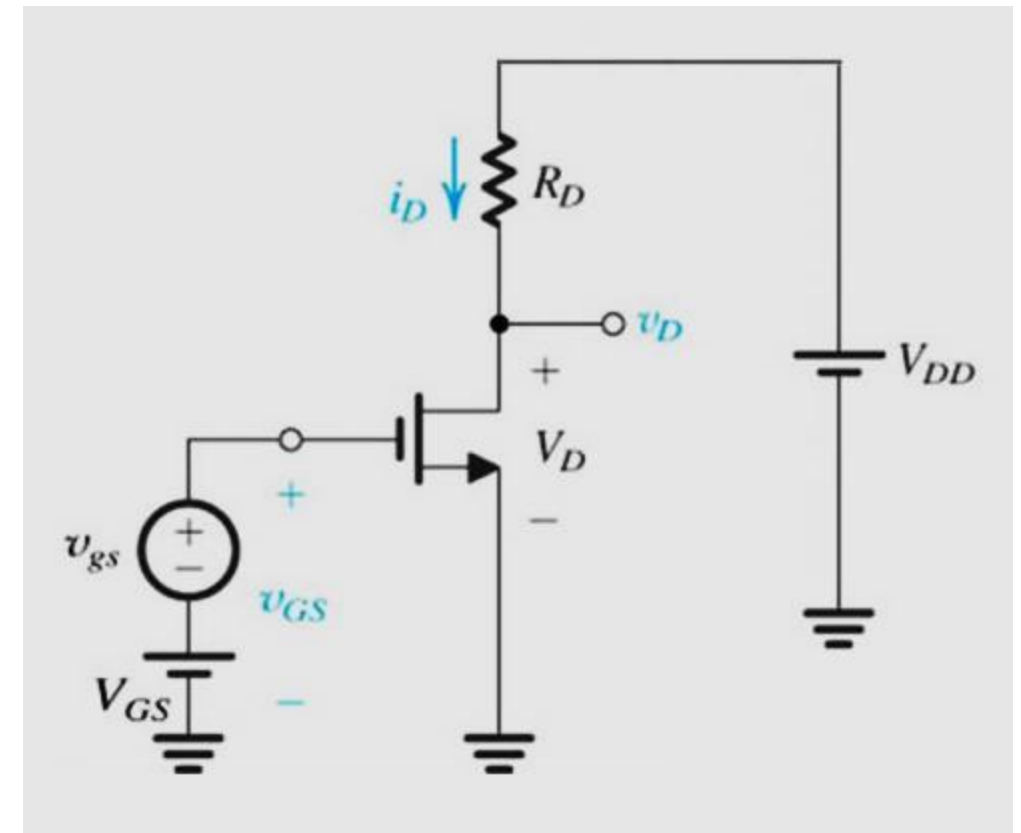




Example 2



- Calculate amplifier gain.
- DC Analysis:
 - $I_D = \frac{K}{2} (V_{GS} - V_{TH})^2$
 - $V_{GS} = V_G - I_D R_S$
 - $I_D = \frac{K}{2} (V_G - I_D R_S - V_{TH})^2 = 0.5(1.5 - I_D)^2$
 - $I_D^2 - 5I_D + 2.25 = 0$
 - $I_D = 4.5mA \rightarrow \text{rejected as } V_{DS} < 0$
 - $I_D = 0.5mA$
 - $g_m = \sqrt{2KI_D} = \frac{1mA}{V}$
 - $V_{DS} = V_{DD} - I_D R_D - I_D R_S = 1.5V > V_{GS} - V_{TH}$

- AC Analysis:
 - $A_v = -\frac{g_m R_D}{1 + g_m R_S} = -\frac{6}{1+1} = -3V/V$
 - $Gain_{tot} = -\left(\frac{R_G}{R_G + R_{sig}}\right) \frac{g_m}{1 + g_m R_S} (R_L || R_D) = -\left(\frac{0.9}{0.9+0.1}\right) \frac{1}{1+1} (9||6) = -1.62V/V$

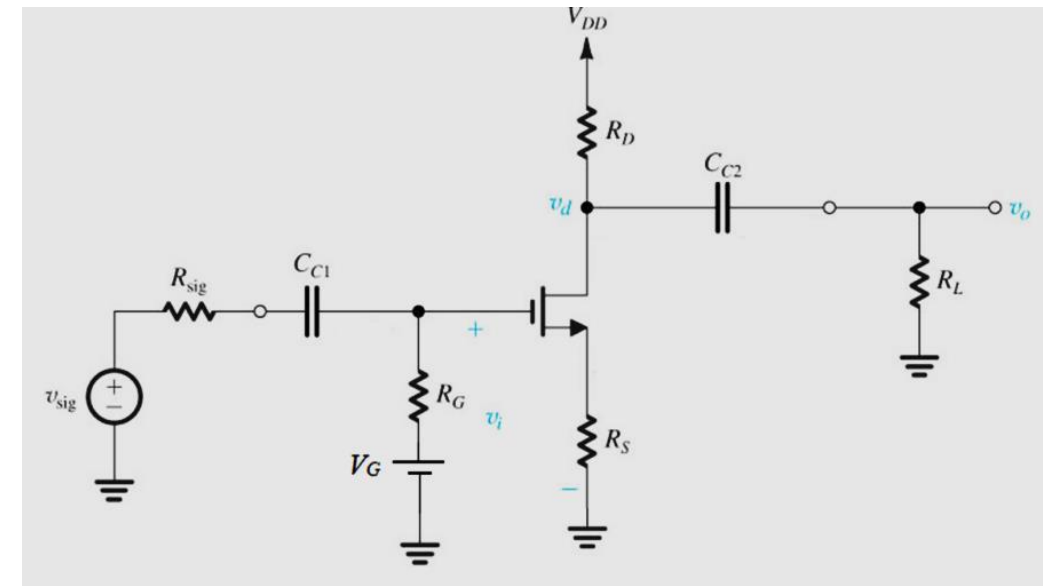

$$\begin{aligned} R_S &= 1K\Omega \\ R_D &= 6K\Omega \\ K &= \frac{1mA}{V^2} \\ V_G &= 2V, \\ V_{TH} &= 0.5V \\ V_{DD} &= 5V \\ R_{sig} &= 0.1K\Omega \\ R_G &= 0.9K\Omega \\ R_L &= 9K\Omega \\ \lambda &= 0 \end{aligned}$$



Example 3



- Calculate the overall gain.
- Assume that both transistors has $g_m = 10\text{mA/V}$, $R_D = 1\text{K}\Omega$, $R_{sig} = 0\Omega$, $R_L = 100\Omega$


• Solution:

$$\bullet \text{Gain}_{tot} = \frac{v_o}{v_i} = \frac{v_o}{v_1} \times \frac{v_1}{v_i}$$

$$\bullet \frac{v_1}{v_i} = -g_m R_D = -10\text{V/V}$$

$$\bullet \frac{v_o}{v_1} = \frac{g_m R_L}{1 + g_m R_L} = 0.5\text{V/V}$$

$$\bullet \text{Gain}_{tot} = \frac{v_o}{v_i} = \frac{v_o}{v_1} \times \frac{v_1}{v_i} = -5\text{V/V}$$


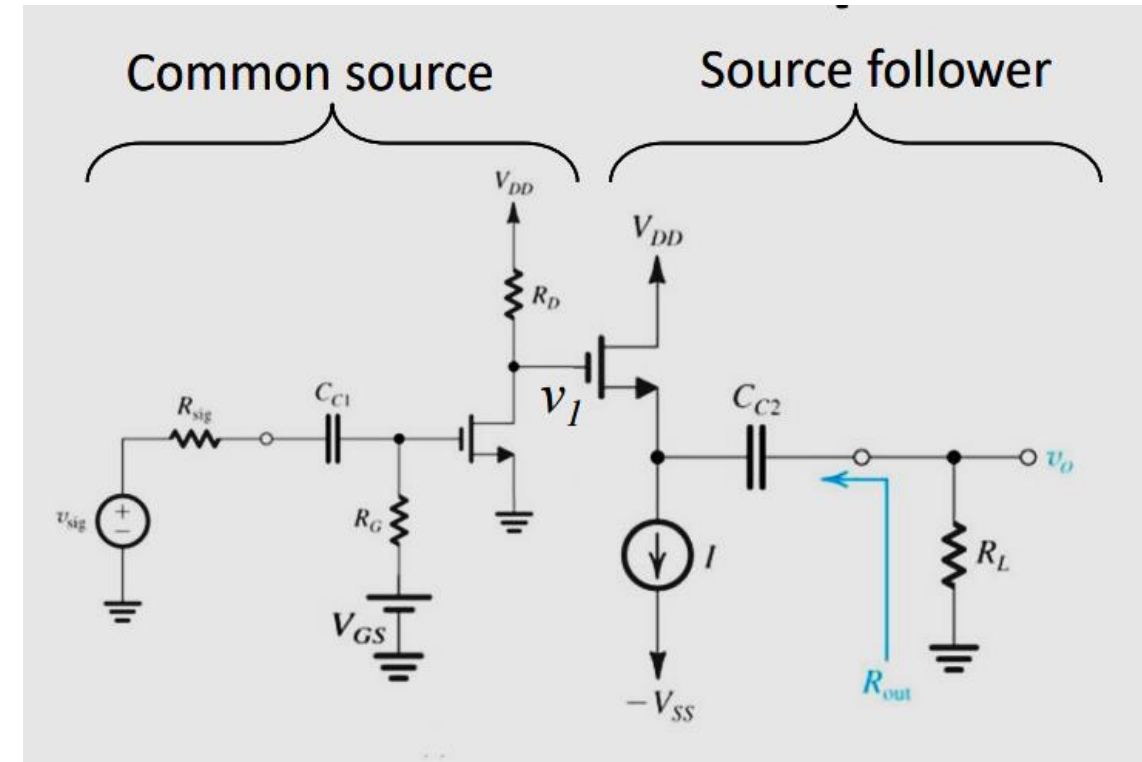




Example 4



- Derive an expression for the voltage gain. Assume M2 and M3 are identical. All transistors are in saturation. Ignore channel length modulation.
- Solutions:
- $A_v = g_m R_1$

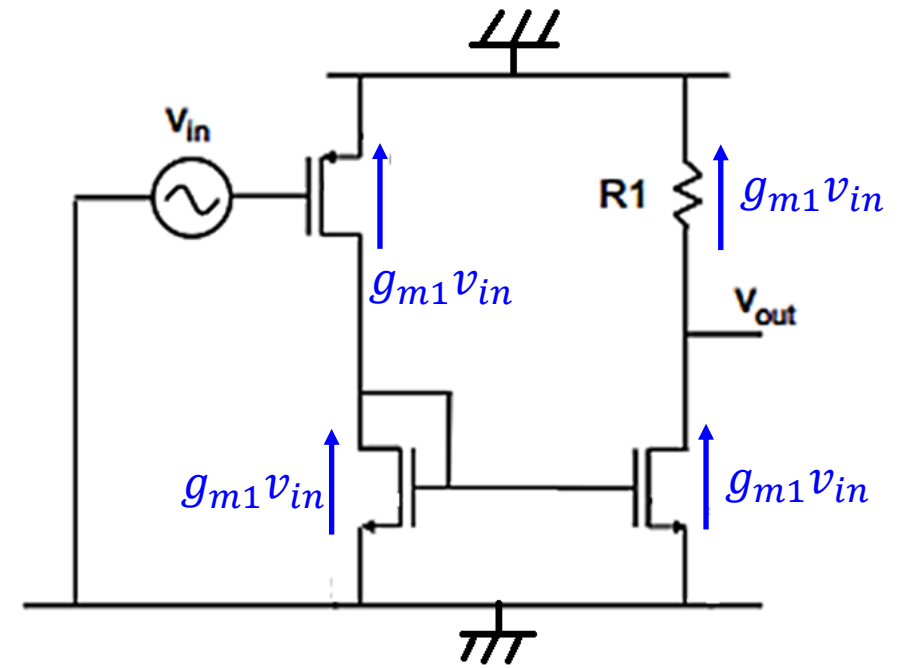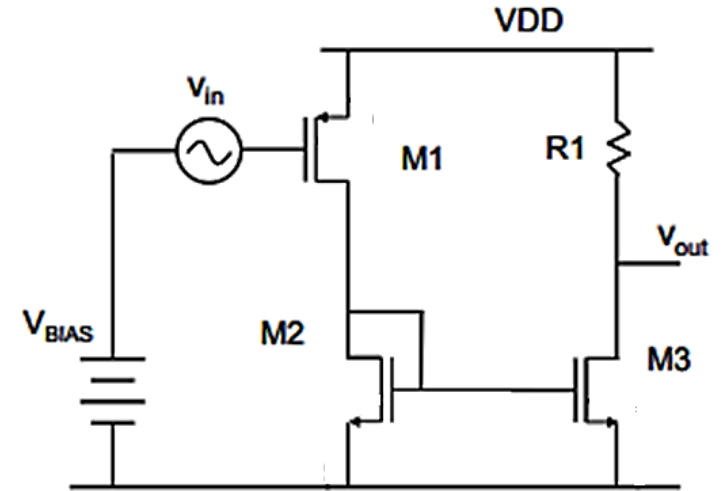



Example 5



- What is the small signal voltage gain?
 - Assume all transistors are in saturation.
 - Assume r_{o2} , r_{o3} and r_{o4} are very large.
- Solution:
 - $A_v = -g_{m4}r_{o1}$

