



ELC2020
Electronics II
Differential Amplifiers – Lecture 2

Dr. Omar Bakry

omar.bakry.eece@cu.edu.eg

Department of Electronics and Electrical Communications

Faculty of Engineering

Cairo University



Fall 2023



Response to AC Common Mode Signal




 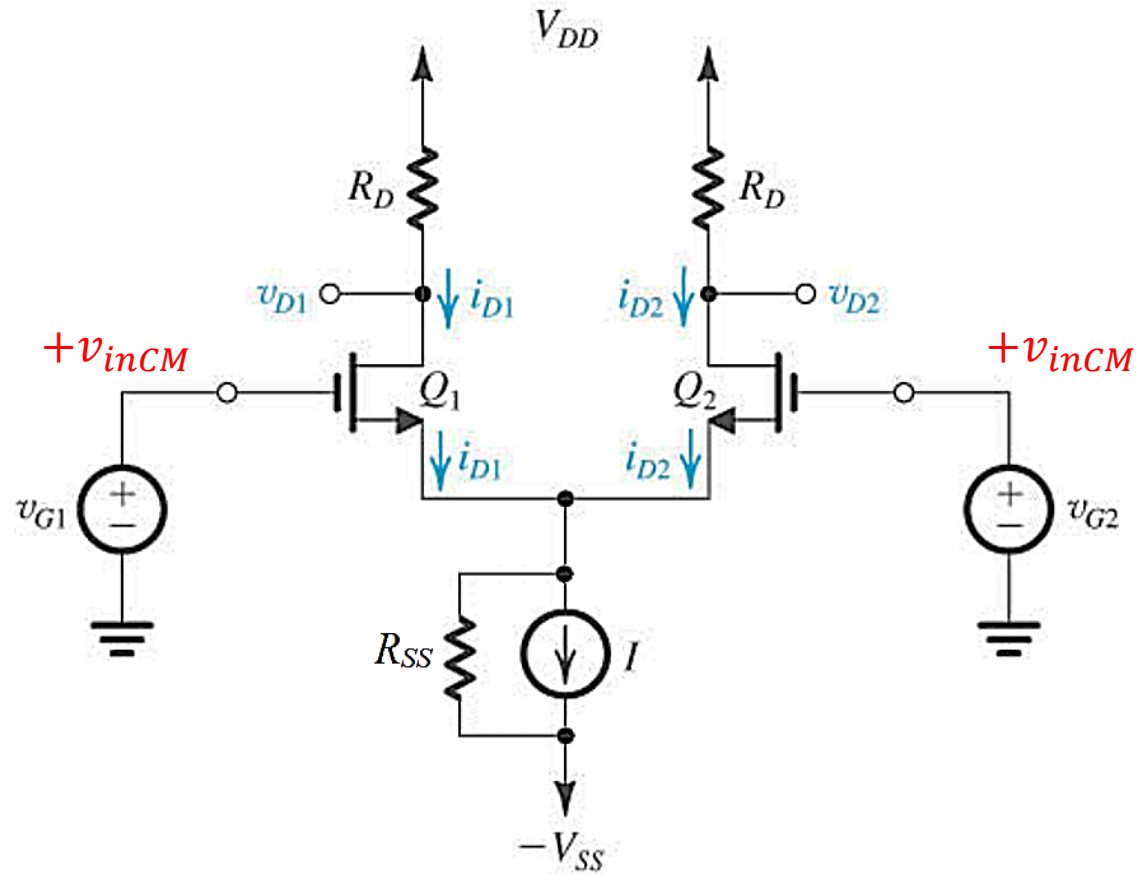- Can this circuit be simplified into two half circuits






Response to AC Common Mode Signal

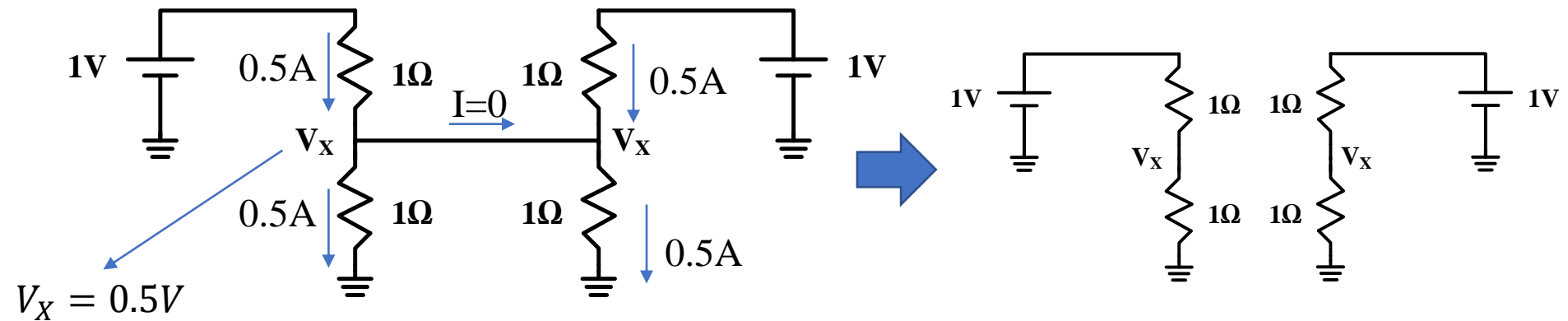

- What is the value of V_x




Response to AC Common Mode Signal

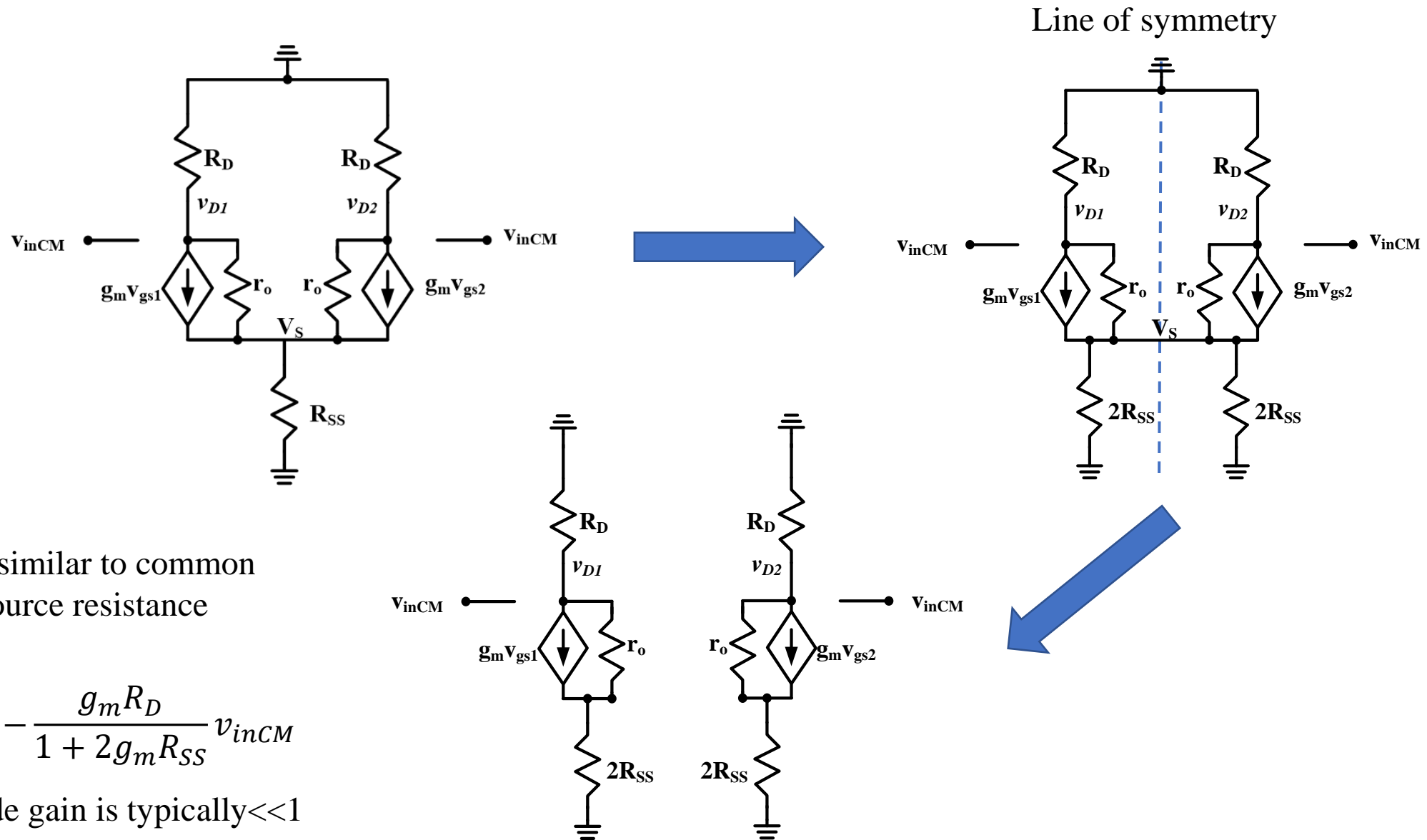



Response to AC Common Mode Signal

 

$$v_{D1} = v_{D2} = -\frac{g_m R_D v_{inCM}}{1 + 2g_m R_{SS}} \approx -\frac{R_D}{2R_{SS}} v_{inCM} \text{ (if } 2g_m R_{SS} \gg 1)$$




Common Mode Rejection Ratio (CMRR)



- Being insensitive to common mode signals is one of the main advantages of the differential pair.
- CMRR is a measure of how ideal the differential pair is:

$$CMRR = \frac{|A_{DM}|}{|A_{CM}|}$$

 - Ideally, CMRR goes to infinity.
- Factors degrading CMRR:
 - Mismatches between MOS, Resistors, current sources,
 - Tail current output resistance.





CMRR: Common Mode Rejection Ratio




- As long as the circuit is symmetric CM variations remains CM
- What is the impact of common mode variations in the presence of circuit asymmetry?
- In case the resistors are mismatched due to fabrication, and neglecting the channel length modulation:

$$\frac{V_{out1}}{V_{in,CM}} = -\frac{R_D}{1/g_m + 2R_{SS}}, \frac{V_{out2}}{V_{in,CM}} = -\frac{R_D + \Delta R_D}{1/g_m + 2R_{SS}}$$

$$V_{out,DM} = V_{out1} - V_{out2} = -\frac{\Delta R_D}{1/g_m + 2R_{SS}} V_{in,CM}$$

 - In the presence of mismatches, input common mode variations introduce a differential component at the output!
- Could lead to input common mode noise appearing at the differential output




$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \frac{g_m R_D}{\Delta R_D / (1/g_m + 2R_{SS})} = \frac{R_D + 2g_m R_{SS} R_D}{\Delta R_D} \approx \frac{2g_m R_{SS} R_D}{\Delta R_D}$$



Differential Pair Summary




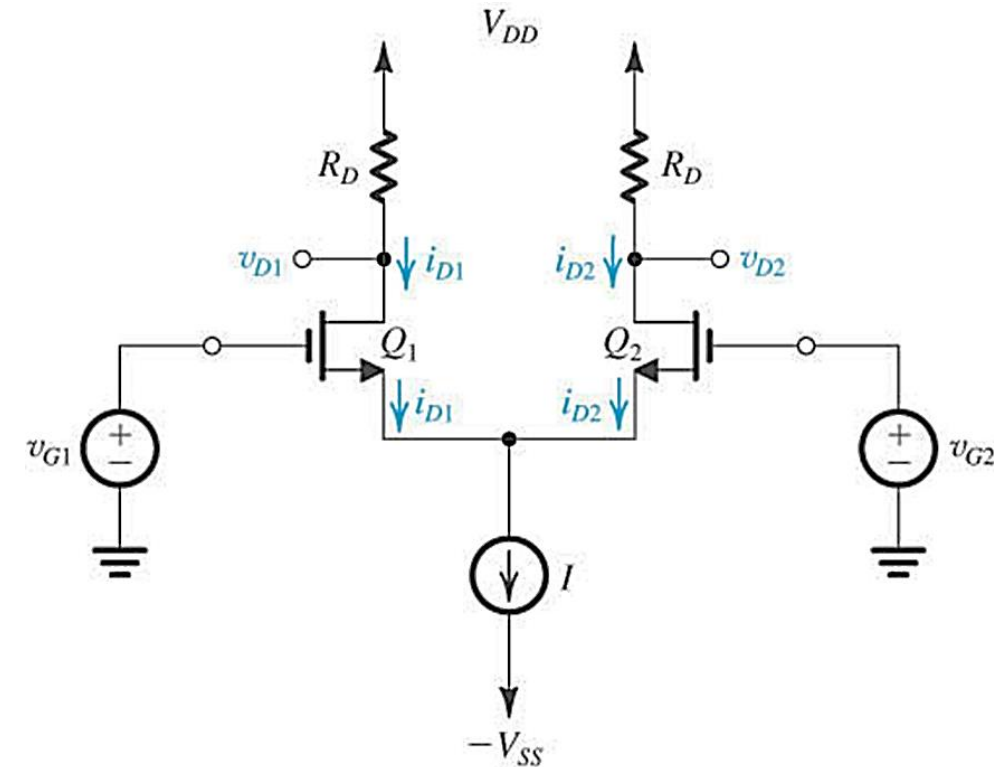- Differential pair rejects common mode noise
- DC voltage is the same on both sides
- Small signal input can be written as common mode component and differential mode component (superposition can be used)
- For differential mode, source node voltage = 0V due to symmetry
- For common mode, circuit can be split into two half circuits due to symmetry (no current from left half to right half)





Half-Circuit Analysis – Example


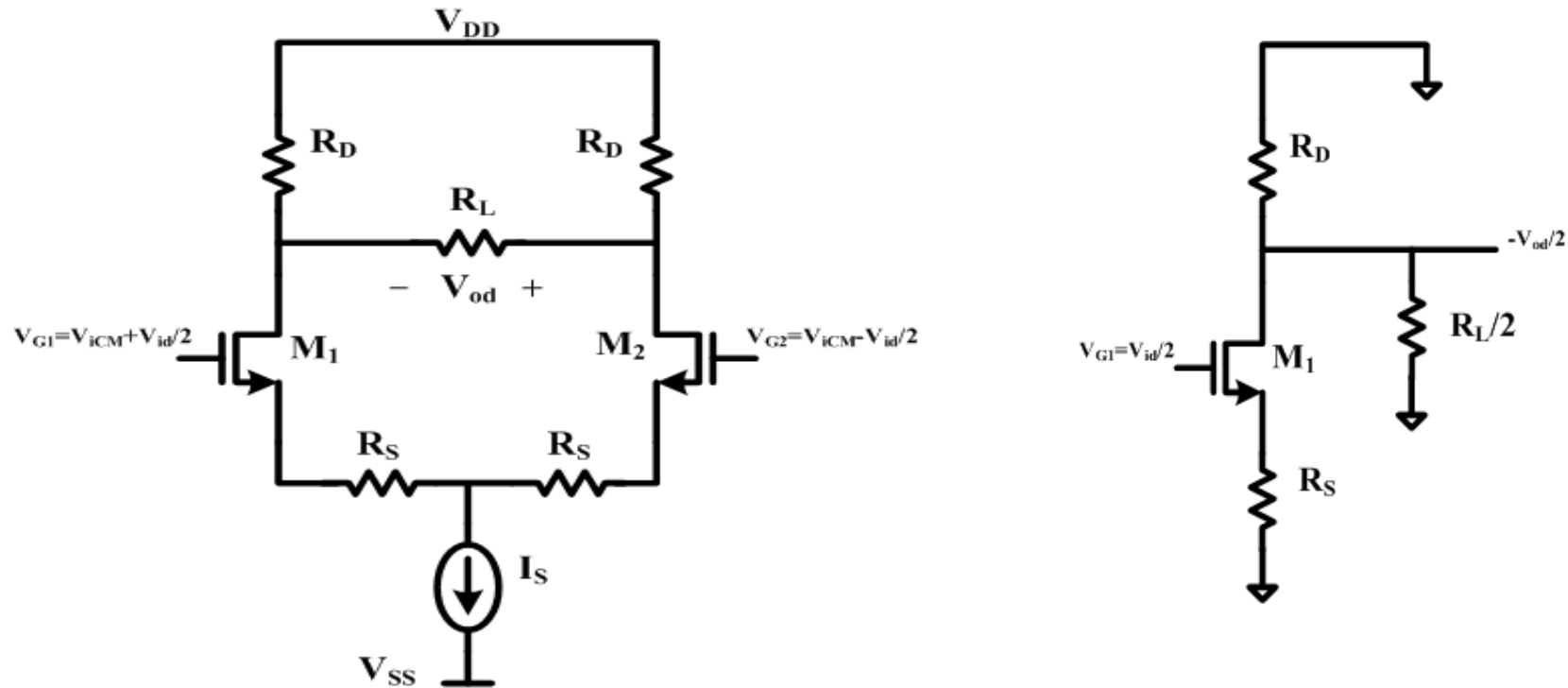


$$\frac{V_{od}}{2} = -G_m \frac{V_{id}}{2} (R_D // \frac{R_L}{2}) = -\frac{g_{m1}}{1 + g_{m1} R_S} \frac{V_{id}}{2} (R_D // \frac{R_L}{2})$$

$$A_d = \frac{V_{od2} - V_{od1}}{V_{id}} = \frac{-V_{od}}{V_{id}} = \frac{g_{m1}}{1 + g_{m1} R_S} (R_D // \frac{R_L}{2})$$



Current Source Load

  

Taking r_o into account, and assuming $r_{o1} = r_{o2}$, and $r_{o3} = r_{o4}$:


$$A_d = g_{m1}(r_{o1} // r_{o3})$$



MOS Differential Pair with Active Load





 - High output impedance
- Single ended output
- Assume Q1 and Q2 has same g_m and r_o
 $g_{m1} = g_{m2} = g_{mn}, r_{o1} = r_{o2} = r_{on}$
- Assume Q3 and Q4 has same g_m and r_o
 $g_{m3} = g_{m4} = g_{mp}, r_{o3} = r_{o4} = r_{op}$





MOS Differential Pair with Active Load

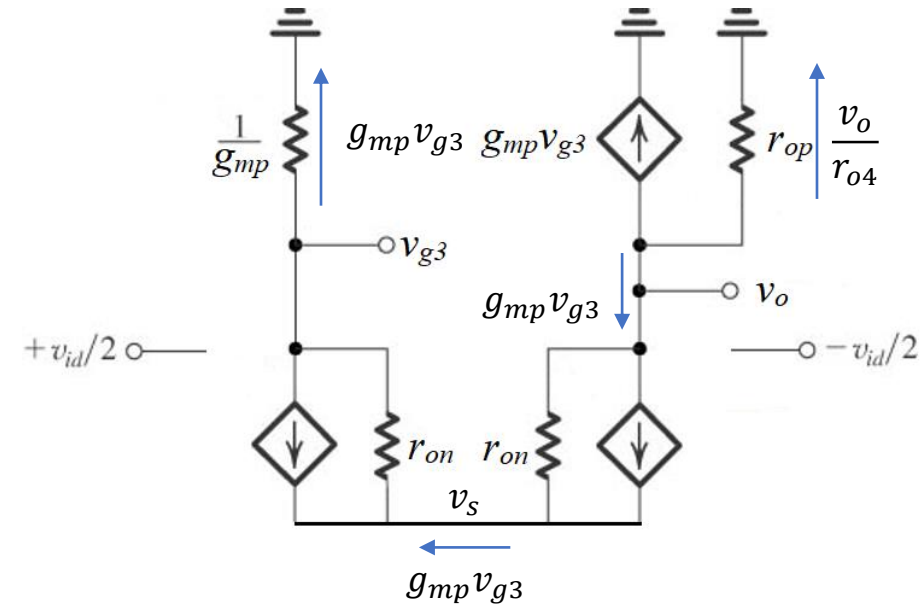 


- KCL at output node $\rightarrow g_{mp}v_{g3} + g_{mp}v_{g3} + \frac{v_o}{r_{op}} = 0 \rightarrow v_{g3} = -\frac{v_o}{2g_{mp}r_{op}}$
- KCL at output node $\rightarrow g_{mp}v_{g3} = \frac{v_o - v_s}{r_{on}} + g_{mn}\left(-\frac{v_{id}}{2} - v_s\right) \dots (1)$
- KCL at v_{g3} node $\rightarrow -g_{mp}v_{g3} = \frac{v_{g3} - v_s}{r_{on}} + g_{mn}\left(\frac{v_{id}}{2} - v_s\right) \dots (2)$
- Subtract (1)-(2) $\rightarrow 2g_{mp}v_{g3} = \frac{v_o - v_{g3}}{r_{on}} - g_{mn}v_{id}$, use $v_{g3} = -\frac{v_o}{2g_{mp}r_{op}} \rightarrow v_o \approx g_{mn}(r_{on} \parallel r_{op})$
- Note that v_s is not 0V (you can prove $v_s \sim v_{id}/4$)



MOS Differential Pair with Active Load



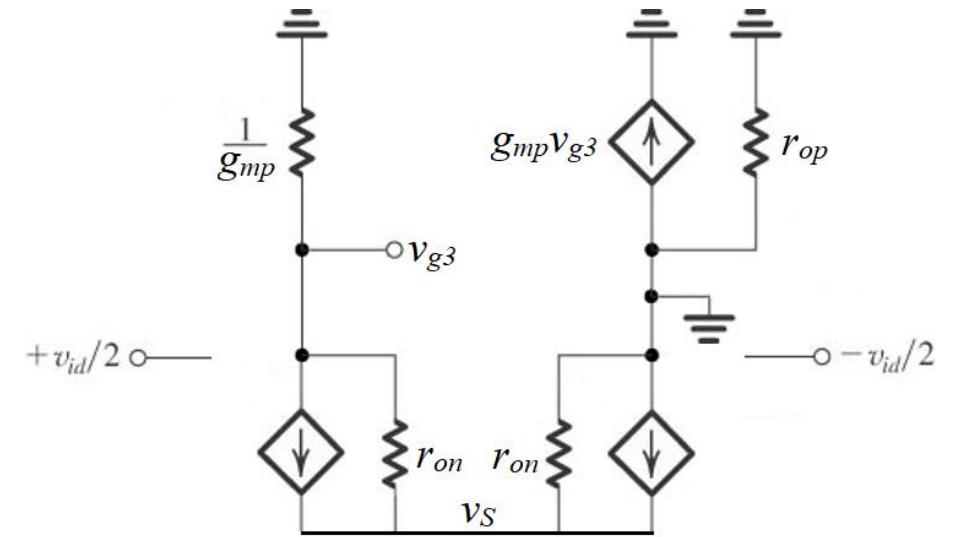- To get differential gain
 - Calculate transconductance G_m
 - Calculate R_{out}
 - $\text{Gain} = G_m R_{out}$
- Circuit is not symmetrical, half circuit concept cannot be used
 - When calculating G_m , output is short circuit to ground, v_S will be close to 0V (Need to prove it first, write KCL at v_{g3} and v_S nodes and get v_S as a function of v_{id})






MOS Differential Pair with Active Load



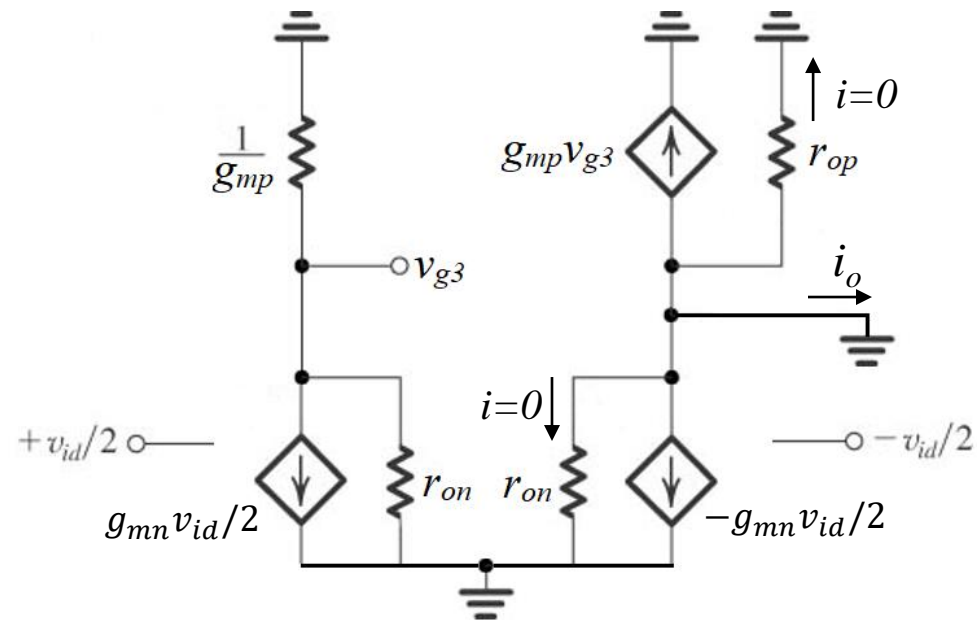- $v_{g3} \approx -\frac{g_{mn}}{g_{mp}} \frac{v_{id}}{2}, i_o = \frac{g_{mn}v_{id}}{2} - g_{mp}v_{g3} = g_{mn}v_{id}$
- Hence $G_m = g_{mn}$






MOS Differential Pair with Active Load




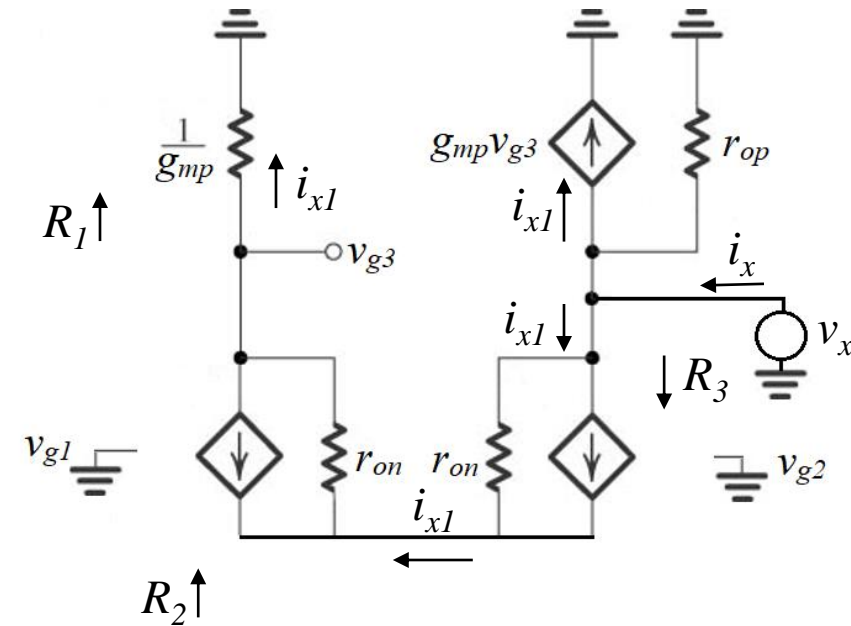- $v_{g3} = \frac{i_{x1}}{g_{mp}}$
- $i_x = 2i_{x1} + \frac{V_x}{r_{op}}$






MOS Differential Pair with Active Load

 

 
$$R_2 = \frac{r_{on} + 1/g_{mp}}{g_{mn}r_{on}} \approx \frac{1}{g_{mn}}$$






MOS Differential Pair with Active Load

 
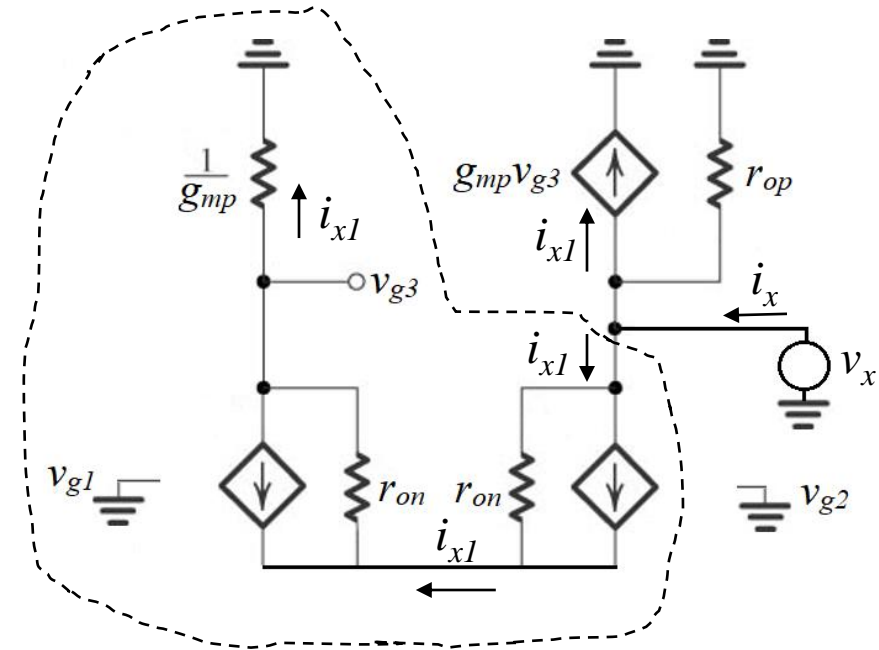
$$R_3 = r_{on} + R_2 + g_{mn}r_{on}R_2 \approx 2r_{on}$$






MOS Differential Pair with Active Load



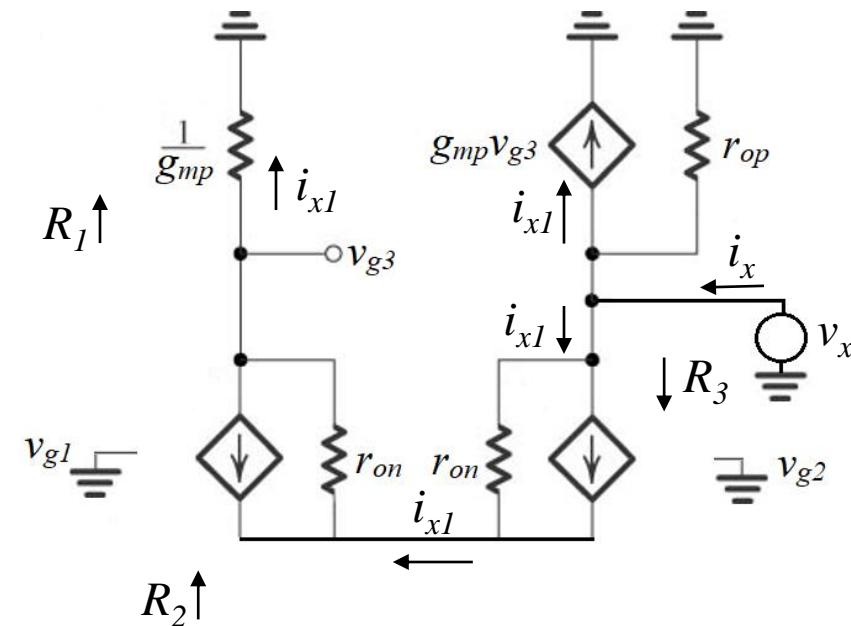- $R_1 = \frac{1}{g_{mp}}$
- $R_2 = \frac{r_{on} + 1/g_{mp}}{g_{mn}r_{on}} \approx \frac{1}{g_{mn}}$
- $R_3 = r_{on} + R_2 + g_{mn}r_{on}R_2 \approx 2r_{on}$
- $i_{x1} = \frac{V_x}{R_3}$
- $i_x = 2i_{x1} + \frac{V_x}{r_{op}} = 2\frac{V_x}{R_3} + \frac{V_x}{r_{op}} = \frac{V_x}{r_{on} \parallel r_{op}}$
- $R_{out} = r_{on} \parallel r_{op}$
- $A_{dm} = G_m R_{out} = g_{mn}r_{on} \parallel r_{op}$





Common Mode Gain Analysis



- Neglecting r_{on} , KCL at source node

$$v_S = 2g_{mn}(v_{iCM} - v_S)R_{SS}$$

$$v_S = \frac{2g_{mn}R_{SS}v_{iCM}}{1 + 2g_{mn}R_{SS}}$$

$$v_{gs} = \frac{v_{iCM}}{1 + 2g_{mn}R_{SS}}$$

- $v_{g3} = -\frac{g_{mn}v_{iCM}}{1 + 2g_{mn}R_{SS}} \left(\frac{1}{g_{mp}} \parallel r_{op} \right)$

- KCL at output node

$$\frac{g_{mn}v_{iCM}}{1 + 2g_{mn}R_{SS}} + g_{mp}v_{g3} + \frac{v_o}{r_{op}} = 0$$

$$v_o = -\frac{g_{mn}v_{iCM}}{1 + 2g_{mn}R_{SS}} \frac{r_{op}}{1 + g_{mp}r_{op}} \approx -\frac{1}{2g_{mp}R_{SS}} v_{iCM}$$

$$A_{cm} = \frac{v_o}{v_{iCM}} = -\frac{1}{2g_{mp}R_{SS}}$$

