



ELC1010

Electric Circuits (I) – Circuit Theory

Part (II) – AC Circuits Lecture (2)

Dr. Omar Bakry

omar.bakry.eece@cu.edu.eg

Department of Electronics and Electrical Communications

Faculty of Engineering

Cairo University

Fall 2023



Outline



- V/I Phasor Relationship for R,L and C components.
- Method of solutions in phasor domain
- KCL, KVL in Phasor domain
- Parallel/series combinations
- Voltage/current divider
- Star/delta conversion
- Examples



Circuit elements and phasors





- We need to find out how R , L , and C affect the magnitude and phase relationships between \mathbf{V} and \mathbf{I} .
- Once we do this, maybe we can rewrite ohm's law in the complex domain and do everything we did for DC exactly the same way
 - This is valid ONLY for steady-state sinusoid stimulus
- But when we rewrite ohm's law, maybe we will find a new definition for the constant of proportionality
 - This defines impedances and reactances



Phasor Relationship for Resistor



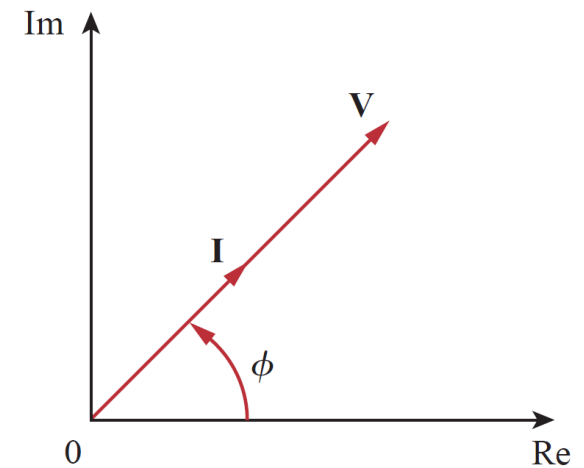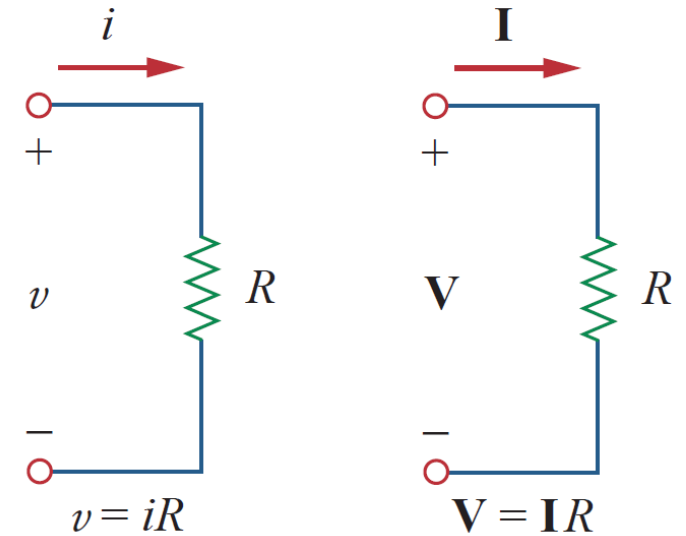- Resistor current:
 - $i = I_m \cos(\omega t + \Phi) = \text{Re}\{I_m e^{j(\omega t + \phi)}\}$
 - $I = I_m \angle \Phi$
- Resistor voltage:
 - $v = iR = RI_m \cos(\omega t + \Phi)$
 - $v = R \times \text{Re}\{I_m e^{j(\omega t + \phi)}\}$
 - $V = RI_m \angle \Phi$
- Phasor relation:
 - $V = RI$
 - V & I are in phase







Phasor Relationship for Inductor



- Inductor current:
 - $i = I_m \cos(\omega t + \Phi) = \text{Re}\{I_m e^{j(\omega t + \Phi)}\}$
 - $I = I_m \angle \Phi$
- Inductor voltage:
 - $v = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \Phi)$
 - $v = \omega L I_m \cos(\omega t + \Phi + 90^\circ)$
 - $v = \text{Re}\{\omega L I_m e^{j(\omega t + \Phi + 90^\circ)}\}$
 - $V = \omega L I_m \angle(\Phi + 90^\circ) = j\omega L I_m \angle \Phi$
- Phasor relation:
 - $V = j\omega L \times I$
 - I lags V by 90°

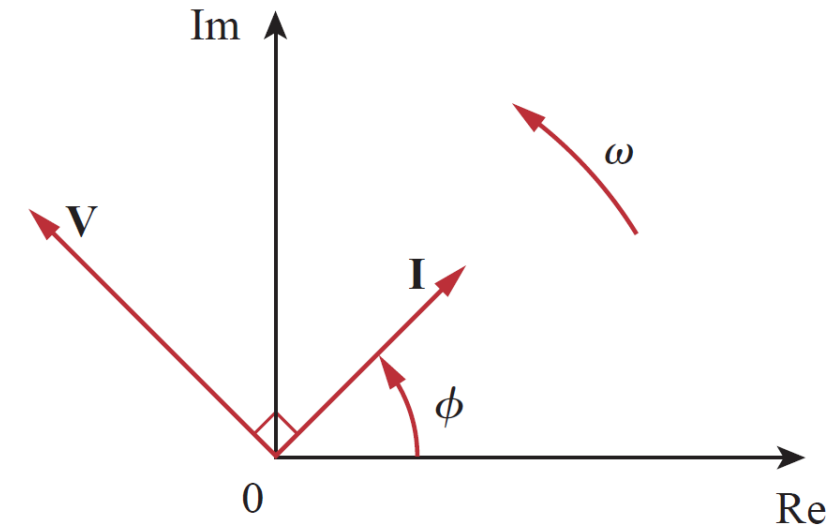
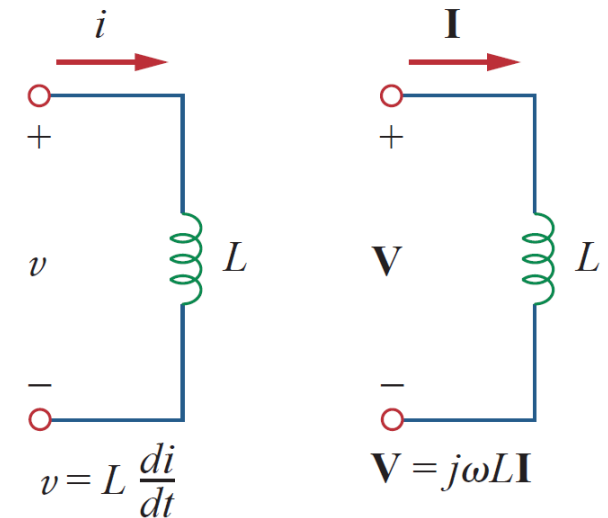




Phasor Relationship for Capacitor



- Capacitor voltage:
 - $v = V_m \cos(\omega t + \Phi) = \text{Re}\{V_m e^{j(\omega t + \Phi)}\}$
 - $V = V_m \angle \Phi$
- Capacitor current:
 - $i = C \frac{dv}{dt} = -\omega C V_m \sin(\omega t + \Phi)$
 - $i = \omega C V_m \cos(\omega t + \Phi + 90^\circ)$
 - $i = \text{Re}\{\omega C V_m e^{j(\omega t + \Phi + 90^\circ)}\}$
 - $I = \omega C V_m \angle(\Phi + 90^\circ) = j\omega C V_m \angle \Phi$
- Phasor relation:
 - $I = j\omega C \times V \rightarrow V = \frac{1}{j\omega C} I$
 - I leads V by 90°

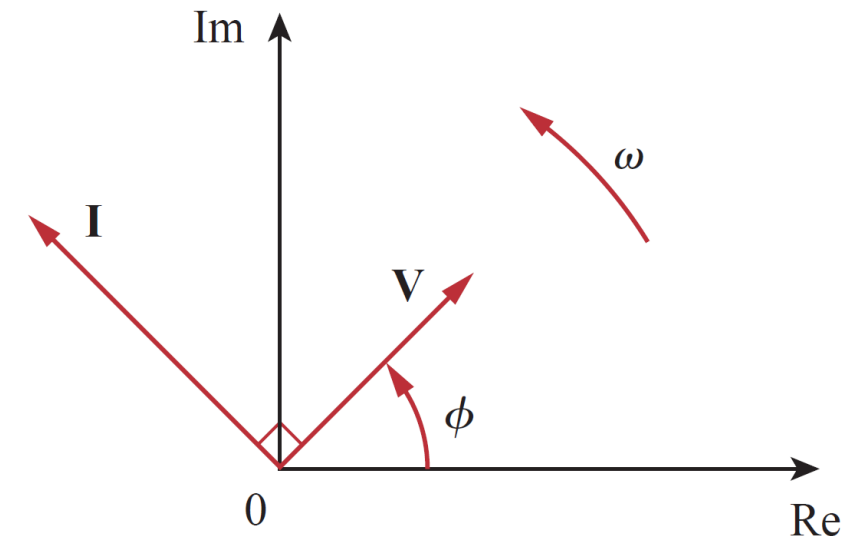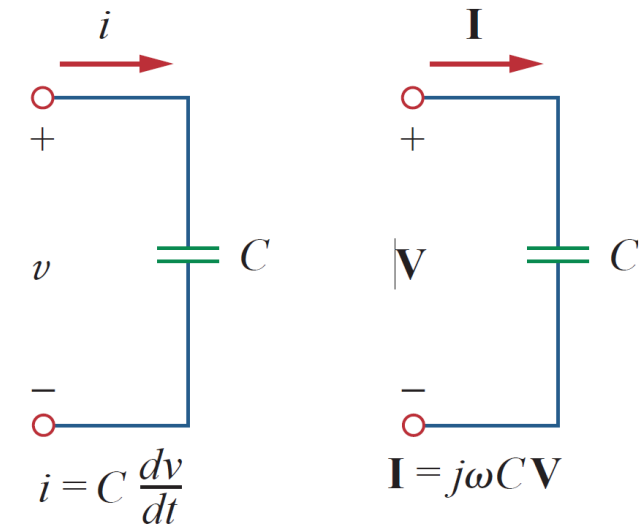



Summary of voltage-current relationships




Element	Time domain	Frequency domain
R	$v = Ri$	$\mathbf{V} = R\mathbf{I}$
L	$v = L \frac{di}{dt}$	$\mathbf{V} = j\omega L\mathbf{I}$
C	$i = C \frac{dv}{dt}$	$\mathbf{V} = \frac{\mathbf{I}}{j\omega C}$



Impedance and Admittance




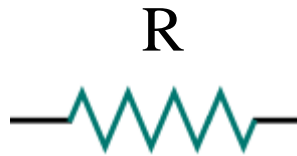- The impedance Z of a circuit is the ratio of the phasor voltage V to the phasor current I , measured in ohms (Ω)
- Ohm's law is now $V = IZ$, always and for everyone
- Just calculate the right Z




$$V = RI$$

$$Z = R$$

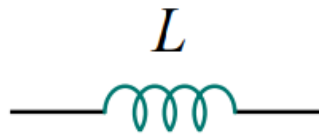

$$V = j\omega LI$$

$$Z = j\omega L$$

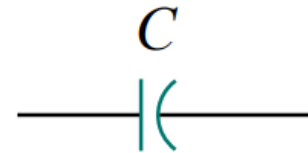

$$V = \frac{I}{j\omega C}$$


$$Z = \frac{1}{j\omega C}$$



Impedance and Admittance




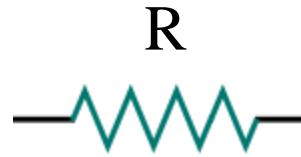- The admittance Y of a circuit is the ratio of the phasor current I to the phasor voltage V , measured in siemens (S or Ω^{-1})




$$I = V/R$$

$$Y = \frac{1}{R}$$

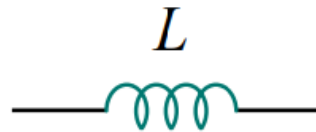

$$I = \frac{V}{j\omega L}$$

$$Y = \frac{1}{j\omega L}$$

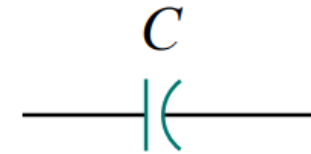

$$I = j\omega CV$$

$$Y = j\omega C$$



Impedance and Admittance



- For a circuit with multiple elements, the equivalent Z can be calculated using parallel and series combinations. It ends up being a complex number.
- Impedance $\mathbf{Z} = \mathbf{R} + j\mathbf{X}$
 - \mathbf{R} is the equivalent, while \mathbf{X} is the reactance
 - \mathbf{Z} is inductive if \mathbf{X} is +ve
 - \mathbf{Z} is capacitive if \mathbf{X} is -ve
 - \mathbf{Z} , \mathbf{R} , and \mathbf{X} have the units of Ω
- Admittance $\mathbf{Y} = \mathbf{G} + j\mathbf{B}$
 - \mathbf{G} is the conductance, while \mathbf{B} is the susceptance
 - \mathbf{Y} is inductive if \mathbf{B} is -ve
 - \mathbf{Y} is capacitive if \mathbf{B} is +ve
 - \mathbf{Y} , \mathbf{G} , and \mathbf{B} have the units of Ω^{-1}

- Resistive impedance is real
 - Resistance is the only thing that dissipates power
- Capacitive and inductive impedance is imaginary
 - They store power
- What part of a complex Z dissipates power and what part stores?
- A purely resistive impedance will not change phase



Impedance and frequency



- Resistive impedance $Z_R = R$ is not a function of frequency
- Capacitance impedance is $Z_C = 1/j\omega C$
- So is inductive impedance $Z_L = j\omega L$
- At DC $\omega = 0$
 - $Z_C = \frac{1}{j\omega C} = \infty \rightarrow$ Capacitors are O.C.
 - $Z_L = j\omega L = 0 \rightarrow$ Inductors are S.C.
 - $Z_R = R \rightarrow$ Only resistors remain
- At very high frequencies $\omega \rightarrow \infty$
 - $Z_C = \frac{1}{j\omega C} = 0 \rightarrow$ Capacitors are S.C.
 - $Z_L = j\omega L = \infty \rightarrow$ Inductors are O.C.
 - $Z_R = R \rightarrow$ Only resistors remain
- This is the basis of filters



Example 1.0



- For the circuit shown find $v(t)$ and $i(t)$


- $V_S = 10\angle 0^\circ$, $\omega = 4\text{rad/sec}$

- $Z = R + \frac{1}{j\omega C}$

- $Z = 5 - j2.5 \Omega$

- $I = \frac{V_S}{Z} = \frac{10}{5 - j2.5}$

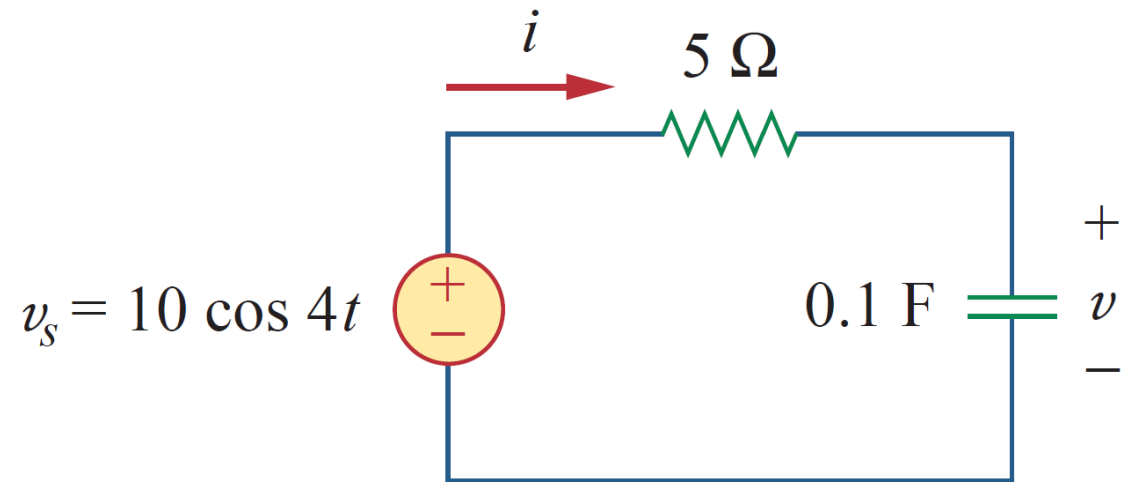- $V = \frac{10}{5 - j2.5} \times (-j2.5) = 10 \times \frac{-j2.5}{5 - j2.5}$ (potential divider)





Note:



- For any complex number $z = x + jy$,
- The conjugate is $z^* = x - jy$
- $z \times z^* = (x + jy)(x - jy) = x^2 - jxy + jxy - j^2y^2$
- *Hence*, $z \times z^* = x^2 + y^2 = |z|^2$



Example 1.0



- $I = \frac{10}{5-j2.5} \frac{5+j2.5}{5+j2.5}$
- $I = \frac{50+j25}{31.25} = 1.6 + j0.8$
- $I = 1.79 \angle 26.57^\circ A$
- $i(t) = 1.79 \cos(4t + 26.57^\circ) A$

- $V = IZ_C = \frac{I}{j\omega C} = \frac{1.79 \angle 26.57^\circ}{j0.4} = \frac{1.79 \angle 26.57^\circ}{0.4 \angle 90^\circ}$
- $V = 4.47 \angle -63.43^\circ$
- $v(t) = 4.47 \cos(4t - 63.43^\circ)$



Summary of AC Circuits



- Voltage and current are written as magnitude and phase
- $v(t) = V_m \cos(\omega t + \phi) = \text{Re}(V_m e^{j\omega t + j\phi})$
 - $V = V_m \angle \phi$
- $i(t) = I_m \cos(\omega t + \theta) = \text{Re}(I_m e^{j\omega t + j\theta})$
 - $I = I_m \angle \theta$
- Impedance is defined as $Z = \frac{V}{I}$
 - For resistors $Z = R$
 - For inductors $Z = j\omega L$
 - For capacitors $Z = \frac{1}{j\omega C}$



Kirchhoff's Laws in the Phasor Domain



- KVL and KCL are valid in phasor domain
- KVL
 - Let v_1, v_2, \dots, v_n be the voltages around a closed loop.

- Then:

$$v_1 + v_2 + \dots + v_n = 0$$

- In the sinusoidal steady state, each voltage may be written in cosine form

$$V_{m1} \cos(\omega t + \Phi_1) + V_{m2} \cos(\omega t + \Phi_2) + \dots + V_{mn} \cos(\omega t + \Phi_n) = 0$$



Kirchhoff's Laws in the Phasor Domain



- Then

$$\text{Re}\{V_{m1}e^{j\Phi_1}e^{j\omega t} + V_{m2}e^{j\Phi_2}e^{j\omega t} + \dots + V_{mn}e^{j\Phi_n}e^{j\omega t}\} = 0$$

$$\text{Re}\{V_{m1}e^{j\Phi_1}\} + \text{Re}\{V_{m2}e^{j\Phi_2}\} + \dots + \text{Re}\{V_{mn}e^{j\Phi_n}\} = 0$$

- Let

$$V_k = V_{mk}e^{j\Phi_k}$$

- Then

$$V_1 + V_2 + \dots + V_n = 0$$

- So, Kirchhoff's voltage law holds for phasors



Kirchhoff's Laws in the Phasor Domain



- Similarly, Kirchhoff's current law holds for phasors at all nodes


$$\mathbf{I}_1 + \mathbf{I}_2 + \cdots + \mathbf{I}_n = 0$$



Impedance Combination



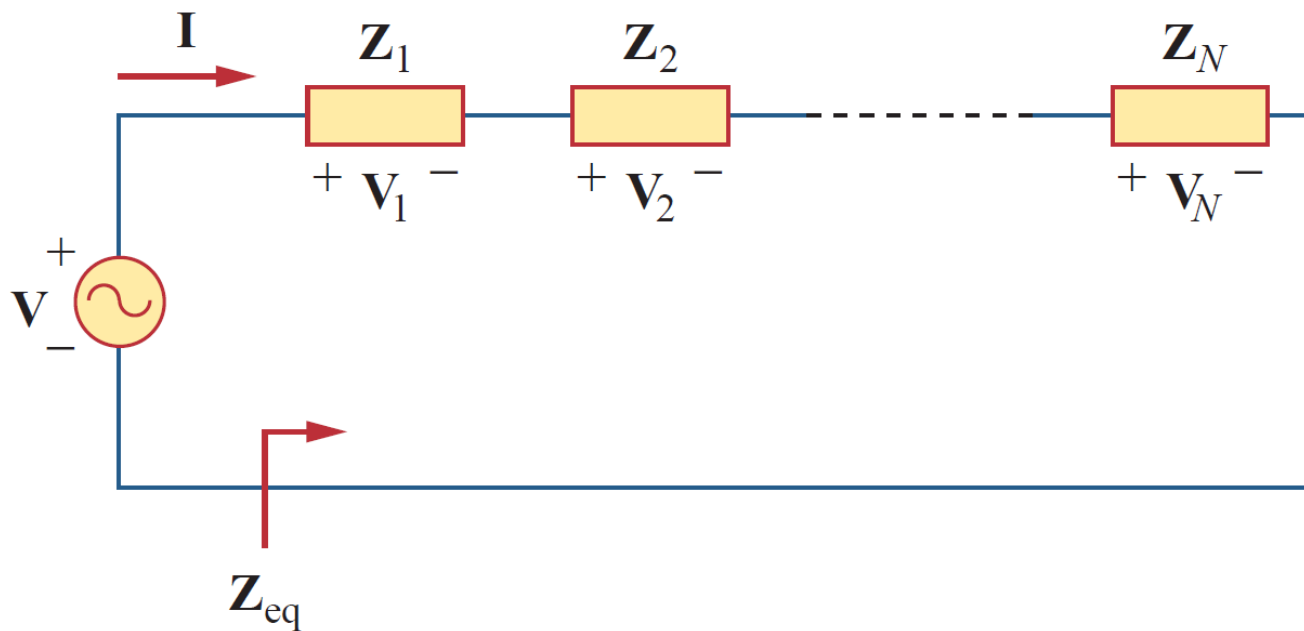- For N series connected impedances, the same current I flows through the impedances
- $V = V_1 + V_2 + \cdots + V_N = I(Z_1 + Z_2 + \cdots + Z_N)$
- $Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + \cdots + Z_N$





Voltage Divider




- For two impedances connected in series

- $I = \frac{V}{Z_1 + Z_2}$

- $V_1 = IZ_1, V_2 = IZ_2$

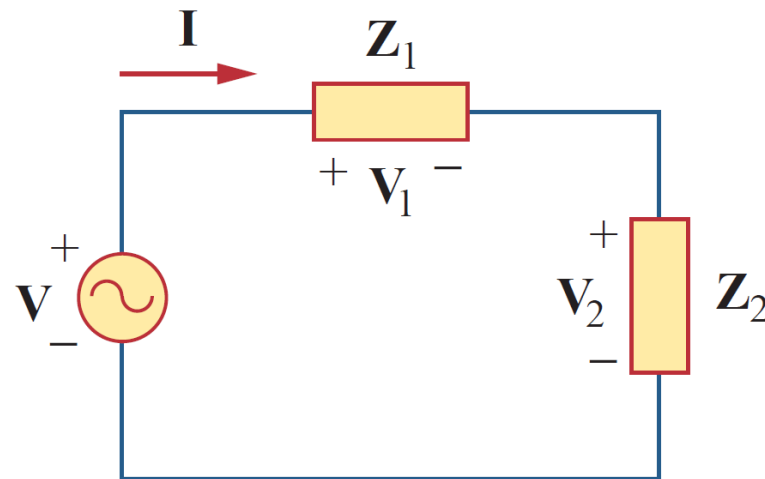- $V_1 = \frac{Z_1}{Z_1 + Z_2} V, V_2 = \frac{Z_2}{Z_1 + Z_2} V$





Admittance Combination




- For N Parallel connected impedance, voltage is the same across all impedances
- Applying KCL

$$I = I_1 + I_2 + \dots + I_N = V \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right)$$

$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$$

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$

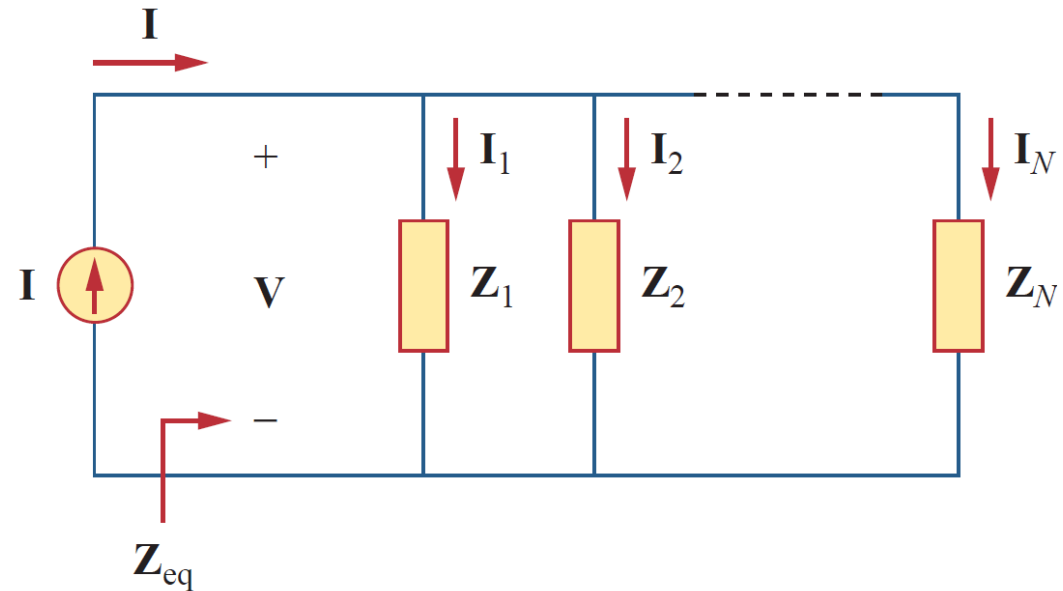




Current Divider



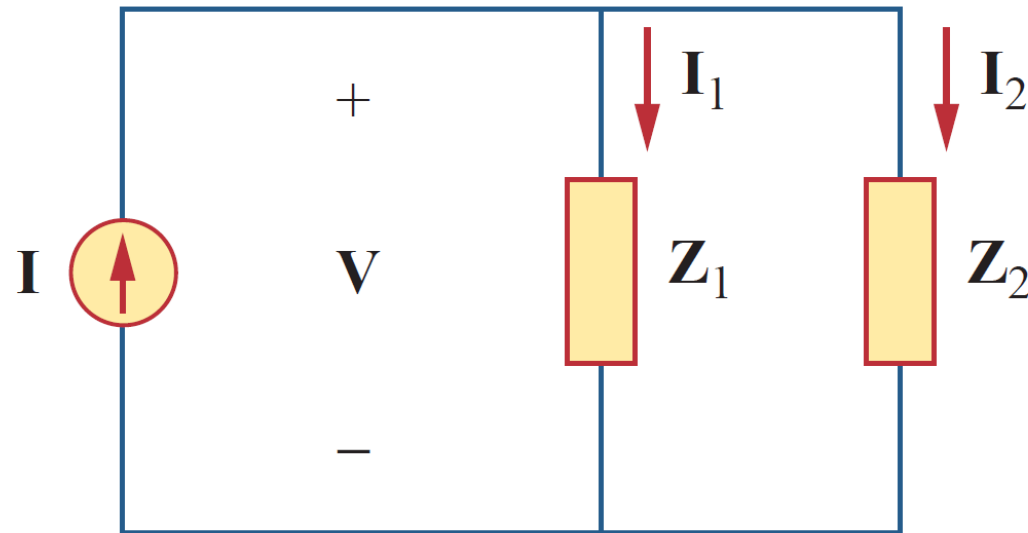- $Z_{eq} = \frac{1}{Y_{eq}} = \frac{1}{Y_1 + Y_2} = \frac{1}{1/Z_1 + 1/Z_2} = \frac{Z_1 Z_2}{Z_1 + Z_2}$
- $V = I Z_{eq} = I \frac{Z_1 Z_2}{Z_1 + Z_2} = I_1 Z_1 = I_2 Z_2$
- $I_1 = \frac{Z_2}{Z_1 + Z_2} I, I_2 = \frac{Z_1}{Z_1 + Z_2} I$






Star-Delta Conversion



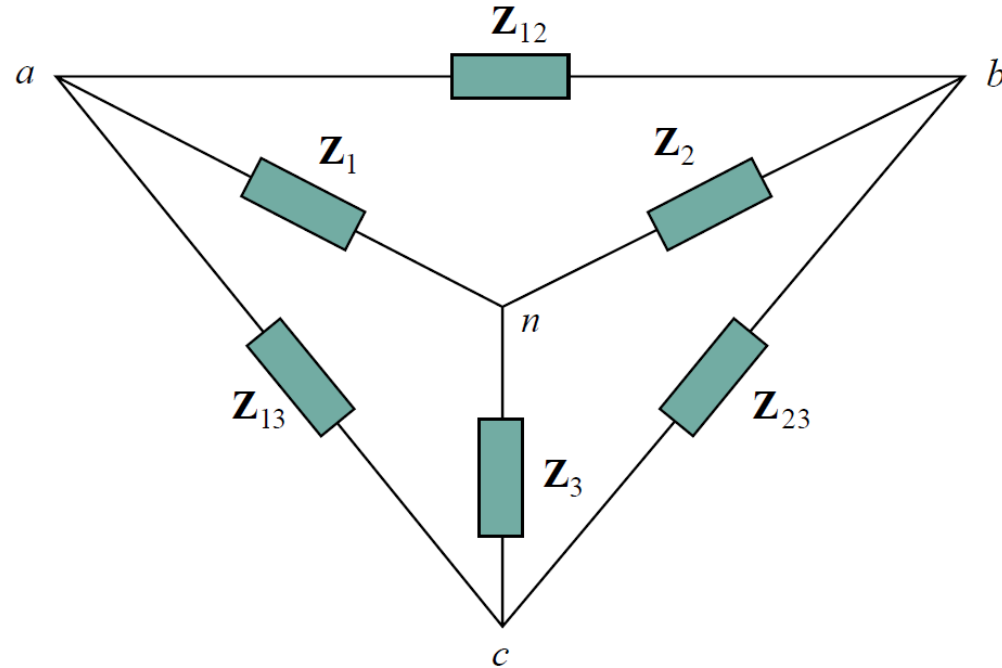- $Z_{12} = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$
- $Z_{23} = Z_2 + Z_3 + \frac{Z_2 Z_3}{Z_1}$
- $Z_{13} = Z_1 + Z_3 + \frac{Z_1 Z_3}{Z_2}$






Delta-Star Conversion



- $Z_1 = \frac{Z_{12}Z_{13}}{Z_{12}+Z_{13}+Z_{23}}$

- $Z_2 = \frac{Z_{12}Z_{23}}{Z_{12}+Z_{13}+Z_{23}}$

- $Z_3 = \frac{Z_{13}Z_{23}}{Z_{12}+Z_{13}+Z_{23}}$

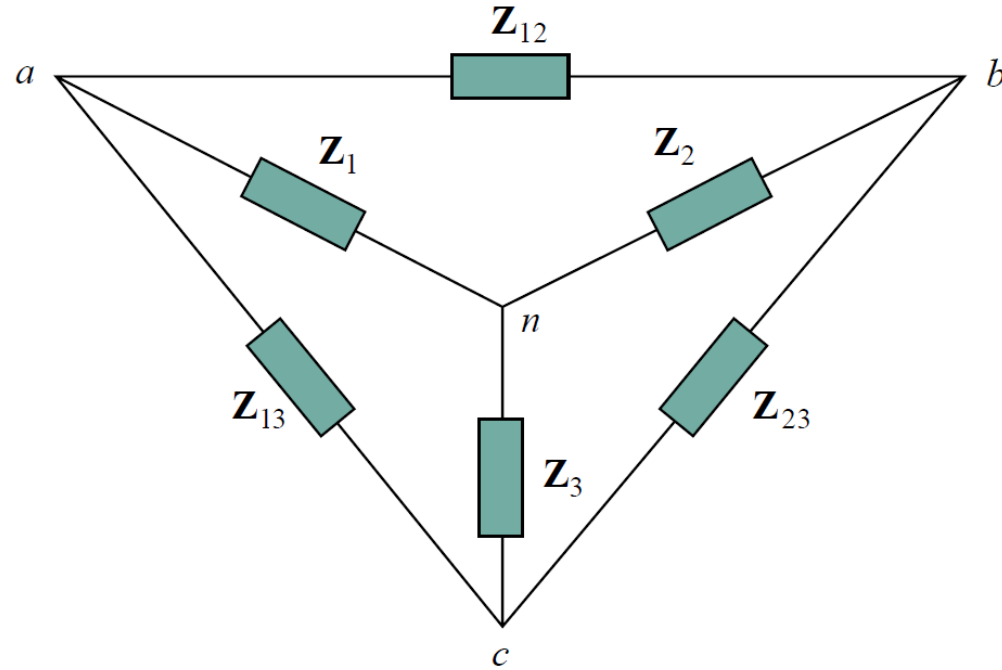




Example 1.0



- Find the input impedance of the circuit shown. Assume that the circuit operates at $\omega = 50$ rad/s

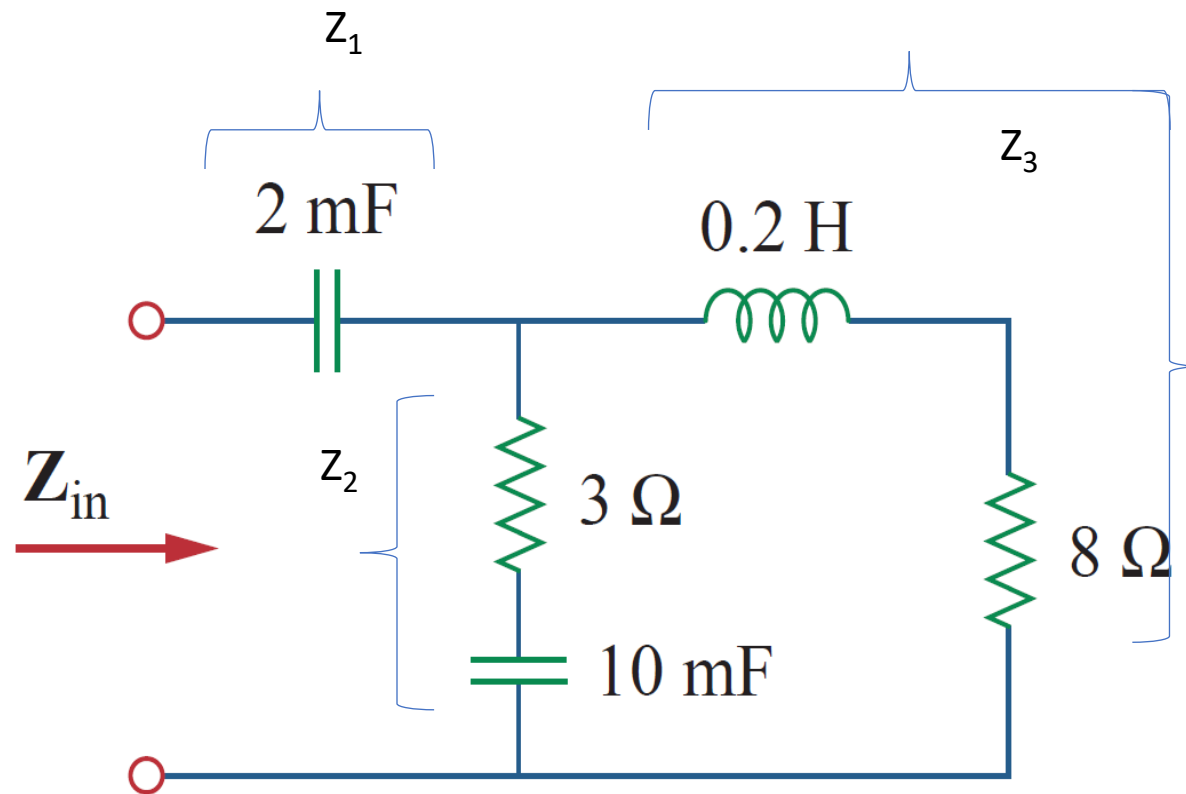



Example 1.0



- Find the input impedance of the circuit shown. Assume that the circuit operates at $\omega = 50$ rad/s

- $Z_1 = \text{Impedance of } 2\text{mF Capacitor}$


- $Z_1 = \frac{1}{j\omega C} = -j10$

- $Z_2 = R + \frac{1}{j\omega C} = 3 - j2$

- $Z_3 =$


Impedance of the 0.2H inductor in series with the 8Ω resistor

- $Z_3 = 8 + j10$

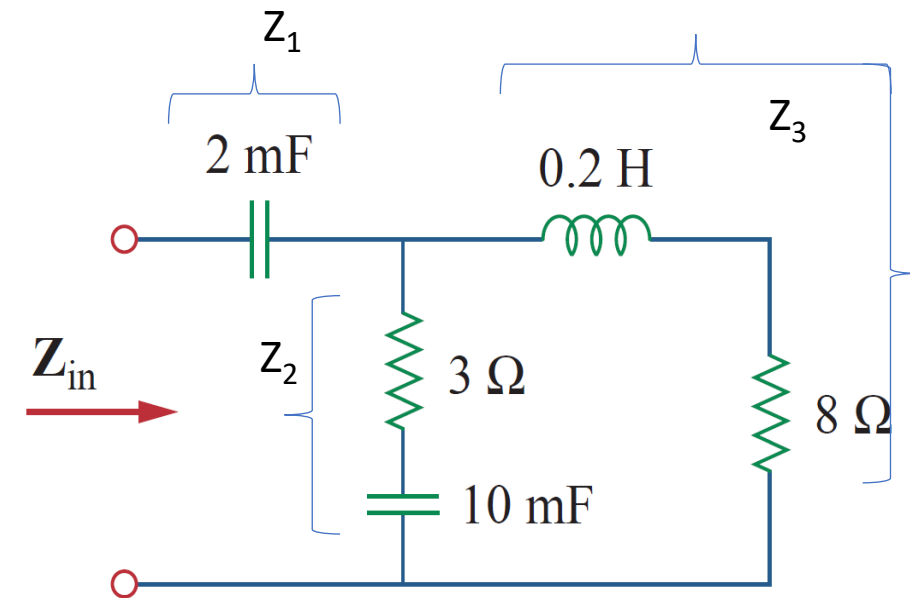



Example 1.0

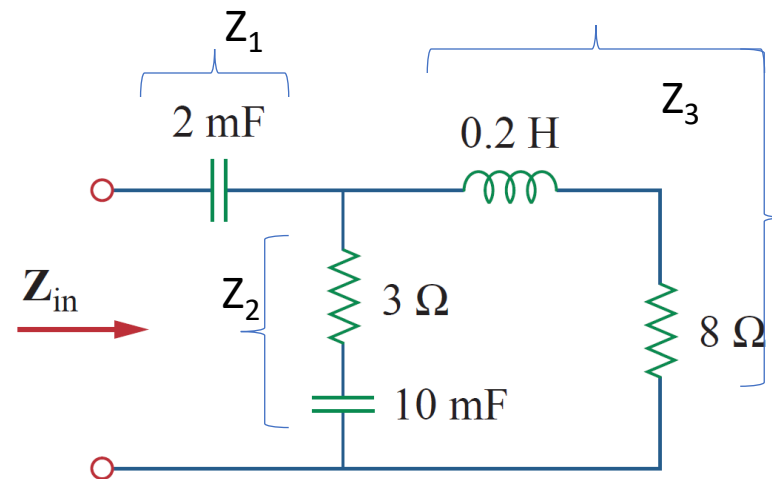


- $Z_1 = \frac{1}{j\omega C} = -j10, Z_2 = R + \frac{1}{j\omega C} = 3 - j2, Z_3 = 8 + j10$
- The input impedance is $Z_{in} = Z_1 + Z_2 || Z_3$
 - $Z_{in} = -j10 + \frac{(3-j2)(8+j10)}{11+j8} = -j10 + \frac{44+j14}{11+j8}$
 - $Z_{in} = -j10 + \frac{(44+j14)(11-j8)}{11^2+8^2} = -j10 + 3.22 - j1.07$
 - $Z_{in} = 3.22 - j11.07$



Example 2.0



- Find the current I for the circuit shown



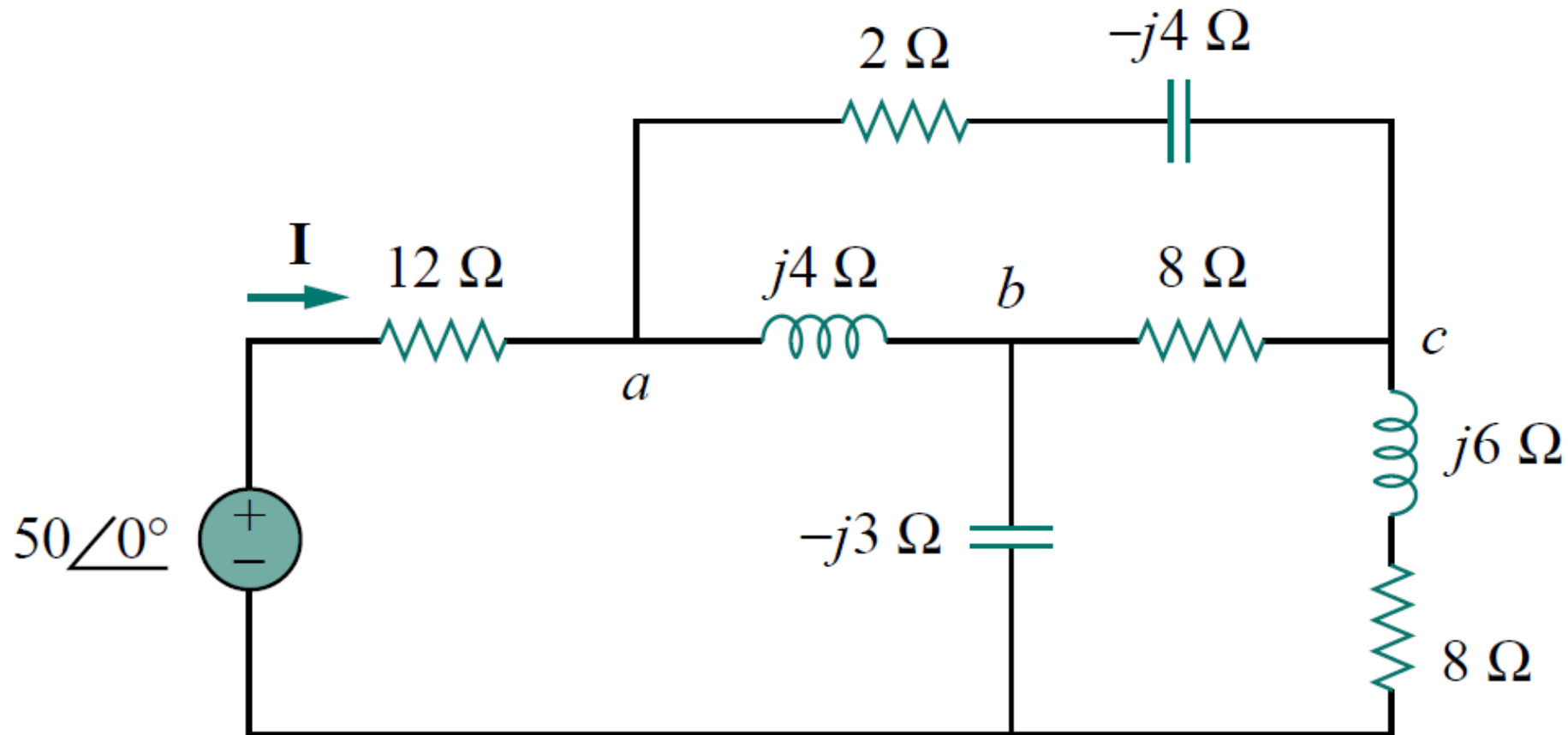




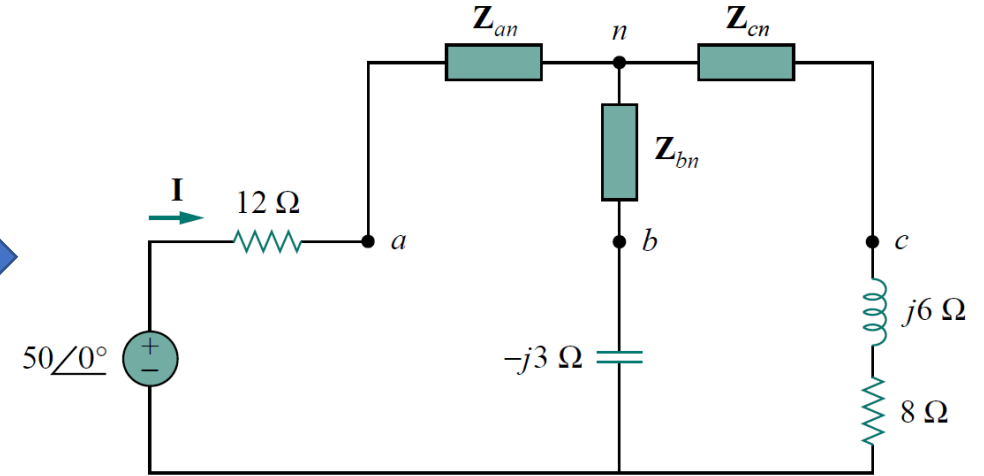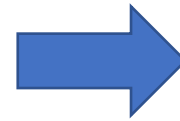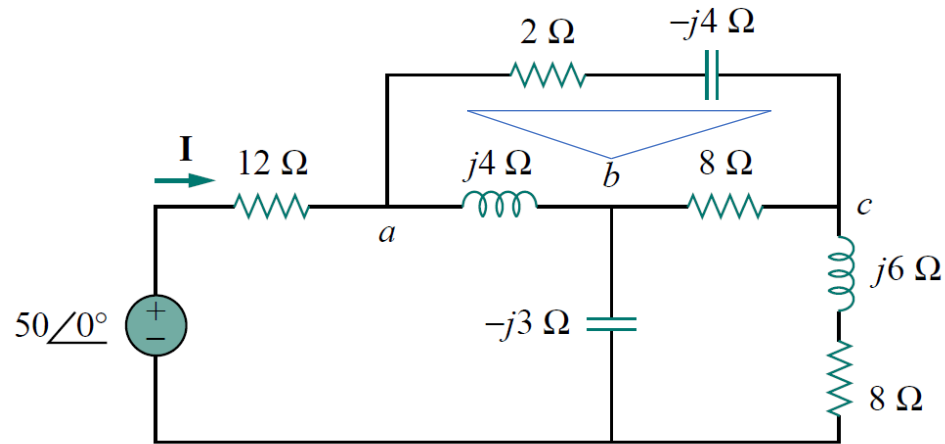
Example 2.0



- Find the current I for the circuit shown



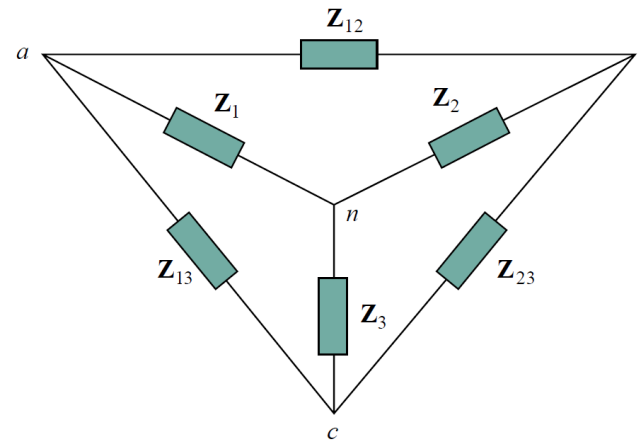- $$Z_{cn} = \frac{8(2-j4)}{10} = 1.6 - j3.2$$
- $$Z_{an} = \frac{j4(2-j4)}{10} = 1.6 + j0.8$$
- $$Z_{bn} = \frac{j4 \times 8}{10} = j3.2$$



$$Z_1 = \frac{Z_{12}Z_{13}}{Z_{12} + Z_{13} + Z_{23}}$$

$$Z_2 = \frac{Z_{12}Z_{23}}{Z_{12} + Z_{13} + Z_{23}}$$


$$Z_3 = \frac{Z_{13}Z_{23}}{Z_{12} + Z_{13} + Z_{23}}$$



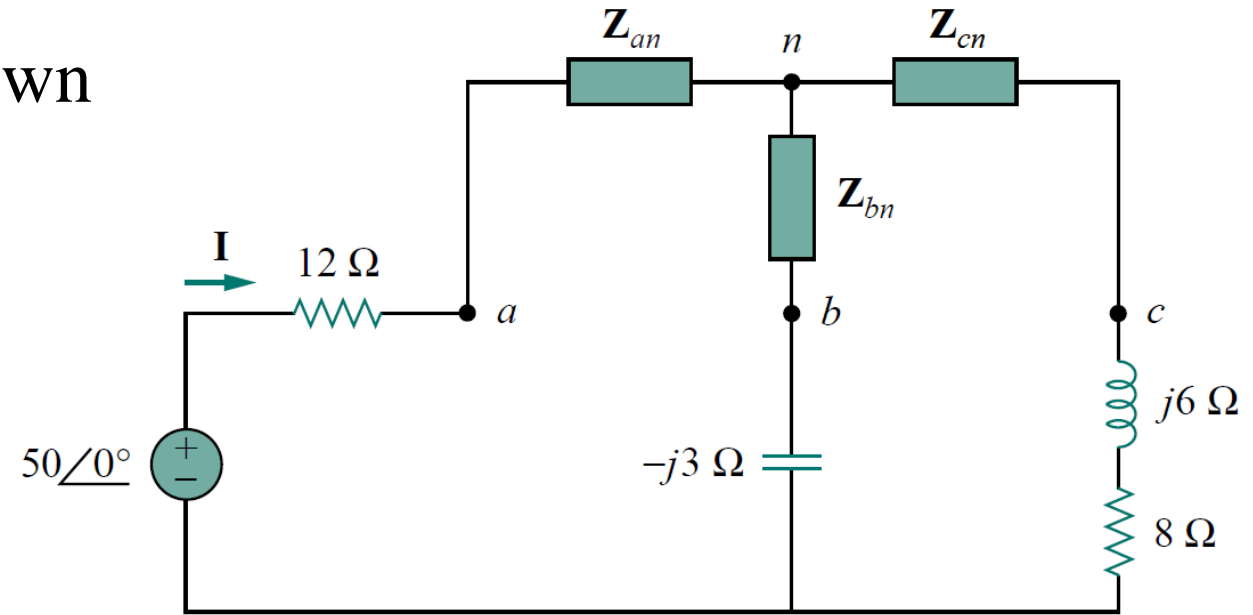Example 2.0



- Find the current I for the circuit shown




- $Z = 12 + Z_{an} + (Z_{bn} - j3) || (Z_{cn} + 8 + j6)$
- $Z = 12 + 1.6 + j0.8 + (j0.2) || (9.6 + j2.8)$
- $Z \approx 13.6 + j1 = 13.64 \angle 4.2^\circ$
- $I = \frac{V}{Z} = \frac{50 \angle 0^\circ}{13.64 \angle 4.2^\circ} = 3.67 \angle -4.2^\circ$



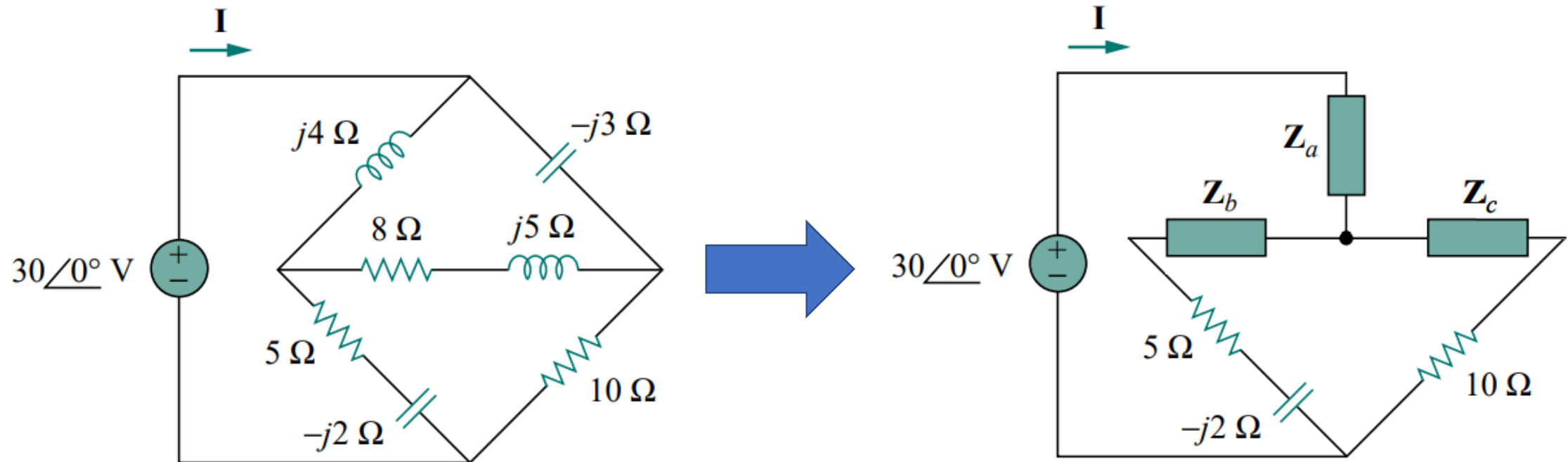Example 3.0



- Find the current I for the circuit shown



- $I = 6.36\angle 3.8^\circ$