



ELC1010



Electric Circuits (I) – Circuit Theory

Part (II) – AC Circuits **Lecture (6)** Sinusoidal Time Domain Analysis

Dr. Omar Bakry

omar.bakry.eece@cu.edu.eg

Department of Electronics and Electrical Communications

Faculty of Engineering

Cairo University

Fall 2023



- Sinusoidal Time Domain Analysis
- Review:
 - Sinusoidal, Average and RMS
 - Phase Shift and Phase Relationship (Lead, Lag)
- Element Response (R, L, C)
- Series RLC Network
- Parallel RLC Network
- Example




- In most power and communication systems, alternating current (AC) is the standard form of electric power used.
- **Power generation and transmission:**
 - Transmitting AC power at high voltages and lower currents is ideal as it minimizes transmission line losses, which are proportional to the square of the current (Power loss: $P_{loss} = I^2 R_{conductor}$)
 - High voltage transmission is a more cost-effective solution for power distribution.
 - At the load end, AC/DC rectifier circuits can convert AC to the required DC form.
- **Communication systems and information theory:**
 - Communication systems utilize various data modulation techniques, including amplitude, frequency, and phase modulation.
 - Advanced communication methods employ higher-order modulations for data transmission.



Time Domain (TD) Analysis



- Passive elements: R, L and C.
- Assume sinusoidal signals (periodic)
 - Integration and differentiation of sinusoidal signals are sinusoidal signals.
- $v(t) = V_m \sin(\omega t + \phi_v)$, $i(t) = I_m \sin(\omega t + \phi_i)$
 - $v(t)$ and $i(t)$ are the instantaneous value of voltage/current
 - V_m and I_m are the max/peak values (amplitudes) of voltage/current
 - ω is the angular frequency (rad/sec) and is equal to $\omega = 2\pi f = \frac{2\pi}{T}$
 - f is the frequency in Hz
 - $T = \frac{1}{f}$ is the period in secs
 - ϕ is the initial phase angle
- Sinusoidal signals are defined by 3 parameters:
 - V_m/I_m , ω and ϕ .

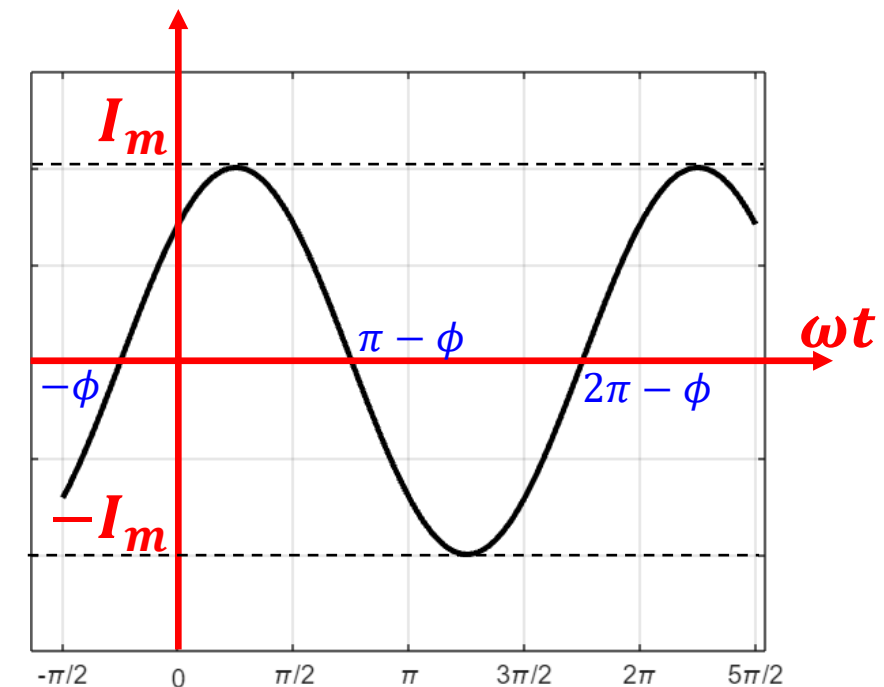




Lead/Lag Phase Relationship in Time Domain



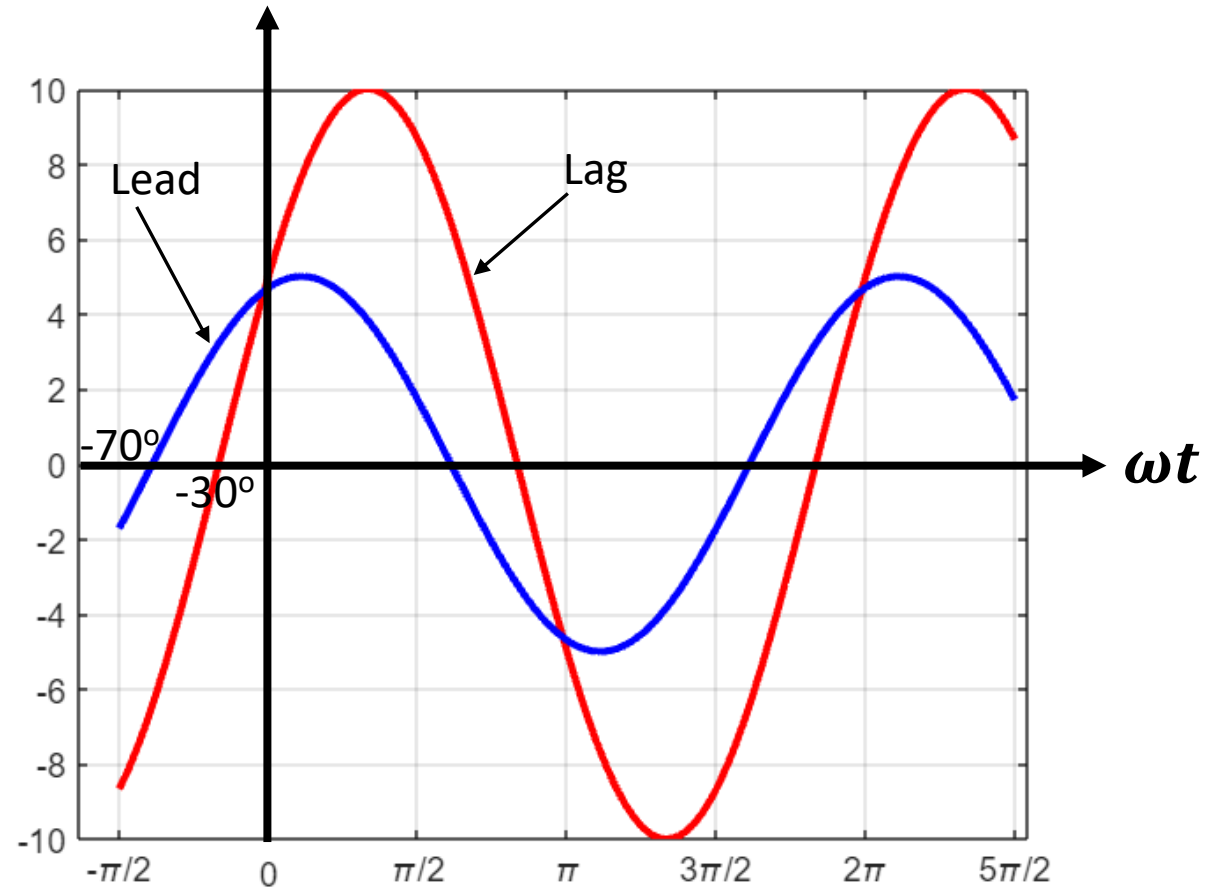- Phase relationship between v and i :
 - Lead
 - Lag
- *Example:*
 - $v(t) = 10 \sin(\omega t + 30^\circ) \text{ V}$
 - $i(t) = 5 \sin(\omega t + 70^\circ) \text{ V}$
 - i leads v by 40°
 - v lags i by 40°





Average and Effective (RMS) Values




- $i(t) = I_m \sin(\omega t)$

- $I_{avg} = \frac{1}{T} \int_0^T i(t) dt = \frac{1}{2\pi} \int_0^{2\pi} i(t) d(\omega t)$

- $I_{avg} = \frac{1}{2\pi} \int_0^{2\pi} I_m \sin(\omega t) d(\omega t) = \frac{I_m}{2\pi} (-\cos(\omega t)) \Big|_0^{2\pi} = 0$

- $I_{rms} = I_{eff} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2(t) d(\omega t)}$

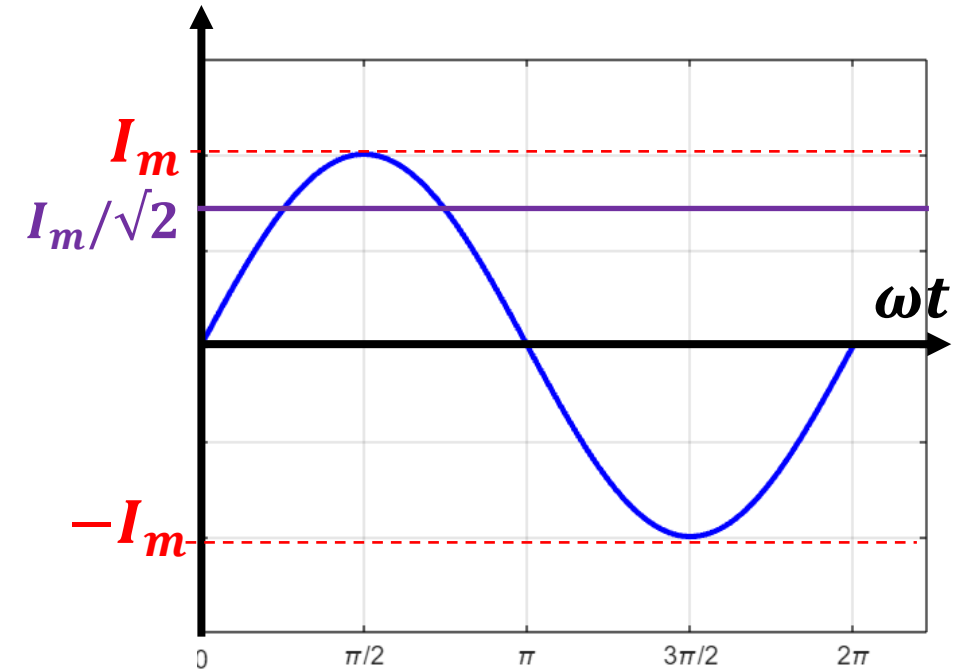- $$I_{rms} = \sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} \sin^2(\omega t) d(\omega t)} = \sqrt{\frac{I_m^2}{4\pi} \int_0^{2\pi} (1 - \cos^2(\omega t)) d(\omega t)}$$
$$= \sqrt{\frac{I_m^2}{4\pi} (2\pi - 0)} = \frac{I_m}{\sqrt{2}}$$







Element Response: Resistors



- Let $i(t) = I_m \sin(\omega t)$
- Resistor (R):
 - $v(t) = R \times i(t)$
 - $v(t) = RI_m \sin(\omega t) = V_m \sin(\omega t)$
 - $V_m = RI_m \rightarrow V_{rms} = \frac{RI_m}{\sqrt{2}} = RI_{rms}$
 - $v(t)$ and $i(t)$ are in phase
- Instantaneous power:
 - $p(t) = i(t) \times v(t) = I_m V_m \sin^2(\omega t)$
- Average power:
 - $P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} I_m V_m \sin^2(\omega t) d(\omega t) = \frac{V_m I_m}{2} = V_{rms} I_{rms}$
 - $P_{avg} = \frac{V_m I_m}{2} = \frac{1}{2} I_m^2 R = \frac{V_m^2}{2R}$
 - $P_{avg} = V_{rms} I_{rms} = I_{rms}^2 R = \frac{V_{rms}^2}{R}$

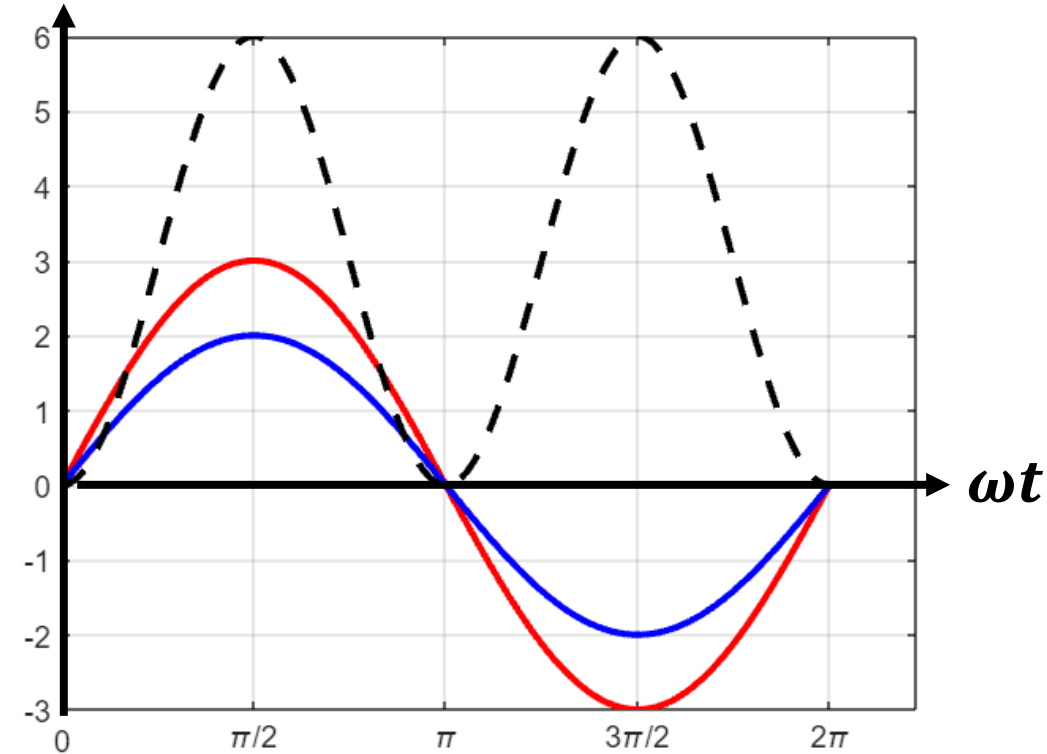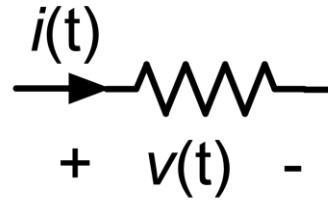



Element Response: Inductors

- Let $i(t) = I_m \sin(\omega t)$

- Inductors (L):



- $v(t) = L \times \frac{di(t)}{dt}$ (Faraday's law)

- $v(t) = \omega L I_m \cos(\omega t) = V_m \cos(\omega t)$

- Reactance: $X_L = \omega L$ (Ω)

- $V_m = X_L I_m \rightarrow V_{rms} = \frac{X_L I_m}{\sqrt{2}} = X_L I_{rms}$

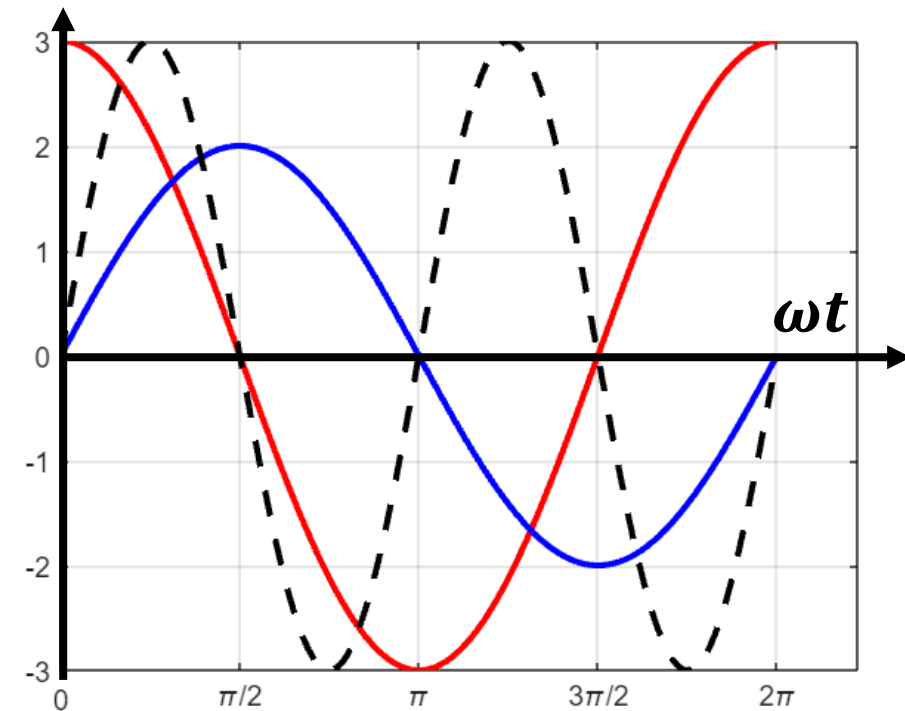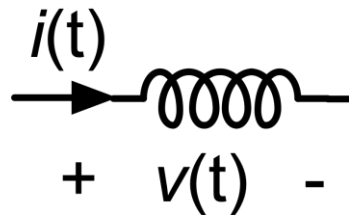- $v(t)$ leads $i(t)$ by 90° or $i(t)$ lags $v(t)$ by 90°



- Instantaneous power:

- $p(t) = i(t) \times v(t) = I_m V_m \sin(\omega t) \cos(\omega t) = \frac{V_m I_m}{2} \sin(2\omega t) = V_{rms} I_{rms} \sin(2\omega t)$

- Average power:

- $P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} I_m V_m \sin(\omega t) \cos(\omega t) d(\omega t) = \frac{V_m I_m}{4\pi} \int_0^{2\pi} \sin(2\omega t) d(\omega t) = 0$

- Power is stored/returned to the source $\rightarrow$ net average power = 0



Element Response: Capacitor

- Let $i(t) = I_m \sin(\omega t)$

- Capacitor (C):

- $i(t) = C \times \frac{dv(t)}{dt}$

- $v(t) = \frac{1}{C} \int i(t) dt$

- $v(t) = \frac{-1}{\omega C} I_m \cos(\omega t) = V_m \cos(\omega t)$

- Reactance: $X_C = \frac{-1}{\omega C} (\Omega)$

- $V_m = X_C I_m \rightarrow V_{rms} = \frac{X_C I_m}{\sqrt{2}} = X_C I_{rms}$

- $i(t)$ leads $v(t)$ by 90° or $v(t)$ lags $i(t)$ by 90°


- Instantaneous power:

- $p(t) = i(t) \times v(t) = I_m V_m \sin(\omega t) \cos(\omega t) = \frac{V_m I_m}{2} \sin(2\omega t) = V_{rms} I_{rms} \sin(2\omega t)$


- Average power:

- $P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} I_m V_m \sin(\omega t) \cos(\omega t) d(\omega t) = \frac{V_m I_m}{4\pi} \int_0^{2\pi} \sin(2\omega t) d(\omega t) = 0$

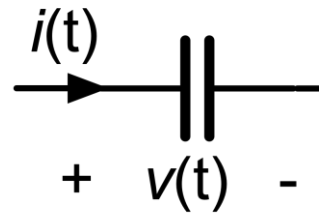- Power is stored/retuned to the source $\rightarrow$ net average power = 0


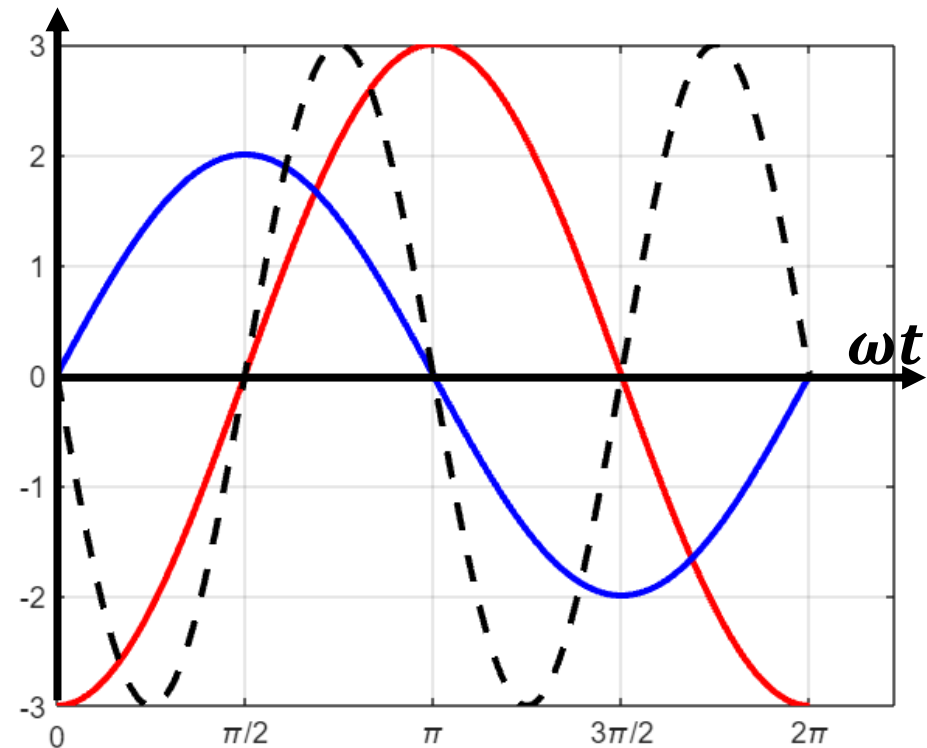
$$\begin{aligned} q &= Cv \\ \frac{dq}{dt} &= i = C \frac{dv}{dt} \end{aligned}$$







R,L Series Combination



- $i(t) = I_m \sin(\omega t)$
- $v(t) = v_R(t) + v_L(t) = Ri(t) + L \frac{di(t)}{dt}$
- $v(t) = RI_m \sin(\omega t) + \omega LI_m \cos(\omega t)$
- $v(t) = I_m [R \sin(\omega t) + \omega L \cos(\omega t)]$
- $v(t) = I_m \sqrt{R^2 + \omega^2 L^2} \sin(\omega t + \phi_Z) = V_m \sin(\omega t + \phi_Z)$
- $\phi_Z = \tan^{-1} \left(\frac{\omega L}{R} \right)$
- $V_m = I_m \sqrt{R^2 + \omega^2 L^2}$
- Impedance: $|Z| = \frac{V_m}{I_m} = \frac{V_{rms}}{I_{rms}} = \sqrt{R^2 + \omega^2 L^2} \text{ } (\Omega)$
- $v(t)$ leads $i(t)$ by ϕ_Z or $i(t)$ lags $v(t)$ by ϕ_Z
- Inductive circuit

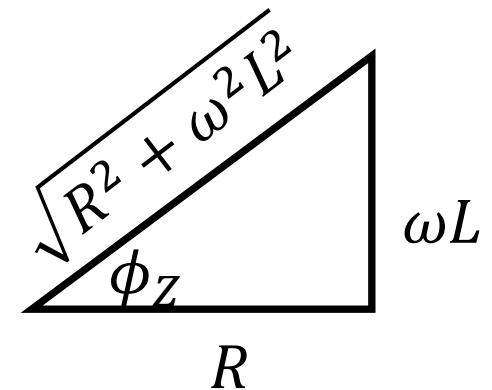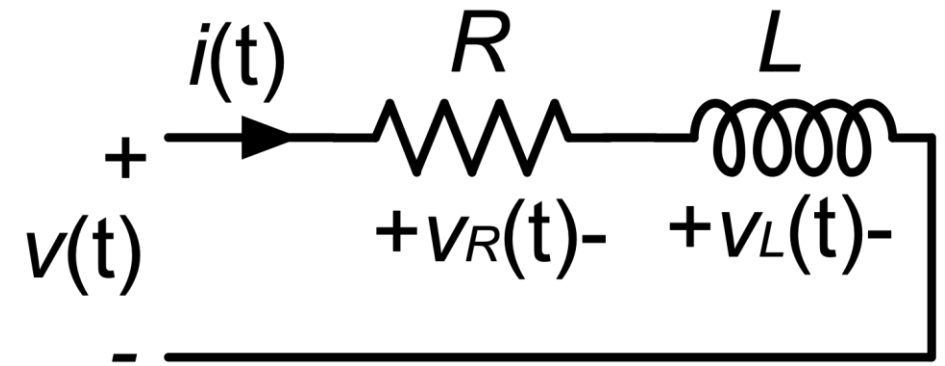

Consider the function

$$f(x) = a \sin(x) + b \cos(x)$$

We shall show that this is a sinusoidal wave

$$f(x) = A \sin(x + \phi)$$


and find that the amplitude is $A = \sqrt{a^2 + b^2}$ and the phase $\phi = \arctan \frac{b}{a}$



R,L Series Combination



- $\phi_z = \tan^{-1} \left(\frac{\omega L}{R} \right)$
 - $0 \leq \phi_z \leq \frac{\pi}{2}$, ϕ_z is +ve
 - $\phi_z = 0 \rightarrow$ Resistor only
 - $\phi_z = \pi/2 \rightarrow$ Inductor only
- $p(t) = i(t) \times v(t) = I_m V_m \sin(\omega t) \sin(\omega t + \phi_z)$
- $p(t) = \frac{I_m V_m}{2} [\cos(\phi_z) - \cos(2\omega t + \phi_z)]$
- $P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} I_m V_m \sin(\omega t) \sin(\omega t + \phi_z) d(\omega t)$
- $P_{avg} = \frac{I_m V_m}{4\pi} \int_0^{2\pi} [\cos(\phi_z) - \cos(2\omega t + \phi_z)] d(\omega t)$
- $P_{avg} = \frac{I_m V_m}{2} \cos(\phi_z) = V_{rms} I_{rms} \cos(\phi_z)$

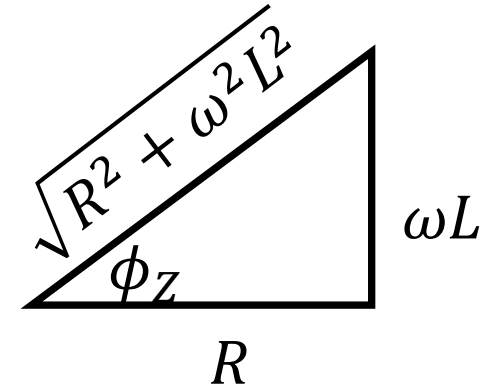



R,L Series Combination



- Power Factor: $pf = \cos(\phi_z)$
 - $0 \leq pf \leq 1$
 - $pf = 1 \rightarrow \phi_z = 0 \rightarrow$ Resistor only
 - $pf = 0 \rightarrow \phi_z = \pi/2 \rightarrow$ Inductor only
- When power factor =1 $\rightarrow$ unity power factor
- Assume we have $v(t) = V_m \sin(\omega t)$
- Then, $i(t) = \frac{V_m}{|Z|} \sin(\omega t - \phi_z) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t - \tan^{-1} \frac{\omega L}{R})$



R,L,C Series Combination



- General Case: R,L, and C are in series

- $i(t) = I_m \sin(\omega t)$

- $v(t) = v_R(t) + v_L(t) + v_C(t) = Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$


- $v(t) = RI_m \sin(\omega t) + \omega LI_m \cos(\omega t) - \frac{1}{\omega C} I_m \cos(\omega t)$

- $v(t) = I_m \left[R \sin(\omega t) + \left(\omega L - \frac{1}{\omega C} \right) \cos(\omega t) \right] = V_m \sin(\omega t + \phi_z)$

- $\phi_z = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$

- $V_m = I_m \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$

- Impedance: $|Z| = \frac{V_m}{I_m} = \frac{V_{rms}}{I_{rms}} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2} \text{ } (\Omega)$

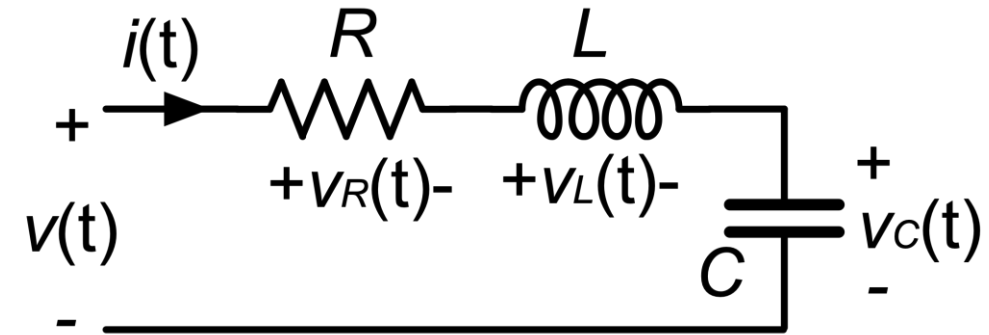




R,L,C Series Combination



- $\phi_Z = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$
- $-\frac{\pi}{2} \leq \phi_Z \leq \frac{\pi}{2}$
- If $\omega L > \frac{1}{\omega C}$
 - ϕ_Z is positive $\rightarrow$ Inductive Circuit
 - $v(t)$ leads $i(t)$ by ϕ_Z
- If $\omega L < \frac{1}{\omega C}$
 - ϕ_Z is negative $\rightarrow$ Capacitive Circuit
 - $i(t)$ leads $v(t)$ by ϕ_Z
- If $\omega L = \frac{1}{\omega C}$
 - ϕ_Z is 0 $\rightarrow$ Resistive Circuit (Series Resonance Condition) $\rightarrow |Z| = R$
 - $i(t)$ and $v(t)$ are in phase

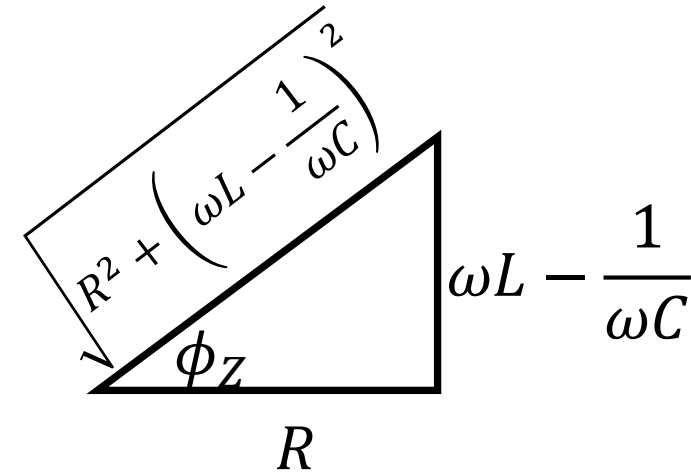




R,L,C Series Combination



- $p(t) = i(t) \times v(t) = I_m V_m \sin(\omega t) \sin(\omega t + \phi_z)$
- $P_{avg} = \frac{I_m V_m}{4\pi} \int_0^{2\pi} [\cos(\phi_z) - \cos(2\omega t + \phi_z)] d(\omega t)$
- $P_{avg} = \frac{I_m V_m}{2} \cos(\phi_z) = V_{rms} I_{rms} \cos(\phi_z)$
- Given that: $|Z| = \frac{V_{rms}}{I_{rms}}$
 - $P_{avg} = I_{rms}^2 |Z| \cos(\phi_z) = I_{rms}^2 R$
 - Note that $P_{avg} \neq \frac{V_{rms}^2}{R}$ in this case as $v(t)$ is across R,L, and C altogether
- Power Factor: $pf = \cos(\phi_z)$
 - $0 \leq pf \leq 1$
 - $pf = 1 \rightarrow \phi_z = 0 \rightarrow$ Resistor only
 - $pf = 0 \rightarrow \phi_z = \pm\pi/2 \rightarrow$ Inductor or Capacitor only $\rightarrow$ Need to know lead/lag?

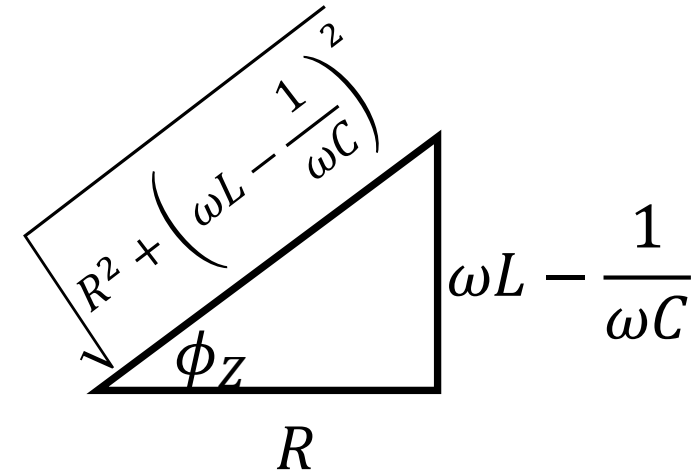



R,C Series Combination



- Special case from the previous discussion ($L = 0$)


- $|Z| = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$

- $\phi_Z = \tan^{-1} \left(\frac{-\frac{1}{\omega C}}{R} \right) = -\tan^{-1} \left(\frac{1}{\omega RC} \right)$

- ϕ_Z is negative $\rightarrow$ Capacitive Circuit

- $i(t)$ leads $v(t)$ by ϕ_Z

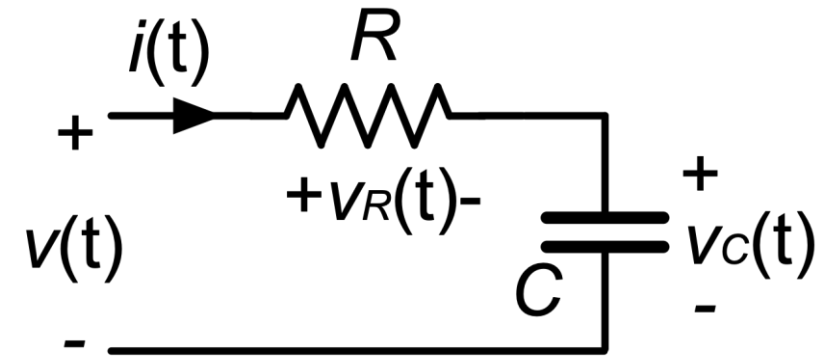- $P_{avg} = V_{rms} I_{rms} \cos(\phi_Z)$






R,L,C Parallel Combination



- $v(t) = V_m \sin(\omega t)$
- $i(t) = i_R(t) + i_L(t) + i_C(t) = \frac{v(t)}{R} + \frac{1}{L} \int v(t) dt + C \frac{dv(t)}{dt}$
- $i(t) = \frac{V_m}{R} \sin(\omega t) - \frac{1}{\omega L} V_m \cos(\omega t) + \omega C V_m \cos(\omega t)$
- $i(t) = V_m \left[\frac{1}{R} \sin(\omega t) + \left(\omega C - \frac{1}{\omega L} \right) \cos(\omega t) \right] = I_m \sin(\omega t + \phi_Y)$
- $\phi_Y = \tan^{-1} \left(\frac{\omega C - \frac{1}{\omega L}}{\frac{1}{R}} \right)$
- $I_m = V_m \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L} \right)^2}$
- Admittance: $|Y| = \frac{I_m}{V_m} = \frac{I_{rms}}{V_{rms}} = \sqrt{\left(\frac{1}{R} \right)^2 + \left(\omega C - \frac{1}{\omega L} \right)^2} \quad (1/\Omega)$

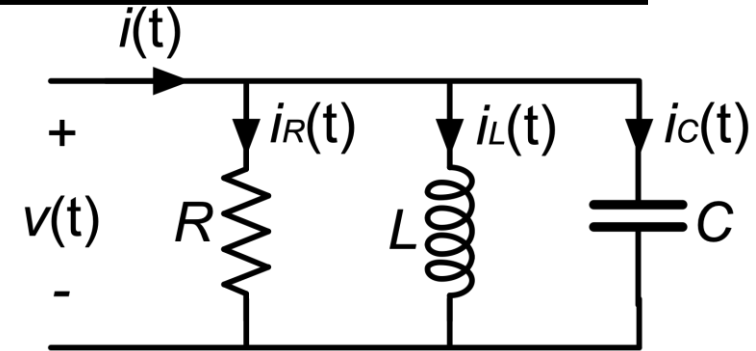



R,L,C Parallel Combination



- $\phi_Y = \tan^{-1} \left(\frac{\omega C - \frac{1}{\omega L}}{\frac{1}{R}} \right)$
- $-\frac{\pi}{2} \leq \phi_Y \leq \frac{\pi}{2}$
- If $\omega C > \frac{1}{\omega L}$
 - ϕ_Y is positive $\rightarrow$ Capacitive Circuit
 - $i(t)$ leads $v(t)$ by ϕ_Y
- If $\omega C < \frac{1}{\omega L}$
 - ϕ_Y is negative $\rightarrow$ Inductive Circuit
 - $v(t)$ leads $i(t)$ by ϕ_Y
- If $\omega C = \frac{1}{\omega L}$
 - ϕ_Y is 0 $\rightarrow$ Resistive Circuit (Parallel Resonance Condition) $\rightarrow |Y| = \frac{1}{R}$
 - $i(t)$ and $v(t)$ are in phase



R,L,C Parallel Combination

- $p(t) = i(t) \times v(t) = I_m V_m \sin(\omega t) \sin(\omega t + \phi_Y)$
- $P_{avg} = \frac{I_m V_m}{4\pi} \int_0^{2\pi} [\cos(\phi_Y) - \cos(2\omega t + \phi_Y)] d(\omega t)$
- $P_{avg} = \frac{I_m V_m}{2} \cos(\phi_Y) = V_{rms} I_{rms} \cos(\phi_Y)$
- Given that: $|Y| = \frac{I_{rms}}{V_{rms}}$
 - $P_{avg} = V_{rms}^2 |Y| \cos(\phi_Y) = V_{rms}^2 \left(\frac{1}{R}\right) = \frac{V_{rms}^2}{R}$
 - Note that $P_{avg} \neq I_{rms}^2 R$ in this case as $i(t)$ is the total R,L, and C current
- Power Factor: $pf = \cos(\phi_Y)$
 - $0 \leq pf \leq 1$
 - $pf = 1 \rightarrow \phi_Y = 0 \rightarrow$ Resistor only
 - $pf = 0 \rightarrow \phi_Y = \pm\pi/2 \rightarrow$ Capacitor or Inductor only $\rightarrow$ Need to know lead/lag?



Example



- If $V_g = 100 \sin(500t) \text{ V}$, $i(t) = 2.5 \sin(500t) \text{ A}$.
- Find $i_1(t)$, $i_2(t)$, L and P_{avg} .
- Sketch the waveforms of all quantities on the same graph.

• Solution:


- $\omega = 500 \text{ rad/sec}$

- $\frac{-1}{\omega C} = \frac{-10^6}{500 \times 100} = -20 \Omega$

- R and C in series:

- $|Z| = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} = 20\sqrt{2} \Omega$

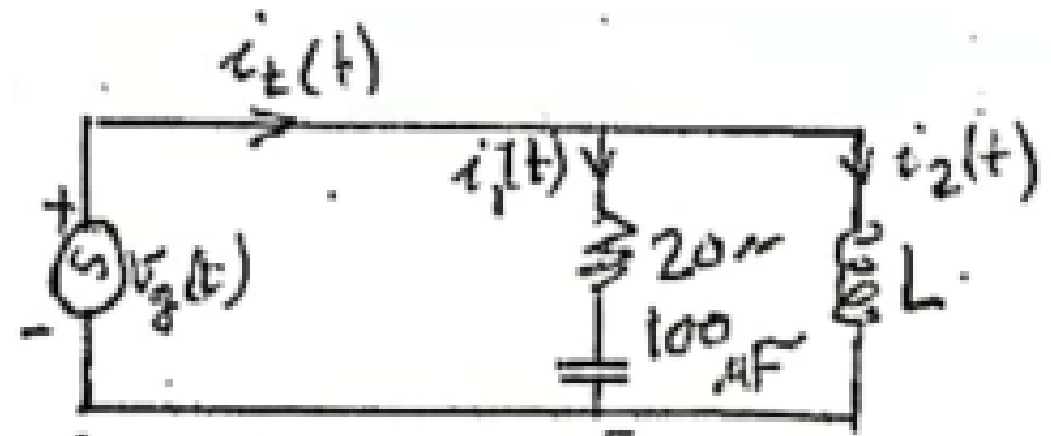- $\phi_z = -\tan\left(\frac{1}{\omega CR}\right) = -45^\circ$





Example



- $i_1(t) = \frac{V_m}{|Z|} \sin(500t - \phi_Z) = \frac{100}{20\sqrt{2}} \sin(500t + 45^\circ) A$
- $i_2(t) = i(t) - i_1(t) = 2.5 \sin(500t) - \frac{5}{\sqrt{2}} \sin(500t + 45^\circ) A$
- $i_2(t) = -2.5 \cos(500t) = 2.5 \sin(\omega t - 90^\circ) A$
- $I_{m2} = 2.5 = \frac{V_m}{\omega L}$
- $L = \frac{V_m}{\omega I_{m2}} = 0.08 H$
- $P_{avg} = \frac{1}{2} V_m I_m \cos(\phi_Z) = 0.5 \times 100 \times 2.5 = 125 W$
- $P_{avg} = \frac{1}{2} I_{m1}^2 R = 0.5 \times \left(\frac{5}{\sqrt{2}}\right)^2 \times 20 = 125 W$