

Faculty of Engineering – Cairo University
Electronics and Electrical Engineering Department
EECE2020 – Electronics II
Problem Set # 1


Unless otherwise specified, use the parameters from the following table for all problems.

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \text{ and } \epsilon_{ox} = 3.9\epsilon_o$$

Parameter	NMOS	PMOS	Units
$ V_{th} $	0.7	0.8	V
λ	0.1	0.2	V^{-1}
μ_o	350	100	$\frac{cm^2}{V \cdot sec}$
t_{ox}	9	9	nm

Problem 1.1: Determine what region of operation (cutoff, linear, or saturation) each of the following circuits is operating in.

a)

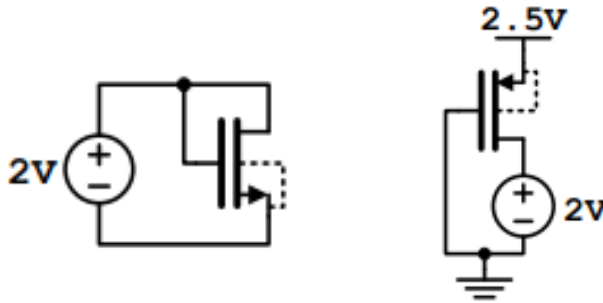

b) For an NMOS with $V_{DS} = 0.5V$, what are the ranges of V_{GS} voltages in which the device operates in the cutoff, linear, and saturation regions?


c) For an NMOS with $V_{GS} = 1V$, what are the ranges of V_{DS} voltages in which the device operates in the cutoff, linear, and saturation regions?

Problem 1.2: For the circuit on the right, answer the following questions. Ignore channel length modulation. $(W/L)_1 = (W/L)_2 = 1.0/0.5$.


a) What is the maximum value of V_{IN} that biases M_1 in the saturation region with $V_{DD} = 5V$?

b) What is the region of operation of each device when $V_{DD} = 5V$ and $V_{IN} = 3V$?

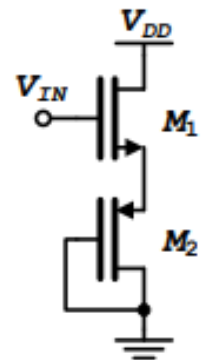c) What is the current through each device when $V_{DD} = 5V$ and $V_{IN} = 3V$?



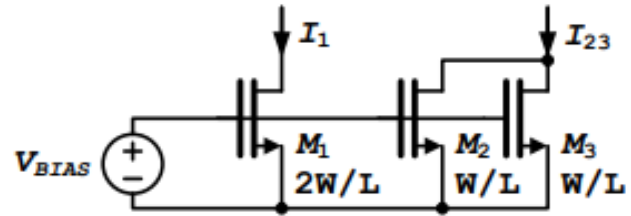Problem 1.3: Using parallel transistors is better from a device matching perspective than varying the width of a transistor. This isn't always apparent when using simplified models of the devices. Ignore channel length modulation for all parts.



NOTE: The body terminals are not shown on these devices. This style is commonly used to show gate terminals connected across devices.


a) Calculate the currents I_1 and I_{23} for the circuit on the right. Assume $V_{BIAS} = 1V$, $V_{DS} = 2V$ for all devices, $(W/L)_1 = 2.0/0.5$, and $(W/L)_2 = (W/L)_3 = 1.0/0.5$.

b) Are the 2 currents in part a) the same or different? Briefly explain why.

c) Suppose you needed to generate a third current I_{OUT} that is $2.5 \cdot I_{23}$ using any number of NMOS devices, but with the size of each NMOS restricted to $W/L = 1.0/0.5$. V_{GS} and V_{DS} are the same as in part a). Draw a schematic of how you could implement this?

Problem 1.4: Stacking transistors and increasing length are techniques used to increase the output impedance and reduce leakage current through devices. You may ignore channel length modulation.

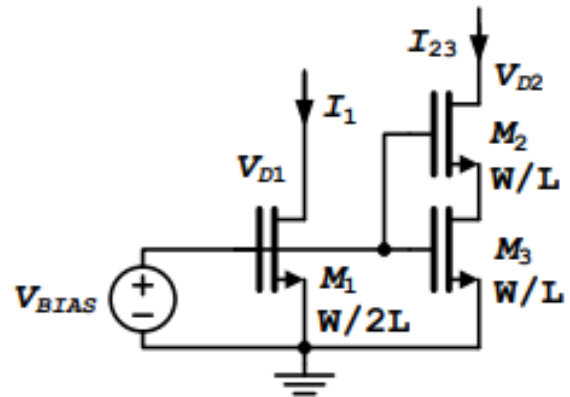
a) Calculate the currents I_1 and I_{23} for the circuit on the right. Assume $V_{BIAS} = 1V$, $V_{D1} = V_{D2} = 2V$, $(W/L)_1 = 1.0/1.0$, and $(W/L)_2 = (W/L)_3 = 1.0/0.5$. Body terminals on all devices are connected to the ground. (Hint: assume an operating region for M2 and M3, calculate the current and voltages, then check your operating region assumption)



b) Are the 2 currents in part a) the same or different?


Problem 1.5: The figure below shows the measured $\log(I_D)$ vs V_{GS} curve of an NMOS transistor.

Assume the sub-threshold current can be approximated with $I_D = I_0 \exp \frac{V_{GS} - V_{TH}}{nV_T}$ where thermal voltage $V_T = 26mV$. Estimate the value of “n” for this transistor.

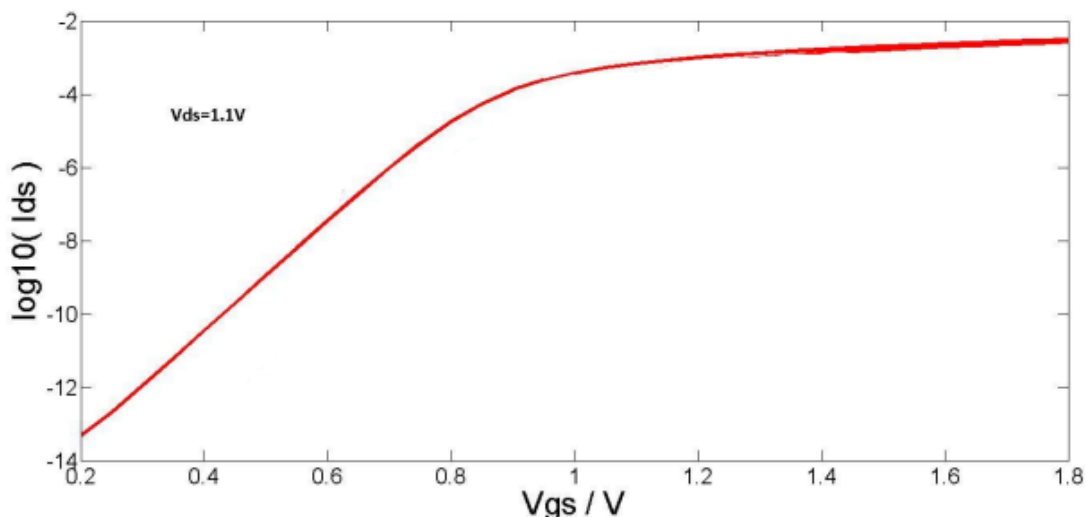

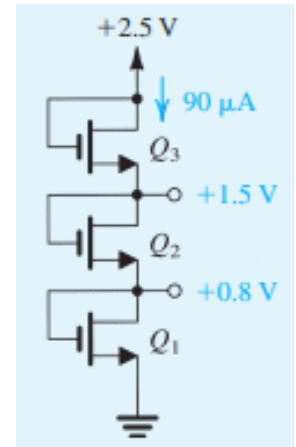
Problem 1.6: The NMOS transistors in the circuit on the right have $V_t = 0.5$ V, $\mu_n C_{ox} = 250 \mu\text{A}/\text{V}^2$, $\lambda = 0$, and $L_1 = L_2 = L_3 = 0.5 \mu\text{m}$.

Find the required values of gate width for each all transistors to obtain the voltage and current values indicated.



Problem 1.7: 1 In the circuit shown on the right, transistors Q1 and Q2 have $V_t = 0.7$ V, and the process transconductance parameter $\mu_n C_{ox} = 125 \mu\text{A}/\text{V}^2$. Find V_1 , V_2 , and V_3 for each of the following cases:

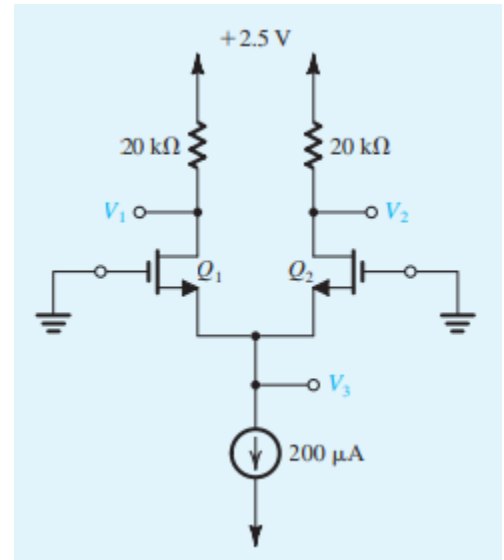- (a) $(W/L)_1 = (W/L)_2 = 20$
- (b) $(W/L)_1 = 1.5(W/L)_2 = 20$



Problem 1.8: For the circuits shown below, assume $\mu_n C_{ox} = 3\mu_p C_{ox} = 270 \mu\text{A}/\text{V}^2$, $|V_t| = 0.5$ V, $\lambda = 0$, $L = 1 \mu\text{m}$, and $W = 3 \mu\text{m}$, unless otherwise specified. Find the labeled currents and voltages.

