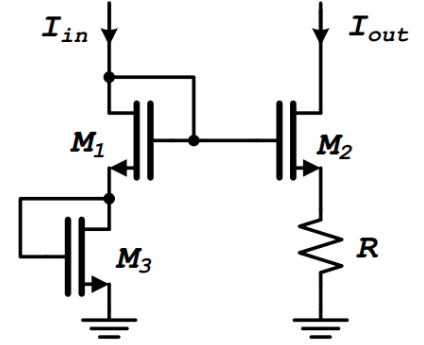


Faculty of Engineering – Cairo University
Electronics and Electrical Communications Department
EECE2020 – Electronics II
Problem Set # 2

$$\lambda = 0.1, K'_n = \mu_n C_{ox} = 0.138 \text{ mA/V}^2$$

Problem 1: Using the circuit on the right, answer the following parts keeping all answers in terms of the device parameters μ_n , C_{ox} , (W/L) , V_{th} . You may ignore channel length modulation.

- Derive a large signal expression relating I_{out} to I_{in} in terms of device parameters and bias voltages (V_{gs}).
- Now assume that the (W/L) ratio of M_3 is very large so that $\sqrt{2I_{D3}/\mu_n C_{ox} (W/L)_3} \approx 0$, also assume that nominally $V_{GS1} \approx V_{GS2}$. What is the approximate value of I_{out} in terms of R ?



Solution:

a)

Assuming all devices are in SAT region

$$I_{in} = \frac{1}{2} K_{n1} (V_{GS1} - V_{TH1})^2 = \frac{1}{2} K_{n3} (V_{GS3} - V_{TH3})^2$$

$$I_{out} = \frac{1}{2} K_{n2} (V_{GS2} - V_{TH2})^2$$

$$V_{GS2} + I_{out}R = V_{GS1} + V_{GS3}$$

$$V_{GS2} + I_{out}R = V_{TH1} + \sqrt{\frac{2I_{in}}{K_{n1}}} + V_{TH3} + \sqrt{\frac{2I_{in}}{K_{n3}}}$$

$$I_{out} = \frac{\sqrt{\frac{2I_{in}}{K_{n1}}} + \sqrt{\frac{2I_{in}}{K_{n3}}} + V_{TH1} + V_{TH3} - V_{GS2}}{R}$$


b)

$$\text{If } M_3 \text{ is large, } \sqrt{\frac{2I_{in}}{K_{n3}}} \approx 0$$

$$\text{Assuming } V_{GS1} = V_{GS2} = V_{TH1} + \sqrt{\frac{2I_{in}}{K_{n1}}}$$

$$I_{out} = \frac{V_{TH3}}{R}$$

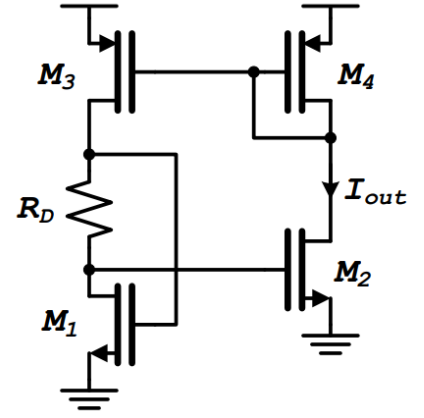Problem 2: Use the circuit shown on the right. Neglect L modulation and assume that $(W/L)_3 = (W/L)_4$. Derive a large-signal expression for the current I_{out} in terms of the $(W/L)_1$, $(W/L)_2$, R_D , and device parameters. Assume $V_{th1} = V_{th2}$.



Solution:

M3 and M4 → forms a current mirror.

$$I_{D3} = I_{D4} = I_{out}$$

$$\text{Assume } V_{TH1} = V_{TH2} = V_{TH}$$

$$I_{out} = \frac{1}{2} K_{n2} (V_{GS2} - V_{TH})^2 = \frac{1}{2} K_{n1} (V_{GS1} - V_{TH})^2$$

$$V_{GS1} = I_{out} R_D + V_{GS2}$$


$$I_{out} R_D = V_{GS1} - V_{GS2} = \sqrt{\frac{2I_{out}}{K_{n1}}} + V_{TH} - \sqrt{\frac{2I_{out}}{K_{n2}}} - V_{TH} = \sqrt{\frac{2I_{out}}{\mu_n C_{ox}}} \left[\sqrt{\frac{1}{\left(\frac{W}{L}\right)_1}} - \sqrt{\frac{1}{\left(\frac{W}{L}\right)_2}} \right]$$

$$I_{out}^2 R_D^2 = \frac{2I_{out}}{\mu_n C_{ox}} \left[\frac{1}{\left(\frac{W}{L}\right)_1} + \frac{1}{\left(\frac{W}{L}\right)_2} - 2 \sqrt{\frac{1}{\left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2}} \right]$$

$$I_{out} = \frac{2}{\mu_n C_{ox} R_D^2} \left[\frac{1}{\left(\frac{W}{L}\right)_1} + \frac{1}{\left(\frac{W}{L}\right)_2} - 2 \sqrt{\frac{1}{\left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2}} \right]$$

Razavi - Problem 5.1: In the circuit shown on the right, assume that $(W/L)_1 = 50/0.5$, $\lambda = 0$, $I_{out} = 0.5$ mA, and M_1 is saturated.

- Determine R_2/R_1 .
- Calculate the sensitivity of I_{out} to V_{DD} , defined as $\partial I_{out}/\partial V_{DD}$ and normalized to I_{out} .
- How much does I_{out} change if V_{TH} changes by 50 mV?
- If the temperature dependence of μ_n is expressed as $\mu_n \propto T^{-3/2}$ but V_{TH} is independent of temperature, how much does I_{out} vary if T changes from 300°K to 370°K?
- What is the worst-case change in I_{out} if V_{DD} changes by 10%, V_{TH} changes by 50 mV, and T changes from 300°K to 370°K?

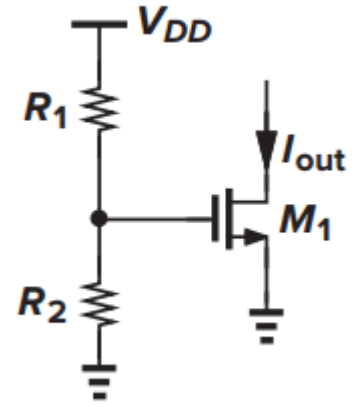

Solution:

a)

$$V_{GS1} = V_{DD} \frac{R_2}{R_1 + R_2} = V_{TH} + \sqrt{\frac{2I}{K'_n \frac{W}{L}}}$$

$$\frac{R_2}{R_1} = \frac{\sqrt{\frac{2I}{K'_n \frac{W}{L}} + V_{TH}}}{V_{DD} - \left(\sqrt{\frac{2I}{K'_n \frac{W}{L}} + V_{TH}} \right)} = 0.44$$

b)

$$I_D = \frac{1}{2} K'_n \left(\frac{W}{L} \right) \left(V_{DD} \frac{R_2}{R_1 + R_2} - V_{TH} \right)^2$$

$$\text{Sensitivity} = \frac{\partial I_D}{\partial V_{DD}} \frac{1}{I_D} = \frac{K'_n \left(\frac{W}{L} \right) \left(V_{DD} \frac{R_2}{R_1 + R_2} - V_{TH} \right) \left(\frac{R_2}{R_1 + R_2} \right)}{\frac{1}{2} K'_n \left(\frac{W}{L} \right) \left(V_{DD} \frac{R_2}{R_1 + R_2} - V_{TH} \right)^2} = \frac{2}{V_{DD} - V_{TH} \left(1 + \frac{R_1}{R_2} \right)} = 2.84$$

c)

$$I_D = \frac{1}{2} K'_n \left(\frac{W}{L} \right) \left(V_{DD} \frac{R_2}{R_1 + R_2} - V_{TH} \right)^2$$

$$\frac{\partial I_D}{\partial V_{TH}} = -K'_n \left(\frac{W}{L} \right) \left(V_{DD} \frac{R_2}{R_1 + R_2} - V_{TH} \right)$$

$$\Delta I_D \approx -K'_n \left(\frac{W}{L} \right) \left(V_{DD} \frac{R_2}{R_1 + R_2} - V_{TH} \right) \Delta V_{TH} = -233 \mu A$$

$$\Delta I_D = I_D(V_{TH} = 0.75V) - I_D(V_{TH} = 0.7) = -205 \mu A$$

d)

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \left(V_{DD} \frac{R_2}{R_1 + R_2} - V_{TH} \right)^2$$

$$\mu_n = \mu_{no} \left(\frac{T}{T_o} \right)^{-\frac{3}{2}}$$

$$\frac{\partial I_D}{\partial T} = -\frac{3}{2} \left(\frac{T}{T_o} \right)^{-\frac{3}{2}} \left(\frac{1}{T} \right) I_{Do}$$

$$\Delta I_D \approx -\frac{3}{2} \left(\frac{T}{T_o} \right)^{-\frac{3}{2}} \left(\frac{1}{T} \right) I_{Do} \Delta T = -103 \mu A$$

$$I_D = I_D(T = 370^\circ K) - I_D(T = 300^\circ K) = -135 \mu A$$


e)

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \left(V_{DD} \frac{R_2}{R_1 + R_2} - V_{TH} \right)^2$$

$$I_{D,W.C.} = \frac{1}{2} \mu_{no} \left(\frac{T_o + \Delta T}{T_o} \right)^{-\frac{3}{2}} C_{ox} \left(\frac{W}{L} \right) \left((V_{DD} - \Delta V_{DD}) \frac{R_2}{R_1 + R_2} - (V_{TH} + \Delta V_{TH}) \right)^2 = 43 \mu A$$


$$\Delta I_{W.C.} = I_{D,W.C.} - I_{Do} = -457 \mu A$$

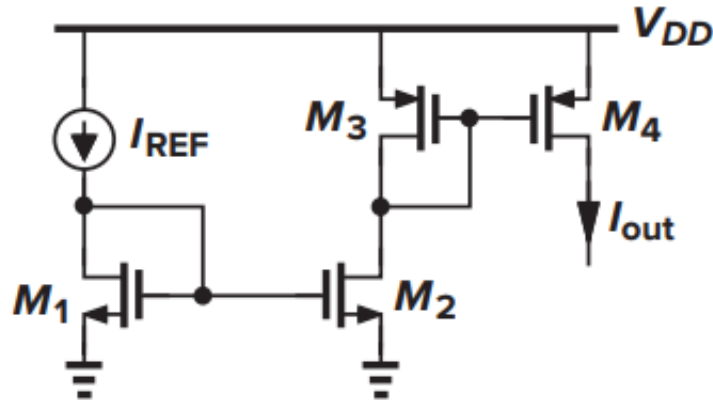Razavi - Problem 5.2: Consider the circuit shown below. Assuming I_{REF} is ideal, sketch I_{out} versus V_{DD} as V_{DD} varies from 0 to 3 V.




Solution:

- If $V_{DD} < V_{THP}$
 - M3 and M4 are off
 - $I_{out}=0$
- At $V_{THP} \leq V_{DD} < V_{SG3,4} + V_{ov2}$
 - M3 and M4 are on and SAT.
 - M3 and M4 act as a current mirror.
 - M2 is in Triode as acts as the I_{ref} for the M3/M4 current mirror.
 - I_{out} current will increase linearly with V_{DD} .
- As $V_{DD} \geq V_{SG3,4} + V_{ov2}$
 - M2 goes into SAT region
 - Two current mirrors in cascade.
 - $I_{out}=I_{ref}$
 - Considering channel length modulation, I_{out} will increase as V_{DD} increases.

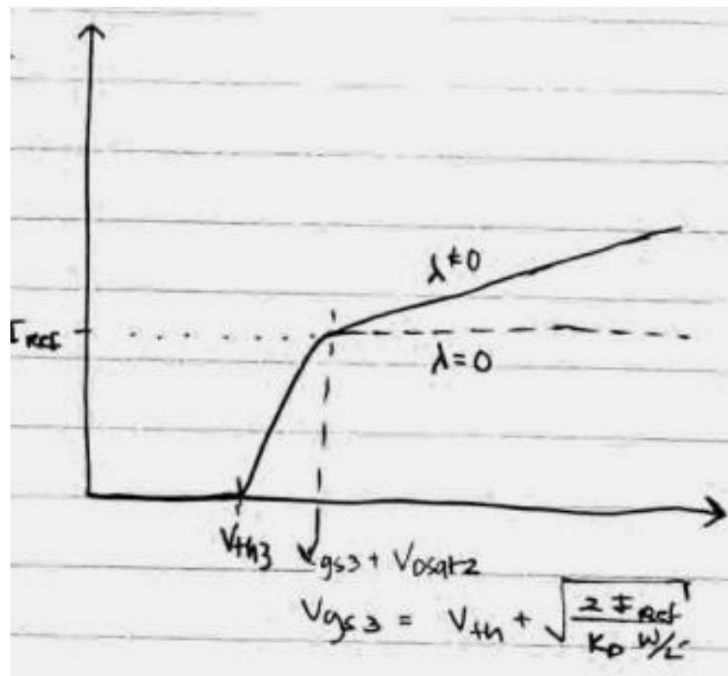

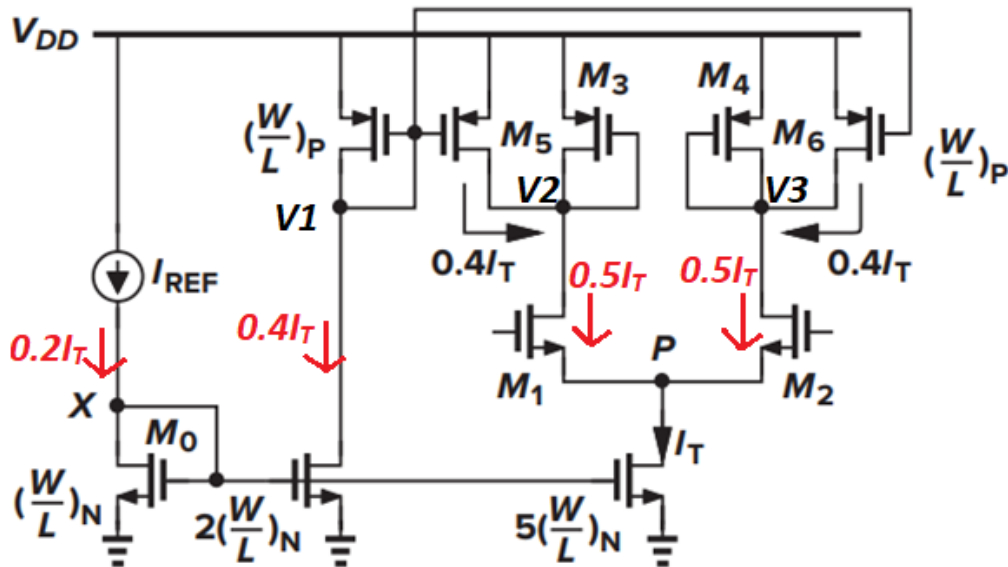Razavi - Problem 5.3: In the circuit shown below, $(W/L)_N = 10/0.5$, $(W/L)_P = 10/0.5$, and $I_{REF} = 100 \mu A$. The input CM level applied to the gates of M1 and M2 is equal to 1.3 V. Assuming $\lambda = 0$, calculate V_P and the drain voltage of the PMOS diode-connected transistors.



Solution:


$$I_D = \frac{1}{2} K_n (V_{GS} - V_{TH})^2$$

$$V_1 = V_{DD} - V_{SGP} = V_{DD} - |V_{THP}| - \frac{2 \times 2I_{REF}}{\sqrt{K'_p \left(\frac{W}{L}\right)_p}} = 3 - 0.8 - \sqrt{\frac{0.4}{0.038 \times \left(\frac{10}{0.5}\right)}} = 1.475V$$

$$V_2 = V_3 = V_{DD} - V_{SG2,3} = V_{DD} - |V_{THP}| - \frac{2 \times 0.5 I_{REF}}{\sqrt{K'_p \left(\frac{W}{L}\right)_{2,3}}} = 3 - 0.8 - \sqrt{\frac{0.1}{0.038 \times \left(\frac{10}{0.5}\right)}} = 1.837V$$

$$V_P = V_{CM} - V_{GS1} = V_{CM} - V_{THN} - \sqrt{\frac{2 \times 2.5 I_{REF}}{K'_p \left(\frac{W}{L}\right)_1}} = 1.3 - 0.7 - \sqrt{\frac{0.5}{0.139 \times \left(\frac{10}{0.5}\right)}} = 0.176V$$

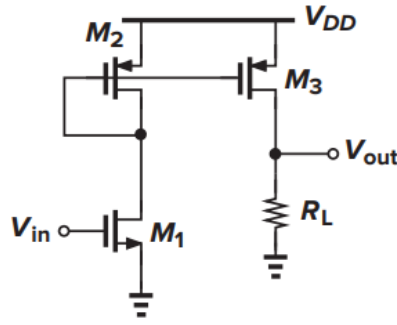Razavi - Problem 5.4: In the circuit shown below, sketch V_{out} versus V_{DD} as V_{DD} varies from 0 to 3V.



Solution:

- If $V_{DD} < V_{THP}$
 - M2 and M3 are off
 - $I_3=0$
 - $V_{out}=0$
- As $V_{DD} \geq V_{THP}$ but less than $(V_{SG2} + V_{ov1})$
 - M1 is in deep triode region, linearly approaching saturation.
 - M2 and M3 are on and are in SAT region and acting as current mirror.
 - V_{out} increasing linearly with V_{DD} .

$$V_{out} = I_{D3} \times R_L$$

$$I_{D3} = I_{D2} = I_{D1}$$

$$I_{D1} = K_{n1}(V_{GS1} - V_{THN})V_{DS1} = K_{n1}(V_{in} - V_{THN})(V_{DD} - V_{SG2})$$

$$V_{out} = K_{n1}(V_{in} - V_{THN})(V_{DD} - V_{SG2})R_L$$

$$\frac{\partial V_{out}}{\partial V_{DD}} = K_{n1}(V_{in} - V_{THN})R_L = \frac{R_L}{R_{on}}$$

- When $V_{DD} \geq V_{SG2} + V_{ov1}$
 - All transistors are on and in the SAT region.
 - As V_{DD} increases, V_{DS1} increases and hence I_{D1} increases.
 - V_{out} increases linearly with V_{DD} with a slope of λ .


$$V_{out} = I_{D3} \times R_L$$

$$I_{D3} = I_{D2} = I_{D1}$$

$$I_{D1} = \frac{1}{2}K_{n1}(V_{GS1} - V_{THN})^2(1 + \lambda V_{DS1}) = \frac{1}{2}K_{n1}(V_{in} - V_{THN})^2(1 + \lambda(V_{DD} - V_{SG2}))$$


$$V_{out} = \frac{1}{2}K_{n1}(V_{in} - V_{THN})^2(1 + \lambda(V_{DD} - V_{SG2}))R_L$$
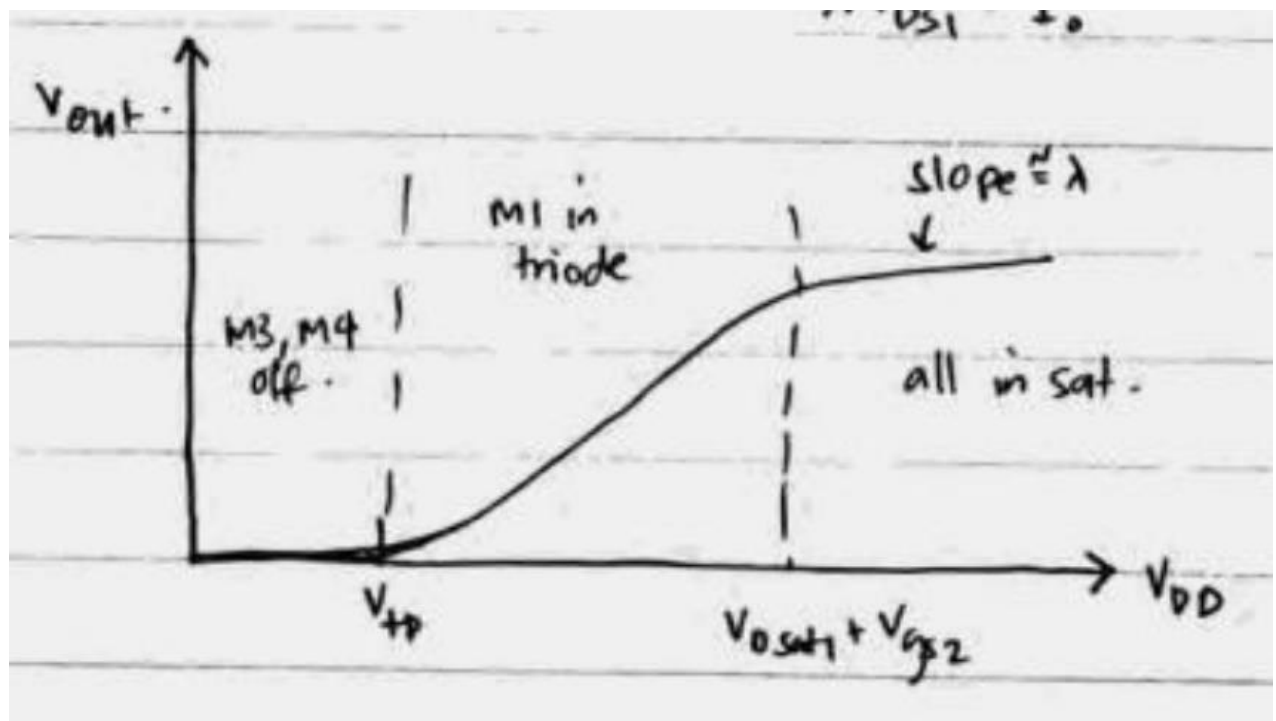
$$\frac{\partial V_{out}}{\partial V_{DD}} = \frac{1}{2}K_{n1}(V_{in} - V_{THN})^2\lambda R_L$$



Razavi - Problem 5.5: Consider the circuit shown below, assume $(W/L)_{1-3} = 40/0.5$, and $I_{REF} = 0.3 \text{ mA}$.

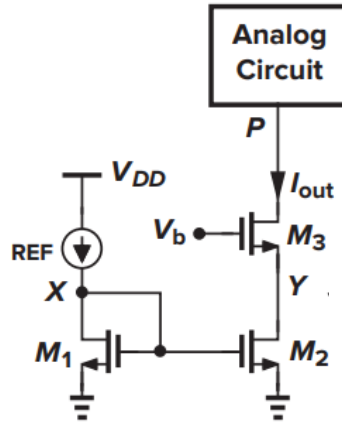- Determine V_b such that $V_X = V_Y$.
- If V_b deviates from the value calculated in part (a) by 100 mV, what is the mismatch between I_{out} and I_{REF} ?
- If the circuit fed by the cascode current source changes V_P by 1V, how much does V_Y change?



Solution:

a)

$$V_{DS2} = V_{DS1} = V_{GS1}$$

$$V_b = V_{GS3} + V_{DS2} = 2V_{GS1}$$

$$I_{REF} = \frac{1}{2} K_{n1} (V_{GS1} - V_{TH})^2 (1 + \lambda V_{DS1})$$

$$0.3 = \frac{1}{2} \times 0.138 \times \frac{40}{0.5} \times (V_{GS1} - 0.7)^2 (1 + 0.1 V_{GS1})$$

$$\frac{5}{92} = (V_{GS1} - 0.7)^2 (1 + 0.1 V_{GS1})$$

$$V_{GS1} = 0.9231V$$

$$V_b = 2V_{GS1} = 1.8462V$$

b)

$$I_{out} = I_{REF} \times \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}} = I_{REF} \times \frac{1 + \lambda (V_{GS1} + \Delta V_y)}{1 + \lambda V_{GS1}} = I_{REF} + I_{REF} \times \frac{\lambda \Delta V_y}{1 + \lambda V_{GS1}} = I_{REF} + \Delta I_{REF}$$

If V_b increases by $\Delta V_b = 100 \text{ mV} \rightarrow V_y$ will increase by $\Delta V_y < \Delta V_b \rightarrow$ We need to get ΔV_y ?

$$I_{D2} = \frac{1}{2} K_{n2} (V_{GS2} - V_{TH})^2 (1 + \lambda V_{DS2}) = \frac{1}{2} K_{n2} (V_{GS1} - V_{TH})^2 (1 + \lambda (V_{GS1} + \Delta V_y))$$

$$I_{D3} = \frac{1}{2} K_{n3} (V_{GS3} - V_{TH})^2 (1 + \lambda V_{DS3}) = \frac{1}{2} K_{n3} (V_{GS1} + \Delta V_b - \Delta V_y - V_{TH})^2 (1 + \lambda (V_{GS1} - \Delta V_y))$$

$$I_{D2} = I_{D3}$$

$$(V_{GS1} - V_{TH})^2 (1 + \lambda(V_{GS1} + \Delta V_y)) = (V_{GS1} + \Delta V_b - \Delta V_y - V_{TH})^2 (1 + \lambda(V_{GS1} - \Delta V_y))$$

$$0.05(1.09231 + 0.1\Delta V_y) = (0.3231 - \Delta V_y)^2 (1.09231 - 0.1\Delta V_y)$$


$$\Delta V_y = 97.49mV$$

$$\text{Mismatch} = \Delta I_{REF} = I_{REF} \times \frac{\lambda \Delta V_y}{1 + \lambda V_{GS1}} = 0.3mA \times \frac{0.1 \times 0.09749}{1 + 0.1 \times 0.9231} = 2.678\mu A$$

c)

If V_P increases by 1V $\rightarrow V_y$ will increase by ΔV_y

We need to get ΔV_y ?

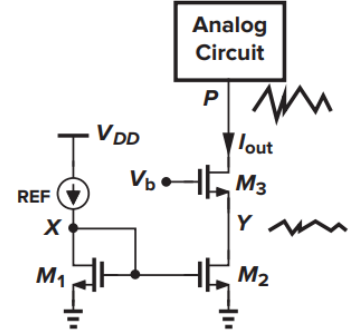

$$I_{out} = I_{D2} = I_{REF} \times \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}} = I_{REF} \times \frac{1 + \lambda(V_{GS1} + \Delta V_y)}{1 + \lambda V_{GS1}} \quad (I)$$

$$I_{out} = I_{D3} = \frac{1}{2} K_{n3} (V_{GS3} - V_{TH})^2 (1 + \lambda V_{DS3}) = \frac{1}{2} K_{n3} (V_{GS1} - \Delta V_y - V_{TH})^2 (1 + \lambda(V_{GS1} + 1 - \Delta V_y)) \quad (II)$$

Equating (I) and (II)

$$I_{REF} \times \frac{1 + \lambda(V_{GS1} + \Delta V_y)}{1 + \lambda V_{GS1}} = \frac{1}{2} K_{n3} (V_{GS1} - \Delta V_y - V_{TH})^2 (1 + \lambda(V_{GS1} + 1 - \Delta V_y))$$


$$0.3m \times \frac{1 + 0.1(0.9231 + \Delta V_y)}{1 + 0.1 \times 0.9231} = \frac{1}{2} \times 0.138m \times \frac{40}{0.5} \times (0.9231 - \Delta V_y - 0.7)^2 (1 + 0.1(0.9231 + 1 - \Delta V_y))$$

$$(1.09231 + 0.1\Delta V_y) = 20.1 \times (0.2231 - \Delta V_y)^2 (1.19231 - 0.1\Delta V_y)$$

$$\Delta V_y = 9.43mV$$

Razavi - Problem 5.6: The circuit shown below is designed with $(W/L)_{1,2} = 20/0.5$, $(W/L)_{3,4} = 60/0.5$, and $I_{REF} = 100 \mu A$.

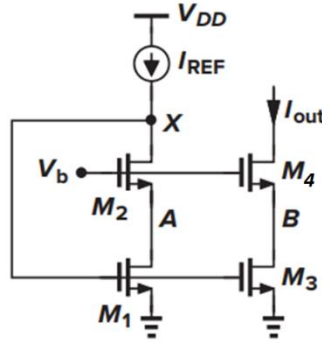- Determine V_X and the acceptable range of V_b .
- Estimate the deviation of I_{out} from $300 \mu A$ if the drain voltage of M_4 is higher than V_X by $1 V$.



Solution:

a)

$$V_X = V_{GS1}$$

$$I_{REF} = I_{D1} = \frac{1}{2} K_{n1} (V_{GS1} - V_{TH})^2 (1 + \lambda V_{DS1})$$

$$0.1 = \frac{1}{2} \times 0.138 \times \frac{20}{0.5} \times (V_{GS1} - 0.7)^2 (1 + 0.1(V_{GS1} - V_{TH}))$$

$$\frac{5}{138} = (V_{GS1} - 0.7)^2 (0.93 + 0.1V_{GS1})$$

$$V_X = V_{GS1} = 0.889V$$

Acceptable range of V_b :

$$V_b \geq V_{GS2} + V_{ov1}$$

$$I_{REF} = I_{D2} = \frac{1}{2} K_{n2} (V_{GS2} - V_{TH})^2 (1 + \lambda V_{DS2})$$

$$0.1 = \frac{1}{2} \times 0.138 \times \frac{20}{0.5} \times (V_{GS2} - 0.7)^2 (1 + 0.1 \times 0.7)$$

$$V_{GS2} = 0.884V$$

$$V_b \geq 0.884 + (0.889 - 0.7)$$

$$V_b \geq 1.073V$$


If V_b increases above $V_{GS1,2} + V_{TH}$:

- M2 and M4 go into triode.
- $V_A = V_X$
- $V_B = V_{D4}$ (Drain of M4)
- As long as V_{D4} doesn't drop below V_{ov3} , I_{out} will reasonably track I_{REF} .

b)

Like previous problem, if $V_{\text{drain},M4}$ increases by 1V $\rightarrow V_B$ will increase by ΔV_B

We need to get ΔV_B ?

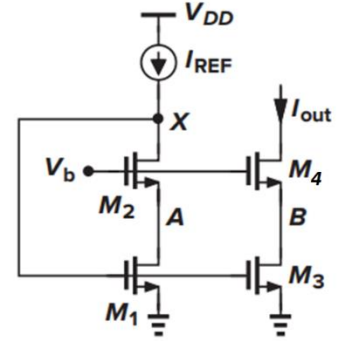

$$I_{out} = I_{D3} = 3I_{REF} \times \frac{1 + \lambda V_{DS3}}{1 + \lambda V_{DS1}} = 3I_{REF} \times \frac{1 + \lambda(V_{ov1} + \Delta V_B)}{1 + \lambda V_{ov1}} \quad (I)$$

$$I_{out} = I_{D4} = \frac{1}{2} K_{n4} (V_{GS4} - V_{TH})^2 (1 + \lambda V_{DS4}) = \frac{1}{2} K_{n4} (V_{GS2} - \Delta V_B - V_{TH})^2 (1 + \lambda(V_{TH} + 1 - \Delta V_B)) \quad (II)$$

Equating (I) and (II)

$$3I_{REF} \times \frac{1 + \lambda(V_{ov1} + \Delta V_B)}{1 + \lambda V_{ov1}} = \frac{1}{2} K_{n4} (V_{GS2} - \Delta V_B - V_{TH})^2 (1 + \lambda(V_{TH} + 1 - \Delta V_B))$$

$$V_{ov1} = V_{GS1} - V_{TH} = 0.889 - 0.7 = 0.189V$$

$$0.3m \times \frac{1 + 0.1(0.189 + \Delta V_B)}{1 + 0.1 \times 0.189} = \frac{1}{2} \times 0.138m \times \frac{60}{0.5} \times (0.884 - \Delta V_B - 0.7)^2 (1 + 0.1(0.7 + 1 - \Delta V_B))$$

$$(1.0189 + 0.1\Delta V_B) = 27.6 \times (0.184 - \Delta V_B)^2 (1.17 - 0.1\Delta V_B)$$

$$\Delta V_B = 6.27mV$$

$$I_{out} = 3I_{REF} \times \frac{1 + \lambda(V_{ov1} + \Delta V_B)}{1 + \lambda V_{ov1}} = 300.2\mu A$$