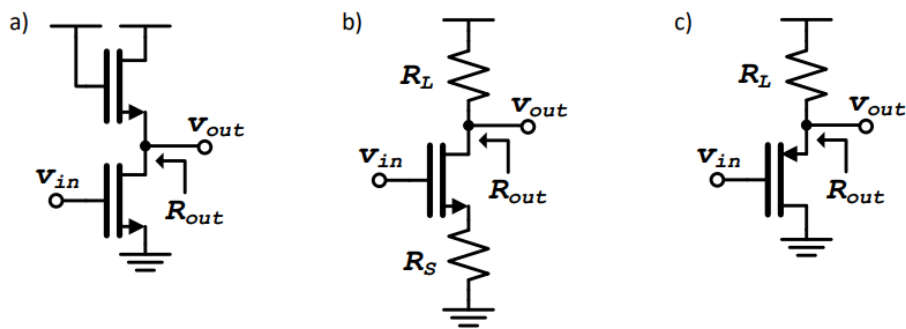


Faculty of Engineering – Cairo University
Electronics and Electrical Communications Department
EECE2020 – Electronics II
Problem Set # 3

Unless otherwise mentioned, assume the following: $k_n' = \mu_n C_{ox} = 200 \mu A/V^2$, $k_p' = \mu_p C_{ox} = 100 \mu A/V^2$, and $V_{TH} = 0.4 V$ for NMOS devices and $-0.4 V$ for PMOS devices.


Problem 1: Practice solving these circuits “by inspection.” For each of the following circuits, write the expression for gain ($A_v = v_{out}/v_{in}$) and R_{out} . It is ok to keep parallel combinations of resistors in the form $(R_1 || R_2)$. For simplicity, assume that g_m and r_o are identical for all devices, and ignore r_o when appropriate. Assume R_L and $R_S \ll r_o$.



Problem 2: The “intrinsic gain” of a MOSFET operating in saturation is defined as $g_m r_o$. Derive an expression for the intrinsic gain and plot the result as a function of I_D for a constant W and L . Assume V_{DS} is constant.


Problem 3: Show that the small-signal equivalent of a transistor whose drain and gate are shorted is a resistance and find its value.

Problem 4: In the common-source amplifier shown, $W/L=30$ and $\lambda=0$. Calculate the gate voltage that yields a drain current of $0.5mA$. verify that the transistor is in saturation. What is the gain of the stage?

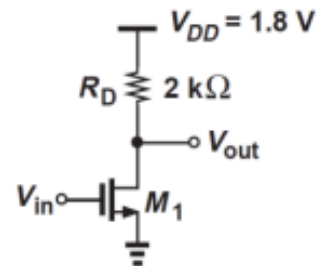


Problem 5: Consider the circuit depicted in the figure shown, where M_1 and M_2 operate in saturation and exhibit channel length modulation coefficients λ_n and λ_p , respectively.


- Construct the small-signal equivalent circuit and explain why M_1 and M_2 appear in “parallel.”
- Determine the small-signal voltage gain of the circuit.

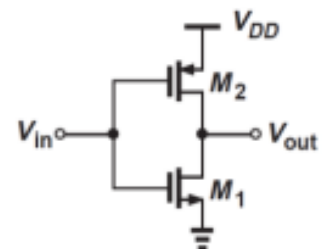

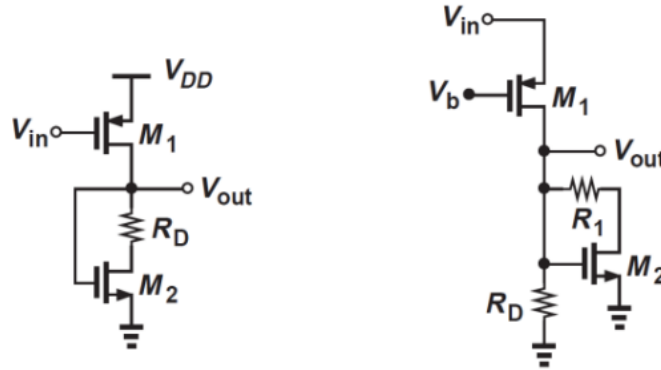
Problem 6: Construct the small-signal model of both circuits shown below. Calculate the voltage gain. Assume all transistors are in saturation region. Consider channel length modulation.




Problem 7: Design for a voltage gain of 5, get $\left(\frac{W}{L}\right)_1$ if $\left(\frac{W}{L}\right)_2 = 2/0.18$. Neglect channel length modulation. What is the maximum allowable current for M1 to remain in saturation.

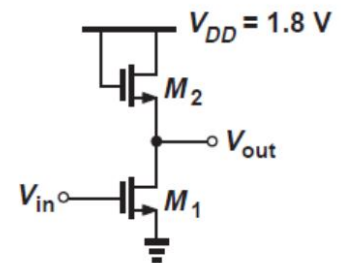

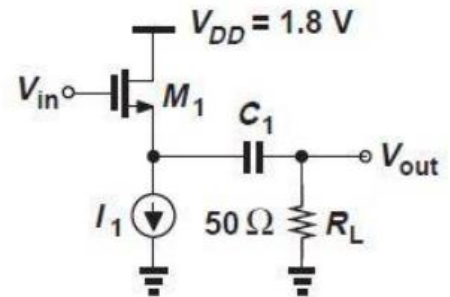
Problem 8: For a power budget of 3mW, $\lambda = 0$ and $C1$ is very large, get the required W/L for a source of follower of gain 0.8.



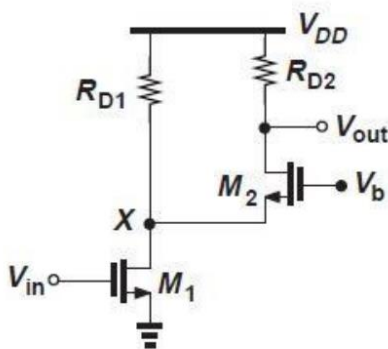
Problem 9: For each of the amplifiers shown below, draw the small signal model and calculate the voltage gain and output impedance in terms of the small signal parameters. Ignore r_o when appropriate ($R \ll r_o$).



(a)

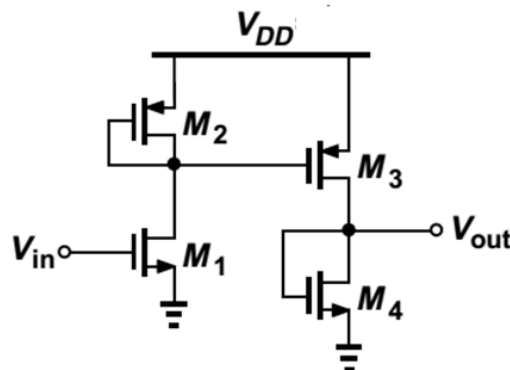

(b)

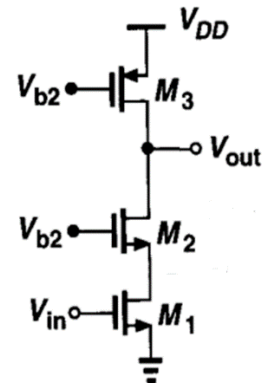

(c)