


SHEET 5

SINUSOIDAL STEADY-STATE ANALYSIS

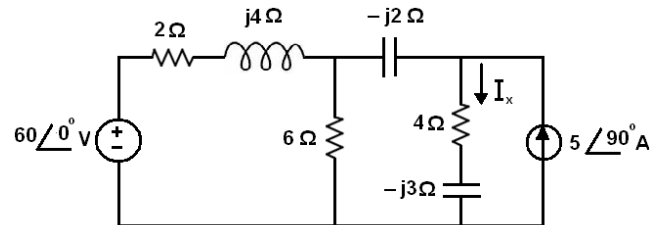Problem [1]:

Use source transformation to find I_x in the circuit shown to the right.


Answers: $I_x = 5.238 \angle 17.35^\circ \text{ A}$



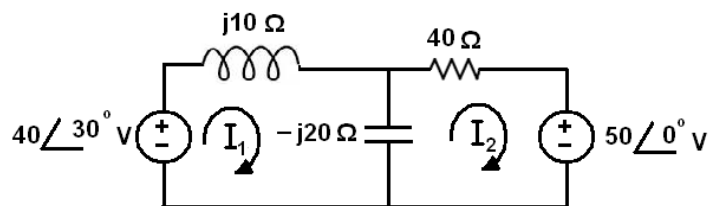Problem [2]:

Using loop analysis, find I_1 and I_2 in the circuit shown.

Answers: $I_1 = 4.698 \angle 95.24^\circ \text{ A}$,
 $I_2 = 0.9928 \angle 37.71^\circ \text{ A}$.




Problem [3]:

Repeat solving problem 2 using source transformation.

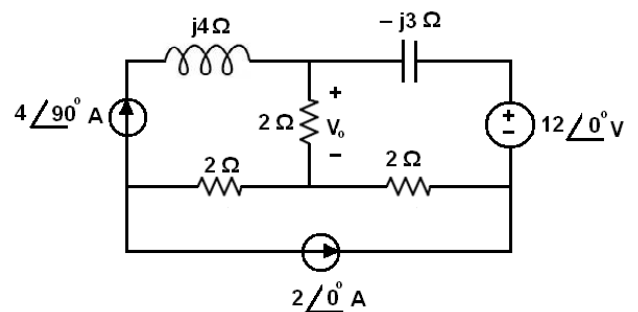Problem [4]:

Compute V_o in the circuit shown using loop analysis.

Answers: $V_o = 11.648 \angle 52.82^\circ \text{ V}$




Problem [5]:

Repeat solving problem 4 using superposition method.

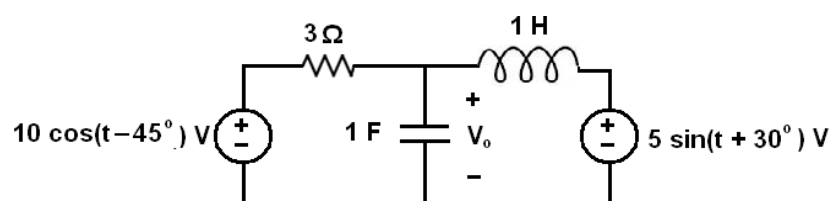Problem [6]:

Use node analysis to find $v_o(t)$ in the circuit shown below.


Answers: $v_o(t) = 15.73 \cos(t + 247.9^\circ) \text{ V}$





Problem [7]:

Use node analysis to find $v_o(t)$ in the circuit shown below.

Answers: $v_o(t) = 6.154 \cos(10^3 t + 70.26^\circ) \text{ V}$

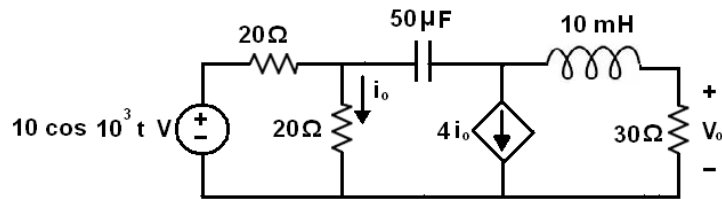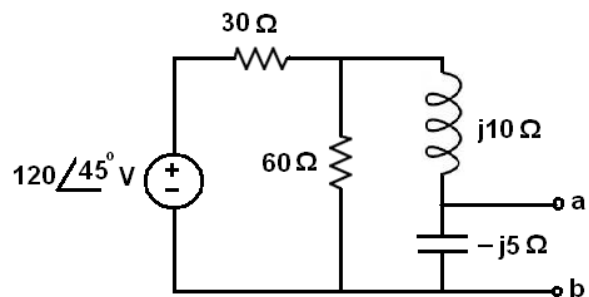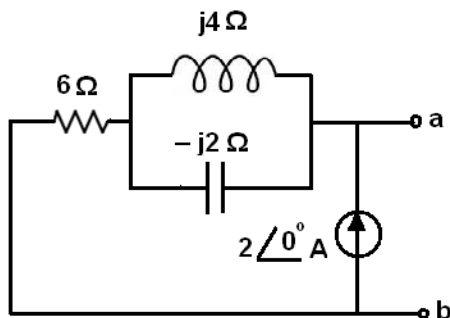**Problem [8]:**

For each of the circuits in the figure shown below, obtain the Thevenin and Norton equivalent circuits at Terminals a - b .



Answers:

$$\begin{aligned} Z_{th} &= Z_N = 7.211 \angle -33.69^\circ \Omega \\ V_{th} &= 14.422 \angle -33.69^\circ \text{ V} \\ I_N &= 2 \angle 0^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} Z_{th} &= Z_N = 5.423 \angle -77.47^\circ \Omega \\ V_{th} &= 19.4 \angle -59^\circ \text{ V} \\ I_N &= 3.578 \angle 18.43^\circ \text{ A} \end{aligned}$$

Homework:

Find $i_o(t)$ and $v_o(t)$ for the circuit shown below.

