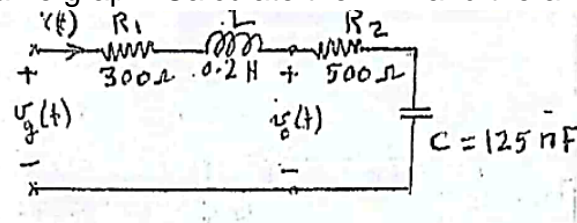


SHEET 7

AC TIME DOMAIN ANALYSIS

Problem [1]:


In the circuit shown below, $v_g(t) = 100 \cos(8000t) \text{ V}$. Find $i(t)$ and $v_o(t)$. Sketch $v_g(t)$, $i(t)$, and $v_o(t)$ on the same graph. Calculate the P.F. and the average power.



Answers: $i(t) = 0.1 \cos(8000t - 36.87^\circ) \text{ A}$, $v_o(t) = 50 \cos(8000t - 100.30^\circ) \text{ V}$,
P.F. = 0.8 Lagging, $P_{avg} = 4 \text{ W}$.

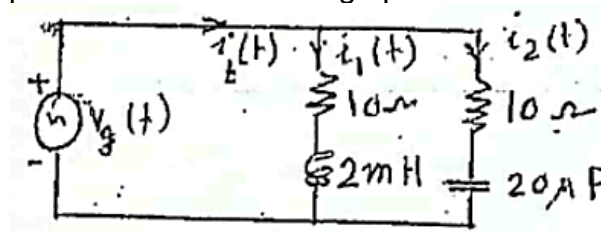Problem [2]:


In the circuit shown below, if $v_g(t) = 100 \sin(5000t) \text{ V}$. Find $i_1(t)$, $i_2(t)$ and $i_t(t)$ and sketch their waveforms on the same graph. Calculate the average power.



Answers: $i_1(t) = 5\sqrt{2} \sin(5000t - 45^\circ) \text{ A}$, $i_2(t) = 5\sqrt{2} \sin(5000t + 45^\circ) \text{ A}$
 $i_t(t) = 10 \sin(5000t) \text{ A}$, $P_{avg} = 500 \text{ W}$

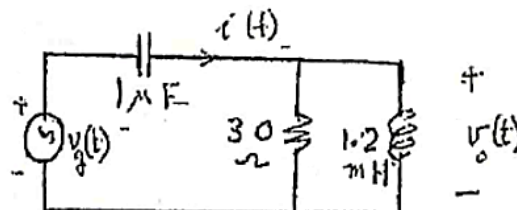Problem [3]:


In the circuit shown below, if $i_t(t) = 0.5\sqrt{10} \cos(50000t + 18.43^\circ) \text{ A}$. Find $v_o(t)$, $v_g(t)$ and calculate the P.F. and P_{avg} .



Answers: $v_o(t) = 30\sqrt{2} \cos(50000t + 45^\circ) \text{ V}$, $v_g(t) = 40 \cos(50000t) \text{ V}$
P.F. = 0.9487 Leading, $P_{avg} = 30 \text{ W}$

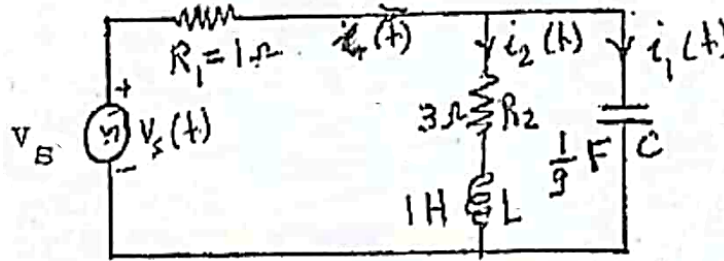Problem [4]:


In the circuit shown below, $i_1(t) = 2\sqrt{2} \cos(3t + 81.9^\circ) \text{ A}$. Find $i_2(t)$, $i(t)$, and $v_s(t)$. Calculate the average power consumption and sketch the waveforms on the same graph.



Answers: $i_2(t) = 2 \cos(3t - 53.1^\circ) \text{ A}$, $i(t) = 2 \cos(3t + 36.87^\circ) \text{ A}$
 $v_s(t) = 10 \cos(3t) \text{ V}$, $P_{avg} = 8 \text{ W}$

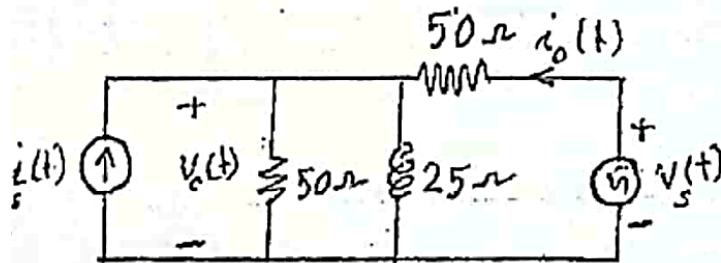Problem [5]:


In the circuit shown below, if $i_s(t) = 2\sqrt{2} \sin(\omega t + 45^\circ) \text{ A}$ and $v_s(t) = 100 \sin(\omega t)$, find $v_o(t)$ and $i_o(t)$. Calculate the average power consumption in R1 and R2.



Answers: $v_o(t) = 25\sqrt{10} \sin(\omega t + 71.565^\circ) \text{ V}$, $i_o(t) = 1.5\sqrt{2} \sin(\omega t - 45^\circ) \text{ A}$
 $P_{avg}(\text{in } R1) = 62.5 \text{ W}$, $P_{avg}(\text{in } R2) = 112.5 \text{ W}$

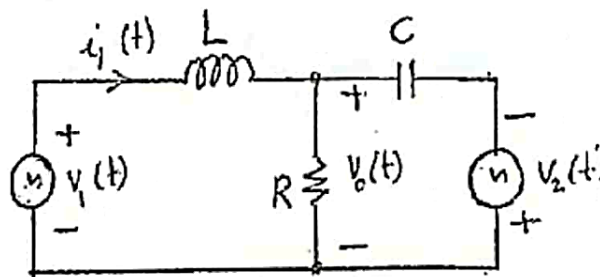Problem [6]:

In the circuit shown below, $v_1(t) = 20 \cos(\omega t - 31.87^\circ) \text{ V}$, $v_2(t) = 50 \cos(\omega t + 73.74^\circ) \text{ V}$, $\omega = 2000 \text{ rad/s}$, $R = 10 \Omega$, $L = 1 \text{ mH}$ and $C = 100 \mu\text{F}$. Use source transformations to find $v_o(t)$ and $i_1(t)$. Calculate the average power consumption in R.



Answers: $v_o(t) = 36 \cos(\omega t) \text{ V}$, $i_1(t) = 11.66 \sin(\omega t - 120.96^\circ) \text{ A}$
 $P_{avg} = 64.8 \text{ W}$

Homework:

In the circuit shown below, $i_g(t) = 3 \cos(200t) \text{ A}$, $L = 2 \text{ mH}$ and $C = 12.5 \text{ mF}$. Find $v_o(t)$ and $i_1(t)$. Calculate the average power supplied by $i_g(t)$ and that dissipated in the circuit. Check the power balance.

